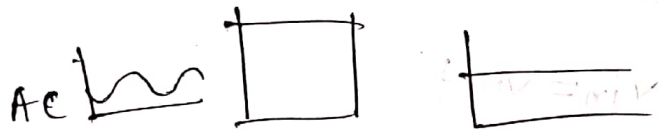


Rectifiers

# short of circuit that converts AC signal to DC signal.




# we can supply the

# Two Types :

1. Halfwave rectifier
2. Fullwave rectifier.

# H.W rectifier. (review of previous)

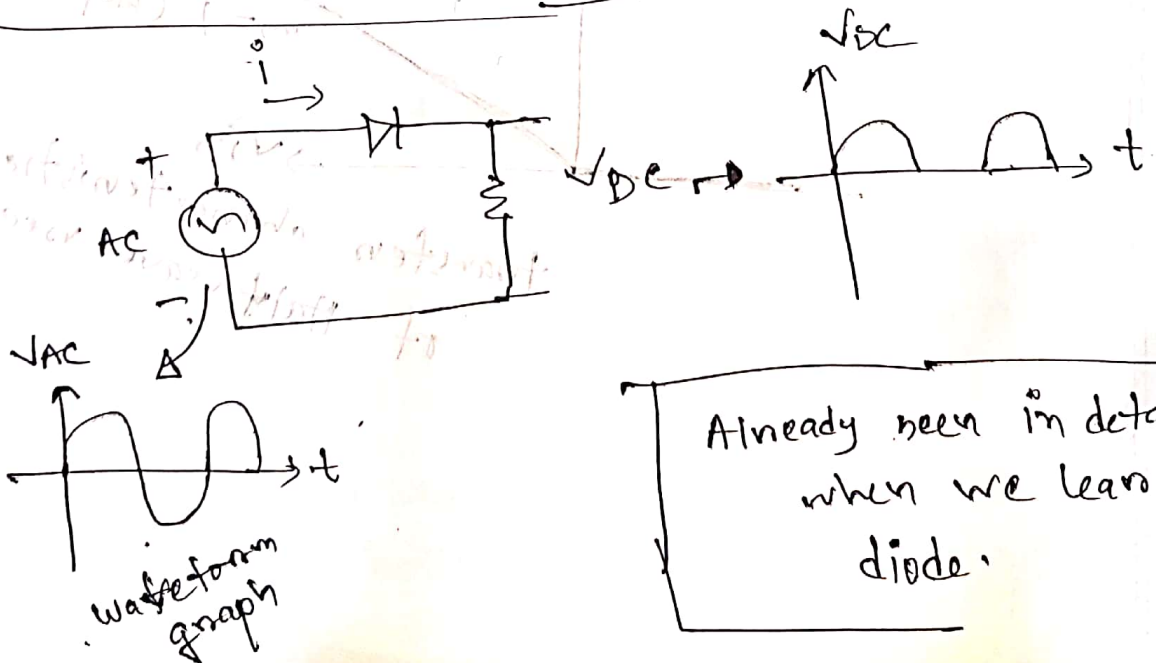


Already seen in details  
when we learned  
diode.

Topic Name : \_\_\_\_\_

Day : \_\_\_\_\_

Time : \_\_\_\_\_




Date : / /

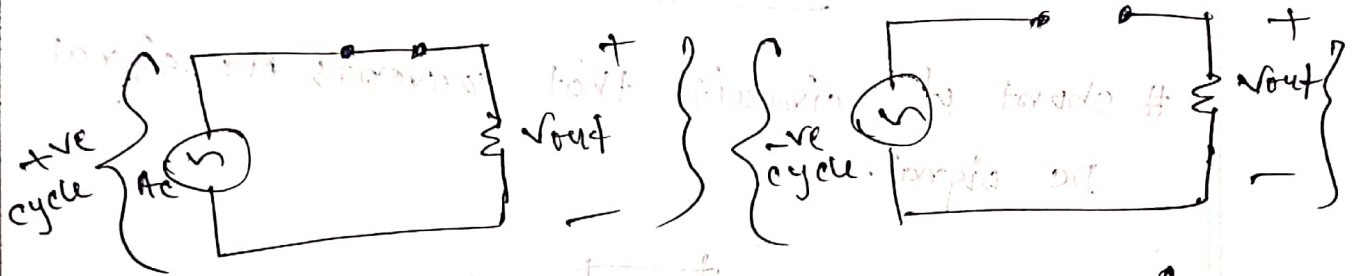

$$V_{in} = V_{out}$$

$$\therefore V_{out} = V_{in}$$

$$V_{out} = 0$$

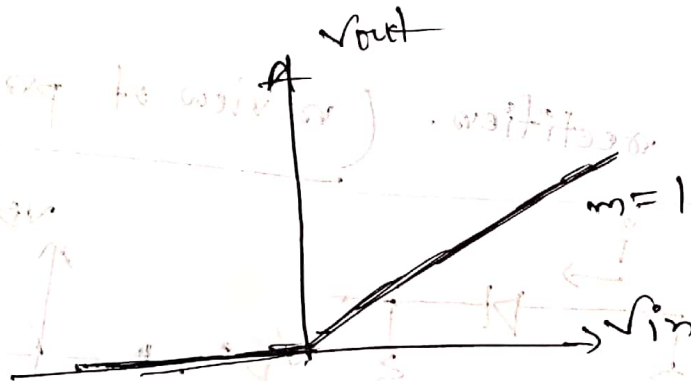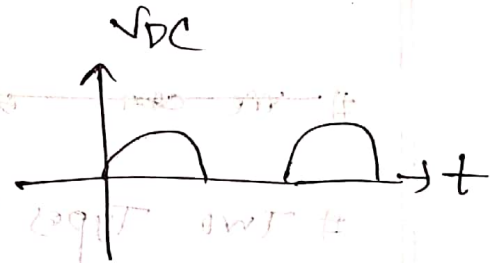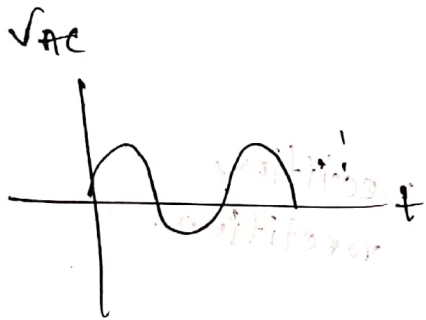

transfer characteristics of Half wave rectifier.

Topic Name : \_\_\_\_\_


Day : \_\_\_\_\_

Time : \_\_\_\_\_ Date : / /


### 3 types of graph

1. IV graph / IV-characteristics  
( $I_D$  vs.  $V_D$ )


↳ Device

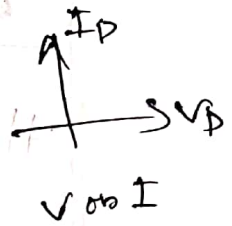

2. Waveform Graph ( $V, I$  vs.  $t$ )

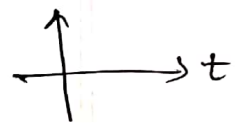


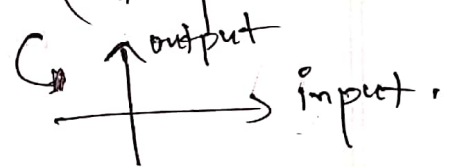3. Transfer characteristics (Input vs. output)




↓  
[circuits with 2 ports]

### # Drawback of H.W rectifier:

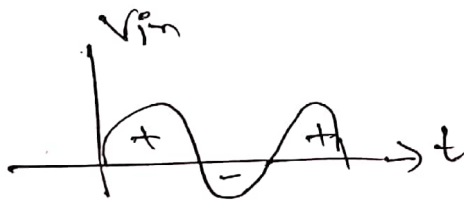

⇒

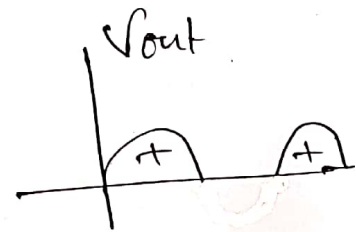

loss of negative cycle voltage.

④ To solve this we use Full-wave rectifier, which use both positive and negative cycle.

Topic Name : \_\_\_\_\_

Day : \_\_\_\_\_

Time : \_\_\_\_\_ Date : / /

Q. Question is

# Is there any power loss in H.V.D. rectifier?

Ans: No power loss.

Because on negative cycle current  $i = 0$  as well so  $p = v i = 0$ , so No loss



no power loss  
in H.V.D. rectifier

no power loss in H.V.D. rectifier



Topic Name : \_\_\_\_\_

Day : \_\_\_\_\_

Time : \_\_\_\_\_


Date : / /

## Full wave Rectifier (F.W " )



# want to utilize both positive and negative cycle of input.

[we don't want our output has 2 polarities cause DC has only 1 polarity]


Let's assume we have some AC source:

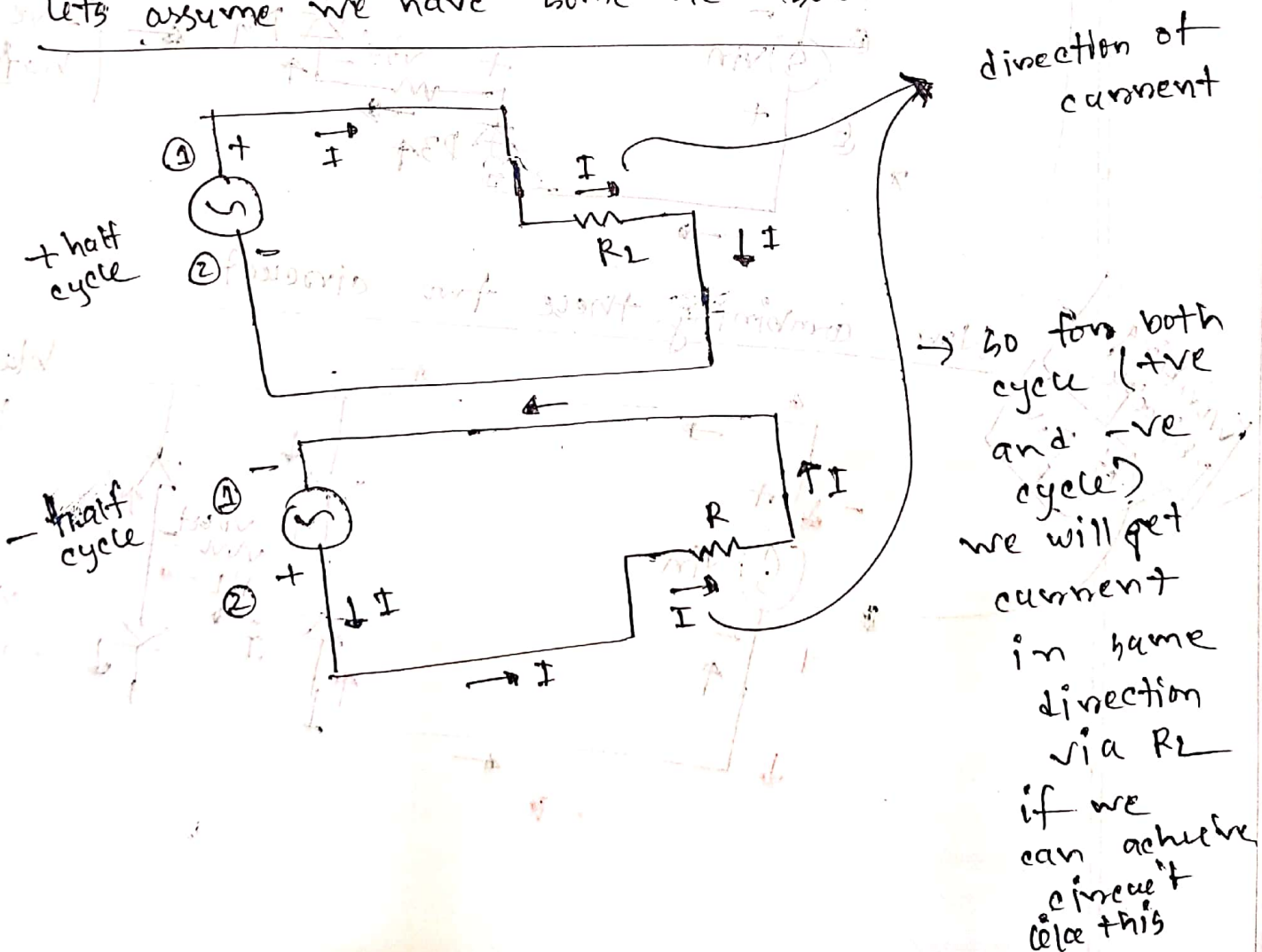

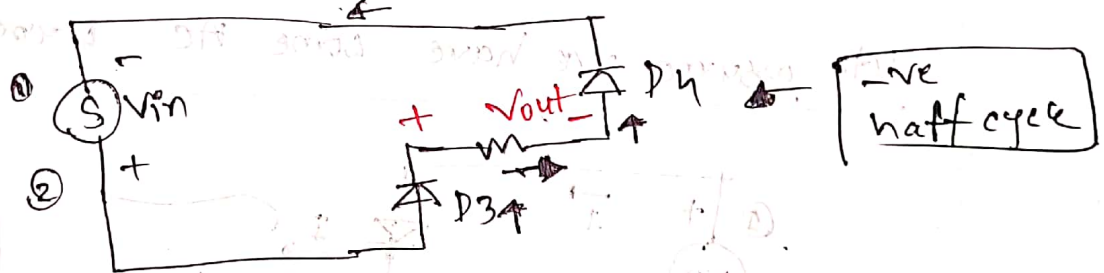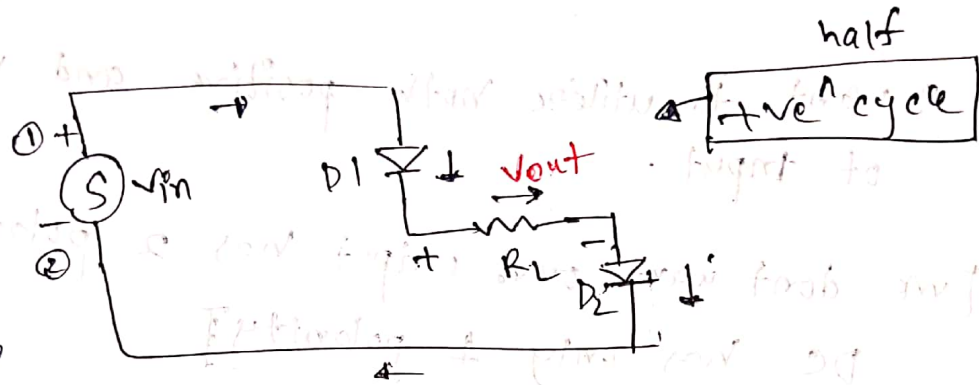\* Q. How can we achieve these two circuit?



Now combining these two circuit:

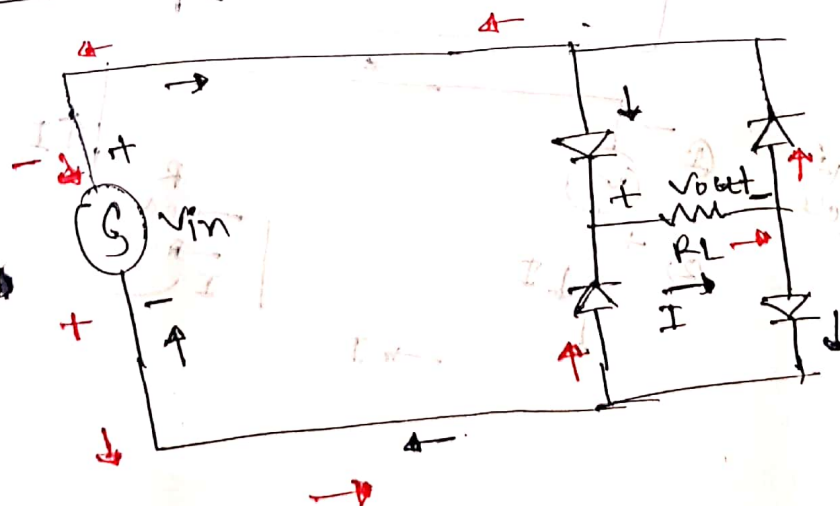

black → positive cycle

red → negative cycle

Topic Name : \_\_\_\_\_

Day : \_\_\_\_\_

Time : \_\_\_\_\_


Date : / /

~~There~~

lets try to find output : of this f.w rectifier

circuit:

wave form of  $V_{in}$

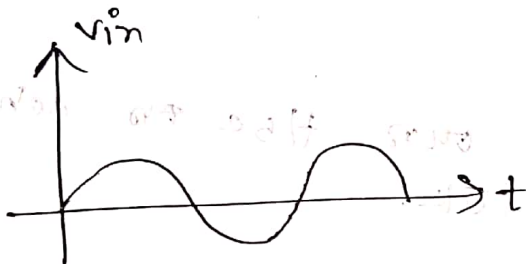

Now we can use both cycle in full wave rectifier.

It utilize full wave that is why its called F.W rectifier

Topic Name : \_\_\_\_\_

Day : \_\_\_\_\_

Time : \_\_\_\_\_


Date : / /

So



→ so this is actually a bridge circuit.

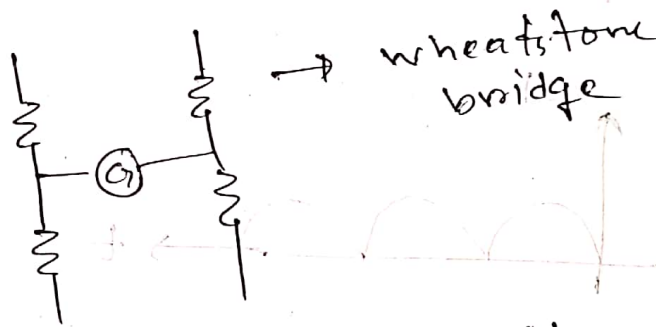[we have learned in our HSC school.  
resistor bridge. like:



so we can actually make bridges with  
- different type of element.

so this full-wave rectifier also called  
bridge rectifier.



Topic Name : \_\_\_\_\_


Day : \_\_\_\_\_

Time : \_\_\_\_\_

Date : / /


## # Transfer characteristic of full wave rectifier :

F.W.  
rectifier

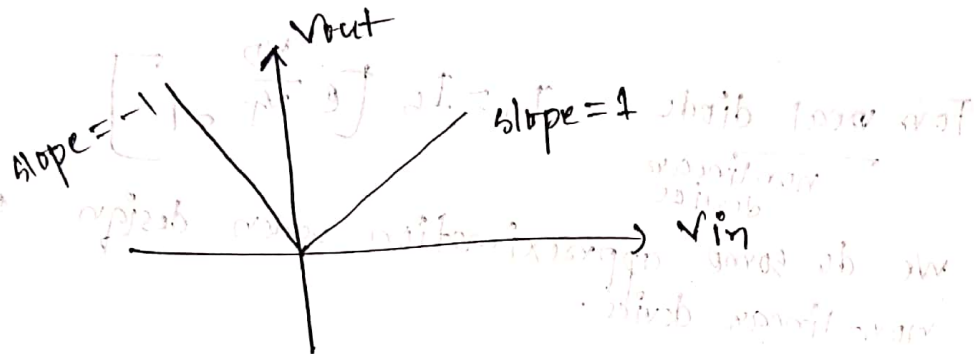

$$\left[ \begin{array}{ll} \text{when +ve cycle,} & V_{out} = V_{in} \\ \text{" -ve " ,} & V_{out} = -V_{in} \end{array} \right]$$
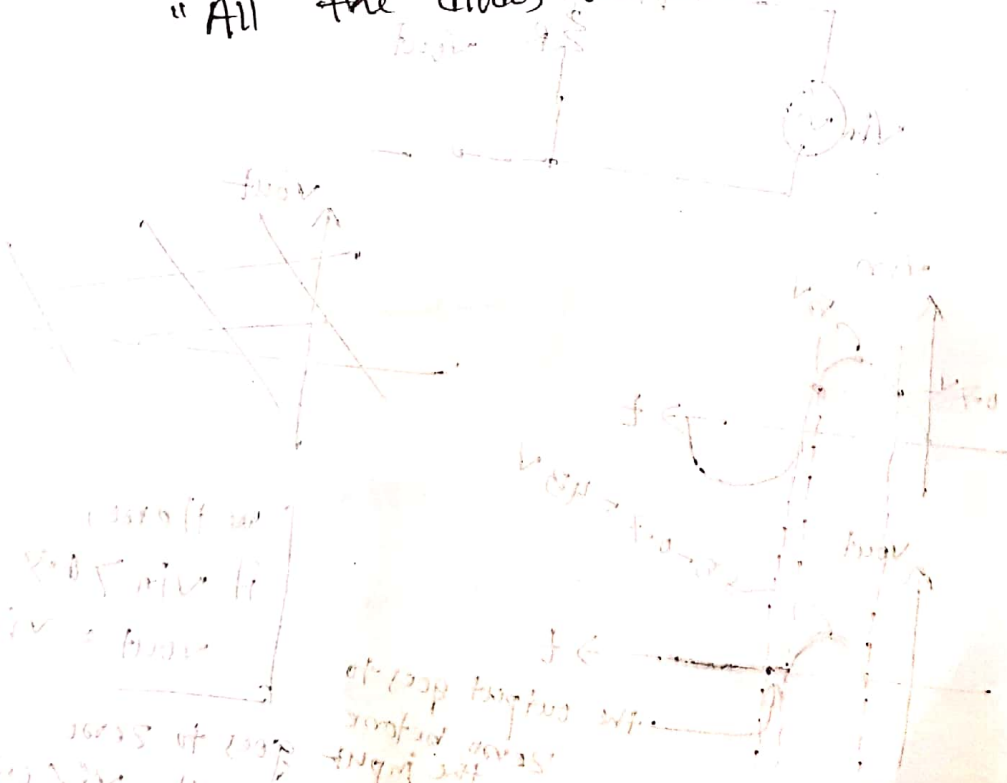
# Here for F.W rectifier we have one  
"All the diodes are ideal"



Topic Name : \_\_\_\_\_

Day : \_\_\_\_\_

Time : \_\_\_\_\_

Date : / /

## Rectifiers with REAL DIODE




For real diode  $I_D = I_S \left[ e^{\frac{V_D}{V_T}} - 1 \right]$

non-linear device

we do some approximation when design circuit with non-linear device.

\*\*\* Here we use CVD model, with  $V_{D0} = 0.7$

### H.W. Rectifiers with real diode :

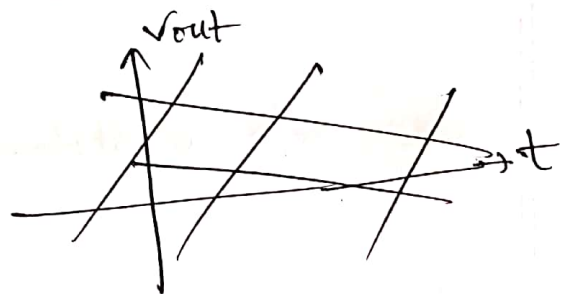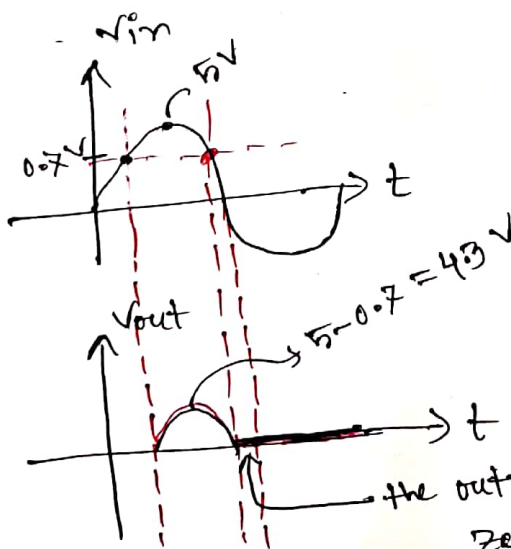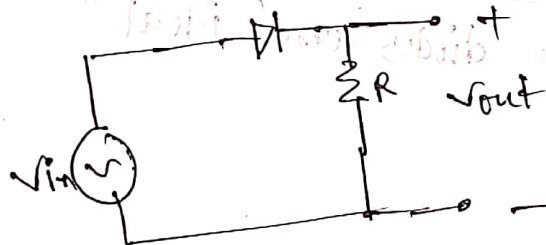

Here,  
if  $V_{in} > 0.7$   
 $V_{out} = V_{in} - 0.7$

the output goes to zero before the input goes to zero as  $V_{in} < 0.7$ ,  $V_{out} = 0$


Day: \_\_\_\_\_

Time :                      Date :        /        /


H.W. rectifier (Real diode)

(\*) peak value .  $V_p = V_i - V_{D0}$   
 $\downarrow$  input  $\rightarrow 0.7V$  for silicon diode

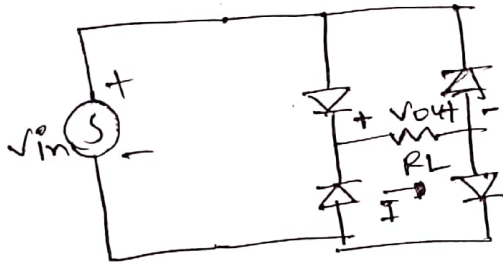Full wave rectifiers using (real diode) %



From positive  
cycle  
and negative  
cycle

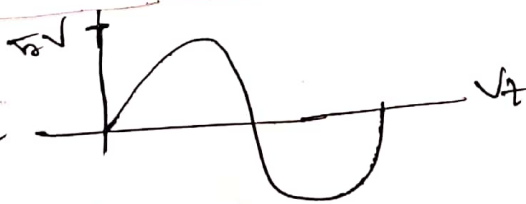

Herre 2 - variation.

$$2 \times 0.7 = 1.4V$$

5 - 1.4v


~~Black have~~  
~~system.~~

Topic Name : \_\_\_\_\_

Day : \_\_\_\_\_

Time : \_\_\_\_\_ Date : / /

## F.W Rectifier circuit

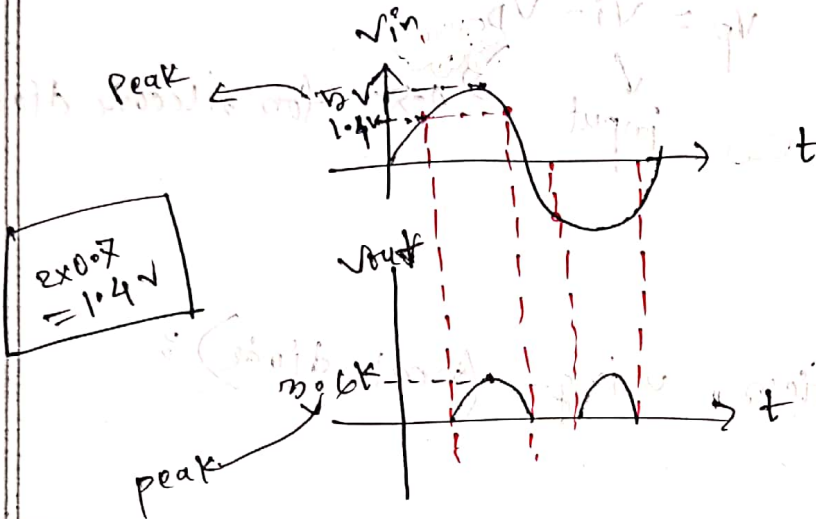

F.W Rectifier

peak voltage,

$$V_p = V_m - 2V_D$$

$$V_{p1} = 1.4V$$

$$V_{p2} = 1.4V$$




Topic Name : \_\_\_\_\_


Day : \_\_\_\_\_

Time : \_\_\_\_\_ Date : / /

# Transfer char. (Real diode)

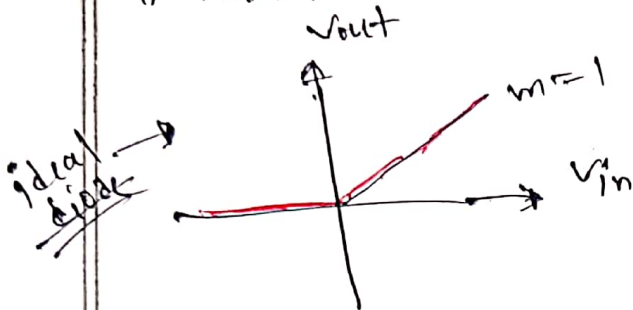


H.W rectifier

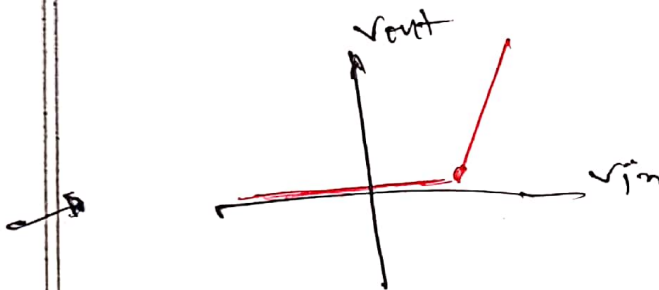


$$V_{out} = V_{in} \sin \omega t$$

F.W rectifier

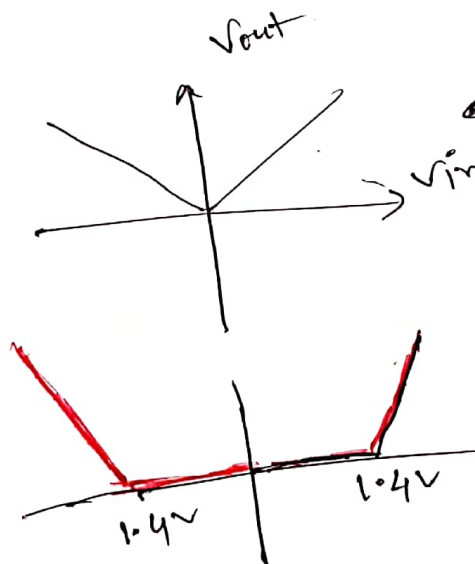


ideal diode

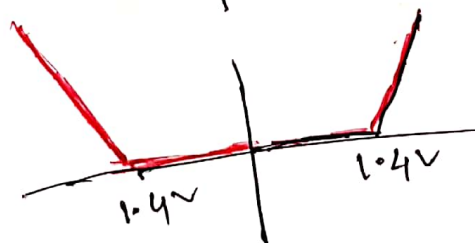


\*\* [see slide] \*\* → For these transfer characteristics for better visualization  
 Topic Name: H.W. Rectifiers filtering Day 25 General

# Transfer char. (Real diode)

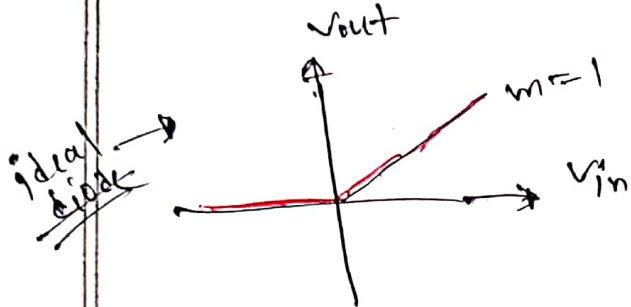


H.W. rectifiers

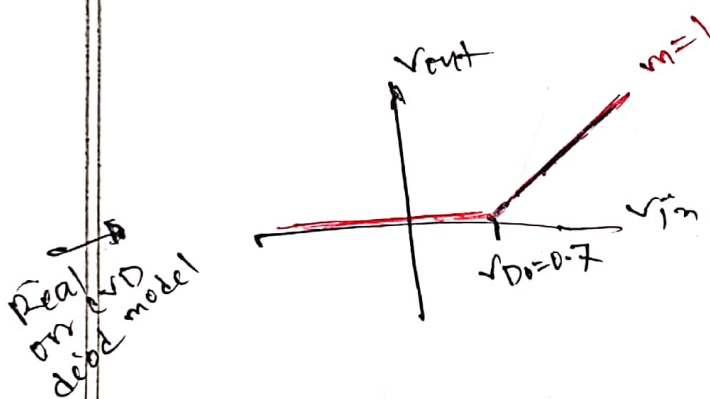

$$V_{out} = V_{in} - 0.7$$

$$y = x - c$$

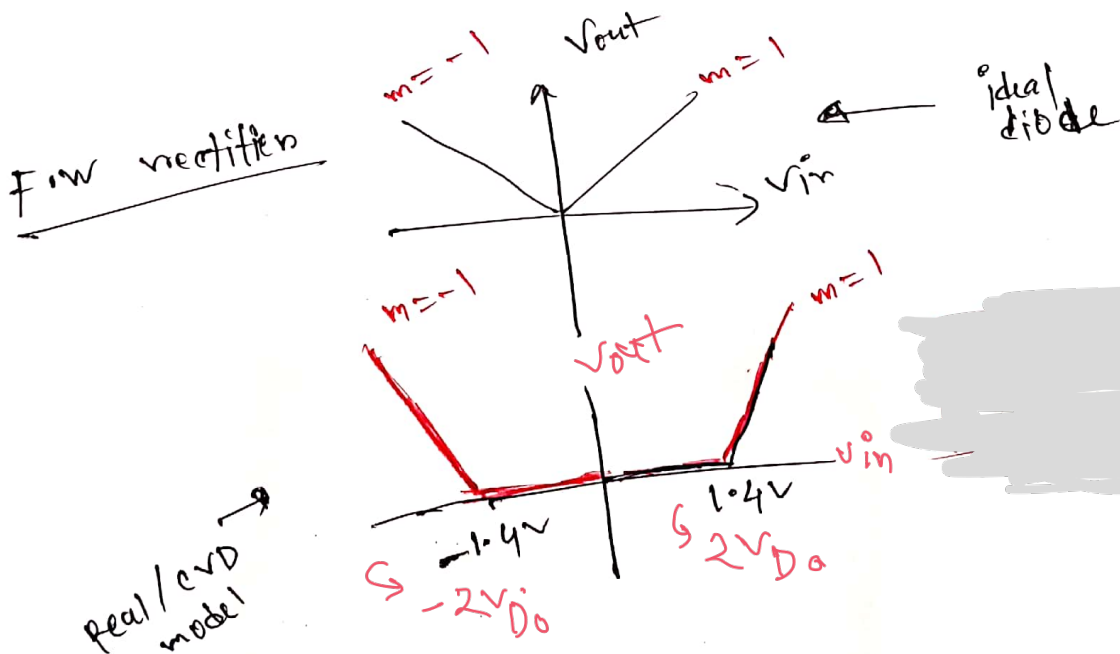

+ve cycle,  $V_{out} = V_{in} - 1.4$   
 $= V_{in} - 2V_{Do}$   
 -ve cycle,  $V_{out} = -V_{in} - 1.4$   
 $= -V_{in} - 2V_{Do}$