
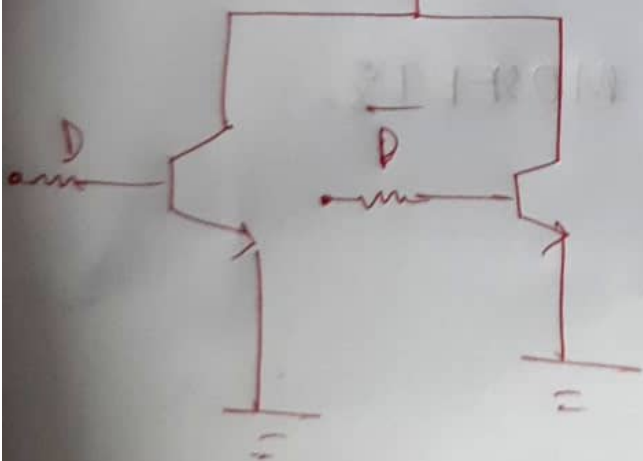


- a) Assume the BJT is in active mode, find
- i_B
 - i_C
 - i_E
 - V_o
- b) Is the assumption correct? verify

(b)

[5]

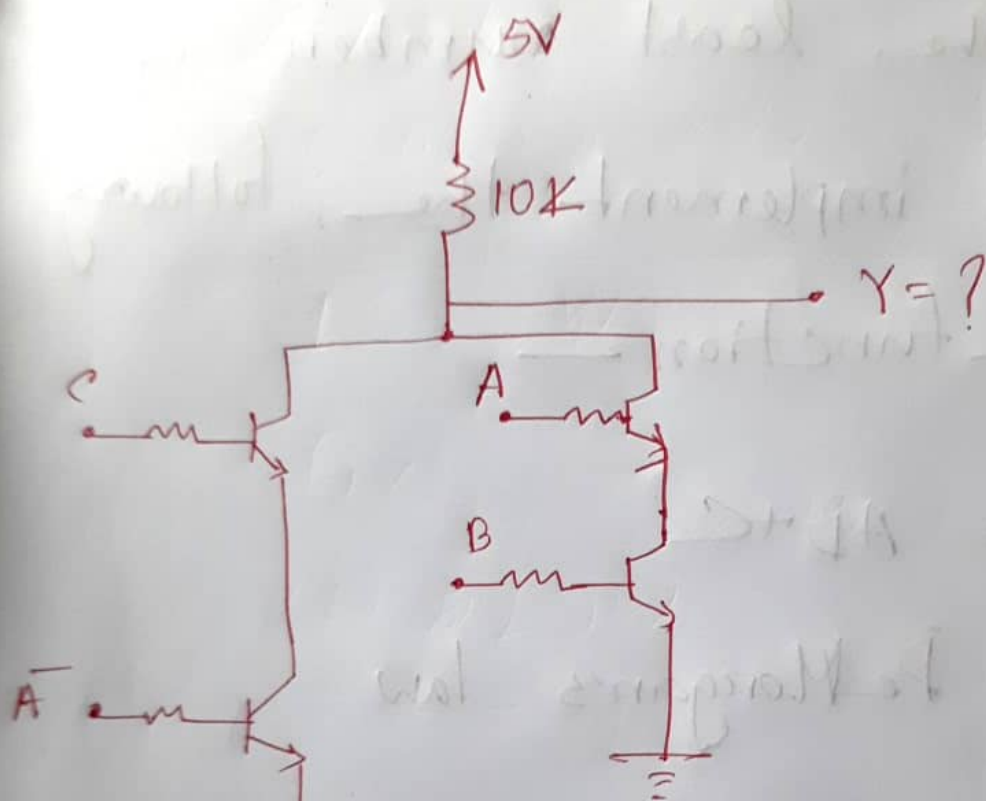

(ii)
Find out the logic function of Y.

Bonus

(i)

Using the least number of Mosfets implement the following logic function —

$$Y = AB + C$$

Hint : De Morgan's law

(ii)

Implement using MOSFET's,
use 'S Model'

$$Y = \overline{AB + (C+D)}$$