
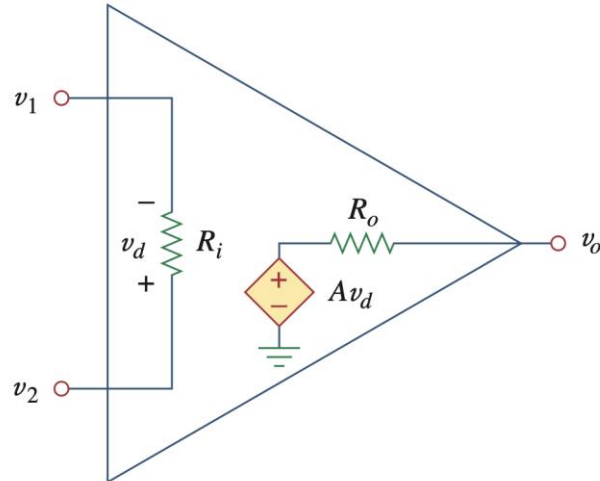


Lecture 4

Op Amp – Part 2

Review – Operational Amplifier

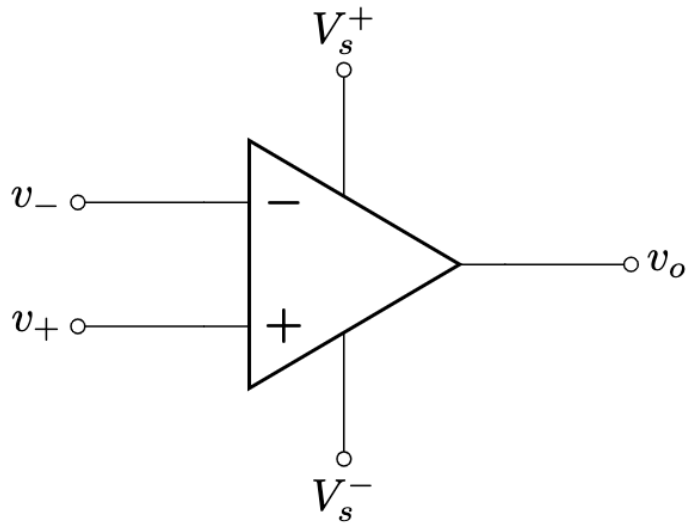

$v_1 = v_-$ = voltage of inverting terminal

$v_2 = v_+$ = voltage of noninverting terminal

$v_d = v_+ - v_- = v_2 - v_1$
= differential input voltage for VCVS

A = Open loop gain

R_i = Input resistance


R_o = Output resistance

Differential amplifier \Rightarrow amplifies the difference

$$v_o = Av_d = A(v_2 - v_1) = A(v_+ - v_-)$$

Review – Ideal Op Amp

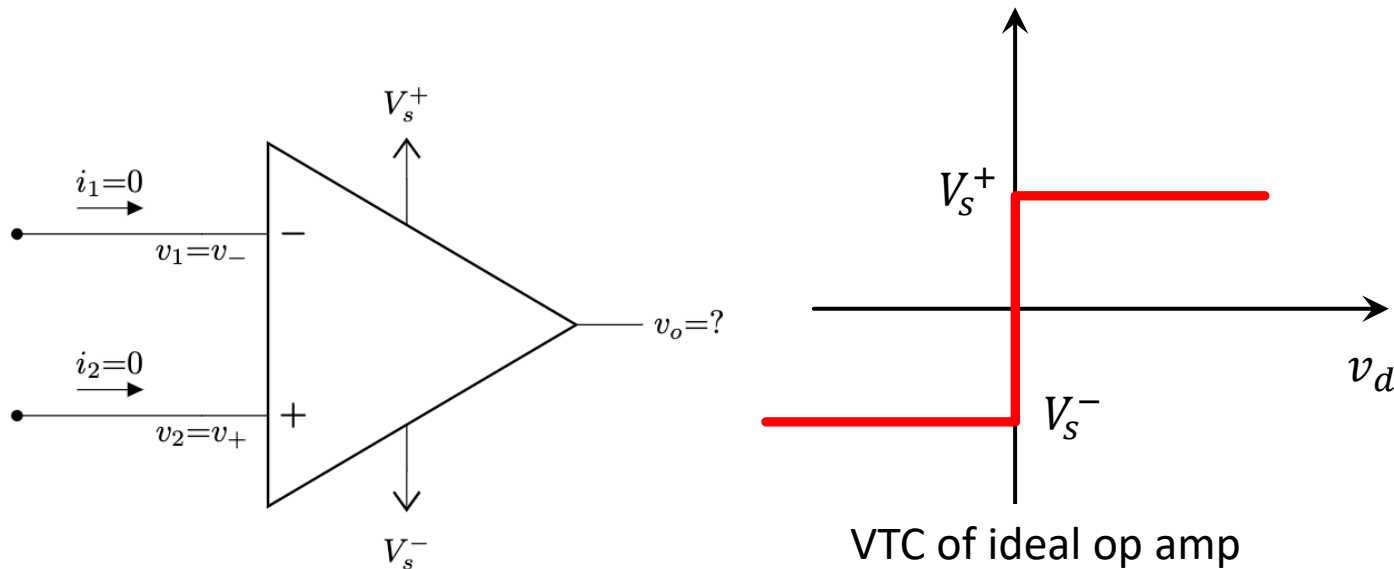- Infinite open-loop gain, $A = \infty$
- Infinite input resistance, $R_i = \infty = \text{open circuit}$
- Zero output resistance, $R_o = 0 = \text{short circuit}$
- As $R_i = \infty$ (open circuit), $i_1 = i_2 = 0$. Therefore, circuit solving become much simpler



$$v_o = \begin{cases} V_s^+ & \text{if } v_d > 0 \Rightarrow v_2 > v_1 \\ V_s^- & \text{if } v_d < 0 \Rightarrow v_2 < v_1 \end{cases}$$

Application of Ideal Op Amp - Comparator

- A comparator compares two voltages to determine which is larger.
- The comparator is essentially an op-amp operated in an open-loop configuration
- Two types –
 - (1) **Non-inverting**: outputs a positive voltage ($V_H = V_S^+$) when input is greater than reference
 - (2) **Inverting**: outputs a negative voltage ($V_L = V_S^-$) when input is greater than reference
- Application – smoke detector, turning AC on/off automatically, etc


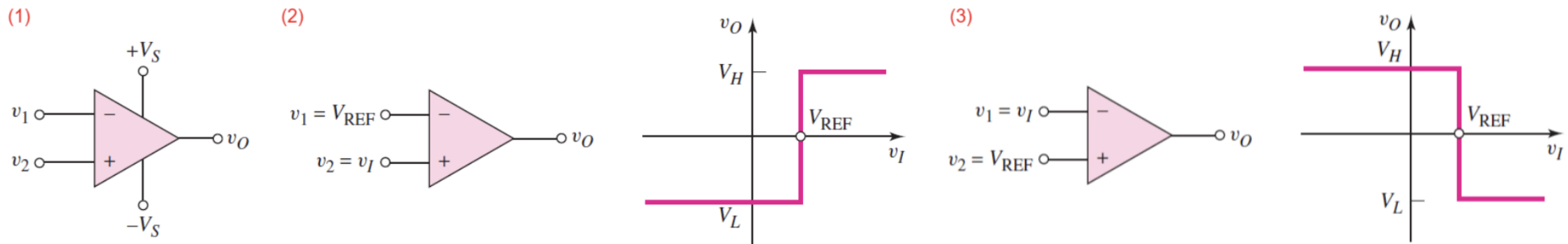


Figure 2: (1) Op-Amp Comparator (2) Noninverting Circuit (3) Inverting Circuit

Comparator Application – Automatic AC

Auto AC on/off

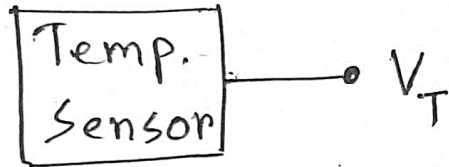


$$V_T \propto T$$

$$23^\circ\text{C} \rightarrow V_T = 1.2\text{v}$$

$$24^\circ\text{C} \rightarrow V_T = 1.4\text{v}$$

$$25^\circ\text{C} \rightarrow V_T = 1.6\text{v}$$

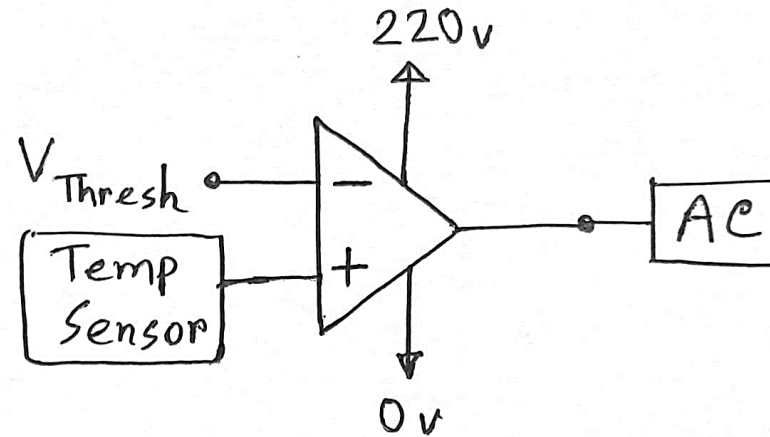AC should be ON if
 $\hookrightarrow T > 24^\circ\text{C}$




Threshold voltage, $V_{\text{Thresh}} = 1.4\text{v}$


if, $V_T > V_{\text{Thresh}} \rightarrow V_o = V_s^+ = 220\text{v}$

if, $V_T < V_{\text{Thresh}} \rightarrow V_o = V_s^- = 0\text{v}$

Smoke Detector

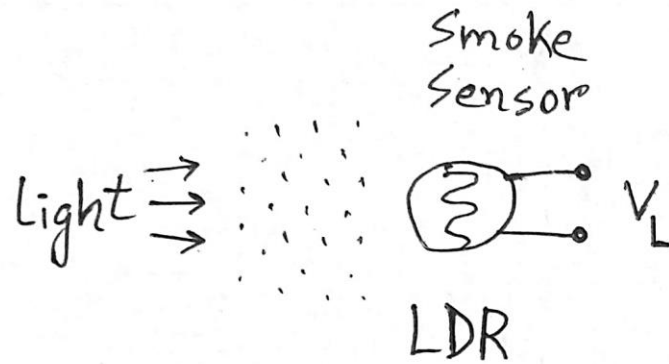

$$V_L \propto R$$

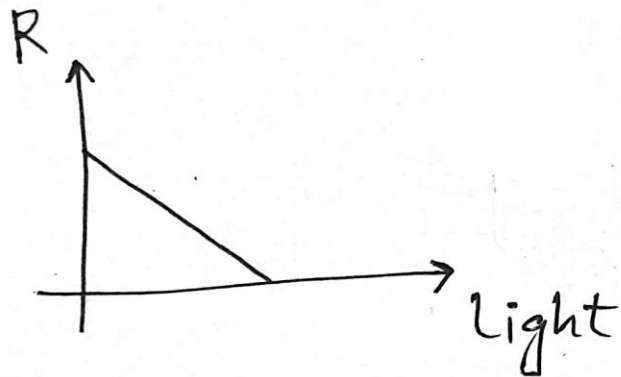


No smoke, $V_L = \text{small} = 2\text{v}$

smoke, $V_L = \text{high} = 4\text{v}$


$V_L > 3\text{v} \rightarrow \text{Alarm on}$

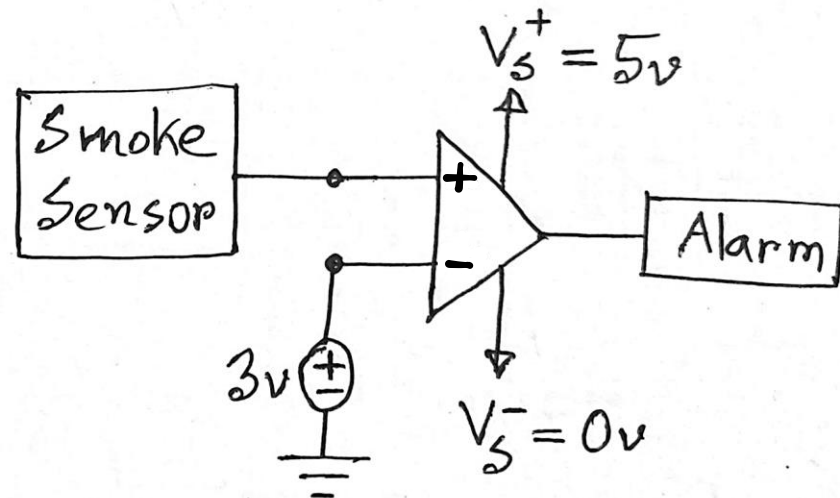$V_L < 3\text{v} \rightarrow \text{Alarm off}$



Introducing Negative Feedback

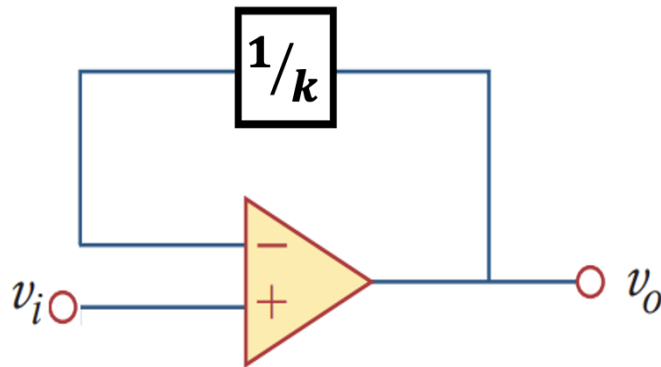- The gain (A) of an ideal op amp is infinity, practically extremely large.
- The power supply (+Vs and -Vs) limits the op amp's output.
- We require a method to have a finite gain. That is what negative feedback does.
- Negative feedback: feeding back **a portion** of output to inverting input
- Idea – the output will become stable due to a self-correcting mechanism




For example, here, $v_- = \text{one } k'\text{'th part of output} = \frac{1}{k}$

If v_o increases, v_- will increase, hence v_d will decrease, eventually v_o decreases

If v_o decreases, v_- will decrease, hence v_d will increase, eventually v_o increase

Negative Feedback – Numerical Example

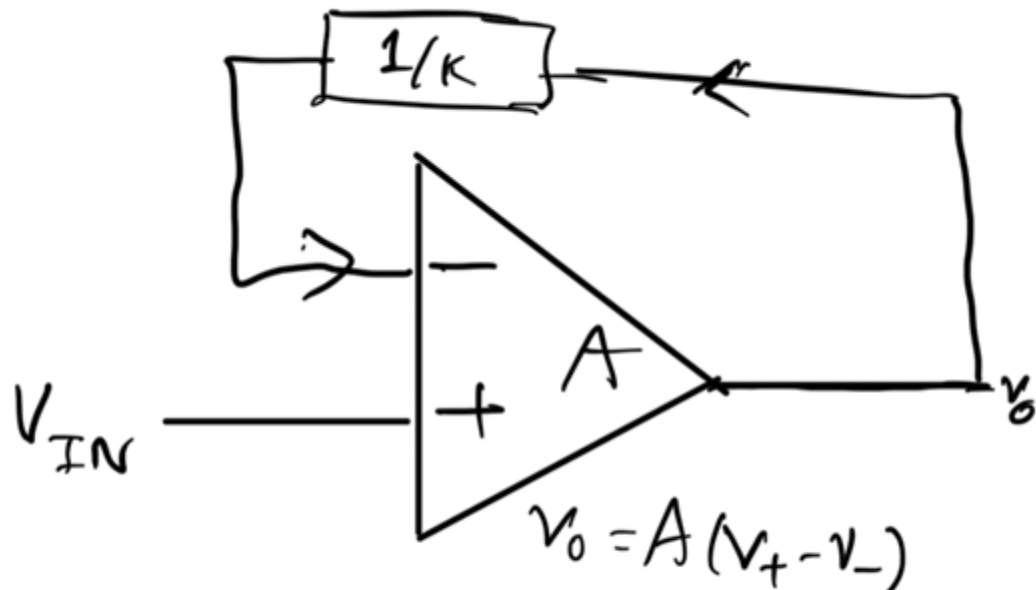


$$Gain = \frac{Out}{In} = 2.307$$

$V_{IN} = 1V$, $K = 10$, $A = 3$

$V_O = 0V$	$V_O = 3V$	$V_O = 2.1V$	} $V_O = 2.307$	
$V_- = 0V$	$V_- = 0.3V$	$V_- = 0.21V$		$V_- = 0.2307$
$V_d = 1V$	$V_d = 0.7$	$V_d = 0.29$		$V_d = 0.2693$
$\therefore V_O = 3V$	$V_O = 2.1V$	$V_O = 2.37$		$V_O = 2.307$



Negative Feedback – Derivation of Gain

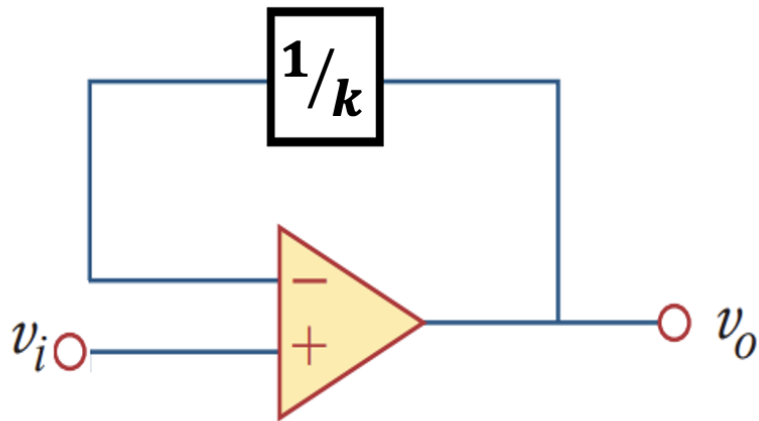

Here, $v_- = \frac{v_o}{k}$

We know, $v_o = A v_d$

$$\Rightarrow v_o = A(v_+ - v_-)$$

$$= A\left(v_i - \frac{v_o}{k}\right)$$

$$= A v_i - \frac{A}{k} v_o$$

$$\Rightarrow v_o \left(1 + \frac{A}{k}\right) = A v_i$$

$$\text{So, } v_o = \frac{A v_i}{1 + \frac{A}{k}}$$

$$\text{or, } v_o = \frac{v_i}{\frac{1}{A} + \frac{1}{k}}$$


A is extremely large,

$$\text{so, } \frac{1}{A} \approx 0$$

$$v_o = \frac{v_i}{\frac{1}{k}} = k v_i$$


If $k = 10$ (meaning we feed back one tenth of the output to negative input), we will get $v_o = 10 * v_i$. that is 10 fold gain.

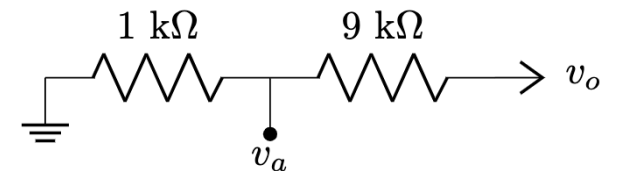How to get $1/k$ of output to input? Voltage dividers!




$$v_a = \frac{1 \text{ k}\Omega}{1 \text{ k}\Omega + 9 \text{ k}\Omega} \times v_o = \frac{v_o}{10}$$

Non-Inverting Amplifier

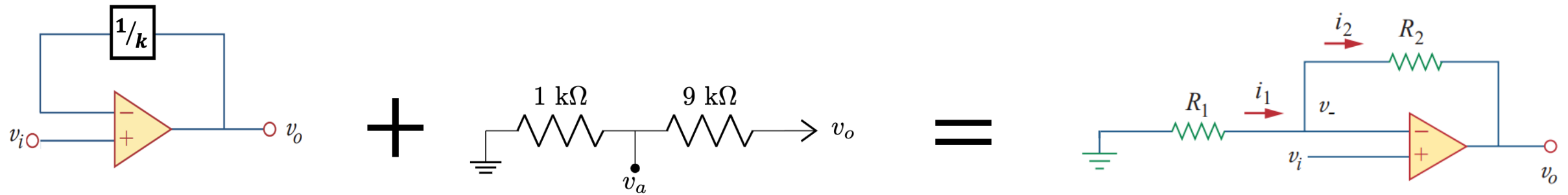


Non-Inverting Amplifier

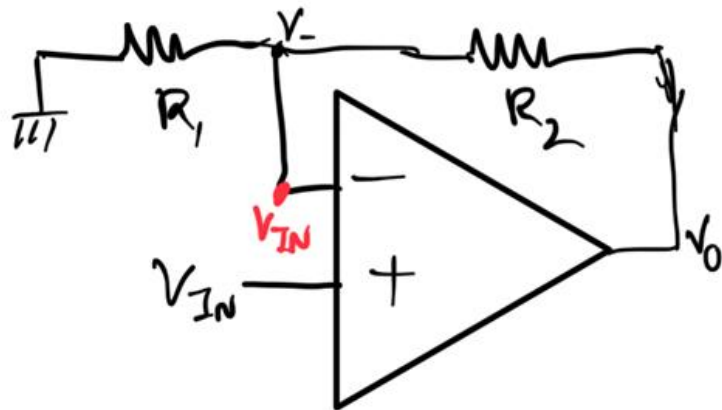

$$V_- = \frac{R_1}{R_1 + R_2} V_O = \frac{1}{1 + \frac{R_2}{R_1}} V_O$$

Gain > 1

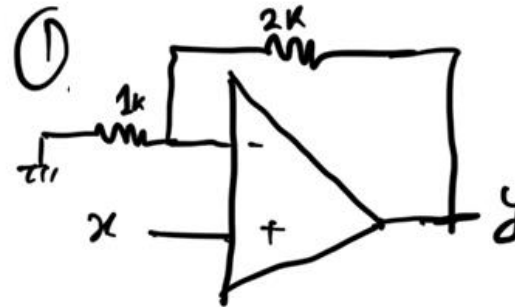
$$\therefore V_O = \left(1 + \frac{R_2}{R_1}\right) V_{IN}$$



$$y = \left(1 + \frac{2}{1}\right)x$$
$$\Rightarrow y = 3x$$

② Design $y = 4x$

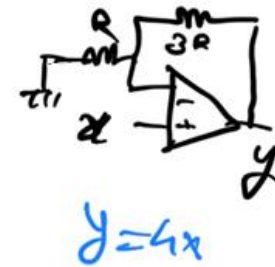
$$1 + \frac{R_2}{R_1} = 4 \Rightarrow \frac{R_2}{R_1} = 3$$



$$y = 4x$$



Solving Circuit with Ideal Op Amp + NF

- For ideal op-amp
 - Infinite input resistance, $R_i = \infty = \text{open circuit}$
 - Zero output resistance, $R_o = 0 = \text{short circuit}$
 - $i_i = 0$ and $i_+ = 0$
- **When there is negative feedback**, For ideal A as is infinitely high, for a finite output voltage v_o , $\frac{v_o}{A} = v_d = 0 \Rightarrow v_+ = v_-$. This is called **virtual short circuit**
- Because of these, solving ideal op-amp circuit with negative feedback is very simple

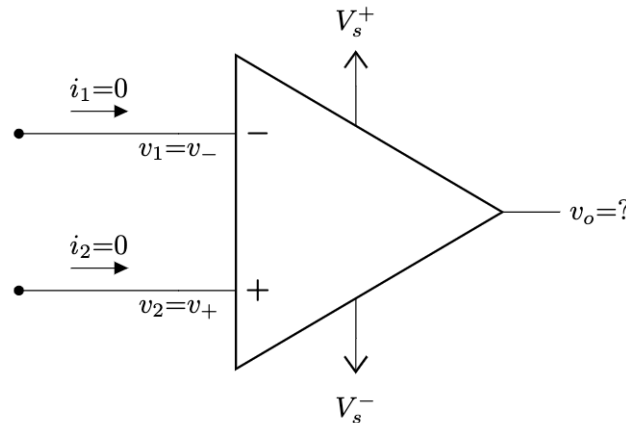


Example – Inverting Amplifier

Solve the circuit to find v_o

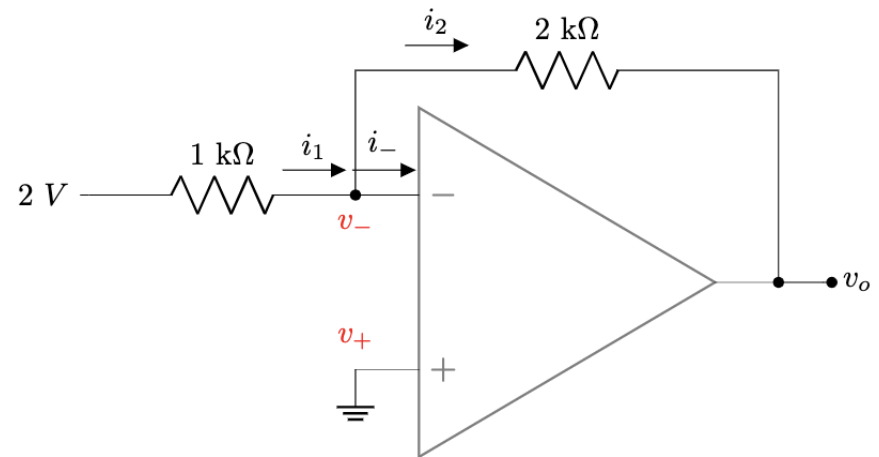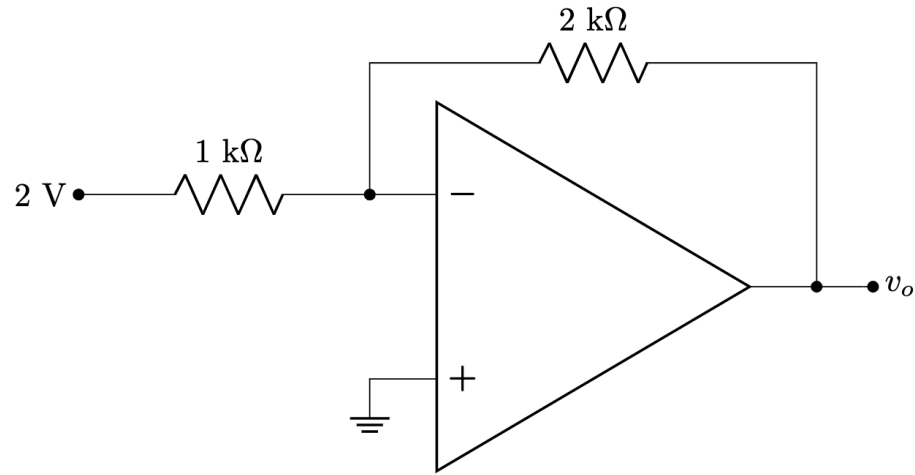

Example – Inverting Amplifier

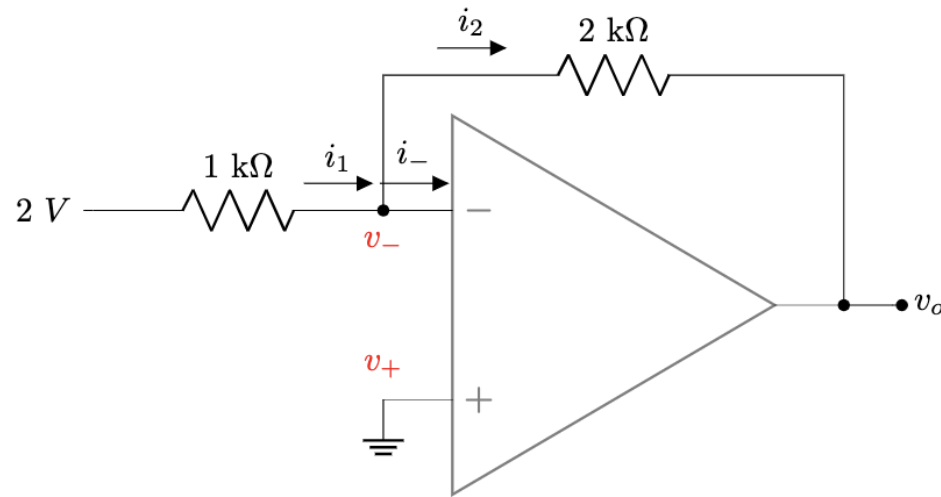

Since v_+ is connected to ground, $v_+ = 0V$

Since there is negative feedback, from virtual short, $v_- = v_+ = 0V$

From Ohm's law for 1 kΩ $\Rightarrow i_1 = \frac{2V - 0V}{1 \text{ k}\Omega} = 2mA$


$$\text{Gain} = -\frac{4V}{2V} = -2 \text{ (hence **inverting**)}$$

Since ideal op-amp, $i_- = i_+ = 0$

From KCL at v_- , $i_1 = i_- + i_2 \Rightarrow i_1 = i_2 = 2 \text{ mA}$

From Ohm's law for 2 kΩ $\Rightarrow i_2 = \frac{v_- - v_o}{2 \text{ k}\Omega} = 2mA \Rightarrow v_o = -i_2 \times 2 = -4V$ [ANS]

General Analysis of Inverting Amplifier

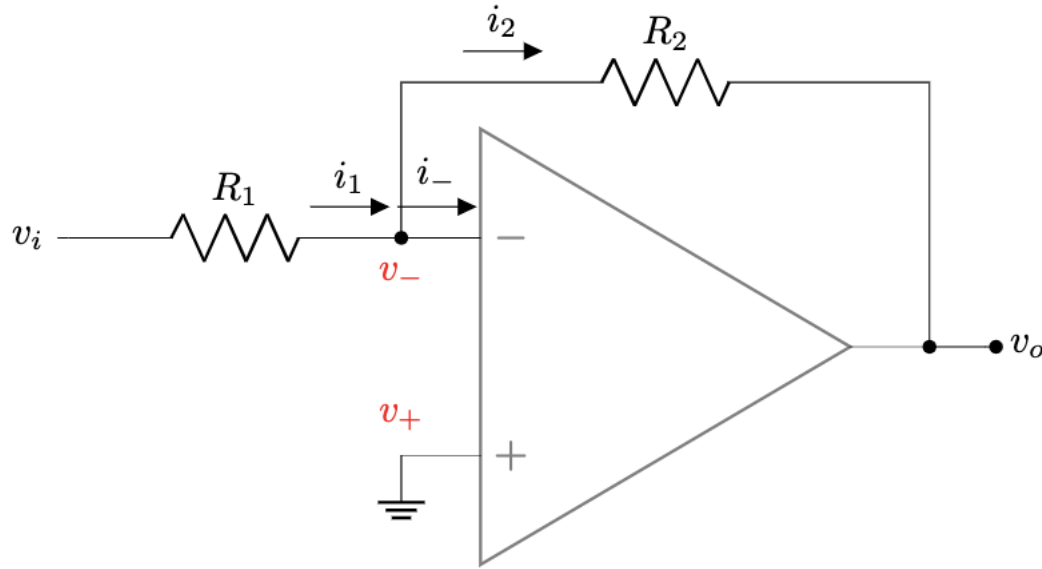

Since v_+ is connected to ground, $v_+ = 0V$

Since there is negative feedback, from virtual short, $v_- = v_+ = 0V$

From Ohm's law for $R_1 \Rightarrow i_1 = \frac{v_i - 0V}{R_1} = v_i/R_1$

Since ideal op-amp, $i_- = i_+ = 0$

From KCL at v_- , $i_1 = i_- + i_2 \Rightarrow i_1 = i_2 = v_i/R_1$

From Ohm's law for $R_2 \Rightarrow i_2 = \frac{v_- - v_o}{R_2} = \frac{v_i}{R_1} \Rightarrow v_o = -i_2 \times R_2 \Rightarrow v_o = -\frac{R_2}{R_1} v_i$ [ANS]

$$\text{Gain} = -\frac{R_2}{R_1}$$

Example

