

1

√1

we are taking this (-) because adder has (-) in the formula




$$f = - \left[\int \left(6x + 3 \frac{d^2 y}{dt^2} \right) dt \right] + \left[3 \frac{dz}{dt} \right]$$

This (-) because integration formula has (-)

$$- \int \left(6x - 3 \frac{d^2 y}{dt^2} \right) dt$$

This minus (-) because adder formula has (-)

$$- (-6x \oplus 3 \frac{d^2 y}{dt^2})$$

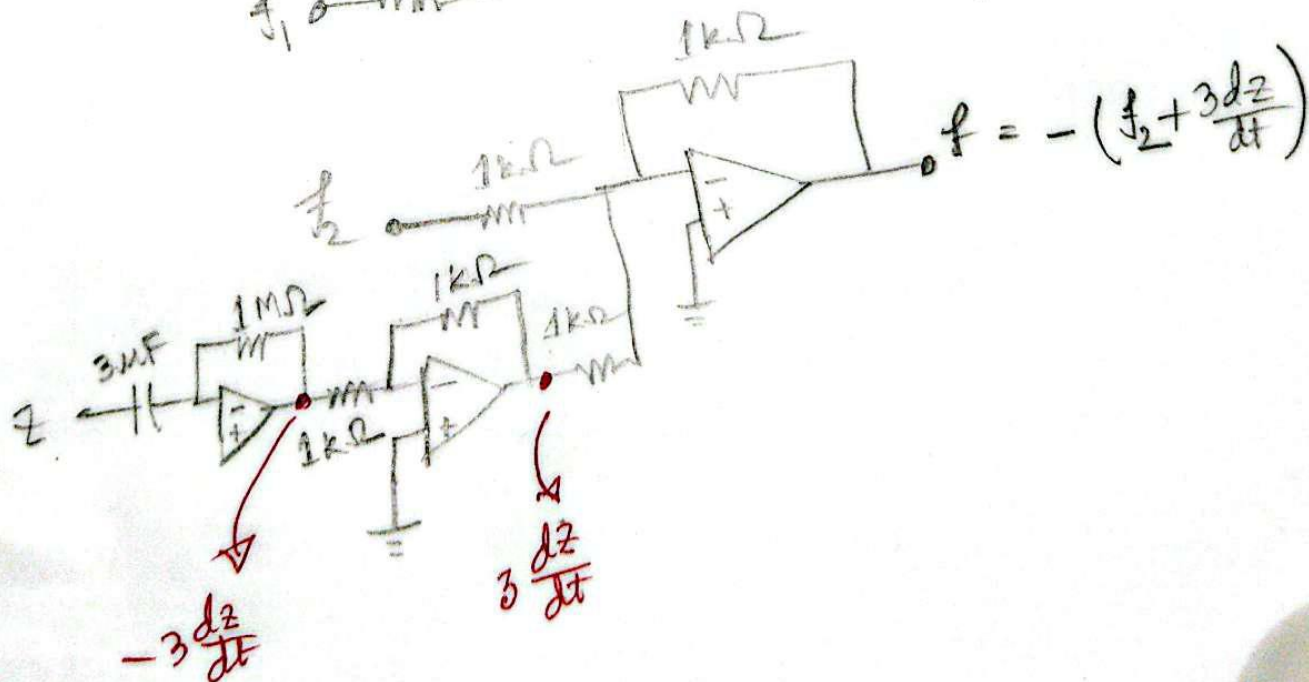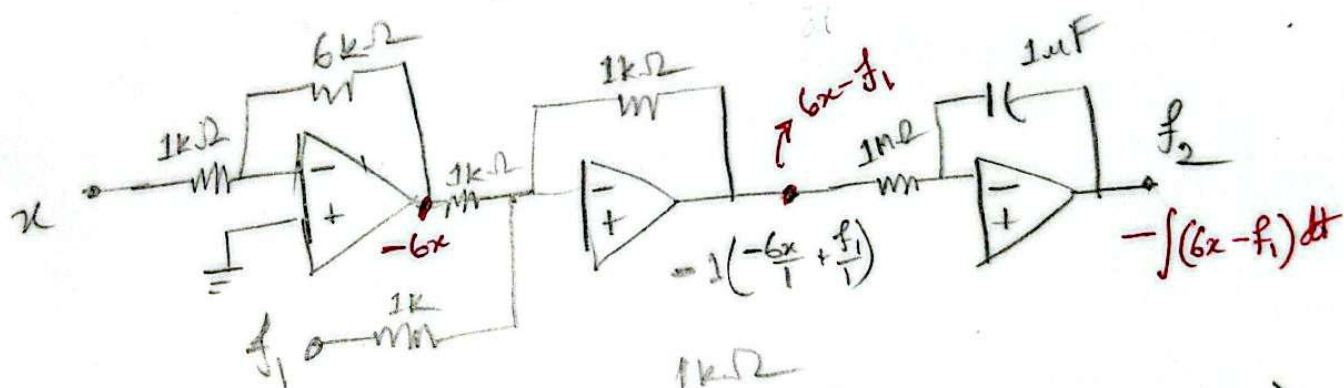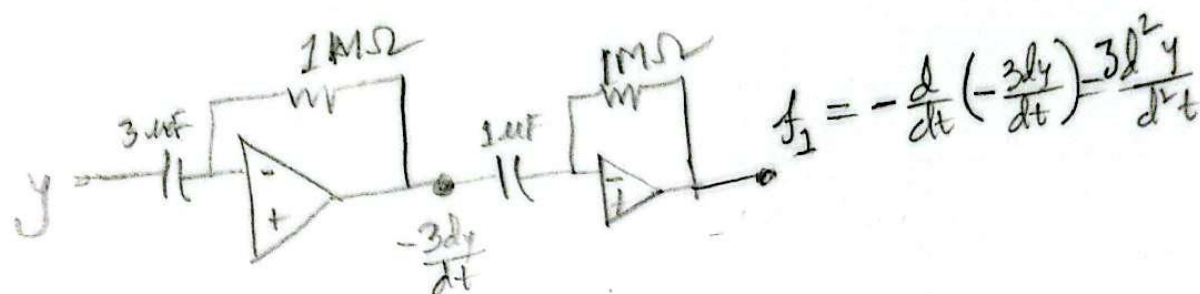


2 [i.] $-V_0 = \frac{V_3}{5} - \frac{V_1}{5} + \frac{V_1}{2} - \frac{V_2}{2}$


Inv. Adder Formula

$$V_0 = -R_f \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$
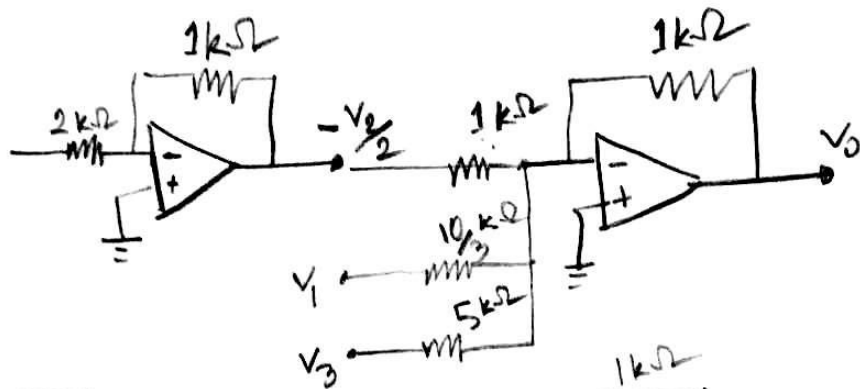
$$\Rightarrow V_0 = - \left(\frac{3V_1}{10} + \frac{V_3}{5} - \frac{V_2}{2} \right)$$




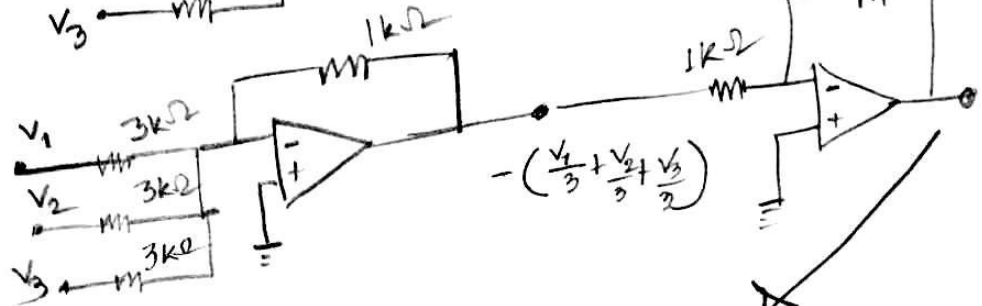[ii] average = $\frac{V_1 + V_2 + V_3}{2}$



$$V_0 = \frac{V_1}{3} + \frac{V_2}{3} + \frac{V_3}{3} = \frac{V_1 + V_2 + V_3}{3}$$

3

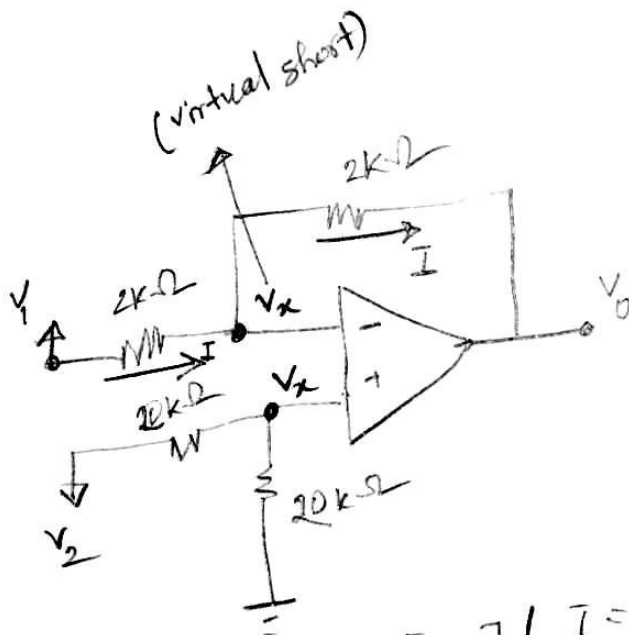


$$V_x = \frac{20}{20+20} \times V_2 = \frac{V_2}{2}$$

$$I = \frac{V_1 - V_x}{2} = \frac{V_x - V_0}{2}$$


$$\Rightarrow \frac{V_1 - \frac{V_2}{2}}{2} = \frac{\frac{V_2}{2} - V_0}{2}$$

$$\Rightarrow \frac{V_1}{2} - \frac{V_2}{4} = \frac{V_2}{4} - \frac{V_0}{2}$$

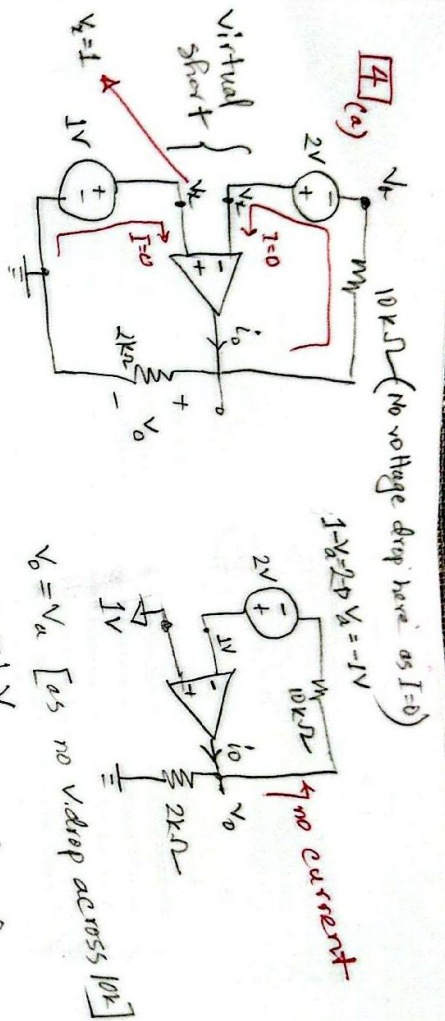
$$\Rightarrow V_0 = \boxed{V_1 - V_2} \text{ difference}$$



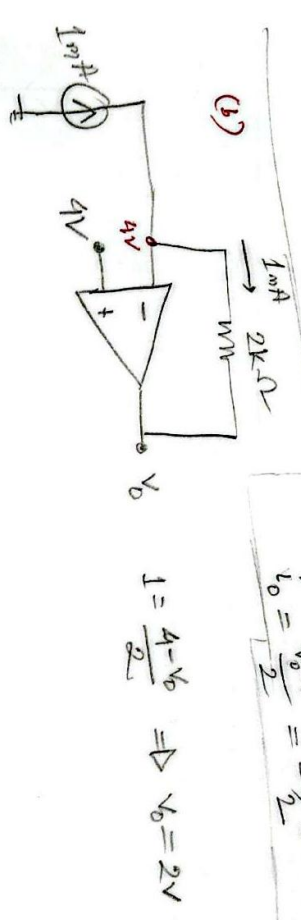$V_0 = V_a$ [as no voltage drop across $10k$]
 $= -1V$
 i_o will flow through $2k\Omega$
 $i_o = \frac{V_0 - 0}{2} = -\frac{1}{2} = -0.5mA$



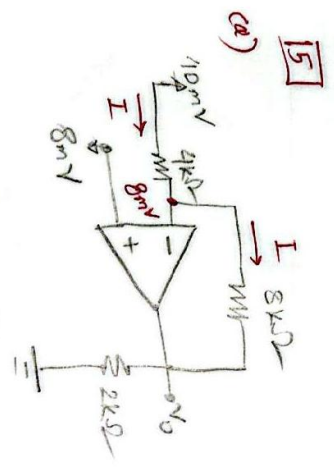
$I = \frac{4 - V_0}{2} \Rightarrow V_0 = 2V$



$I = \frac{10 - 8}{1} = \frac{2}{1} = 2mA$

$\Rightarrow \frac{2}{2} = \frac{8 - V_0}{2}$

$\Rightarrow V_0 = 9mV$

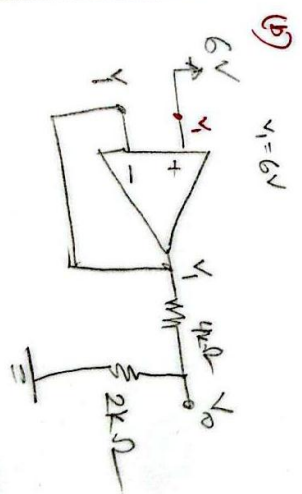


$V_0 = \frac{6}{2+4} \times 4$
 $= 2V$


16 $V_o = -50 \left(\frac{-3}{10} + \frac{V_2}{20} + \frac{5}{50} \right)$
 -16.5

$V_o = 10.6$

2

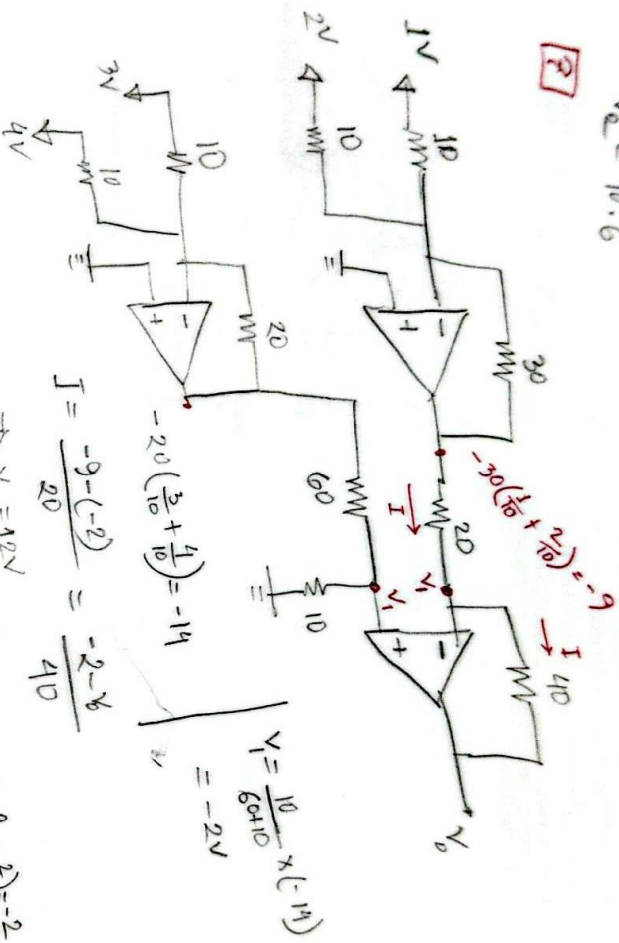

8

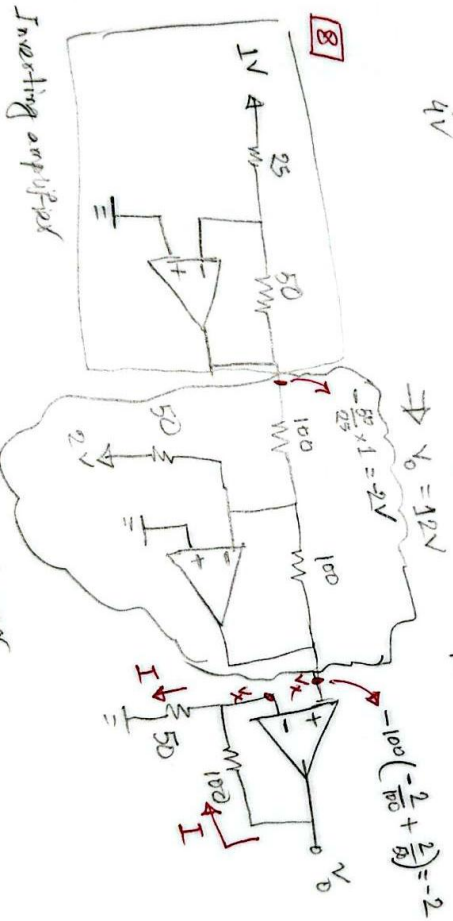



Inverting Summed

Handwritten calculations for problem 8:


$$I = \frac{V_o - 0}{50} = \frac{V_o - V_x}{100}$$

$$\Rightarrow \frac{-2}{50} = \frac{V_o - (-2)}{100} \Rightarrow V_o = -6$$

19

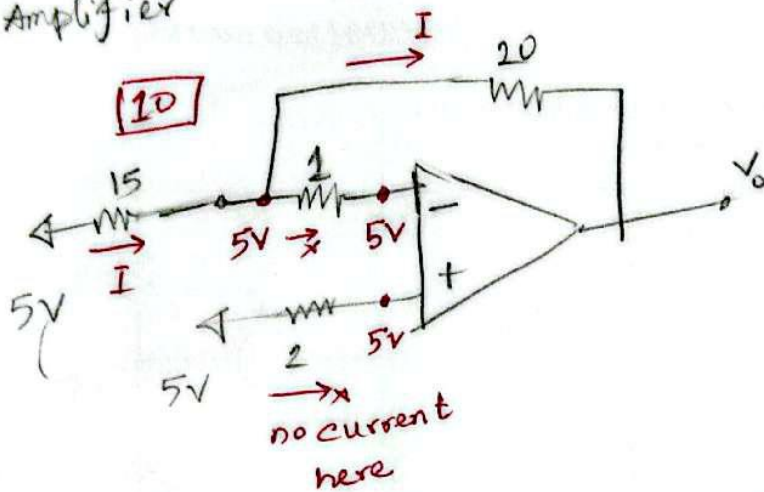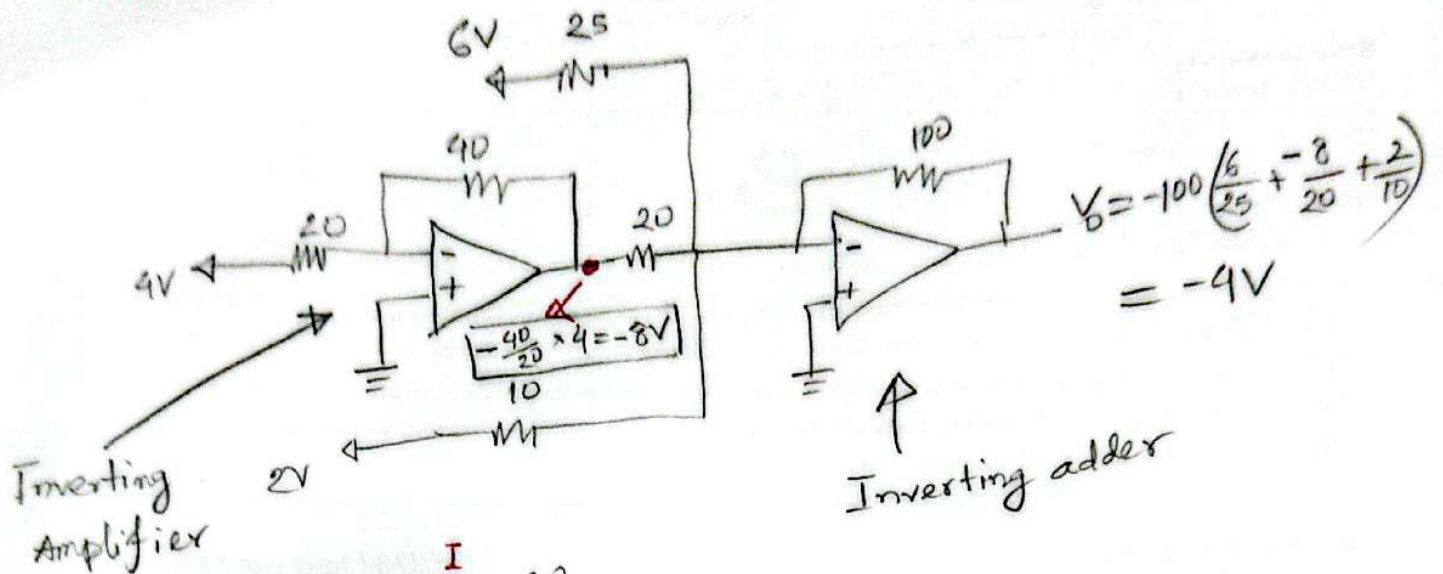

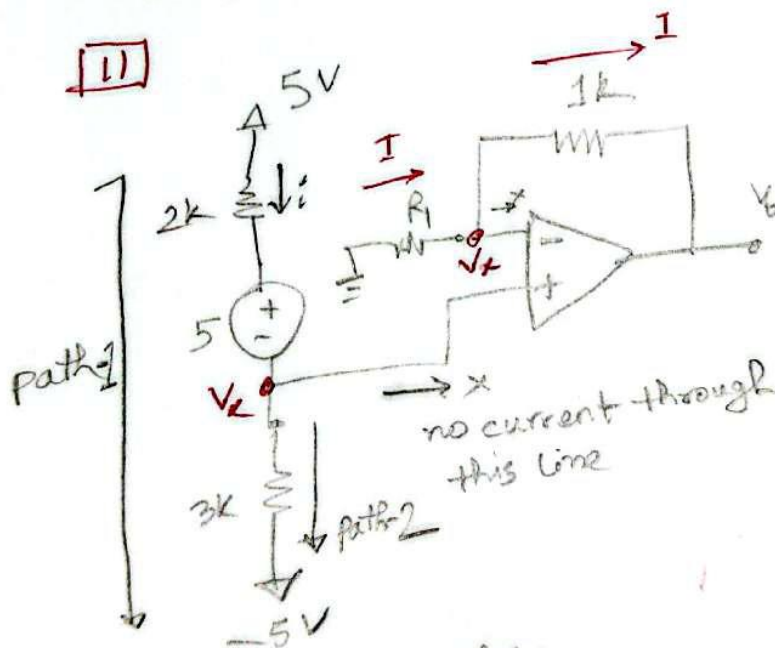[no current passes through $1k\Omega$ & $2k\Omega$, so no voltage drop]



KVL through the path-1:

$$2i + 5 + 3i = 5 - (-5)$$

$\Rightarrow i = 1A$

KVL through path-2:

$$3i = V_x - (-5)$$

$$\Rightarrow 3 \times 1 = V_x + 5$$

$$\Rightarrow V_x = -2V$$


$$I = \frac{0 - V_x}{R_1} = \frac{V_x - V_o}{1}$$

$$\Rightarrow \frac{-(-2)}{R_1} = \frac{-2 - (-4)}{1}$$

$$\Rightarrow R_1 = 1k\Omega$$

$\int N(B) \cdot f(x) dx = Y + C \rightarrow \text{Integration constant}$

~~12~~ **13**

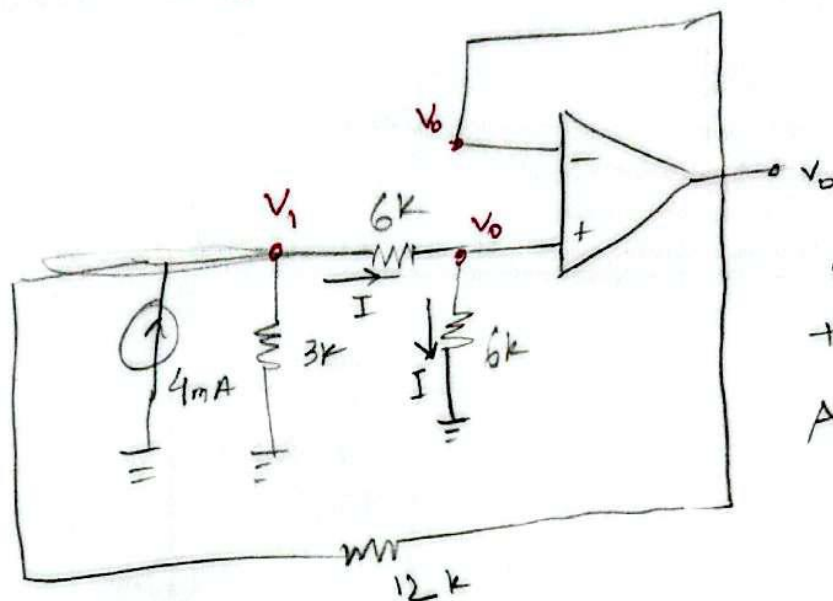

$I = \frac{V_0 - 0}{6} = \frac{V_0}{6}$
 Same, I will flow through the other 6k

Again, $I = \frac{V_1 - V_0}{6}$

$$\Rightarrow \frac{V_0}{6} = \frac{V_1 - V_0}{6}$$

$$\Rightarrow V_1 = 2V_0$$


KCL @ node 1 (V_1):

$$4 = \frac{V_1 - 0}{3} + \frac{V_1 - V_0}{6} + \frac{V_1 - V_0}{12}$$

$$\Rightarrow 4 = \frac{2V_0}{3} + \frac{V_0}{6} + \frac{V_0}{12}$$

$$\Rightarrow V_0 = 4.36$$

17

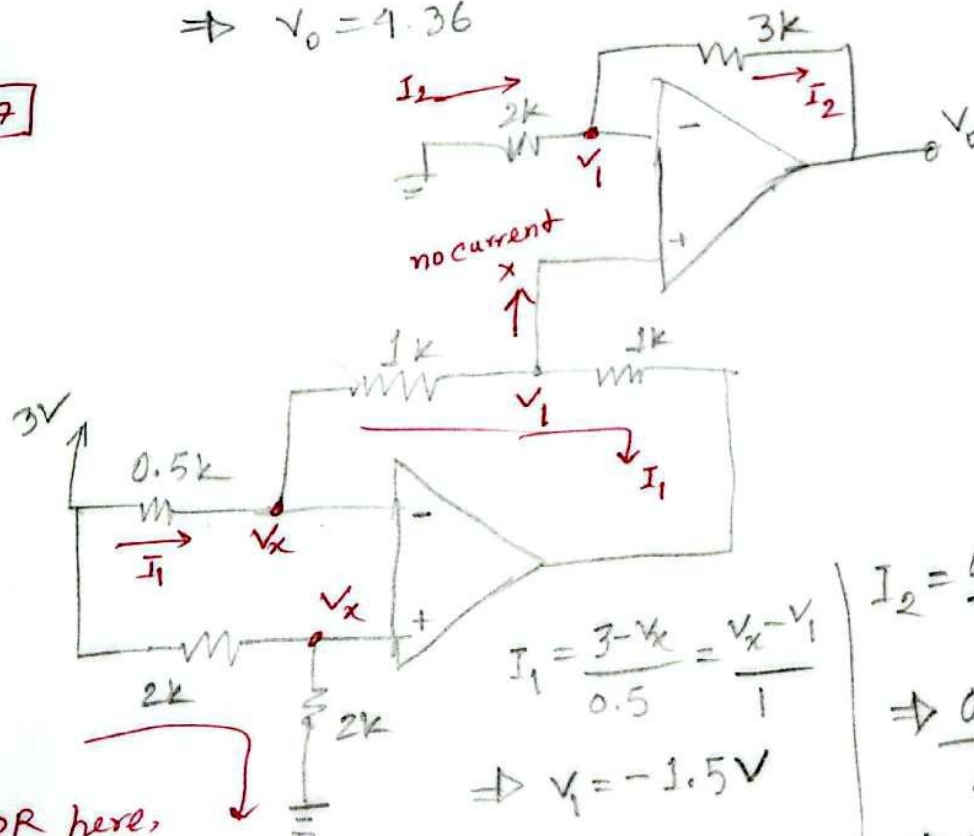

VDR here,

$$V_x = \frac{2}{2+2} \times 3 = 1.5V$$

$$I_1 = \frac{3 - V_x}{0.5} = \frac{V_x - V_1}{1}$$

$$\Rightarrow V_1 = -1.5V$$

$$I_2 = \frac{0 - V_1}{2} = \frac{V_1 - V_0}{3}$$

$$\Rightarrow \frac{0 - (-1.5)}{2} = \frac{-1.5 - V_0}{3}$$

$$\Rightarrow V_0 = -3.75$$

[19]

Integrator out:

$$V_o = -\frac{1}{R_c} \int V_i dt + V_{\text{initial}}$$

$$= -\frac{1}{5 \times 0.1} \int V_i dt + V_{\text{initial}}$$

$$= -2 \int V_i dt + V_{\text{initial}}$$

from 0 to 0.5 ms, $V_i = 1$

for any time
 $0 \leq t \leq 0.5$

$$V_o = -2 \int_0^t 1 dt + V_{\text{initial}}$$

$$= -2 [t]_0^t = -2(t-0) = -2t$$

At $t=0$, $V_o=0$
At $t=0.5\text{ms}$, $V_o=-1\text{V}$

from 0.5 to 1 ms, $V_i = -1$

for any time
 $0.5 \leq t \leq 1$

$$V_o = -2 \int_{0.5}^t (-1) dt + V_{\text{initial}}$$

$$= 2 [t]_{0.5}^t = 1$$


$$= 2(t-0.5)$$

At $t=0.5\text{ms}$, $V_o=-1$
At $t=1\text{ms}$, $V_o=0$

** The pattern will repeat.

N.B: $\int y dx = Y + c \rightarrow$ Integration constant
 c is the value of Y at the start of the incident

$y = mx$

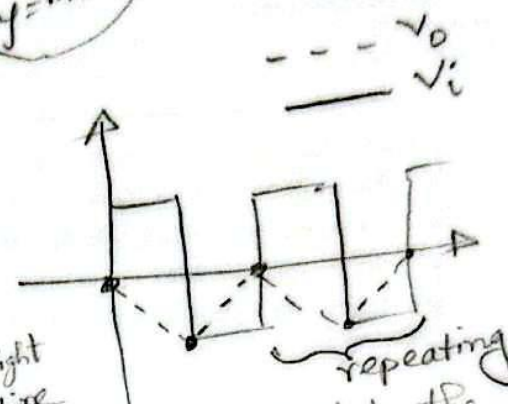

We calculate the corner values and join them through a straight line

$y = mx + c$

join them through a straight line

[20]

$$V_o = -\frac{1}{10 \times 0.1} \int V_i dt + V_{\text{initial}} \Rightarrow V_o = -\int V_i dt + V_{\text{initial}}$$


from 0 to 0.05 ms, $V_i = -4$

for any time in $0 \leq t \leq 0.05$,

$$V_o = -\int_0^t (-4) dt + V_{\text{initial}}$$

$$= 4 [t]_0^t = 4t$$

At $t=0$, $V_o=0$
At $t=0.05$, $V_o=0.2$

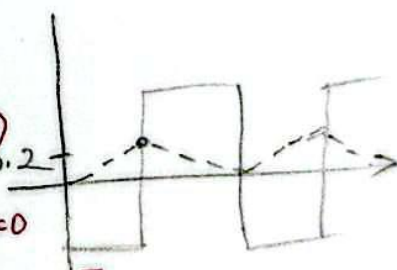

for any time in $0.05 \leq t \leq 0.1$ [$V_i = 4$]

$$V_o = -\int_{0.05}^t 4 dt + V_{\text{initial}}$$

$$= -4(t-0.05) + 0.2$$

At $t=0.05$, $V_o=0.2$
At $t=0.1$, $V_o=0$

22

$$\frac{V_x - (-3)}{3} = 3$$

$$\Rightarrow V_x = 6$$

$$I = \frac{V_i - V_x}{2} = \frac{V_x - V_o}{4}$$

$$\Rightarrow \frac{V_i - 6}{2} = \frac{6 - V_o}{4}$$

$$\Rightarrow 2V_i - 12 = 6 - V_o$$

$$\Rightarrow V_o = -2V_i + 18$$

KCL @ V_o , $I + i_o = I_1$



$$i_o = I_1 - I$$

$$= \frac{V_o}{2} - \frac{V_i - 6}{2}$$

$$= \frac{-2V_i + 18}{2} - \frac{V_i - 6}{2}$$

$$= -V_i + 9 - \frac{V_i}{2} + 3$$

$$= -\frac{3V_i}{2} + 12$$

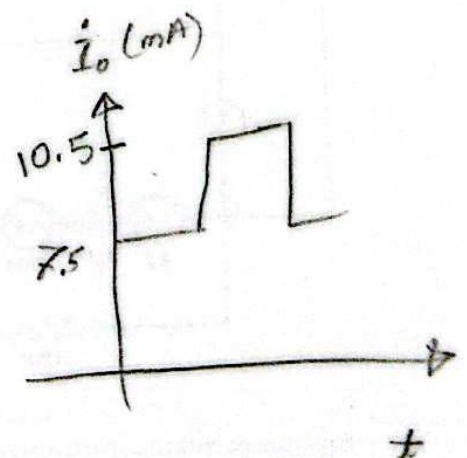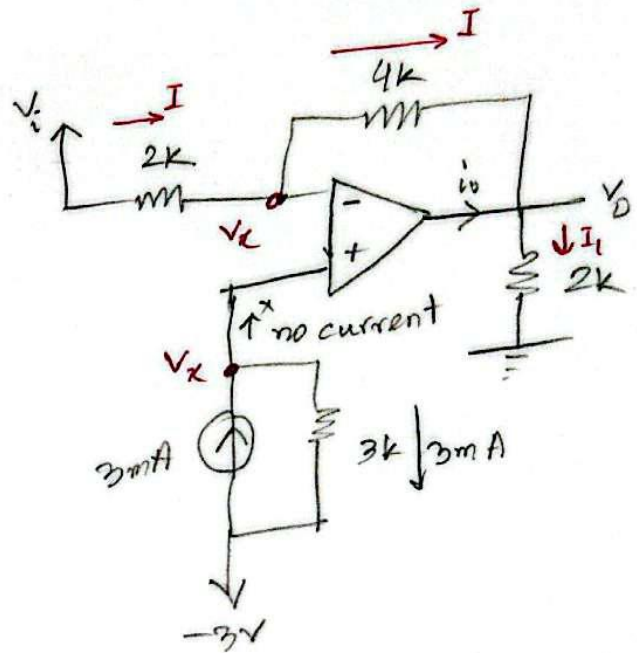

$V_i = 3, i_o = 7.5 \mid V_i = 1, i_o = 10.5$

23

The op amp is acting as an inverting summer

$$V_o = -10 \left(\frac{E_{ac}}{10} + \frac{-E_{dc}}{10} \right)$$

$$= -E_{ac} + E_{dc}$$



$$= -E_{ac} - 5$$

** If you think, V_o is inverted E_{ac} , then add -5

$$t=0, E_{ac} = -5, V_o = 0$$

$$t=1, E_{ac} = 5, V_o = -10$$

$$t=2, E_{ac} = -5, V_o = 0$$

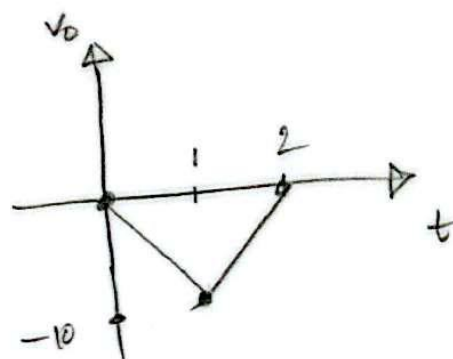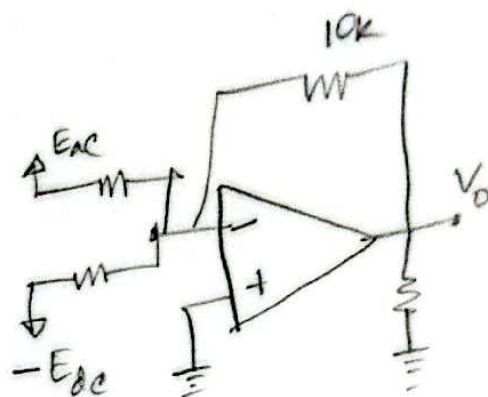


24

This is non-inverting op-amp.

$$V_o = \left(1 + \frac{R_f}{R_i} \right) V_i$$

$$= \left(1 + \frac{40}{10} \right) E_i$$


$$= 5 E_i$$

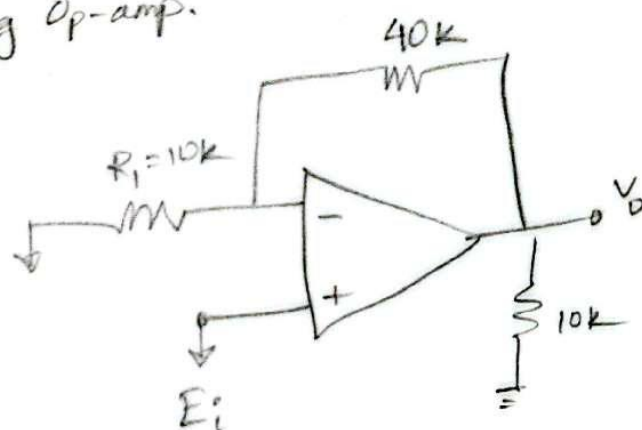

$$t=0 \rightarrow E_i = -2, V_o = -10$$

$$t=5 \rightarrow E_i = 2, V_o = +10$$

$$t=10 \rightarrow E_i = -2, V_o = -10$$

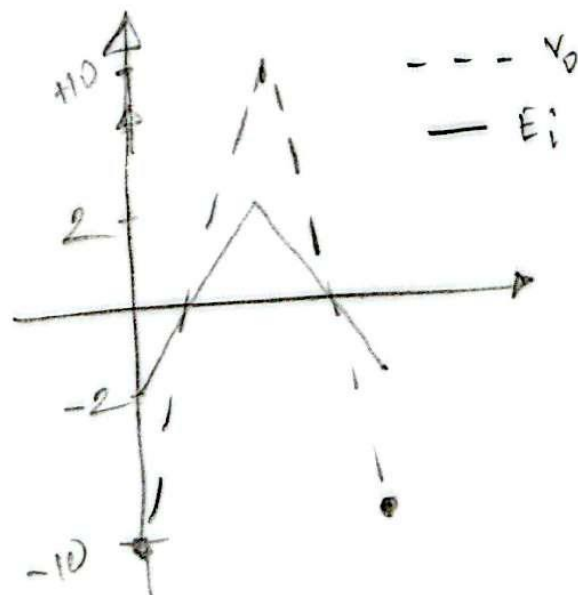

25

Gain = Slope
 (a) positive slope = positive gain
 \therefore non-inverting amplifiers

take two points $\rightarrow (1, 2), (4, 8)$


$$\text{slope} = \frac{8-2}{4-1} = 2$$

$$\text{Gain} = 1 + \frac{R_f}{R_1} = 2$$

$$\Rightarrow \frac{R_f}{R_1} = 1$$

$$R_f = R_1 = 1k\Omega$$

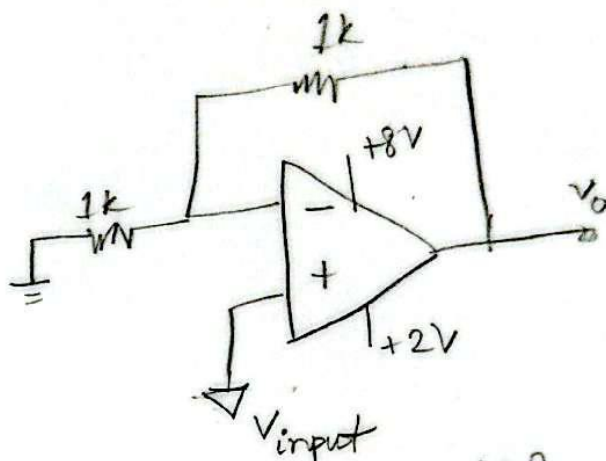
$$V_{\text{sat}}^+ = 8V, V_{\text{sat}}^- = 2V$$



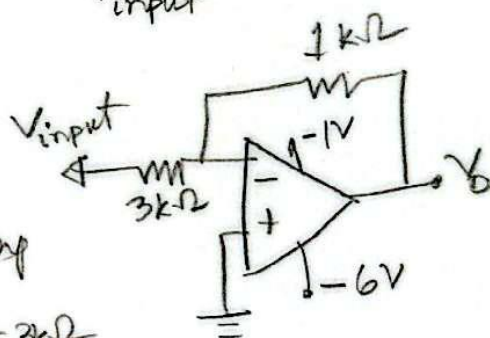(b) slope = $\frac{-6 - (-1)}{18 - 3} = \frac{-5}{15} = -\frac{1}{3}$

negative slope \rightarrow inverting op-amp

$$-\frac{R_f}{R_1} = -\frac{1}{3} \Rightarrow R_f = 1k\Omega, R_1 = 3k\Omega$$




26

$$\text{slope} = \frac{5 - (-2)}{6 - (-2.4)} = \frac{7}{8.4} = \frac{5}{6}$$

slope positive \rightarrow non-inverting
 but gain < 1 . formula: $\left(1 + \frac{R_2}{R_1}\right)$

So, we need voltage division as
 we have to use only one op-amp.
 Let's say, we will halve the input
 then amplify $\left(2 \times \frac{5}{6}\right) = \frac{5}{3}$
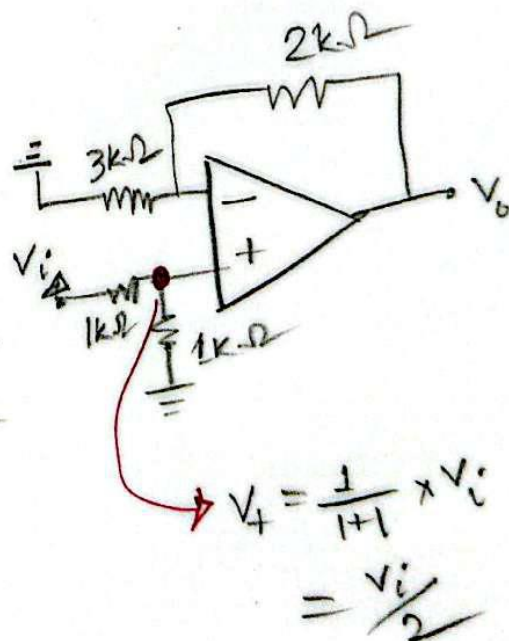
$$\left(1 + \frac{R_2}{R_1}\right) = \frac{5}{3} \Rightarrow \frac{R_2}{R_1} = \frac{2}{3}$$



$$V_4 = \frac{1}{1+1} \times V_i = \frac{V_i}{2}$$