

Lecture X


Sub.: _____

Rough

| | | | | | | |
|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|
| SAT | SUN | MON | TUE | WED | THU | FRI |
| <input type="checkbox"/> |

DATE: / /

Example: [from lecture 6]

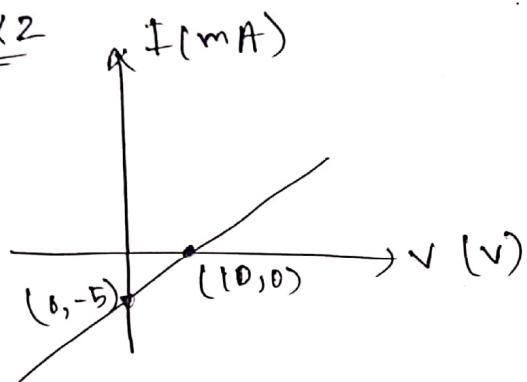
Ex 2

① model = ?


② parameters = ?

60%

① model:

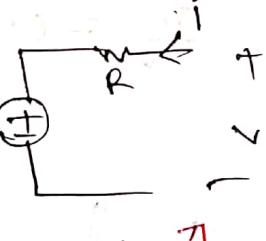

model 1

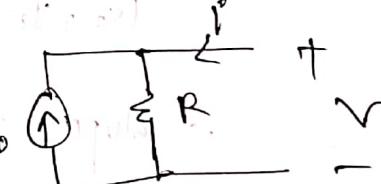

② parameters V_0 , R on i_0 , R

For solving we need equation like $y = mx + c$

$$\text{slope} = \frac{y_2 - y_1}{x_2 - x_1}$$

where (x_1, y_1) and (x_2, y_2)

if voltage source with resistor $V_0 = x \text{ intercept}$ ($y=0$)


if dependent source with resistor $R = \frac{1}{m}$

$i_0 = y \text{ intercept}$

Sub.: _____

| | | | | | | |
|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|
| SAT | SUN | MON | TUE | WED | THU | FRI |
| <input type="checkbox"/> |

DATE: / /

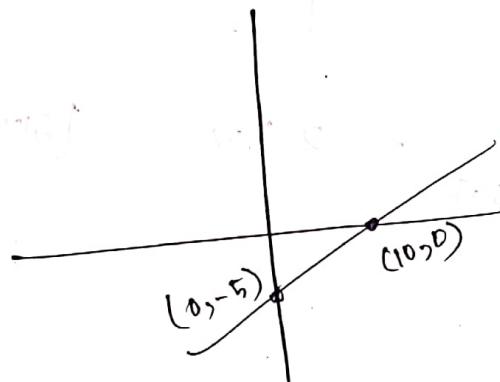Solve

$$\therefore (x_1, y_1) \equiv (0, -5)$$

$$(x_2, y_2) \equiv (10, 0)$$

$$\therefore \text{slope} = \frac{y_2 - y_1}{x_2 - x_1} = \frac{0 - (-5)}{10 - 0} = \frac{5}{10} = 0.5$$

$$\therefore y = mx + c$$

$$= 0.5x + c$$

$$\text{Now pass from the point } (x_2, y_2) = (10, 0)$$

$$y = mx + c$$

$$0 = m \times 10 + c$$

$$\Rightarrow 0 = 0.5 \times 10 + c$$

$$\therefore c = -5$$

\therefore equation will be


$$\boxed{y = 0.5x - 5}$$

Sub.: _____

SAT SUN MON TUE WED THU FRI

DATE: / /

Now let's the model is

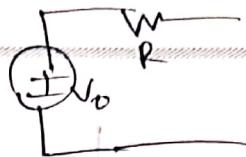

$$\therefore R = \frac{1}{m} = \frac{1}{0.5} = 2 \text{ k}\Omega \quad (\text{since } I \text{ is in mA})$$


For V_0 , $y = 0$

$$\therefore 0 = 0.5x - 5$$

$$\Rightarrow 0.5x = 5$$

$$\therefore x = 10$$

$$\therefore V_0 = x = 10$$

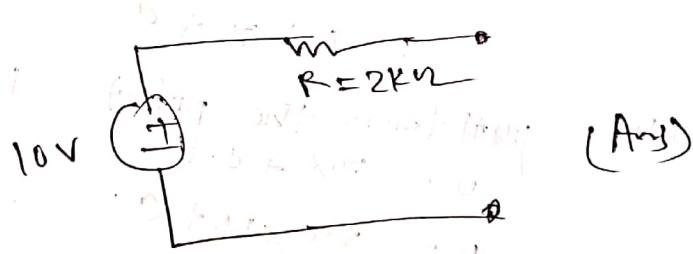

Sub.: _____

| | | | | | | |
|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|
| SAT | SUN | MON | TUE | WED | THU | FRI |
| <input type="checkbox"/> |

DATE: / /

So lets the model is like



$$V = \frac{F}{R} = \frac{1}{m} = 2 \text{ kN}$$

Initial force is zero at the top of the spring

For F_0 , $x = 0$


$$\therefore y = -0.5 \times 0^{-5}$$

At $x = 0$, which is initial position of the spring

$$\Rightarrow y = -5$$

$$\therefore I_0 = y = -5$$

model:

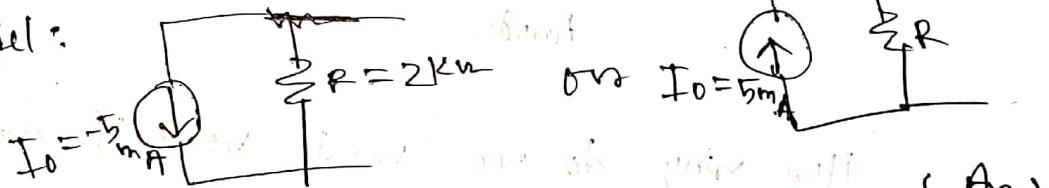

Explain the circuit with respect to the given circuit (Ans)

The initial condition is present in the model.

Initial force is zero at the top of the spring

Initial displacement

Initial current in the loop

Initial voltage across the loop

Initial current in the left vertical branch is zero

Initial force is zero at the top of the spring

Initial displacement is zero

Sub.: _____

| | | | | | | |
|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|
| SAT | SUN | MON | TUE | WED | THU | FRI |
| <input type="checkbox"/> |


Actual lec X

DATE: / /

IV characteristic of non linear device:

Non-linear device: Those devices, whose IV curve can't be possible to represent with straight line.

(a) Generic Non-linear device symbol

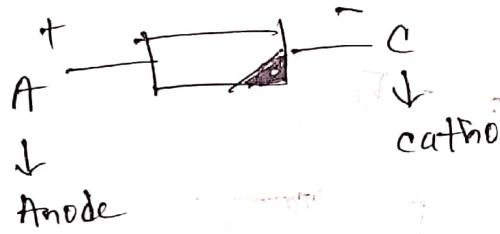

Now why do we need non-linear device.

① Because linear devices have limited application. (can only perform linear operation like $ax+by=0$ but not possible

$$x^2 + b \ln x + c$$

ex, sin x , etc

② we need non-linear device for logic gate. For example

0 → 1 (5V)

5V → out

multiple segment IN not linear


Sub.: _____

(*) Technically, pure non-linear device is not possible.

| | | | | | | |
|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|
| SAT | SUN | MON | TUE | WED | THU | FRI |
| <input type="checkbox"/> |


DATE: / /

② Linear device have no control.

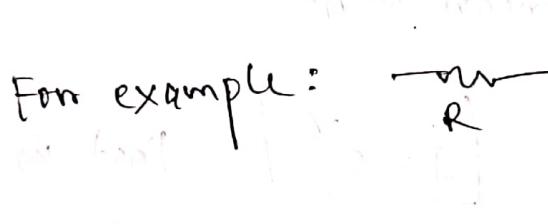For example:  No current direction if not specified manually.


But previously we talked about valve that is not a linear device (Have 3 terminal) and we can control the flow of current.

Non linear device we see in this course:

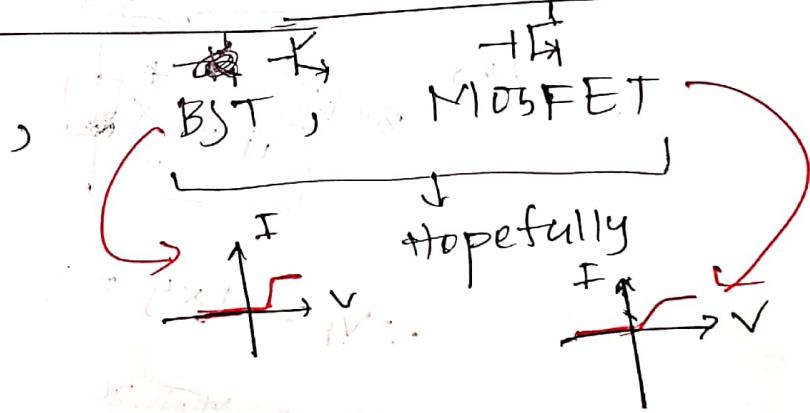


But there are

Down sides of Non-linear device

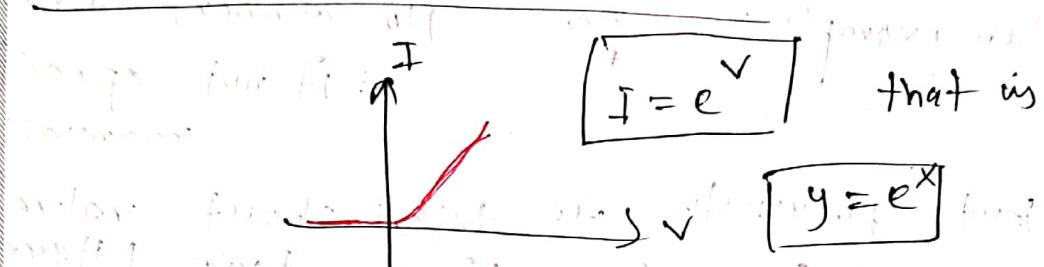


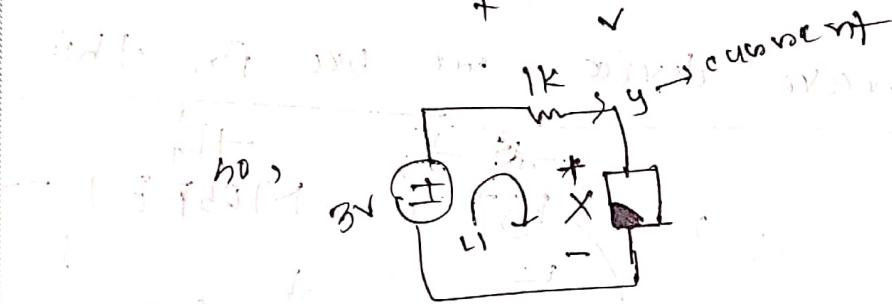Suppose the device associated with this graph is



$$\therefore V_R = 1 \times y = y$$

~~graph~~

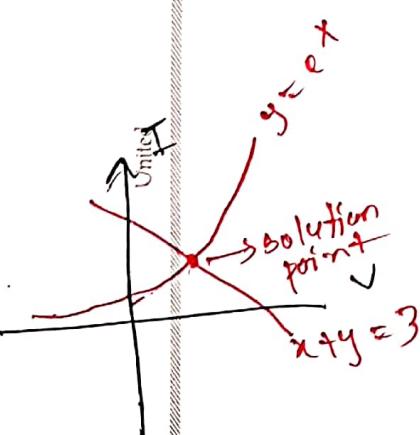

$$\begin{aligned} \text{By KVL} \\ 3 &= 1 \times y + x \\ \therefore x + y &= 3 \\ \text{again } y &= e^x \end{aligned}$$


But it's very hard to solve
(have to use numerical technique or graphical solution)

but doesn't get actual result

therefore biggest disadvantage is that there's no actual solution (or close form solution), OR can say, can't solve easily. (numerical methods)

But solution is we can solve it this type of non-linear I.V. using piecewise linear approximation.

piece wise linear approximation:

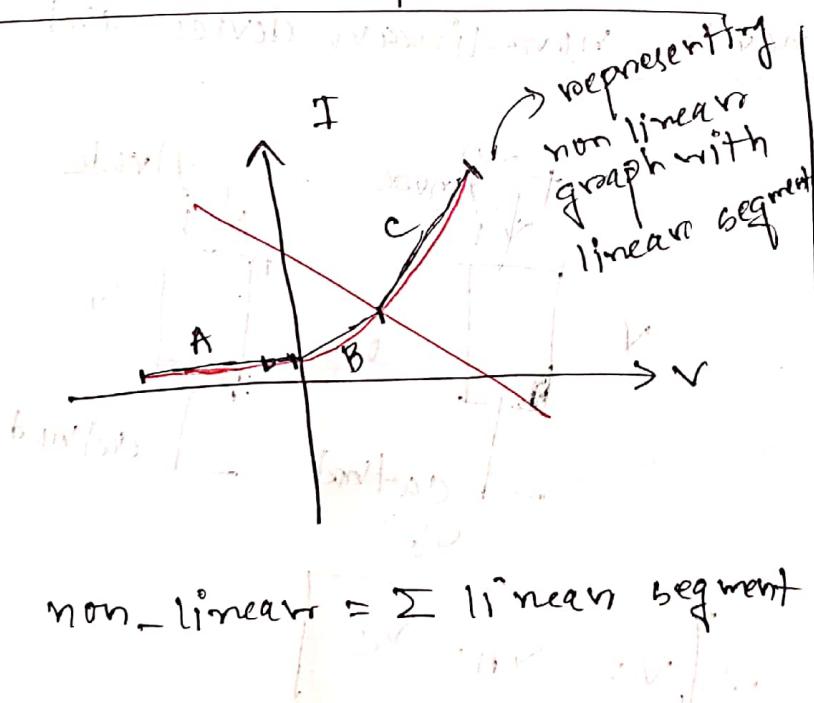

Main idea is, if we have any non-linear graph, we divide it small pieces so that each piece works like straight line.

advantage is now equation become linear. ~~we~~ can easily solve it. But there will be some error.

Sub.: _____

| | | | | | | |
|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|
| SAT | SUN | MON | TUE | WED | THU | FRI |
| <input type="checkbox"/> |


DATE: / /

But another problem is in this piecewise linear approximation that in which segment our device (non-linear) works.

↳ solution: method of assumed state.


So if there's in question non-linear then we assumed it piece-wise linear approximation.

Generic, non-linear device and its model

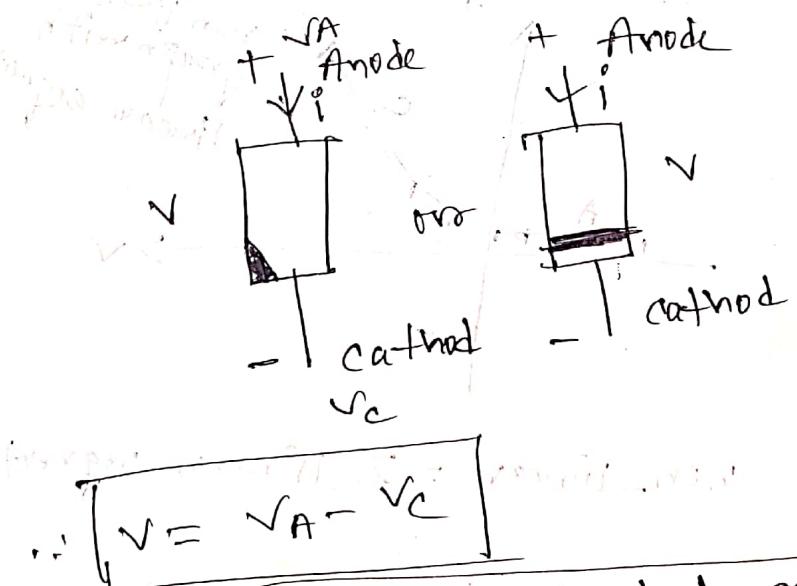

$V = V_A - V_C$

i from anode to cathode

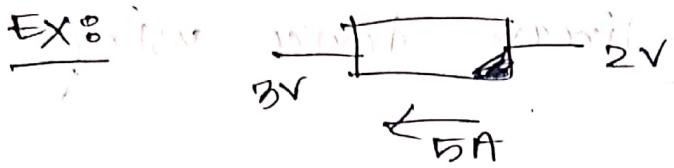Ex:

Ans:

$$\sqrt{A} = ?$$

$$\sqrt{C} = ?$$

$$\sqrt{V} = ?$$

$$I = ?$$

~~$$\sqrt{A} = 3V$$~~

~~$$\sqrt{C} = 2V$$~~


~~$$\sqrt{V} = \sqrt{A} - \sqrt{C}$$~~

~~$$= 3 - 2 = 1V$$~~


~~$$I = -5A$$~~

Q) Diodes operate with the following circuit

Suppose the IV curve of this device,

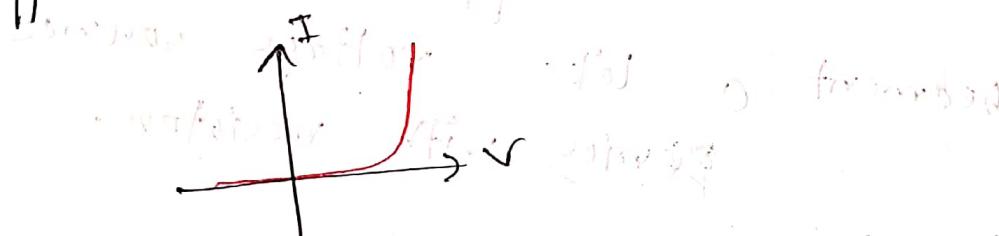

Now according to piecewise approx.

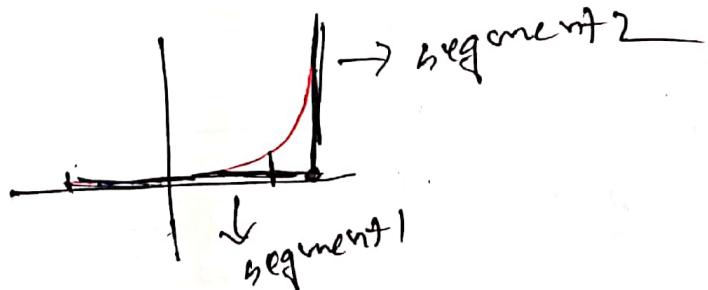


Now question how can we model it using linear device.

Sub.: _____

SAT SUN MON TUE WED THU FRI
□ □ □ □ □ □ □

DATE: / /

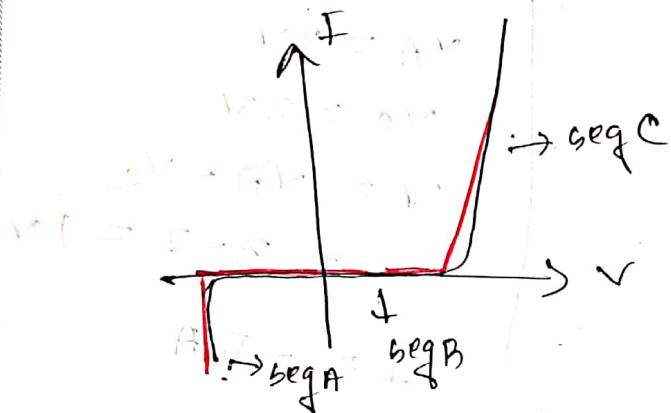modeling non-linear device using linear device:



Hence segment A like voltage source V

segment B like open circuit or $R = \infty$

segment C like voltage source
series with resistor.

the behavior of resistor in





modeling of non-linear device using linear device with help of resistor

Sub: Electronics

SAT SUN MON TUE WED THU FRI

DATE: / /

Ex:

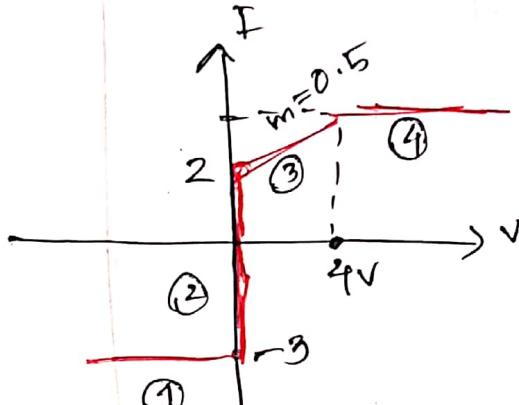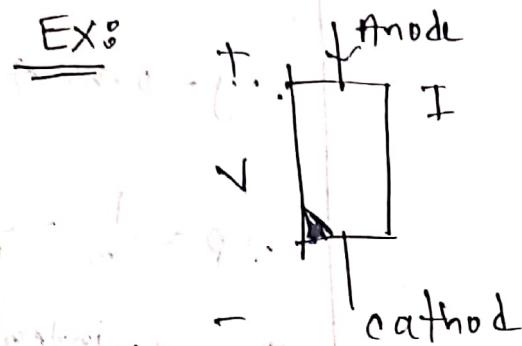

(Q1) Find pwl modeling of the device above?

Soln: Have to find condition, model & parameters

Condition

segment condition

$$\text{segment } (1) \quad V \leq 0$$

model


current source

$$I = I_0$$

parameters

$$I_0 = 3 \text{ mA}$$
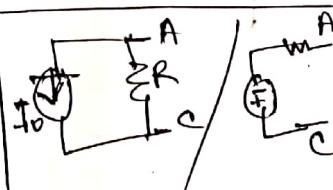
$$\text{segment } (2) \quad -3 \leq I \leq 2 \text{ mA}$$



$$\text{segment } (3) \quad 0 \leq V \leq 4 \text{ V}$$

$$y = mx + c$$

$$m = 0.5$$

$$\therefore y = 0.5x + c$$

(0, 2) point on y axis

$$\Rightarrow 2 = 0.5 \times 0 + c$$

$$\Rightarrow c = 2$$

include less than $[a < v \leq b]$
in condition

Sub.: _____

SAT SUN MON TUE WED THU FRI
Better

DATE: / /



$$\therefore y = 0.5x + 2$$


$$\therefore R = \frac{1}{m} = \frac{1}{0.5} = 2 \text{ k}\Omega$$

$I_0 = y - \text{intercept}$

$$\therefore I_0 = c = 2 \text{ mA}$$

segment ④

$$V > 4 \text{ V}$$

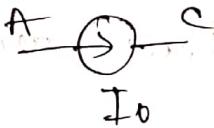

From segment ③

$$y = 0.5x + 2$$

$$\text{now } x = 4$$

$$\therefore y = 0.5 \times 4 + 2 \\ = 4$$


$$\therefore I_0 = y = 4 \text{ mA}$$

United

Sub.: _____

| | | | | | | |
|--------------------------|--------------------------|--------------------------|--------------------------|-------------------------------------|--------------------------|--------------------------|
| SAT | SUN | MON | TUE | WED | THU | FRI |
| <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> | <input checked="" type="checkbox"/> | <input type="checkbox"/> | <input type="checkbox"/> |

DATE: 1/2/

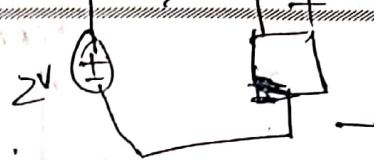Now Question:Q2# Find I when $V = 2\text{V}$?

so have to go to match with the condition.

so if matches with segment (3) condition.
so from segment (3) no device operate at segment (1)


$$y = 0.5x + 2$$

$$\therefore I = 0.5V + 2$$


$$\Rightarrow I = 0.5 \times 2 + 2 \\ = 3 \text{ mA} \quad (\text{Answer})$$

Q3 Find V when $I = 1\text{mA}$?

Soln: will operate in segment (2).

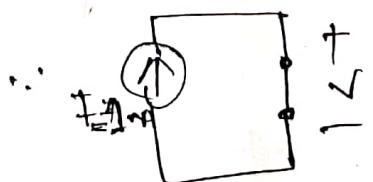

$$V = 0V$$

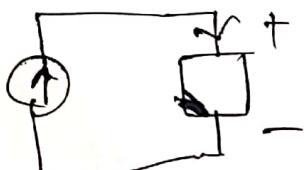


Sub.: _____



Goal: AC \rightarrow DC converter circuit

SAT SUN MON TUE WED THU FRI

DATE: / /

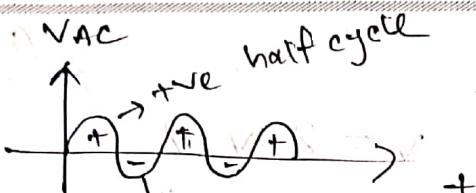

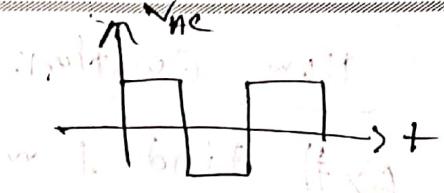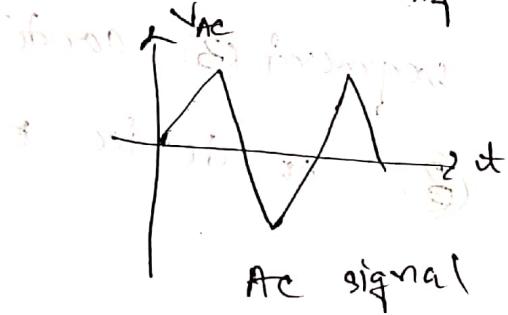Left off from performance of op amp with diff. amplifiers




Ac signal



Ac signal

affine combination of
positive and negative half cycles

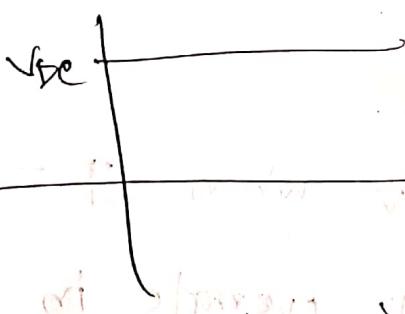affine combination of
positive and negative half cycles



DC signal after

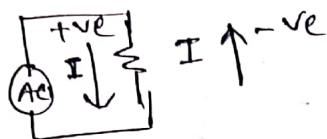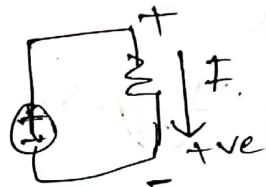For ACBut for DC

~~As we have AC supply in our electricity line because we can reduce transmission loss or power loss using AC [$P = VI$] via increasing or decreasing voltage using transformer (step up or step down)].~~


$$I = \frac{P}{V} \rightarrow \text{constant}$$

Historical perspective


But AC supply has more power loss than DC and noise.

So now a days in China they use DC transmission for long transmission line.


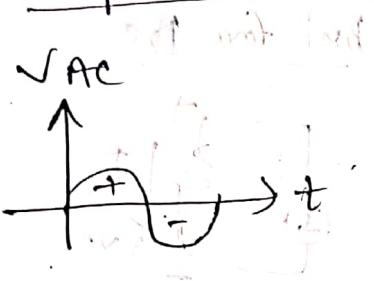
Step of conversion technique of from AC to DC



rectification

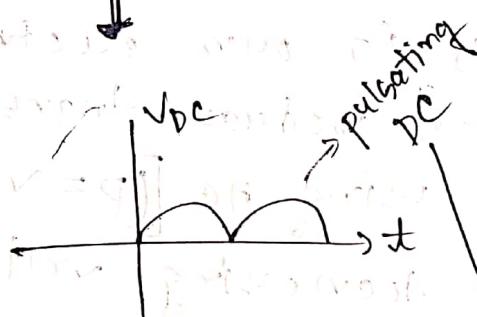


Filtering

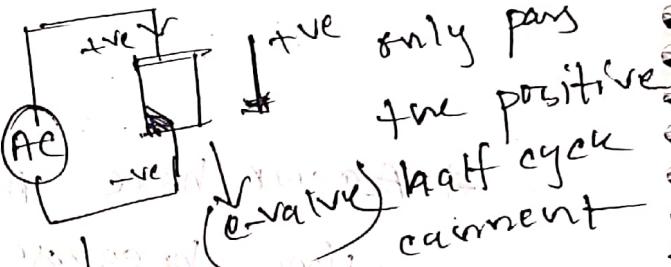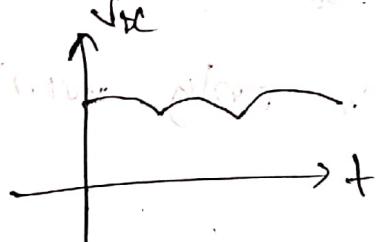

How we develop it.

pulsating voltage means it's not constant its values it changes over time

regulation

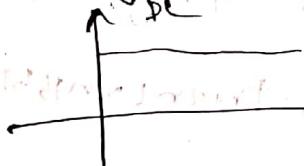


Sub.: _____

SAT SUN MON TUE WED THU FRI


DATE: / /

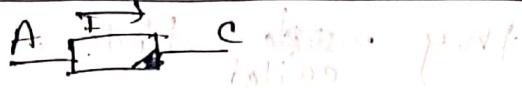what should be the IV of an ideal e-valve.



If $I > 0$, allow current (no resistance)


It should behave like
short circuit

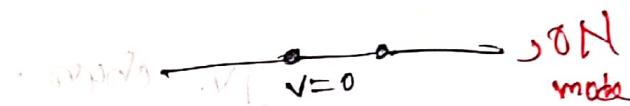

If $I \leq 0$, doesn't allow current

It should behave like
Infinite resistance,

should behave like
open circuit

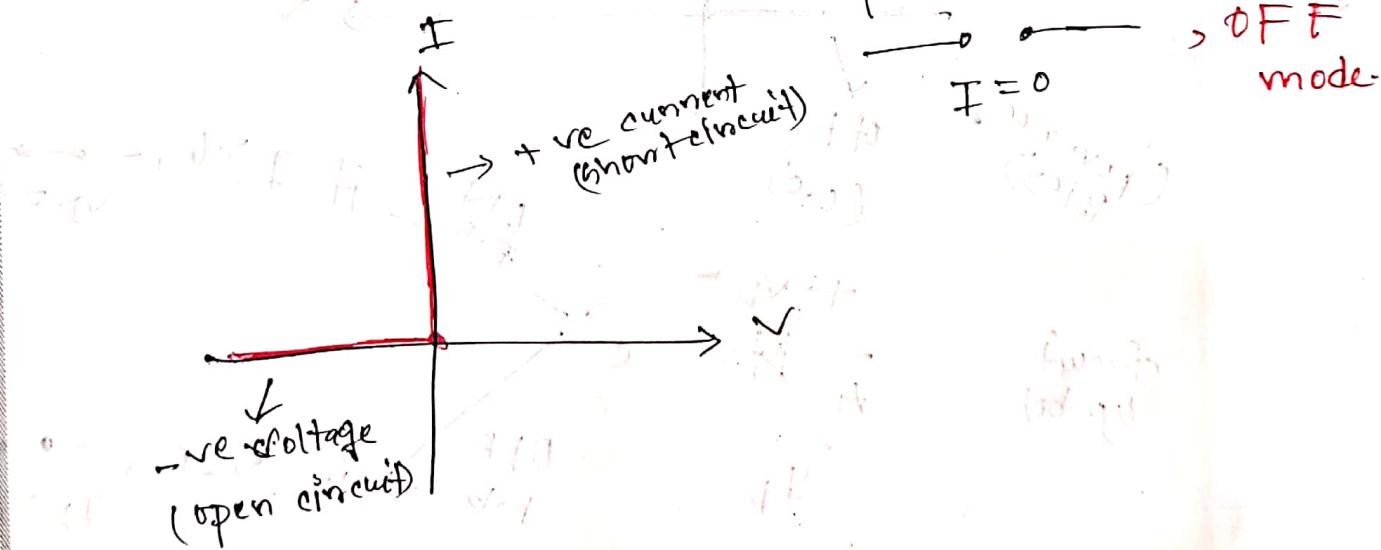

• In short form of off-shunt circuit

Sub.: _____

| | | | | | | |
|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|
| SAT | SUN | MON | TUE | WED | THU | FRI |
| <input type="checkbox"/> |

DATE: / /


And this value (after many refinements)
they ~~were~~ called diode.

(Comparison) forward voltage, $V_{F.C}$ & I_F



#Diode (Ideal)

IV-chars.

forward voltage graph. V_D vs I_D

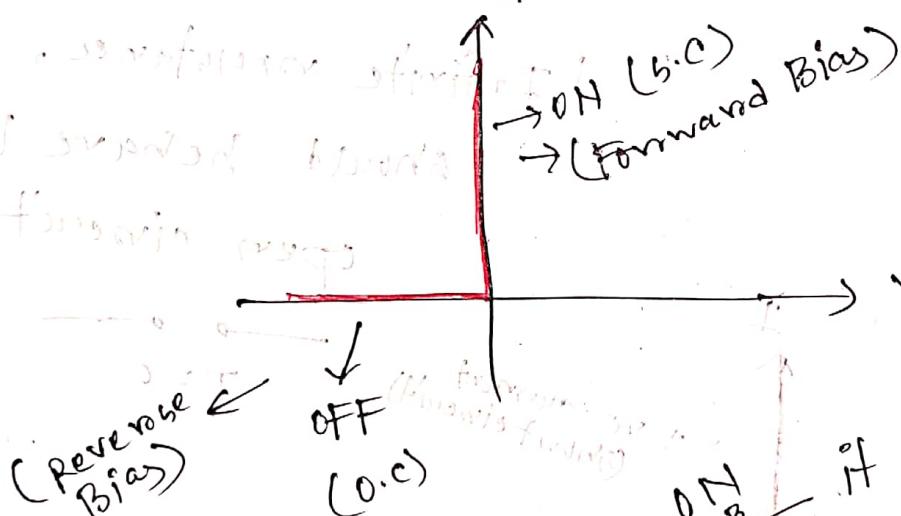


circuit
symbol

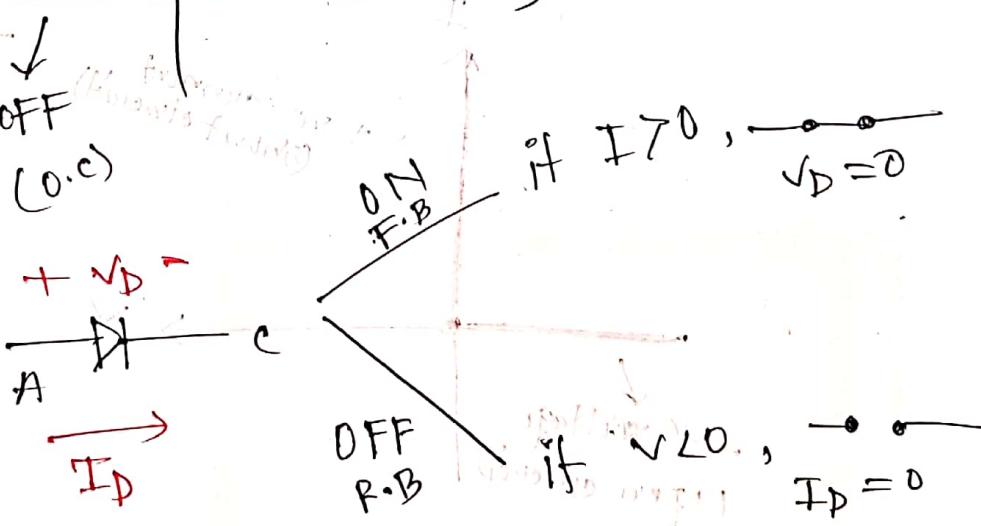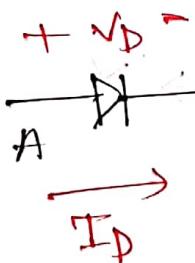

$$V_D = V_A - V_C$$

I_D = from Anode A to cathode C,

Real diode: (making) briefly:

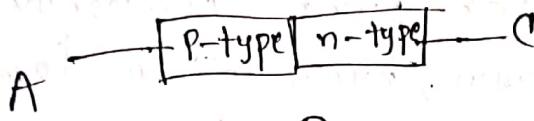

P-type semiconductor:

⇒ carriers: Holes (absence of electron)

⇒ Difference with pure semiconductors: It has empty electron spaces (called holes) in certain bonds with neighbouring atoms.

⇒ Electrons from neighbouring bonds try to fill up the empty spaces by creating a flow of electrons hence increasing the conductivity.

~~next~~

Sub.: _____

SAT SUN MON TUE WED THU FRI


DATE: / /

n type semiconductor: (positive) charge sign

carriers: electron

Difference with pure semiconductors: it has more free electrons, even after forming bonds with the neighbouring atoms.


Free electron increase conductivity.

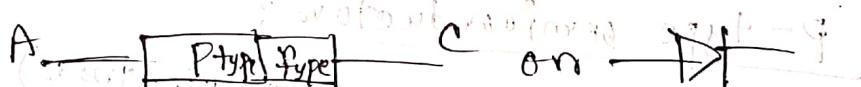

(A) If AC is applied across the junction between p-type and n-type semiconductors, it forms a diode.

current flows only in one direction.

current flows only in one direction.

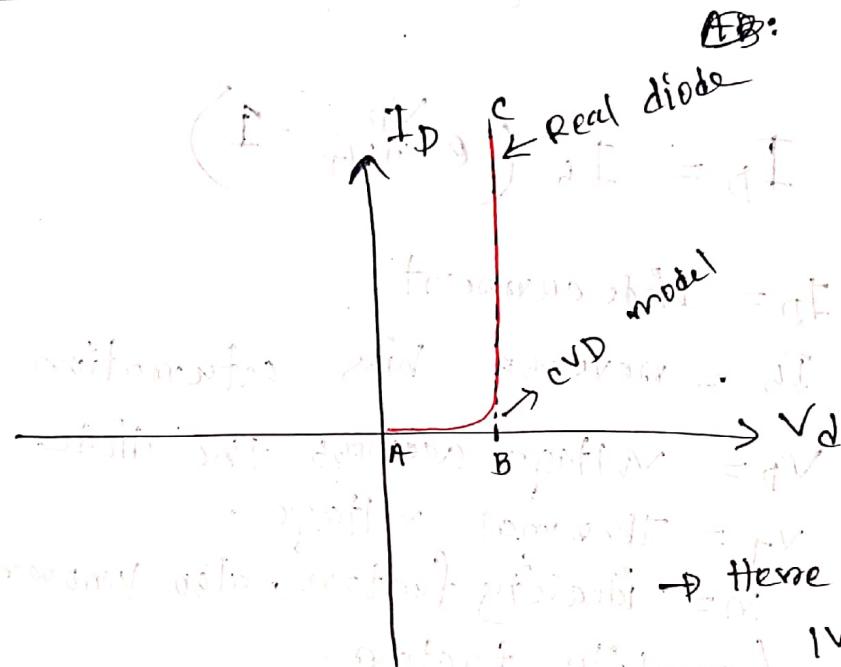Real Diode IVCondition

i. $V_d > V_{\text{threshold}}$.

→ The diode will be ON

→ It will act as constant voltage source.

ii. $V_d < V_{\text{threshold}}$

→ The diode will be OFF

→ It will act as a open circuit.

Shockley Diode equation or diode equation

$$I_D = I_S \left(e^{\frac{V_D}{nV_T}} - 1 \right)$$

I_D = Diode current

I_S = reverse bias saturation current

V_D = voltage across the diode

V_T = thermal voltage

n = ideality factor, also known as the quality factor.

$$n = 1$$

diffusion

- breakdown voltage $\approx 3V$
- junction depletion region width $\propto V^{1/2}$
- junction capacitance $\propto V^{-1/2}$

diffusion voltage $\approx 0.7V$


- forward bias voltage $\approx 0.7V$
- forward current $\propto e^{q(V - 0.7)/kT}$

Sub.: _____

| | | | | | | |
|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|
| SAT | SUN | MON | TUE | WED | THU | FRI |
| <input type="checkbox"/> |

DATE: / /

Ex.

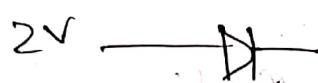

$$V_A = ?$$

$$V_C = ?$$

$$V_D = ?$$

$$I_D = ?$$

$$3V$$

Ans:

$$V_A = 2V$$

$$V_C = 3V$$

$$\therefore V_D = V_A - V_D$$

$$= 2 - 3 = -1V$$

$I_D = 0$ [since here
 V_D is less than 0]

so it behaves like
 open circuit.]

[So diode is OFF]

Ex:

$$I_D = ?$$

$$V_A = ?$$

$$V_D = ?$$

$$V_C = ?$$

Ans:

$$I_D = 2 \text{ mA}$$

$$V_A = 3V$$

$$V_D = 0$$

$$V_C = 3V$$

[Diode ON]



[can replace
the diode
with
short circuit]

Diode works in 2 modes

1. When it is off

2. When it is on

Let's discuss about 2nd mode

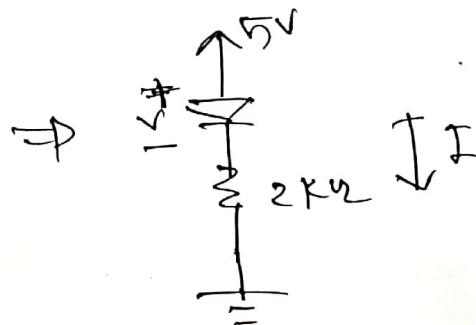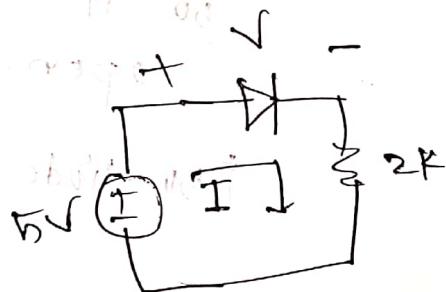Ex

Points: If we have circuit like this having non-linear device, first we have to find in which mode it is operating. For example: for diode ON or OFF mode.] For this we have to find the direction of current.

Sub.: _____

SAT SUN MON TUE WED THU FRI

DATE: / /

For this circuit

current will flow : \downarrow (From 5V to GND)

∴ Diode will be ON. (to behave like short circuit)
so circuit will be forming loop



$$\therefore V = 0$$

$$I = \frac{5 - 0}{2k\Omega} = 2.5 \text{ mA}$$


Sub.: _____

SAT SUN MON TUE WED THU FRI

DATE: / /

- current always want to flow from higher potential to lower potential.

Ex:

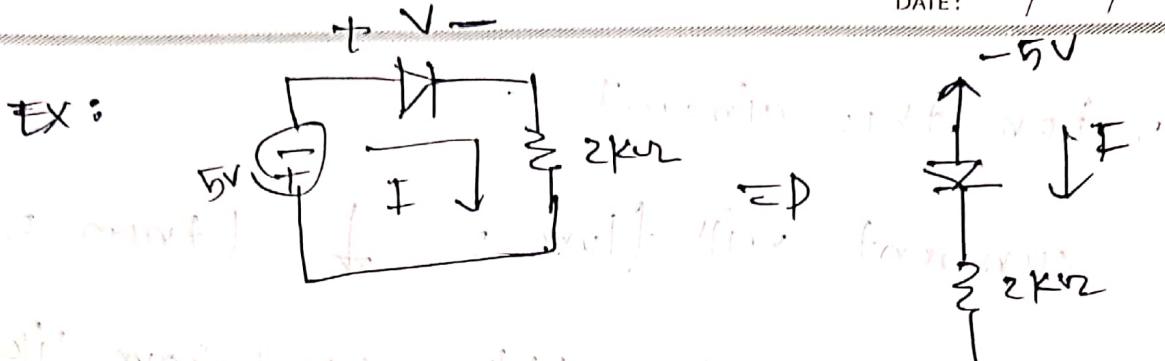


Now current want to flow from

or to $-5V$

so diode = OFF

Behave like open circuit.

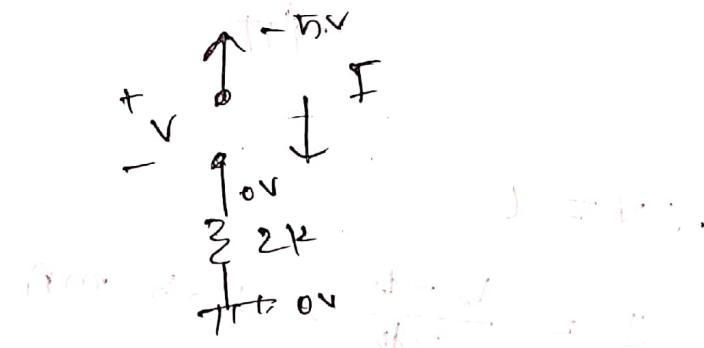


$$\therefore I = 0$$


$$V = -5 - 0$$

$$= -5 V$$

Ex

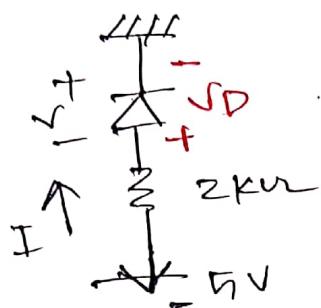

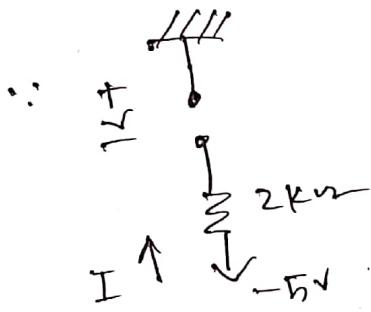
\therefore Current wants to flow from $12V$ to $-5V$
so Diode will ^{not} allow it so Diode = OFF



$$\begin{aligned}\therefore I &= 0 \text{ mA} \\ V &= 0 - (-5) \\ &= 5V\end{aligned}$$



But if you ask to know
the voltage of Diode
then it will be

$$\boxed{\begin{aligned}V_D &= -5 - 0 \\ &= -5V\end{aligned}}$$

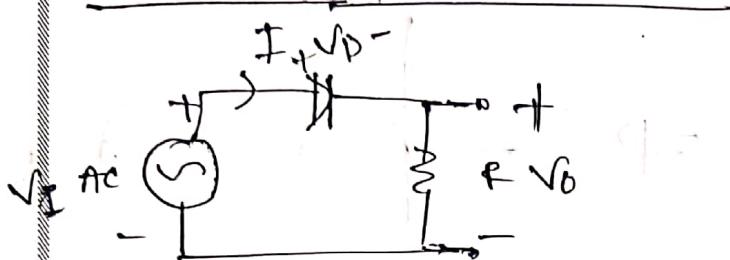Rectification: (Half wave)

$$V_d = \sqrt{I} - V_0$$

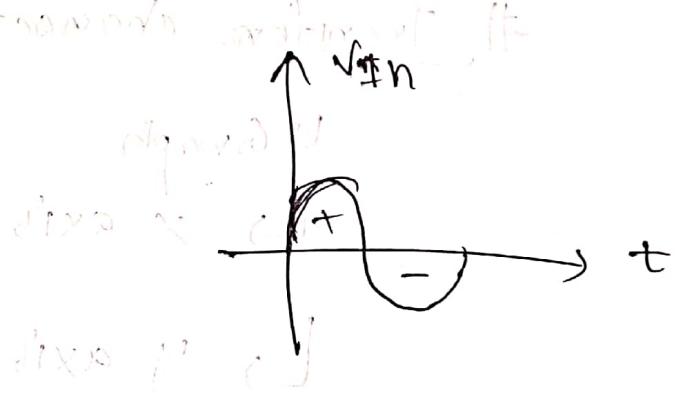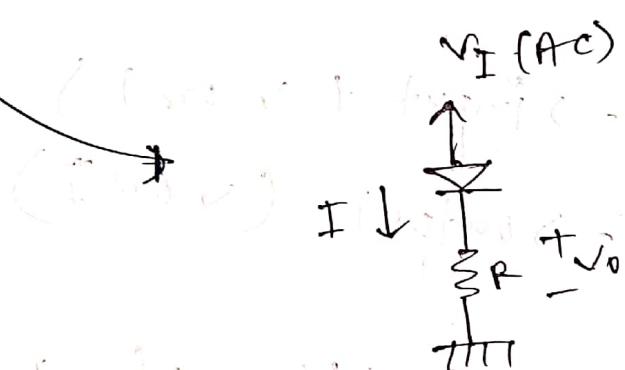
when positive cycle, current will flow through the diode.



+ve half cycle

ON [conducting]

\Rightarrow short circuit

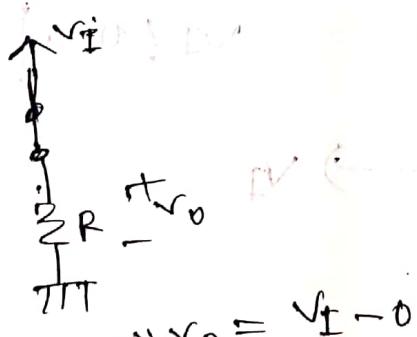

$$\therefore V_0 = \sqrt{I} - 0$$


$$\therefore V_0 = \sqrt{I}$$

$$I = \frac{V_0}{R} = \frac{\sqrt{I}}{R}$$

-ve half cycle

OFF (not conducting)

\Rightarrow open circuit

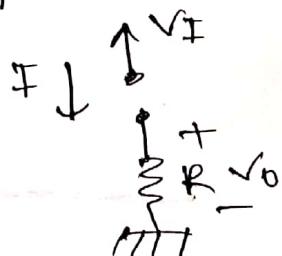


$$V_0 = 0$$


$$I = 0$$

so we get

$$\sqrt{V_{DC}}$$

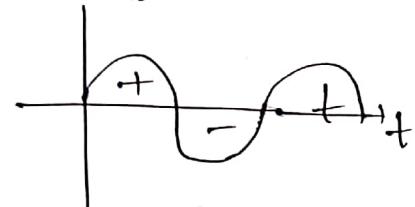

Full Wave rectifier

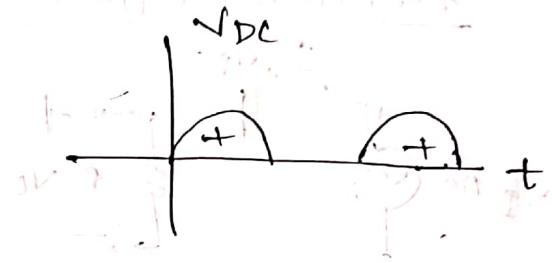

Half Wave rectifier mapping

Transfer characteristic

Graph


\hookrightarrow x axis \rightarrow input (v or I)

\hookrightarrow y axis \rightarrow output (v or I)

Voltage transfer characteristic of a

half-wave rectifiers.

United

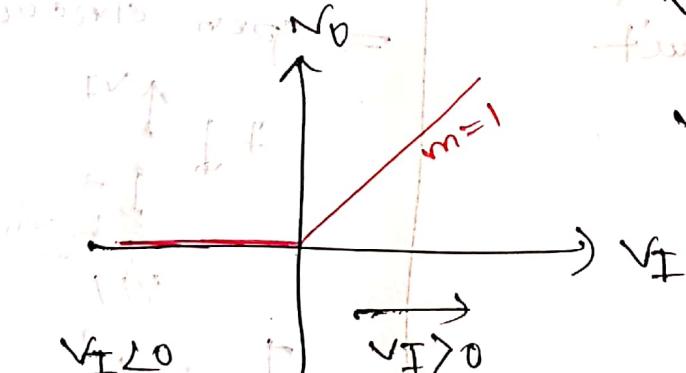


$$v_I > 0 \Rightarrow v_O = v_I \quad \therefore y = x$$

$$v_I \leq 0 \Rightarrow v_O = 0 \quad \therefore y = 0$$

Sub.: _____


SAT SUN MON TUE WED THU FRI

DATE:

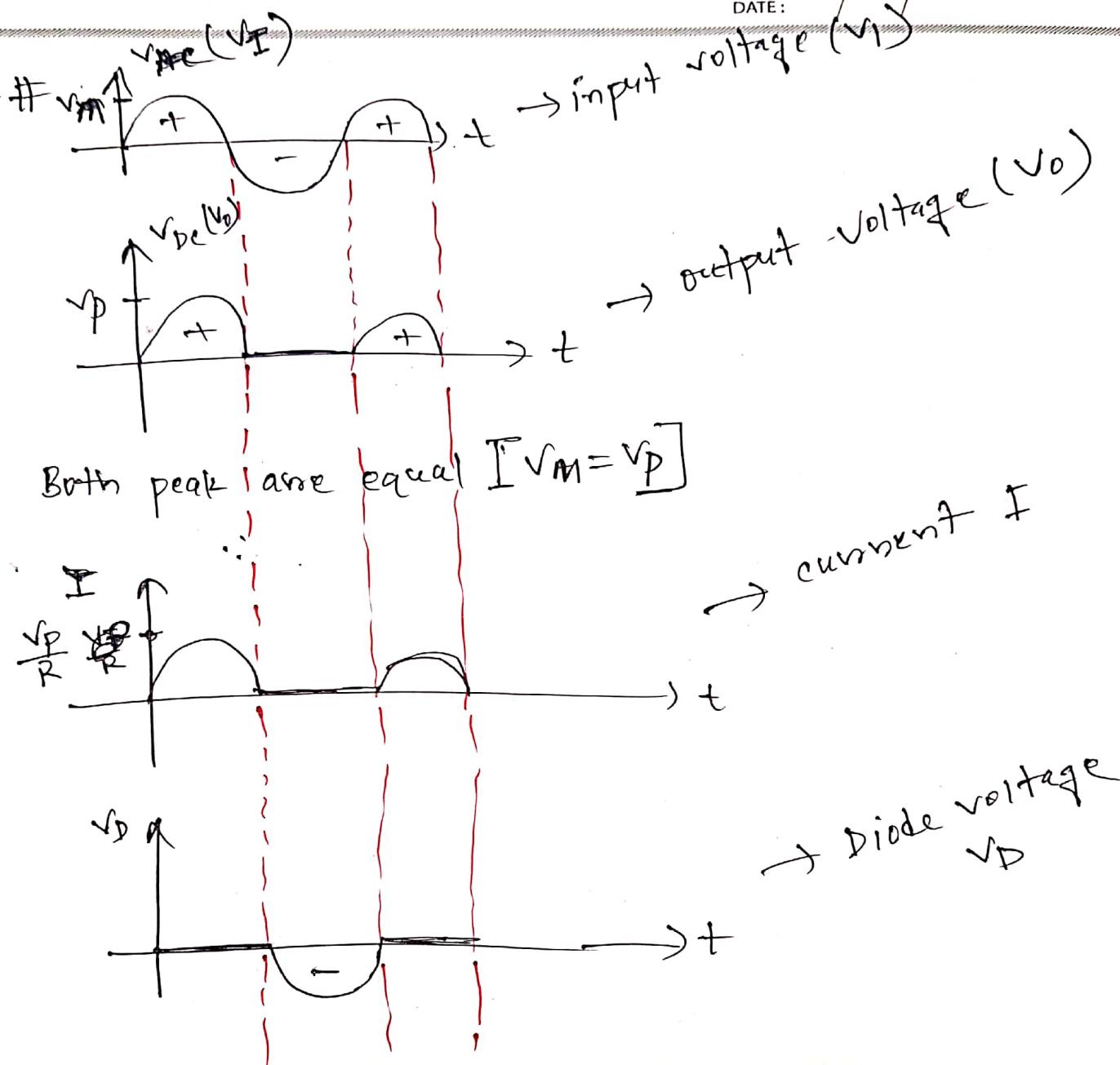

Diode logic gates

IDEAL Diode (Review)

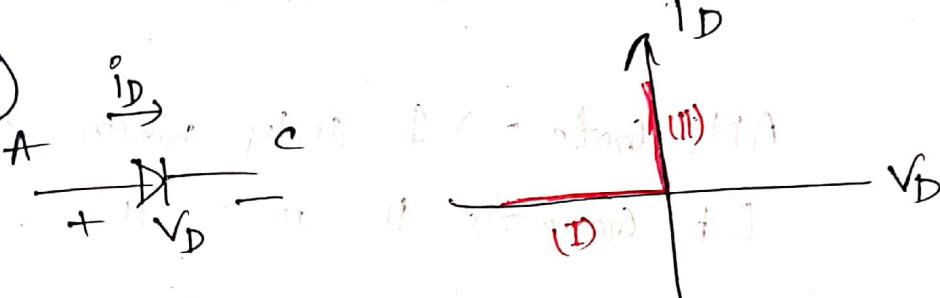

$$V_D = V_A - V_C$$

\vec{F}_D = from A to C with west first
length of 10 cm and angle 30°

(P. 603) (4) (1943) ~~and~~ ^{not} with ~~forward~~ ^{forward} Bicy

If $V_D \Rightarrow +ve \rightarrow$ Forward Bias.

$V_D \Rightarrow -V_e \rightarrow$ reverse bias.

Region I: $V_{DL0} \rightarrow$ OFF mode / Reverse Bias \rightarrow DC $\rightarrow i_D = 0$

Region II: ~~VS~~

~~$I_D > 0$~~ $I_D > 0 \rightarrow$ OH mode / Forward Bias \rightarrow 
 state equation.

Sub.: _____

SAT SUN MON TUE WED THU FRI

DATE: / /

Logic levels: $0 \rightarrow \text{False}$
 $1 \rightarrow \text{True}$

AND Gate $\rightarrow 1$ only when all inputs = 1

OR Gate $\rightarrow 0 \quad 1 \quad 1 \quad 1 \quad 1 \quad 1 \quad 1 = 1$

(*) But for this course we will use voltage values to define logic level (0 or 1)

0 $\rightarrow -5V$

1 $\rightarrow +5V$

or

0 $\rightarrow 0V$
1 $\rightarrow 5V$

or

0 $\rightarrow +12V$
1 $\rightarrow -12V$

we will use
this type
of convention.

OR operation

| x_1 | x_2 | y |
|-------|-------|-----|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

$$y = x_1 \text{ or } x_2$$

Logical

Truth table of OR operation.

converting it into voltage value

| $\sqrt{x_1}$ | $\sqrt{x_2}$ | \sqrt{y} |
|--------------|--------------|------------|
| 0V | 0V | 0V |
| 5V | 5V | 5V |
| 5V | 0V | 5V |
| 5V | 5V | 5V |


Voltage truth table

Sub.: _____

SAT SUN MON TUE WED THU FRI
□ □ □ □ □ □ □

DATE: / /

Circuit of logical OR using Diode:

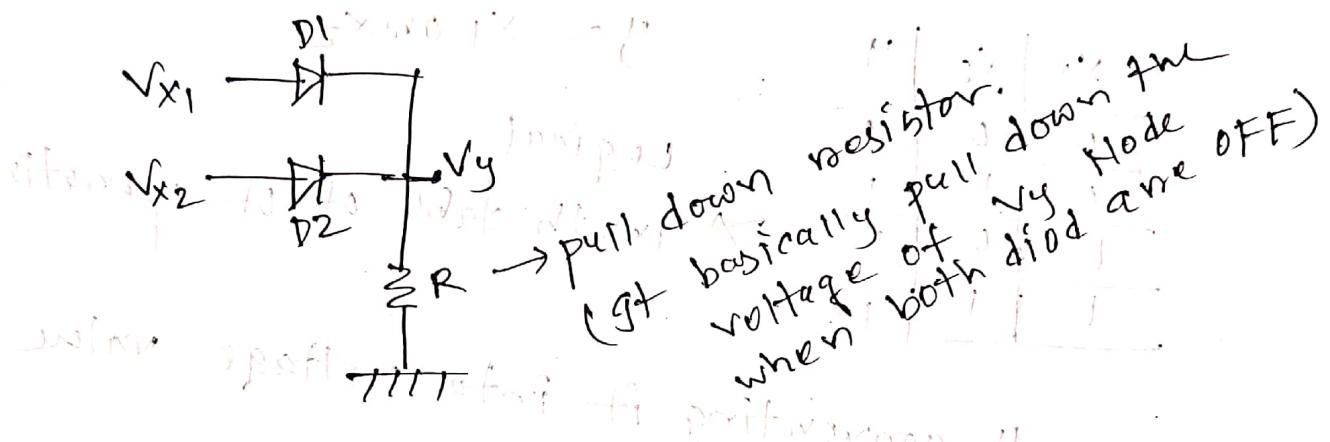


Hence V_{x_1} , V_{x_2} and V_y all are node voltages (terminal voltages (voltage respect to ground))

Proof of voltage truth table

Case 1

| V_{x_1} | V_{x_2} | V_y |
|-----------|-----------|-------|
| High | Low | High |
| Low | High | High |
| High | High | Low |

case 4: $\boxed{V_{x_1}, V_{x_2} = 0}$

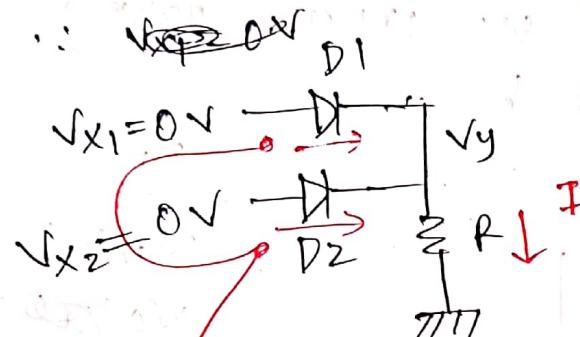

if diod are ON current will flow to this direction.

And we also know current flow from higher potential to lower potential.

For this flow of I there's need $V_y > 0V$

so we can say the cathod of both of the diod connected to 0V or higher than zero volt. (As connected to V_y node)

And here Both diod Anode V_{x_1} and $V_{x_2} = 0V$ But for conducting current on to ON diode we need $V_d > 0$ or $V_A > V_C$ For this case $V_{x_1} > V_y$ and $V_{x_2} > V_y$. so Here Both D1 and D2 is OFF (reverse bias)

Now OFF means

D1 and D2 creates open circuit.
No current flow.

$$\begin{aligned} &\text{from ohm's law} \\ &V_y - 0 = IR \\ &\Rightarrow V_y = 0 \\ &\therefore V_y = 0V \end{aligned}$$


Sub.: _____

| | | | | | | |
|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|
| SAT | SUN | MON | TUE | WED | THU | FRI |
| <input type="checkbox"/> |

DATE: / /

Case II: $V_{X_1} = 0V, V_{X_2} = 5V$

For this (see previous case),
circuit will be:

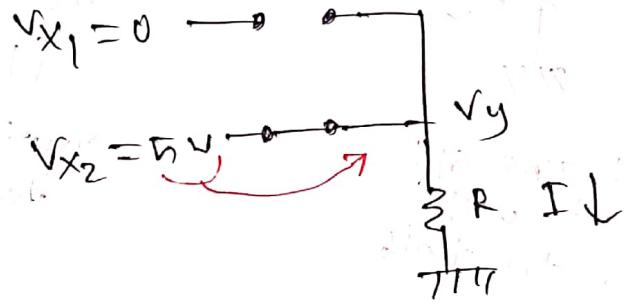 D_1 $V_A = 0V$ $V_C = V_D = V_y > 0V$ $D_1 = \text{OFF}$
(O.C.)

$$\therefore V_y = V_{x_2}$$

$$\therefore V_y = 5V$$

 $V_A = 5V$ $V_y > 0V$ $D_2 = 0N$


S.C.

Case III: $V_{X_1} = 5V, V_{X_2} = 5V$

Similar to Case II

Sub: _____

case 1 $V = ?$ | $\sqrt{x_1} = 5V, \sqrt{x_2} = 5V$

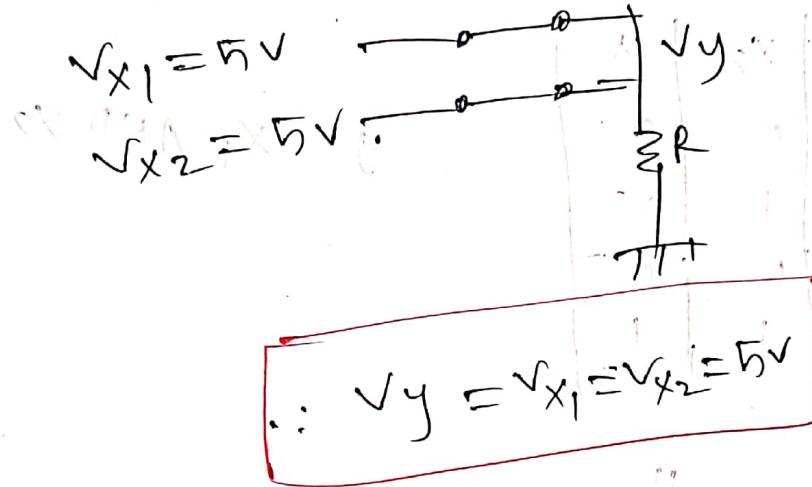


D1
 $V_A = 5V$
 $V_C = Vy > 0$
 ON
 (S.C)

Worst
off condition

D2
 $V_A = 5V$
 $V_C = Vy > 0$
 ON
 (S.C)

so all case for voltage touch
table fulfill.

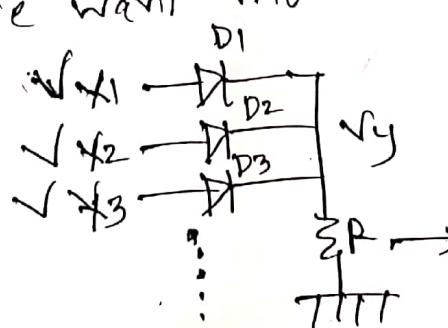* Now if we want more input just add them like this:



(*)

pull down resistors.


AND operation

| x_1 | x_2 | y |
|-------|-------|-----|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

$$y = x_1 \text{ AND } x_2$$

| v_{x_1} | v_{x_2} | v_y |
|-----------|-----------|-------|
| 0V | 0V | 0V |
| 0V | 5V | 0V |
| 5V | 0V | 0V |
| 5V | 5V | 5V |



voltage truth table

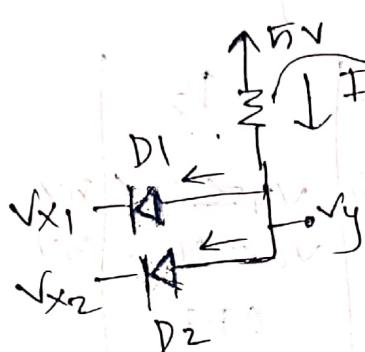diode circuit op A for AND operation

pull up resistor.
pulling up the voltage
of Vy Node when both
diodes are off and Node
Vy is floating.

case 1: $V_{x_1} = 0V, V_{x_2} = 0V$ [flowing current]

$$\text{D1 } V_y \leq 5 \text{ V}$$

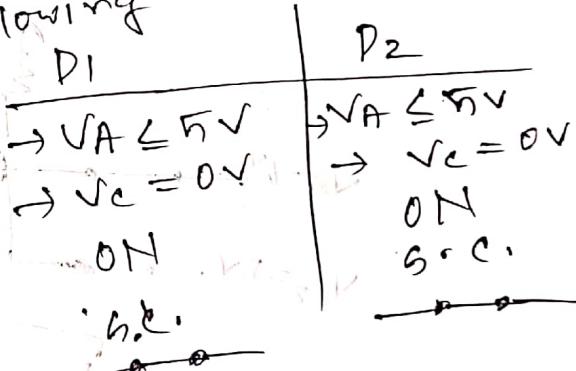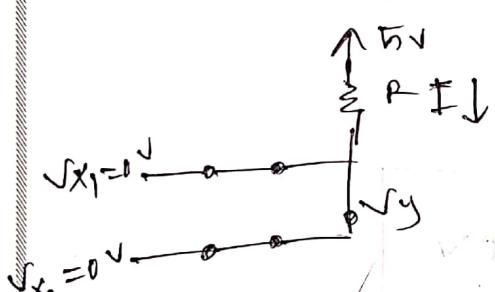

$$\therefore V_y = V_{x_1} = V_{x_2} = 0V$$

Sub.: _____


SAT SUN MON TUE WED THU FRI

DATE: / /

Case 2: $V_{X_1} = 0V, V_{X_2} = 5V$

$V_y \geq 5V$, to allow current

| | D ₁ | A | D ₂ |
|-------------------------------|------------------------|------------|----------------------|
| $V_A \Rightarrow V_y \leq 5V$ | $V_A \leq V_y \leq 5V$ | $V_C = 0V$ | $V_C = V_{X_2} = 5V$ |
| ON | OFF | | OFF |

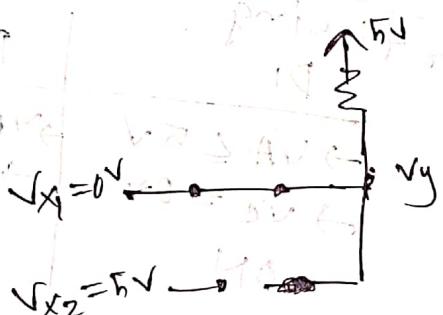

$$\therefore V_y = V_{X_1} = 0V$$

Case 3: $V_{X_1} = 5V, V_{X_2} = 0V$

same as case 2

$$V_y = V_{X_2} = 0V$$

Sub.: _____

SAT SUN MON TUE WED THU FRI

DATE: / /

Case 4:

$$V_{X_1} = 5V, V_{X_2} = 5V$$

$$\sqrt{A} \Rightarrow V_y \leq 5V$$

$$\sqrt{C} \Rightarrow V_{X_1} = 5V$$

OFF

O.C.

D₂

$$\sqrt{A} \Rightarrow V_y \leq 5V$$

$$\sqrt{C} \Rightarrow V_{X_2} = 5V$$

OFF

O.C.




$V_y = 5V$ → pull up resistor.

$$\therefore V_{X_1} = 5V \rightarrow V_y$$

$$V_{X_2} = 5V \rightarrow V_y$$

$$V_y = 5V$$

* * * For multiple input

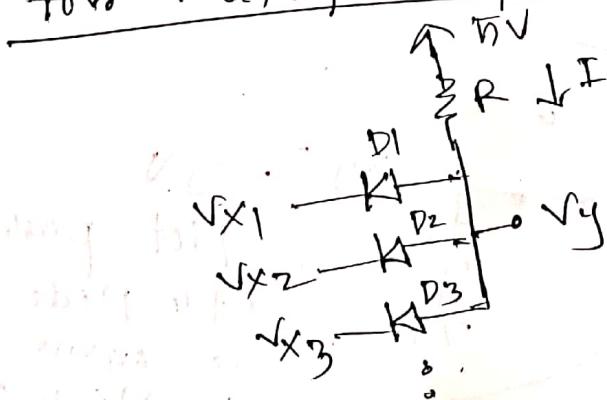


Sub.: _____

SAT SUN MON TUE WED THU FRI

DATE: / /

what will we input different type of voltage? [For OR operation]


lets we have this OR gate configuration:

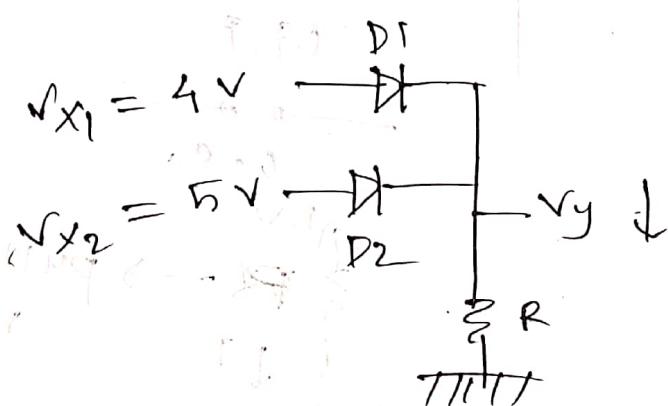

$$\begin{aligned} \text{D}_1 \\ \text{V}_A &= \cancel{\text{V}_x_1} = \text{V}_x_1 = 4\text{V} \\ \text{V}_c &= \text{V}_y > 0 \end{aligned}$$

$$\begin{aligned} \text{D}_2 \\ \text{V}_A &= \cancel{\text{V}_x_2} = \text{V}_x_2 = 5\text{V} \\ \text{V}_c &= \text{V}_y > 0 \\ \text{ON} \end{aligned}$$


ON

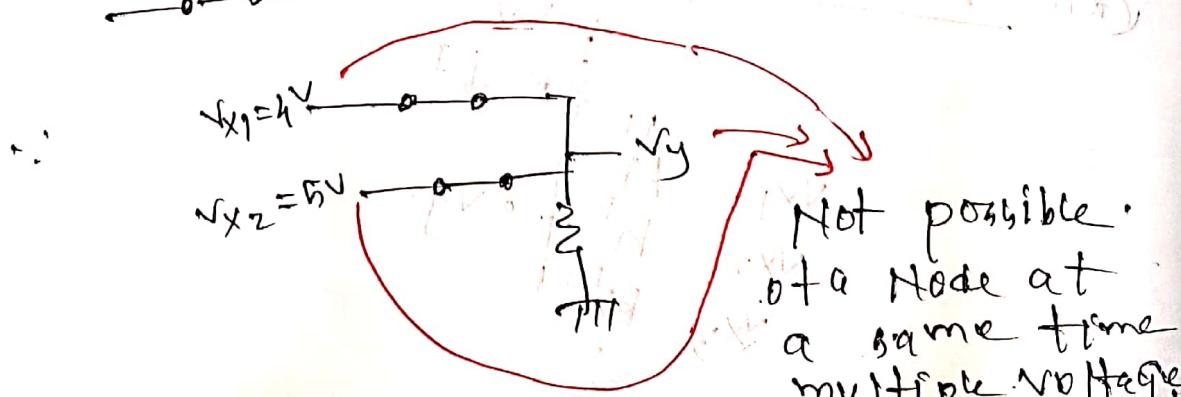

Not possible.
at a Node at
a same time
multiple voltage.

So what will be the right case?

Assume D₁ and D₂ are off.

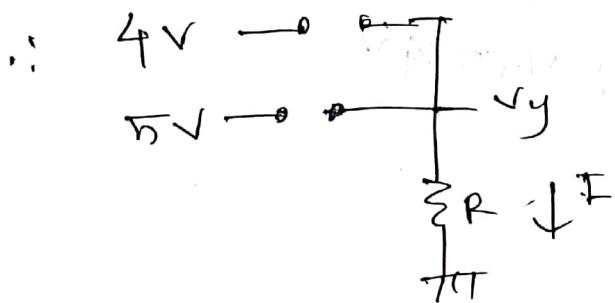

∴ here $I = 0$

$$\text{Vf} \rightarrow \therefore V_y - 0 = 1 \text{ V}$$

$$\Rightarrow V_y = 0 \times R$$

$$= 0 \text{ V}$$

But here ~~Both~~ D₁'s

Anode has 4V

and D₂ anode has

5V

by this case not
possible. (Because)

According to anode

and cathode voltage

Both should be ON.


Sub: _____

SAT SUN MON TUE WED THU FRI

DATE: / /

Assuming $D_1 \Rightarrow ON$ $D_2 \Rightarrow OFF$

∴ The output voltage is zero.

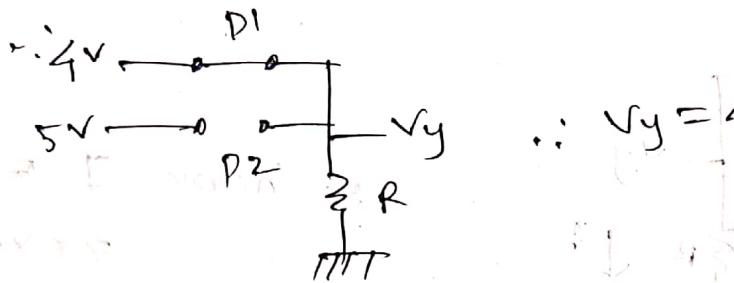Now if $V_y = 4V$ So ~~for~~ for D_2 ,

$$\begin{aligned} V_A &= 5V \\ V_C &= 4V \end{aligned}$$

V_A > V_C so D_2 should be ON also


But here we assume OFF.

But this is not possible

Sub.: _____

SAT SUN MON TUE WED THU FRI

DATE: / /

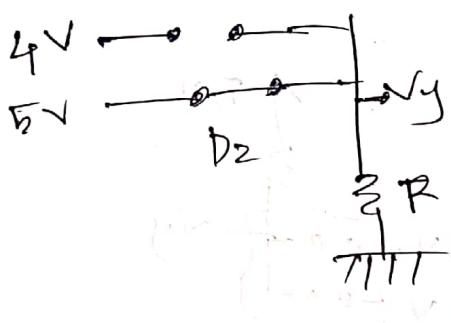Now Assuming $D_1 \Rightarrow \text{OFF}$ $D_2 \Rightarrow \text{ON}$ Hence D_1 is off.

$$\therefore V_y = 5V$$

Now if $V_y = 5V$ then for D_1

$$V_A = 4V$$

$$V_C = V_y = 5V \quad \therefore V_A < V_C$$


Hence D_1 is OFF \therefore OFFHence this assumption is correct.
So this assumption is correct.

Ques. From this we can say if we have multiple voltage source with different voltage source then the output voltage will be equal to the voltage of higher voltage source [For of operation]


Now For ϕ AND operation [Different

voltage input]

Diffrent
V_{x1} & V_{x2}

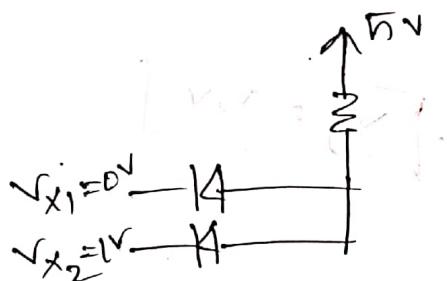


D₁, D₂ \rightarrow ON

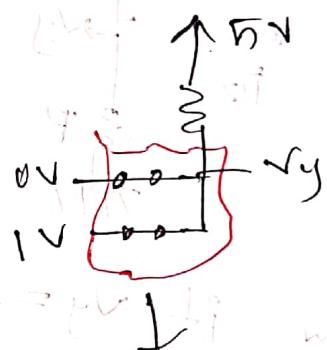

1V and Not possible because one node

can't have different value

Now Assume D₁ and D₂ \Rightarrow OFF

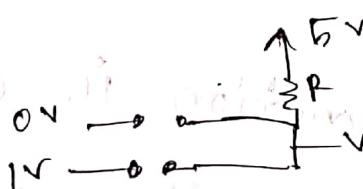

I = 0A


Sub.: _____

| | | | | | | |
|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|--------------------------|
| SAT | SUN | MON | TUE | WED | THU | FRI |
| <input type="checkbox"/> |

DATE: / /

Now assume

$$\begin{cases} D_1 = \text{OFF} \\ D_2 = \text{ON} \end{cases}$$

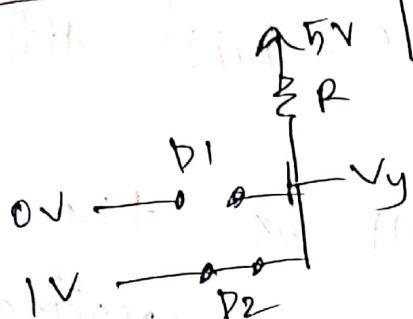Now for D1

$$V_A = \cancel{0V} = V_Y$$

$$V_C = 0V$$

∴ ON


But we assume here OFF
so Not possible

Now Assume

$$D_1 = \text{ON}$$

$$D_2 = \text{OFF}$$

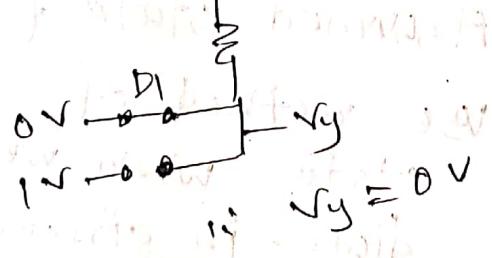For bottom button off
to work one of the following must be true



$$\begin{cases} D_2 \\ V_A = 0V \\ V_Z = 1V \end{cases}$$

$$V_A = V_C$$


∴ OFF

so this assumption correct.

**

So from this we can say we if we have more diodes with different voltage input.

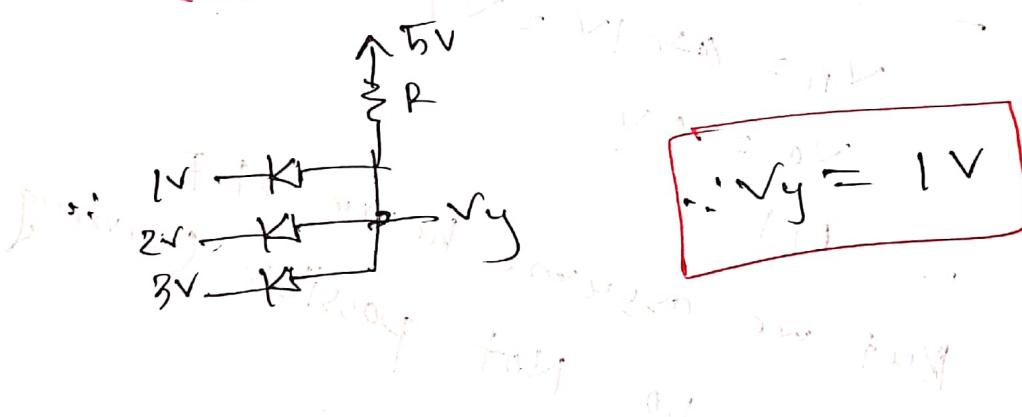then output will be the lowest voltage source voltage for AND operation



Ans: This is called method of Assumed state if we have to use method of assumed state when we have multiple diode in circuit)