
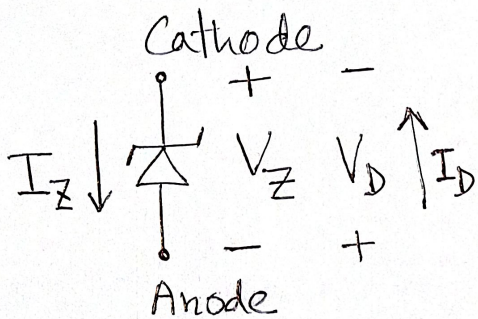



Zener Diode

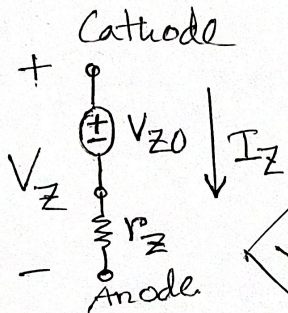

In breakdown region, zener diode can be modeled as,



$$V_Z = V_{Z0} + I_Z r_Z$$

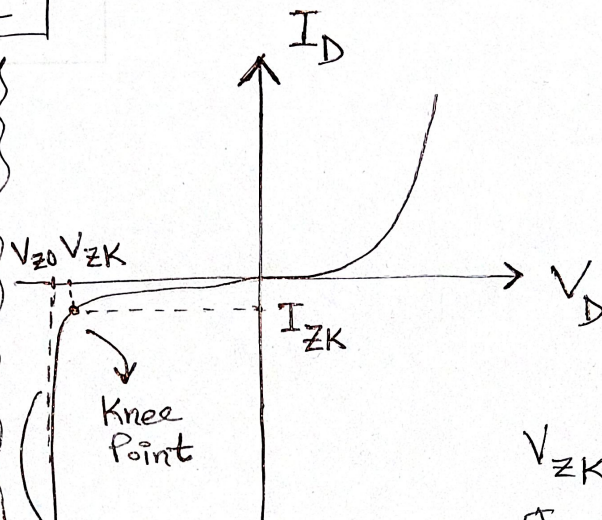

Slope = $\frac{1}{r_Z}$

This region is called the Breakdown Region

for breakdown region, $I_Z \gg I_{ZK}$

$V_{ZK} \rightarrow$ knee voltage


$I_{ZK} \rightarrow$ knee current

$r_Z \rightarrow$ zener resistance

$$V_{Z0} \approx V_{ZK}$$

Zener Diode As A Regulator

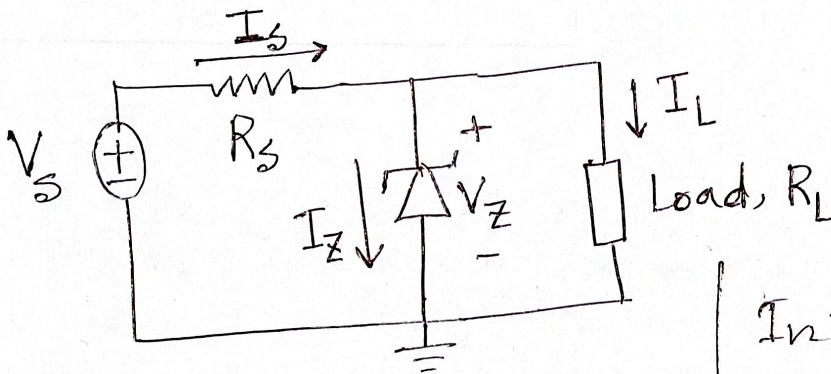→ zener diode has to be in the breakdown region



It will be best for zener diode if,

$$V_S \rightarrow \max$$

$$I_L \rightarrow \min$$

$$I_Z \rightarrow \max$$

In the worst case,

$$I_L \rightarrow \max$$

$$\text{i.e. } I_Z \rightarrow \min = I_{ZK}$$

$$V_S \rightarrow \min$$