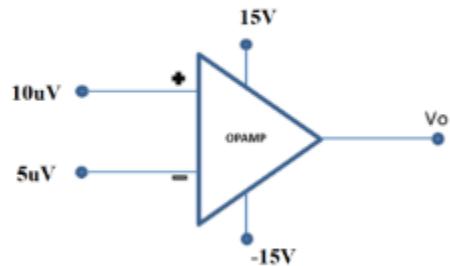



Op-Amp

1. Observe the following circuit.



Calculate the value of V_o . Repeat the problem with $V_+ = 1 \text{ mV}$ and $V_- = 0.2 \text{ mV}$. Consider $A = 2105$.

①

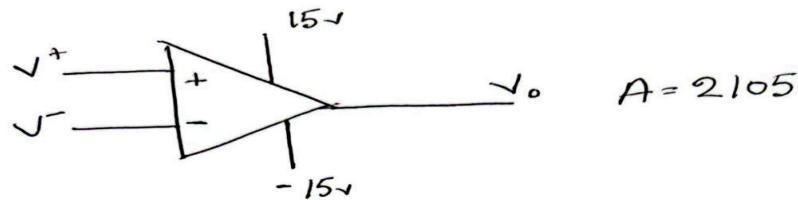

$$\textcircled{i} \quad V^+ = 10 \times 10^{-6} \text{ V}, V^- = 5 \times 10^{-6} \text{ V}$$



$$V_o = A (V^+ - V^-) = 2105 \times (10 - 5) \times 10^{-6}$$
$$V_o = 0.0105 \text{ V}$$

$$\textcircled{ii} \quad V^+ = 1 \times 10^{-3} \text{ V}, V^- = 0.2 \times 10^{-3} \text{ V}$$


$$V_o = A (V^+ - V^-) = 2105 \times (1 - 0.2) \times 10^{-3}$$
$$V_o = 1.684 \text{ V}$$

Vorifix
Voriconazole USP

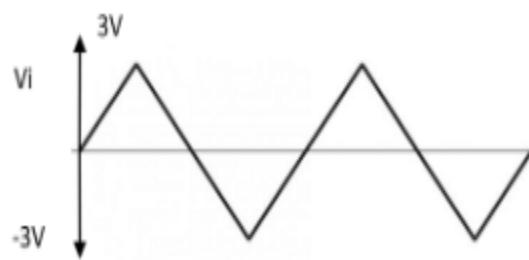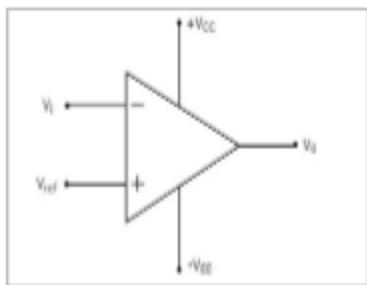
2. Draw output V_o for the following op-amp circuit.



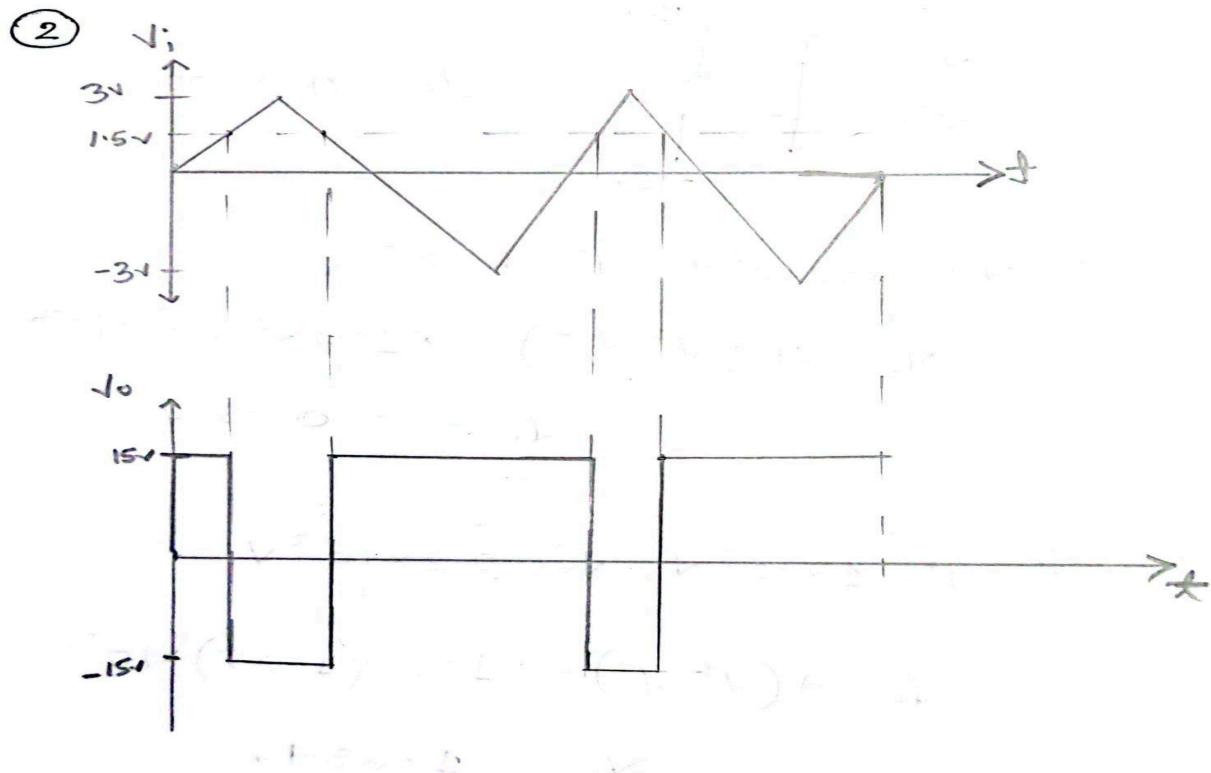
$V_{CC} = 15V = -V_{EE}$, $V_{ref} = 1.5V$, V_i is a 6V p-p triangular signal as shown below.



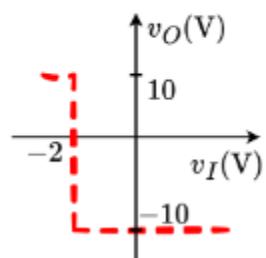3. Design a circuit using op-amp that has the voltage transfer characteristics as shown in the figure below. $v_o(V)$ is the **output voltage** and $v_I(V)$ is the **input voltage**.



(3) Ans:

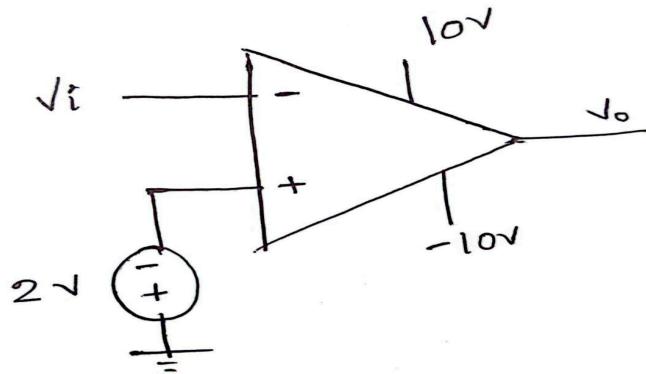

5.

A valve is used to release (when valve is OPEN,) or maintain (when valve is CLOSED,) water pressure in a water tank. The valve operates on ACTIVE LOW logic. (i.e., the valve is OPENED when given a LOW voltage of 1 V, but remains CLOSED when provided a HIGH voltage of 6 V.)

A pressure sensor is installed in the water tank that outputs a voltage linearly proportional to pressure, as shown in the table below.

At 0.5 atm pressure	At 1 atm pressure	At 1.5 atm pressure
$v_{0.5\text{ atm}} = 0.5\text{ V}$	$v_{1\text{ atm}} = 3\text{ V}$	$v_{1.5\text{ atm}} = 5.5\text{ V}$

The pressure in the water tank can be measured by the formula $P = h\rho g$, where P , (in Pascals (Pa) unit) is the water pressure, h is the height of water in the tank (in metres), $\rho (= 1000 \text{ kg m}^{-3})$ is the density of water and g is the acceleration due to gravity (in m s^{-2}).

[1 atm = 101325 Pa]

- Design a circuit using Op-Amp comparator to automatically turn OPEN the valve if water level exceeds 10 m.
- Draw the voltage transfer characteristics (VTC) of the designed Op-Amp.

(A) i

$$\text{Given, } P = \rho gh$$

$$= 10 \times 1000 \times 9.8$$

$$= 98000 \text{ Pa}$$

$$h = 10 \text{ m}$$

$$\rho = 1000 \text{ kg m}^{-3}$$

$$g = 9.8$$

$$\text{Converting to atm} = \frac{98000}{101325} \quad [1 \text{ atm} = 101325 \text{ Pa}]$$

$$= 0.967$$

Now,

Pressure change

For $(1-0.5) = 0.5 \text{ atm}$, voltage change is $(3-0.5) = 2.5 \text{ V}$

$$1 \quad " \quad " \quad " \quad " \quad " \quad \frac{2.5}{0.5} \text{ V}$$

$$(0.967-0.5) \quad " \quad " \quad " \quad " \quad " \quad \frac{2.5 \times 0.967}{0.5} \text{ V}$$


$$= 2.335$$

So, for 0.967 atm pressure


$$\text{Voltage in} = (0.5 + 2.335)$$

$$= 2.835 \text{ V}$$

OP-Amp Circuit →

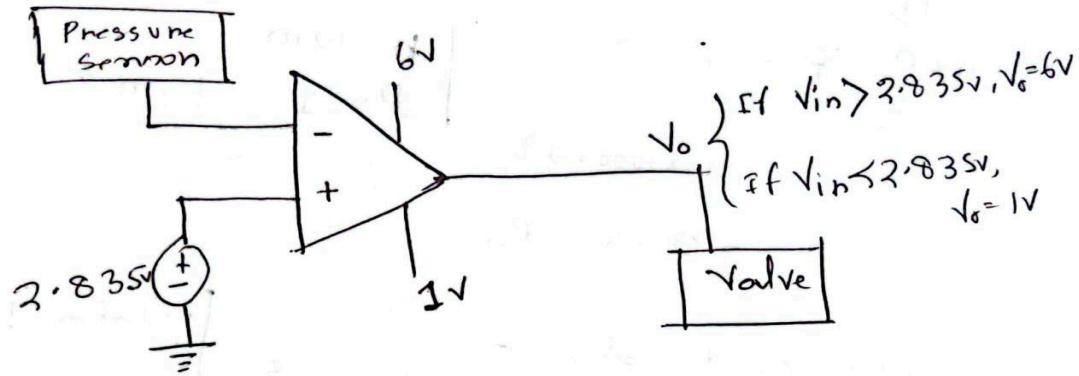

(ii)

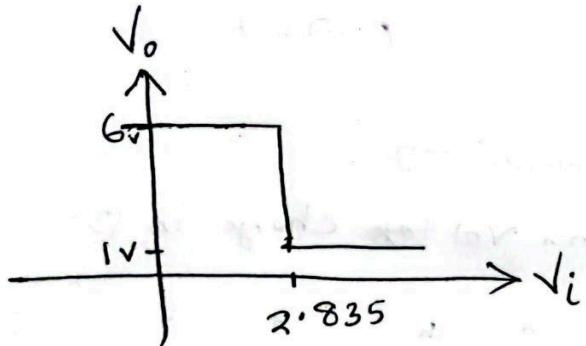

Fg: VTC of the OP-AMP (i)


Given, determine the output voltage at t = 1 ms.

L1J

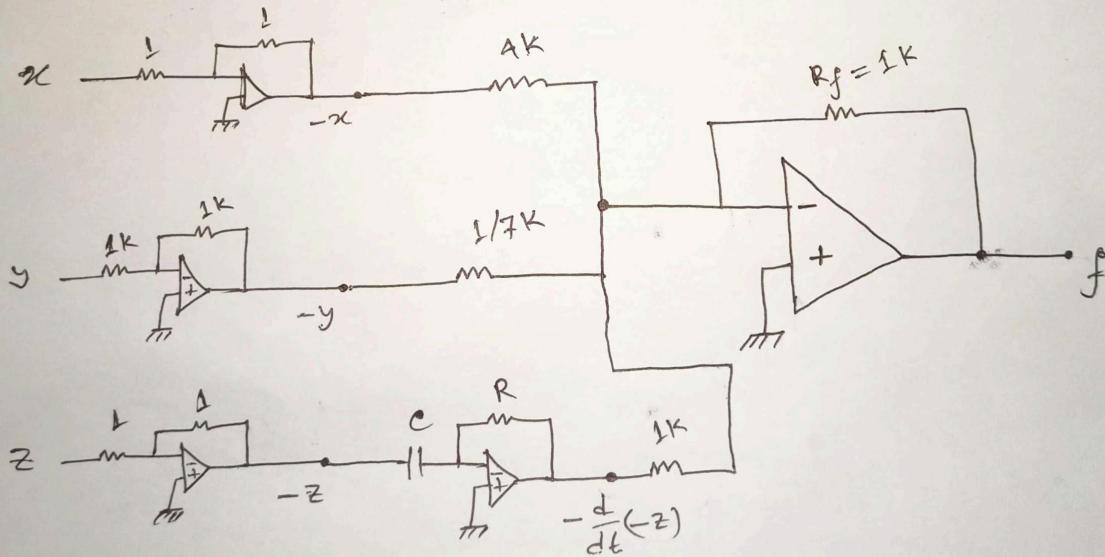
- (e) Design a circuit using Op-Amps to implement the following expression: [4]

$$f = \frac{1}{4}x + 7y - \frac{d}{dt}z$$

$$\begin{aligned} f &= \frac{1}{4}x + 7y - \frac{d}{dt}(z) \\ &= - \left[-\frac{1}{4}x - 7y + \frac{d}{dt}(z) \right] \\ &= - \left[\frac{1}{4}(-x) + 7(-y) + \left\{ -\frac{d}{dt}(-z) \right\} \right] \end{aligned}$$




8.

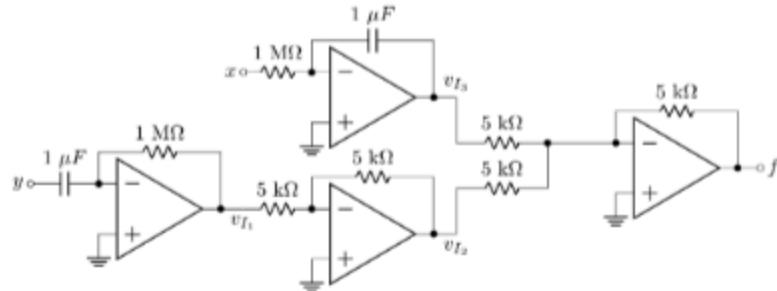

- (a) **Analyze** the circuit above to find an expression of f in terms of inputs x and y . Also, **determine** the intermediate outputs v_{I_1} , v_{I_2} , and v_{I_3} as denoted in the circuit. [4]
- (b) Draw the circuit of an inverting amplifier and **design** it in such a way that the voltage gain, $k = -4$. (*i.e.*, find the values of R_1 and R_2). [3]
- (c) **Show** the input and output waveforms of the inverting amplifier of part (b) assuming a sinusoidal input of 0.5 V amplitude. **Calculate** the amplitude of the output. [2]
- (d) Consider the inverting amplifier of part (b) again. Assume the input voltage can provide a maximum current of $0.5 \mu\text{A}$. **Determine** the design changes required, if any, for the circuit to work. [1]

Date: / /

Q. (a)

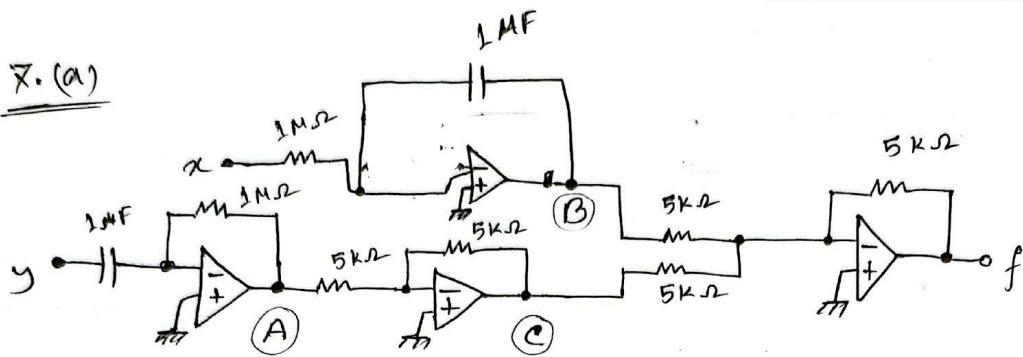

$$A = -R_C \left[\frac{d}{dt}(y) \right] = -(1\text{M}\Omega \times 1\text{MF}) \left[\frac{d}{dt}(y) \right] \\ = -\frac{1}{dt}(y)$$

$$B = -\frac{1}{R_C} \left[\int x dt \right] \Rightarrow c = -\frac{5}{5} \left(-\frac{1}{dt}(y) \right) \\ = -\int x dt \qquad \qquad \qquad = \frac{1}{dt}(y)$$

$$f = - \left[\frac{R_f(B)}{R_1} + \frac{R_f(c)}{R_2} \right] \\ = - \left[\frac{5}{5} (-\int x dt) + \frac{5}{5} \frac{1}{dt}(y) \right] \\ = \int x dt - \frac{1}{dt}(y)$$

(Ans.)

7.(b) Given,

$$K = -4$$

for inverting,

$$V_{out} = -\frac{R_2}{R_1} (V_{in})$$

here,

$$\therefore -\frac{R_2}{R_1} = -4$$

$$\Rightarrow \frac{R_2}{R_1} = \frac{4}{1}$$


$$\Rightarrow 4R_1 = R_2$$

$$\therefore R_1 : R_2 = 1 : 4$$


ref,

$$R_1 = 1 \text{ k}\Omega$$

$$R_2 = 4 \text{ k}\Omega$$

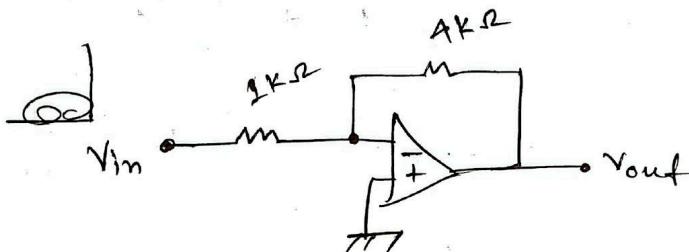


12.

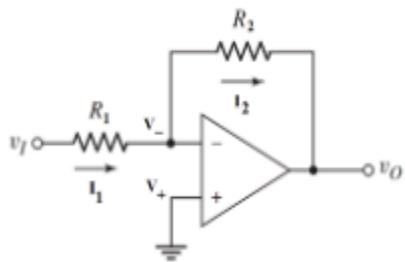

- (a) Design an inverting amplifier (i.e., find the values of R_1 and R_2 of the circuit shown in the Figure above) in such a way that the voltage gain is -5 .
 - (b) Consider the circuit you drew in (a) again. Assume the input $v_I = 0.1 \text{ sin}(\omega t) \text{ V}$ has a maximum current rating of $5 \mu\text{A}$. What design changes, if any, are required for this input, if the voltage gain remains the same?
 - (c) Draw the input and output waveforms of the circuit you designed in (c).
- Analyze the following circuit and derive the expression for the output voltage (V_{out}) in terms of the inputs. If $V_1 = 1 \text{ V}$, $V_2 = 2 \text{ V}$, and $V_3 = 1.5 \text{ V}$, and all the resistors have equal values, calculate V_{out} .

Date: / /

11. (a) Given,
gain = -5

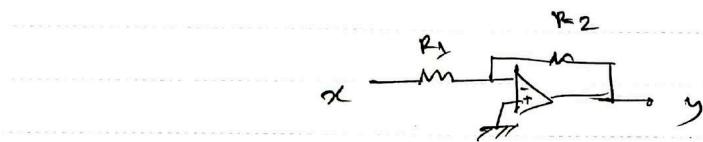

we know,

$$y = -\frac{R_2}{R_1} (x)$$

here,


$$-\frac{R_2}{R_1} = -5$$

$$\Rightarrow 5R_1 = R_2$$


let,

$$R_1 = 1K\Omega$$


$$R_2 = 5K\Omega$$

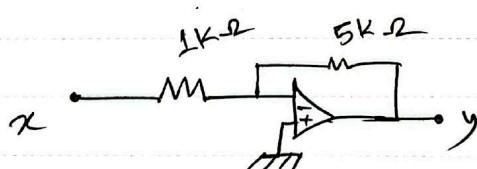

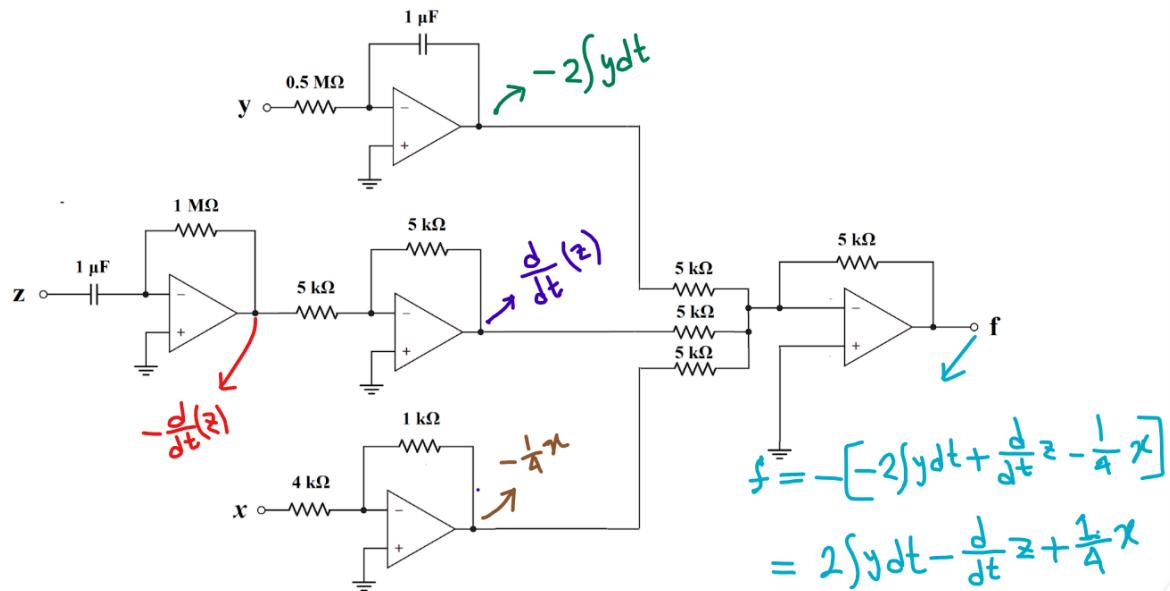
12. Analyze the following circuit to find an expression of f in terms of x , y , and z .



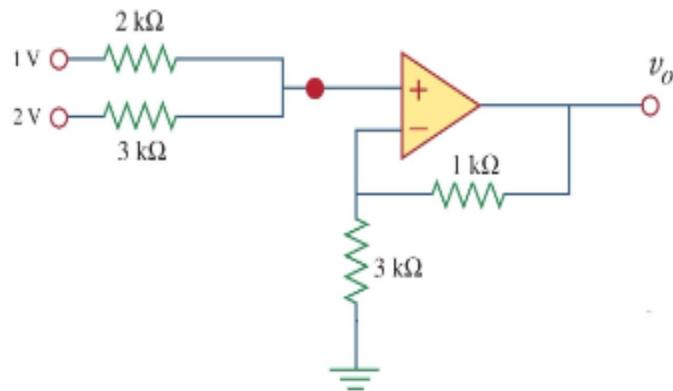14. Consider the Ideal Op-Amp and find the value of V_o .



(13)

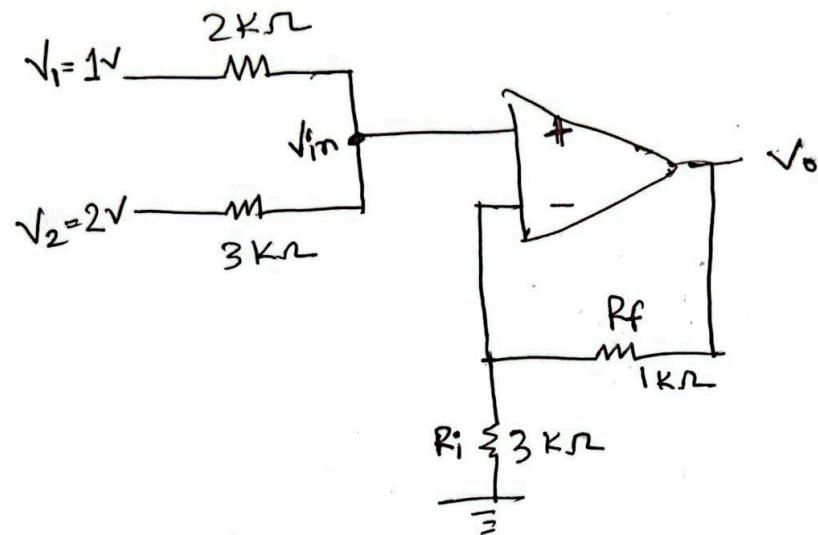At V_{in} ,

$$\frac{V_1 - V_{in}}{2} + \frac{V_2 - V_{in}}{3} = 0$$

$$\Rightarrow \frac{1 - V_{in}}{2} + \frac{2 - V_{in}}{3} = 0$$

$$\Rightarrow \frac{3 - 3V_{in} + 4 - 2V_{in}}{6} = 0$$

$$\Rightarrow 5V_{in} = 7$$

$$\Rightarrow V_{in} = 1.4$$

We know for non-inverting OP-Amp,

$$V_o = \left(1 + \frac{R_f}{R_i}\right)V_{in}$$

$$= \left(1 + \frac{1}{3}\right)1.4$$

$$= 1.867 \text{ V}$$

Diode Logic Gates

- Implement the following expressions using ideal diodes:

i. $xy + yz$


ii. XOR

iii. XNOR

iv. $(A+B)XY$


- Implement expression using ideal diodes \rightarrow

i. $xy + yz$

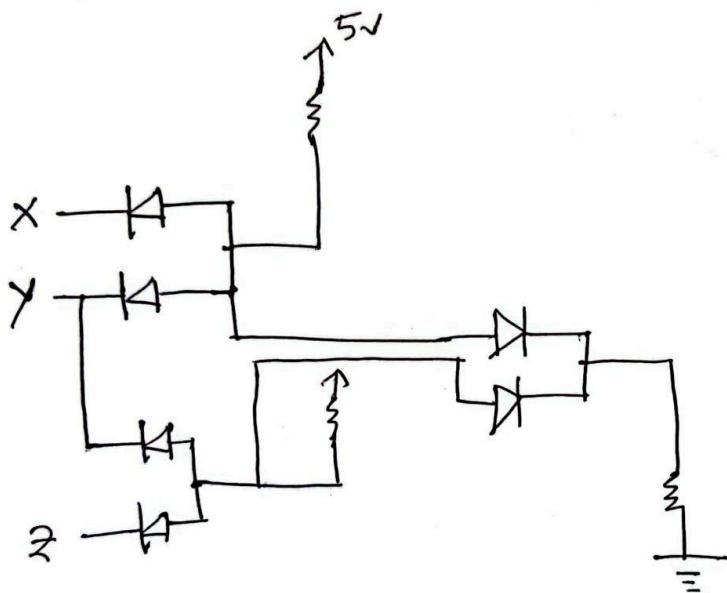


(ii and iii) \rightarrow You can only implement OR/And gates with diode. NOT, XOR, XNOR, NAND gates can be implemented using diode.

iv.

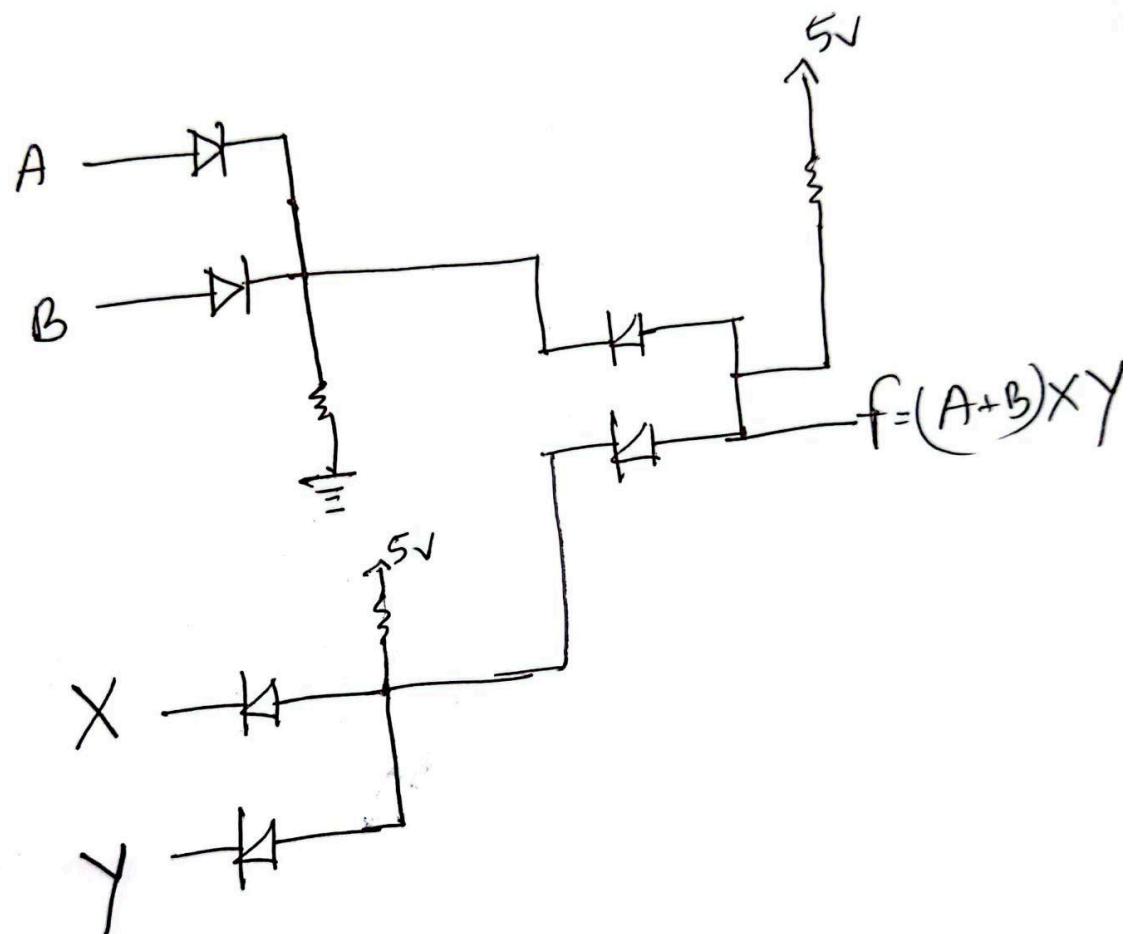


- Design a 4 input AND gate using ideal diodes
- Design a 3 input OR gate using ideal diodes

.. 4 input And Gate →

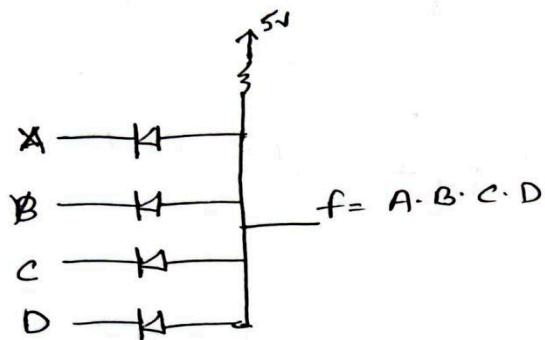

• 3 input OR gate →

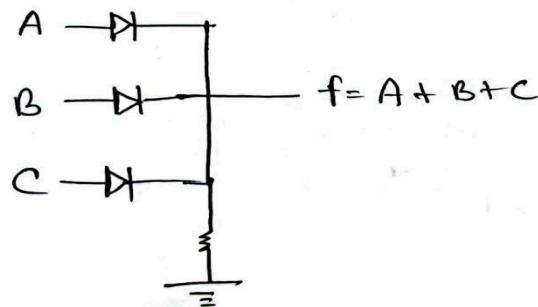

• Five Question problem →

Ans: $A \cdot B \cdot C \cdot (D \oplus E)$

You cannot ~~not~~ use diodes for implementing XOR functions.

- For this question, assume all the diodes are ideal.


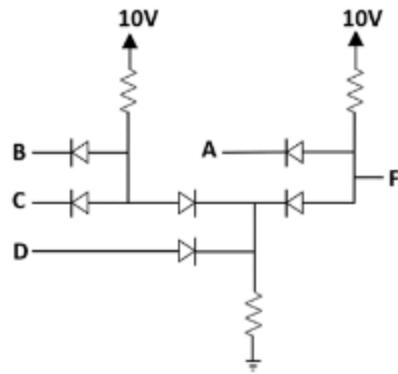


Figure 1

- Assuming A, B, C, D are boolean variables, analyze the circuit of Figure 1 to find an expression of F in terms of A, B, C and D.
- Analyze the circuit in Figure 1 to find the output voltage(s) F and complete the table in Figure 2, assuming A, B, C and D are voltage signals

A	B	C	D	F
4V	3V	4V	6V	
5V	3V	4V	2V	
13V	3V	4V	15V	

Figure 2

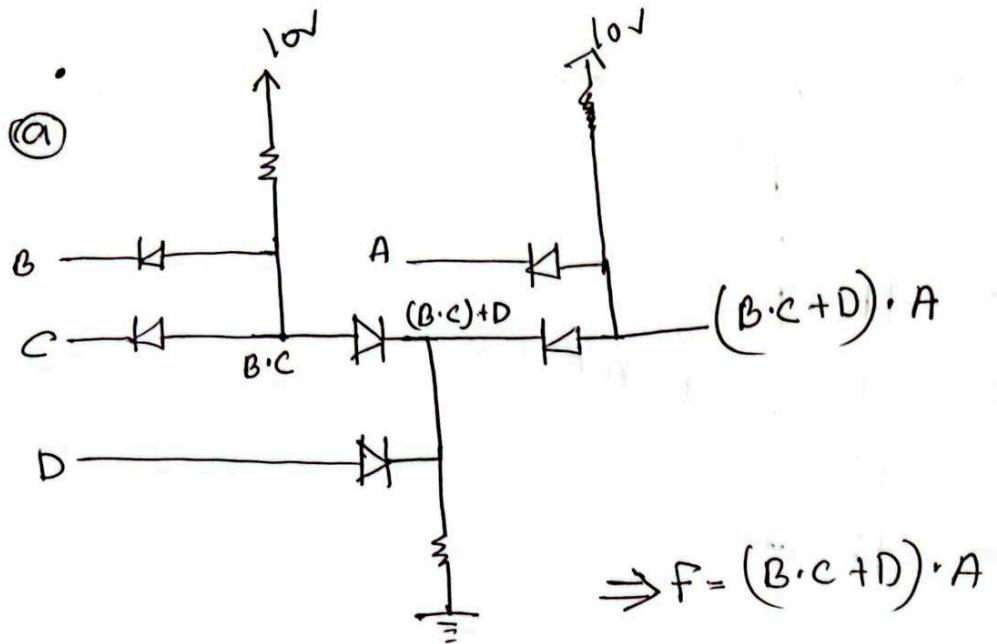

(b)

A	B	C	D	F
1	3	4	6	4
5	3, 4	2	3	
13	3	4	15	10

$\min \curvearrowleft B \cdot C = 3 \Rightarrow (B \cdot C) + D \Rightarrow 6 \Rightarrow ((B \cdot C) + D) \cdot A \Rightarrow 4$

$\max \curvearrowright B \cdot C = 3 \Rightarrow (B \cdot C) + D \Rightarrow 15$

\downarrow

$((B \cdot C + D) \cdot A) \Rightarrow 13$

But our
saturation/Power
supply in 10V.
so, $A_{mz} = 10V$

- Maisha is designing a game where she needs to determine an algorithm for level upgrades. The quests in level-1 are expressed using Boolean variables A, B, C, D, and E. For upgrading from level-1 to level-2 she will need to fulfill the following conditions-

- Quest "A" and "B" must be completed
- At Least one quest has to be completed from "C", "D" and "E"

(a) **Deduce** the logic function, F, using Boolean variables A, B, C, D, and E to implement Maisha's algorithm. [3]

(b) **Determine** the values of "F" in the following table using the logic function from (a). [2]

A	B	C	D	E	F
0	0	1	0	1	?
0	1	1	1	0	?
1	0	0	0	0	?
1	1	1	0	0	?

(c) **Draw** the circuit diagram implementing the logic function from (a). [3]

(d) **Discuss** whether you can design a NAND gate with Si diodes. [2]

• Maisha's Designing Game →


(a)

$$F = A \cdot B \cdot (C + D + E)$$

(b)

A	B	C	D	E	F
0	0	1	0	1	0
0	1	1	1	0	0
1	0	0	0	0	0
1	1	1	0	0	1

(c)

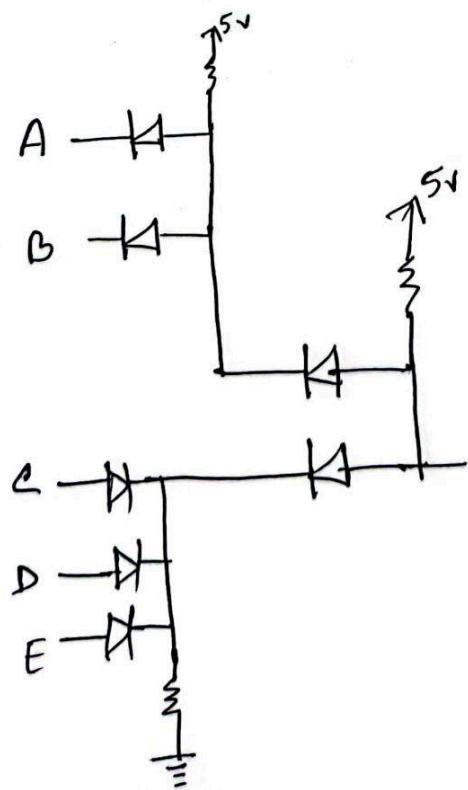

$$F = A \cdot B \cdot (C + D + E)$$


(d) Ans:

You can not design NANA, NOR, XOR, Gates using diodes. Because they need Not Gate, which can not be implemented by diodes.


Diode: Method of assumed states

Diode & Method of Assumed State


$$V_{D_0} = 0.3V$$

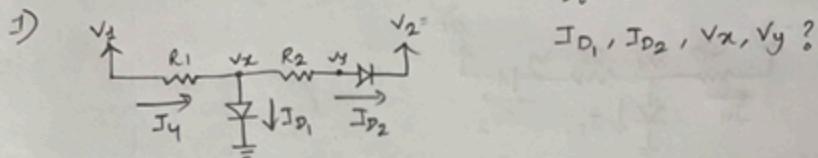

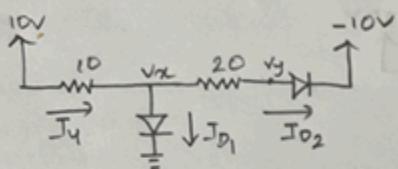① When, $V_1 = 10V$, $V_2 = -10V$, $R_1 = 10k\Omega$, $R_2 = 20k\Omega$



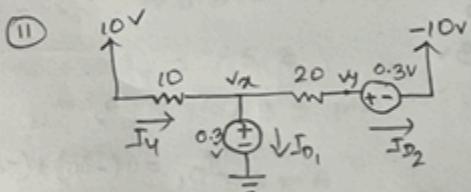① $D_1 \rightarrow ON, D_2 \rightarrow OFF$



$$\underline{V_2}$$

$$V_2 - 0 = 0.3 \\ \Rightarrow V_2 = 0.3V$$

$$\underline{V_y}$$

$$V_y - (-10) = 0.3 \\ \Rightarrow V_y = 0.3 - 10 \\ = -9.7V$$

$$\underline{I_4}$$

$$I_4 = \frac{10 - V_x}{10} \\ = \frac{10 - 0.3}{10} \\ = 0.97mA$$

$$\underline{I_{D_2}}$$

$$I_{D_2} = \frac{V_x - V_y}{20} \\ = \frac{0.3 - (-9.7)}{20} \\ = 0.5mA$$

$$I_4 = I_{D_1} + I_{D_2}$$

$$\Rightarrow I_{D_1} = I_4 - I_{D_2} \\ = 0.97 - 0.5 \\ = 0.47mA$$

iii) Verifying


$$I_{D_1} > 0 \\ I_{D_2} > 0 \quad \therefore \text{assumption correct}$$

Clonatril®
clonazepam USP




(ii)

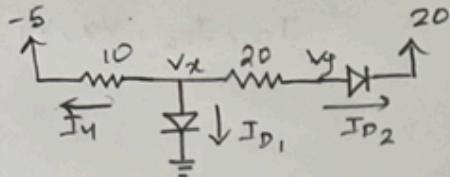When $V_1 = -5V$, $V_2 = 20V$, $R_1 = 10k\Omega$, $R_2 = 20k\Omega$



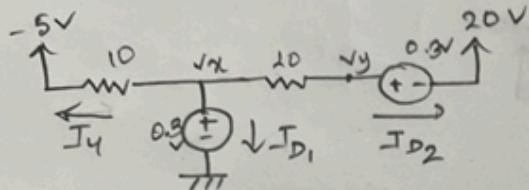① $D_1 \rightarrow ON, D_2 \rightarrow ON$



$$\begin{aligned} \frac{Vx}{Iy} & \quad \frac{Vy}{ID_2} \\ Vx - 0 &= 0.3 \quad Vy - 20 = 0.3 \\ \Rightarrow Vx &= 0.3V \quad \Rightarrow Vy = 20.3V \end{aligned}$$

$$\begin{aligned} \frac{Iy}{Iy} & \quad \frac{ID_2}{ID_2} \\ Iy &= \frac{0.3 - (-5)}{10} \\ &= -0.53mA \end{aligned}$$


$$\begin{aligned} \frac{ID_2}{ID_2} & \quad \frac{ID_1}{ID_1} \\ ID_2 &= \frac{Vx - Vy}{20} \\ &= \frac{0.3 - 20.3}{20} \\ &= -1mA (\neq 0) \end{aligned}$$

$$\begin{aligned} ID_1 &= (-Iy) + (-ID_2) \\ &= -0.53 + 1 \\ &= 0.47mA \end{aligned}$$

Current flows from the left node to the right node.

Therefore, assumption not correct.

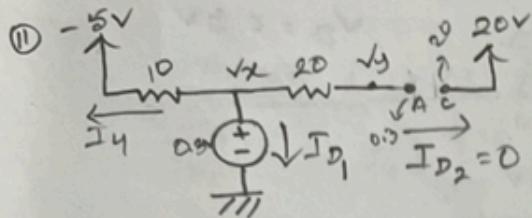① $D_1 \rightarrow ON, D_2 \rightarrow OFF$



$$I_y = I_{D_1}$$

$$V_x = 0.3V$$

$$V_x = V_y = 0.3V$$

KVL

$$-10I_y + 0.3 = -5 - 0$$

$$\Rightarrow +10I_y = +5.3$$

$$\Rightarrow I_y = 0.53mA$$

$$I_{D_1} = 0.53mA$$

$$V_D = V_A - V_C$$

$$= 0.3 - 20$$

$$= -19.7V$$

③ Verifying


$$I_{D_1} > 0 \quad \therefore \text{Assumption correct}$$

$$V_D \leq V_{D0}$$

2) D When $V_1 = 5V$, $V_2 = -3.5V$, $R_1 = 1k\Omega$, $R_2 = 10k\Omega$

① $D_1 \rightarrow ON$, $D_2 \rightarrow ON$

$$V_{D_0} = 0.3V$$

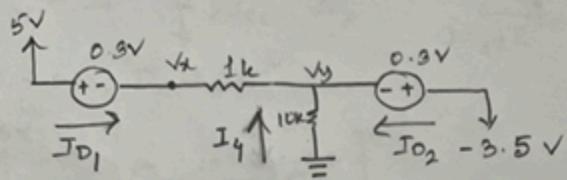

$$\frac{V_x}{5 - V_x = 0.3}$$

$$\frac{V_y}{-3.5 - V_y = 0.3}$$

$$\Rightarrow V_x = 4.7V$$

$$\Rightarrow V_y = -3.8V$$

$$I_{D_1} = \frac{V_x - V_y}{1}$$

$$I_4 = \frac{0 - (-3.8)}{10}$$

$$= 4.7 - (-3.8)$$

$$= 0.38mA$$

$$= 8.5mA (>0)$$

$$I_{D_1} = I_4 + I_{D_2}$$

$$\Rightarrow I_{D_1} = -I_4 - I_{D_2}$$

$$\Rightarrow -I_{D_2} = I_{D_1} + I_4$$


$$\Rightarrow -I_{D_2} = 8.5 + 0.38$$

$$\Rightarrow I_{D_2} = -8.88mA (>0)$$

I_{D_2} isn't greater than zero

Therefore, assumption not correct

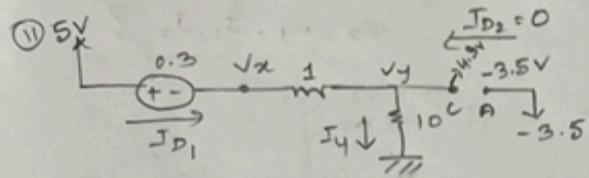① $D_1 \rightarrow ON$, $D_2 \rightarrow OFF$



$$\frac{V_x}{5 - V_x} = 0.3$$

$$\Rightarrow V_x = 4.7V$$

$$I_{D_1} = I_4$$

$$0.3 + I_{D_1} + 10I_4 = 5 - 0$$

$$\Rightarrow 0.3 + I_{D_1} + 10I_{D_1} = 5$$

$$\Rightarrow 11I_{D_1} = 4.7$$

$$\Rightarrow I_{D_1} = 0.43mA$$

$$I_4 = 0.43mA$$

③ Verifying

$$I_4 = \frac{V_y - 0}{10}$$

$$I_{D_1} > 0$$

$$\Rightarrow V_y = 10 \times 0.43 \\ = 4.3V$$


$$V_D < V_{D_s}$$

∴ Assumption correct


$$V_D = V_A - V_C$$

$$= -3.5 - (4.3)$$

$$= -7.8V$$

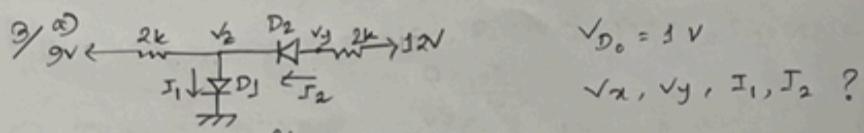

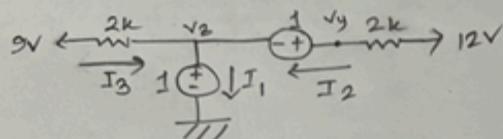b) $D_1 \rightarrow \text{ON}$, $D_2 \rightarrow \text{ON}$



$$\frac{\sqrt{v_2}}{\sqrt{v_2} - 0} = 1 \quad \frac{\sqrt{y}}{\sqrt{y} - 1} = 1$$

$$\Rightarrow \sqrt{v_2} = 1 \text{ V} \quad \Rightarrow \sqrt{y} = 2$$

$$\begin{aligned} I_3 &= \frac{9 - \sqrt{v_2}}{2} & I_2 &= \frac{12 - \sqrt{y}}{2} \\ &= \frac{9 - 1}{2} & &= 5 \text{ mA} \end{aligned}$$

$$\frac{I_3}{I_1} = I_3 + I_2$$

$$= 4 + 5 \\ = 9 \text{ mA}$$

Verifying

$$I_1 > 0 \quad \therefore \text{Assumption correct}$$

$$I_2 > 0$$

c) $P = I_1 \times V$

$$= 9 \times 1$$

$$= 9 \text{ mW} \rightarrow \text{tve}$$


$\therefore D_1$ is consuming power

4

$D_1 \rightarrow ON, D_2 \rightarrow ON^-$

$$V_{D_0} = 0.8V$$

$I_1, I_2, I_3 ?$

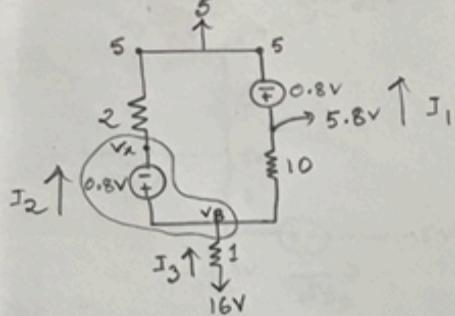

$V_B - V_x$ supermode,

$$V_B\left(\frac{1}{1} + \frac{1}{10}\right) + V_x\left(\frac{1}{2}\right) - \frac{16}{1} - \frac{5}{2} = 0$$

$$\Rightarrow 1.1V_B + (2^{-1})V_x = 18.5 \quad \textcircled{1}$$

$V_B - V_x$ constraint \Rightarrow

$$V_B - V_x = 0.8$$

$$\Rightarrow V_B + (-1)V_x = 0.8 \quad \textcircled{11}$$

Solving $\textcircled{1}$ & $\textcircled{11}$

$$V_B = 11.8V$$

$$V_x = 11.01V$$

Now,

$$I_3 = \frac{16 - 11.8}{5} = 0.96mA$$

$$I_2 = \frac{V_x - 5}{2} = \frac{11.01 - 5}{2} = 3.005mA$$

$$I_1 = \frac{V_B - 5.8}{10} = \frac{11.8 - 5.8}{10} = 0.6mA$$

Verifying




$I_2 > 0, \therefore \text{Assumption correct}$ **Clonatrip[®]**
clonazepam USP

5/

 $D_1 \rightarrow ON, D_2 \rightarrow ON^-$

$$\sqrt{D_0} = 0.7V$$

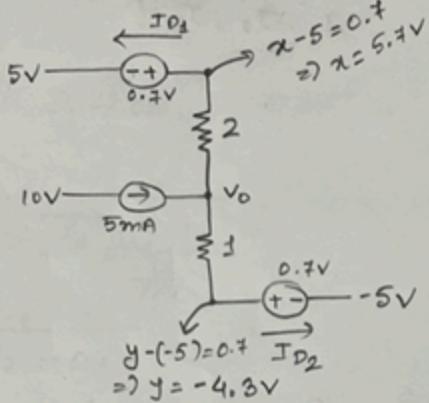KCL at V_0

$$V_0 \left(\frac{1}{2} + \frac{1}{1} \right) - \frac{5.7}{2} - (-4.3) - 5 = 0$$


$$\Rightarrow \frac{3}{2} V_0 = 3.55$$

$$\Rightarrow V_0 = 2.37V$$

$$\begin{aligned} I_{D1} &= \frac{V_0 - 5.7}{2} & I_{D2} &= \frac{V_0 - (-4.3)}{1} \\ &= \frac{2.37 - 5.7}{2} & &= 2.37 + 4.3 \\ &= -1.67mA (\neq 0) & &= 6.67mA (> 0) \end{aligned}$$

I_{D1} isn't greater than zero

∴ Therefore, assumption not correct

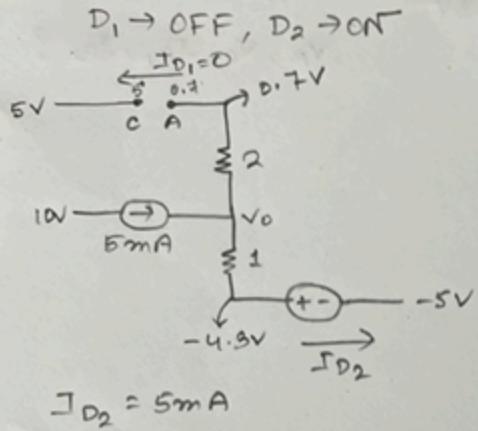

$$V_{D2} = 0.7V$$

$$ID_2 = 5mA$$

$$ID_2 = \frac{V_0 + 4.3}{1}$$


$$\Rightarrow V_0 = 5 - 4.3 \\ = 0.7V$$

$$V_D = V_A - V_C \\ = 0.7 - 5 \\ = -4.3V$$

Verifying

$$ID_2 > 0$$


$$V_D < V_{D0}$$

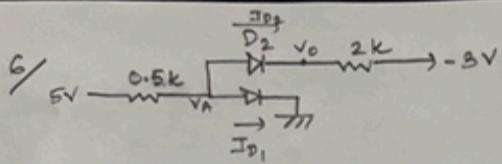

$$V_{D_0} = 0.6$$

$V_A, V_O, I_{D_1}, I_{D_2} ?$

$D_1 \rightarrow ON, D_2 \rightarrow ON$

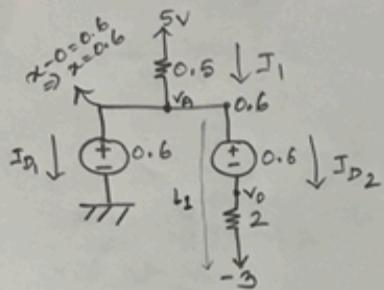

$$V_A = 0.6$$

$$0.6 - V_O = 0.6$$

$$\Rightarrow V_O = 0$$

$$I_1 = \frac{5 - 0.6}{0.5}$$

$$= 8.8 \text{ mA}$$

$I_1 \rightarrow$

$$0.6 + 2I_{D_2} = 0.6 - (-3)$$

$$\Rightarrow 2I_{D_2} = 3.6 - 0.6$$

$$\Rightarrow I_{D_2} = 1.5 \text{ mA}$$

Verifying

$$I_{D_1} > 0$$

$$I_{D_2} > 0$$

\therefore Assumption correct

$$I_1 = I_{D_1} + I_{D_2}$$

$$\Rightarrow I_{D_1} = I_1 - I_{D_2}$$

$$= 8.8 - 1.5$$

$$= 7.3 \text{ mA}$$

Rectifiers

1.

The input of a full-wave rectifier is a cosine voltage with peak $V_M = 5$ V and frequency 60 Hz, and output load resistance is $R = 2 \text{ k}\Omega$. Silicon diodes are used in this circuit for which the forward drop is $V_{D0} = 0.7$ V.

- (a) Briefly explain the purpose of a rectifier and describe its operation.
- (b) Show the input and output waveforms.
- (c) Calculate the DC value of the output voltage.

Now after connecting a capacitor in parallel with the load, the output becomes a ripple voltage $\mathbf{V}_{\text{out}} = V_{DC} \pm 0.2$ V

- (d) Calculate the **peak-to-peak ripple voltage**, and from that, the value of the capacitor.
- (e) Calculate the average of the output voltage V_{DC} after connecting the capacitor. Compare this with the DC value determined in 'c' and comment on the difference between these two.

Practice Sheet Rectifiers


DD MM CVV

1. Full-Wave Rectifier, $V_m = 5V$, $f_i = 60\text{ Hz}$, $R = 2\text{k}\Omega$

$$V_{D_o} = 0.7V$$


a) The purpose of a rectifier is to convert AC to DC. The rectifier does this operation by allowing current to flow in 1 direction only.

b)

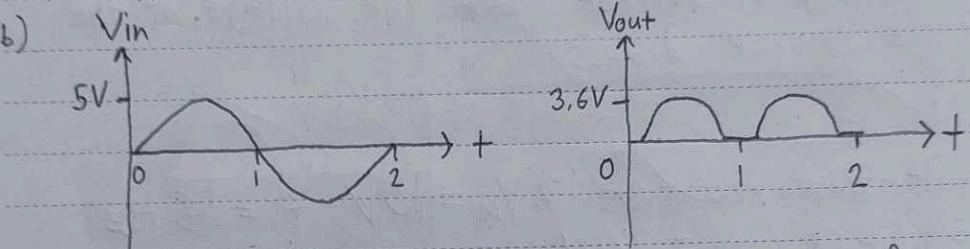

Input Waveform

Output Waveform

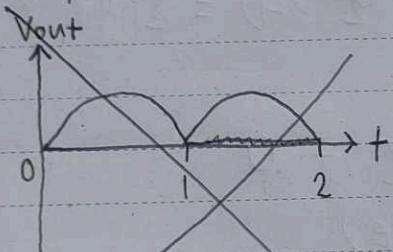

Output Waveform

$$c) V_{DC} = \frac{2}{\pi} V_m - 2 V_{D_o} = \frac{2}{\pi} (5) - 2(0.7) = 1.78V$$

~~$$d) V_{DC} = V_{D_o} = 0.2 + 0.2 = 0.4V$$~~

$$V_{r(p-p)} = \frac{V_p}{f_r X R C} = 0.4$$

$$\Rightarrow \frac{5 - 0.7 \times 2}{120 \times 2 \times C} = 0.4$$

$$\Rightarrow C = 0.0375 \text{ mF}$$

$$1,e) V_{DC} = V_p - \frac{1}{2} V_{r(p-p)} = 3.6 - \frac{1}{2}(0.4) = 3.4V$$

After connecting the capacitor the DC value increased compared to when capacitor was not connected.

This is because of the smoothing effect of the capacitor, which discharges when output of the voltage source is not maximum, and this stops drastic drop of voltage when the voltage of the voltage source drops.

2.

The input of a **Half-wave rectifier** is a sine voltage with peak $V_M = 10V$ and frequency 55 Hz , and output load resistance is $R = 2.5\text{ k}\Omega$. Silicon diodes are used in this circuit for which the forward drop is $V_{D0} = 0.4\text{ V}$.

(a) Calculate the DC value of the output voltage.

Now after connecting a capacitor in parallel with the load, the output becomes a ripple voltage $V_{out} = V_{DC} \pm 0$

V.

(d) Calculate the **peak-to-peak ripple voltage**, and from that, the value of the capacitor.

(e) Calculate the average of the output voltage V_{DC} after connecting the capacitor. Compare this with the DC value determined in 'c' and comment on the difference between these two.

(f) Draw the **Voltage Transfer Characteristic (VTC)** curve

2. Half-Wave rectifier, $V_M = 10V$, $f_i = 55\text{Hz}$,
 $R = 2.5\text{k}\Omega$, $V_{D_0} = 0.4V$

a) $V_{DC} = \frac{V_M}{\pi} - \frac{1}{2} V_{D_0} = \frac{10}{\pi} - \frac{1}{2}(0.4) = 2.98\text{V}$

b) $V_{r(p-p)} = 0\text{V}$


~~$V_{r(p-p)} = V_p - \frac{1}{2} V_r = \frac{V_p}{f_r X R X C} = 0$~~

$\Rightarrow C = \infty$ (infinite)

c) $V_{DC} = V_p - \frac{1}{2} V_{r(p-p)} = (10 - 0.4) - \frac{1}{2}(0) = 9.6\text{V}$

After connecting the capacitor the DC value increased compared to when capacitor was not connected. This is because of the smoothing effect of the capacitor, which discharges when output of the voltage source is not max, and this stops drastic drop of voltage when output of the voltage source drops.

2)f)

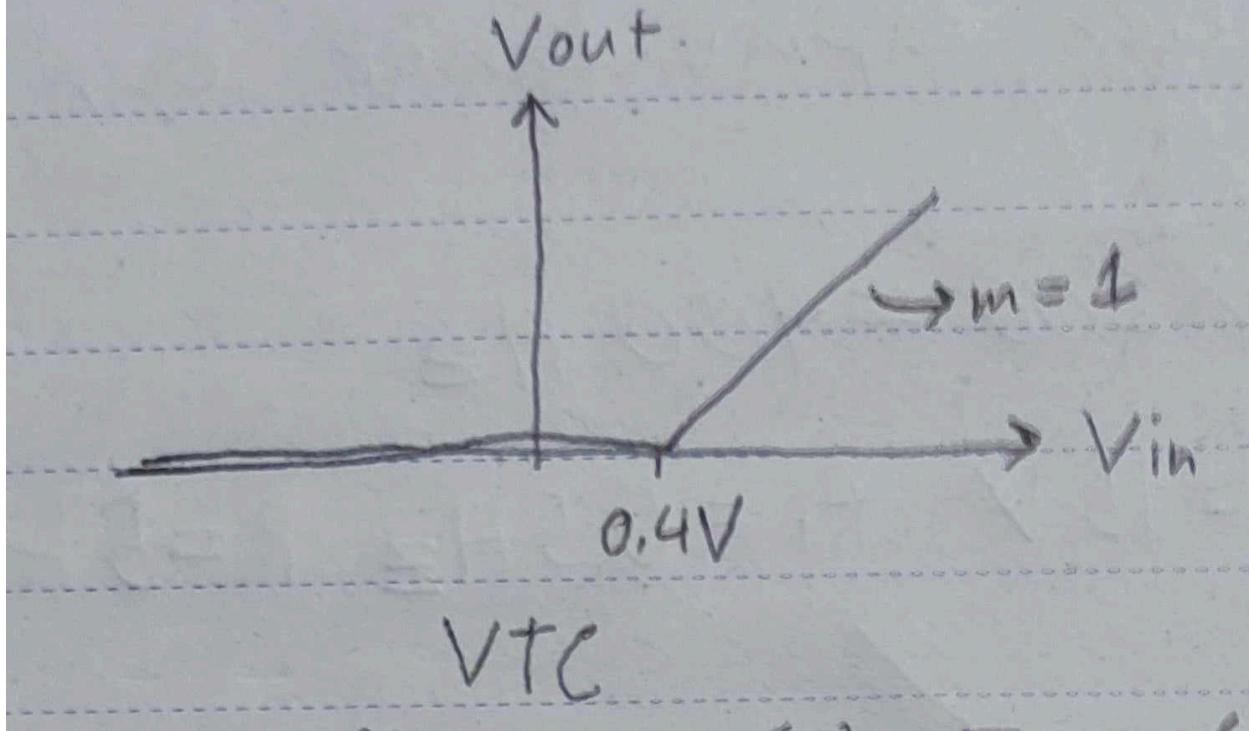

3.

The input of a full-wave rectifier is expressed by, $V_s(t) = 7\sin(400\pi t)$, and output load resistance is $R = 5 \text{ k}\Omega$. Silicon diodes are used in this circuit for which the forward drop is $V_{D0} = 0.3 \text{ V}$.

- (a) Calculate the input and output wave frequency.
- (b) Show the input and output waveforms.
- (c) Calculate the DC value of the output voltage.

Now after connecting a capacitor, $C = 100 \mu\text{F}$ in parallel with the load.


- (d) Calculate the peak-to-peak ripple voltage,
- (e) Calculate the average of the output voltage V_{DC} after connecting the capacitor. Compare this with the DC value determined in 'c' and comment on the difference between these two.
- (f) How can you provide better filtering for the output waves?
- (g) What is the frequency of the Ripple voltage?

3. F W Rectifier, $V_s(t) = 7 \sin(400\pi t)$, $R = 5k\Omega$,


$$V_{D_0} = 0.3V, V_M = 7, f_i = \frac{400}{2} = 200 \text{ Hz}, V_p = 6.4V$$

$$\text{a)} f_i = 200 \text{ Hz}, f_o = 2f_i = 400 \text{ Hz}$$

b) V_{in}

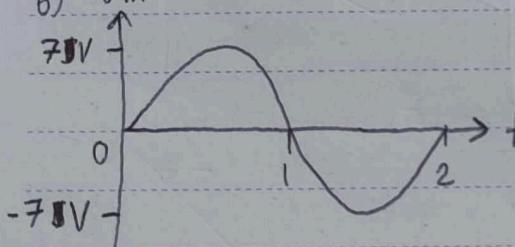

Input waveform

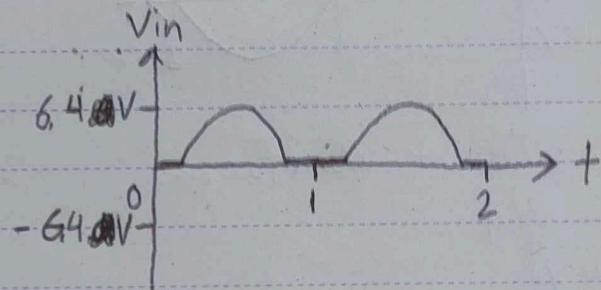

Output waveform

$$\text{c)} V_{DC} = \frac{2}{\pi} V_M - 2V_{D_0} = \frac{2}{\pi}(7) - 2(0.3) = 3.86 \text{ V}$$

$$\text{d)} C = 100 \mu\text{F}, V_r = \frac{V_p}{f_r \times R \times C} = \frac{6.4}{400 \times 5 \times 10^3 \times 100 \times 10^{-6}} = 0.032 \text{ V}$$

$$\text{e)} V_{DC} = V_p - \frac{1}{2} V_r = 6.4 - \frac{1}{2}(0.032) = 6.38 \text{ V}$$

The V_{DC} value is higher and close to the peak voltage after connecting the capacitor due to the capacitor's smoothing effect.

f) For better filtering of output waves a capacitor of higher capacitance can be used.

$$\text{g)} f_r = 2f_i = 2 \times 200 = 400 \text{ Hz}$$


4.

The input of a **Half-wave rectifier** is a **Square** wave voltage with peak $V_M = 15$ V and frequency 0.5 Hz, and output load resistance is $R = 5 \text{ k}\Omega$. Silicon diodes are used in this circuit for which the forward drop is $V_{D0} = 0.7$ V.


- i. Show the input and output waveforms.
- ii. Draw the VTC curve

4. HW rectifier, $V_M = 15V$, $f_i = 50\text{Hz}$, $R = 5k\Omega$,
 $V_{D_0} = 0.7V$

i)

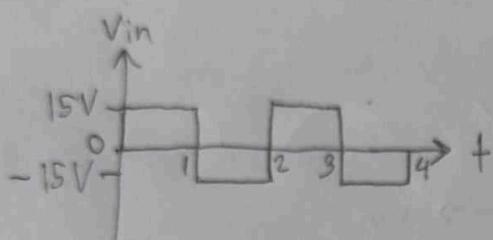


Input Waveform

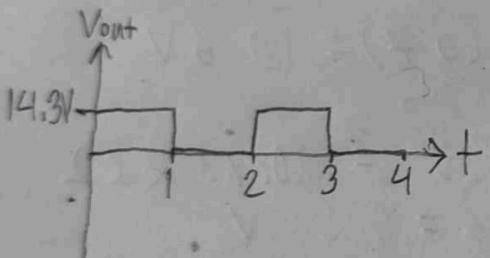

Output Waveform

ii)

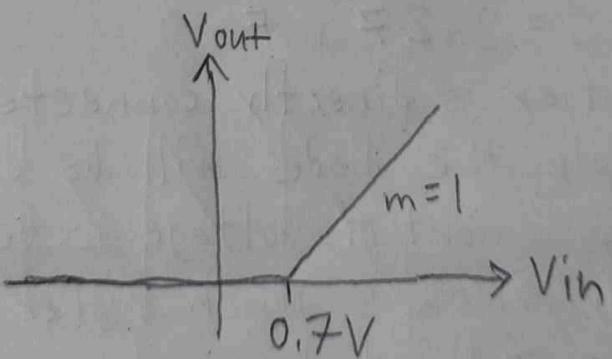

VTC


5.

The input of a **full-wave rectifier** is a **Square** wave voltage with peak $V_M = 15$ V and frequency 0.5 Hz, and output load resistance is $R = 5 \text{ k}\Omega$. Silicon diodes are used in this circuit for which the forward drop is $V_{D0} = 0.7$ V.

- i. Show the input and output waveforms.
- ii. Draw the VTC curve


5. FW, $V_M = 15V$, $V_{D_0} = 0, 7V$

i) V_{in}

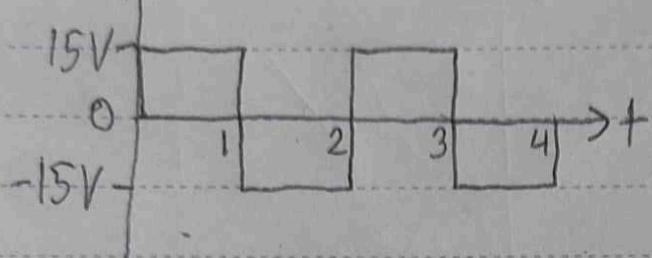


Input Waveform

V_{out}

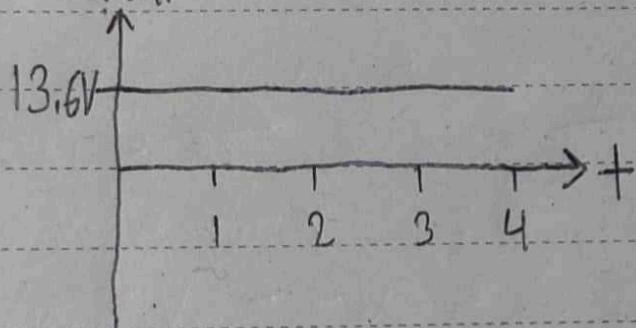


ii)

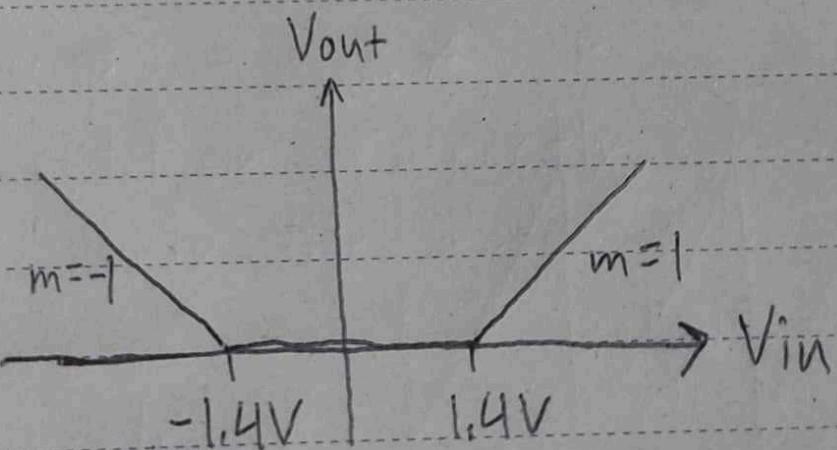


VTC


6.

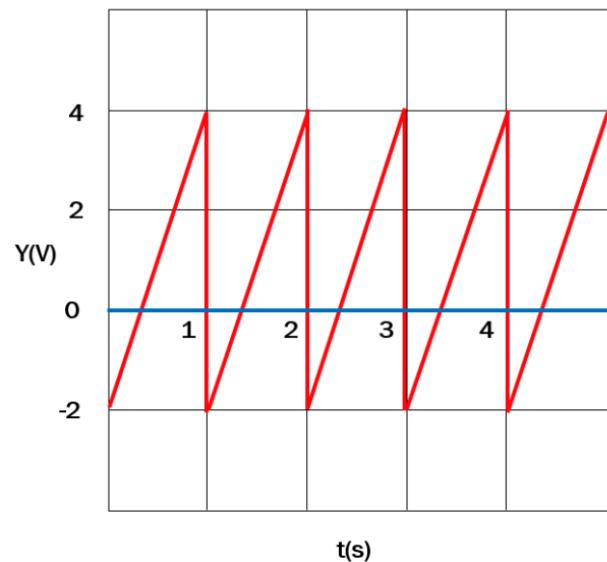


The input of a Half-wave rectifier is exhibited in the Figure above and output load resistance is $R = 5 \text{ k}\Omega$. Silicon diodes are used in this circuit for which the forward drop is $V_{D0} = 0.7 \text{ V}$.

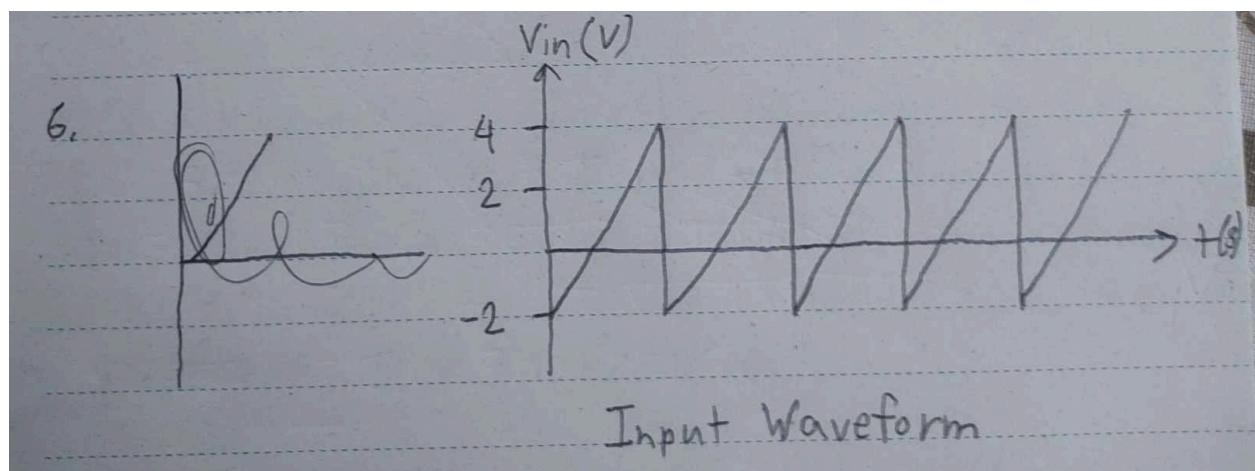- Show the input and output waveforms.
- Draw the VTC curve



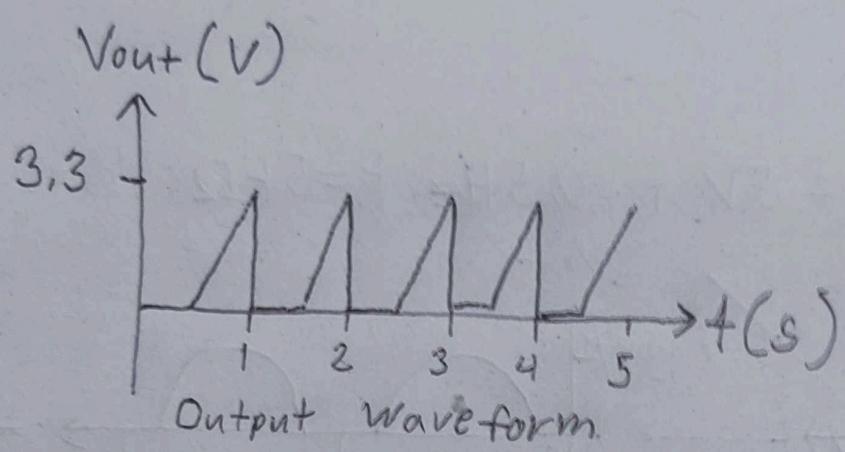


ii)

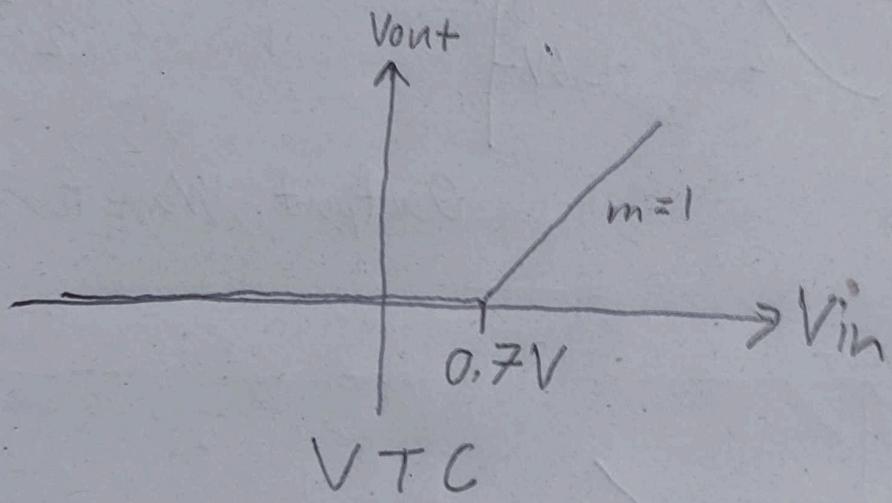

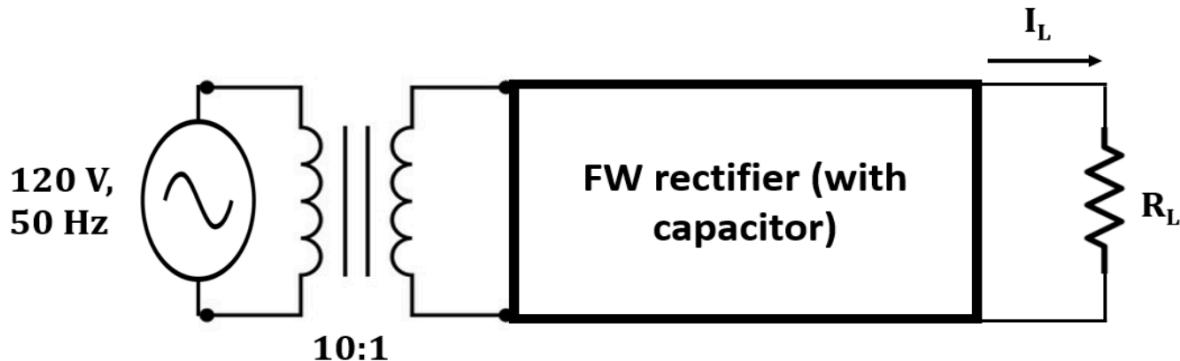7.


A full-wave rectifier is designed to deliver a maximum current $I_L = 120 \text{ mA}$ to the load. The rectifier produces an output with a ripple of 5% of the peak output voltage. An input line voltage of 120 V (peak), 50 Hz is available. A 10:1 step-down transformer is used to transform the supply voltage to 12 V (peak).



- (a) Draw the Voltage Transfer Characteristics of the full-wave rectifier. [2]
- (b) Calculate the peak output voltage. [1]
- (c) Determine the value of the Load Resistor to deliver a maximum load current of 120mA. [2]
- (d) Deduce the value of the Capacitor and the DC average value. [1]
- (e) Assume the transformer is removed and the rectifier is directly connected to the AC power supply line. Discuss the state of the diodes. [Hint: use the Peak Input Value of the rectifier input] [3]

7. FW Rectifier, $V_M = 12V$, $f_i = 50Hz$, $V_{D_0} = 0.7V$ (Assumed)

a)

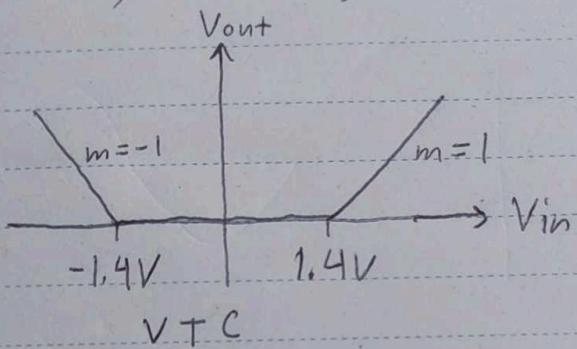

$$b) V_p = V_M - 2V_{D_0} = 12 - 2(0.7) = 10.6V$$

$$c) I_L = 120mA$$

$$I_L = \frac{V_p}{R_L} \Rightarrow R_L = \frac{V_p}{I_L} = \frac{10.6}{120 \times 10^{-3}} = 0.0883k\Omega$$

$$d) V_r = \frac{5}{100} \times V_p = 0.05 \times 10.6 = 0.53V$$

$$V_{DC} = V_p - \frac{1}{2} V_r = 10.6 - \frac{1}{2}(0.53) = 10.335V$$

$$V_r = \frac{V_p}{f_r R_C} \Rightarrow 0.53 = \frac{10.6}{100 \times 0.0883 \times C}$$
$$\Rightarrow C = 2.27mF$$

e) If the rectifier is directly connected to the AC power supply the diodes will be damaged because a huge amount of voltage is being supplied by the AC supply which is much higher than the voltage ratings of the diodes used.