

Mosfet

S model (switch model) (ideal model)

$$V_{GS} = V_G - V_S$$

$$\text{i. } V_{GS} \geq V_T \text{ (ON)}$$

$$\text{ii. } V_{GS} \leq V_T \text{ (OFF)}$$


S model (switch model) (ideal model)

$$\rightarrow C=0, V_{GS} < V_T \text{ (OFF)}$$

$$I_S^0 \text{ & } I_{DS} = 0$$



$$\rightarrow C=1, V_{GS} \geq V_T \text{ (ON)}$$

$$I_S^0 \rightarrow V_{DS} = 0$$

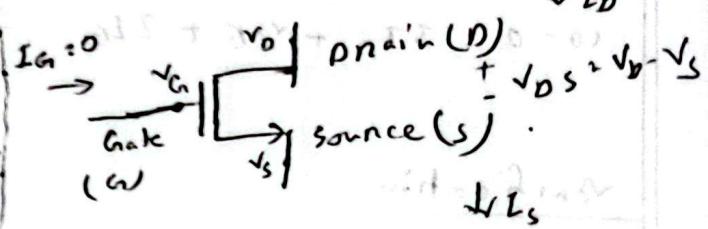


$$I_{DS} = I_D = I_S$$


DC load approach

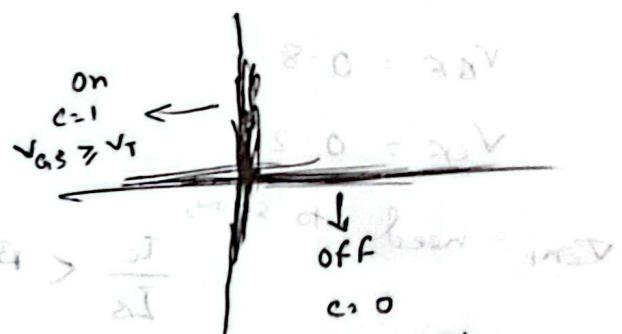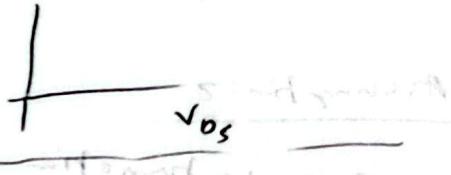

NAND - 2

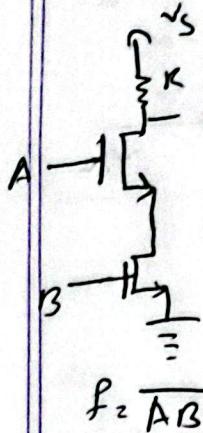


NOT - 2

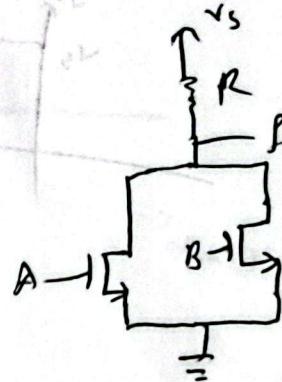


NOT Gate

(Inverter)

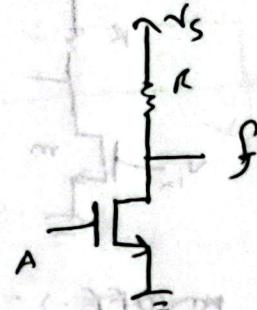



$\Sigma n - 1$:

$$f = (A + B)C$$

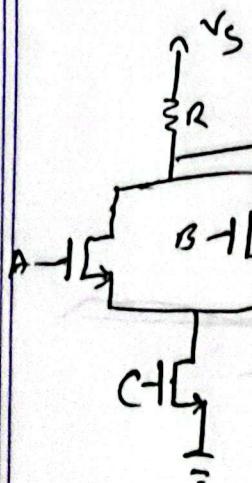

$$\overline{(A + B)C} = (A + B)\overline{C}$$

VTC of Inverter (NOT Gate)

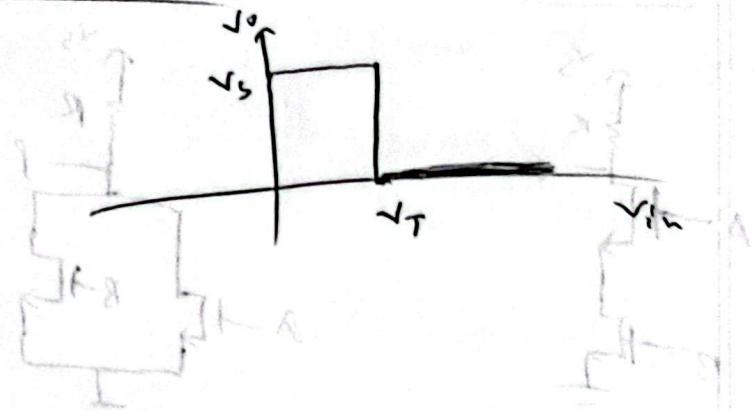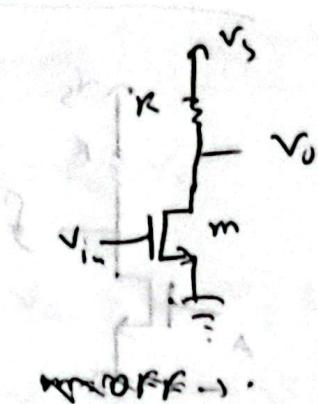


$V_{in} < V_T, m = OFF$






$$\frac{I_D}{I_S}$$

$V_{in} \geq V_T, m = ON$

$$\frac{I_D}{I_S}$$

VTC of NAND2 Gate

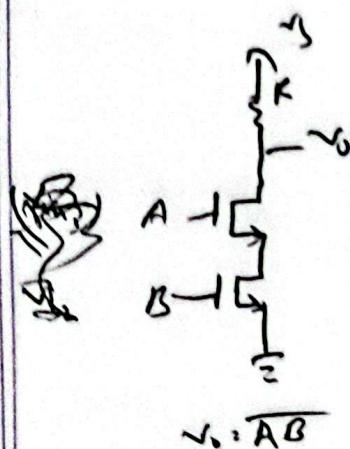

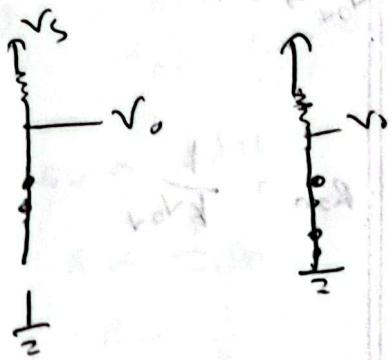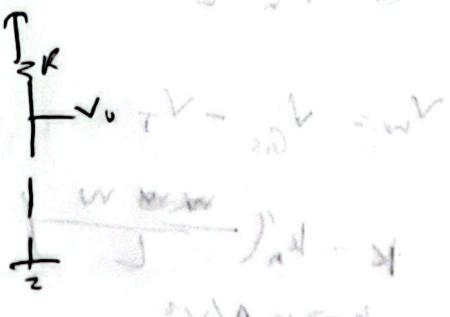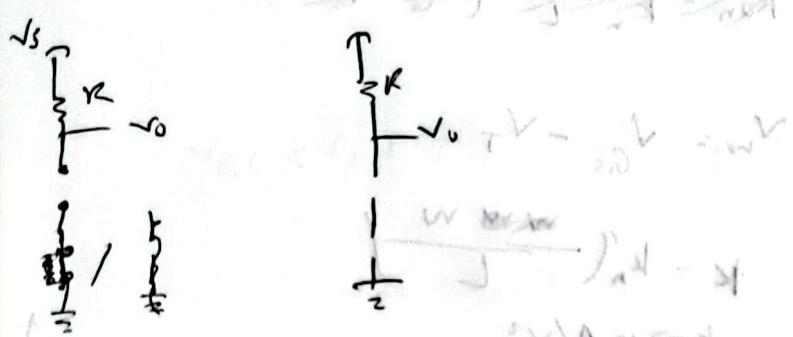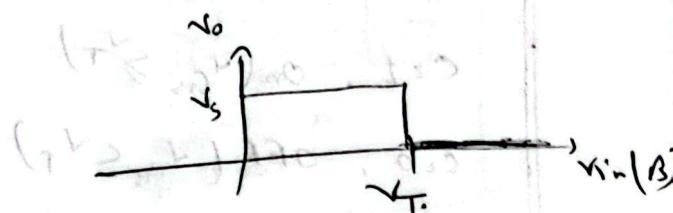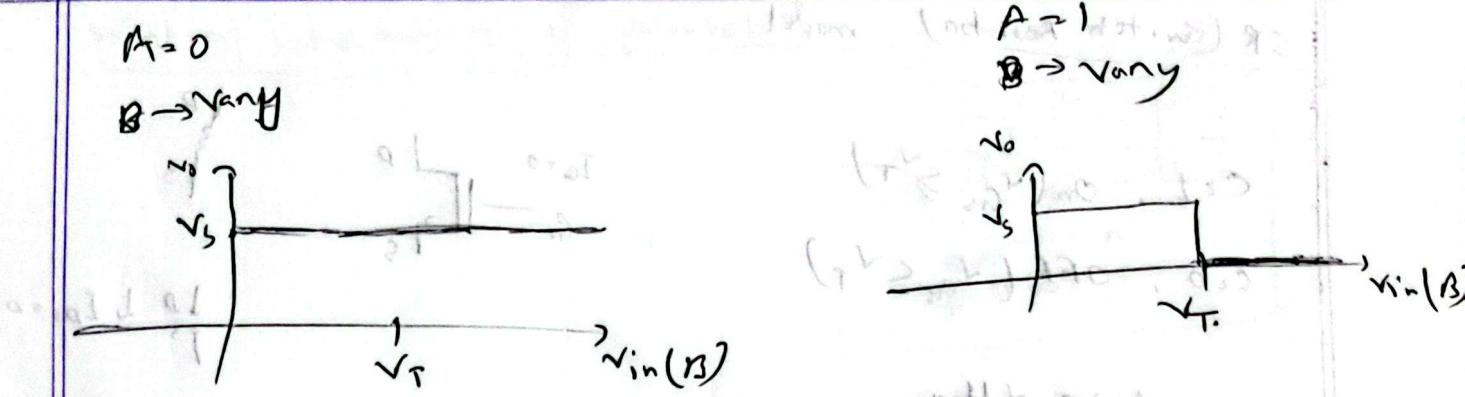

$Hv \rightarrow N \sigma R-2,3$ Grade
 $v_0 < 2eV$ then formed $> 2eV$
 $v_0 > 2eV$ not filtered

$v_0 < 2eV$ not filtered



26/8/25

25)

SR (switch resistor) model

$C = L$, On ($\sqrt{G_{ds}} \geq \sqrt{T}$)

C.O., OFF ($\sqrt{G_{ds}} < \sqrt{T}$)

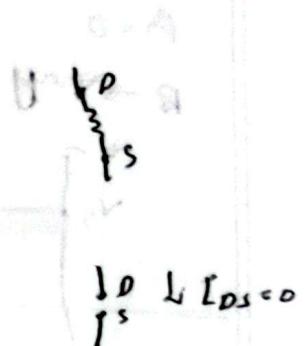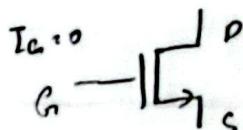

$V_{ov} \rightarrow$ Overdrive voltage

$$R_{on} = \frac{W}{k' L} \left(\sqrt{G_{ds}} - \sqrt{T} \right)$$

$$R_{on} = \frac{1}{k V_{ov}}$$


$$V_W = \sqrt{G_{ds}} - \sqrt{T}$$

$$k = k_n' \left(\frac{W}{L} \right)$$

$$k \rightarrow \text{mA/V}^2$$


$V_{ov} \propto$ Channel width

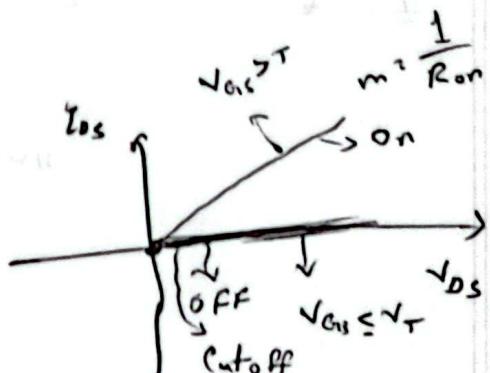SR valid till $(\sqrt{V_{ds}} < \sqrt{V_{ov}})$



Invalid on fails when $\sqrt{V_{ds}} \geq \sqrt{V_{ov}}$

Working mechanism of mosfet

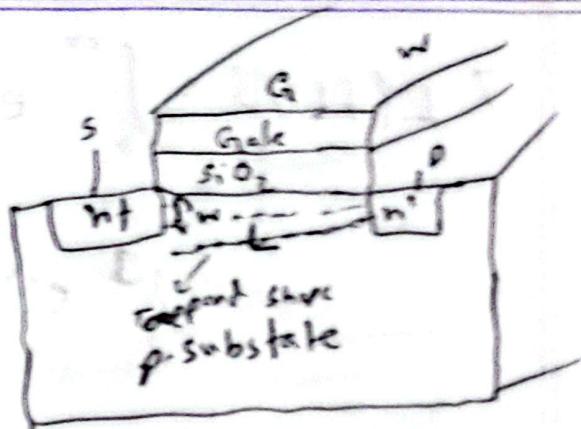

$$V_{GS} \geq V_T, \text{ on} \begin{cases} \text{Triode } (V_{DS} < V_S) \\ \text{Saturation } (V_{DS} \geq V_{OV}) \end{cases} \quad V_{OV} = V_{GS} - V_T$$

$$V_{GS} < V_T, \text{ off}$$

$V_{DS} \propto \text{width}$

$$R \propto \frac{1}{\text{width}}$$

$$V_{DS} = V_D - V_S$$

$$R \propto \frac{1}{A}$$


$$V_{OV} = V_{GS} - V_T$$

$$R \propto \frac{1}{V}$$

$$\therefore V_G - V_S - V_T$$


$$R \propto L$$

$$\sim V_G - V_T$$

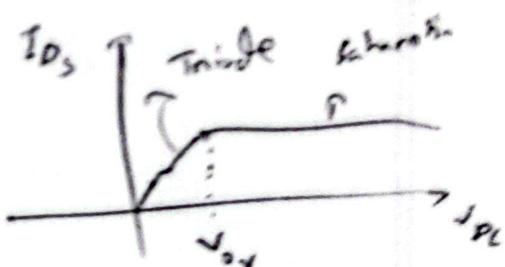

31/8/25

251

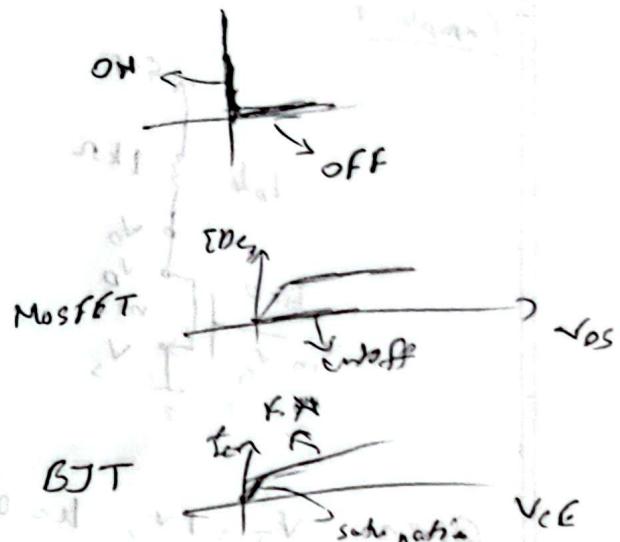

operating Region	condition	state eqn.
cutoff	$V_{GS} < V_T$	$I_{DS} = 0$
Triode	$V_{GS} > V_T$ $V_{DS} < V_{OV}$	$I_{DS} = k [V_{OV} - V_{DS} - \frac{1}{2}V_{DS}]$
Saturation	$V_{GS} \geq V_T$ $V_{DS} \geq V_{OV}$	$I_D \geq \frac{1}{2}kV_{OV}^2$


$$k = k'_n \left(\frac{\omega}{L} \right)$$

$$\hookrightarrow \text{unit} \rightarrow \text{mA/V}^2$$

$$V_{OV} = V_{GS} - V_T$$

$$V_{OV} = V_{GS} - V_T$$

Example - 1

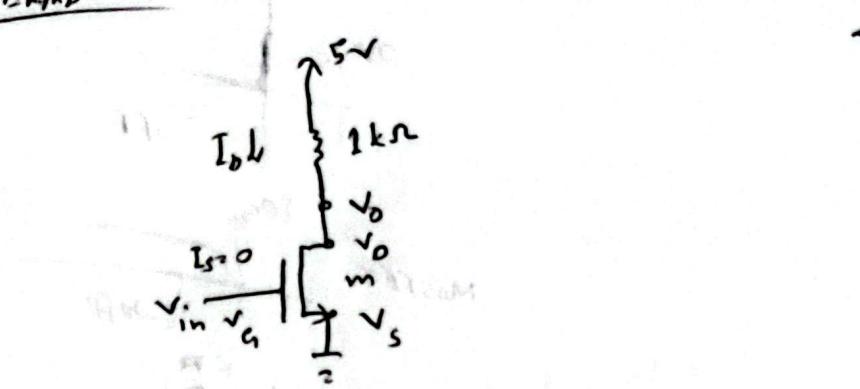

saturation.

Given: $v_T = 1V$, $m = 0.5 \text{ mA/V}^2$, $v_{in} = 2V$.

saturate I_D and v_o .

Ans.

Assumption - 1,

$m \rightarrow \text{saturation}$

$$v_{DS} = v_G - v_S \geq v_T$$

$$v_{DS} \geq v_T$$

$$v_{GS} = v_G - v_S$$

$$\geq 2 - 0$$

$$\approx 2$$

$$v_T = 1V$$

$$v_{DS} = v_D - v_S = v_D$$

$$v_{DS} \geq 2V$$

$$v_{DS} \geq 1V$$

$$v_{DS} \leq 2V$$

$$v_{DS} \leq 1V$$

$$\left(\frac{w}{l}\right) \cdot 2V = 2$$

$$w/l = 1 \rightarrow w = l$$

$$V_{ov} = V_{as} - V_T$$

$$= 2 - 1$$

$$= 1$$

From equation,

$$I_{DS} = \frac{1}{2} k V_{ov}^2 = \frac{1}{2} \times 0.5 \times (1)^2 = 0.25 \text{ mA} \quad (i)$$

Omms law on $1\text{k}\Omega$,

$$I_{DS} = \frac{5 - V_D}{1}$$

$$\Rightarrow I_{DS} = 5 - V_D \quad \text{infimum}$$

$$\Rightarrow 0.25 = 5 - V_D$$

$$\therefore V_D = 4.75$$

$$V_{DS} = 4.75 \text{ V}$$

Verification

$$V_{as} = 2 \geq V_T = 1 \quad \checkmark$$


$$V_{DS} = 4.75 \geq V_{ov} = 1 \quad \checkmark$$

Assumption - i) is correct

$$I_D = 0.25 \text{ mA}$$

$$V_D = V_D = 4.75$$

Example 2:

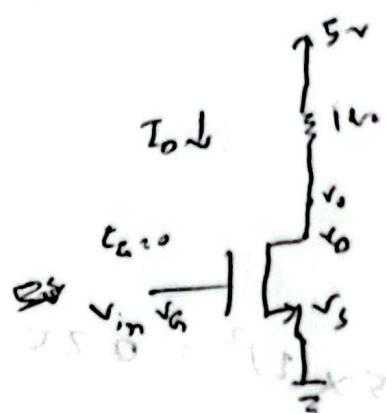

$$v_T = 1V$$

$$k = 0.5 \text{ mA/V}^2$$

$$V_{in} = 5V$$

Assumptions:

• I_D and v_o ?

Ans: Assumption is,
→ saturation

$$\begin{aligned} v_{GS} &> v_T \\ v_{DS} &> v_{ov} \end{aligned}$$

$$v_G = V_G - v_S = 5 - 0 = 5$$

$$v_T = 1V$$

$$v_{DS} = v_D = 5V \rightarrow v_S = v_D - 0 = v_D$$

$$v_{ov} = v_{GS} - v_T = 5 - 1 = 4V$$

From eqn: $v_o = v_D - v_S$

$$\begin{aligned} I_{DS} &\approx \frac{1}{2} k(v_{ov})^2 \\ &= \frac{1}{2} \times 0.5 \times (4)^2 \\ &= 4 \text{ mA} \quad \dots (i) \end{aligned}$$

Ohm's law or $I = \frac{V}{R}$

$$I_{DS} \approx I_D = \frac{5 - v_D}{2}$$

$$\Rightarrow I_{DS} = 5 - v_D$$

$$\Rightarrow 4 = 5 - v_D \quad \dots (ii)$$

$$\Rightarrow v_D = 1V$$

$$v_{DS} = v_D = 1V$$

Verification:

$$v_{GS} = 4V \geq v_T = 1V \quad \checkmark$$

$$v_{DS} = 1V \neq v_{ov} = 4V \quad \times$$

Assumption wrong

Assumption-II

m = Triode

$$\begin{aligned} \sqrt{V_{GS}} &\geq \sqrt{T} \\ \sqrt{V_D} &< \sqrt{V_{OV}} \end{aligned}$$

$$\sqrt{V_{GS}} = \sqrt{V_g - V_s} = 5 - 0 = 5$$

$$\sqrt{T} \approx 1$$

$$\sqrt{V_{DS}} = \sqrt{V_D - V_S} = \sqrt{V_D - 0} = \sqrt{V_D}$$

$$V_{OV} = \sqrt{V_{GS}} - \frac{\sqrt{T}}{T} = 5 - 1 = 4$$

From eqn.

$$I_{DS} = k \left[\sqrt{V_{GS}} \sqrt{V_{DS}} - \frac{1}{2} V_{DS}^2 \right]$$

$$\Rightarrow I_{DS} = 0.5 \left[4 \sqrt{V_D} - \frac{1}{2} V_D^2 \right]$$

$$\Rightarrow I_{DS} = 2\sqrt{V_D} - 0.25 V_D^2 \dots (i)$$

Ons Zew un 16n

$$I_{DS} \approx \frac{5 - \sqrt{V_D}}{1}$$

$$\Rightarrow I_D = 5 - \sqrt{V_D} \dots (ii)$$

from (i), (ii)

$$2\sqrt{V_D} \approx 0.25 \sqrt{V_D}^2 \Rightarrow 5 - \sqrt{V_D}$$

$$\therefore \sqrt{V_D} = 20V \quad | \quad \sqrt{V_D} = 2V$$

$$\sqrt{V_{GS}} = \sqrt{V_D} = 2V$$

Verification:

$$\sqrt{V_{GS}} = 5 \geq \sqrt{T} = 1 \quad \checkmark$$


$$\sqrt{V_{DS}} = 2V < \sqrt{V_{OV}} = 4V \quad \checkmark$$

Assumption-II comes

$$I_D = 5 - \sqrt{V_D} = 5 - 2 = 3mA$$

$$V_o = V_D = 2V$$

Example - 2 :

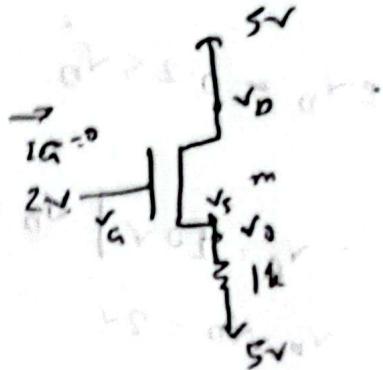

$$V_T = 1V$$


$$V_D = 2V \quad V_S = 0V \quad I_D = 0A$$

$m = \text{cutoff}$


$$I_D = 0$$

$$V_D = 5V$$

no voltage difference

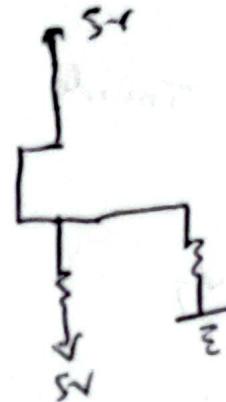

Example - 4:

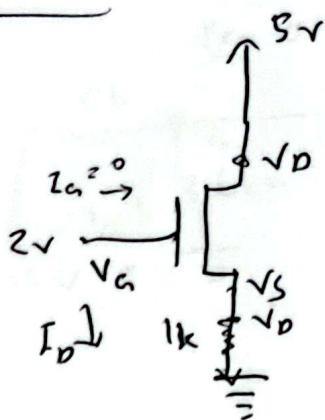

$$V_{DS} = V_D - V_S$$

$$V_T = 1V$$

$$k = 4 \text{ mA/V}^2$$

Calc V_o , I_o

$$V_{DS} \approx V_{GS} \approx V_T$$

$$= 2 - V_S - 1$$

$$= 1 - V_S$$

From eqn

$$I_{DS} = \frac{1}{2} k(V_{DS})^2$$

$$\Rightarrow I_{DS} = \frac{1}{2} \times 4 \times (1 - V_S)^2$$

$$\Rightarrow I_{DS0} = 2(1 - 2V_S - V_S^2)$$

$$\Rightarrow I_{DS} = 2 - 4V_S + 2V_S^2 \quad \dots(i)$$

Ons 1m on 1f n

$$I_{DS} = \frac{V_S - 0}{1}$$

$$\Rightarrow I_{DS} = V_S - 0$$

$$\therefore I_{DS} = V_S \dots(ii)$$

(i), (ii).

$$2 - 4V_S + 2V_S^2 = V_S$$

$$\Rightarrow 2V_S^2 - 5V_S + 2 = 0$$

$$\therefore V_S = 2 \quad | \quad V_S = 0.5$$

$$V_G = V_a - 3 = 2 - V_S$$

$$V_T = 1V$$

$$V_{DS} = V_D - V_S = 5 - V_S$$

~~Approximation~~

$$V_{GS} = 2 - 0.5V = 1.5V$$

$$V_T \approx 1$$

$$V_{DS} = 5 - V_S = 5 - 0.5 = 4.5V$$

$$V_0 \approx 1 - V_S \approx 0.5$$

~~Ansatz~~

$$V_{GS} \gg V_T$$

$$V_{DS} \gg V_{OV}$$

Assumption correct

$$V_0 = V_D = 0.5V$$

$$I_D = V_S = 0.5mA$$

$$Q = 0.5mA$$

$$r_i = 2V = 20\Omega$$


$$(i) \quad (ii)$$

Startups

$$V_{GS} = V_{DS} = 0$$

$$V_0 = 0.5V$$

Example 6:

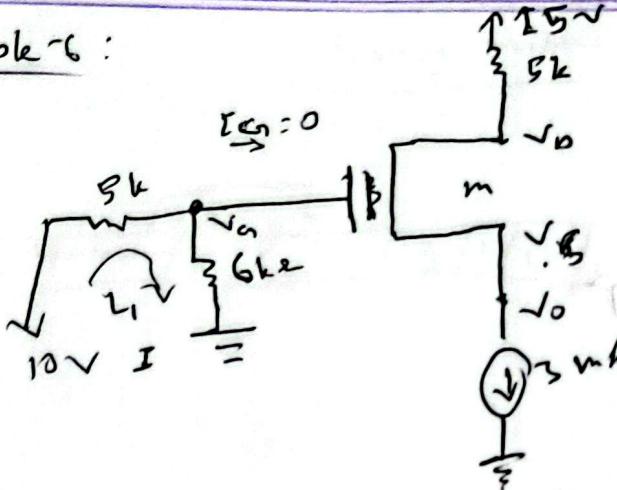

ohms law on $5k\Omega$,

$$\frac{V_D - V_S}{5} = 1$$

$$V_{DS} = \frac{6 \times 10}{11}$$

$$= 5.45$$

Assumption:

$$V_T = 1V$$

$$k = 5mA/V^2$$

$$\text{calc } V_0, I_{D0}$$

$$V_{GS} = 5.45 - V_S$$

$$V_T = 1V$$

$$V_{DS} = V_D - V_S$$

$$V_{DS} = V_S - V_T$$

Ans Assumption-1, $m \rightarrow$ saturation

$$\boxed{\begin{aligned} V_{GS} &\gg V_T \\ V_{DS} &\geq V_{OV} \end{aligned}}$$

$$V_{GS} = V_G - V_S$$

$$V_{DS} = 3$$

ohms law on $5k\Omega$

$$V_{DS} = \frac{15 - V_D}{5}$$

$$3 = \frac{15 - V_D}{5}$$

$$\therefore V_D = 0$$

KVL on L_1 :

$$10 = 0 + 5I + 6E$$

$$\therefore Z = \frac{10}{11}$$

Firm equations

$$I_{ns} = \frac{1}{2} k (\bar{v}_s)^2$$

$$\Rightarrow 3 = \frac{1}{2} \times 0.5 \times (\bar{v}_s)^2$$

~~Roots~~ \approx

$$\Rightarrow 6 = 5(4.45 - \bar{v}_s)^2$$

$$5[\bar{v}_s^2 - 2 \times 4.45 \bar{v}_s + (4.45)^2] = 6$$

$$\bar{v}_s = 1 / \bar{v}_s = 1$$

$$\bar{v}_{ds} = 5.45 - 1 = 4.45$$

$$\bar{v}_{rs} = 4.45 - 1$$

$$= 3.45$$

$$\bar{v}_{bs} = \bar{v}_d - \bar{v}_s = 0 - 1 = -1$$

$$\Sigma = 0.5$$


Verification

$$\bar{v}_{as} = 4.45 - \bar{v}_r$$

$$\bar{v}_{bs} = -1 \neq \bar{v}_{as}$$

i. Why?

$$\frac{0.1}{0.1} = 1 \neq -1$$

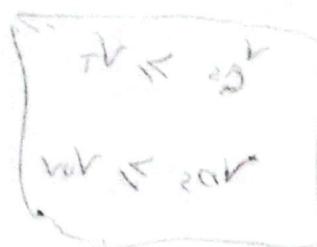


$$\bar{v} - \bar{v} = 2\bar{v}$$

21/9/25

251

Ex. 1:

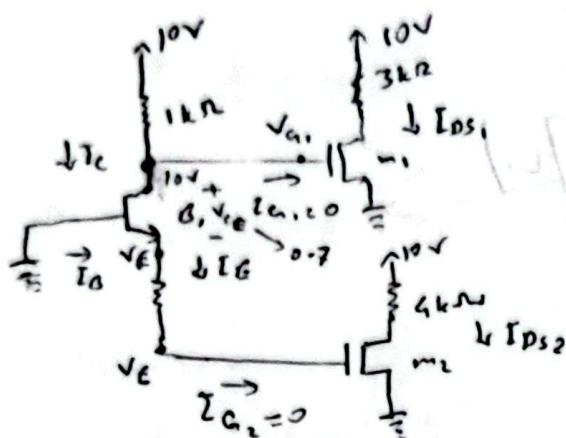

$$V_T = 1V$$

$$k = 5mA/V^2$$

$$\beta = 100$$

$$\alpha = 0.99$$

1. calculate I_C, I_B, I_E

2. calculate I_{D_s1}

3. calculate I_{D_s2}

Sln.

2. $\beta \rightarrow \text{cutoff}$

$$I_B = I_D, I_C = 0$$

$$I_B = I_C = I_E = 0$$

$$\therefore V_{CE} = V_C - V_T = 0.7 \text{ [best case]}$$

$$0.7 = 10 - V_T$$

$$\therefore V_T = 9.3$$

2. $V_s \rightarrow \text{saturation}$

$$\boxed{\begin{aligned} V_{GS} &\geq V_T \\ V_{DS} &\geq V_{UR} \end{aligned}}$$

$$I_{DS} = k * 5mA * \frac{1}{2} k * V_{DS}^2$$

$$V_{GS} = V_{G1} - V_S$$

$$= 10 - 0$$

$$= 10$$

$$V_T = 1V$$

$$V_{DS1} = V_D - V_{S1} = V_D - 0$$

$$= V_D$$

$$V_{DS1} = V_{G1} - V_T = 10 - 1 = 9V$$

From eqn.

$$I_{D_s1} = \frac{1}{2} k (V_{DS1})^2$$

$$\Rightarrow I_{D_s1} = \frac{1}{2} \times 5 \times (9)^2 = 202.5mA$$

Ohms law on $3\text{k}\Omega$

$$\Rightarrow I_{DS1} = \frac{10 - V_{D1}}{3}$$

$$\therefore 20\text{k}\Omega \cdot 5 = \frac{10 - V_{D1}}{3}$$

$$V_{D1} = 10 - (20 \cdot 5 \times 3)$$

$$= -597.5 \text{ mA}$$

$$V_{DS1} = V_{D1} = -597.5 \text{ V}$$

Verification:

$$V_{GS1} \approx 10 > V_T \approx 1 \text{ V}$$

$$V_{DS1} = -597.5 \neq V_{DS} = 9 \text{ V}$$

\therefore Assumption wrong

Assumption 2: $V_D = 0 \text{ V}$

\rightarrow Triode

$$\begin{cases} V_{GS} \geq V_T \\ V_{DS} \leq 0 \text{ V} \end{cases}$$

$$I_{DS} = k [V_{DS} \cdot V_{GS} - \frac{1}{2} V_{DS}^2]$$

$$V_{GS1} = V_{GS} - V_{S1} = 10 - 0 = 10 \text{ V}$$

$$V_{T2} = 1 \text{ V}$$

$$V_{DS1} = V_{D1} - V_{S1} = V_{D1} = 0$$

$$V_{DS1} = V_{GS1} - V_T = 10 - 1 = 9 \text{ V}$$

From eqn:

$$I_{DS1} = k [V_{DS1} \cdot V_{GS1} - \frac{1}{2} V_{DS1}^2]$$

$$I_{DS1} = 5 [9V_{D1} - \frac{1}{2} V_{D1}^2]$$

$$I_{DS1} = 45V_{D1} - 2.5V_{D1}^2$$

Ohms law on $3\text{k}\Omega$

$$I_{DS1} = \frac{10 - V_{D1}}{3} \quad \dots (ii)$$

(i), (ii),

$$\frac{10 - V_{D1}}{3} = 45V_{D1} - 2.5V_{D1}^2$$

$$V_{D1} = 18.06 \text{ V} \quad V_{D1} = 0.072 \text{ V}$$

\times

$$\sqrt{V_{AS}} = \sqrt{V_D} = 0.072V$$

Verification


$$\sqrt{V_{AS}} = 10 > \sqrt{V_T} = 1V$$

$$\sqrt{V_{DS}} = 0.072 < V_{DD} = 5V$$

\therefore Assumption correct

$$I_{DS1,2} = \frac{10 - 0.072}{3} mA$$

Ex-2 :

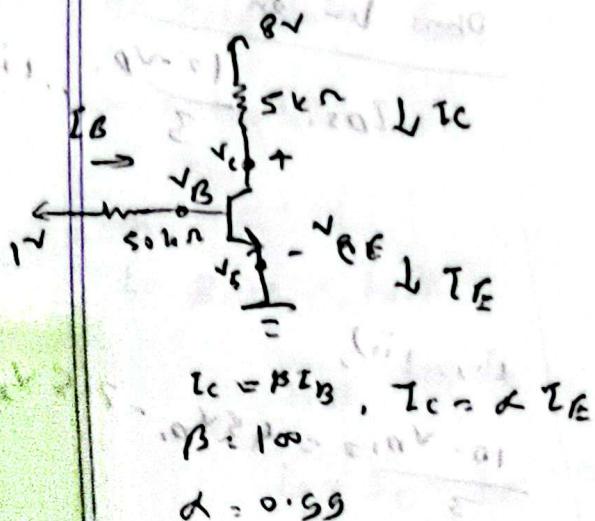

$$I_C = \beta I_B, I_C \approx I_E$$

$$\beta = 100$$

$$\alpha = 0.99$$

$$\sqrt{V_{BE}} (\text{active}) = 0.7$$

$$\sqrt{V_{BE}} (\text{sat}) = 0.8V$$

$$\sqrt{V_{EE}} (\text{sat}), 0.2V$$

calculate I_B, I_c, I_E ?

* calculate I_B, I_c, I_E ?

Ans: Assumptions - 1.

Active

$$I_B, I_c, I_E > 0$$

$$\sqrt{V_{CE}} \geq 0.2V$$

$$\sqrt{V_{BE}} = 0.7V$$

$$\Rightarrow V_B - V_C = 0.7$$

$$\Rightarrow V_B = 0.7$$

$$\sqrt{V_B} = 0.7$$

Ohms law on $50k\Omega$

$$\frac{1 - \sqrt{V_B}}{50} = I_B$$

$$I_B = \frac{1 - 0.7}{50} = 0.006 mA$$

$$I_E = I_B + I_C$$

$$I_C = \beta I_B \cdot 100 \times 0.006 = 0.6 mA$$

$$I_E = 0.006 + 0.6 = 0.606 mA$$

Ohns low on 52n:

$$I_C = \frac{8 - \sqrt{c}}{5}$$

$$\Rightarrow 0.6 = \frac{g - v_c}{5}$$

$$\therefore V_c = 8 \left(5 \times 10^{-6} \right)$$

$$= 5\sqrt{}$$

$$\sqrt{C_E} = \sqrt{C} - \sqrt{R}$$

~5.0

- 5 -

Von: Sicht...

$$I_B = 0.006,$$

$$I_C = 0.6$$

$$T_E = 0.606 > 0$$

$$\sim_{\mathcal{R}} = 5 \rightarrow 0.2$$

Assumption 1 correct

$$T_B = 0.006 \text{ ms}$$

and

76.06 m

Ex-3:

$$f = \overline{c \cdot (A+B)} \cdot (A + \overline{B} + c)$$

