

Assignment 2 - CSE251  
Total Marks: 170

1. Op-Amp Open Loop :  
Solve Problem No: 2 , 4, 5, 7, 10, 12, 16 from here [\[click here\]](#)
  
2. Op-Amp Open Loop :  
Solve Problem No: 1 (IV), 2, 4, 10, 14 from here [\[click here\]](#)
  
3. Diode :  
Solve Problem No: 8, 9, 15, 16 from here [\[click here\]](#)  
Solve Problem No: 1 (II), 3 from here [\[click here\]](#)