

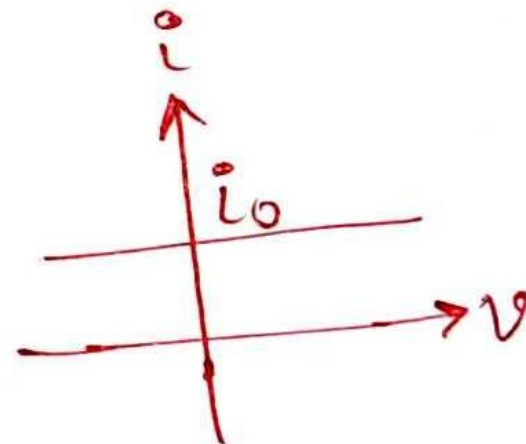
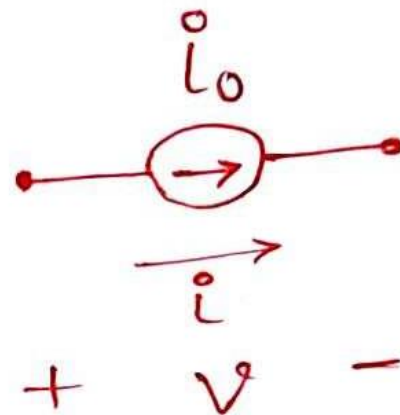
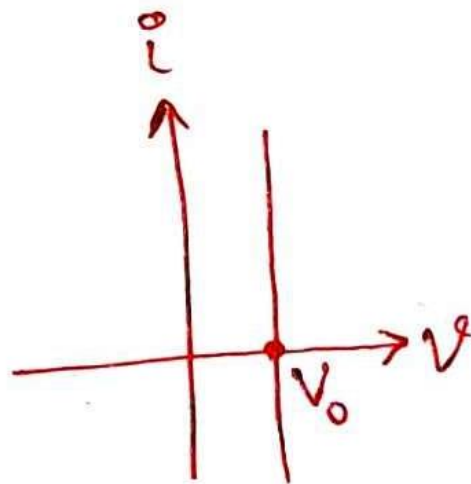
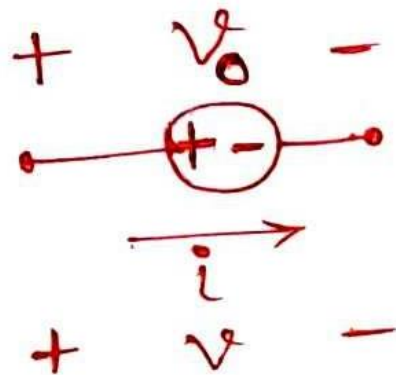
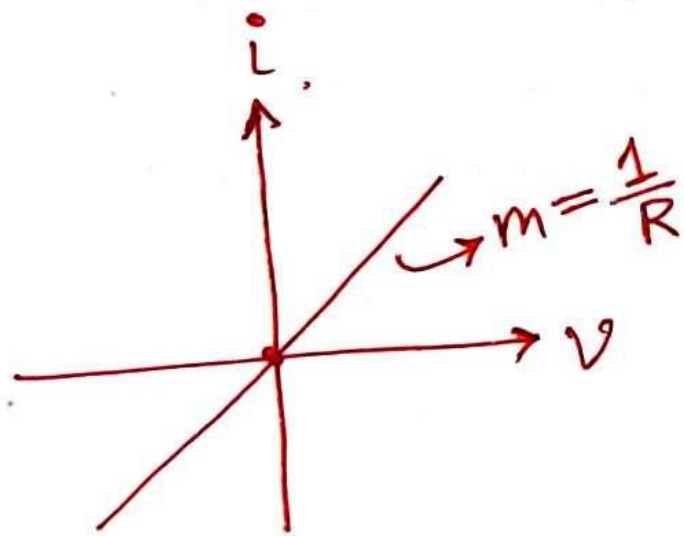


IV Characteristics

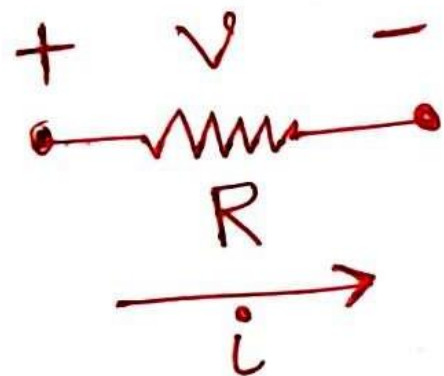


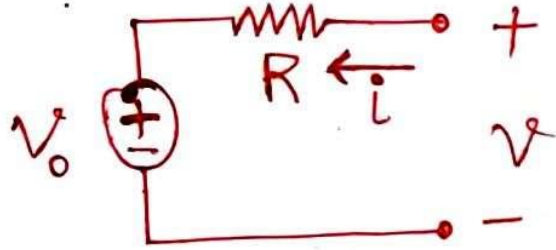


$$i = \left(\frac{1}{R}\right)v - \frac{V_0}{R}$$

This is equivalent to,

$$y = mx + c$$

where, $m = 1/R$, $c = -\frac{V_0}{R}$

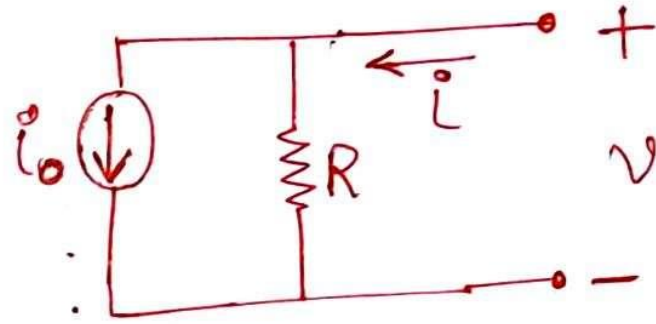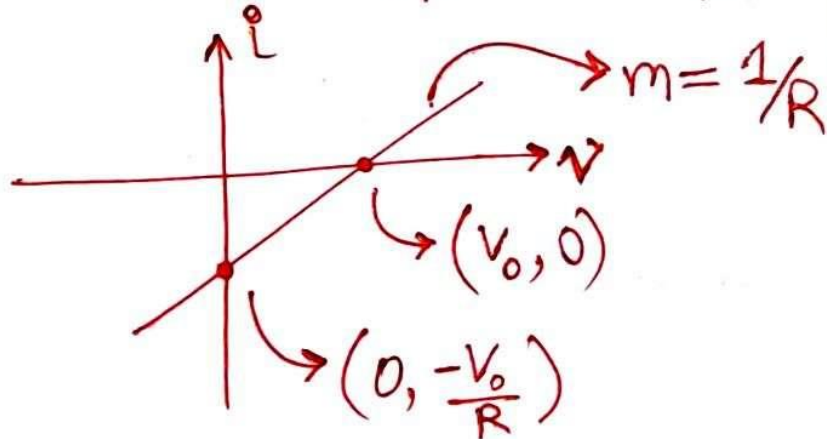


$$i = \left(\frac{1}{R}\right)v + i_0$$

This is equivalent to,

$$y = mx + c$$

where, $m = 1/R$, $c = i_0$

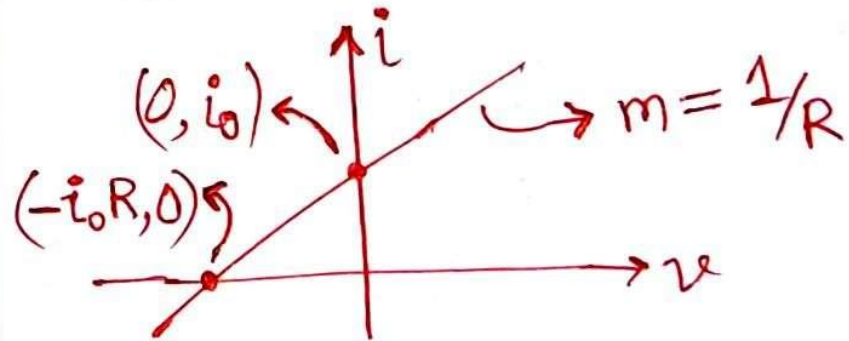

Diode

ideal diode

if $V_D > 0$,

ON/Forward Bias

hence, short ckt


$$i_D > 0, V_D = 0$$

if $V_D \leq 0$,

OFF/Reverse Bias

hence, open ckt

$$i_D = 0.$$


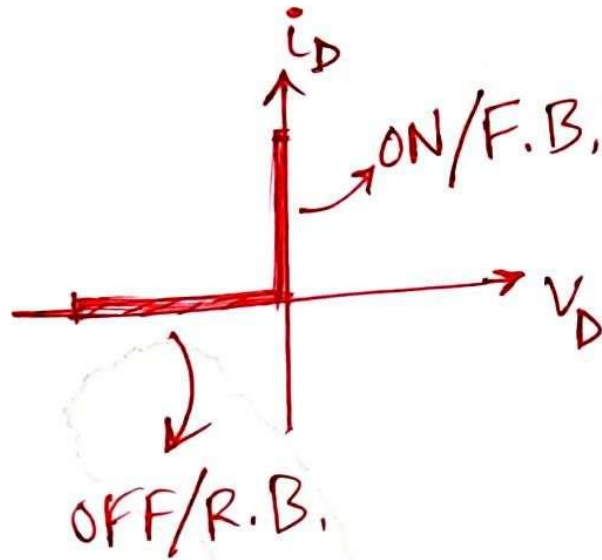


Verification conditions
in method of assumed
state for ideal diode,

$$\text{ON} \rightarrow i_D > 0$$


$$\text{off} \rightarrow V_D \leq 0$$

Real Diode

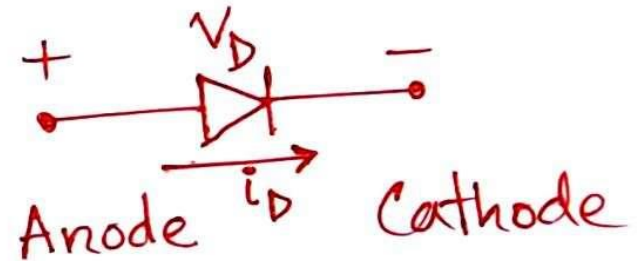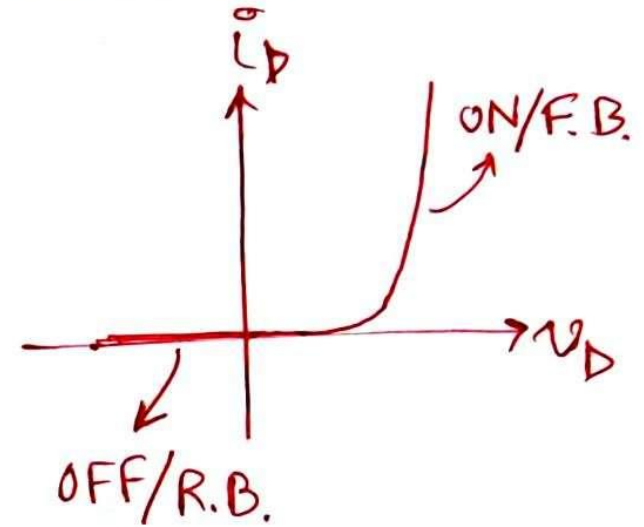


CVD+R model

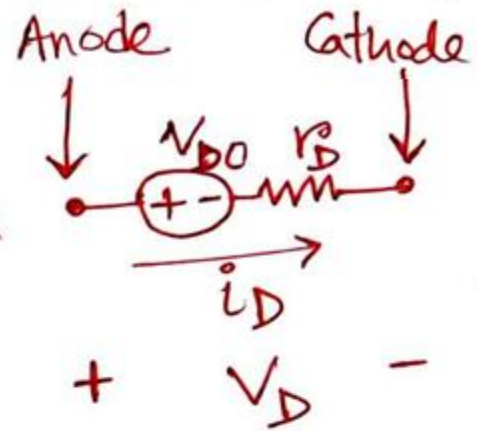ON/F.B. \rightarrow if $V_D > V_{D0} \rightarrow$ replace with




$$V_D = V_{D0} + i_D r_D$$

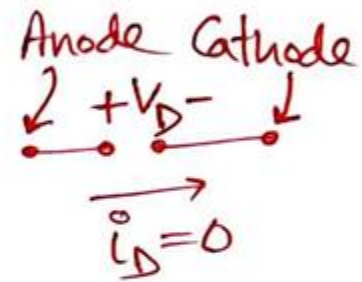OFF/R.B. \rightarrow if $V_D \leq V_{D0} \rightarrow$ replace with




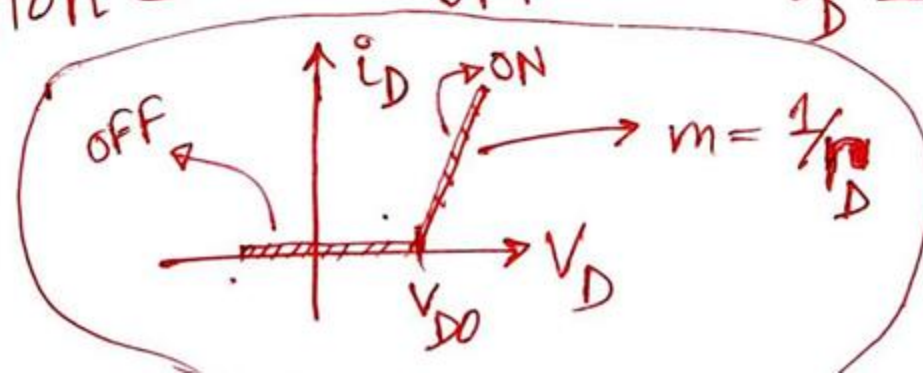
M.A.S conditions in verification \rightarrow ON $\rightarrow i_D > 0$
OFF $\rightarrow V_D \leq V_{D0}$



Diode Logic Gates



only AND, OR gates can be implemented

OR Gate

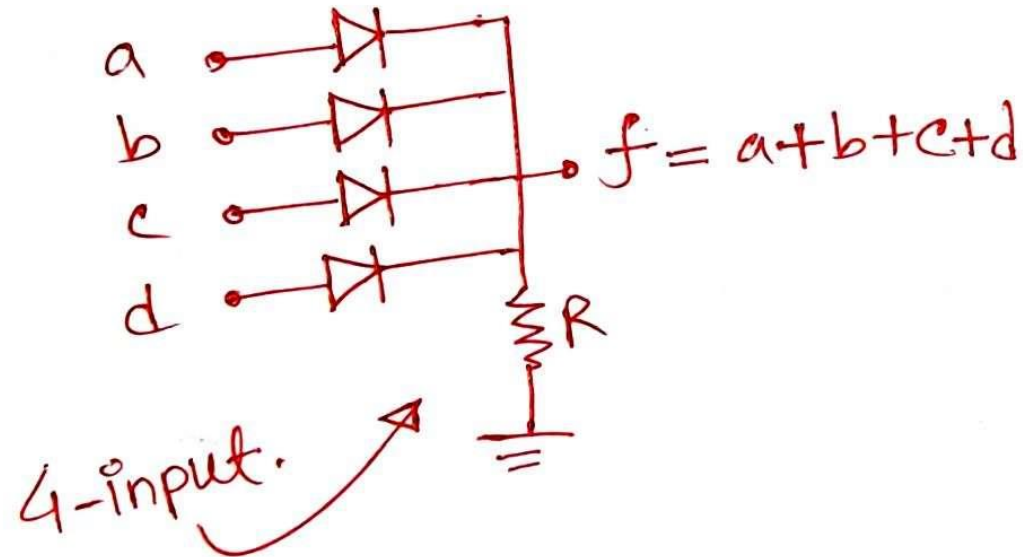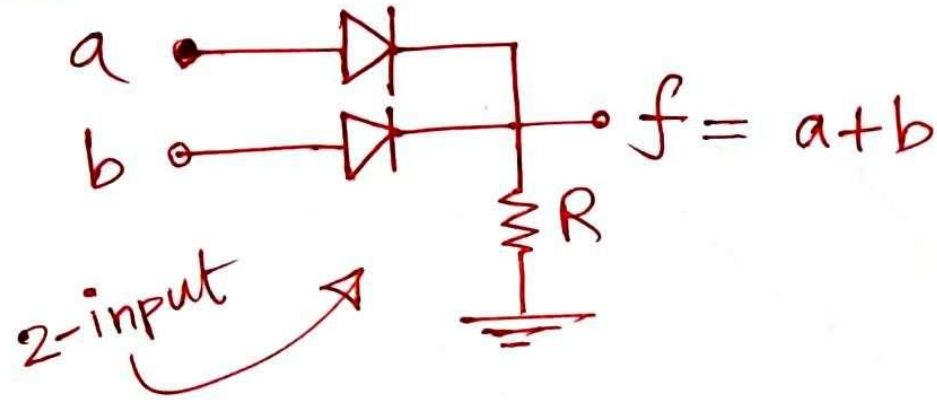


AND Gate

2-input

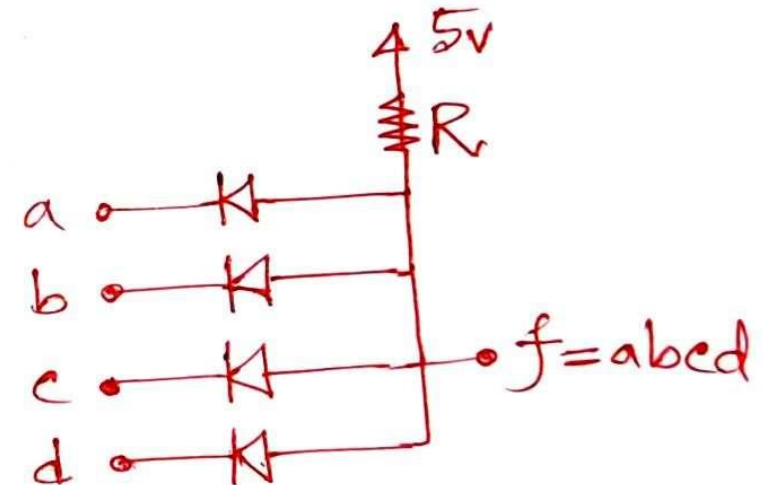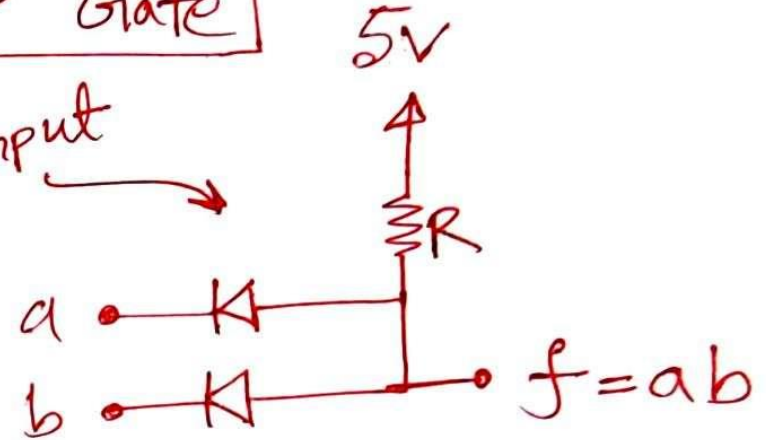


OR Gate \rightarrow also does
Max operation

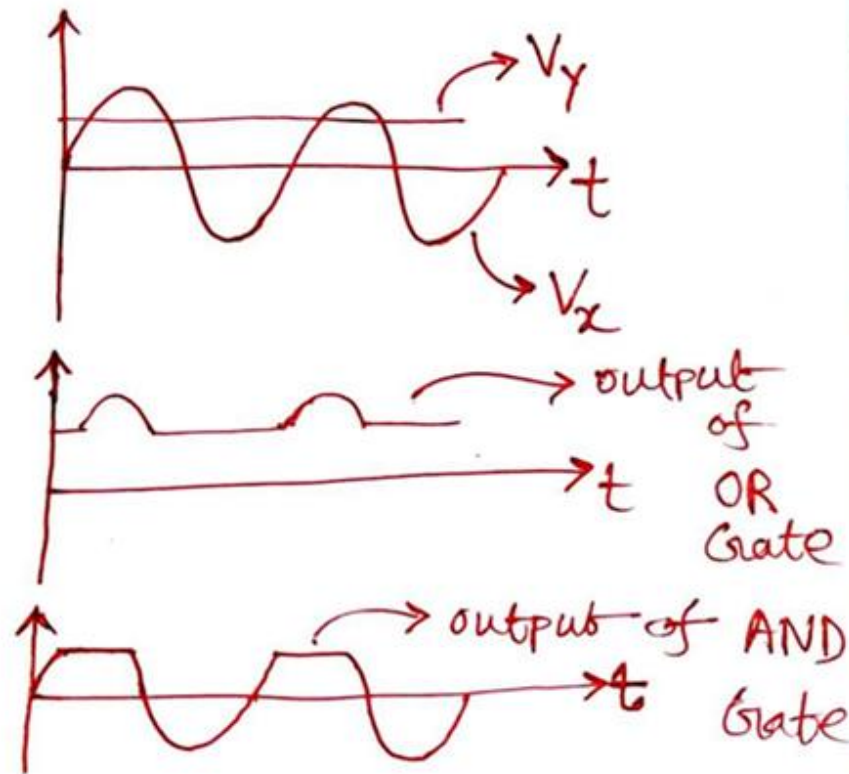
AND Gate \rightarrow also does
Min operation




$$\# f = (x+y)z$$

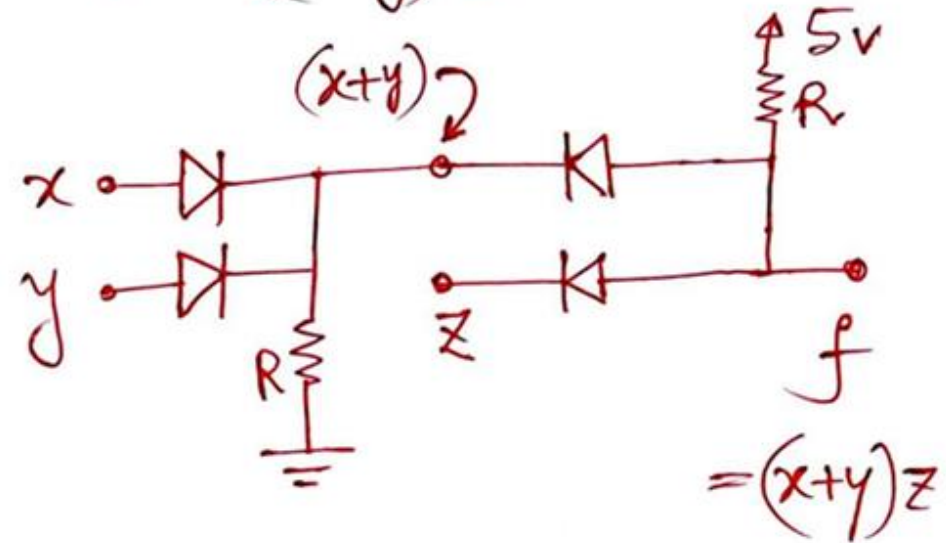




$$\# f = xy + z$$

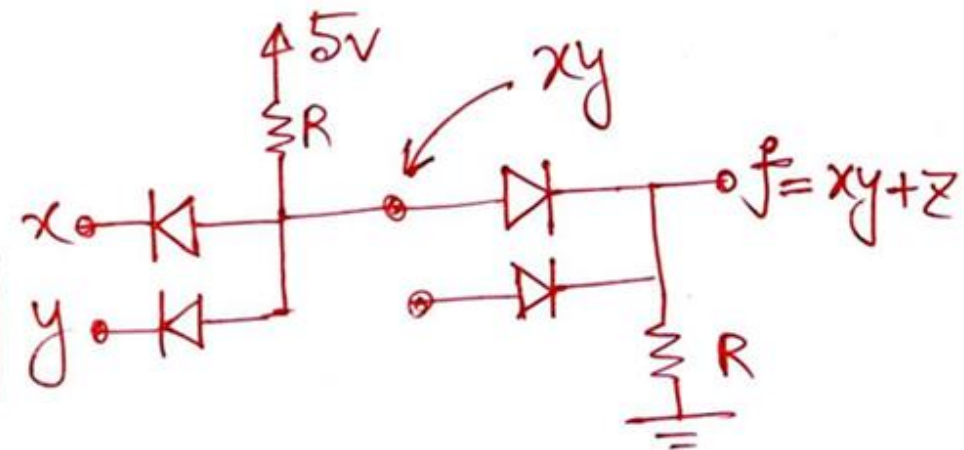


Half Wave Rectifier

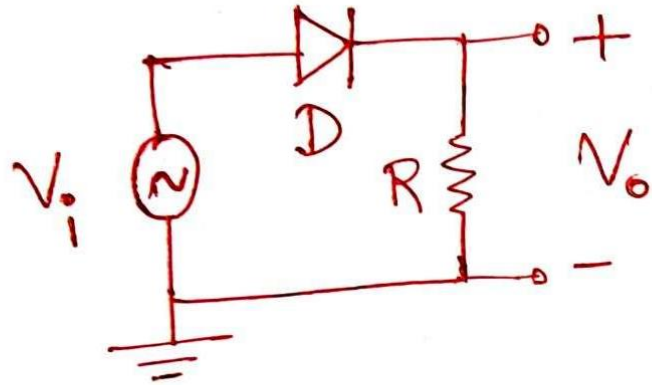


$$V_i = V_M \sin(\omega t)$$

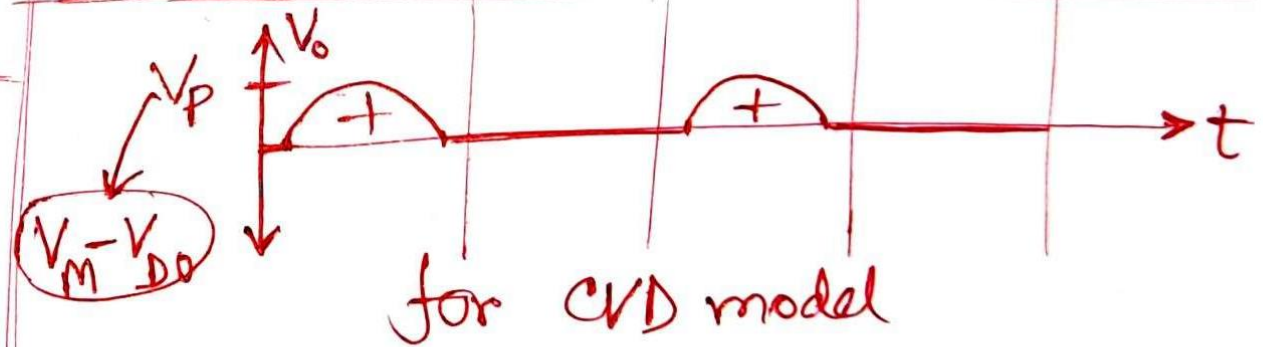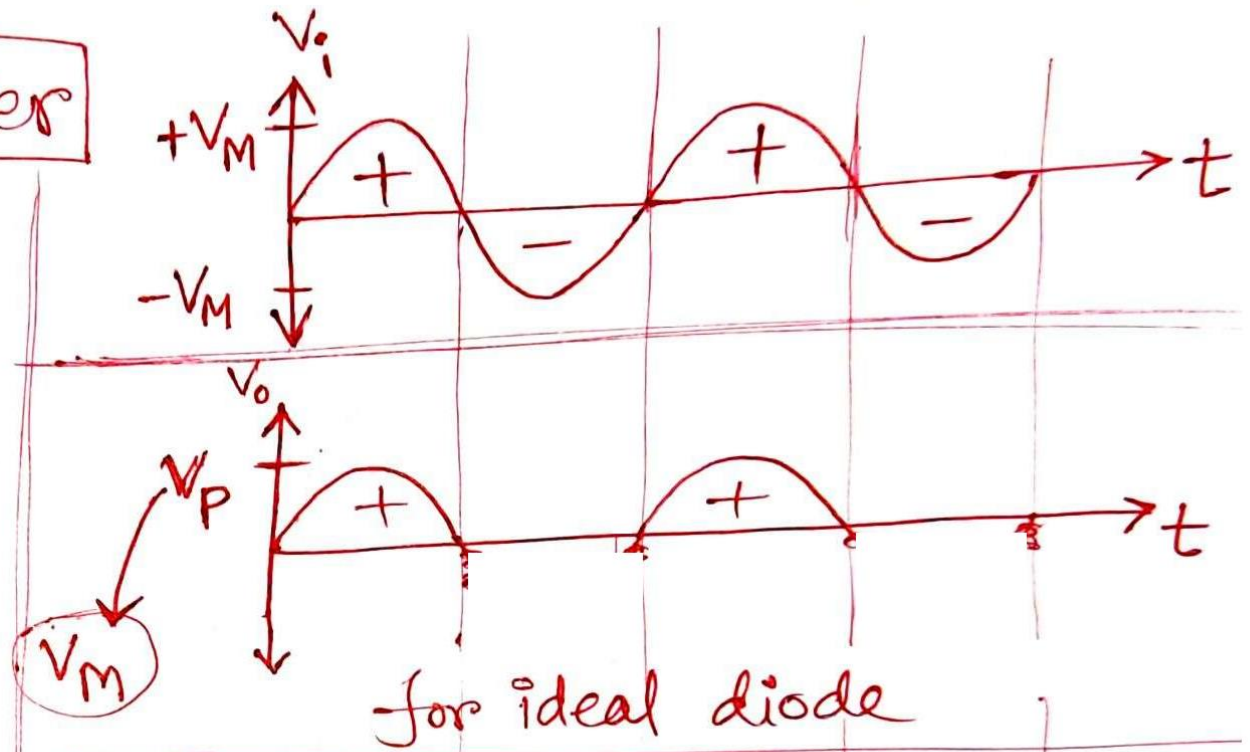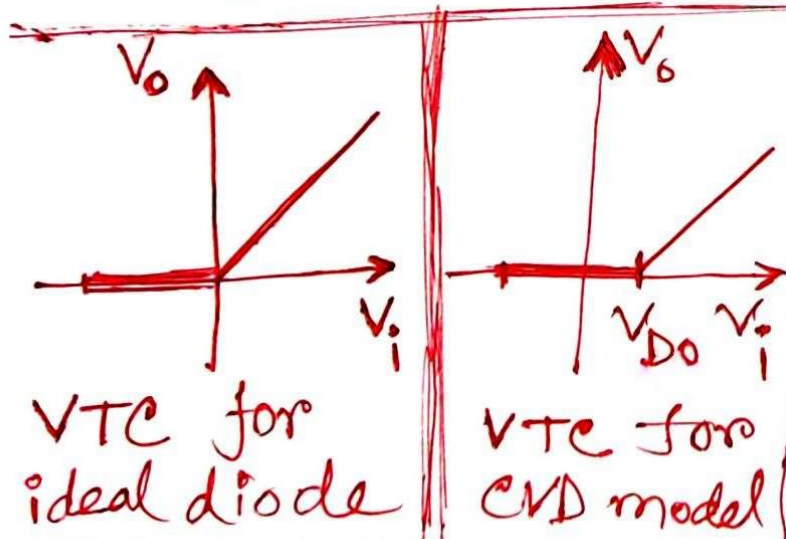





Full Wave Rectifier

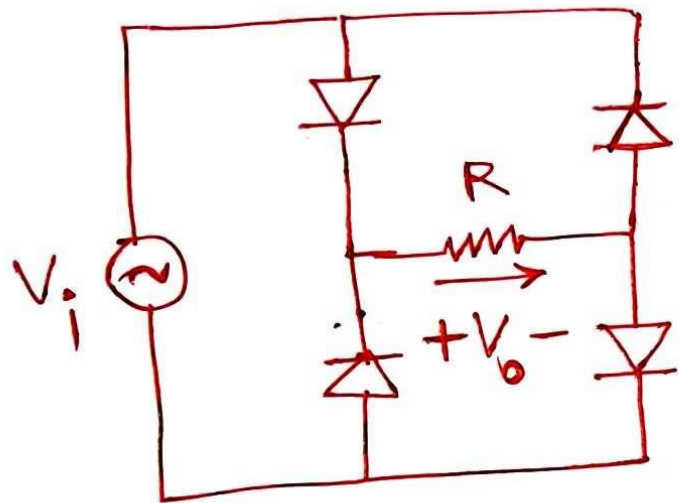

$$V_i = V_m \sin(\omega t)$$

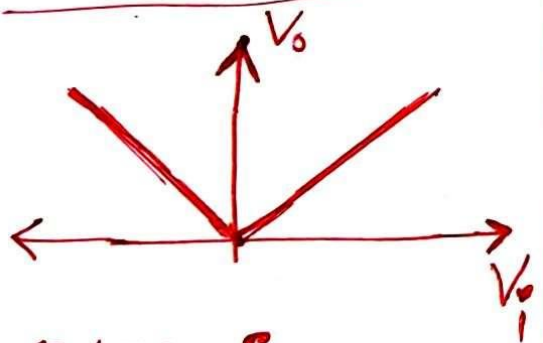

VTC for
ideal diode

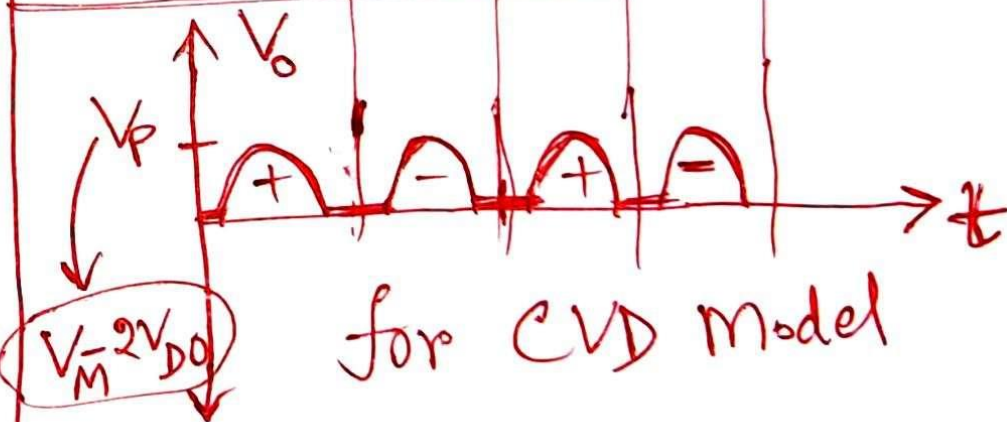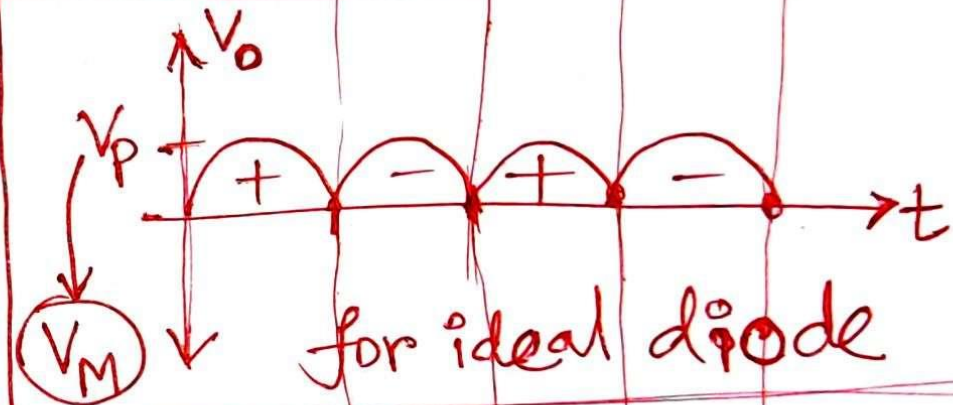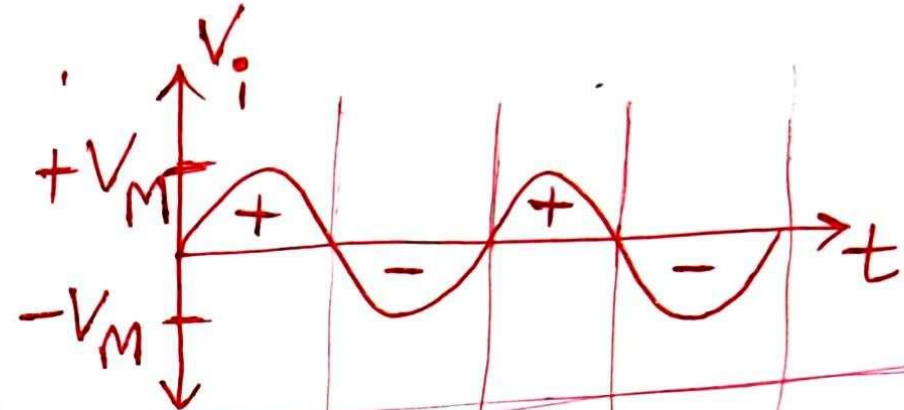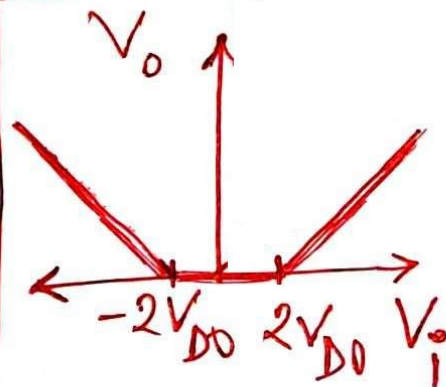

Rectifier without Capacitor

Half Wave \rightarrow ideal diode $\rightarrow V_{dc}$ or, $V_{avg} = \frac{1}{\pi} V_M$
 \rightarrow real diode $\rightarrow V_{dc}$ or, $V_{avg} = \frac{1}{\pi} V_M - \frac{1}{2} V_{DO}$

Full Wave \rightarrow ideal diode $\rightarrow \frac{2}{\pi} V_M$
 \rightarrow real diode $\rightarrow \frac{2}{\pi} V_M - 2V_{DO}$

Rectifier with Capacitor


Half Wave $\rightarrow f_r = f_i$

Full Wave $\rightarrow f_r = 2f_i$


$$V_{r(P-P)} = \frac{V_P}{f_r R C}$$

$$V_{dc} \text{ or, } V_{avg} = V_P - \frac{1}{2} V_{r(P-P)}$$


Half Wave Rectifier without capacitor

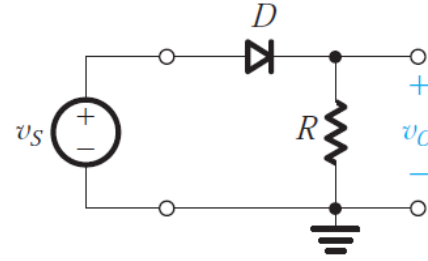


(a)

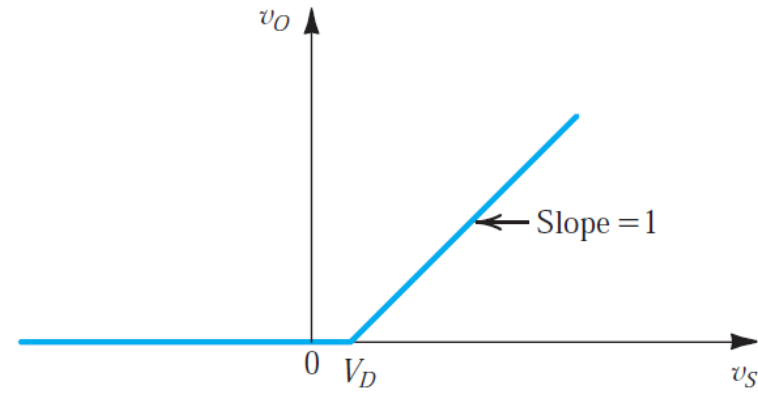

(b)

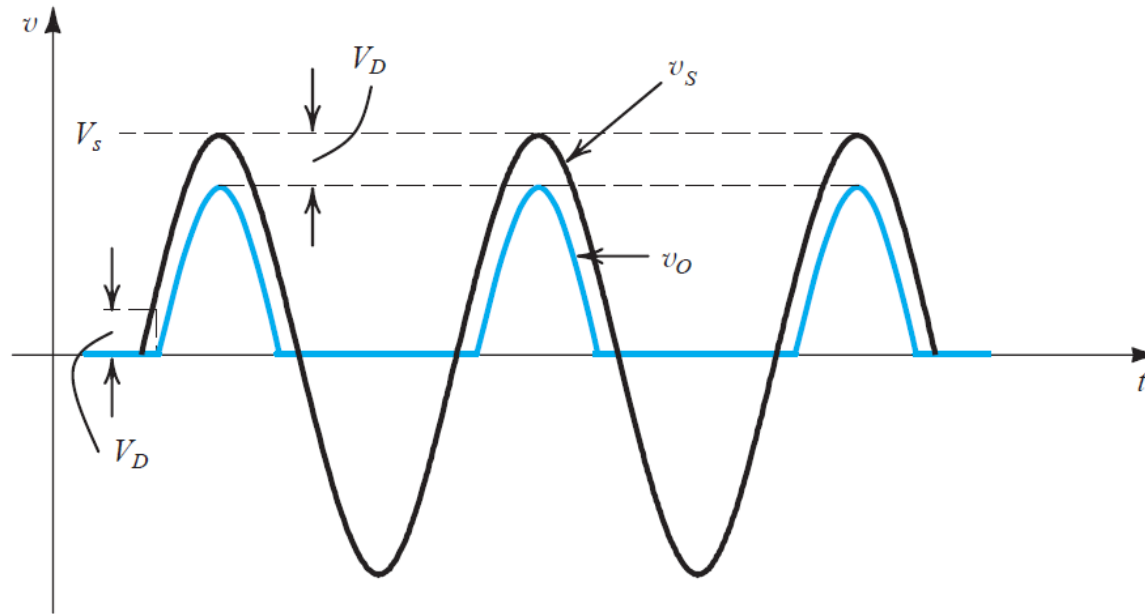

Half Wave Rectifiers with capacitor

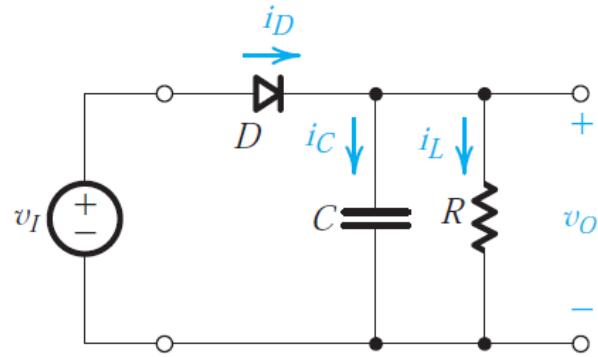

(a)

