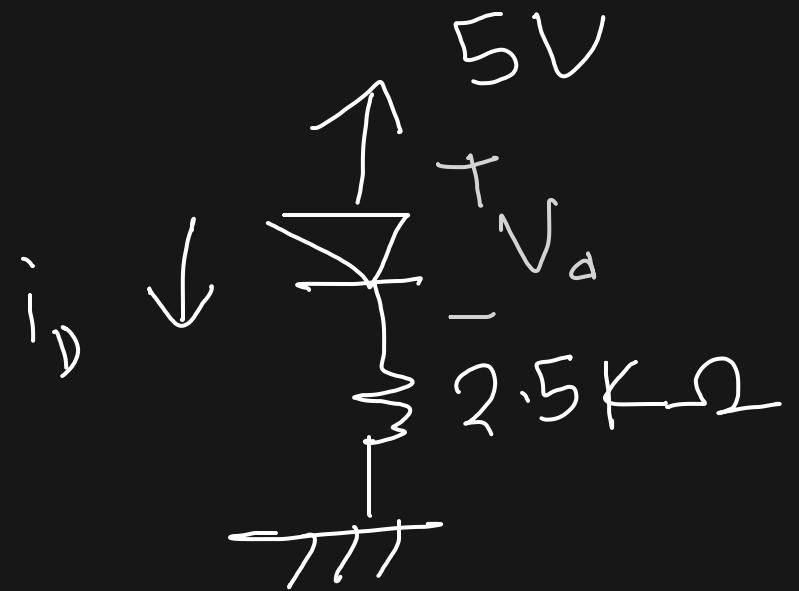


Lecture7

Diode Non-idealities




$$\# \text{Power} = V_i$$

$$= V_{d\text{,id}}$$

$$= 0$$


$$\# \text{Resistance} = 0$$

2.5 k

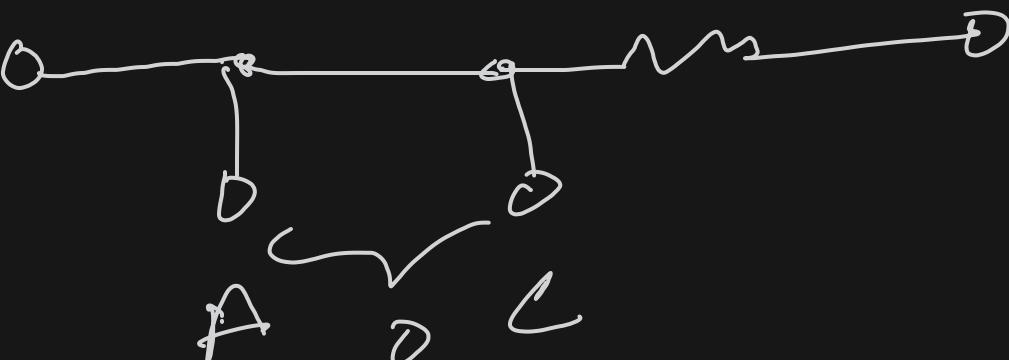

Non-ideality

Power

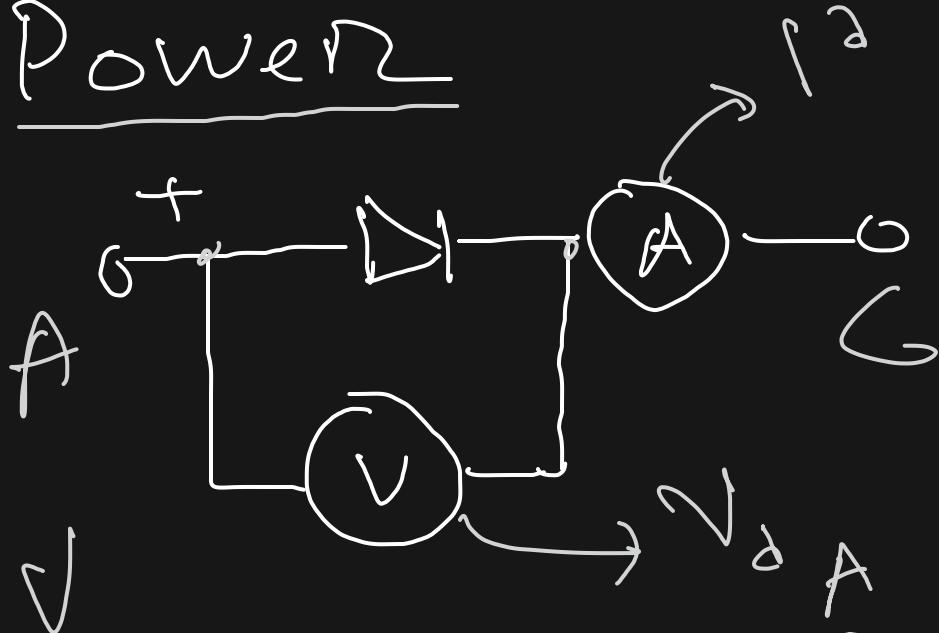


Diode:

Power $\approx 6 \cdot i_d^2$

ON: $P \propto I$

\Rightarrow Like voltage source

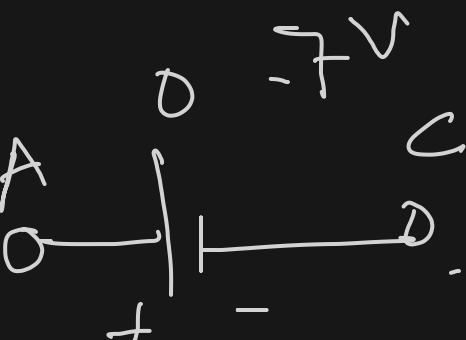

Si: $0.7V$




$0.7V$

OFF: Still open circuit!



$$V_A - V_C \approx 0.7V$$

Ge: $0.5V$



Resistance

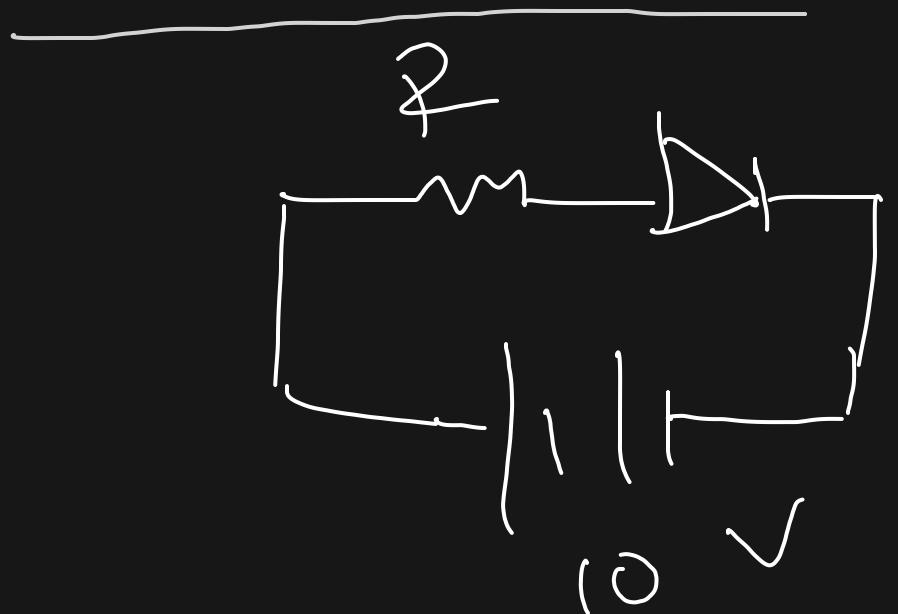

\Rightarrow

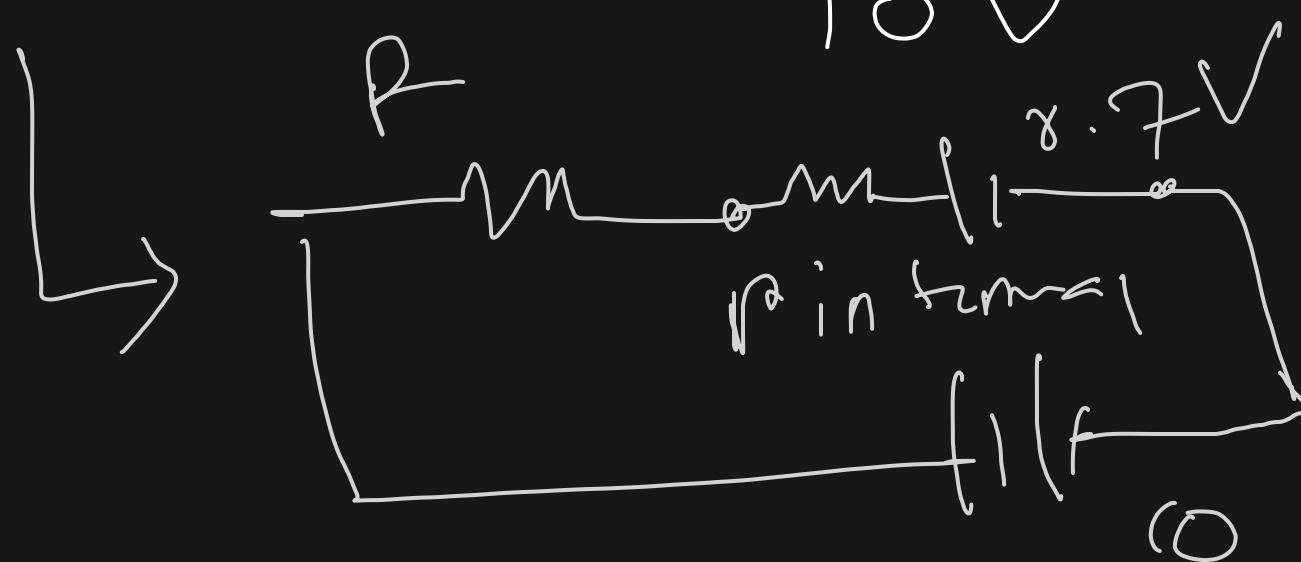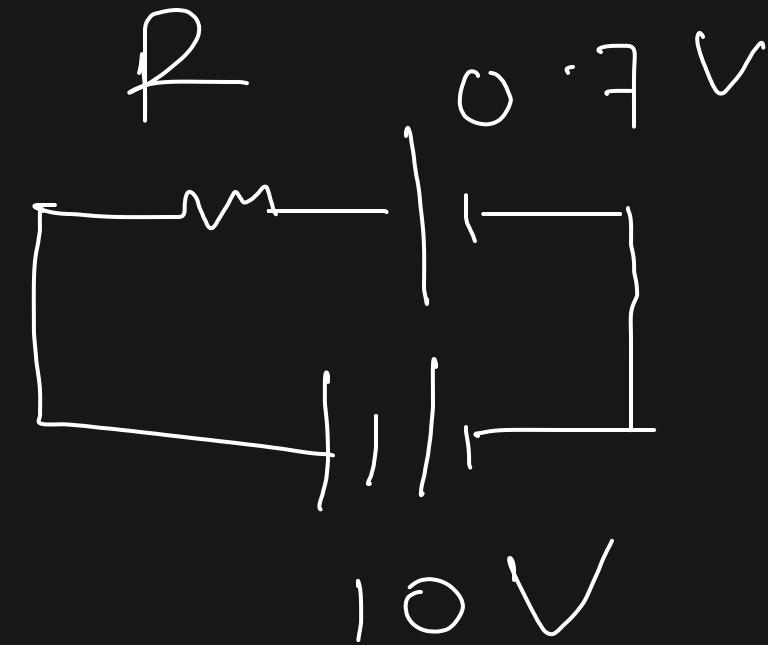


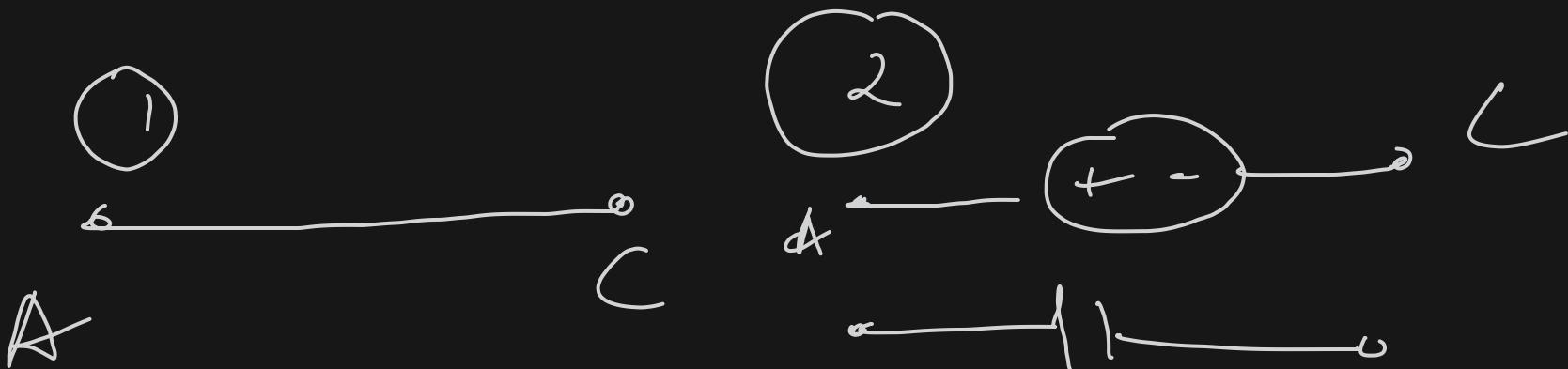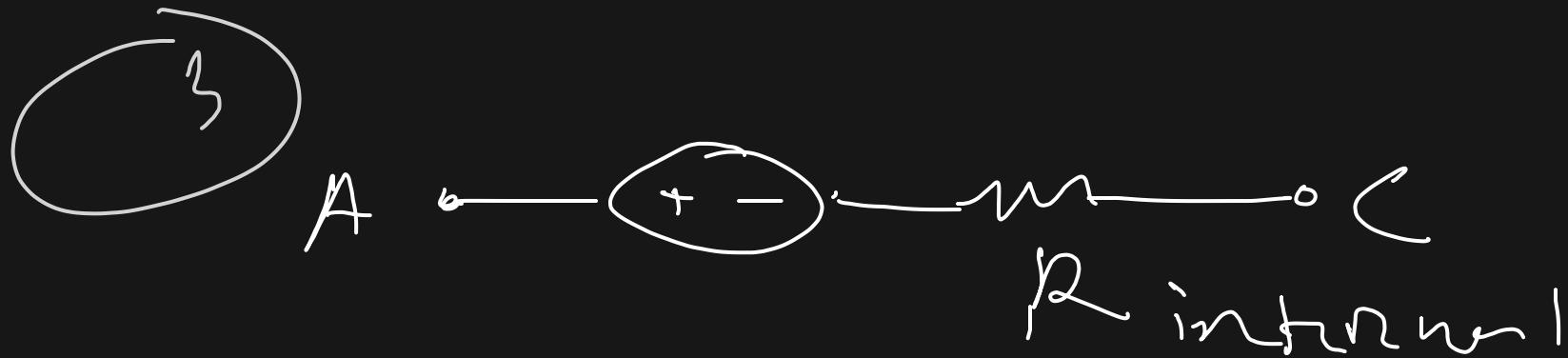 Material : \rightarrow Every material
has some resistance!



Piecewise Linear model (Non-ideal)

② Constant Voltage drop model (CVI)

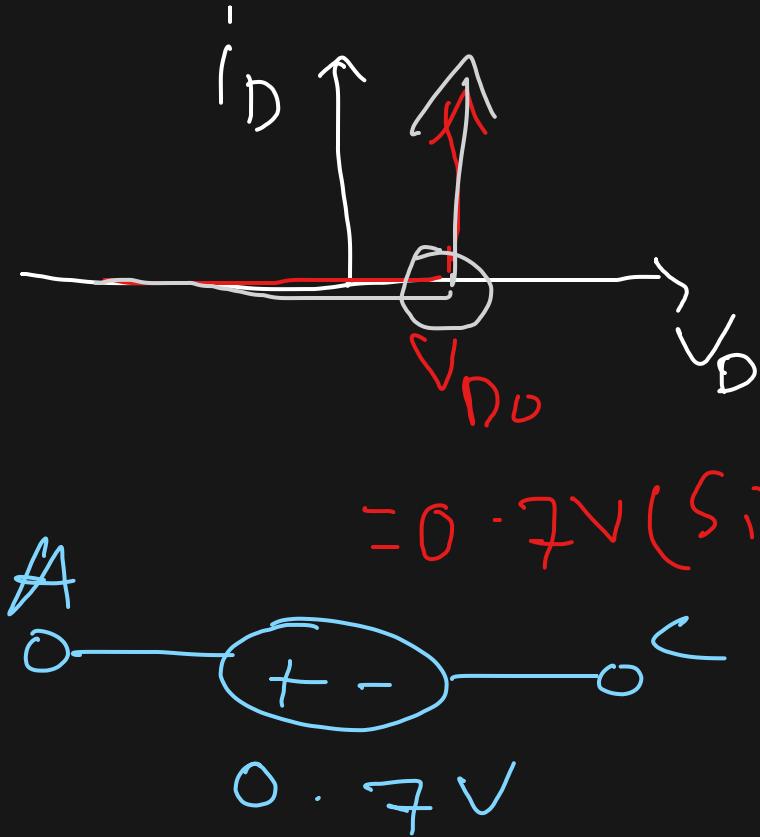

ON Condition:

$$i_D > 0$$

State eqn.:

$$V_D = V_{D0}$$


OFF Condition:

$$V_D < V_{D0}$$


State eqn.:

$$i_D = 0$$


③ Voltage source + Resistance Model

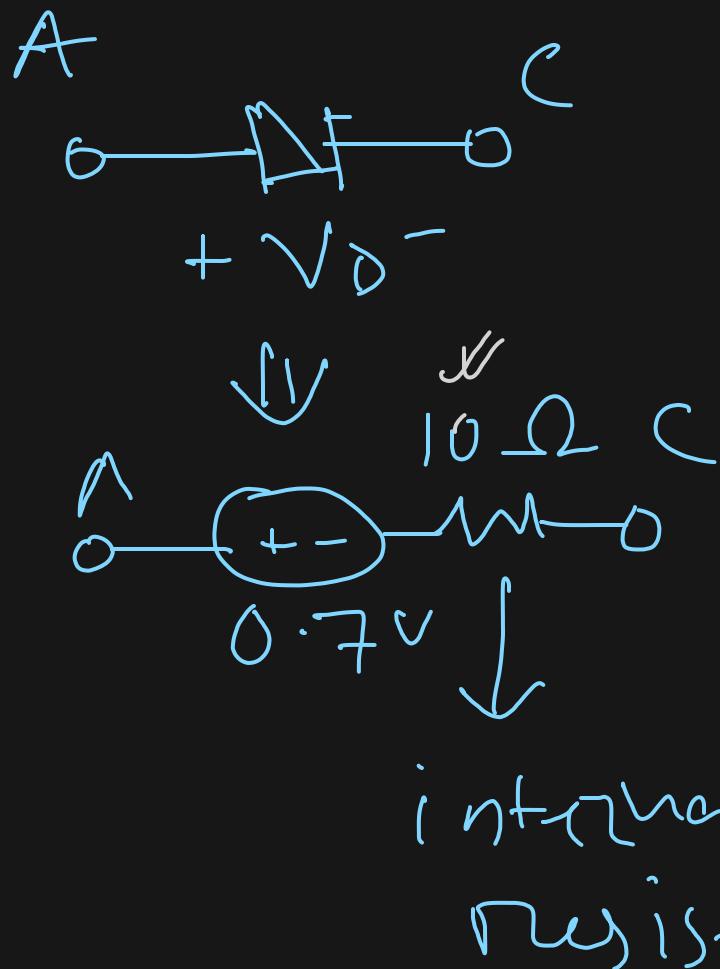

More Accurate

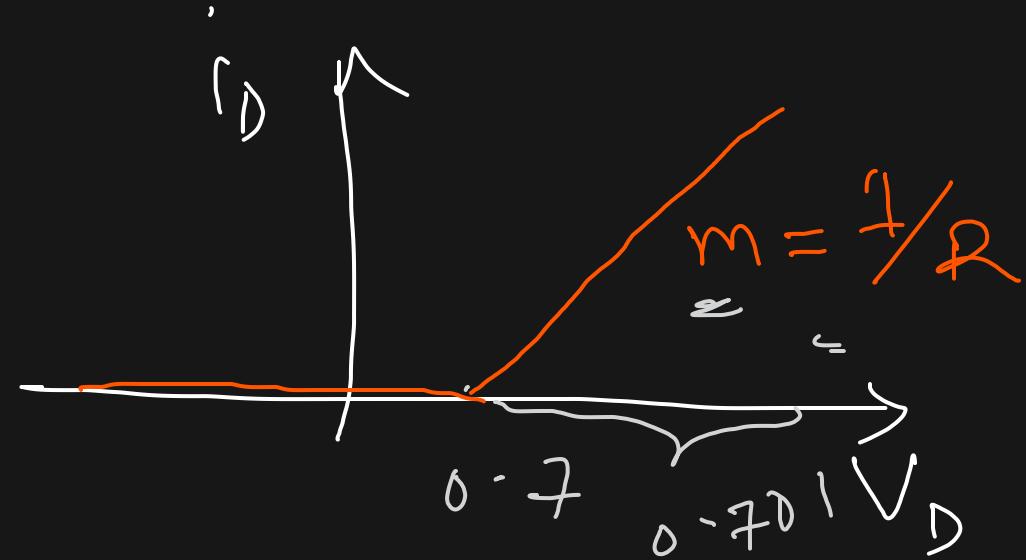

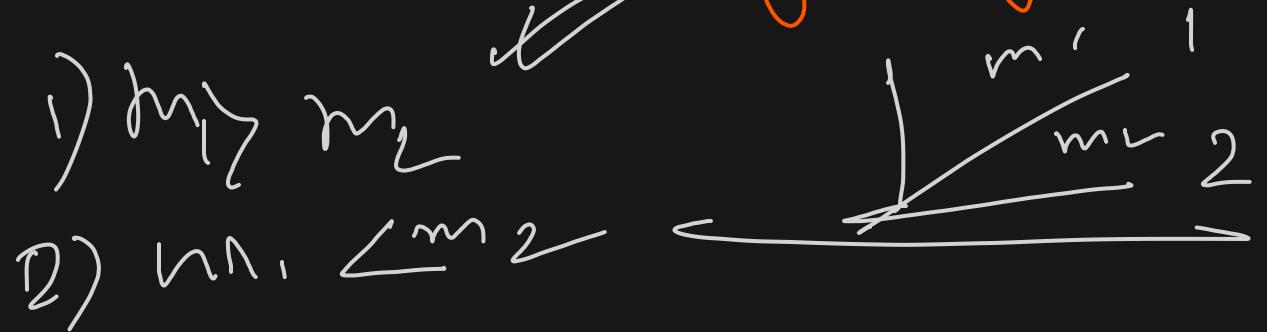
$R \rightarrow$ very low
 $\rightarrow m$ very high



Which ONE To use?


- 1) Most accurate: Voltage source + Res
- 2) Fastest : Ideal

Example

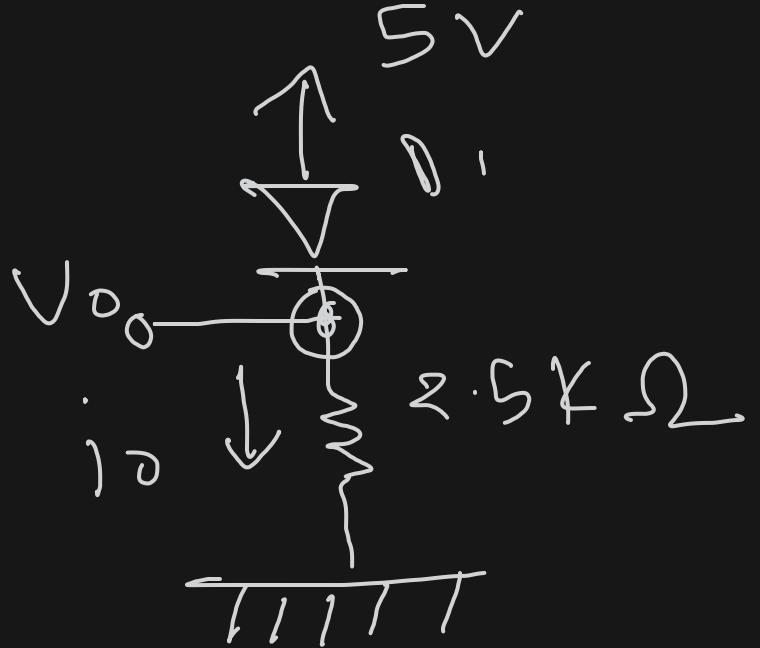


Find V_O and i_O

(I) Ideal Model

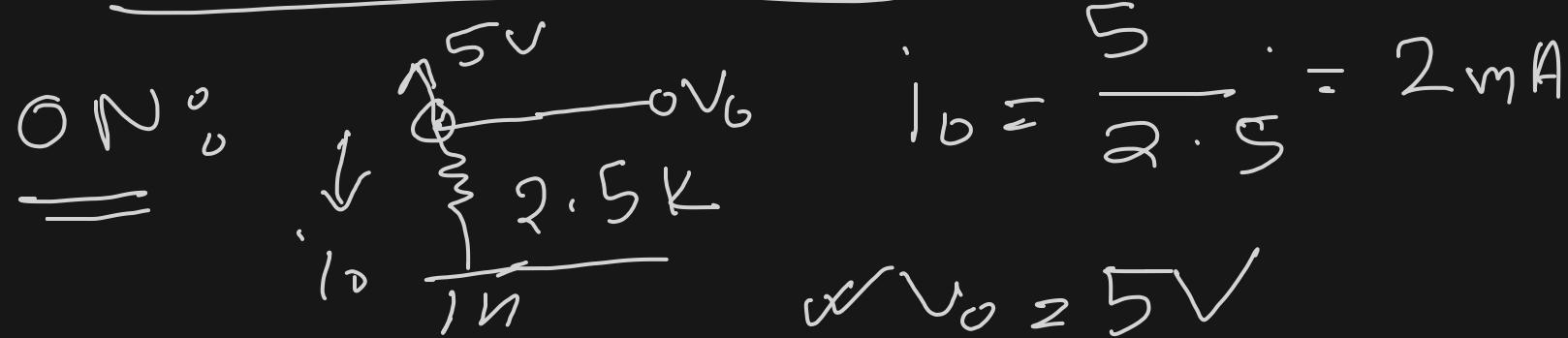


(II) CVD Model ($V_D = 0.7V$)



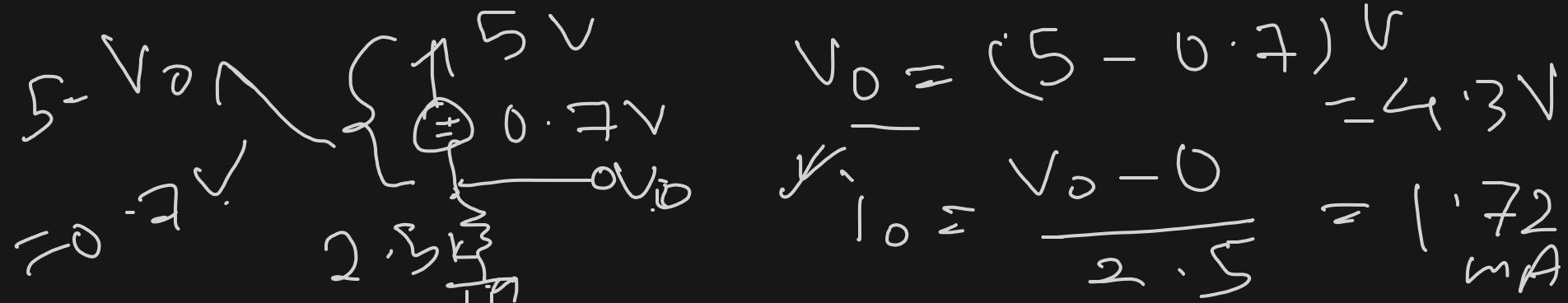


(III) CVD + resistance

$$V_D = 0.7 \text{ V}, R_o = 10 \Omega$$

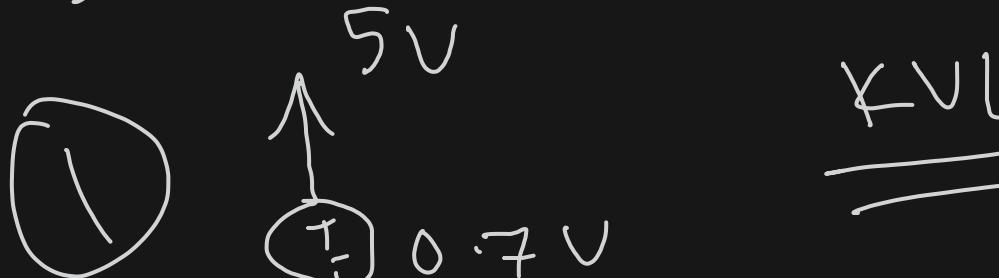

KVL

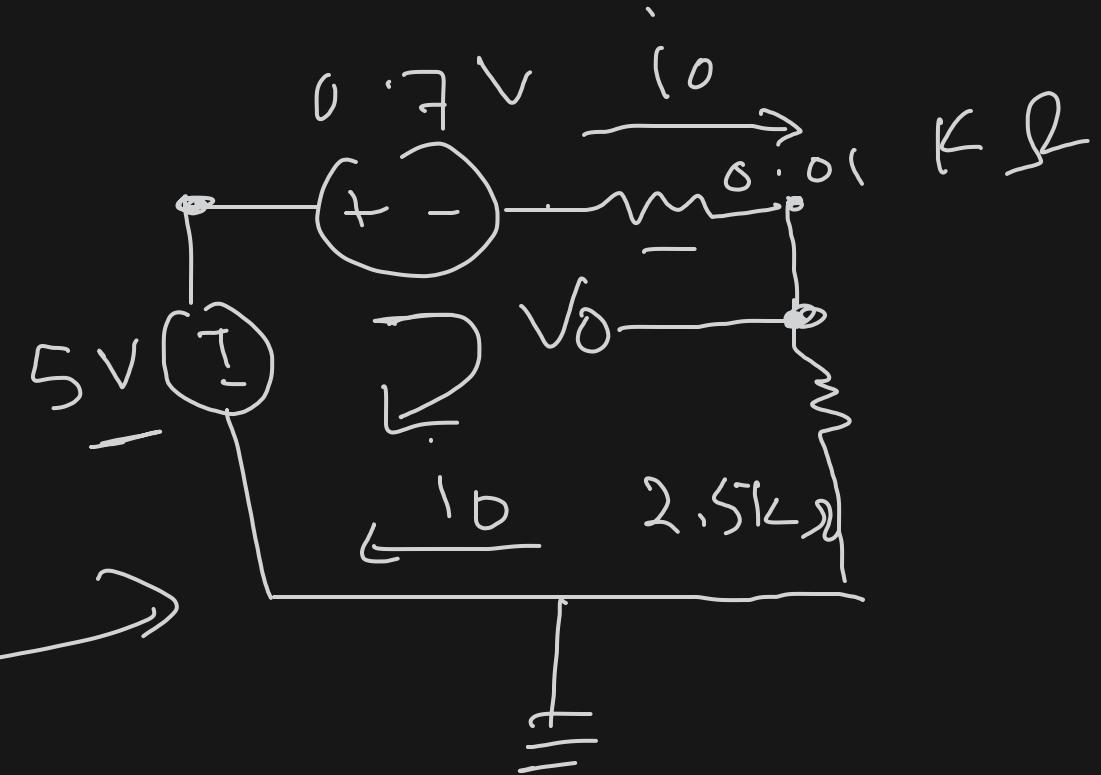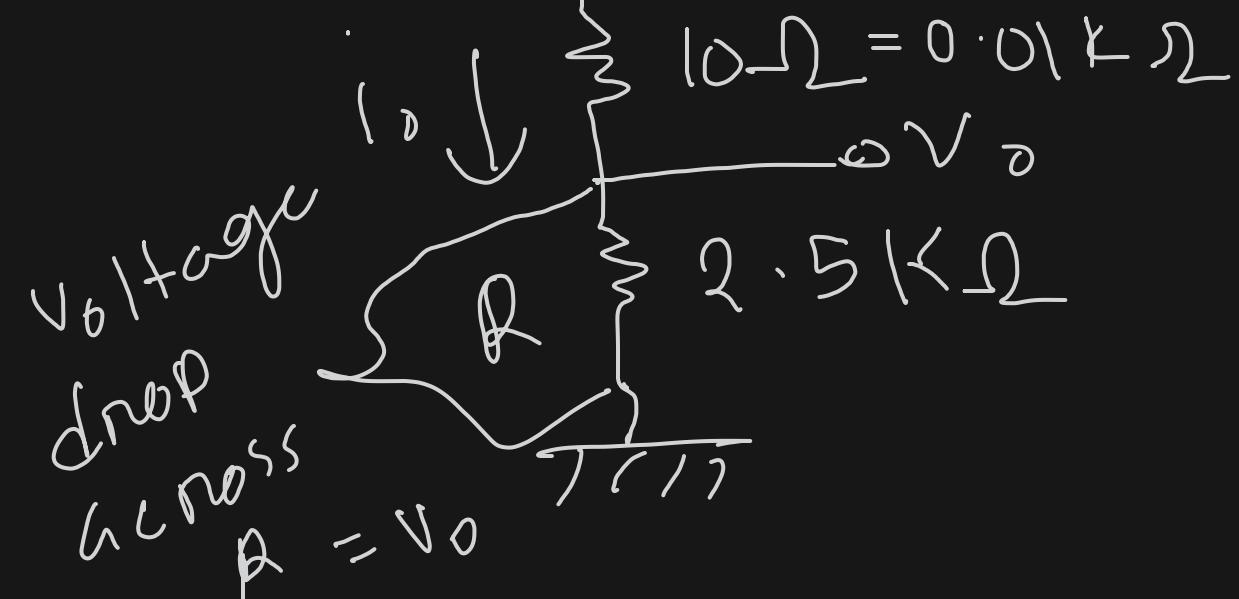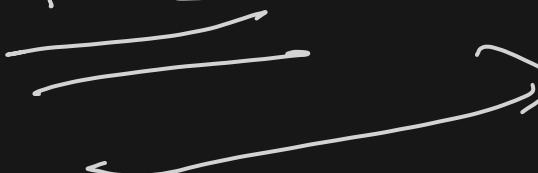

$$0.7 + i_o \times 0.01$$

$$+ 2.5 \times i_o = 5$$

$$\Rightarrow i_o = 1.713 \text{ mA}$$

$$\therefore V_o = i_o \times R = 4.28$$