

# **Assignment - 2**

**Name:** Md. Minhazul Mowla

**ID:** 23201390

**Section:** 01

**Course:** CSE251

**Submission Date:** 26/7/25

Ans. to the que No. 1


3

KCL at  $v_2$ ,

$$i_1 = i + i_2 : [\because i = 0]$$

$$\therefore i_1 = i_2$$

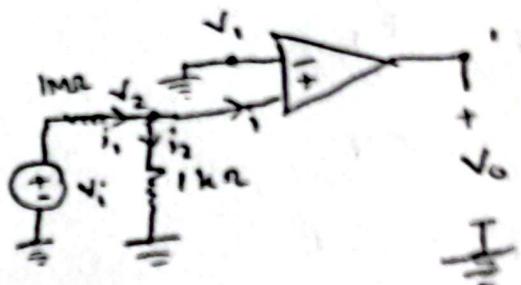$\therefore v_i, 1\text{M}\Omega, 1\text{k}\Omega - \text{all in series.}$



Voltage Divider,

$$v_2 = \frac{1\text{k}\Omega}{1\text{k}\Omega + 1\text{M}\Omega} \times v_i = \frac{10^3 \times}{10^3 + 10^6} \times 2\text{V}$$

$$= 1.998 \times 10^{-3} \text{V}$$

$$= 1.998 \text{ mV}$$

$$v_o = A(v_2 - v_1) \dots$$

$$\Rightarrow 4 = A(1.998 \text{ mV} - 0)$$

$$\Rightarrow A = \frac{4}{1.998 \times 10^{-3}}$$

$$= 2000$$

(Ans)

4

$$v_2 = 0$$



$$v_1 = E_i$$

$$v_s^+ = 15V$$

$$v_s^- = -15V$$

$$\therefore v_2 > v_1 \rightarrow v_o = +v_s^+$$
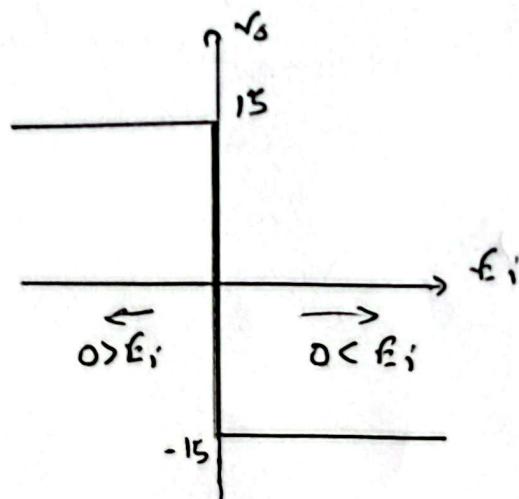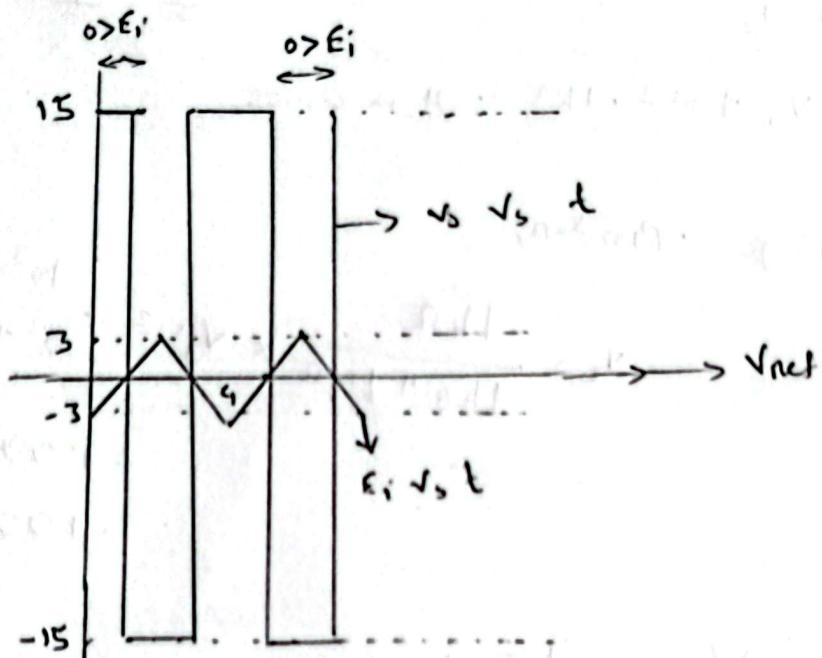
$$\therefore v_2 < v_1 \rightarrow v_o = -v_s^-$$





. 5

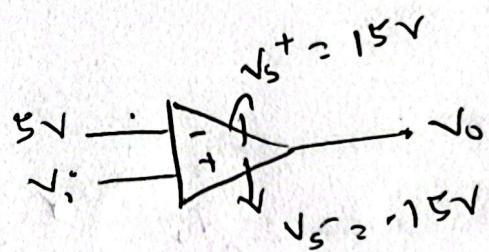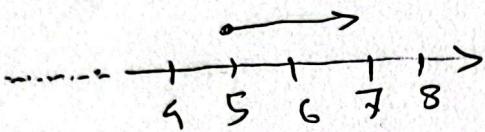i)  $v_i > 5V$

$$v_o = 15V \quad [v_s^+ = 15V]$$

$$\left. \begin{array}{l} v_2 > v_1, v_o = v_s^+ \\ v_2 < v_1, v_o = v_s^- \end{array} \right\}$$




ii)  $v_i < -4$

$$v_o = 15V \quad ] \text{ case-ii}$$

$v_i > -4$

$$v_o = -15 \quad ] \text{ case-ii}$$


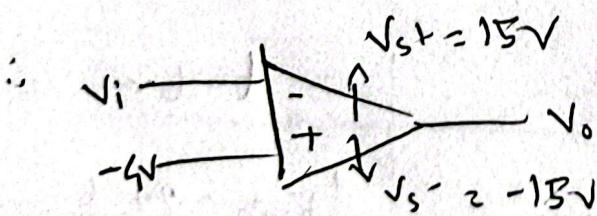


7

$$v_2 = E_C$$

$$v_1 = \sqrt{\text{temp}} = 3\sqrt{}$$
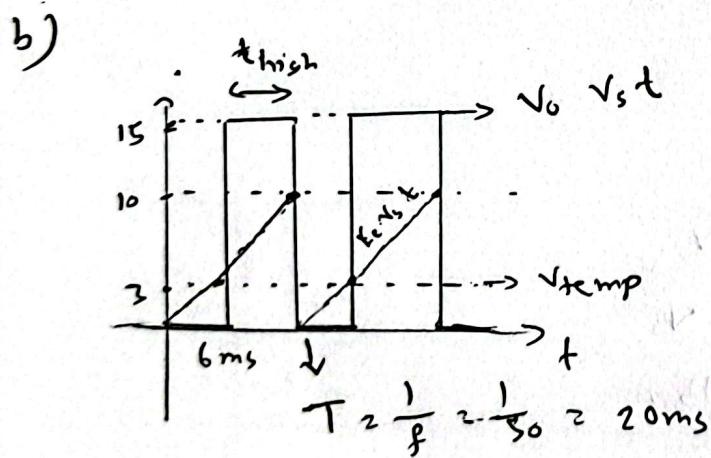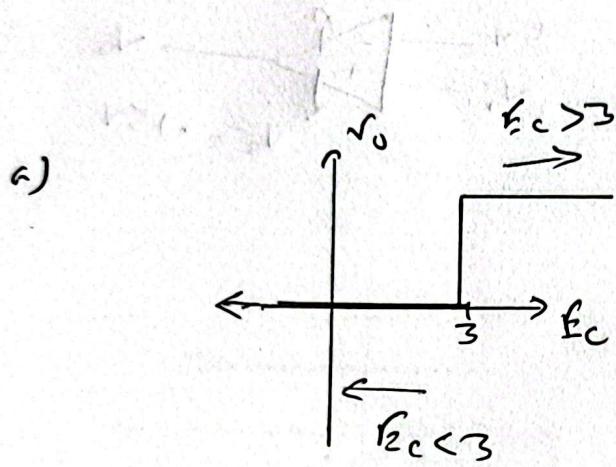
$$\begin{cases} E_C > 3, v_0 = \sqrt{s^+} = 15\sqrt{1} \\ E_C < 3, v_0 = \sqrt{s^-} = 0 \end{cases}$$



$$\begin{aligned} c) (0,0) \\ (20\text{ms}, 10\sqrt{}) \end{aligned}$$

$$\therefore v = 0 \vdash \frac{10 - 0}{20 - 0} (t - 0)$$

$$\Rightarrow v = \frac{1}{2}t$$

$$v = 3,$$

$$3 = \frac{1}{2}t$$




$$\therefore t = 6\text{ms}$$

$$\begin{aligned} t_{\text{high}} &\approx 20 - 6 \\ &= 14\text{ms} \end{aligned}$$

10


a)  $E_{in} > 3$ ,  $v_o = v_s^+ = 15V$

$E_{in} < 3$ ,  $v_o = v_s^- = 0V$

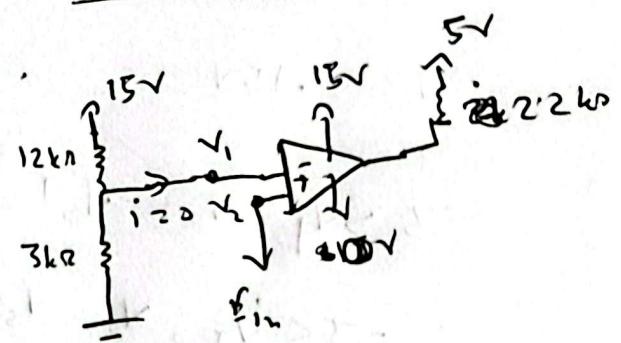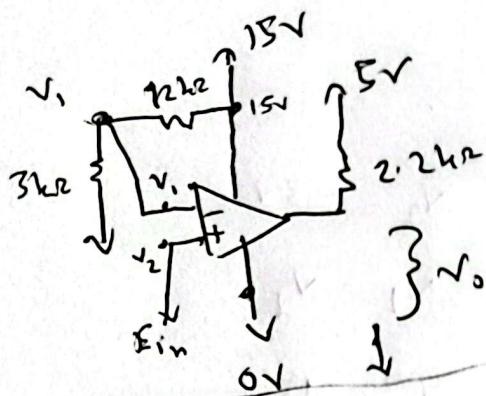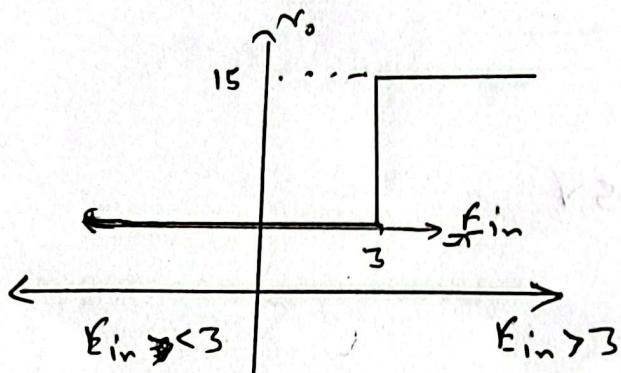

$$v_1 = \frac{3}{12+3} \times 5 = 3V$$



b)

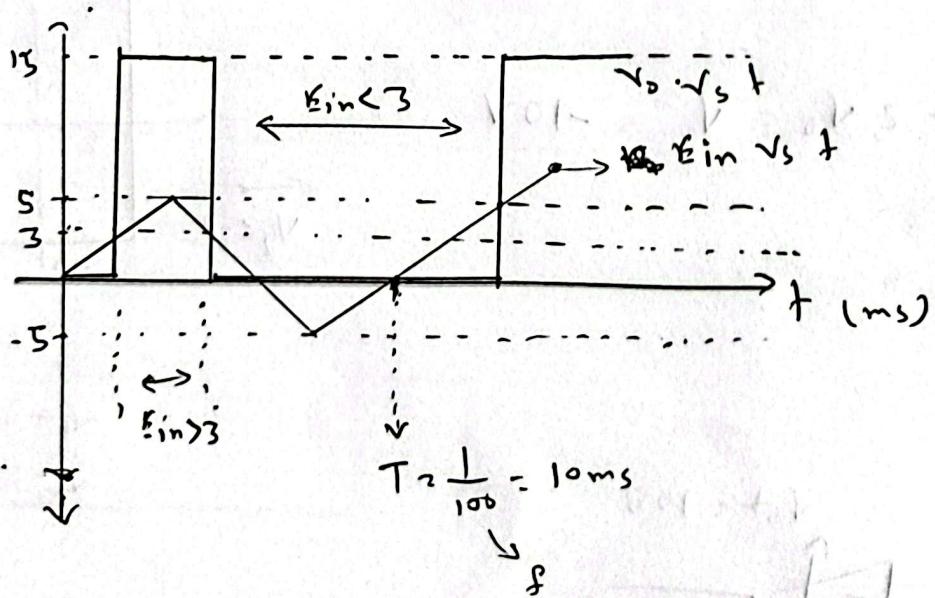

12

$$v_i < -2, v_o = v_s + 10V$$

$$v_i > -2, v_o = v_s - 10V$$

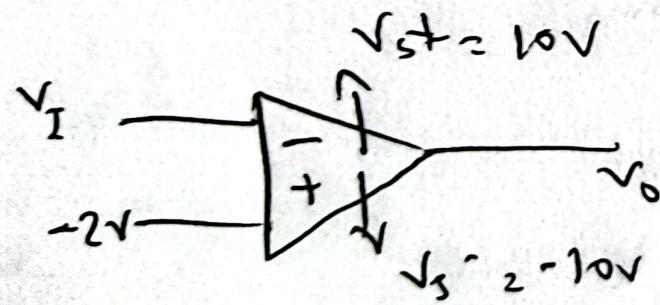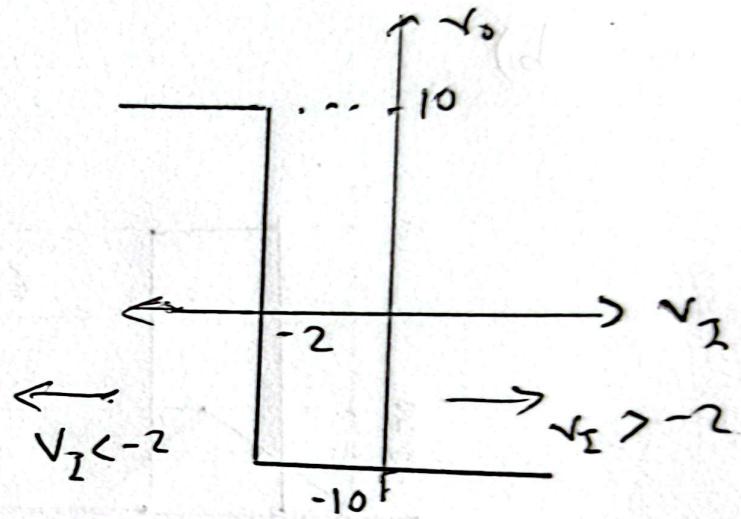

$$v_s^+ = 10$$
$$v_s^- = -10$$

if  $V_i > 3V$ ,  $V_A = 8V$

if  $V_i < 3V$ ,  $V_A = 0V$




2nd Diode,

$$3 - V_x = -3 \quad \therefore V_x = 6V$$

$$\therefore V_+ = 6V$$

if  $V_- > 6V$ ,  $V_o = 4V$


if  $V_- < 6V$ ,  $V_o = 8V$

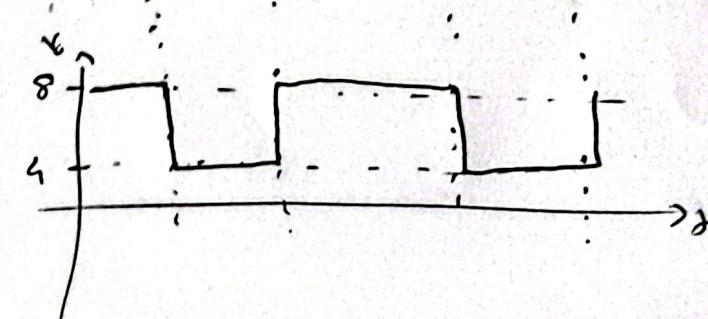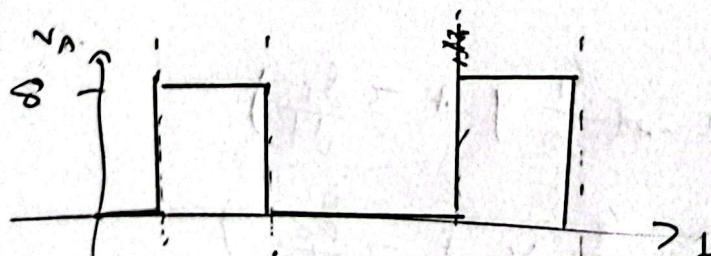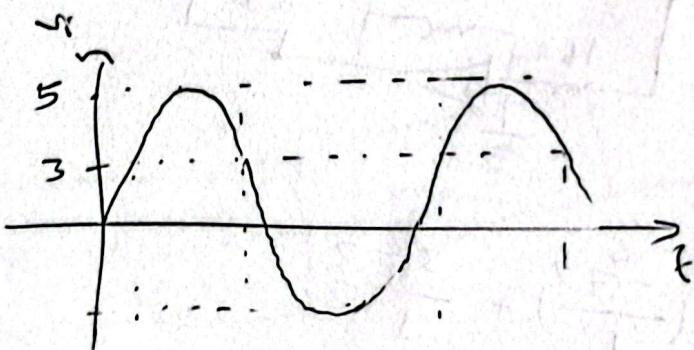

Ans. to Ques. No. - 2

$$\frac{1}{iV}$$
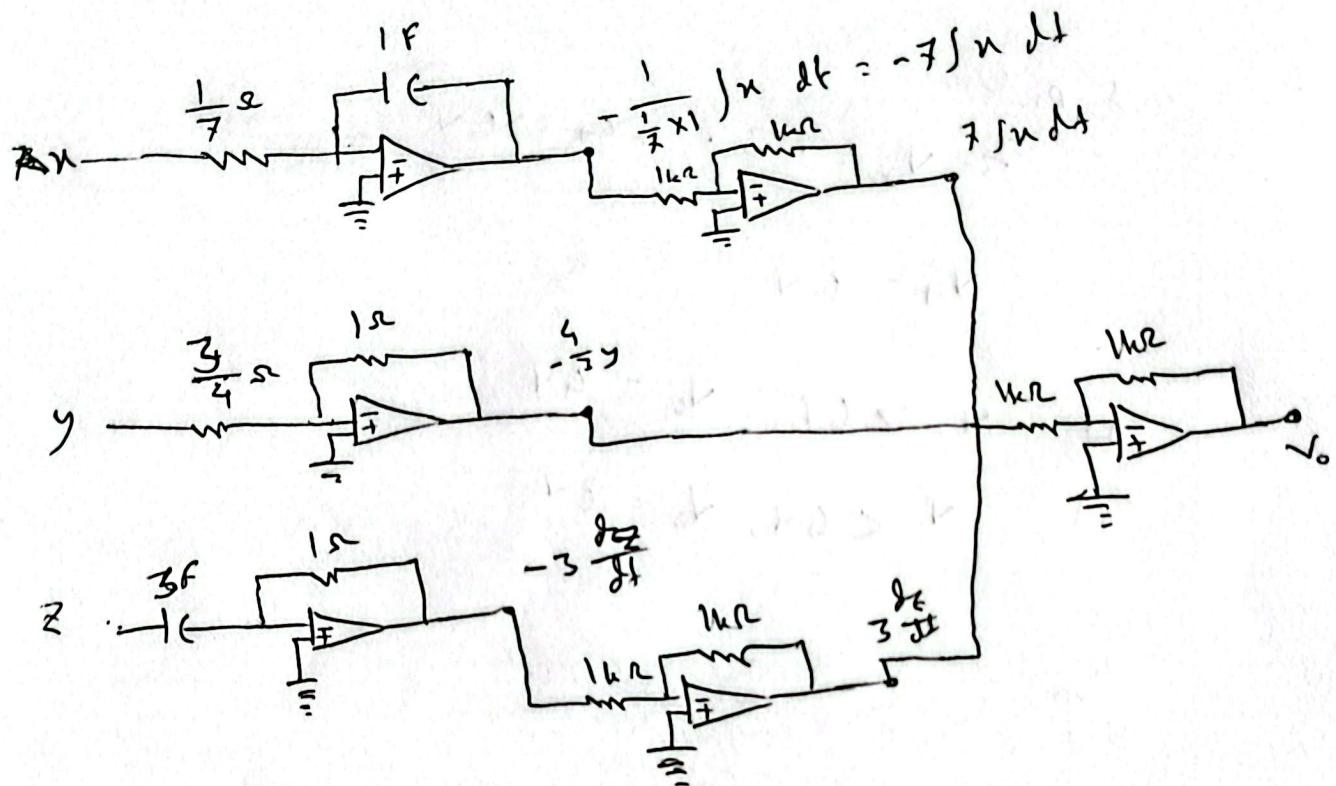
$$f = -7 \int u dt + \frac{4}{3} y - 3 \frac{d}{dt} z = -\left\{ 7 \int u dt + \left( -\frac{4}{3} y \right) + 3 \frac{d z}{dt} \right\}$$



$$v_o = -R_o \left\{ \frac{7 \int u dt}{1} + \left( -\frac{4}{3} y \right) + \frac{3 \frac{dz}{dt}}{1} \right\}$$

$$= -1 \left( 7 \int u dt - \frac{4}{3} y + 3 \frac{dz}{dt} \right)$$


$$= -\left( 7 \int u dt - \frac{4}{3} y + 3 \frac{dz}{dt} \right)$$

1 1 1 1

i


$$-\nu_o = \frac{\nu_3}{5} - \frac{\nu_1}{5} + \frac{\nu_1}{2} \neq -\frac{\nu_2}{2}$$
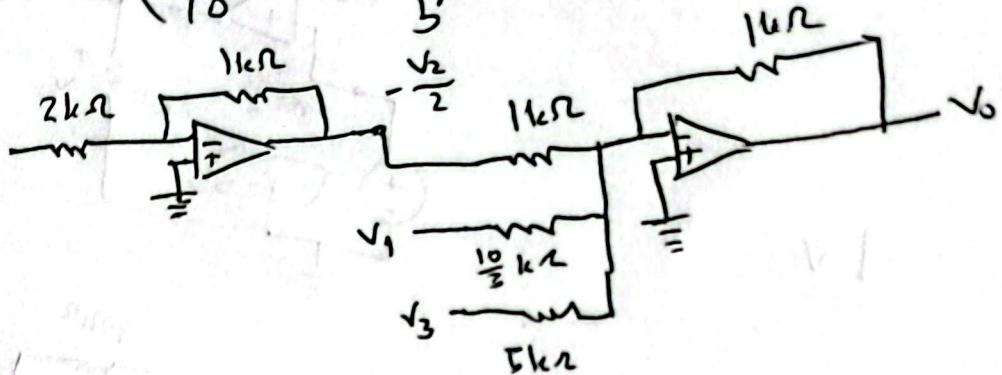
$$\Rightarrow \nu_o = -\left(\frac{3\nu_1}{10} + \frac{\nu_3}{5} - \frac{\nu_2}{2}\right)$$



ii
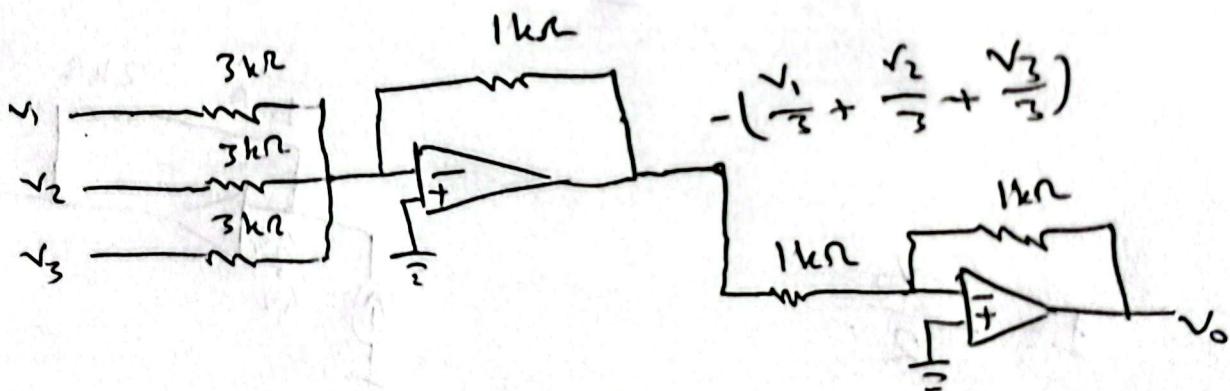
$$\text{Average} = \frac{\nu_1 + \nu_2 + \nu_3}{3}$$



$$\nu_o = \frac{\nu_1}{3} + \frac{\nu_2}{3} + \frac{\nu_3}{3}$$


$$\Rightarrow \frac{\nu_1 + \nu_2 + \nu_3}{3}$$

$$\frac{4}{\alpha}$$

$$1 - \alpha \approx 2$$

$$\therefore \alpha = -1/2$$


$$\gamma_0 = \alpha \approx -1/2$$

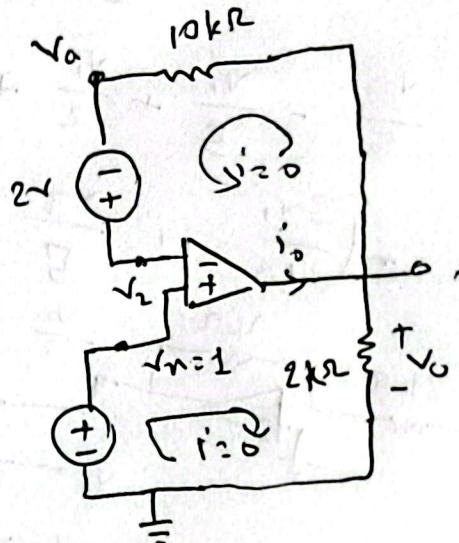

$$i_o = \frac{V_o - 0}{2} = -\frac{1}{2} \text{ mA}$$


$$\approx -0.5 \text{ mA}$$

b

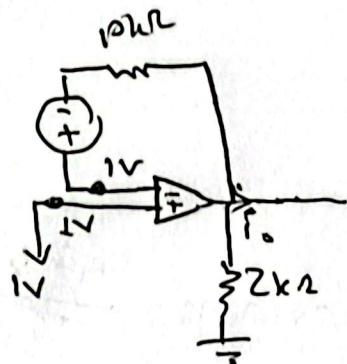


$$1 = \frac{\gamma \gamma_0}{2}$$

$$\therefore \gamma_0 \approx 2V$$

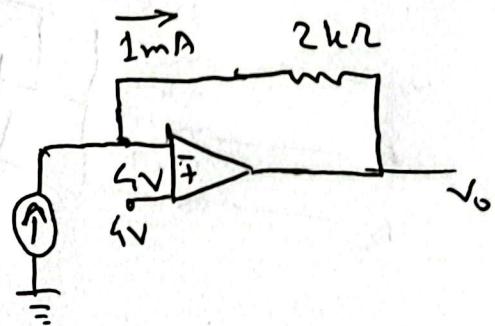

$$\frac{10}{1}$$

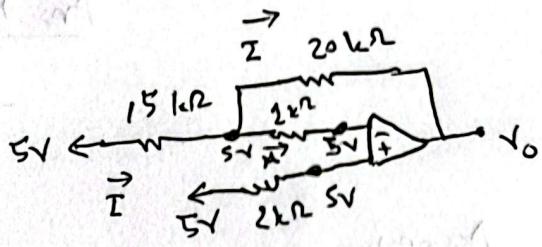

$$I = \frac{5 - V_o}{15} = 0$$

$$I = \frac{5 - V_o}{20}$$

$$\therefore \frac{5 - V_o}{20} = 0$$

$$\therefore V_o = 5V$$

14

$$\frac{V_2}{2} + \frac{V_2 - V_o}{18} + \frac{V_2 - V_3}{1} = 0$$

$$\Rightarrow \frac{9V_2 + V_2 - V_o + 18V_2 - 18V_3}{18} = 0$$

$$\Rightarrow -V_o + 28V_2 - 18V_3 = 0$$

$$\therefore -V_o + 18V_3 = -150 \dots (i)$$


$$\frac{V_3 - V_o}{5} + \frac{V_3 - V_2}{1} + \frac{V_3}{3} = 0$$

$$\Rightarrow \frac{3V_3 - 3V_o + 12V_3 - 12V_2 + 5V_3}{12} = 0$$

$$\Rightarrow -3V_o - 12V_2 + 19V_3 = 0$$

$$\therefore -3V_o - 19V_3 = 60 \dots (ii)$$
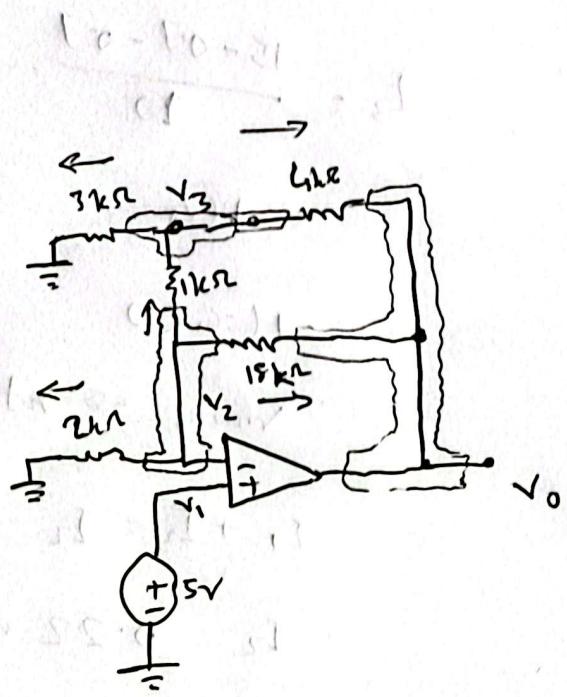
$$\therefore I_o = \frac{V_3}{5} + \frac{V_2}{18} = 1.92mA$$



$$V_1 = 5V$$

$$V_2 = 5V$$

Ans. to the Ques No. - 3

Part - i

8

Assuming, - i

Both  $D_1, D_2$  on

$$I_1 = \frac{10 - 0.7}{5} = 1.86 \text{ mA}$$

$$I_3 = \frac{-15 - 0.7 - 0.7}{20} \\ = -1.64$$

$$\therefore -1.64 < 0$$



∴ Wrong assumption for  $D_2$

$$I_1 + I_3 = I_2$$

$$\therefore I_2 = 0.22 \text{ mA}$$

$$\therefore 0.22 > 0$$

∴ Right assumption for  $D_1$

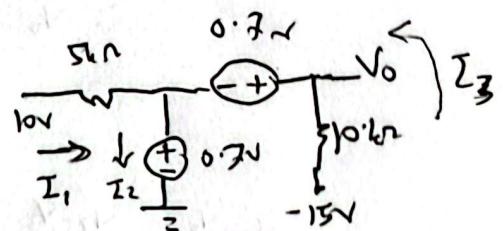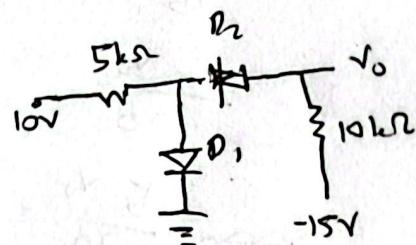


Assuming, - ii

$D_1 = 0_n$

$D_2 = \text{off}$

$$I_1 = 1.86 \text{ mA}$$

$$I_1 = I_2 = 1.86$$

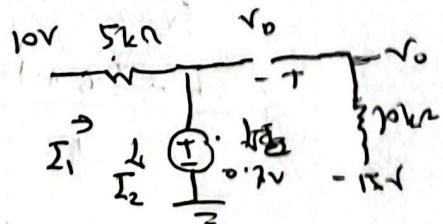

$$\therefore 1.86 > 0.$$

$\therefore$  Right assumption for  $D_1$

$$V_d = -15 - 0.7 = -15.7$$

$$\therefore -15.7 < 0.7$$

$\therefore$  Right assumption for  $D_2$

$$\therefore V_d = -15V.$$


$\therefore$  Assumption-ii correct.

9

Assuming,  $D_1$  is off,  $D_2$  is on

$$\frac{V_n - 5}{2} = -5$$

$$\therefore V_n = -5V$$

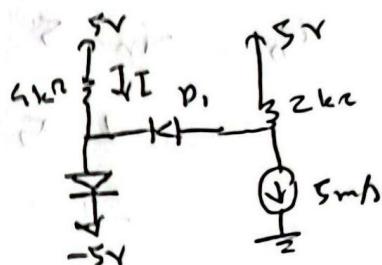


~~V<sub>n</sub>~~

$$5 + 5 = 4I + 0.7$$

$$\therefore \Sigma = 2.325 > 0$$

$\therefore D_2$  is on

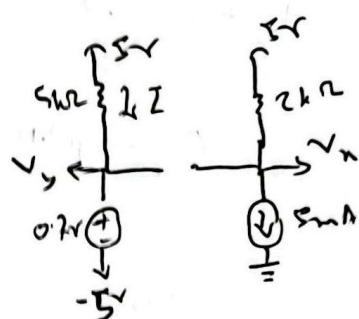

$$\frac{V_y - 5}{1} = -2.325$$

$$\therefore V_y = -4.35$$

$$V_y = -5 + 4.35$$

$$\approx -0.65$$

$\therefore -0.65 < 0$

$\therefore D_1$  is off

$\therefore$  Assumption correct

15

Assuming,

$$D_1 = \text{off}$$

$$D_2 = \text{on}$$

$$V_o = 0.7V$$

$$\frac{V_n - 0.7}{2} \approx 0$$

$$\therefore V_n \approx 0.7$$

$$V_{D_1} = V_n - 5$$

$$\approx 0.7 - 5$$



$$= -4.3 < 0$$

~~$$10 > 5 \Rightarrow I = 5 \text{ mA} > 0$$~~

$\therefore$  Assumption correct.

$$V_o, \quad 5 = \frac{V_o - 0.7 + 5}{1}$$

$$\therefore V_o \approx 0.7V$$

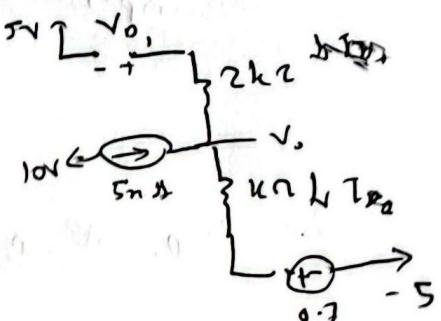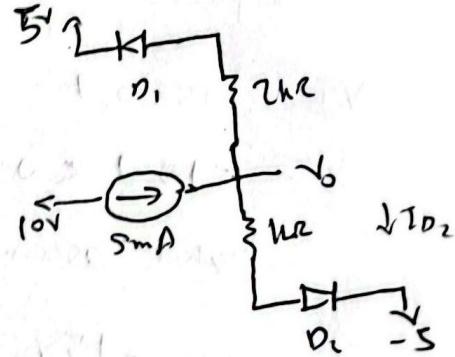

16

Assuming,

Both  $D_1, D_2$  on

KCL,

$$i) I_{D_1} + 0.5 = I_{D_2}$$

$$\therefore I_{D_1} - I_{D_2} = -0.5 \dots (i)$$

$$5 + 5 = 0.7 + 2I_{D_1} + 0.7 + 10I_{D_2}$$

$$\Rightarrow 10 - 2 \times 0.7 = 2I_{D_1} - 10I_{D_2}$$

$$\therefore 2I_{D_1} + 10I_{D_2} = 8.6 \dots (ii)$$

$$I_{D_1} = 0.3 > 0$$

$$I_{D_2} = 0.8 > 0$$



KCL on  $V_A$ ,

$$I_{D_1} + 0.5 = I_{D_2}$$

$$\Rightarrow \frac{5 - V_A - 0.7}{2} + 0.5 = 0.8$$

$$\therefore V_A = 3.7 V$$

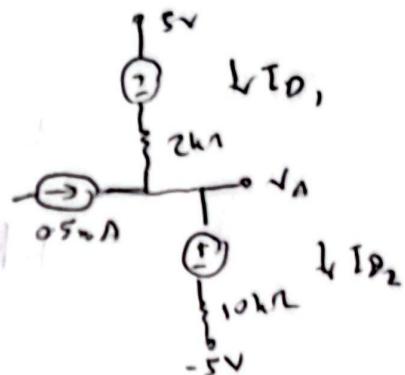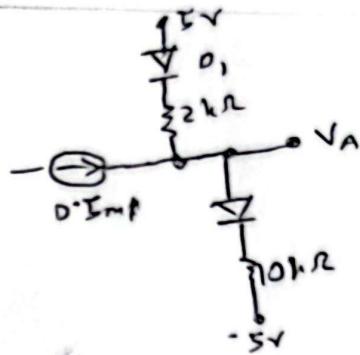$\therefore D_1$  and  $D_2$  both on.  
∴ Assumption correct.




Ans. to the Ques. No. - 3

Part-ii

$$\frac{1}{ii}$$

$$A \cdot C + B \cdot D$$

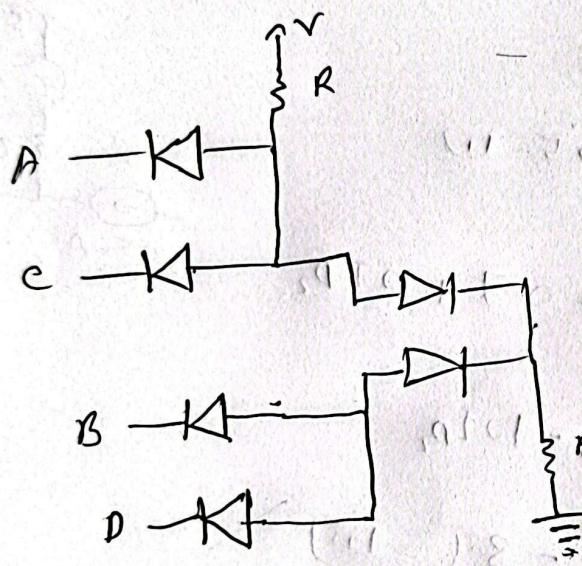

3

$x$	$y$	$z$	$f$
4V	3V	4V	4V
5V	3V	4V	4V
13V	3V	4V	4V