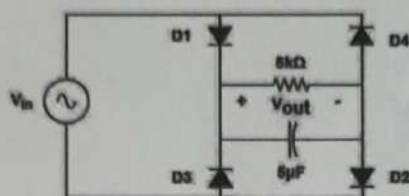


Student ID:		Section:	
Name:			

[CO2] [8+4+3+3+7]



Here,  $V_m = 10\sqrt{2} \sin 500\pi t$

[All diodes are with silicon having forward voltage drop  $V_{D0} = 0.6V$ ]

1. Show the input and output waveform in separate planes considering there is no capacitor connected parallel to the load resistor in the diagram. [You need to label the peak voltage and time period appropriately for both waveforms].
2. Justify all 4 diodes of a Full Wave rectifier can not be ON at the same time.
3. Calculate peak to peak ripple voltage of the output.
4. Calculate the DC or Average value of the output.
5. Consider the new peak to peak ripple voltage is 50% of the previous value of it found in question 3 and the new ripple frequency is 300 Hz. Now keeping the load resistor and capacitor value same as mentioned in the diagram, find the new equation of the input waveform of this Full Wave rectifier.

$$\textcircled{3} \quad V_{o(p-p)} = \frac{V_p}{f_{ro} RC}$$

$$= 1.0352V$$

(Am)

$$V_p = V_m - 2V_{D0}$$

$$= 12.94$$

$$f_{ro} = 25042$$

$$= 500$$

$$R = 5 \times 10^3 \Omega$$

$$C = 5 \times 10^{-6} F$$

$$\textcircled{4} \quad V_{DC} = V_p - \frac{V_{o(p-p)}}{2}$$

$$= 12.94 - 0.5176 = 12.4224V \text{ (Am)}$$

5

$$V_{ro}'(p-p) = \frac{50}{100} \text{ of } V_m'(p-p)$$

$$= 0.5 \times 1.0352 = 0.5176 \text{ V}$$

$$f_{ro}' = 300 \text{ Hz}$$

$$\therefore V_{ro}'(p-p) = \frac{V_p'}{f_{ro}' RC}$$

$$\Rightarrow V_p' = 3.882 \text{ V}$$

$$\text{now } V_p' = V_m' - 2V_D$$

$$\therefore V_m' = 5.082 \text{ V}$$

$$\begin{aligned} \therefore V_m &= V_m' \sin \omega t \\ &= V_m' \sin 2\pi f \\ &= 5.082 \sin 300\pi t \\ &\quad (\text{Am}) \end{aligned}$$

$$\omega = 2\pi f$$

$$f = \frac{1}{2} f_{ro}'$$

$$= 150$$



BRAC UNIVERSITY  
Dept. of Computer Science and Engineering


Quiz 4  
CSE251: Electronic Devices and Circuits  
Total Marks: 25  
Time: 25 minutes

Student ID:

Section:

Name:


[CO2, CO3] [4+6+15+3]

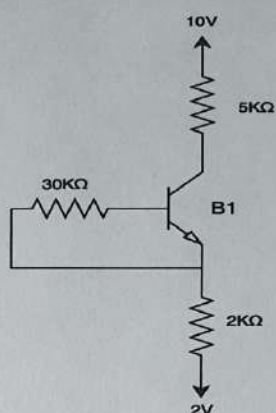


For the BJT,  $\beta = 200$

1. Draw the **equivalent circuit** of a BJT when it is operating in **active region**.
2. Design the logic function  $f = (x+yz)z$  using BJTs. [Note that  $x, y, z$  are voltages]
3. Calculate the values of base, collector, emitter voltages and currents that is  $V_B, V_C, V_E$  and  $I_B, I_C, I_E$  for the BJT above. [You need to verify your assumption].
4. Make a **meme** about your current situation. [Bonus]

①

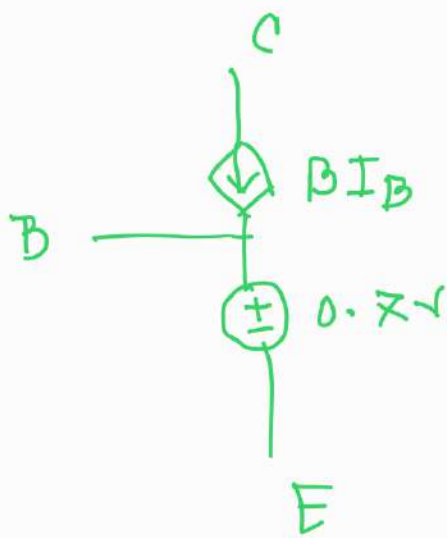

②

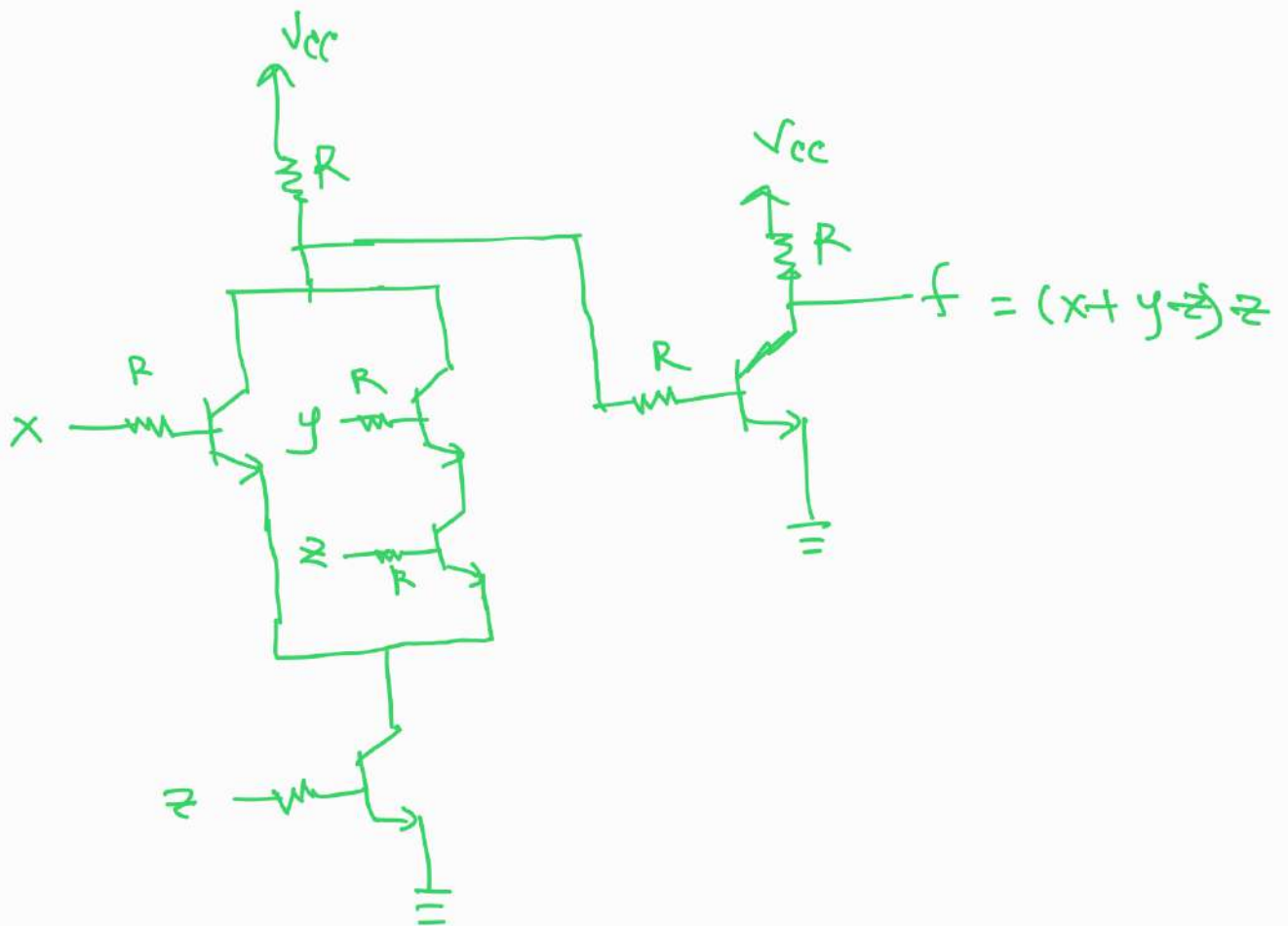

Here  $\beta = 200$


③ Assumption 1,  $B_1 \rightarrow$  cutoff

$\therefore$



Since

$$I_B = I_C = I_E = 0$$

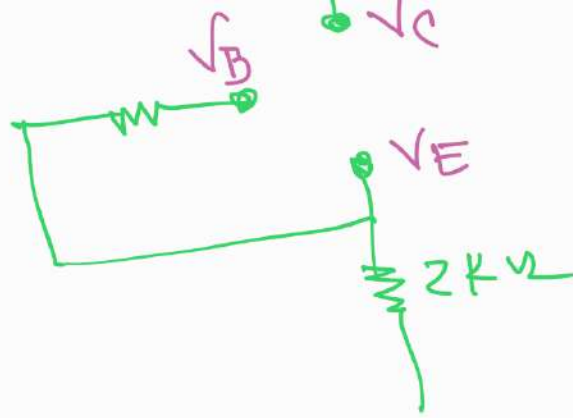

$$\therefore V_C = 10V$$

$$V_E = 2V$$

$$\text{and } V_B = V_E = 2V$$

$$\begin{aligned}\therefore V_{BE} &= V_B - V_E \\ &= 2 - 2 = 0V\end{aligned}$$

$$\begin{aligned}\therefore V_{BC} &= V_B - V_C \\ &= 2 - 10 \\ &= -8V\end{aligned}$$

Verification

$$\therefore V_{BE} \leq 0.7V$$

$$V_{BC} \leq 0.6V$$

$$\therefore I_B = I_C = I_E = 0$$

$$V_C = 10V$$

$$V_B - V_E = 2V$$

} (Ans)





BRAC UNIVERSITY  
Dept. of Computer Science and Engineering


Quiz 5  
CSE251: Electronic Devices and Circuits  
Total Marks: 25  
Time: 30 minutes

Student ID:

Section:

Name:

[CO2, CO3] [5+10+5+5]

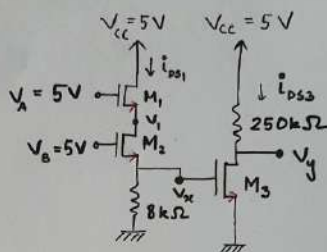

For the following circuit with MOSFETs, assume that  $V_t = 1V$ ,  $k_n' = 50 \mu A/V^2$  and the aspect ratio  $W/L$  is 1 for all the MOSFETs.

1. If the gate voltage to M3 MOSFET,  $V_g = 0.938V$ , and MOSFET M2 is in triode mode, find the voltage  $V_x$ .
2. Determine the value of  $V_y$ .
3. If  $W/L=2$ , then  $V_x = 2.1454V$ . Find  $V_g$  for this case.
4. Will there be any changes in the output voltage at  $V_y$  for  $W/L = 2$  from that in 'part-b'? Explain briefly. Also, comment on whether a larger or smaller value of  $W/L$  ratio is preferred in this case.

$$K'_n = 50 \mu A$$

$$\frac{W}{L} = 1$$

$$\therefore K = 0.05 mA/V^2$$

①

Given  $m_2 \rightarrow$  Triode

Assuming  $m_1 \rightarrow$  Saturation



$$\therefore I_{D1} = I_{D2}$$

ohm's law on  $4k\Omega$

$$I_{D1} = \frac{V_X - 0}{8} = \frac{V_X}{8} = \frac{0.038}{8} \quad \text{--- (1)}$$

From assumption (saturation)  
of  $M_1$

$$\begin{aligned} I_{D1} &= \frac{1}{2} k V_{ov1}^2 \\ \Rightarrow I_{D1} &= \frac{1}{2} \cdot 0.05 \cdot (4 - V_{S1})^2 \end{aligned} \quad \left. \begin{aligned} V_{ov1} &= V_{GS1} - V_T \\ &= 5 - V_{S1} - 1 \\ &= 4 - V_{S1} \\ V_{GS1} &= 5 - V_{S1} \end{aligned} \right\} \quad \text{--- (2)}$$

From (1) and (2)

$$\frac{0.038}{8} = \frac{0.05}{2} (4 - V_{S1})^2$$

$$\therefore \boxed{V_{S1} = 1.83435} \quad \checkmark \checkmark$$

or

$$V_{S1} = 6.16564$$

$\therefore$  verification

$$\text{for } M_1: \quad V_{GS1} = V_A = 5V$$

$$\sqrt{D_1} = \sqrt{e_c} = \bar{h} \sqrt{V}$$

$$\begin{aligned} \therefore \sqrt{Dh_1} &= \sqrt{D_1} - \sqrt{h_1} \\ &= \bar{h} - 1.435 \\ &= 3.165 \end{aligned}$$

$$\begin{aligned} \sqrt{ov_1} &= 4 - \sqrt{h_1} = 4 - 1.435 \\ &= 2.565 \end{aligned}$$

$$\sqrt{Th_1} > \sqrt{ov_1}$$

and

$$\begin{aligned} \sqrt{Th_1} &= \bar{h} - 1.435 \\ &= 3.165 > \sqrt{T} = 1 \end{aligned}$$

(correct)

For  $m_2$ :

$$\sqrt{D_2} = \sqrt{h_1} = \sqrt{V} = 1.435$$

$$\sqrt{h_2} = \sqrt{x} = 0.034$$

$$\begin{aligned} \therefore \sqrt{Dh_2} &= \sqrt{D_2} - \sqrt{h_2} \\ &= 1.435 - 0.034 \\ &= 0.402 \sqrt{V} \end{aligned}$$

$$\begin{aligned} \sqrt{ov_2} &= \sqrt{ov_2} - \sqrt{T} \\ &= \bar{h} - 0.034 - 1 \\ &= 3.062 \end{aligned}$$

$$\therefore \sqrt{Dh_2} < \sqrt{ov_2}$$

Triangle  $\Rightarrow$  (correct)



$$\therefore \boxed{V_1 = 1.835 \text{ V}}$$

② For  $m_3$

$$V_{G3} = V_x = 0.938 \text{ V}$$

$$\begin{aligned} V_{G5m} &= V_{G3} - V_{H3} \\ &= 0.938 - 0 \\ &= 0.938 \end{aligned}$$

$$\therefore V_{G5m} < V_T = 1 \text{ V}$$

$$\therefore \boxed{\text{cutoff}} \quad \therefore I_{D53} = 0$$

$$\therefore V_g = V_{cc} = 5 \text{ V}$$

③  $\frac{W}{L} = 2$

$$I_{D51} = \frac{V_x}{R} = \frac{0.05}{2} \left( \frac{W}{L} \right) (5 - 2 \cdot 145 - 1)^2$$

$$\therefore V_x = 1.377 \text{ V}$$

④ No changes since  $m_3$  is cutoff.

