

## Lecture 11

Topic Name : \_\_\_\_\_

(Rough)

Day : \_\_\_\_\_

Time : \_\_\_\_\_

Date : / /


# DC value / Average value :

[# The signal must be periodic.]

$$V_{AV} = \frac{1}{T} \int_0^T v(t) dt$$

$T \rightarrow$  time period  
 $v(t) \rightarrow$  signal  
 $\int_0^T \rightarrow$  Time period.
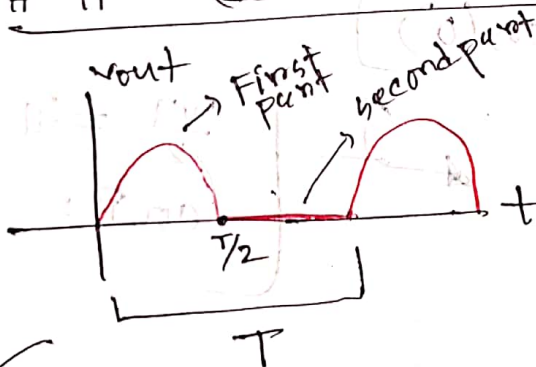
# H.W (Half wave rectifier) (Ideal diode) :



suppose input is  $V_{in} = V_m \sin(\omega t)$



$$\begin{aligned}
 \therefore \text{Area} &= \int_0^T v_{out}(t) dt \\
 &= \int_0^{T/2} v_{out}(t) dt + \int_{T/2}^T v_{out}(t) dt \\
 &= \int_0^{T/2} v_{out}(t) dt + 0
 \end{aligned}$$

$\int_0^{T/2} \rightarrow$  first part  
 $\int_{T/2}^T \rightarrow$  second part

Topic Name : \_\_\_\_\_

Day : \_\_\_\_\_

Time : \_\_\_\_\_ Date : / /

$$= \int_0^{T/2} V_m \sin(\omega t) dt$$

[For H.W. rectification  
of ideal diode  
 $V_{out} = V_{in}$ ]

$$= V_m \int_0^{T/2} \sin(\omega t) dt$$

$$= V_m \left[ -\frac{\cos \omega t}{\omega} \right]_0^{T/2}$$

$$= V_m \left[ \frac{1}{\omega} \right]$$

$$= V_m \frac{1}{\omega} \left[ -\cos\left(\frac{\omega T}{2}\right) + \cos(0) \right]$$

$$= V_m \cdot \frac{1}{\omega} \cdot 2$$

$$= V_m \frac{1}{\frac{2\pi}{T}} \cdot 2$$

$$= \frac{T \cdot V_m}{\pi}$$

$$= \frac{T}{\pi} V_m \rightarrow \text{only Area.}$$

$\therefore$  Average/dc value of H.W.R.

$$V_{AV} = \frac{\text{Area}}{T} = \frac{T}{\pi} V_m \cdot \frac{1}{T} = \frac{1}{\pi} V_m$$


$$\therefore V_{AV} = \frac{1}{\pi} V_m$$

Topic Name : \_\_\_\_\_

Day : \_\_\_\_\_

Time : \_\_\_\_\_ Date : / /

## H.W.R (Real diode)

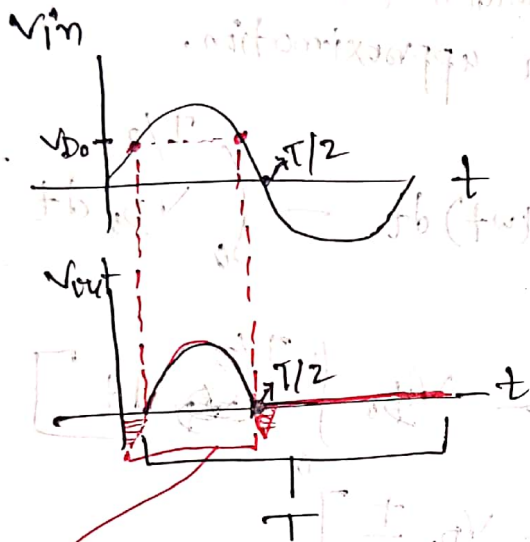

$$v_{in} = V_m \sin(\omega t)$$

$$v_{out} = V_m \sin(\omega t) - V_{D0}$$

∴ Area of output waveform:

$$\frac{1}{T} \int_0^T v_{out}(t) dt$$

$$= \frac{1}{T} \int_0^{T/2} v_{out}(t) dt + \int_{T/2}^T v_{out}(t) dt$$

$$= \frac{1}{T} \int_0^{T/2} v_{out}(t) dt + 0$$

$$= \frac{1}{T} \int_0^{T/2} [V_m \sin(\omega t) - V_{D0}] dt$$

but this not 100%

exact correct equation because if we consider it small part of wave still include below the time axis

Topic Name : \_\_\_\_\_

Day : \_\_\_\_\_

Time : \_\_\_\_\_

Date : / /

but as  $V_{D0} = 0.7V$  is too small

we can take consider this

(+ve) error. This is an approximation.

$$= \frac{1}{T} \left[ \int_0^{T/2} V_m \sin(\omega t) dt - \int_0^{T/2} V_{D0} dt \right]$$

$$= \frac{1}{T} \left[ \frac{T}{\pi} V_m - V_{D0} \int_0^{T/2} dt \right]$$

$$= \frac{1}{T} \left[ \frac{T}{\pi} V_m - V_{D0} \frac{T}{2} \right]$$

↓  
only Area.

↓  
 $V_{AV}$   
Average Value / DC Value of  
H.W.R (real diode)

$$V_{AV} = \frac{1}{\pi} V_m - \frac{1}{2} V_{D0}$$

↓  
Half wave rectifier  
loss (real diode)



Topic Name : \_\_\_\_\_

Day : \_\_\_\_\_

Time : \_\_\_\_\_ Date : / /

~~Full~~

Full wave rectifier (F.W.R) (Ideal diode)

Average Value / DC value,

$$V_{AV} = \frac{2}{\pi} V_m$$


[similar way, you can  
prove it.]

Topic Name : \_\_\_\_\_

Day : \_\_\_\_\_

Time : \_\_\_\_\_ Date : / /

## Full wave rectifiers (Real diode)

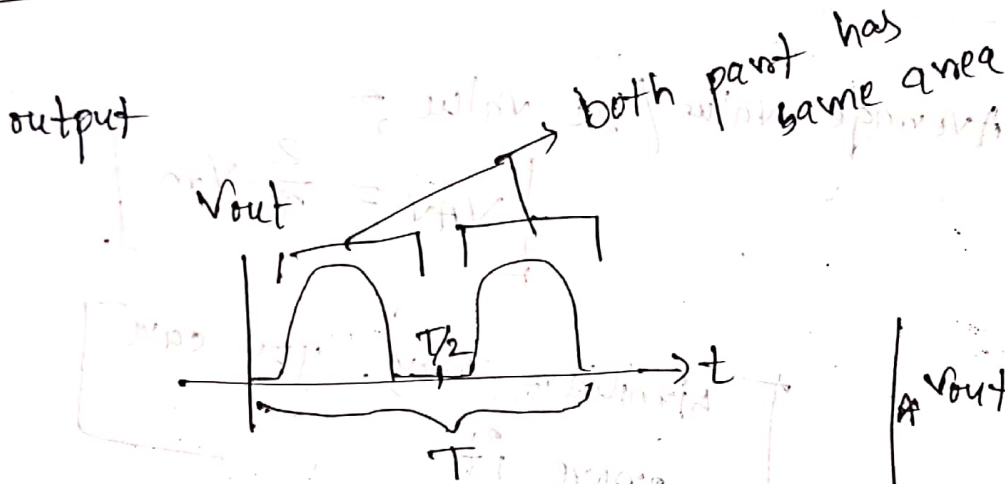

$$V_{out} = V_m \sin(\omega t) - 2V_{Do}$$

$$\therefore \text{Area} = \int_0^T V_{out}(t) dt$$

$$= 2 \int_0^{T/2} V_{out}(t) dt$$

$$= 2 \int_0^{T/2} [V_m \sin(\omega t) - 2V_{Do}] dt$$

$$= 2 \left[ \int_0^{T/2} V_m \sin(\omega t) dt - \int_0^{T/2} 2V_{Do} dt \right]$$

$$= 2 \left[ \frac{T}{\pi} V_m - 2V_{Do} \frac{T}{2} \right]$$

Topic Name : \_\_\_\_\_

Day : \_\_\_\_\_

Time : \_\_\_\_\_ Date : / /

$$\therefore V_{AV} = \frac{A_{area}}{T}$$

$$\therefore \boxed{V_{AV} = \frac{2}{\pi} V_m - 2V_{D0}} \quad \checkmark \text{ F.W. rectifiers (Real diode) Average / DC value}$$

$$\boxed{\begin{array}{l} V_m = \text{input peak} \\ V_p = \text{output peak} \end{array}} \quad \text{summary}$$

H.W. rectifiers F.W. rectifiers

Model		H.W. rectifiers	F.W. rectifiers
Ideal diode	Peak value of output $V_p$	$V_m$	$V_m$
Real diode (CVD)	Peak value of output $V_p$	$V_m - V_{D0}$	$V_m - 2V_{D0}$
Ideal diode	Average/DC value, $V_{AV}$ or $V_{DC}$	$\frac{1}{\pi} \cdot V_m$	$\frac{2}{\pi} \cdot V_m$
Real diode (CVD)	Average/DC value, $V_{AV}$ or $V_{DC}$	$\frac{1}{\pi} \cdot V_m - \frac{1}{2} V_{D0}$	$\frac{2}{\pi} \cdot V_m - 2V_{D0}$

Topic Name : \_\_\_\_\_

Day : \_\_\_\_\_

Time : \_\_\_\_\_ Date : / /

Ex: 4

~~Supp~~  $V_{in} = 5 \sin(\omega t)$

and  $V_{D0} = 0.7$

what is  $V_{DC}/V_{AV}$  for F.W. rectifier (Real diode)?

Soln:

$$V_{DC} \text{ or } V_{AV} = \frac{2}{\pi} V_m - 2V_{D0}$$

$$= \frac{2}{\pi} \cdot 5 - 2 \times 0.7$$

$$= 1.7830 \text{ V (Ans)}$$

Here

$$5 \sin(\omega t)$$

$$V_m \sin(\omega t)$$

$$\therefore V_m = 5$$

Load  
resistor  
connected

Load  
resistor  
disconnected

Load  
resistor  
connected

Load  
resistor  
disconnected

Load  
resistor  
connected

Load  
resistor  
disconnected

Load  
resistor  
connected

Load  
resistor  
disconnected

Load  
resistor  
connected



Topic Name : \_\_\_\_\_

Day : \_\_\_\_\_


Time : \_\_\_\_\_

Date : / /


## Pulsating to Flat DC

### # Rectifier - smoothing


without  
cap  
smoothing

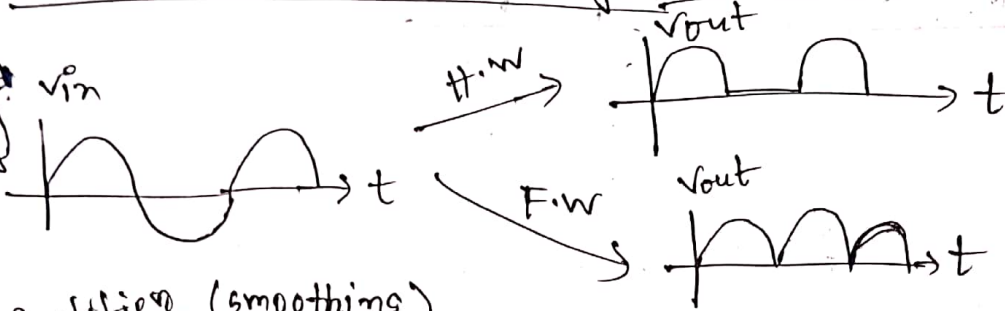

### H.W Rectifier (smoothing)

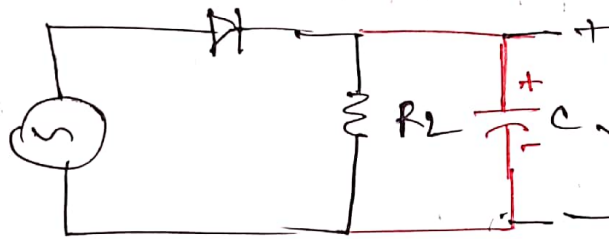


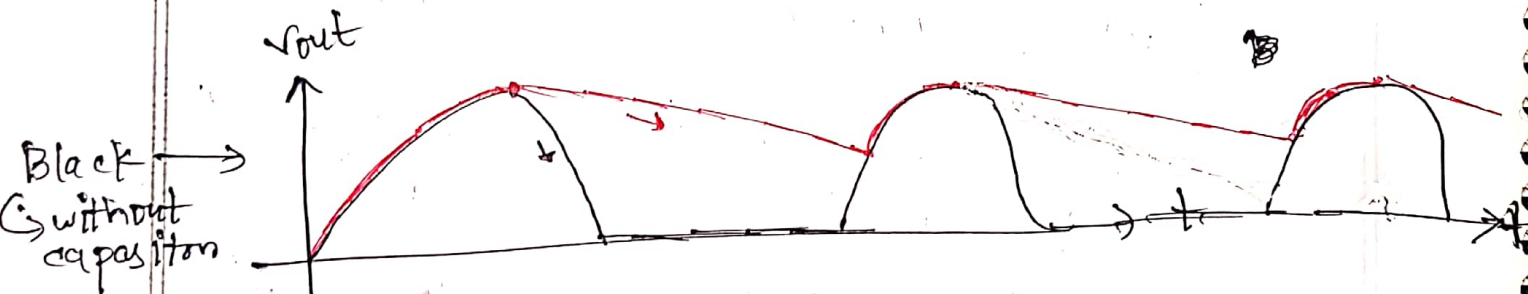Just need to add a capacitor parallel to the load resistor



Red with capacitor

so we get  
after  
smoothing

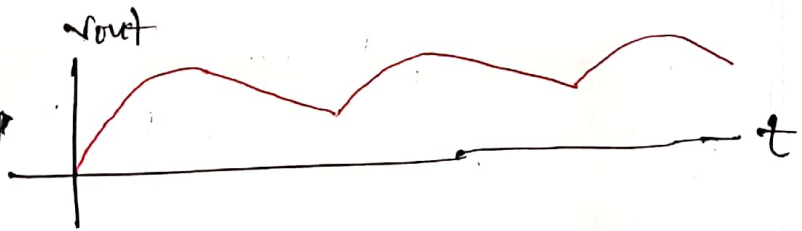

capacitor  $\rightarrow$  stores charges  
 $\rightarrow$  does not allow to fall the voltage suddenly.

⊛ if capacitance (capacitor value) is high enough it will discharge slowly.

Topic Name : \_\_\_\_\_

Day : \_\_\_\_\_

Time : \_\_\_\_\_ Date : / /




⊕ If ~~cap~~ value of capacitor is slow, it will discharge fastly.

So, what do we want?

⇒ As we want on our Aim is to ~~Ac to~~ make Ac to Dc. That is Dc is flat. And since higher value of capacitor provide more flat output as it discharge slowly. So we want higher value of capacitor.

For full wave rectifiers

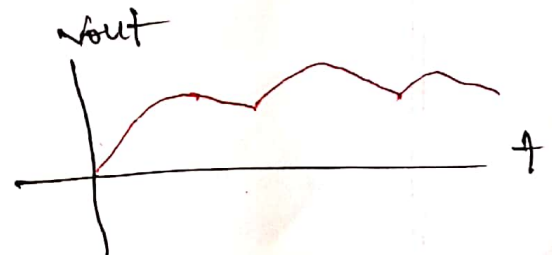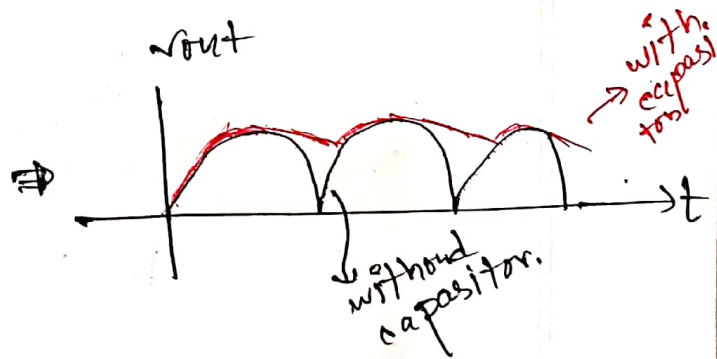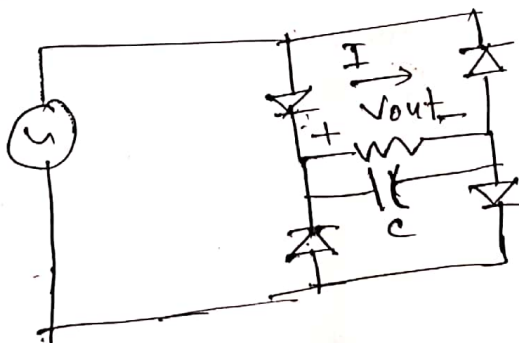same as half wave, just need to add a capacitor parallel to load.



Topic Name : \_\_\_\_\_


Day : \_\_\_\_\_

Time : \_\_\_\_\_

Date : / /


But they are not still smooth enough.

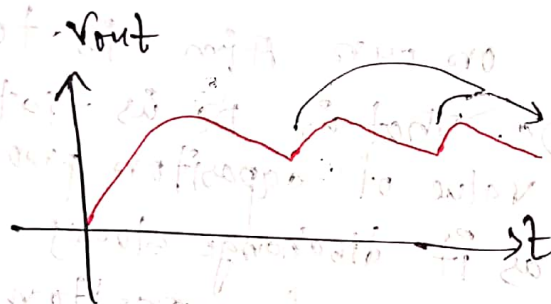They are like wave and the small wave called Ripple.



The less Ripple we have in our output the more flatter will be it.

Figure

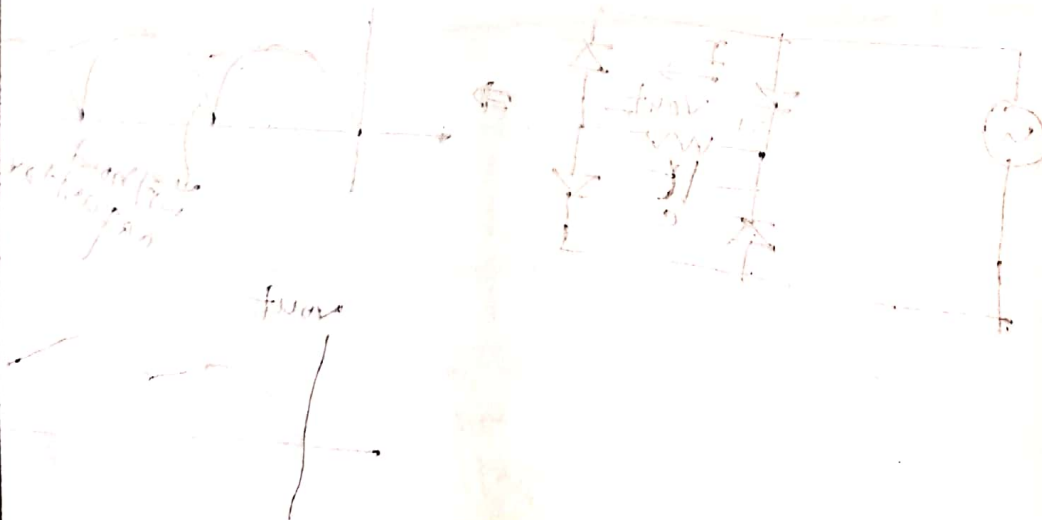


Topic Name : \_\_\_\_\_

Day : \_\_\_\_\_

Time : \_\_\_\_\_ Date : / /

H.W rectifier

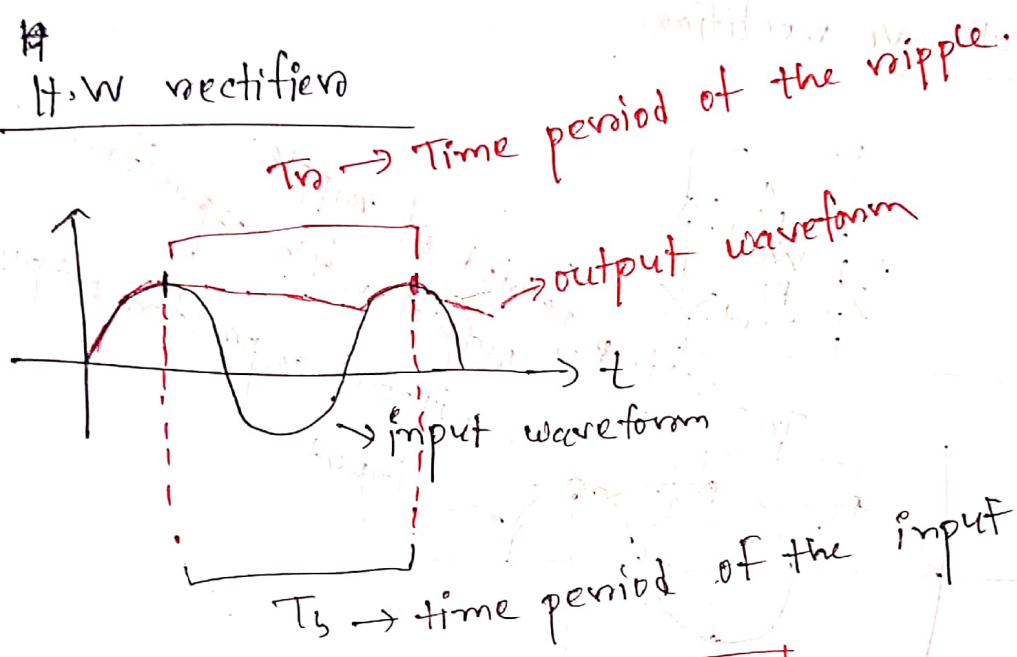

$$\therefore T_r = T_s$$

Now we know, frequency  $f = \frac{1}{T}$

$$\therefore f_r = f_s$$

frequency  
of the  
ripple

frequency  
of the signal.





Topic Name : \_\_\_\_\_

Day : \_\_\_\_\_

Time : \_\_\_\_\_ Date : / /

## For Fullwave rectifier

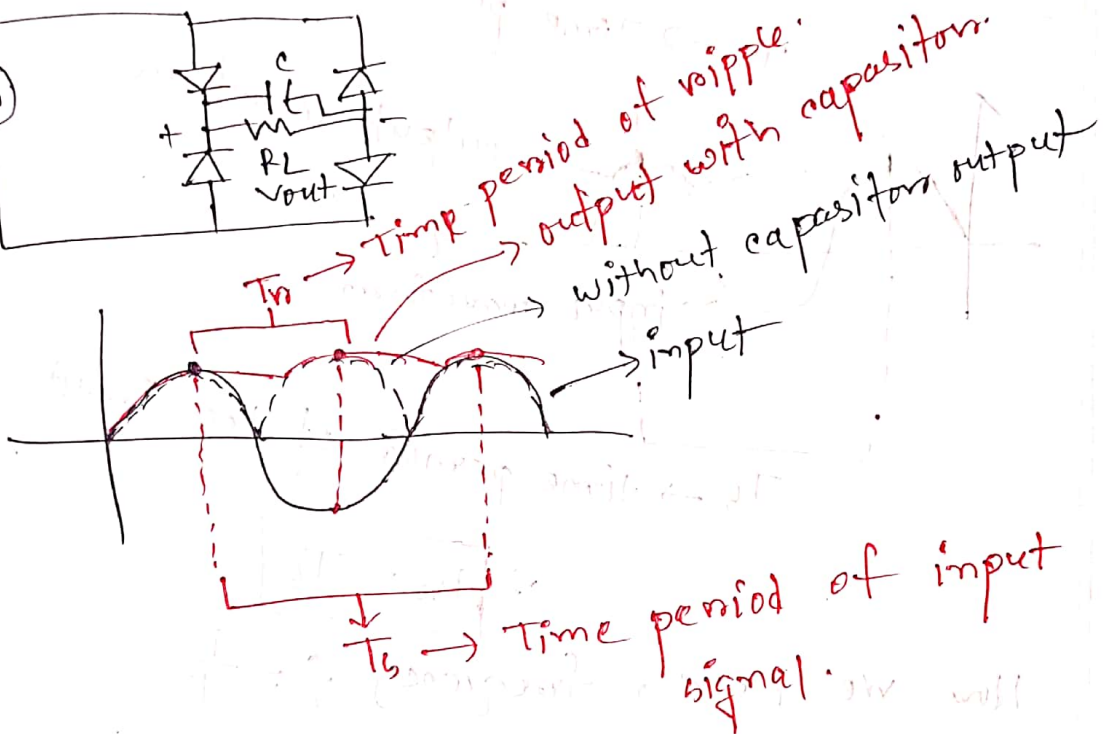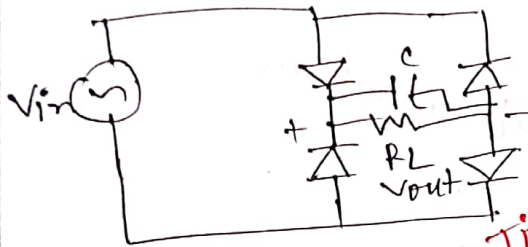

$$\therefore T_{in} = \frac{T_b}{2}$$

Again  $f = \frac{1}{T}$

$$\therefore f_{in} = 2f_b$$

frequency of ripple

frequency of signal (input)

Topic Name : \_\_\_\_\_


Day : \_\_\_\_\_

Time : \_\_\_\_\_

Date : / /
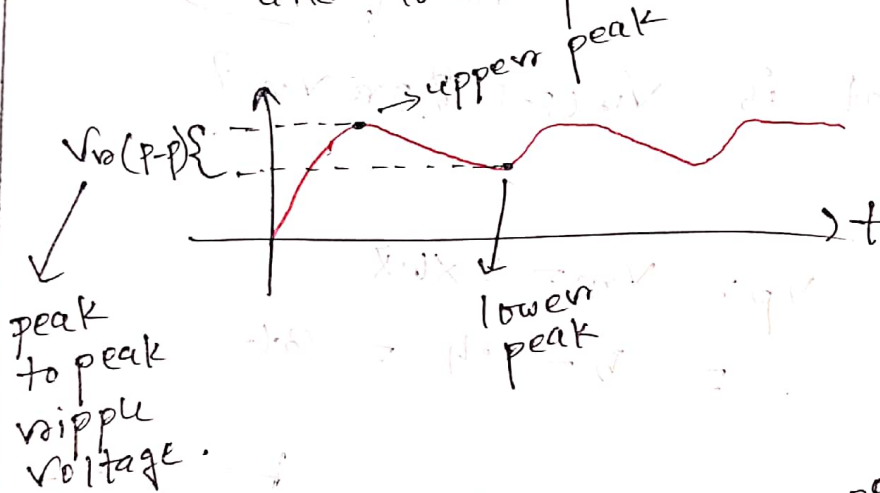
## # Peak to peak Ripple voltage ( $V_{r(p-p)}$ or $V_r$ )

Basically, voltage difference of upper peak and lower peak of the ripple.



$$\therefore V_r (\text{peak to peak}) = \frac{V_p}{f_r \cdot RC}$$

$\swarrow$  or  $V_r$  ripple voltage       $\downarrow$  frequency of ripple

Both for H.W and F.W rectifier

$R$  = output/Load resistor value  
 $C$  = capacitance value

Topic Name : \_\_\_\_\_

Day : \_\_\_\_\_

Time : \_\_\_\_\_

Date : / /

Ex:

$$V_i = 5 \sin(2\pi \times 60 \times t) ; \text{ F.W. rectifier}$$

$$R = 10 \text{ k}\Omega, C = 10 \mu\text{F}, V_{D_0} = 0.7 \text{ V}$$

$$\downarrow \text{micro } 10^{-6}$$

Ⓐ what is  $V_r(p-p)$  or  $V_r$ ?

$$\text{Soln: } V_p = V_m + 2 \times 0.7$$

$$= 5 + 1.4 = 3.6$$

$$\text{Here } \omega = 2\pi \times 60$$

$$\Rightarrow 2\pi f = 2\pi \times 60$$

$$\Rightarrow f = 60$$

$$\omega = 2\pi f$$

frequency of ripple,

$$f_r = 2f_s$$

$$= 2 \times 60$$

$$= 120 \text{ Hz}$$

$$[f_s = f = 60]$$

$$\therefore V_r \text{ or } V_r(p-p) = \frac{V_p}{f_r \times R \times C} = \frac{3.6}{120 \times (10 \times 10^3) \times (10 \times 10^{-6})}$$

$$= \frac{3}{10} = 0.3 \text{ V (Ans)}$$


Topic Name : \_\_\_\_\_

Day : \_\_\_\_\_

Time : \_\_\_\_\_

Date : / /

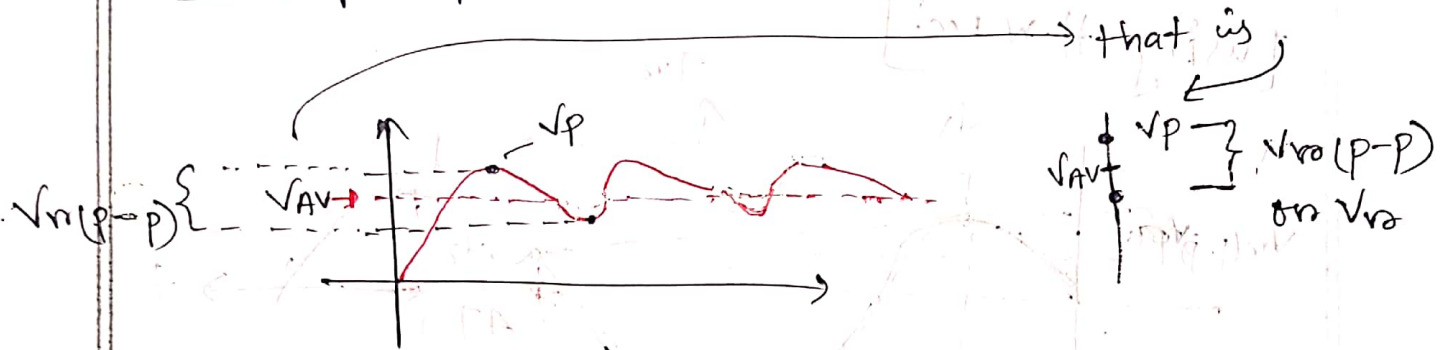what will be the DC/Average value after adding capacitor?  $V_{AV}$  or  $V_{DC}$



$$V_{AV} \text{ or } V_{DC} = V_p - \frac{V_{p-p}}{2}$$

$$V_{rms} = \frac{V_{p-p}}{2\sqrt{3}} = \frac{V_p}{2\sqrt{3}f_n \cdot RC}$$

summary

	HW	FW
ripple frequency, $f_{ro}$	$f_s$	$2f_s$
$V_{p-p}$ on $V_{ro}$	$\frac{V_p(\text{output})}{f_n \cdot RC}$	$\frac{V_p(\text{output})}{f_{ro} \cdot RC}$
$V_{AV} / V_{DC}$ after adding capacitor	$V_p - \frac{V_{p-p}}{2}$	$V_p - \frac{V_{p-p}}{2}$

~~Vrms~~

$$\frac{V_{p-p}}{2\sqrt{3}f_{ro}RC}$$



Topic Name : \_\_\_\_\_

[ Don't need any derivation ]


Day: \_\_\_\_\_

Time: \_\_\_\_\_

for exam, Date: \_\_\_\_\_

[ Derivation of  $V_o(p-p) = \frac{V_p}{f_r \times RC}$  ]

[using H.W Rec.]

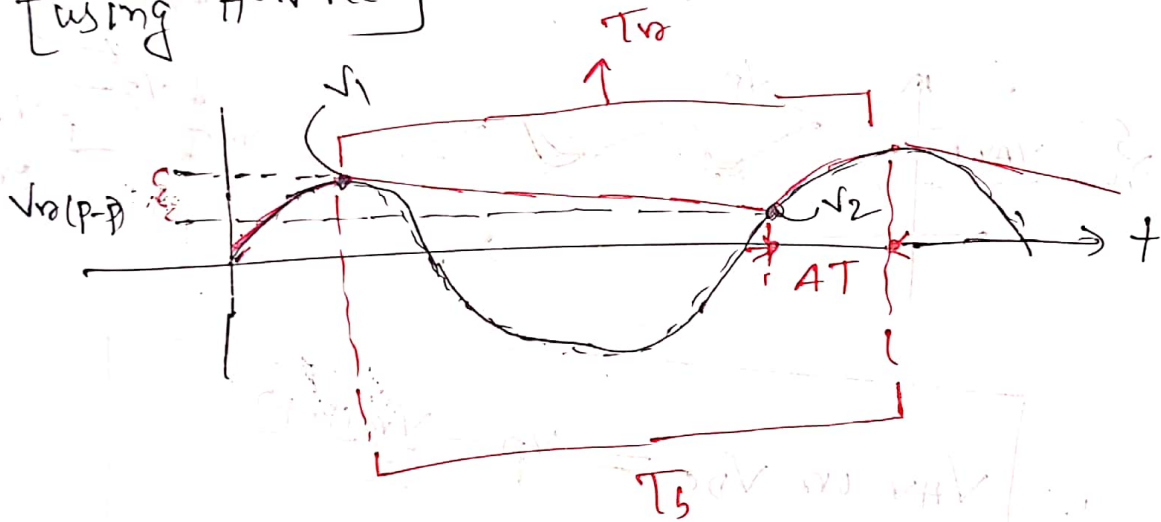

$\therefore$  Discharging time of capacitor  $(T_s - 4T)$   
 $4T \rightarrow$  charging time



Voltage of cap.  $V_c(t) = V_o e^{-t/RC}$

$V_1 = V_p e^{-(T_s - 4T)/RC}$   
 $V_2 = V_p e^{-4T/RC}$

Topic Name : \_\_\_\_\_

Day : \_\_\_\_\_

Time : \_\_\_\_\_ Date : / /

Assumptions

1.  $AT \ll T_b$

$$\therefore V_2 \approx V_p e^{-T_b/RC}$$

$$= V_p \left[ 1 + \left( -\frac{T_b}{RC} \right) + \left( -\frac{T_b}{RC} \right)^2 \frac{1}{2!} + \left( -\frac{T_b}{RC} \right)^3 \frac{1}{3!} + \dots \right]$$

2.  $T_b \ll RC$

So,  $\rightarrow \approx V_p \left[ 1 - \frac{T_b}{RC} \right]$

How  $\therefore V_p(p-p) = V_1 - V_2$

$$= V_p - V_p \left[ 1 - \frac{T_b}{RC} \right]$$

$$= V_p \cdot \frac{T_b}{RC}$$

$$= \frac{V_p}{f_b \cdot RC}$$

$[T_b = \frac{1}{f_b}]$

Similarly,

F.w  $V_p(p-p) = \frac{V_p}{2f_b \cdot RC}$

Topic Name : \_\_\_\_\_

Day : \_\_\_\_\_

Time : \_\_\_\_\_ Date : / /

Q.0

$$V_{ro} (p-p) = \frac{V_p}{f_r \times RC}$$

$$V_{DC} = \frac{V_1 + V_2}{2}$$
$$= V_1 - \frac{V_0}{2}$$