
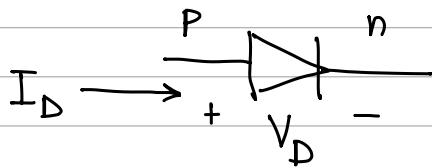


Diode (Lecture-2)

22/2/21

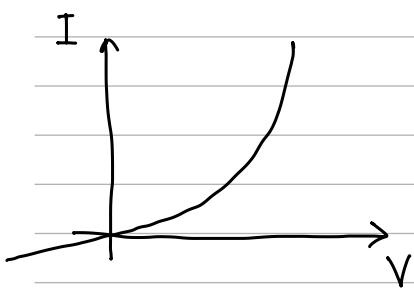


$$D) I_D = I_s \left[\exp\left(\frac{V_D}{nV_T}\right) - 1 \right] \quad | \quad \text{(Constant Voltage Drop)}$$




Approximation :

$$- I_D > 0 : V_D = 0.7 \text{ V}$$

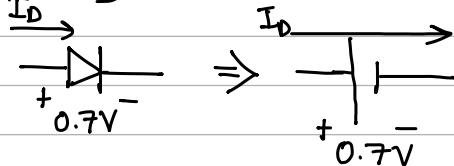


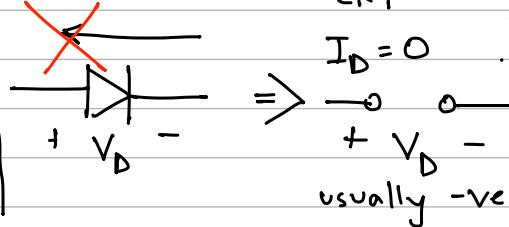- $I_D < 0$ if ckt tries to do this : Diode "open ckt"




3) Ideal model :

- $I_D > 0$: Diode "shorted"

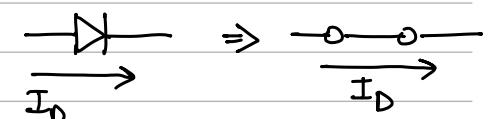

- $I_D < 0$: Diode "open"

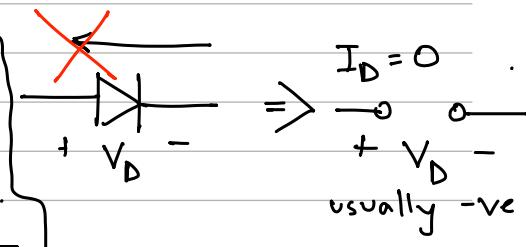


Diode has 2 states : ① ON ② OFF
 $[I_D > 0]$ $[I_D = 0]$

Objective : ① Solve circuit with diodes and finding the right state of operation of diodes.

② Assume a state of operation, then solve the ckt, then check if diode state is consistent with its operating conditions.

This method of solving : Method of Assumed States
 [MAS]


Example 1:

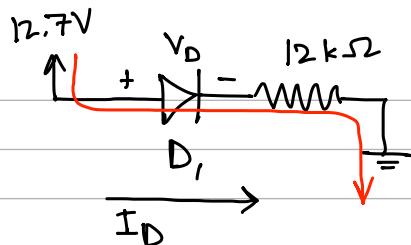


find I_D .

$I_D > 0$ since ckt tries to flow current from source to ground.

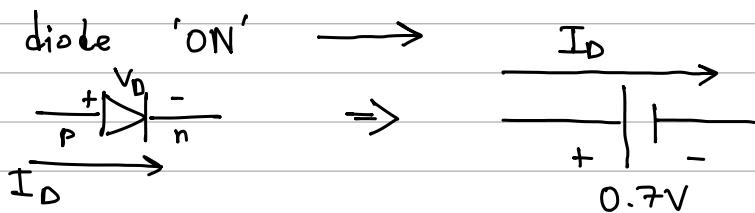\therefore Diode should be 'ON'. Assume D_1 is 'ON'.



Ckt becomes:

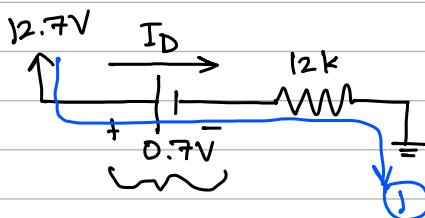

Line ① KVL:

$$0.7 + 12I_D = 12.7 - 0$$

$$\Rightarrow I_D = \frac{12.7 - 0.7}{12}$$

We know, diode 'ON':


$$I_D > 0, V_D = 0.7V \quad = 1 \text{ mA}$$

$$\rightarrow I_D = 1 \text{ mA} \quad \text{W} [I_D > 0]$$

$$\rightarrow V_D = 0.7V \quad \text{W} [V_D = 0.7V]$$

\therefore Assumption correct! Ckt solved!


Ex 2:

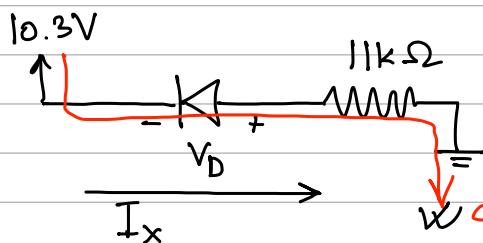

Find I_x .

W ckt tries to flow current like this.

Assume Diode 'ON':

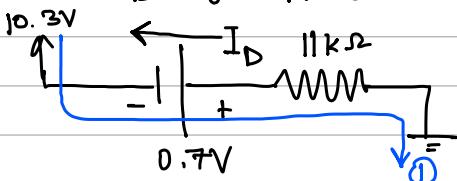

but $I_D < 0$. Diode should be OFF

Line ① KVL:

$$-0.7 + 11I_x = 10.3 - 0$$




$$I_x = \frac{11}{11} = 1 \text{ mA}$$

$$I_D = -I_x = -1 \text{ mA} \Rightarrow I_D < 0$$

\therefore Inconsistency. So, assumption wrong.

\therefore So, Diode must be OFF

Assume Diode 'OFF' :

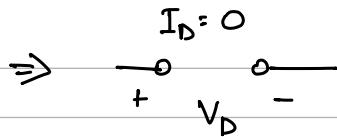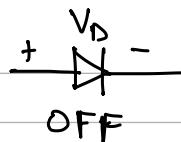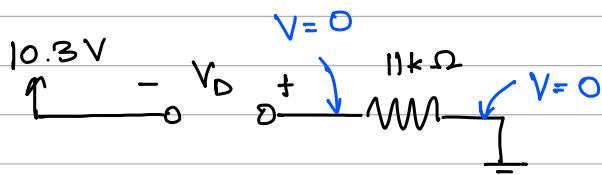


$$I_x = 0, I_D = 0$$

$$V_D = 0 - 10.3 = -10.3 \text{ V}$$

Diode OFF: $I_D = 0, V_D -\text{ve} (< 0.7 \text{ V})$

Ex 2:

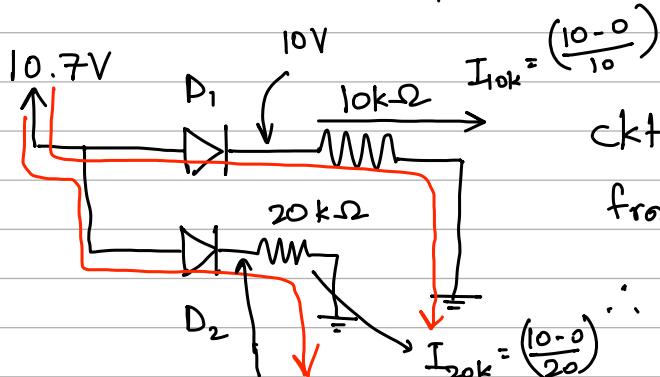

Ckt trying to flow current from p side of both diodes

Assume D_1, D_2 ON :

$$0.7 + 10I_1 = 10.7 - 0$$


$$I_1 = \frac{10}{10} = 1 \text{ mA}$$

$$0.7 + 20I_2 = 10.7 - 0$$


$$\Rightarrow I_2 = \frac{10}{20} = 0.5 \text{ mA}$$

$$I = I_1 + I_2 = 1.5 \text{ mA}$$

Ex 3:

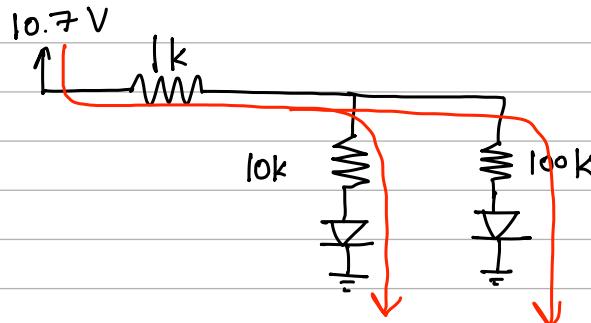

Assume diodes ON :

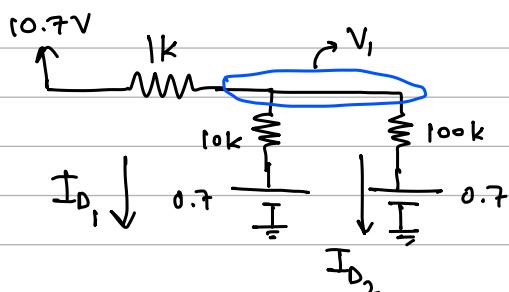

$$\frac{V_1 - 10.7}{1} + \frac{V_1 - 0.7}{10} + \frac{V_1 - 0.7}{100} = 0$$


$$\Rightarrow 100V_1 - 1070 + 10V_1 - 7 + V_1 - 0.7 = 0$$

$$\Rightarrow 111V_1 = 1077.7 \Rightarrow V_1 = 9.709 \text{ V}$$

$$I_{D_1} = \frac{V_1 - 0.7}{10k} = 0.9009 \text{ mA} > 0 \quad D_1 \text{ 'ON' correct}$$

$$I_{D_2} = \frac{V_1 - 0.7}{100k} = 0.09009 \text{ mA} > 0 \quad D_2 \text{ 'ON' correct}$$


Ex 4:

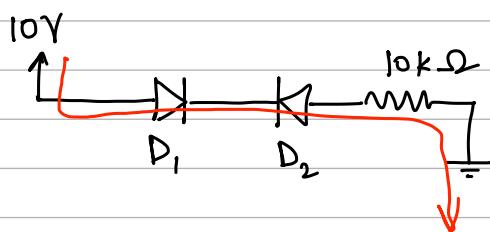

D₁ should be ON. But


D₂ should be OFF

D₁ ON, D₂ OFF :

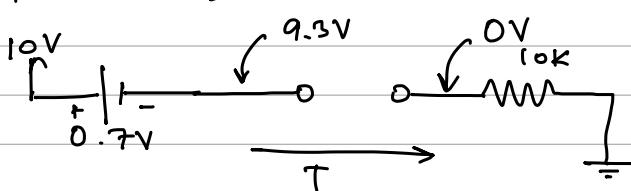


I = 0. D₁ cannot be ON! Inconsistency, V_{D₂} = -9.3V D₂ assumption must likely correct.

Then, D₁, D₂ OFF :

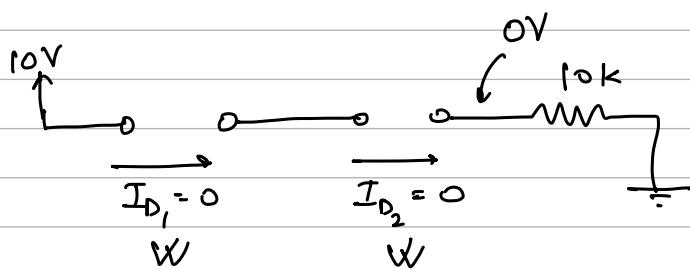


D₁, D₂ off is correct assumption.

Ex 5:

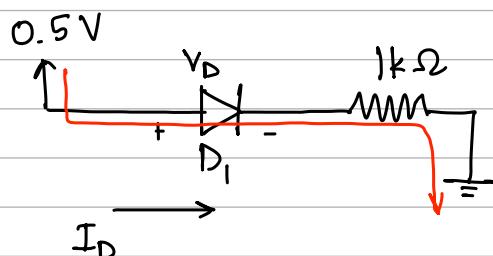

Assume D₁ 'ON': Line ① KVL:



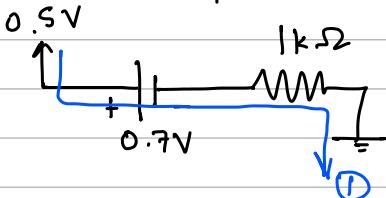


$$0.7 + I \times 1 = 0.5 - 0$$


$$\Rightarrow I = 0.5 - 0.7 = -0.2 \text{ mA} < 0$$

$\Rightarrow I < 0$: Diode cannot be 'ON'

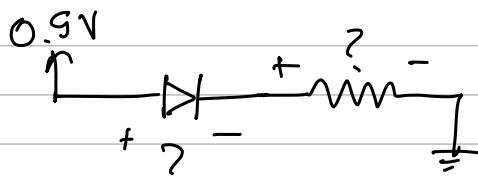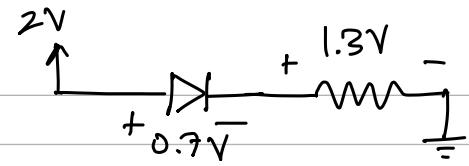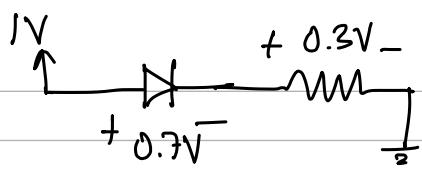Diode is 'OFF'. Ckt must provide 0.7V drop to diode to function and turn on diode.



* If $V_s = 0.7V$:

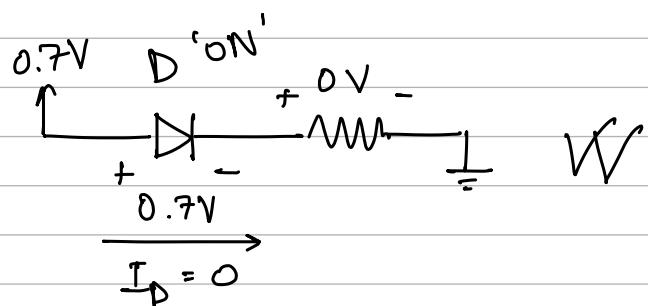


Diode Logic :

→ Can implement AND, OR Logic.

→ Can't implement NOT logic. [OV input \rightarrow 5V output]


Since, diode cannot generate voltage on its own.

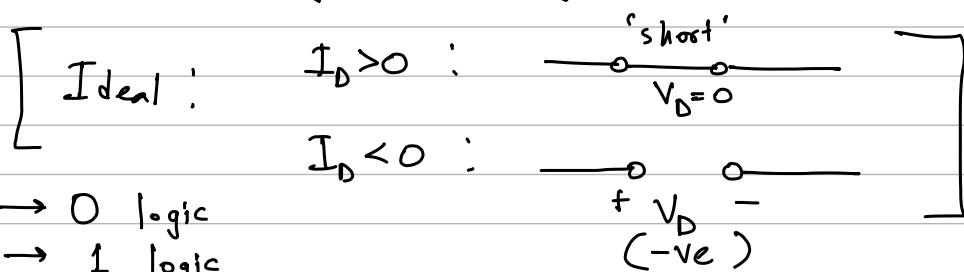→ We will verify diode logic with ideal diode model.



OV \rightarrow 0 logic
5V \rightarrow 1 logic

OR Logic :

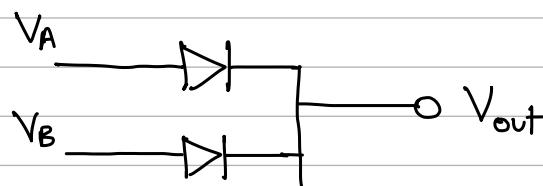


(0) (0)
 $V_A = 0V, V_B = 0V$

(0) (1)
 $V_A = 0V, V_B = 5V$


(1) (0)

$V_A = 5V, V_B = 0V$


$V_A = 5V, V_B = 5V$

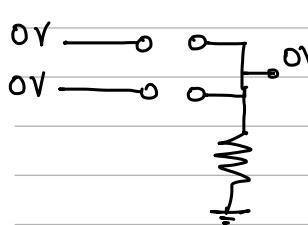


$$V_{out} = 0V$$

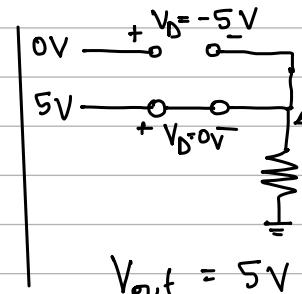

$$V_{out} = 5V$$

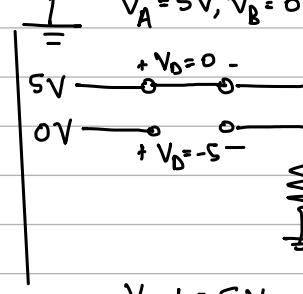


$$V_{out} = 5V$$

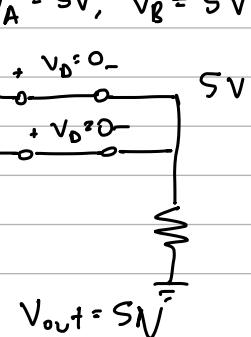


$$V_{out} = 5V$$

V_A	V_B	V_{out}
0	0	0
0	5	5
5	0	5
5	5	5


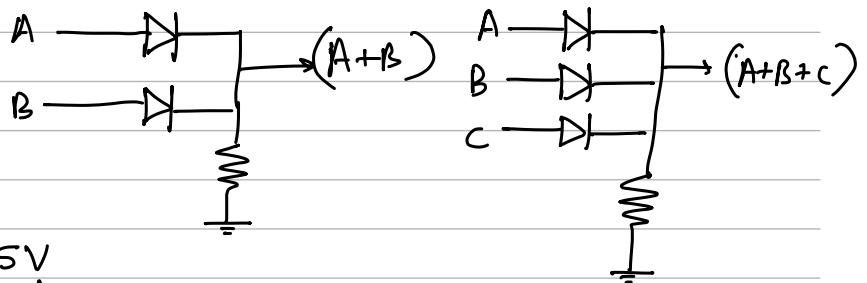


AND Logic :

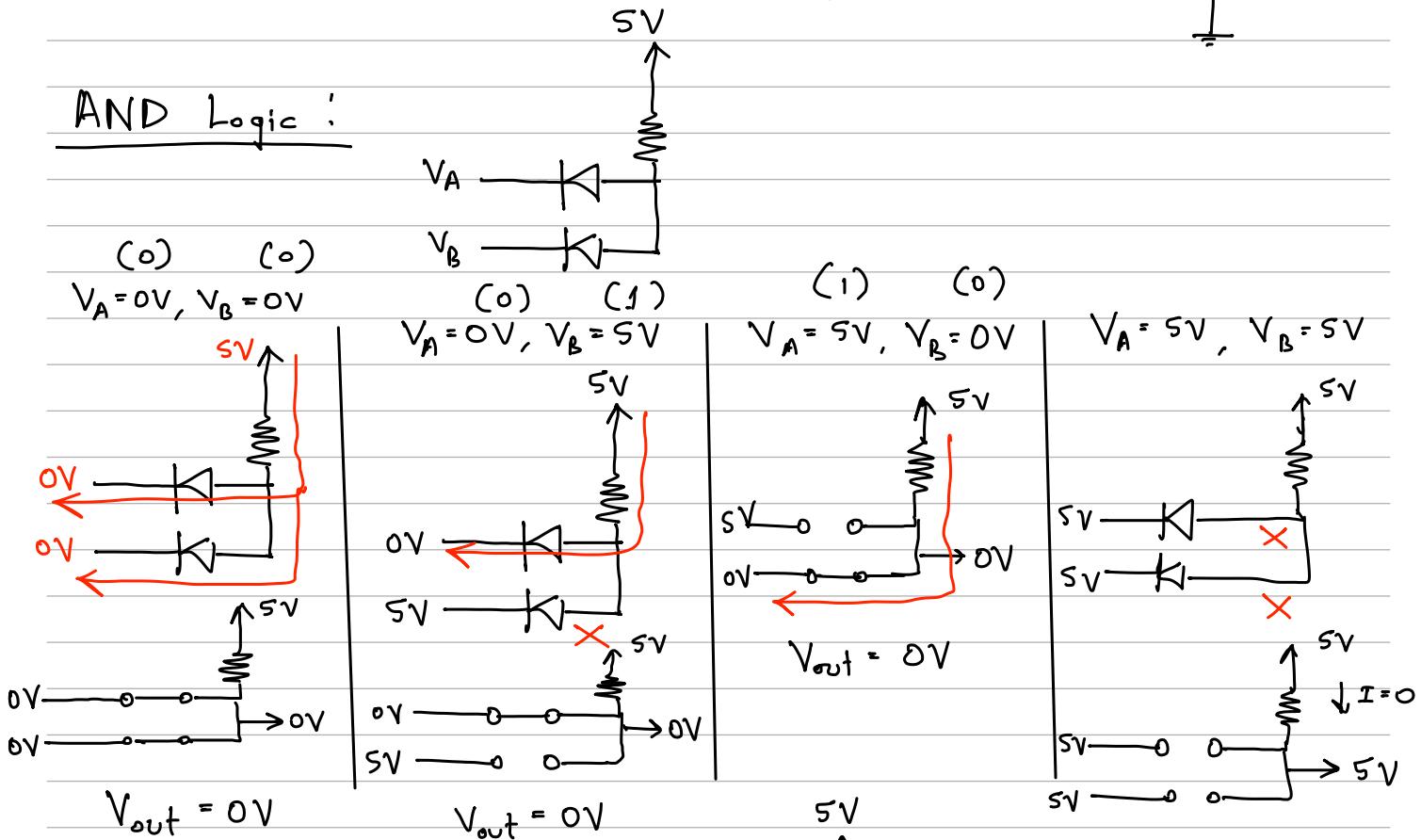

V_A	V_B	V_{out}
0	0	0
0	5	0
5	0	0
5	5	5

'AND'

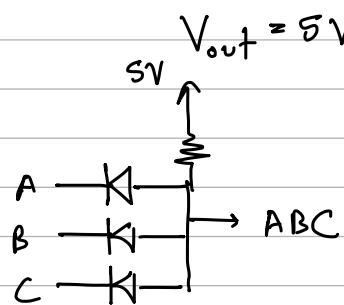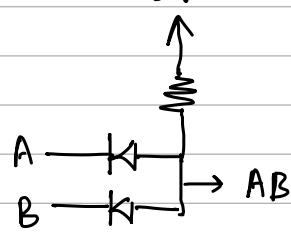


* Input high voltage and low voltage is same for these ($5V$) ($0V$) analysis.

If not kept same, they implement something different.


* We can implement complex boolean logic with these gates.
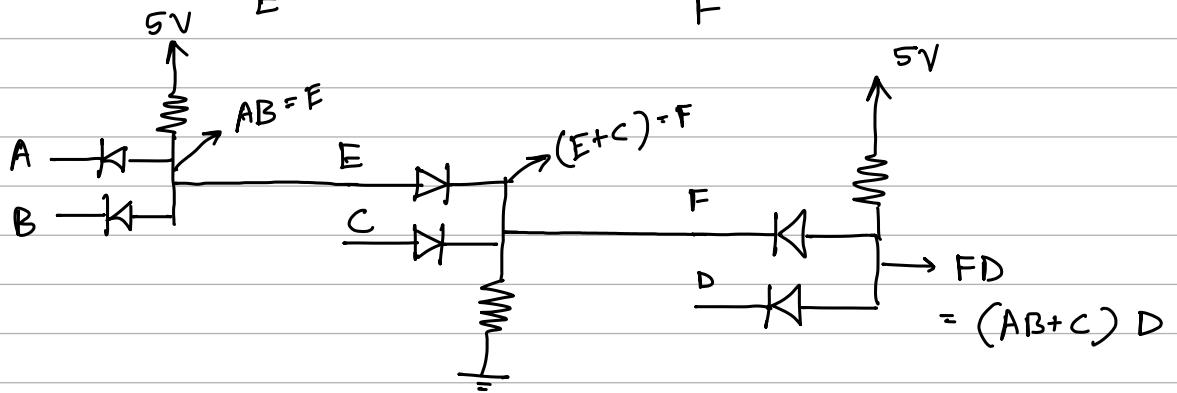
$$\text{Ex: } f = \underbrace{(AB + C)}_E D = \underbrace{(E + C)}_F D = FD$$



Q. What happens for unequal voltage in OR / AND logic?


① OR :

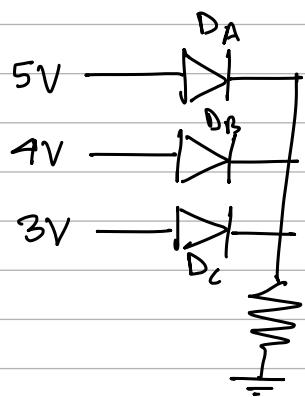

Ckt looks like all 3 should be ON.


[all 3 should conduct current in right dir]

Assume all 3 'ON' :

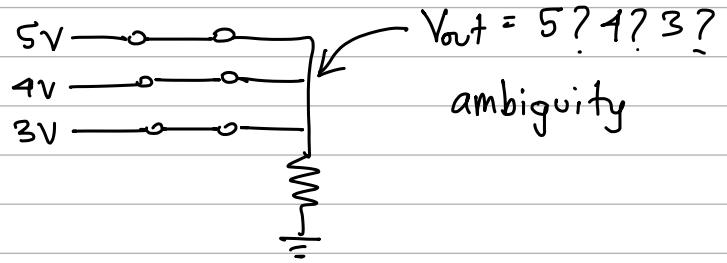

①


If $V_{out} = 5V$:

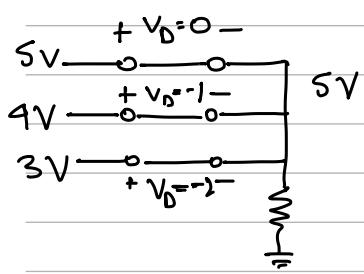

D_A is correct [$V_D = 0$]
 $I_D > 0$

②

If $V_{out} = 4V$

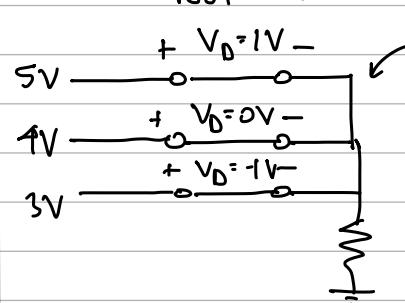

D_A must be on [$V_D = 1V$]


③

D_B, D_C wrong [$V_D < 0$]

$\Rightarrow V_{out}$ must be $5V$

Then D_B, D_C must be off


$\therefore 5V$ diode only ON. Rest off.

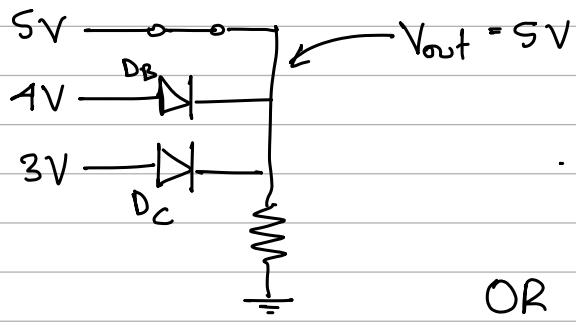

$$\therefore V_{out} = \max(V_A, V_B, V_C)$$


OR gate replicates max function. Gives max of input voltages.

AND:

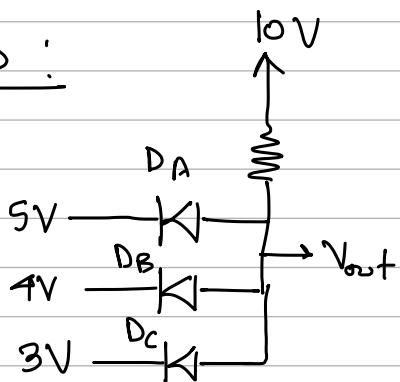


Current should flow through all three?

Then

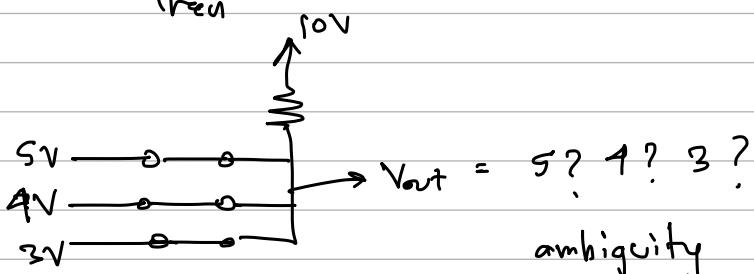

If $V_{out} = 5V$:

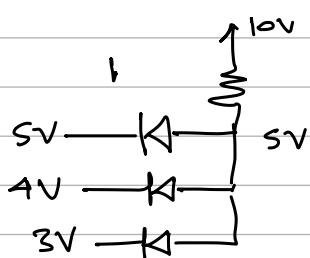

D_A 'ON' \rightarrow short


D_B 'ON' $\rightarrow V_D = 5 - 1 = 4V$

D_C 'ON' $\rightarrow V_D = 5 - 3 = 2V$

but V_{out} cannot be 3V, 4V, 5V at once



$V_{out} = 4V$:

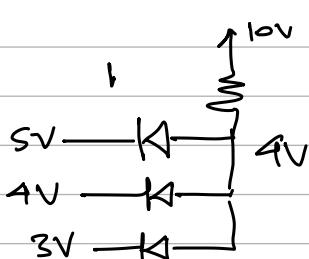

D_A 'OFF' $\rightarrow V_D = -1V$


D_B 'ON' $\rightarrow V_D = 0V$ [short]

D_C 'ON' $\rightarrow V_D = 4 - 3 = 1V$

V_{out} cannot be 4V, 3V at once



$V_{out} = 3V$:

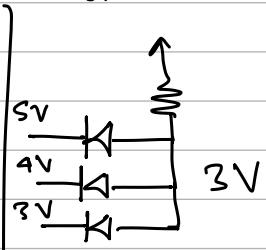

D_A 'OFF' $\rightarrow V_D = -2V$

D_B 'OFF' $\rightarrow V_D = -1V$

D_C 'ON' $\rightarrow V_D = 0V$

$V_{out} = 3V$



no ambiguity.

\therefore Correct is $V_{out} = 3V$. D_A, D_B OFF. D_C ON.

Thus, implementing

$$V_{out} = \min(V_A, V_B, V_C)$$

* OR ckt with unequal inputs: $V_{out} = \max(V_1, V_2, \dots, V_n)$
AND " " " " " : $V_{out} = \min(V_1, V_2, \dots, V_n)$

* When inspecting such unequal input ckt's, find case where
 V_{out} has no ambiguity.