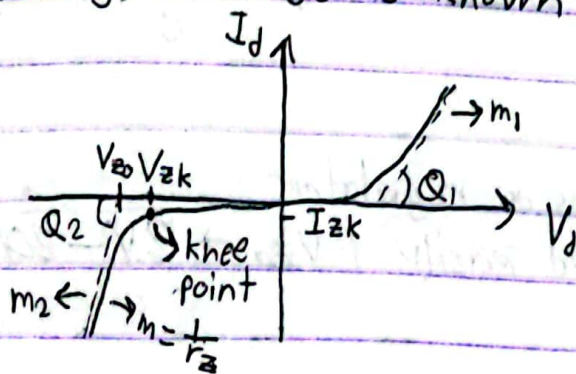



Breakdown Region:

- * In reality current does flow in the opposite direction of a diode but it is really small i.e. $10^{-9} \sim 10^{-12} A$
- * At a certain negative voltage, current starts to flow through a diode just like it does when the diode is on this ~~voltage~~ voltage is known as Breakdown region.




$$\begin{aligned} Q_2 &> Q_1 \\ \tan Q_2 &> \tan Q_1 \\ m_2 &> m_1 \\ \frac{1}{r_2} &> \frac{1}{r_1} \\ r_2 &< r_1 \end{aligned}$$

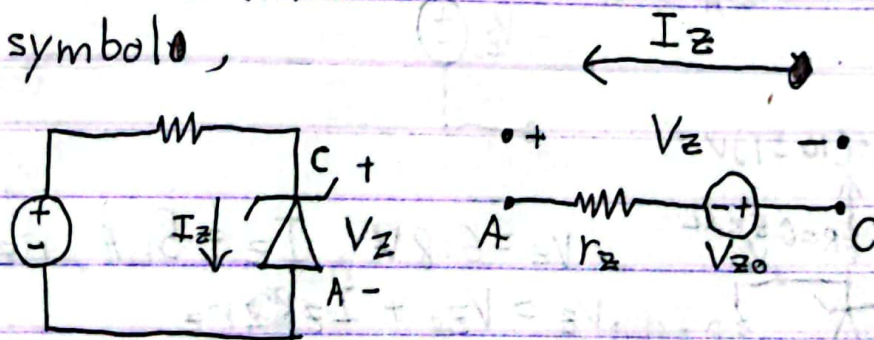
- * Normal diodes ~~are~~ become unusable if it goes to breakdown region once.
- * ~~Zener~~ Zener diodes can be used in the breakdown region.
- * These diodes are better regulators because the value of r is smaller as $r_2 < r_1$.
- * Zener diode symbol,





$$V_z = V_{z0} + I_z r_z$$

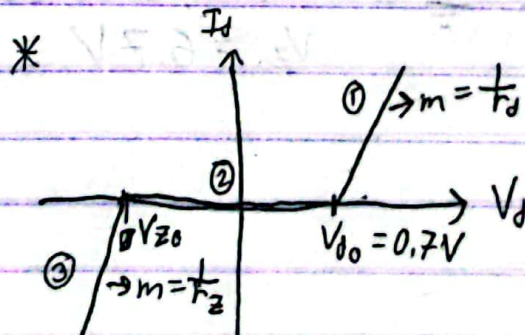

piecewise model of zener diode

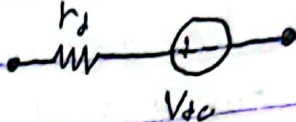• region - ①: $I_d > 0 \rightarrow \text{ON} \rightarrow$ 


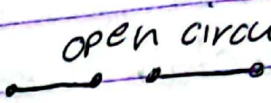
• region - ②: $-I_{zk} \leq I_d < 0 \rightarrow \text{OFF} \rightarrow$  open circuit

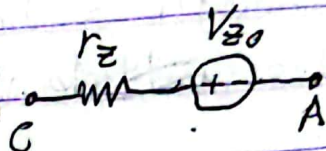• region - ③: $I_d < -I_{zk} \rightarrow \text{Breakdown Region} \rightarrow$ 


* Why use zener diode:

- $r_z < r_d \rightarrow$ works better as a regulator
- V_{zo} can be controlled easily ($V_{zo} \rightarrow 2V - 200V$)

* Example:

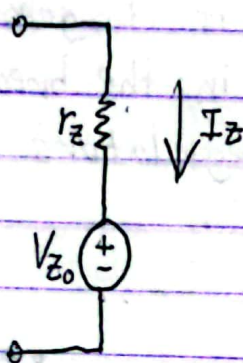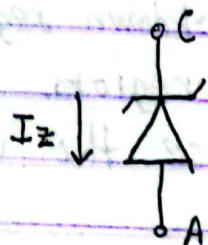

$$I_z > I_{zk}$$

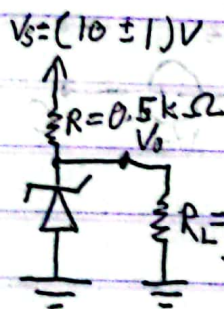


$$V_z = 6.8V, I_z = 5mA, r_z = 20\Omega, I_{zk} = 0.2mA$$

$$V_z = V_{zo} + I_z r_z$$

$$6.8 = V_{zo} + (5 \times 10^{-3} \times 20)$$

$$V_{zo} = 6.7V$$

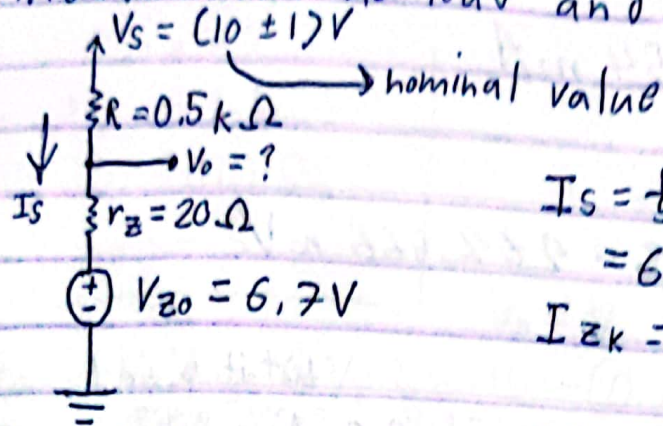① Find V_o with no load and V_s at its nominal value.



$$I_s = \frac{10 - 6.7}{500 + 20} = 6.34 \times 10^{-3} \text{ A} = 6.34 \text{ mA}$$


$$I_{zk} = 0.2 \text{ mA} \quad (I_s \text{ should be greater than } I_{zk})$$

$$\begin{aligned} V_o &= V_{Z0} + I_s r_z \\ &= 6.7 + 6.34 \times 10^{-3} \times 20 \\ &= 6.827 \text{ V} \end{aligned}$$

② $\pm 1 \text{ V}$ change in $V_s \rightarrow \Delta V_o = ?$

$$\frac{\Delta V_o}{\Delta V_s} = \frac{r_z}{R + r_z} = \frac{20}{500 + 20} = \frac{2}{52} = 0.038 \text{ V/V} = 38 \text{ mV/V}$$
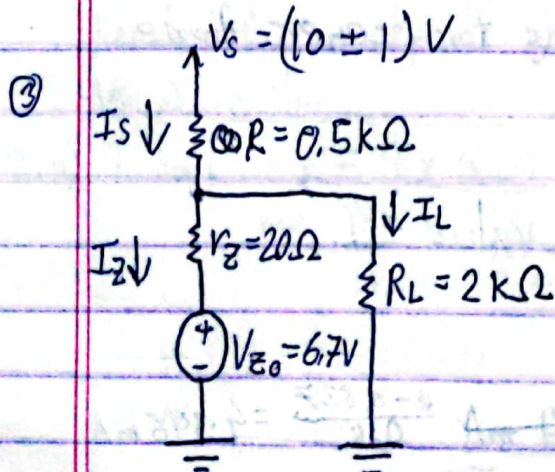
$$\Delta V_o = \Delta V_s \times 38 \text{ mV/V} = \pm 38 \text{ mV/V} \quad (\text{Line regulation})$$



$$V_o = 6.827 \text{ V}$$

$$\begin{aligned} I_L &= \frac{V_o}{R_L} \\ &= \frac{6.827}{2000} \\ &= 3.413 \text{ mA} \end{aligned}$$

$$\text{Load Regulation} \rightarrow \frac{\Delta V_o}{\Delta I_L} = \frac{-R r_z}{R + r_z} = \frac{-500 \times 20}{500 + 20}$$

$$\frac{\Delta V_o}{\Delta I_L} = -19.27 \text{ V/A} = -19.23 \text{ mV/mA}$$

$$\Delta V_o = 3.413 \times -19.23 = -65.632 \text{ mV}$$

④ $R_L = 0.5 k\Omega$

$$I_L = \frac{V_o}{R_L} = \frac{6.827}{0.5} = 13.654 \text{ mA}$$

$$\Delta I_L = 13.654 \text{ mA}$$

$$\frac{\Delta V_o}{\Delta I_L} = -19.23 \text{ mV/mA}$$

$$\Delta V_o = 13.654 \times -19.23 = -262.566 \text{ mV}$$


$$I_s = I_Z + I_L$$

$$6.36 = I_Z + 13.654$$

$$I_Z = -7.35 \text{ mA}$$

but it is not

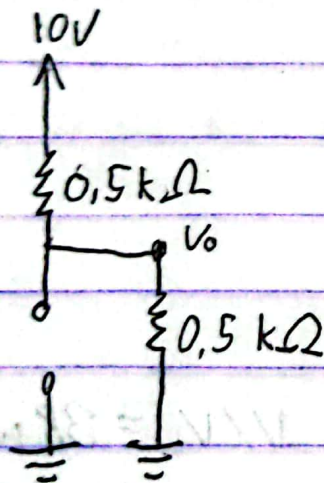$[I_Z > I_{ZK} = 0.2 \text{ mA}]$ so the zener diode will be off



$$V_o = 10 \times \frac{0.5}{0.5 + 0.5}$$


$$V_o = 5 \text{ V}$$

* Load resistance should be kept big for zener diode to work.

⑤ Minimum possible Load resistance value = ?

• $V_s \rightarrow \min$

• $I_z = I_{zk}$

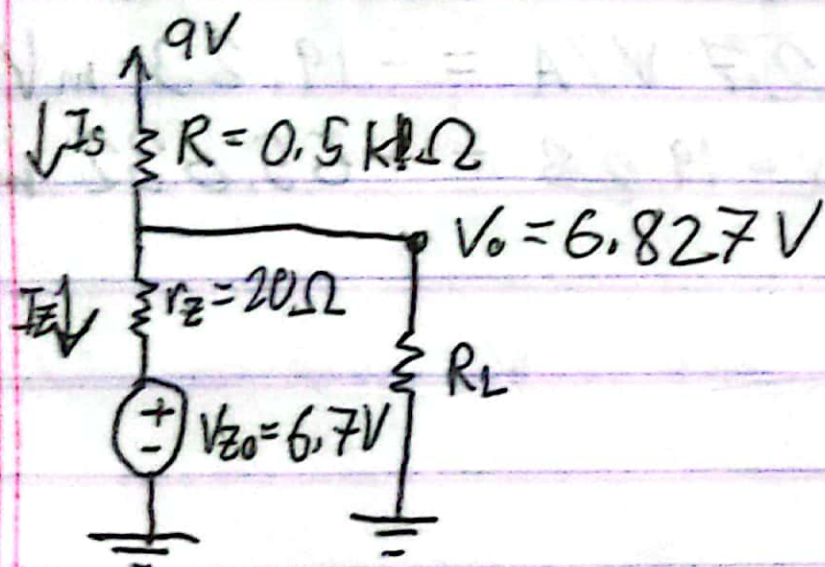

$$I_s = \cancel{6.34 \text{ mA}} \frac{9 - 6.827}{0.5} = 4.346 \text{ mA}$$

$$I_s = I_z + I_L$$

$$I_L = \cancel{0.84} \overset{4.346}{- 0.2} = \cancel{0.74} \overset{4.146}{\text{mA}}$$

$$R_L = \frac{V_o}{I_L} = \frac{6.827}{4.146} = 1.6466 \text{ k}\Omega$$

* The output voltage (V_o) is constant because Zener diode's purpose is to give a constant output voltage.