


## VTC (Voltage Transfer Characteristics):

Y axis → output voltage, X axis → Input voltage
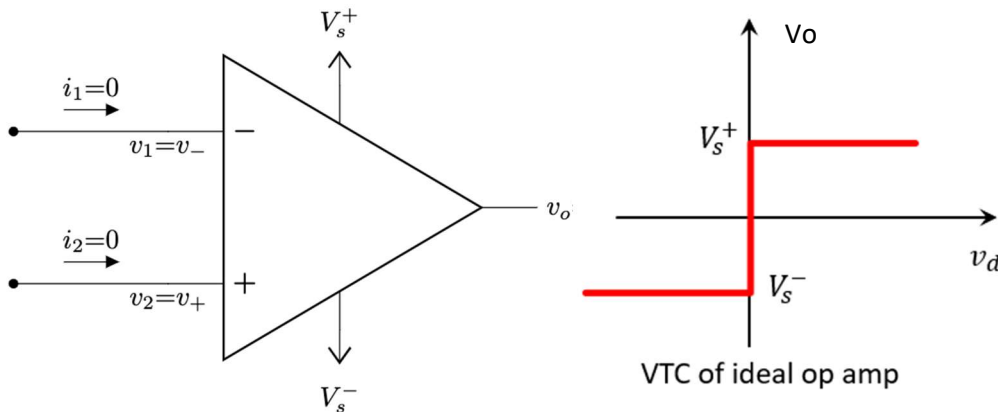
### Ideal Op-Amp VTC:

Y axis → output voltage =  $V_o$ , X axis → Input voltage =  $V_d$

Differential voltage,  $V_d = (V_+) - (V_-) = V_2 - V_1$



$$v_o = \begin{cases} V_s^+ & \text{if } v_d > 0 \Rightarrow v_2 > v_1 \\ V_s^- & \text{if } v_d < 0 \Rightarrow v_2 < v_1 \end{cases}$$


### Non-inverting comparator VTC:

A *non-inverting comparator* is an op-amp based *comparator* for which a reference voltage ( $V_{REF}$ ) is applied to the inverting terminal and the input voltage ( $V_i$ ) is applied to the **non-inverting terminal**


Y axis → output voltage =  $V_o$ , X axis → Input voltage =  $V_i$

$$V_H = V_{s+} = V_{CC}$$

$$V_L = V_{s-} = -V_{CC}$$

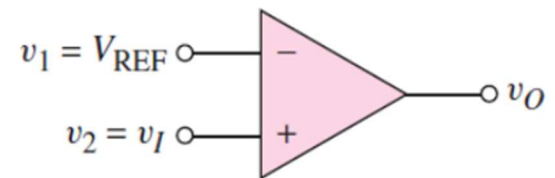
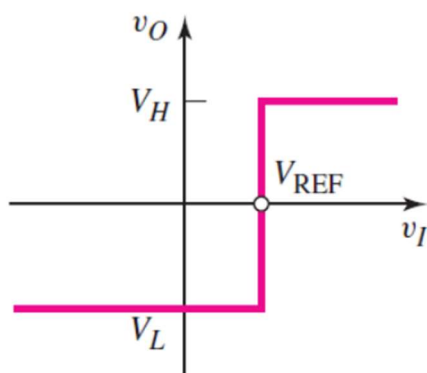
$$v_o = \begin{cases} V_s^+ & \text{if } v_d > 0 \Rightarrow V_i - V_{REF} > 0 \Rightarrow V_i > V_{REF} \\ V_s^- & \text{if } v_d < 0 \Rightarrow V_i - V_{REF} < 0 \Rightarrow V_i < V_{REF} \end{cases}$$



If  $V_i$  is a sine/triangular/square wave or DC signal, the VTC graph would be same. **The graph would change if  $V_{REF}$  changes.**

Now, try to draw the VTC of non-inverting op-amp when-

a)  $V_{REF} = 3V$ , b)  $V_{REF} = -2V$



## Inverting comparator VTC:

An *inverting comparator* is an op-amp based *comparator* for which a reference voltage ( $V_{REF}$ ) is applied to the non-inverting terminal and the input voltage ( $V_I$ ) is applied to the **inverting terminal**

Y axis  $\rightarrow$  output voltage =  $V_O$ , X axis  $\rightarrow$  Input voltage =  $V_I$

$$V_H = V_{S+} = V_{CC}$$

$$V_L = V_{S-} = -V_{CC}$$

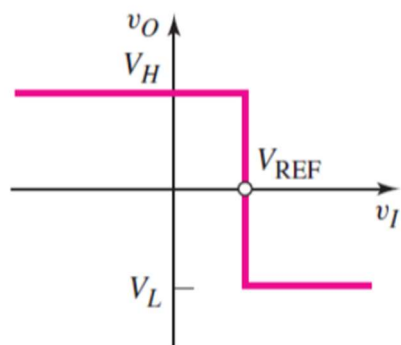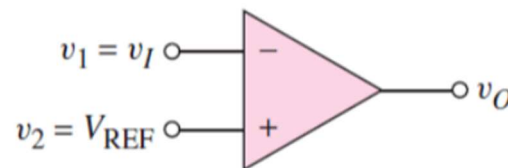

$$v_o = \begin{cases} V_s^+ & \text{if } v_d > 0 \Rightarrow V_{REF} - V_I > 0 \Rightarrow V_I < V_{REF} \\ V_s^- & \text{if } v_d < 0 \Rightarrow V_{REF} - V_I < 0 \Rightarrow V_I > V_{REF} \end{cases}$$

(Opposite graph of non-inverting comparator VTC)

If  $V_I$  is a sine/triangular/square wave or DC signal, the VTC graph would be same. **The graph would change if  $V_{REF}$  changes.**

Now, try to draw the VTC of inverting op-amp when



a)  $V_{REF} = 4V$ , b)  $V_{REF} = -3V$

## Waveform Graph:

Y axis  $\rightarrow$  Voltage/Current, X axis  $\rightarrow$  **time**

**Q1:**  $V_{CC} = 15V = V_{EE}$ ,  $V_{ref} = 1V$ ,  $V_i$  is a 6V p-p triangular signal as shown below

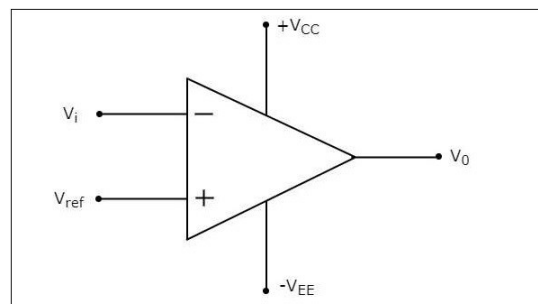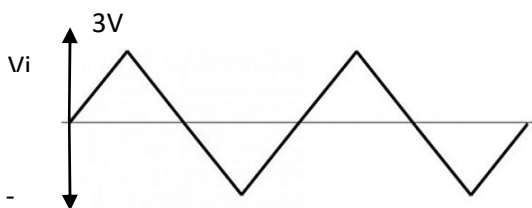**Draw output  $V_o$  for the following op-amp circuit.**




**Sol:**

$V_i$  (input voltage) in the -ve terminal &  $V_{ref}$  (reference voltage) in the +ve terminal  $\rightarrow$  inverting comparator. So,

$$V_o = \begin{cases} +V_{CC} & \text{if } v_d > 0 \Rightarrow V_{ref} - V_i > 0 \Rightarrow V_i < V_{ref} \\ -V_{EE} & \text{if } v_d < 0 \Rightarrow V_{ref} - V_i < 0 \Rightarrow V_i > V_{ref} \end{cases}$$

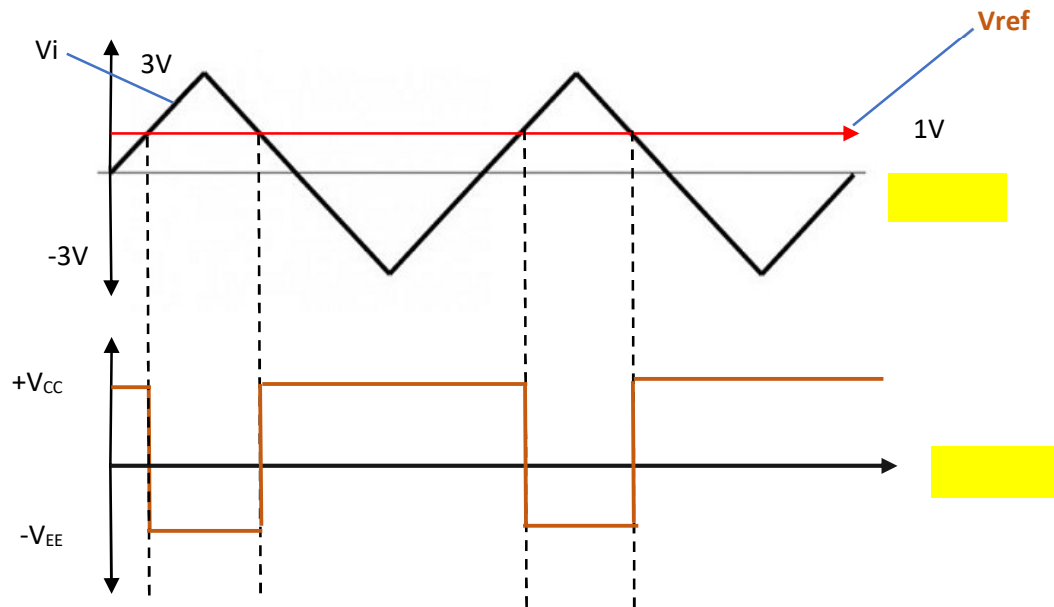[Here, drawing output  $V_o$  means drawing waveform graph of  $V_o$  vs time not VTC graph.]



**Q1:**  $V_{s+} = 15V = V_{s-}$ ,  $V_{REF} = 1V$ ,  $V_i$  is a 6V p-p sinusoidal signal.  
**Draw output  $V_o$  for the following op-amp circuit**

**Sol:**

$V_i$  (input voltage) in the +ve terminal &  $V_{REF}$  (reference voltage) in the -ve terminal  $\rightarrow$  non-inverting comparator. So,

$$v_o = \begin{cases} V_s^+ & \text{if } v_d > 0 \Rightarrow V_i - V_{REF} > 0 \Rightarrow V_i > V_{REF} \\ V_s^- & \text{if } v_d < 0 \Rightarrow V_i - V_{REF} < 0 \Rightarrow V_i < V_{REF} \end{cases}$$

