

Alternative Representation, KCL-KVL, Nodal Analysis

Lecture 2

Course No: CSE 251



Course Title: Electronic Devices and Circuits

Alternative Circuit Representation: Line diagrams


Goal: representing circuits using Shorthand notations

Steps

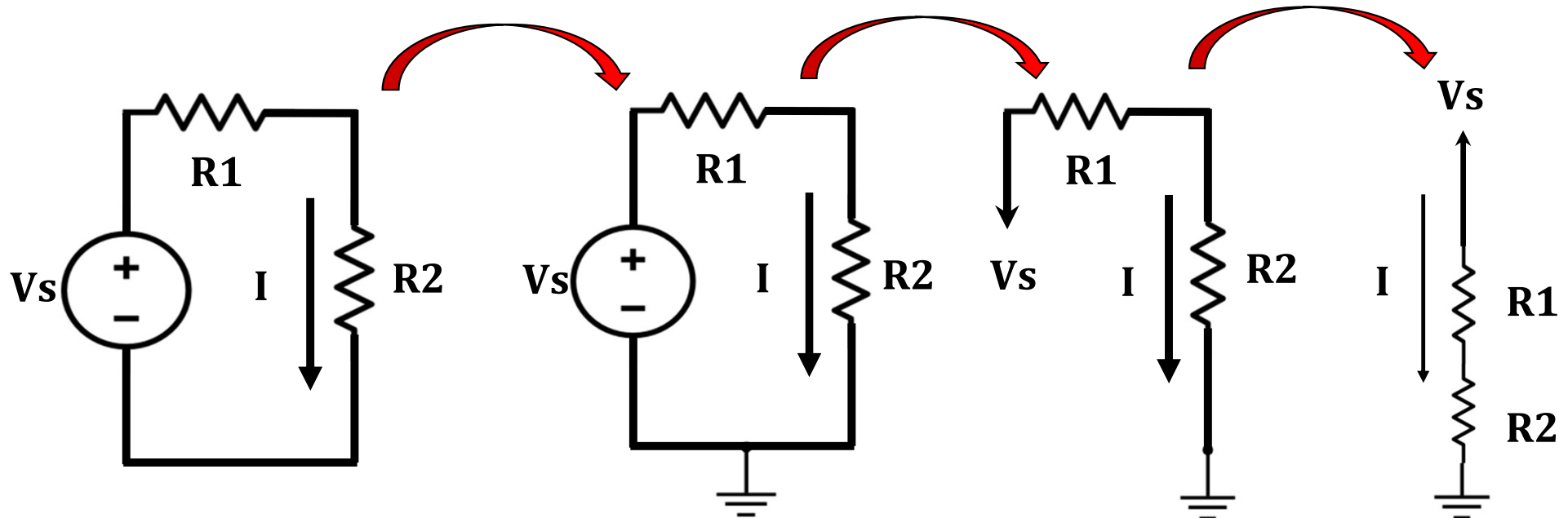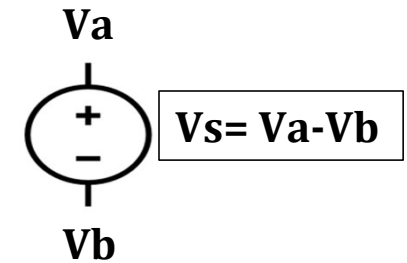- Identify the 'Nodes'
- Select one node as 'Ground'
- Replace the other known voltage nodes with an arrow



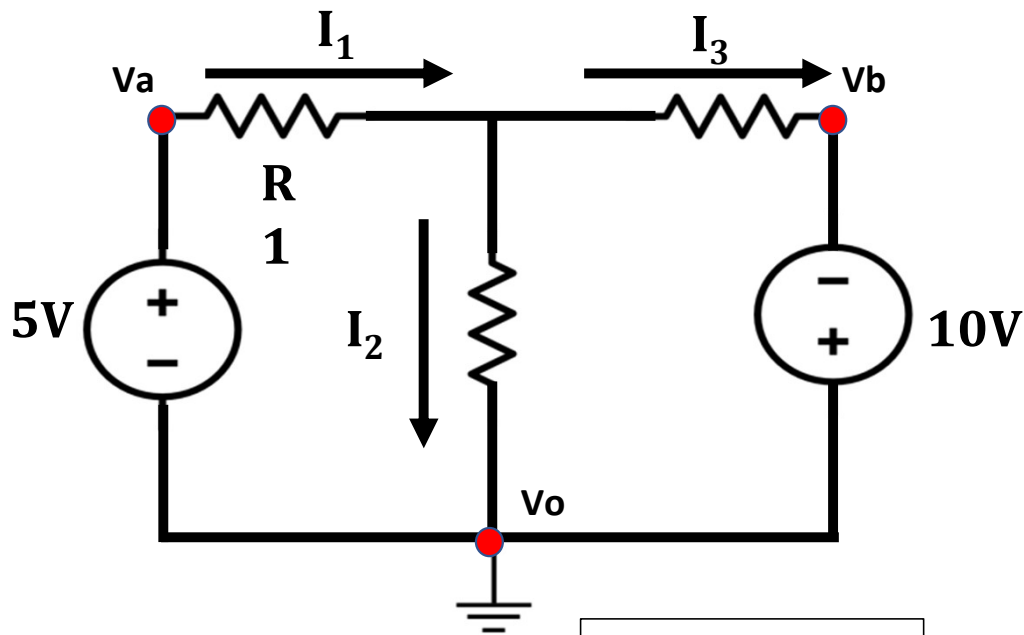- Circuits with voltage sources of opposite polarities



$V_o = 0V$ [Ground]

For 5V :


$V_a - V_o = (5 - 0) V$

$\Rightarrow V_a = 5V$


For 10V :

$V_o - V_b = (0 - 10) V$

$\Rightarrow V_b = -10V$


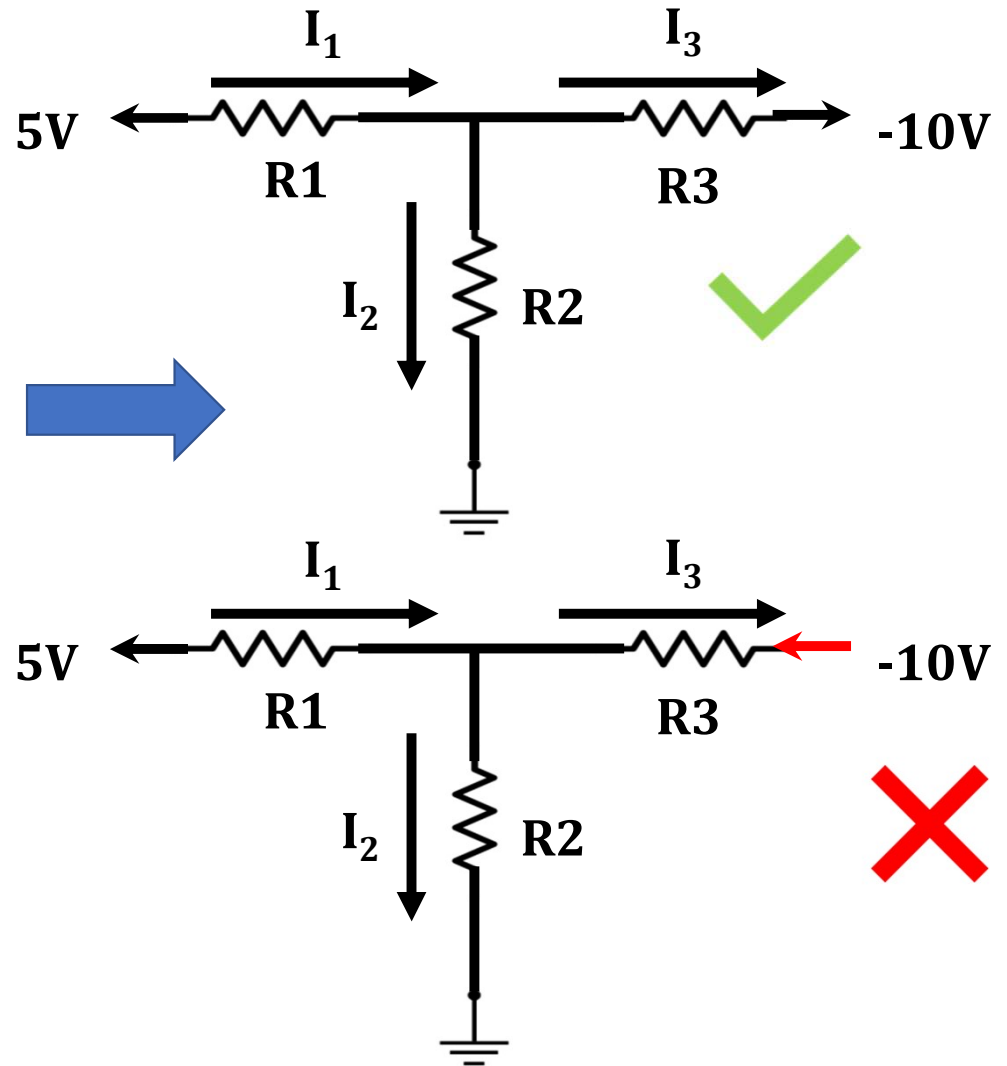


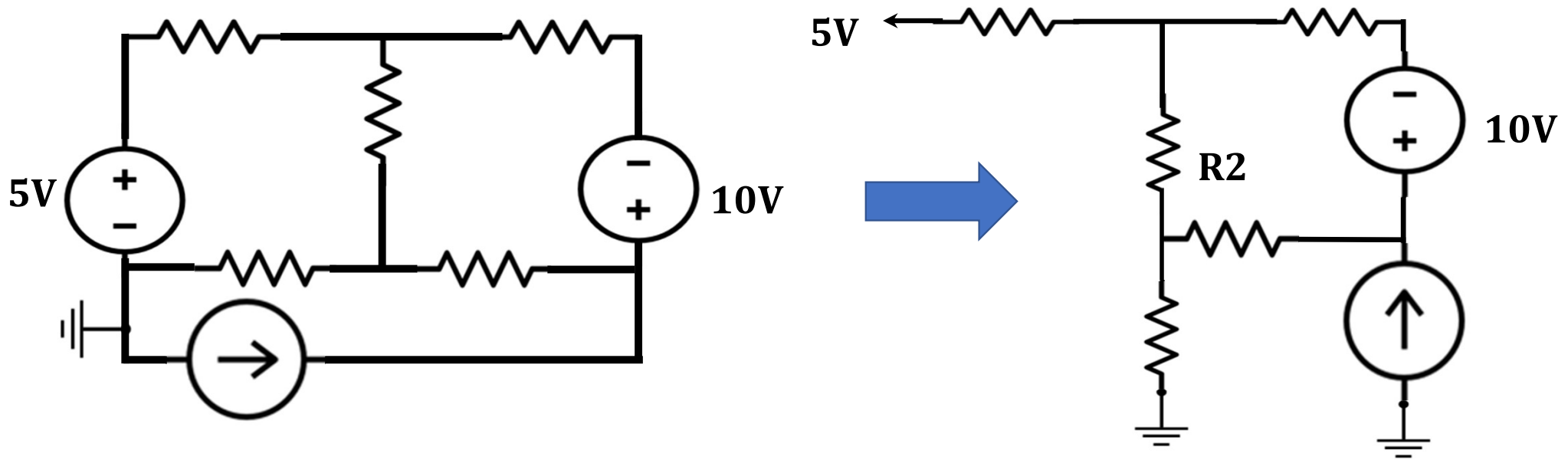- Circuit with a current source/ floating voltage source: Keep them as they are!



- Floating voltage sources:** None of the terminals of the voltage source is connected to the reference i.e. ground node

Practice Problem

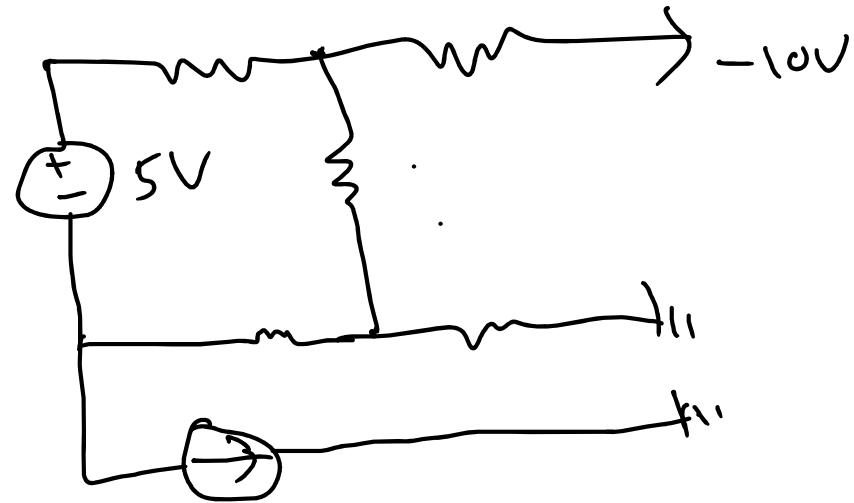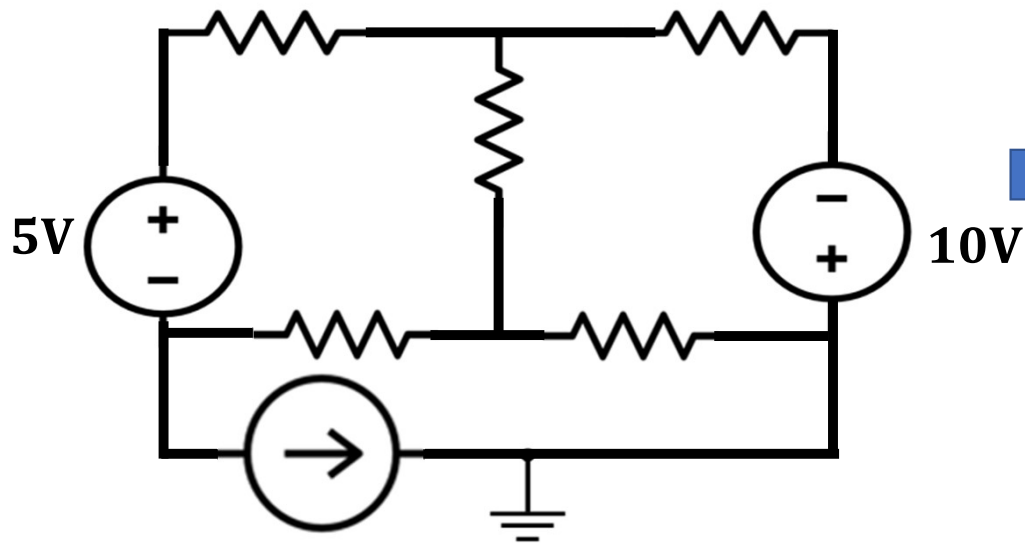


The fundamentals ...

Ohm's Law –

- the voltage v across a resistor is **directly proportional** to the current i flowing through the resistor (R)

$$v \propto i$$
$$v = iR$$

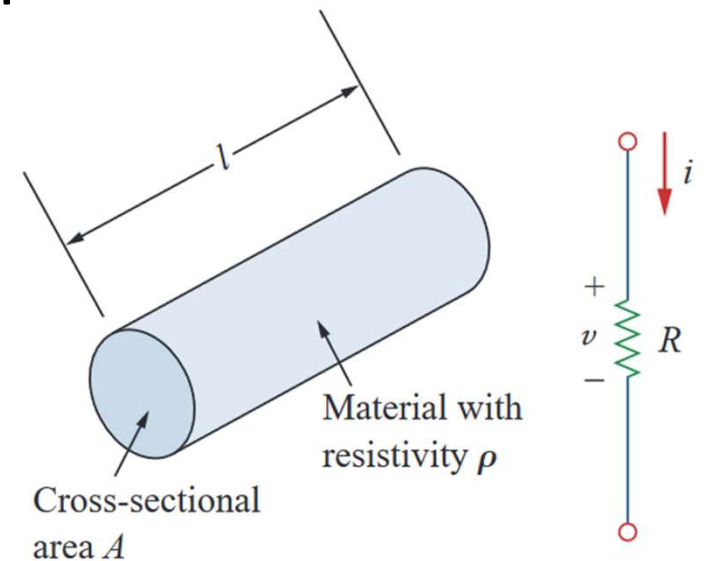


Series Resistors and Voltage Division

The **equivalent resistance** of any number of resistors connected in **series** is the sum of the individual resistances.

Principle of voltage division

Source voltage v - is divided among the resistors in direct proportion to their resistances; the larger the resistance, the larger the voltage drop.
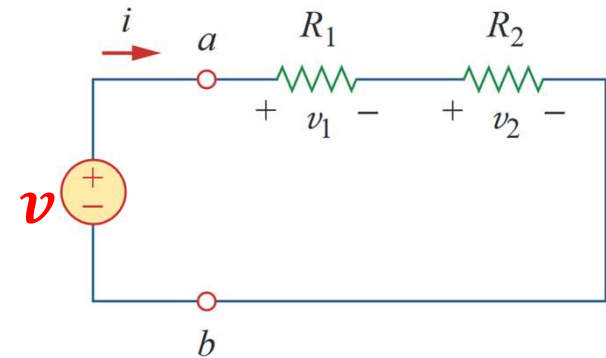
$$v_1 = \frac{R_1}{R_1 + R_2} v \quad v_2 = \frac{R_2}{R_1 + R_2} v$$





KCL: Kirchhoff's Current Law

The algebraic sum of the **currents** entering a **node (closed boundary)** is equal to the sum of the currents leaving the node.

$$i_1 + (-i_2) + i_3 + i_4 + (-i_5) = 0$$


Current Entering node: **Positive**
Current Exiting node: **Negative**

Or vice versa...

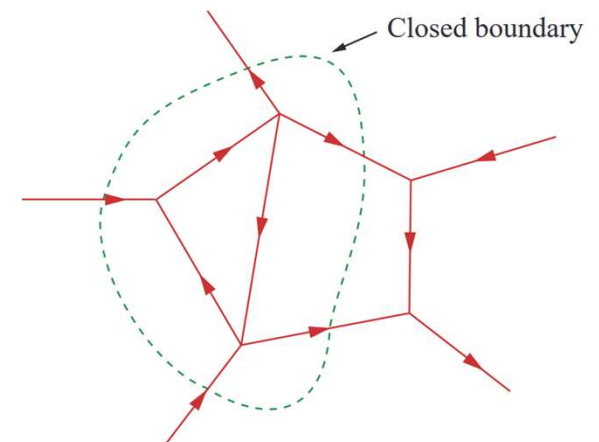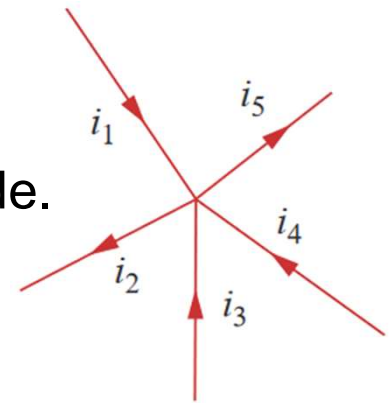

Kirchhoff's Current Law (KCL):

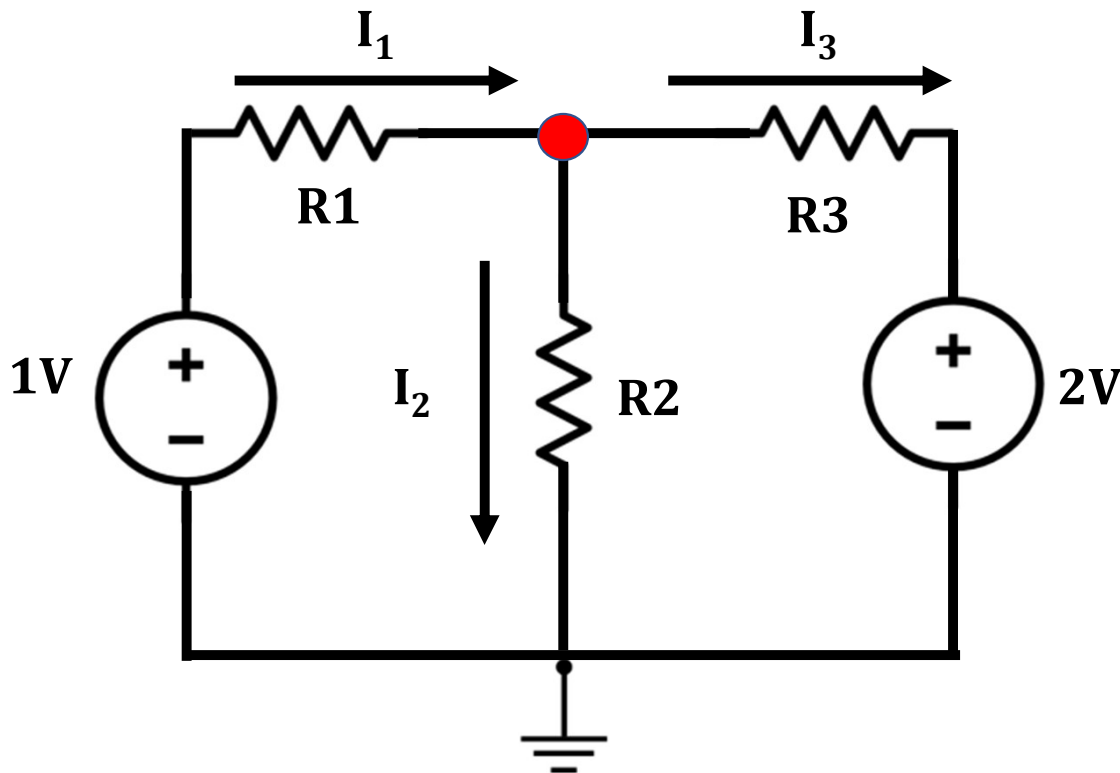
- “The algebraic sum of all currents entering and exiting a node must equal zero.”
- “Currents flowing into a node (or a junction) must be equal to the currents flowing out of it.”



$$I_1 = I_2 + I_3$$


Kirchhoff's Current Law (KCL):

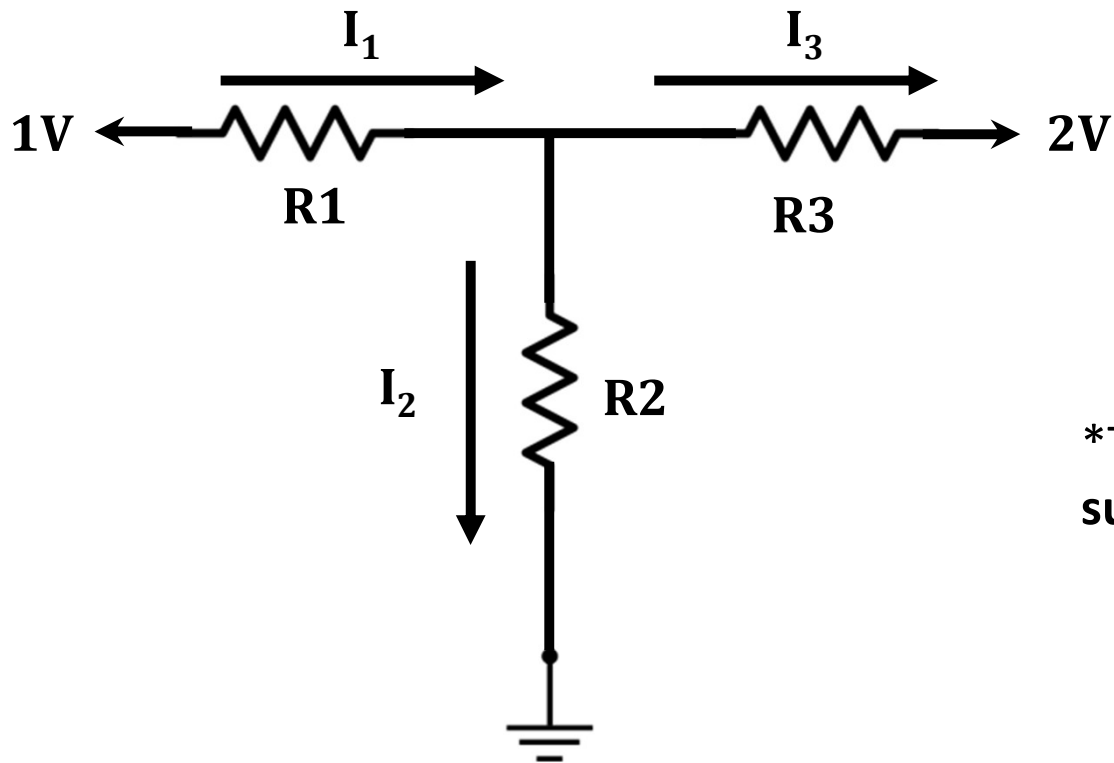- “The algebraic sum of all currents entering and exiting a node must equal zero.”
- “Currents flowing into a node (or a junction) must be equal to the currents flowing out of it.”



$$I_1 = I_2 + I_3$$

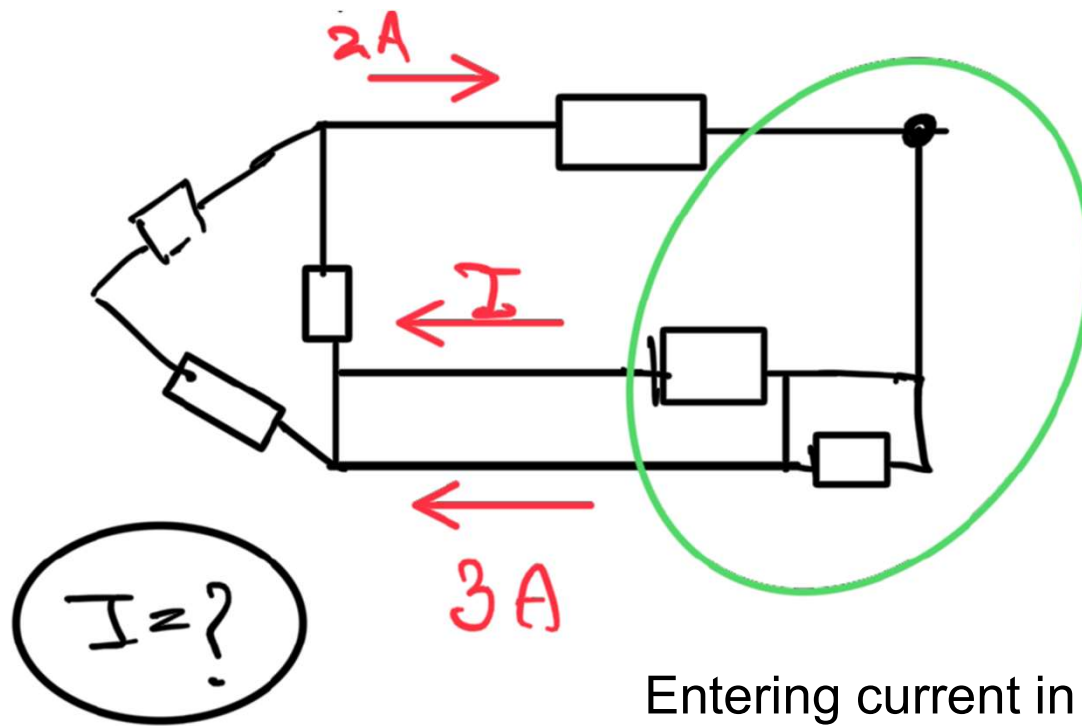
*This is also applicable to **supernodes!**



Entering current in the green closed region= 2A
 Leaving current from the closed region= I & 3A

$$\text{KCL} \rightarrow I + 3A = 2A$$

$$\therefore I = -1A$$

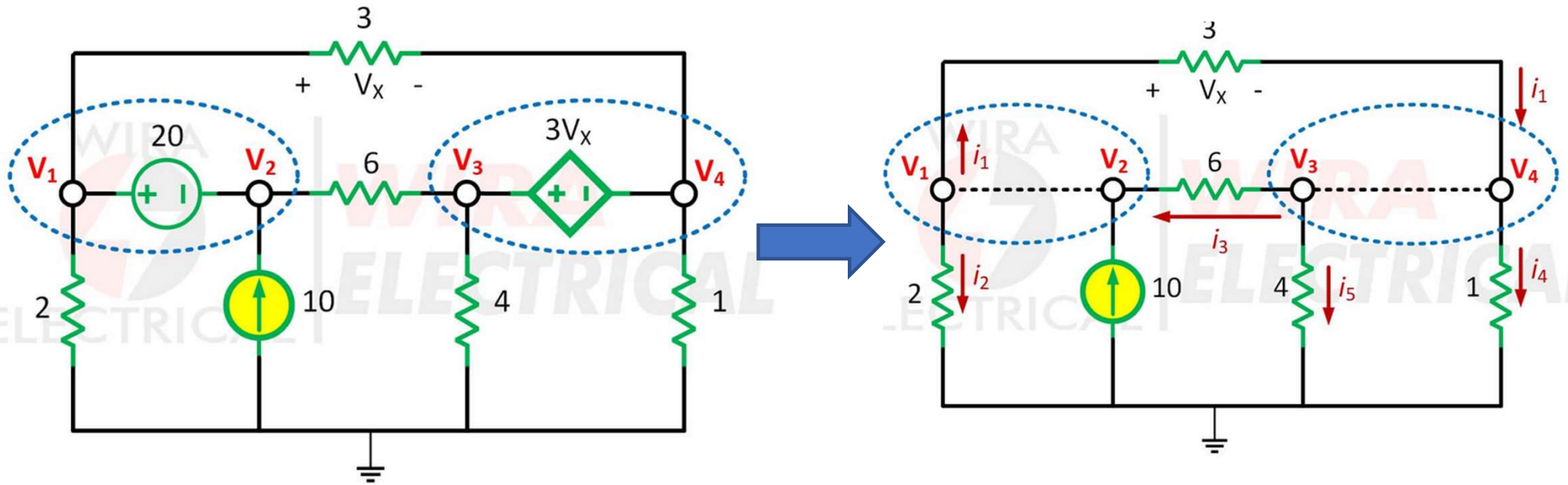

KCL for Super node 1:


$$i_1 + i_2 = i_3 + 10A$$


KCL for Super node 2:


$$i_1 = i_3 + i_4 + i_5$$

Kirchhoff's Voltage Law (KVL)

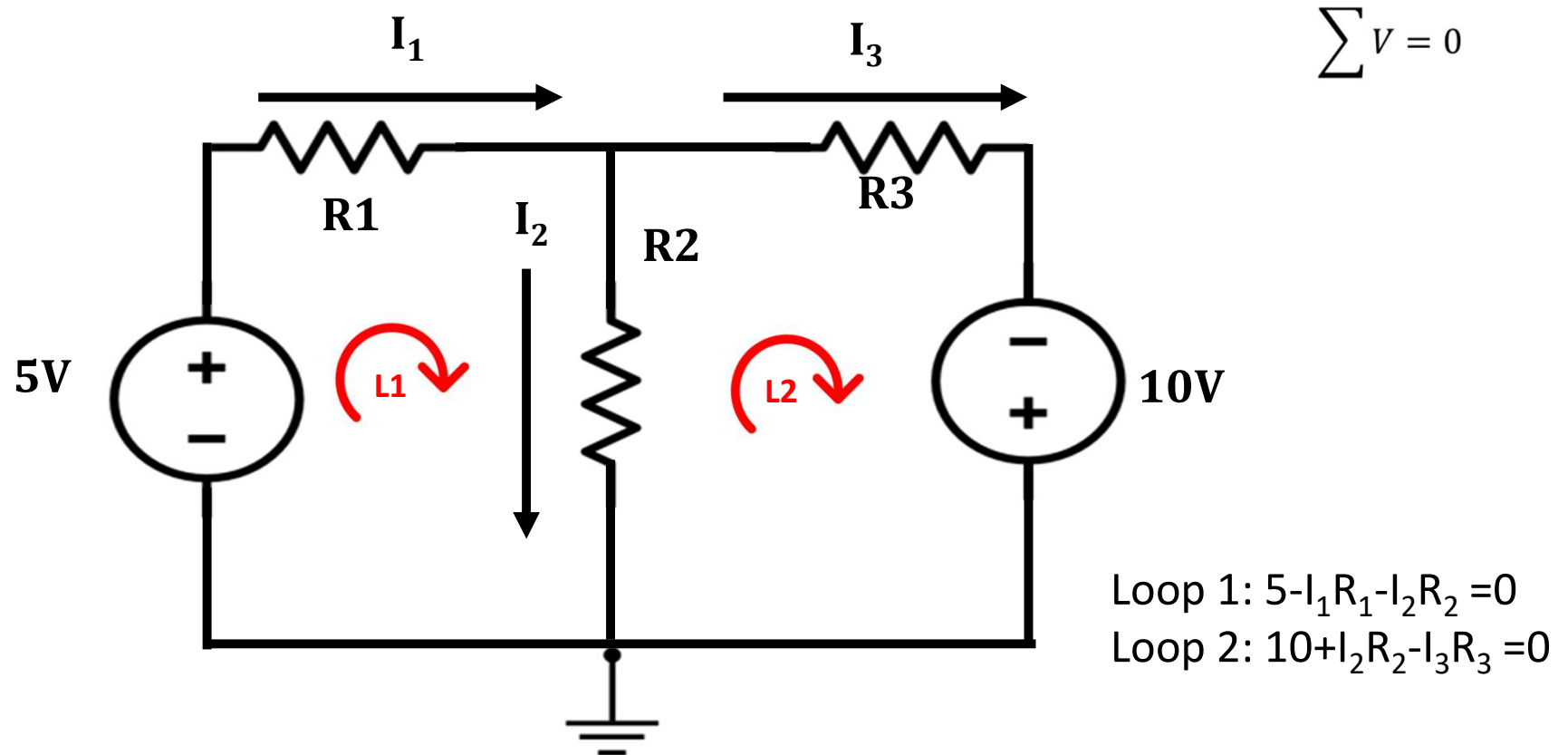The algebraic sum of all voltages in a loop must equal zero



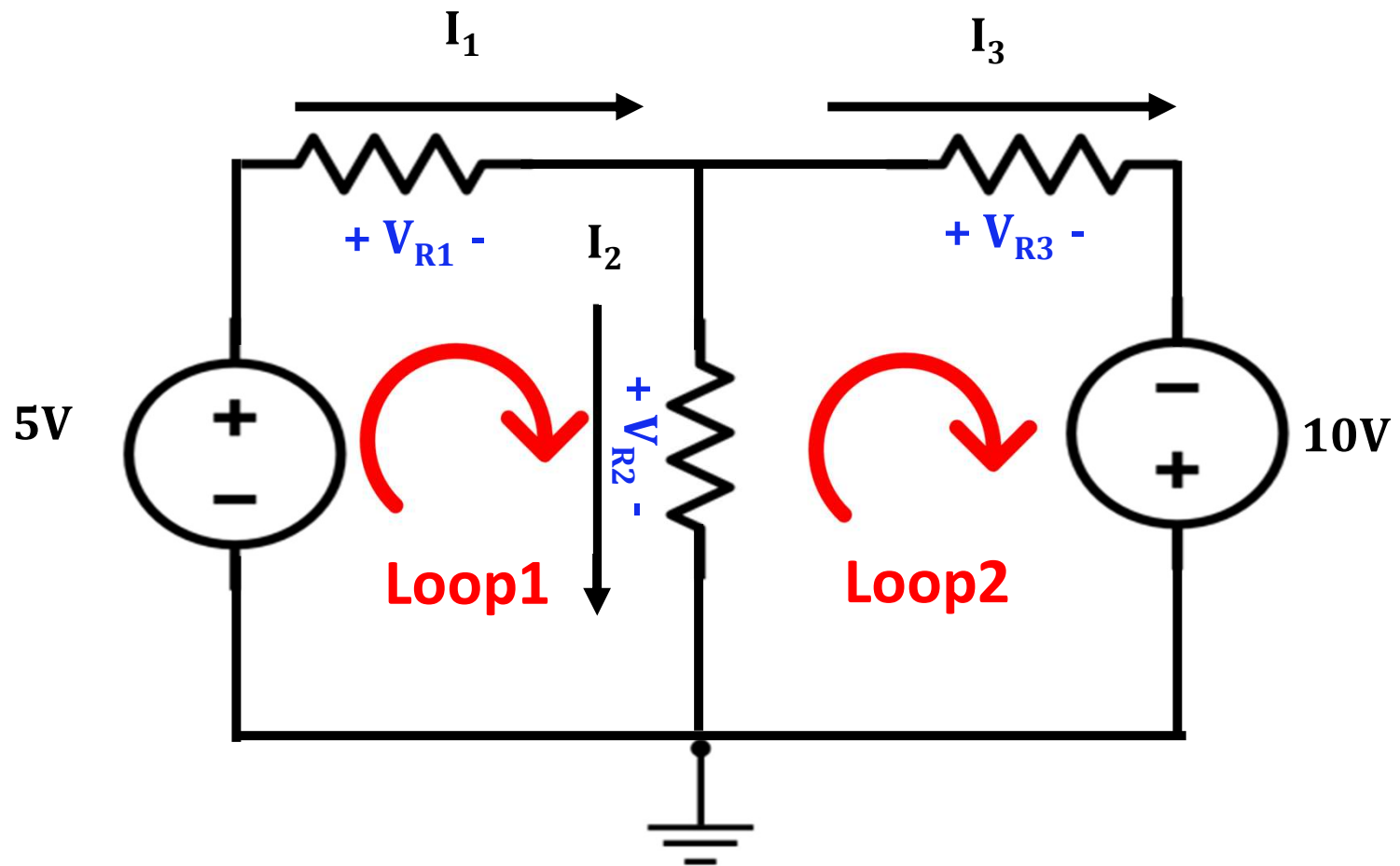

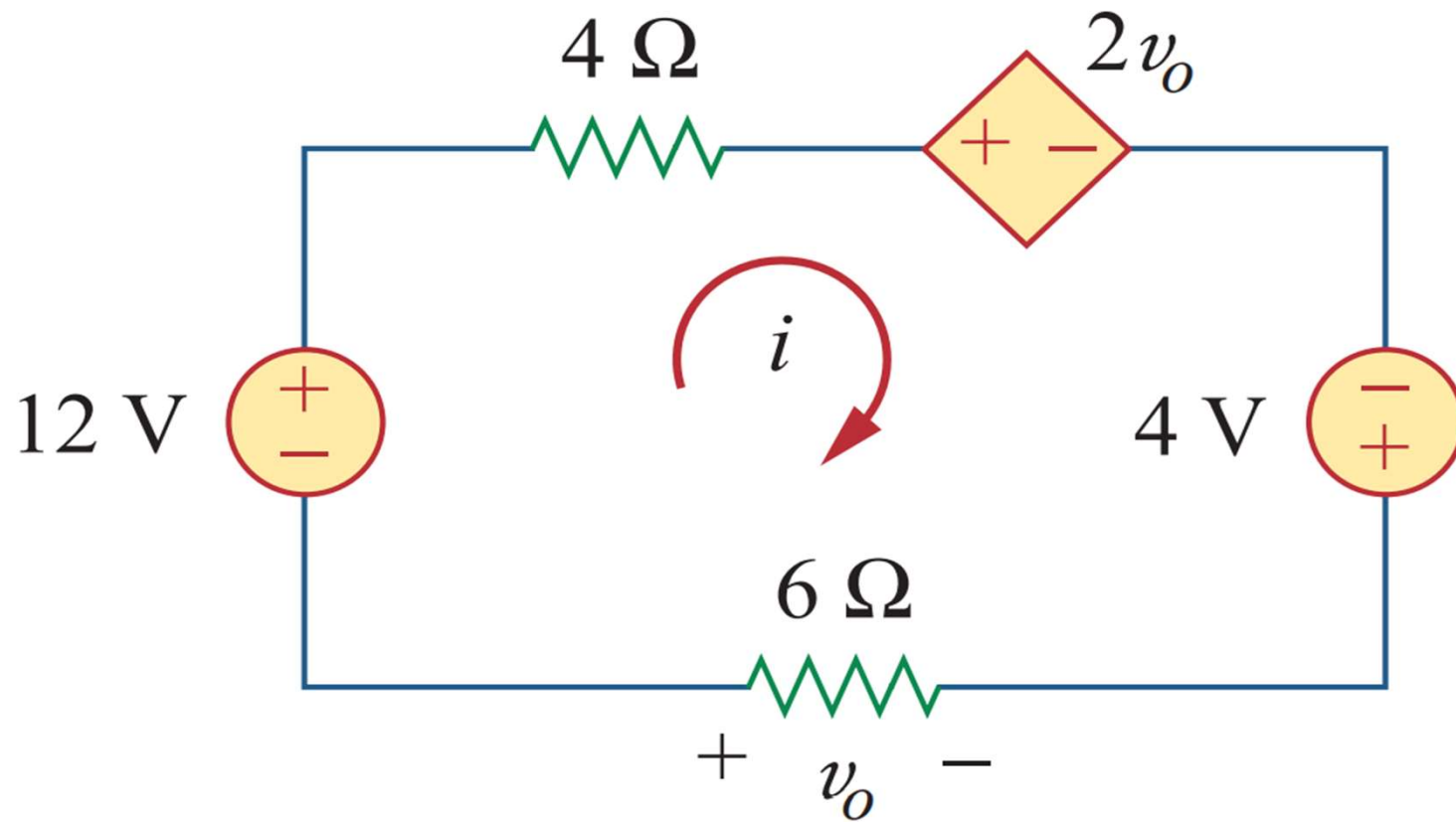



Hint:

KVL: $-12\text{V} + 4i + 2v_o - 4\text{V} - v_o = 0$ --- (1)

$v_o = -6i$ --- (2)
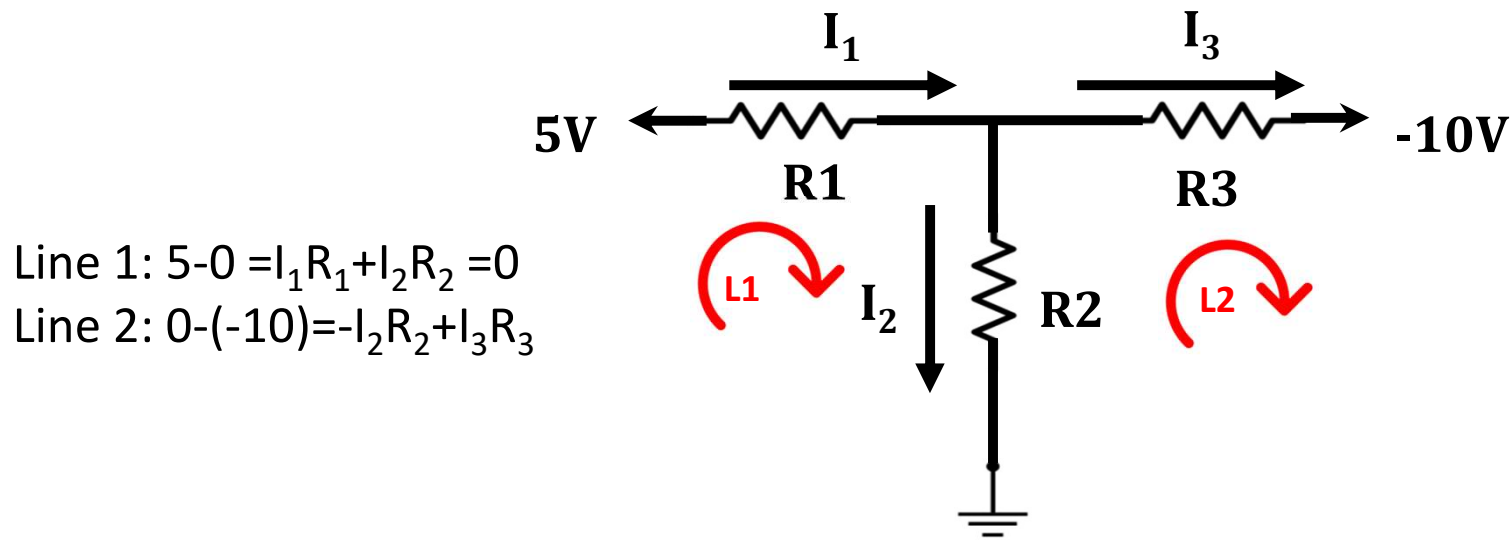
$$\sum V [\text{along line}] = \text{Voltage at the starting of the node} - \text{Voltage at the ending of the node}$$




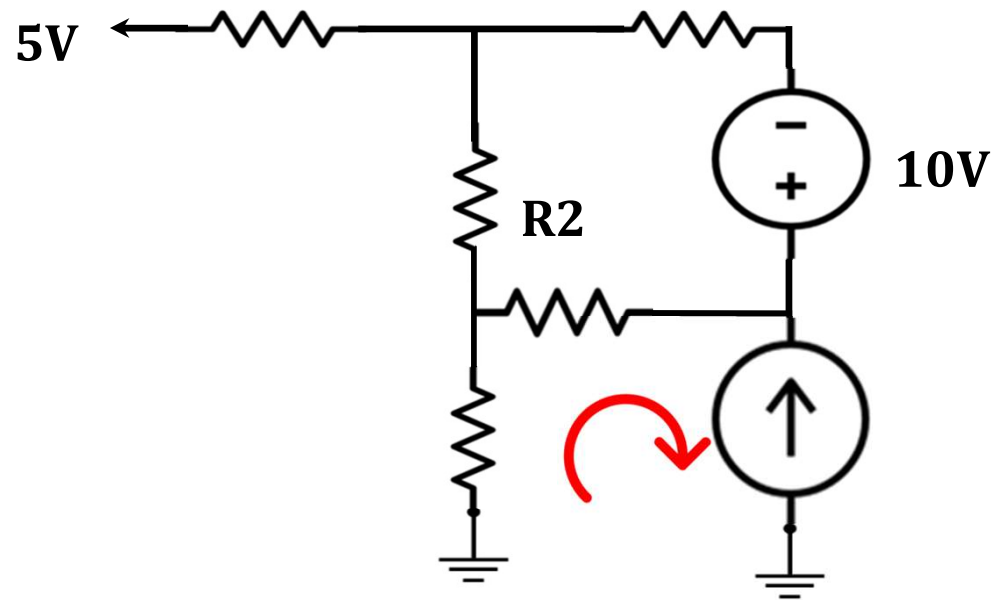


Can you write a KVL equation along this line?

Nodal analysis:

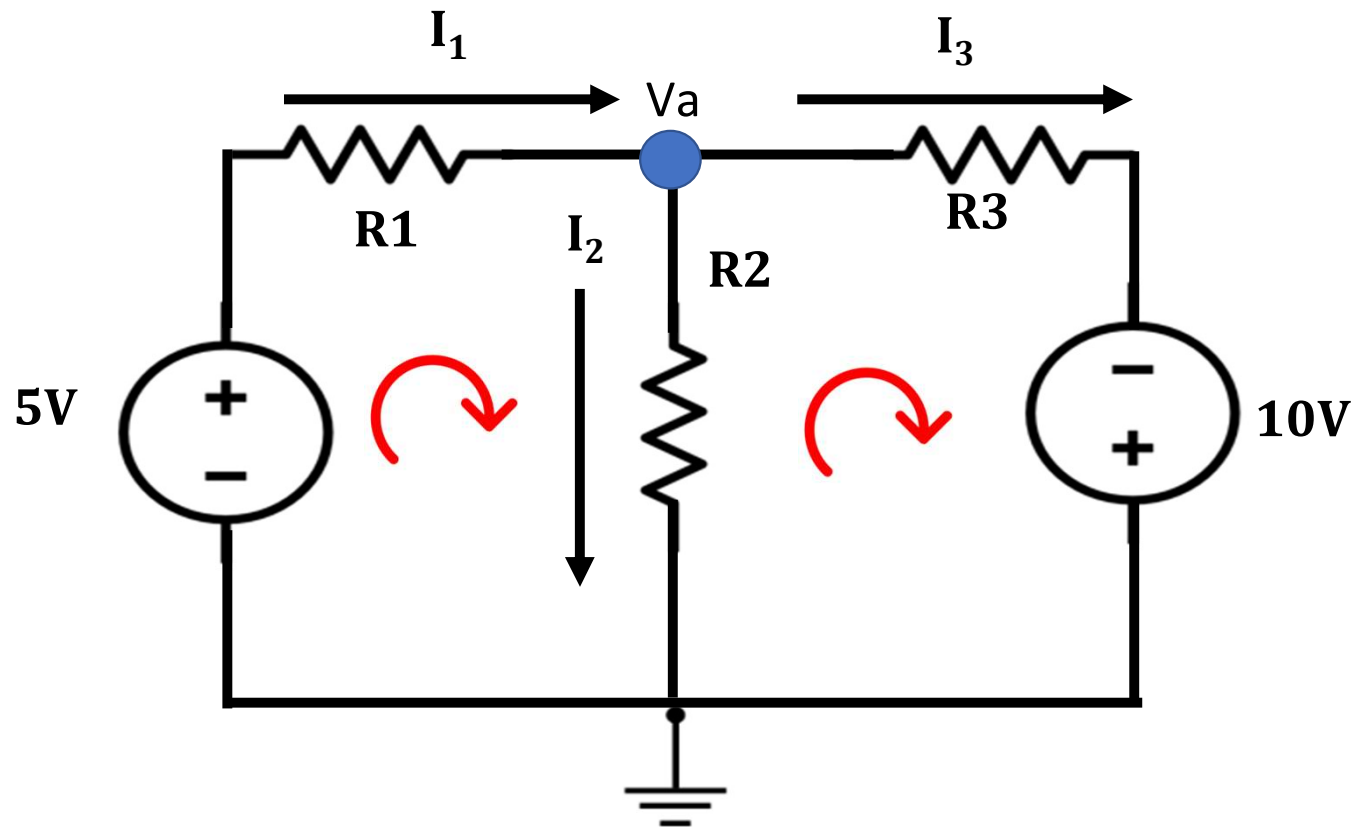
$$V_a \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) - \frac{5}{R_1} - \frac{0}{R_2} - \frac{-10}{R_3} = 0 ; \text{Derived from applying KCL at node } V_a$$






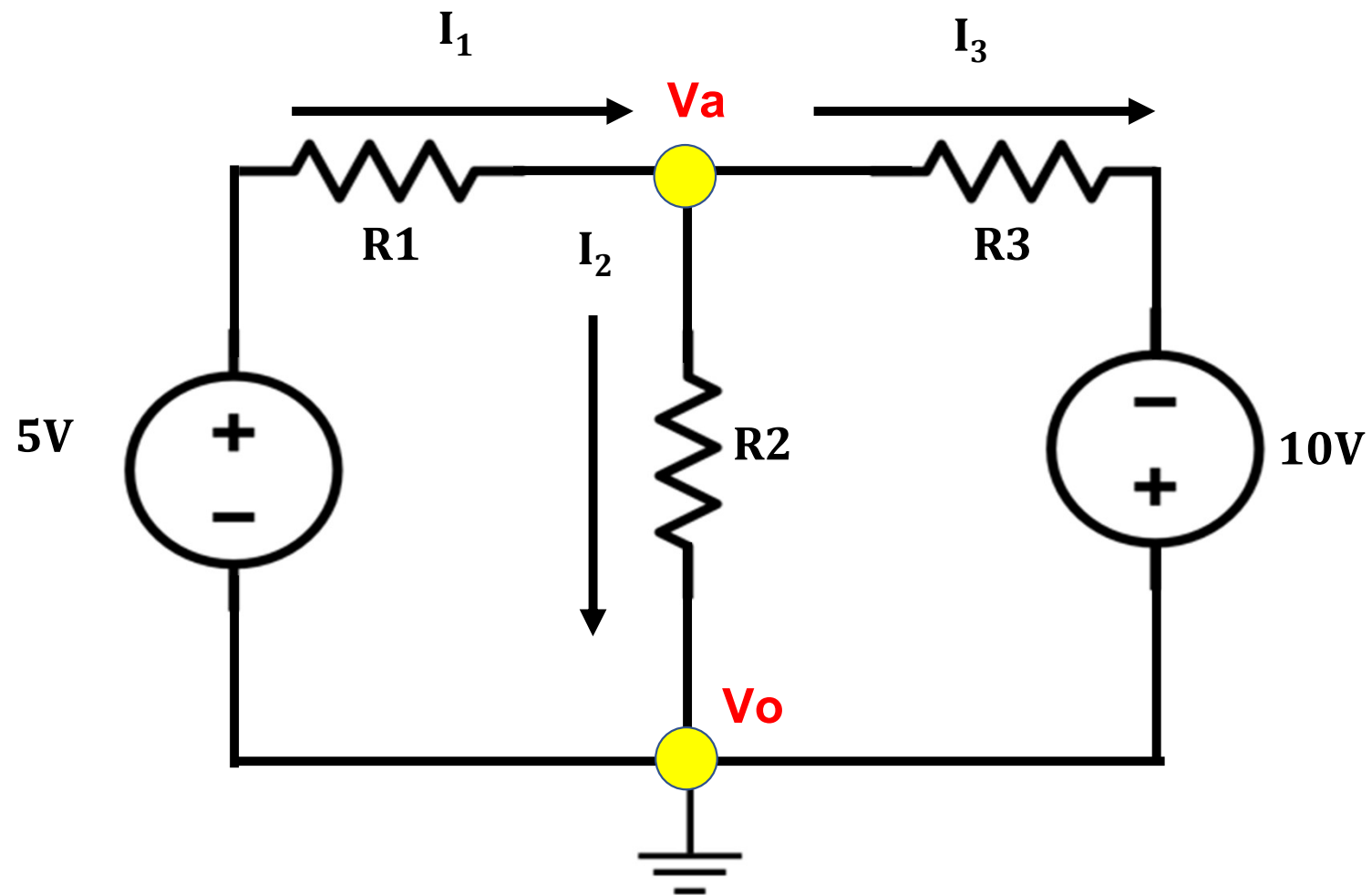



Nodal analysis:
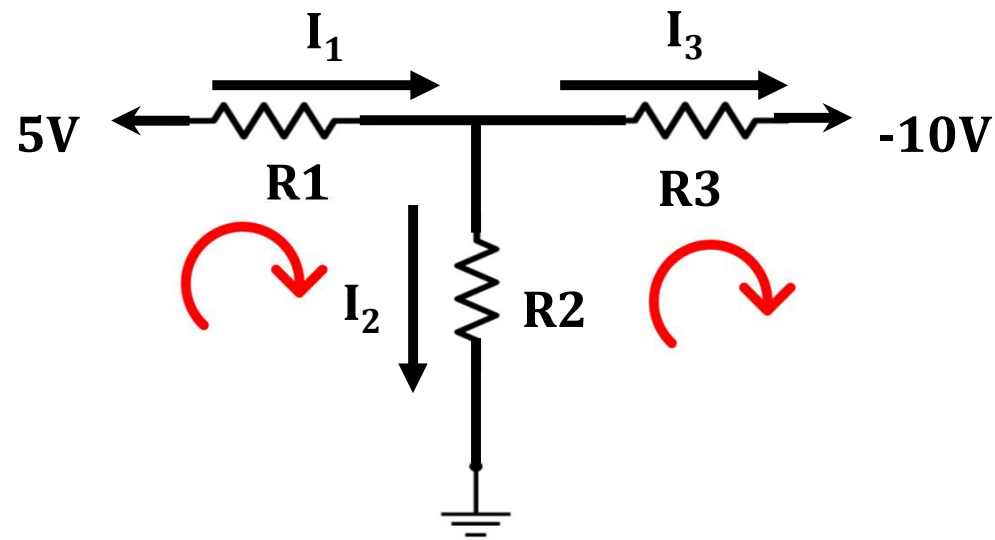
$$V_a \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) - \frac{5}{R_1} - \frac{0}{R_2} - \frac{-10}{R_3} = 0$$



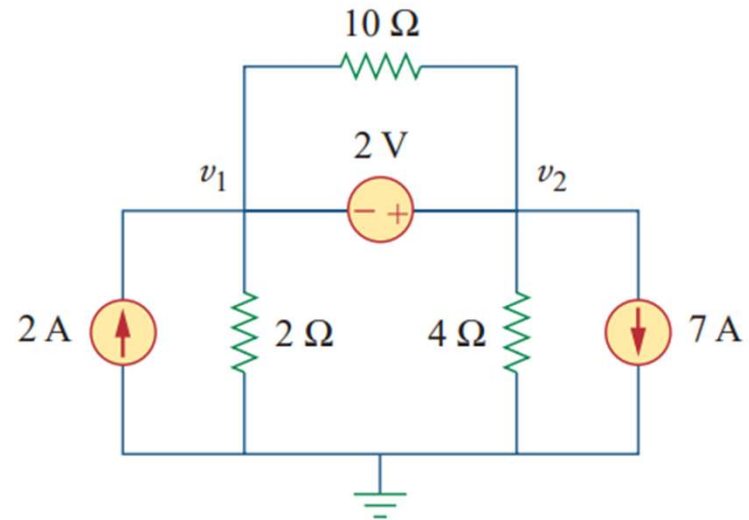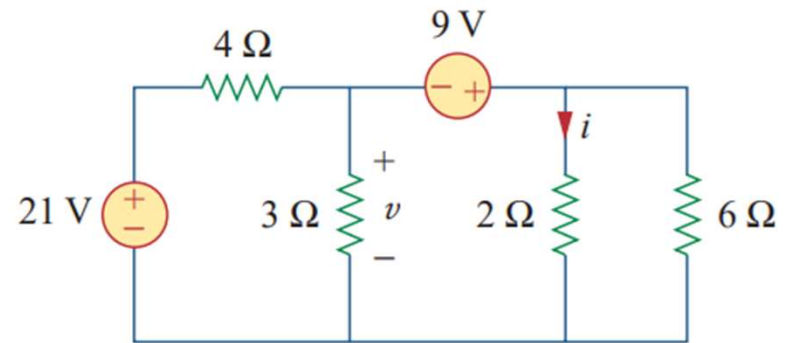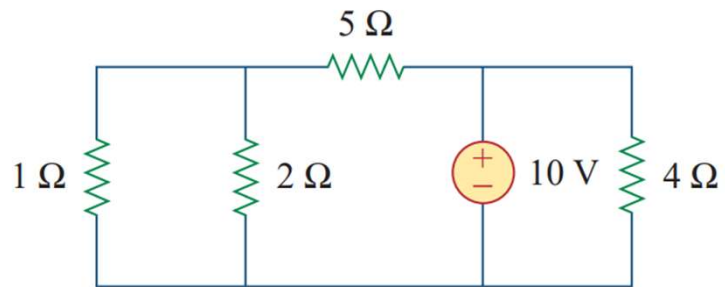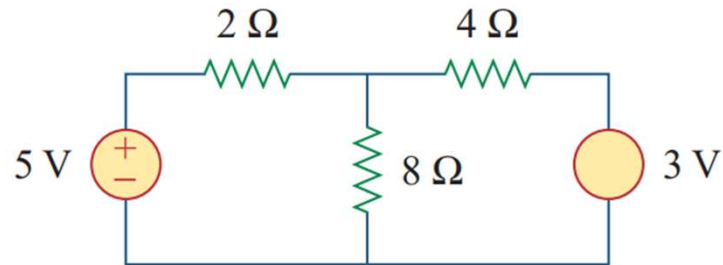Practice Problems: i) Draw Alternative Circuit Diagrams , ii) Write down KCL equations, iii) Write down KVL equations and iv) Nodal equation



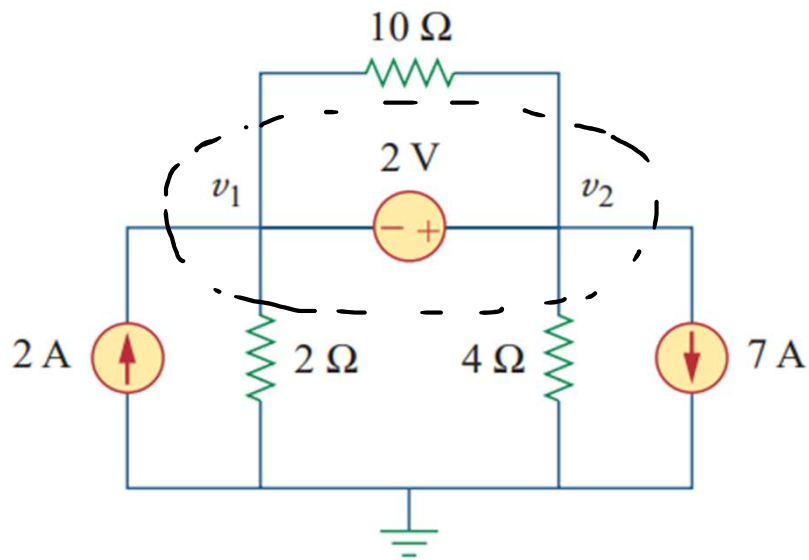

Nodal Analysis:

$$\frac{V_1 - 0}{2} + (-2 \text{ A}) + \frac{V_2 - 0}{4} + 7 \text{ A} = 0 \text{ -----(1)}$$

$$V_1 - V_2 = -2 \text{ -----(2)}$$

Thank You