

Example 1




Step 1

Device model:

Region A: $V \leq 5V$,

Open circuit,  Anode Cathode

Region B: $V > 5V$

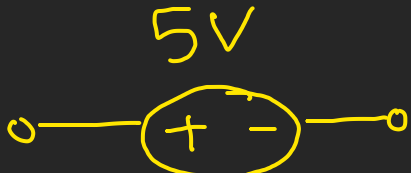Voltage source:  5V Anode Cathode

Step 2


Device parameters:

Region A: no parameters

Region B: $V_0 = 5V$

— x —

Example 2

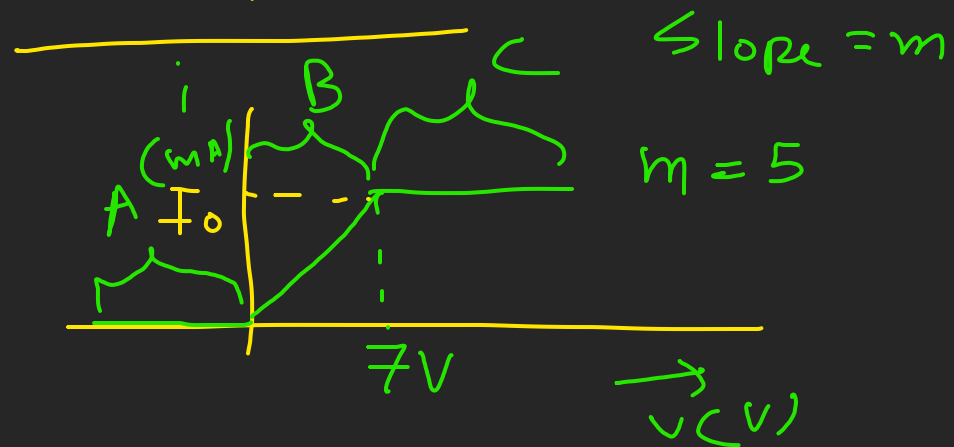

Step 2:

Device Parameters:

A: W/A

B: $R = 1/m = 0.2 \text{ K}\Omega$

C: $\gamma = m \times 7V$ (from B)
 $\Rightarrow I_0 = m \times (7V) = 35 \text{ mA}$

Step 1

A: Anode } Not the regions!
 C: Cathode }

Device Model:

Region A: $V \leq 0V$; open circuit




Region B: $0 < V \leq 7V$; Resistor



Region C: $V > 7V$; Current source




Example 3

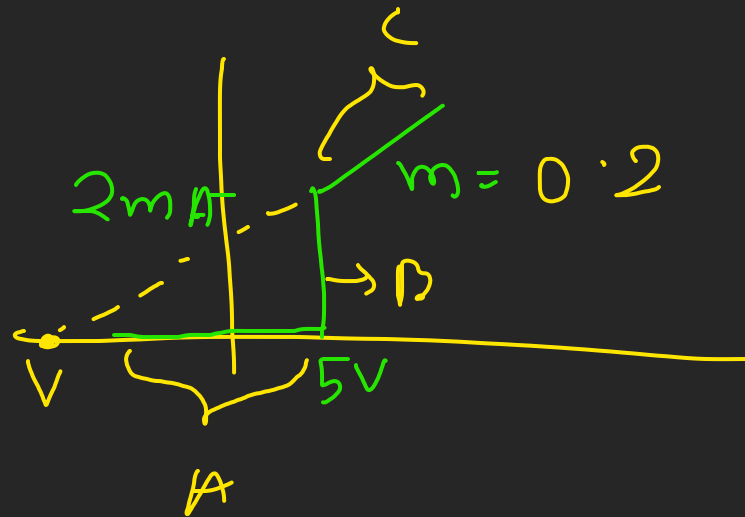

1) Device Model:



$A: V \leq 5V$;

$B: 0 < i \leq 2mA$; Voltage source

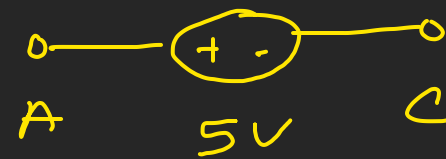

$C: V > 5V$; Two possible

model:

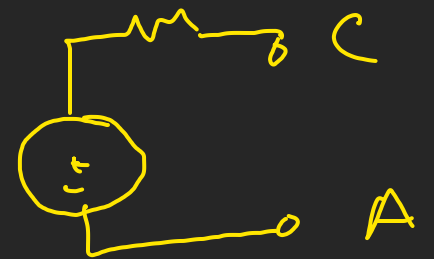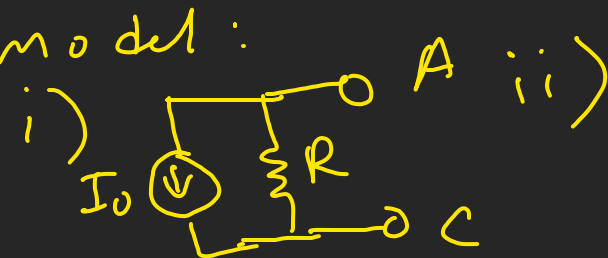

2) Device Parameters:

A: No parameters can be found!

B: $V_0 = 5V$

C: Equation for this region: $y = mx + c$

↗ voltage

↓ ↓ ↘ I_0

current slope

At 5V, the current is 2mA.

$$\therefore 2 = (0.2 \times 5) + c$$

$$\Rightarrow C = (2 - 1) \text{ mA} = 1 \text{ mA}$$

$$I_0 = 1 \text{ mA}, \quad R = 1/m = 5 \text{ k}\Omega$$

at V_0 , $i = 0$

↖ Cathode
↗ Anode

$$y = mx + c$$
$$\Rightarrow 0 = 0.2x + 1$$
$$\Rightarrow x = -5V$$
$$= V_0$$

Method of Assumed State:

