


Diode: Method of Assumed States

Lecture 8

Course No: CSE 251

Course Title: Electronic Devices and Circuits

Real diode

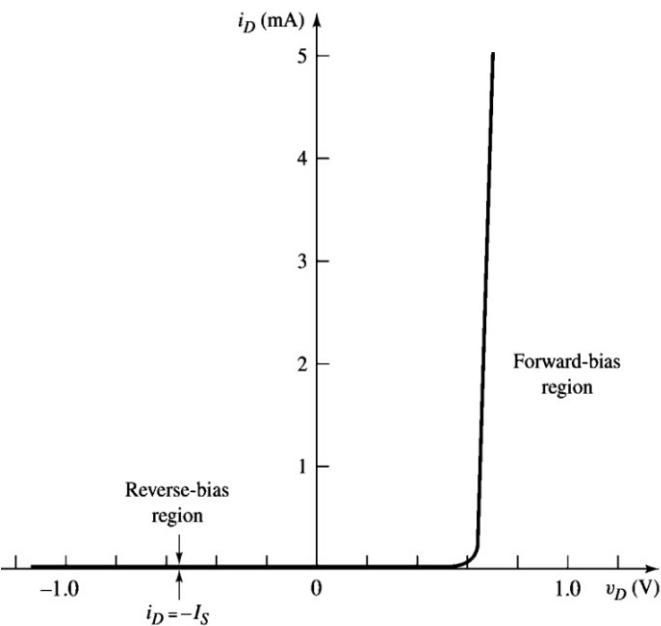

Relation between diode current and diode voltage:


$$i_D = I_S \left(e^{\frac{v_D}{\eta V_T}} - 1 \right)$$

where $v_D (= v_A - v_C)$ is the voltage across the diode, i_D is the current through the diode (from anode to cathode) and V_T , called the thermal voltage, is a temperature dependent constant. For temperature $T = 300K$, $V_T = 25 mV$.

η is called the ideality factor (try to recall, you measured this in the lab!)


I-V characteristics of a real diode

1. Ideal Diode Model

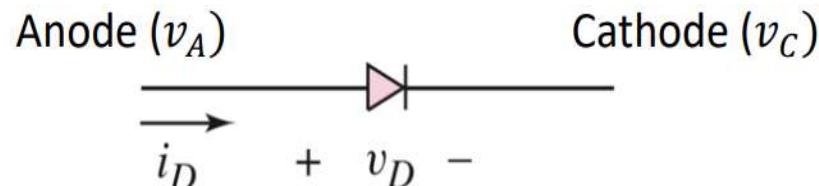


OFF State: Open circuit


ON State: Short circuit

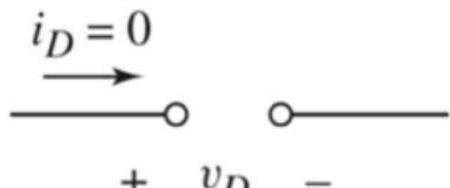

$$(v_D < 0, i_D = 0)$$

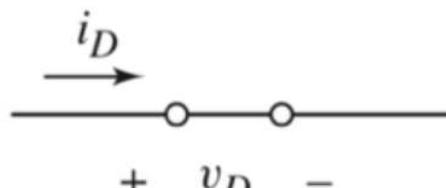


$$(i_D > 0, v_D = 0)$$

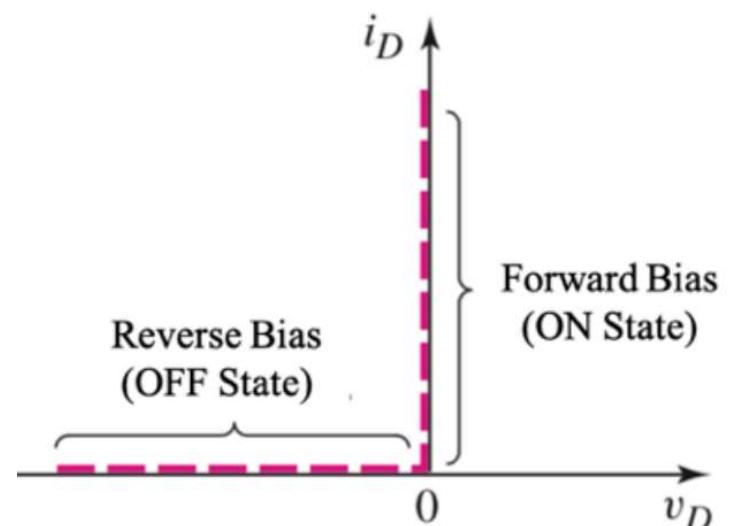

So, Power, $P = v_D \cdot i_D = 0W$

Modeling the real diode

2. Constant voltage drop (CVD) model

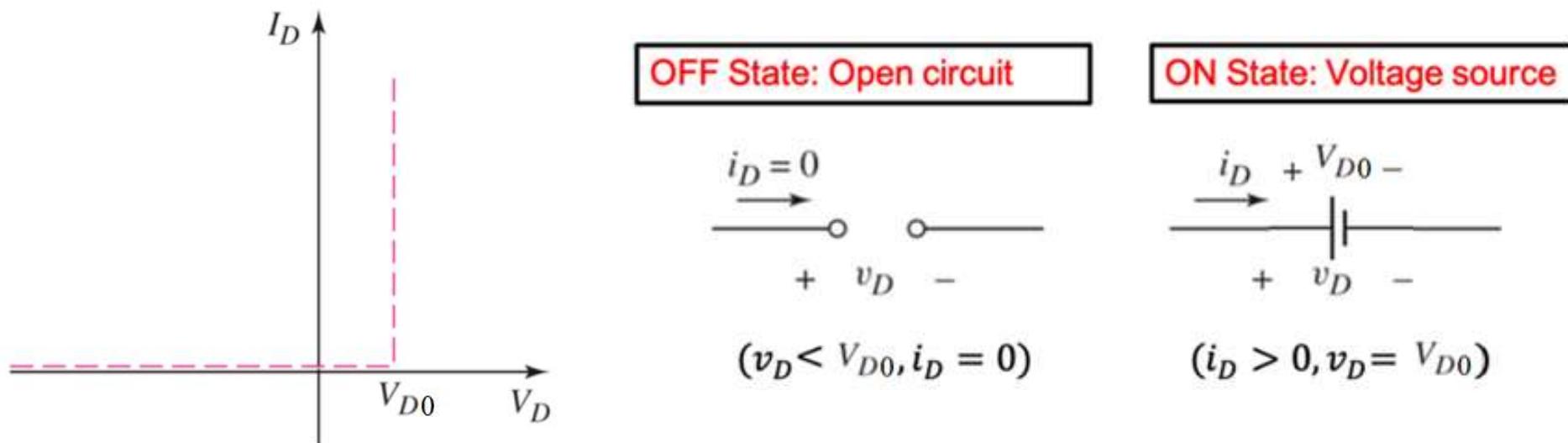


Usually, $v_{D0} = 0.7V$ (Si)
 $v_{D0} = 0.3V$ (Ge)


So, Power, $P = v_{D0} \cdot i_D > 0W$
 $\therefore P \propto i_D$

Modeling the real diode

3. CVD+R model

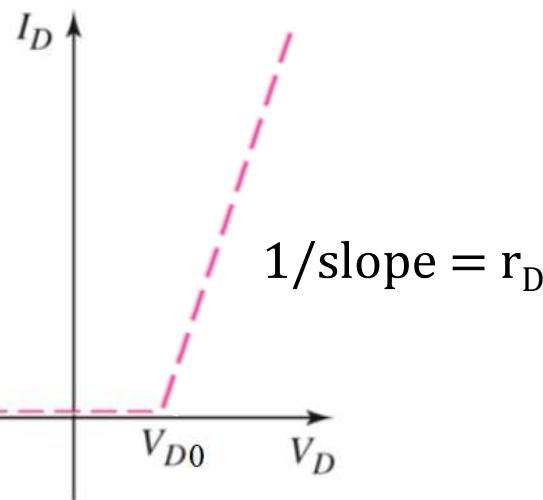


OFF State: Open circuit

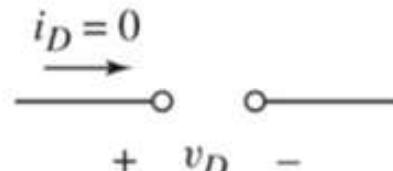

$$(v_D < V_{D0}, i_D = 0)$$

ON State: Voltage source

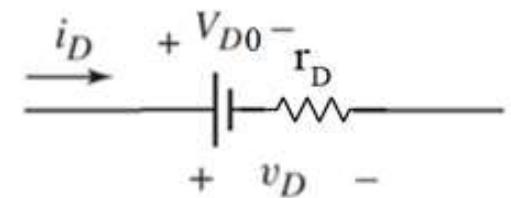

$$(i_D > 0, v_D = V_{D0} + i_D r_D)$$

$$i_D = \frac{v_D}{r_D} - \frac{V_{D0}}{r_D}$$

$$r_D \sim 10-20\Omega$$


Comparison of Models

Ideal: Simple, Less Accuracy

CVD+R: Complex, Better Accuracy

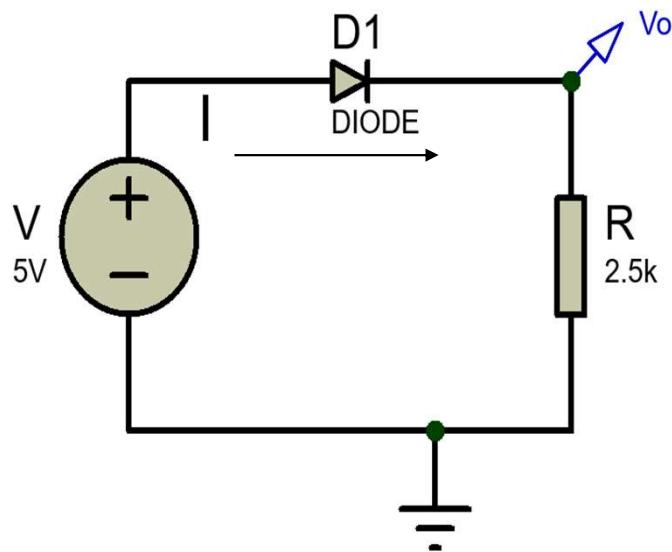Example

Find V_o , I using a) Ideal diode, b) CVD and c) CVD + r model ($r = 10 \Omega$)



a) D1 ON \rightarrow Replace with short ckt

$$V_o = 5V$$

$$I = 5V / 2.5k\Omega = 2mA$$

b) D1 ON \rightarrow Replace with constant voltage source of 0.7V

$$V_o = 5 - 0.7 = 4.3V$$

$$I = 4.3V / 2.5k\Omega = 1.72mA$$

c) D1 ON \rightarrow Replace with constant voltage source of 0.7V & $r = 10\Omega$

$$\text{KVL: } 5 = 0.7 + I(10 + 2500) \rightarrow \therefore I = 1.713 mA$$

$$V_o = 2.5I = 4.283V$$


Steps for Method of Assumed States

Analyzing multi-diode circuits requires determining if the individual diodes are ON or OFF. In many cases, the choice is not obvious, so we must initially guess the state of each diode, then analyze the circuit to determine if we have a solution consistent with our initial assumption.

1. Assume state for diode (on/off)
2. Solve circuit
3. Verify




Ideal Model	ON $i_D > 0$	OFF $v_D < 0$
CVD Model	ON $i_D > 0$	OFF $v_D \leq v_{D0}$

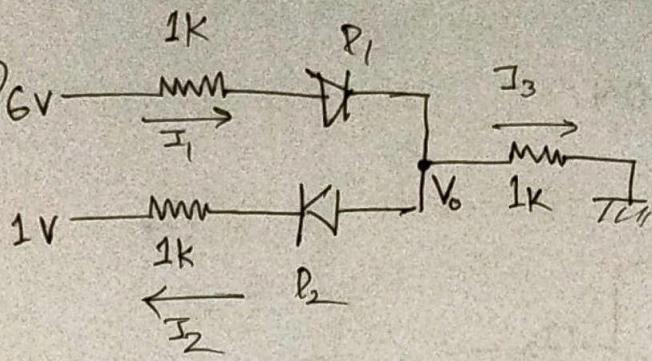

Find I_1 , I_2 , I_3 , V_0 . Use CVD model with $V_f = 0.2V$

Solⁿ: Assume $D_1 = ON$, $D_2 = OFF$

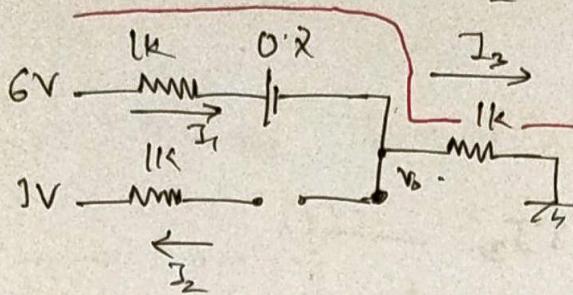

$$I_2 = 0. \quad [OFF]$$

$$I_1 = I_2 + I_3 \quad [KCL]$$

$$\therefore I_1 = I_3$$

Writing KVL along 6V to GND [Red line]

$$6 = 1I_1 + 0.2 + I_3 + 0$$

$$\Rightarrow 2I_1 = 6 - 0.2 \quad [since I_1 = I_3]$$

$$\Rightarrow I_1 = I_3 = 2.65 \text{ mA}$$


$$\therefore V_0 = 1I_3 = 2.65V$$

Now $I_1 = +ve$, so D_1 assumption correct

$\begin{aligned} & \text{Ans for } D_2, \\ & V_A = V_0 = 2.65V \\ & V_C = 1V \\ & \therefore V_D = 1.65V \end{aligned}$

So assumption wrong

Assume $D_1 = ON, D_2 = ON$

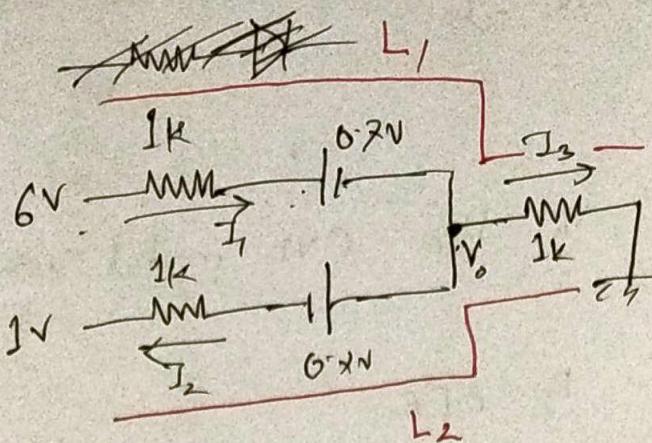

KVL along L_1

$$6 = 1I_1 + 0.2 + 1I_3 \quad \text{--- (1)}$$

$$\text{KVL along } L_2 \\ 1 = -1I_2 - 0.2 + 1I_3 \quad \text{--- (1')}$$

KCL \Rightarrow

$$I_1 = I_2 + I_3 \quad \text{--- (1'')}$$

Solving (1), (1') and (1'')


$$I_1 = 2.96 \text{ mA}$$

$$I_2 = 0.63 \text{ mA}$$

$$I_3 = 2.33 \text{ mA}$$


$$\therefore V_o = 1I_3 = 2.33 \text{ V}$$

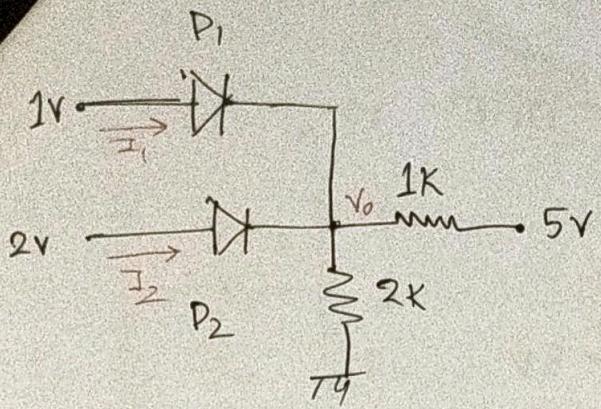$I_1 = +ve \Rightarrow D_1 \text{ assumption correct} \checkmark$
 $I_2 = +ve \Rightarrow D_2 \text{ assumption correct} \checkmark$



Find I_1 , I_2 and V_o . Assume the diodes are ideal.

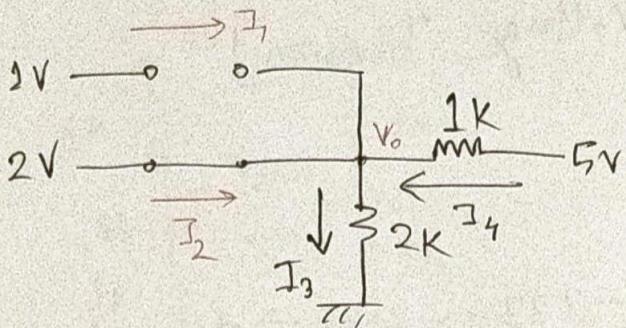Sol'n.: Assume $D_1 = \text{OFF}$, $D_2 = \text{ON}$



$$\therefore I_1 = 0 \quad (\text{OFF})$$

$$\therefore V_o = 2V$$

$$\therefore I_3 = \frac{V_o}{2} = 1\text{mA}, \quad I_4 = \frac{5 - V_o}{1} = \frac{5 - 2}{1} = 3\text{mA}$$


$$\text{KCL} \Rightarrow I_2 + I_4 = I_3 \Rightarrow I_2 = I_3 - I_4$$

$$\therefore [I_2 = -2\text{mA}]$$

D_2 assumption wrong

For D_1 , $V_D = V_A - V_C = 1 - 2 = -1 \Rightarrow$ Assumption correct

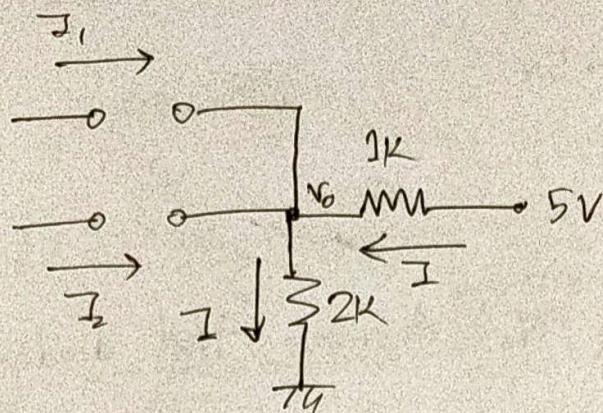Assume $D_1 = \text{OFF}$, $D_2 = \text{OFF}$



$$I_1 = 0$$

$$I_2 = 0$$

$$V_o = \frac{2}{2+1} \times 5 \quad [\text{Voltage Division}]$$


$$\Rightarrow V_o = 3.33V$$

For $D_1 \Rightarrow V_D = V_A - V_C = 1 - 3.33 = -2.33 \Rightarrow \text{Assumption correct}$

For $D_2 \Rightarrow V_D = V_A - V_C = 2 - 3.33 = -1.33 \Rightarrow$


✓ ↴

(3)

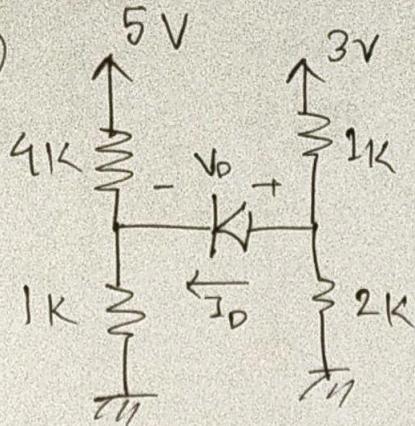

Find V_D and I_D . Use CVD with $V_g = 0.8V$.

Solⁿ: Assume diode OFF

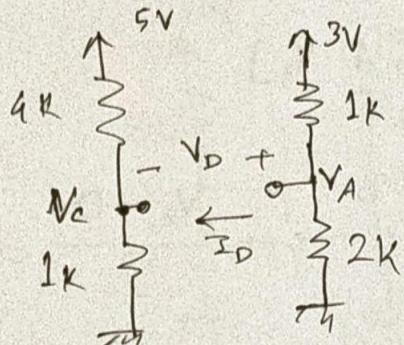

$$\therefore I_D = 0$$


$$V_A = \frac{2}{2+1} \times 3 = 2V \quad [\text{Voltage division}]$$

$$V_C = \frac{1}{9+1} \times 5 = 1V \quad [\quad \quad \quad]$$

$$\therefore V_D = V_A - V_C = 2 - 1 = 1V$$

∴ Assumption wrong!

So, the diode would be on!

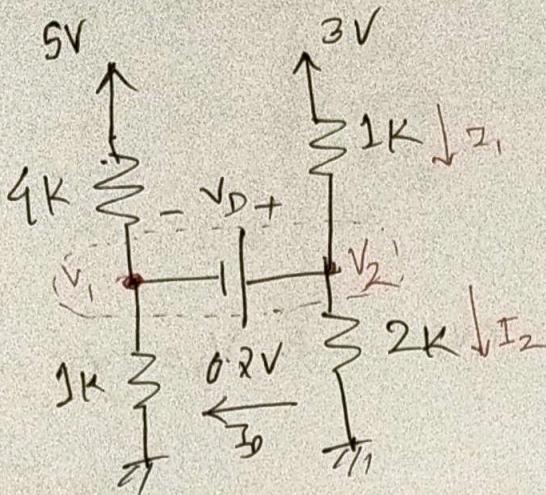

$$\therefore V_D = 0.2V$$

Super node equation (V_1 and V_2)

$$\frac{V_1 - 5}{4} + \frac{V_1 - 0}{1} + \frac{V_2 - 3}{1} + \frac{V_2 - 0}{2} = 0 \quad (1)$$

$$V_2 - V_1 = 0.2 \quad (II)$$


Solving (I) and (II)

$$V_1 = \cancel{1.636V} \approx 1.63V$$

$$V_2 = 1.863V$$

$$I_1 = \frac{3 - V_2}{1} = 1.137 \text{ mA}, \quad I_2 = \frac{V_2 - 0}{2} = 0.932 \text{ mA}$$

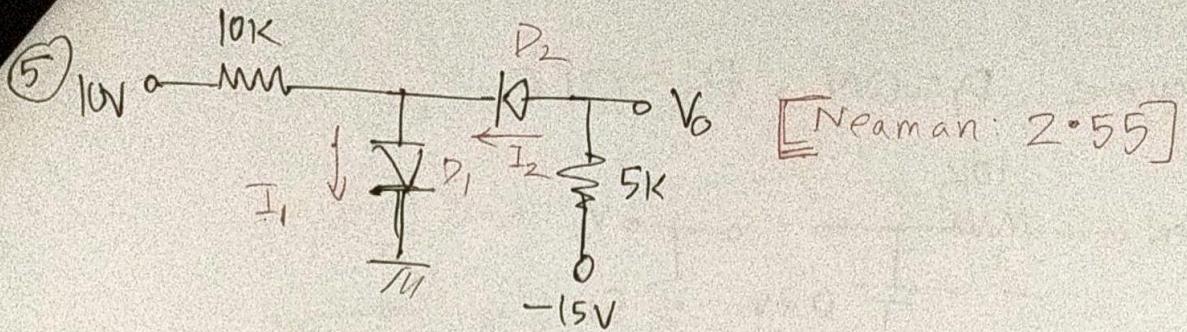
$$\therefore I_D = I_1 - I_2 \quad [\text{KCL}] = 0.205 \text{ mA} \quad [\text{Correct assumption}]$$



[Neaman: 2.55]

Find V_0, I_1, I_2 . Use CVD model with $V_2 = 0.2V$.

Soln: Assume $D_1 = ON, D_2 = ON$.

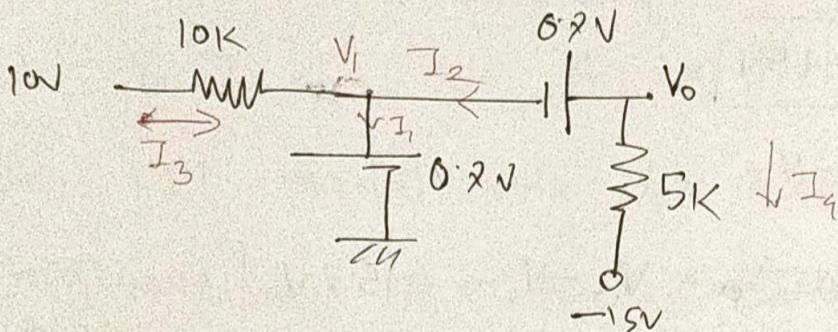

$$V_1 = 0.2V$$

$$V_0 = V_1 + 0.2V = 1.4V$$

$$I_3 = \frac{10 - 0.2}{10} = 0.93mA$$


$$I_4 = \frac{1.4 - (-15)}{5} = 3.28mA$$

From KCL, $I_2 = -I_4 = -3.28mA$ [Assumption wrong for D_2]

$$I_1 = I_3 + I_2 = -2.35mA$$

[Assumption wrong for D_1]

Assume $D_1 = ON$, $D_2 = OFF$

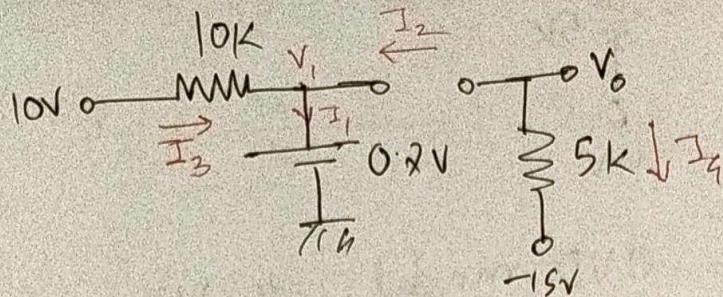

$$\text{open } CKT \Rightarrow I_2 = 0$$

$$I_4 = 0$$

$$\therefore \boxed{V_0 = -15V}$$

$$V_1 = 0.2V$$

$$\therefore V_{D_2} = \cancel{V_0} - \cancel{V_D} = V_0 - V_1 = -15.2V$$

[Assumption correct for D_2]

$$I_3 = \frac{10 - V_1}{10} = \frac{10 - 0.2}{10} = 0.93mA$$


$$I_1 = I_3 = 0.93mA$$

[Assumption correct for D_1]

$$\therefore \boxed{V_0 = -15V}$$

Ans


(6)

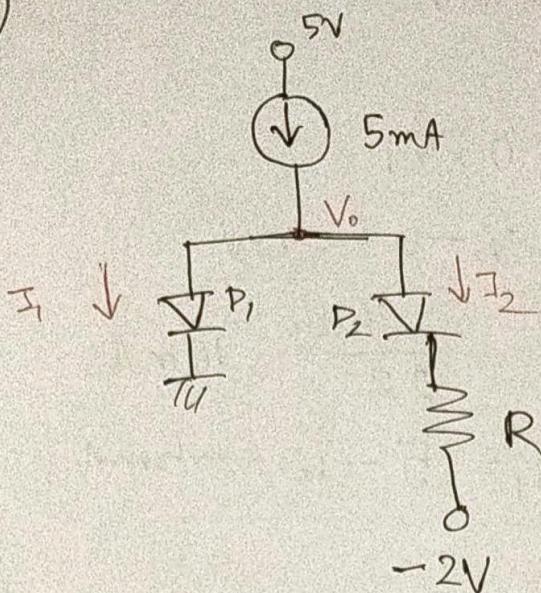

Find V_o , I_1 and I_2 for (a) $R = 100\text{ k}\Omega$, (b) ~~$R = 1\text{ k}\Omega$~~ .

Use CVD model with $V_T = 0.2\text{ V}$.

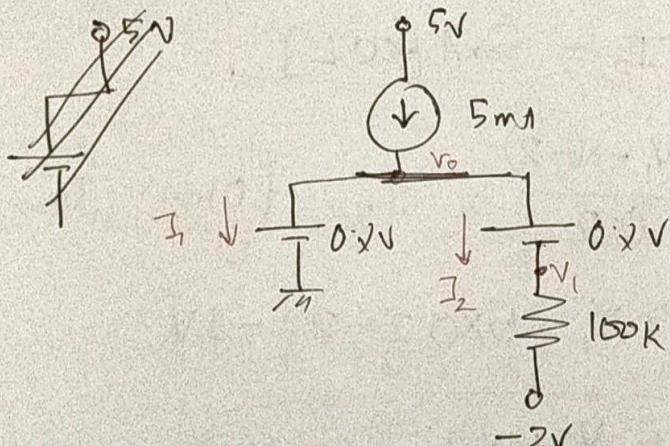Solⁿ: (a) assume $D_1 = \text{ON}$, $D_2 = \text{ON}$




$$V_o = 0.2\text{ V}$$

$$V_i = V_o - 0.2 = 0\text{ V}$$

$$\therefore \begin{cases} I_2 = \frac{0 - (-2)}{100} = 0.02\text{ mA} \\ I_1 = 5 - I_2 \quad [\text{KCL}] = 4.98\text{ mA} \end{cases}$$

Since I_1 and I_2 both are positive, Assumption correct.

b) Assume $D_1 = ON, D_2 = ON$

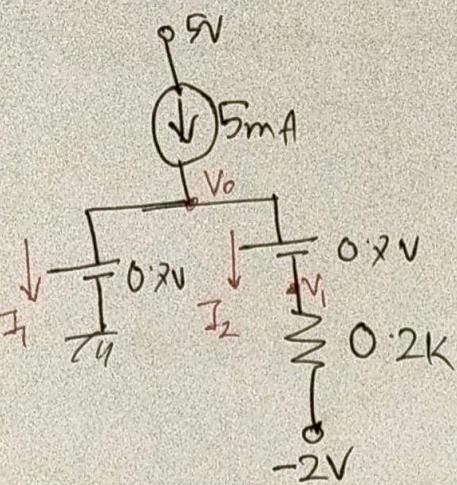

$$V_o = 0.2V$$


$$V_i = V_o - 0.2 = 0V$$

$$I_2 = \frac{0 - (-2)}{0.2} = 10mA$$

$$\therefore I_1 = 5 - I_2 = -5mA$$

Since current through D_1 is negative, assumption wrong.

Assume $D_1 = OFF, D_2 = ON$

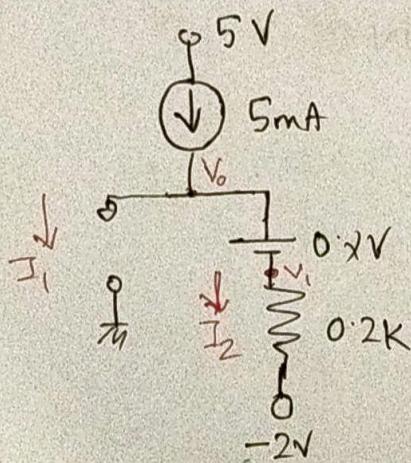

$$I_1 = 0mA$$

$$I_2 = 5mA [FCL]$$

$$\frac{V_i - (-2)}{0.2} = I_2 \quad [Ohm's Law]$$

$$\Rightarrow V_i = 5 \times 0.2 - 2 = -1V$$

$$V_o = V_i + 0.2 = -0.3V$$

Since $V_D = -0.3V$ for D_1 and $V_D < 0.2V$

assumption for D_1 correct.

$I_1 = +ve \Rightarrow$ Assumption for D_2 correct.