

CSE 251: Electronic Devices and Circuits




Lecture 2

Operational Amplifier:

Introduction, Open Loop Configuration, Circuit Modeling

Operational Amplifiers

Textbook

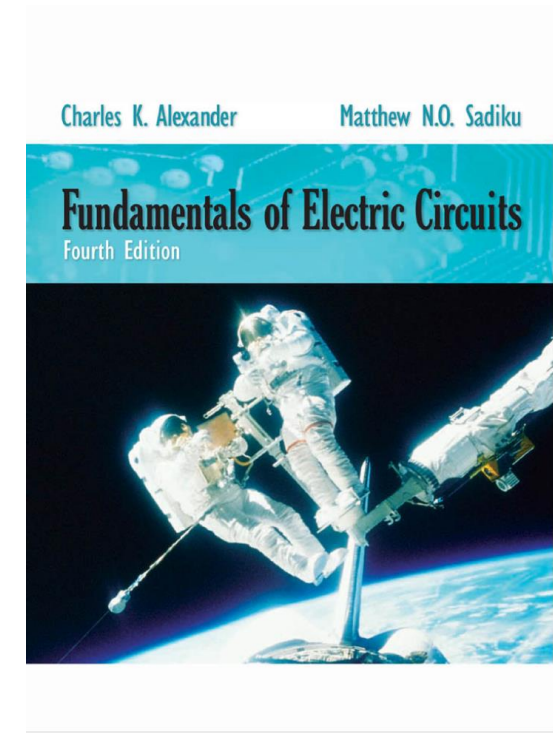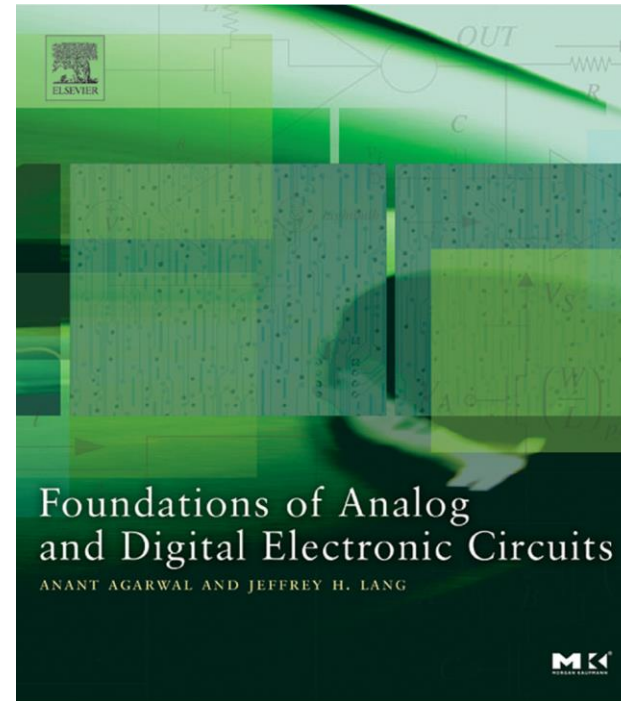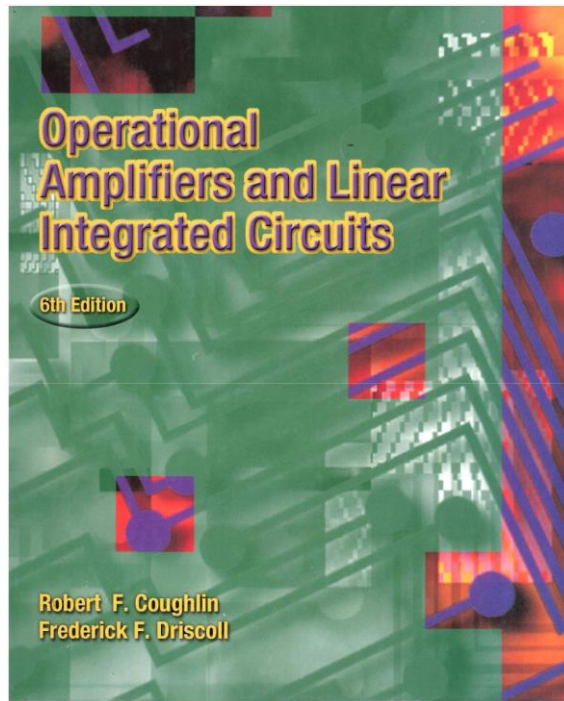

Outline


- **Operational Amplifier: Introduction**
 - Dependent Sources
 - Op-Amp: Circuit Symbols and terminal
 - Op-Amp: VTC (Voltage Transfer Characteristics)
 - Linear Amplification
 - (Positive and Negative) Saturation
 - Op-Amp: Examples
 - Op-Amp: Physical Entity

Dependent Sources


To analyze op-amps, we must understand **dependent source**.

A dependent source generates a voltage or current whose value depends on another voltage or current.

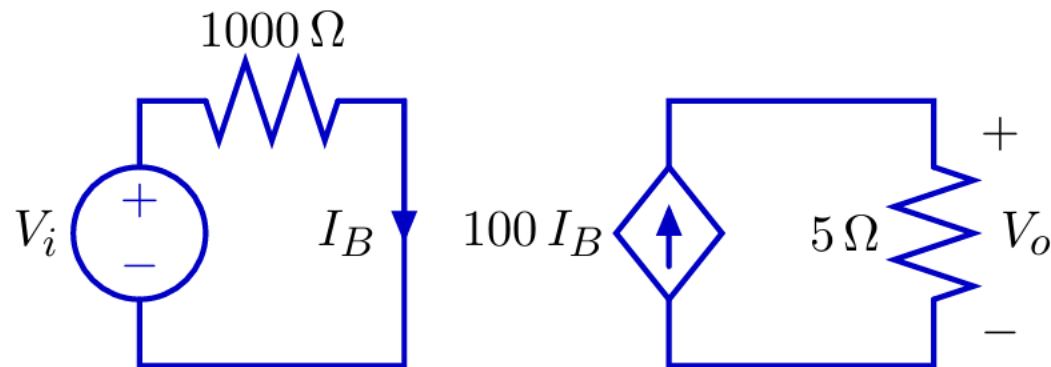Example: current-controlled current source



Dependent Sources

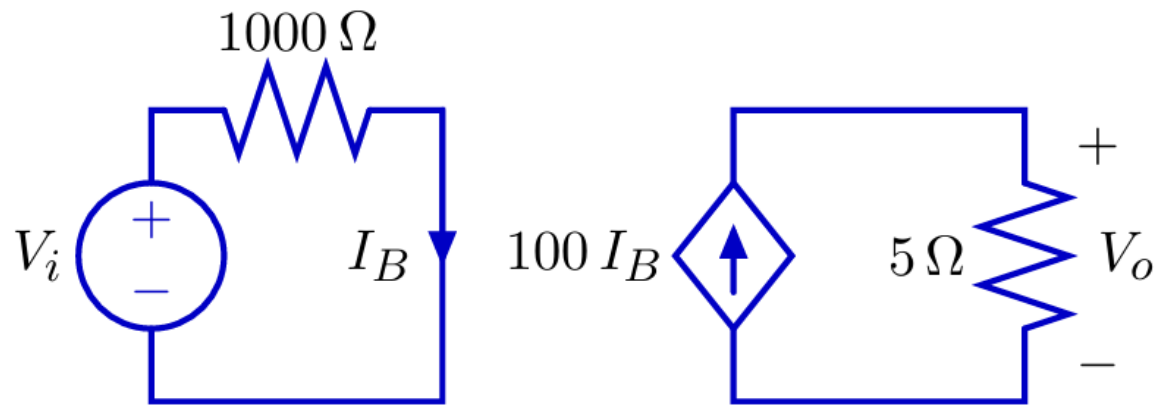

$$I_B = \frac{V_i}{1000\ \Omega}$$



$$V_o = 100 I_B \times 5\ \Omega$$

$$\text{Voltage Gain: } \frac{V_o}{V_i} = \frac{1}{2}$$


$$= 100 \frac{V_i}{1000\ \Omega} \times 5\ \Omega = \frac{1}{2} V_i$$

Dependent Sources

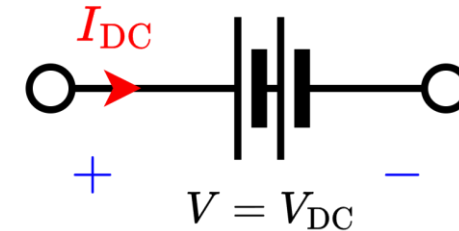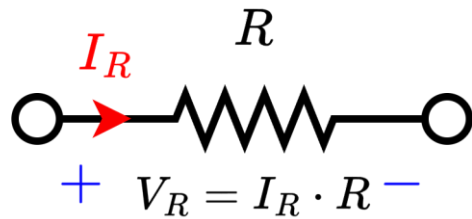Resistors, (Ind.) Voltage sources, (Ind.) Current sources are single “**port**” device. They are characterized by a **single equation**.



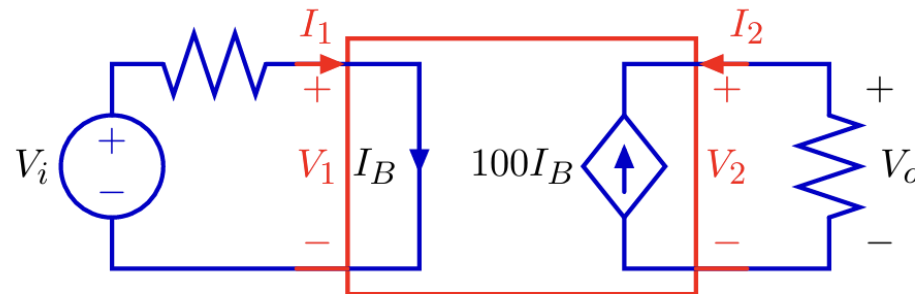
Dependent sources are two-ports: characterized by **two** equations.




Here $V_1 = 0$ and $I_2 = -100 I_1$.

Operational Amplifier: Introduction

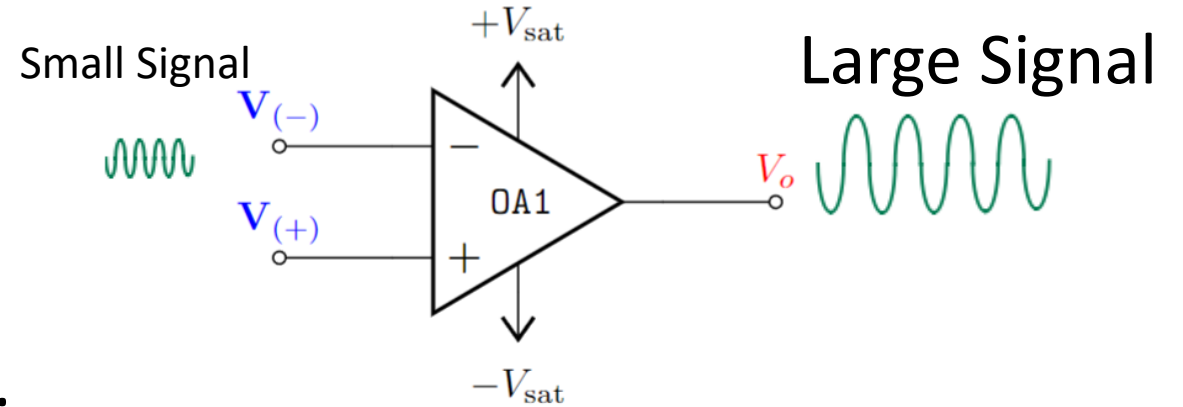- **Operational:**
Mathematical Operations
- **Amplifier:**
Amplifies input signal/voltage.




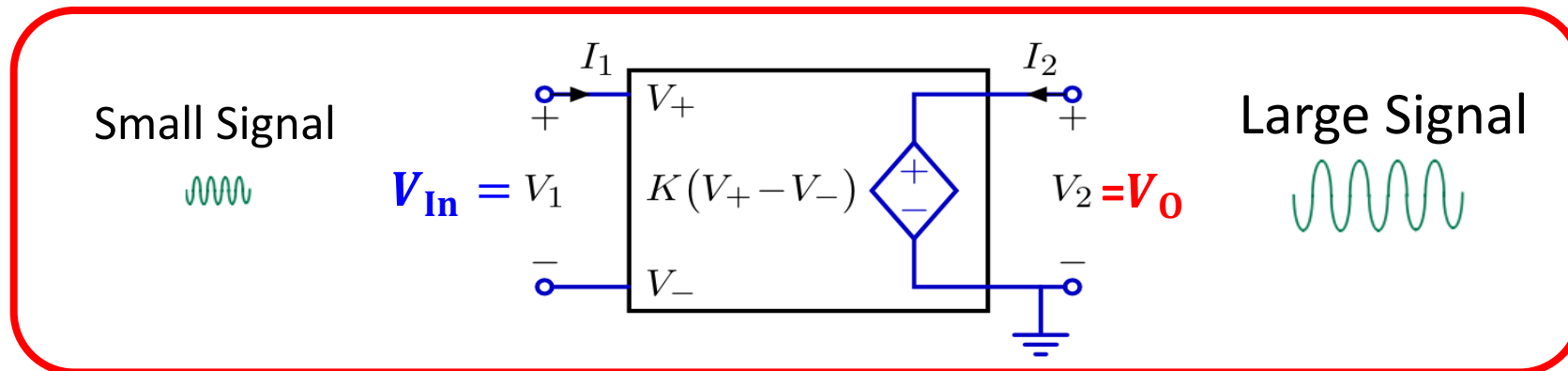An **op-amp (operational amplifier)** can be modelled by a **voltage- controlled voltage source**.




Operational Amplifier: Introduction

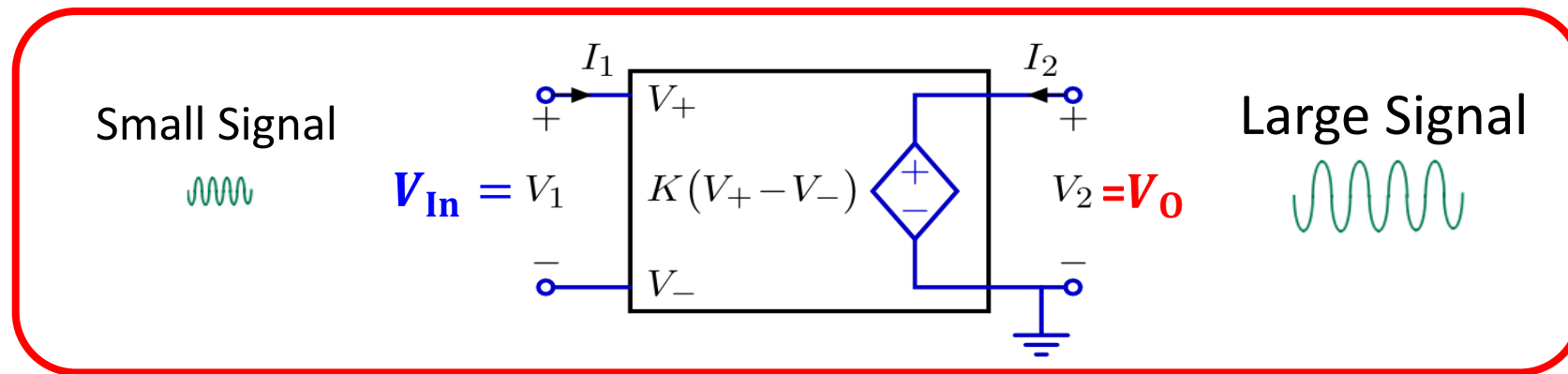An **op-amp (operational amplifier)** can be represented by a **voltage- controlled voltage source**.




$I_1 = 0$ and $V_O = K V_{In}$ where K is large (typically $K > 10^5$).

Op-Amp: Circuit Symbols and terminal

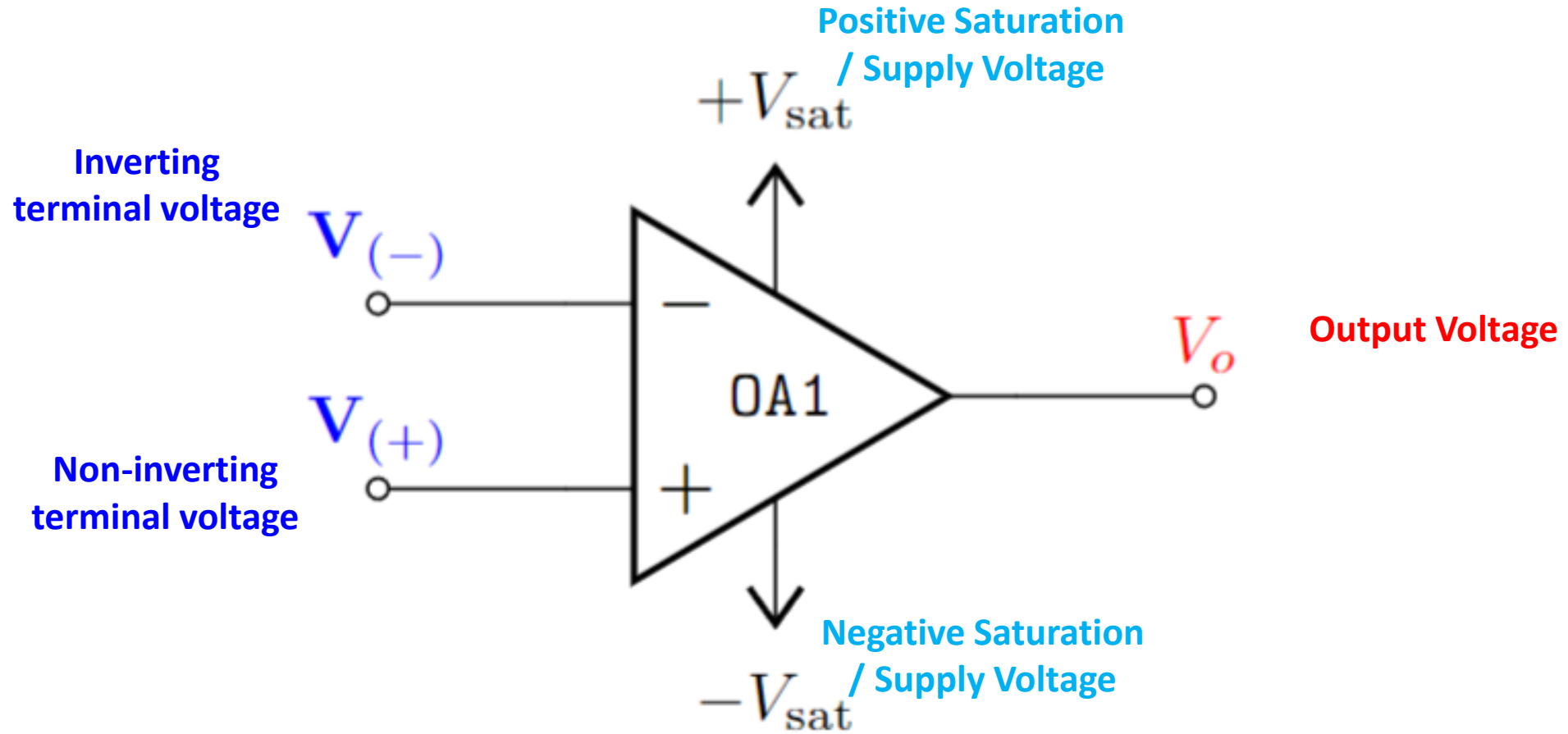

Op-Amp: Circuit Symbols and terminal

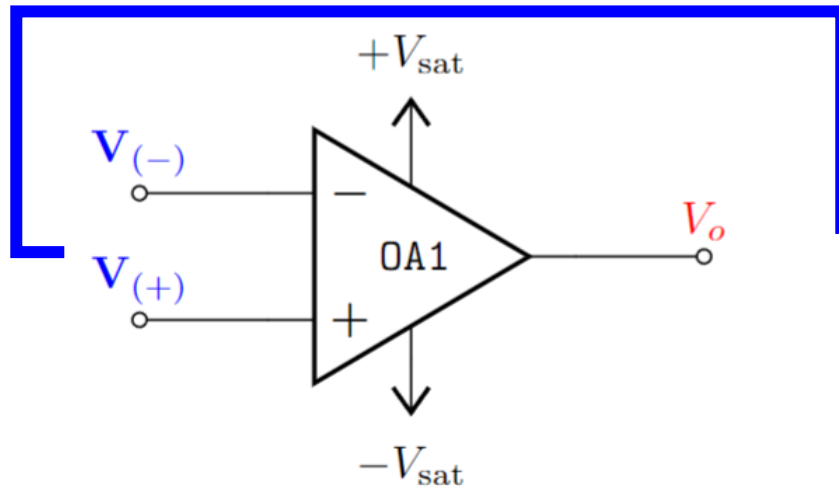


$$V_d = V_{(+)} - V_{(-)}$$


Difference Amplifier –

Amplifies the voltage difference between two terminals.

V_d **Differential input voltage**

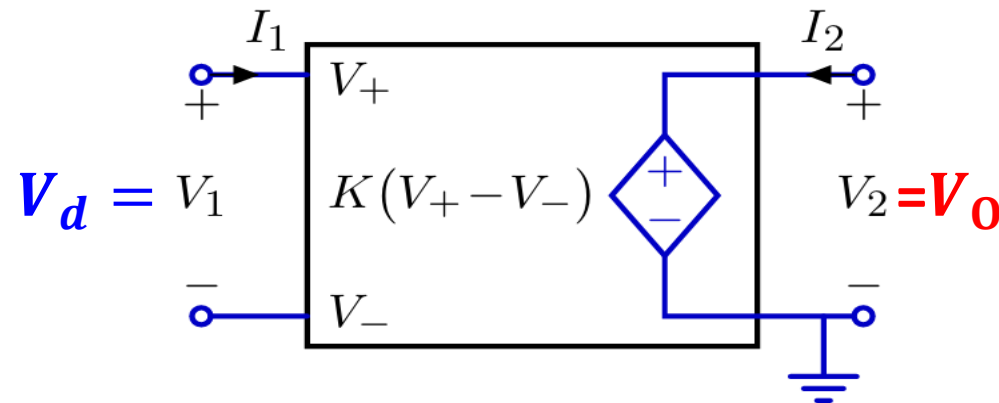

Voltage Transfer Characteristics (VTC)

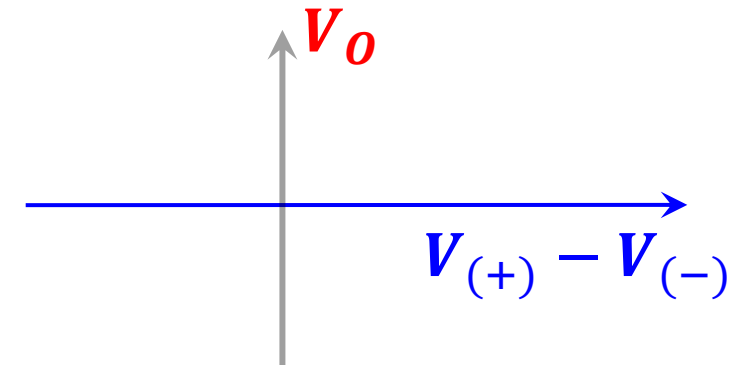

Op-Amp: VTC – Linear Amplification

Voltage Transfer Characteristics (VTC)

- Shows how the **output voltage** varies with the **input voltage** $V_O(V_d)$


- y –axis $\rightarrow V_O$

- x –axis $\rightarrow V_d$

- Slope: $K = \frac{\Delta V_O}{\Delta V_d} = \frac{V_O}{V_d}$

If the line passes through origin:



$$y = K \cdot x$$
$$V_O = K \cdot V_d$$

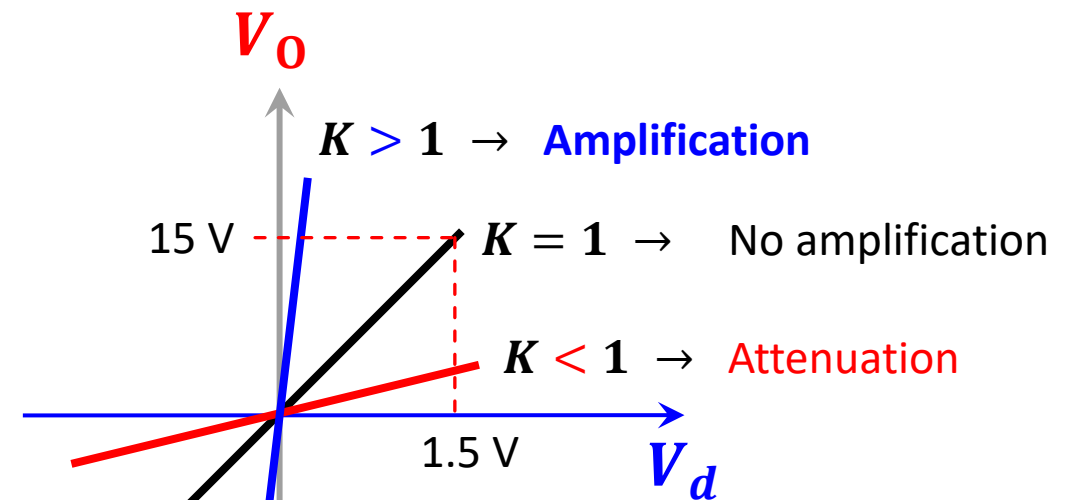

LINEAR AMPLIFICATION


Op-Amp: VTC – Linear Amplification

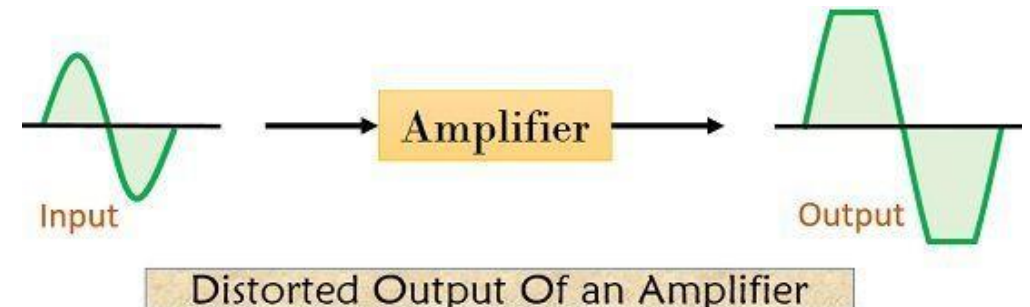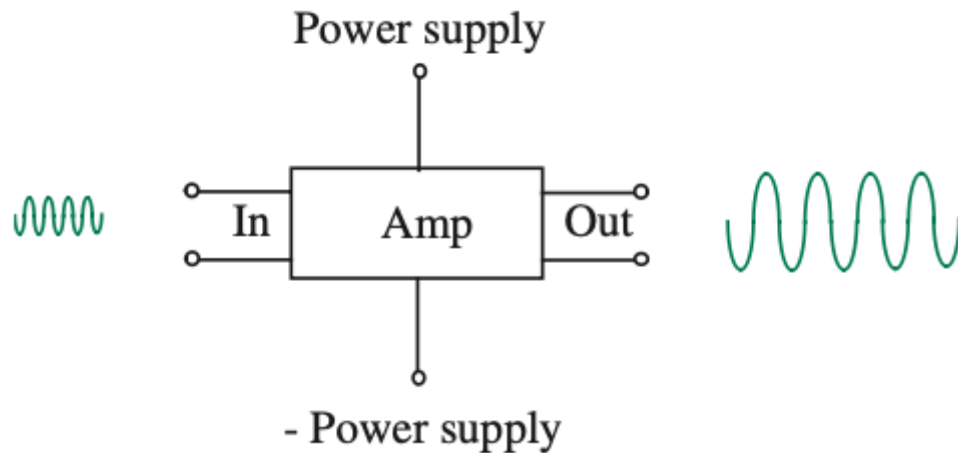- **Linear Amplification** only takes place within a [valid input range](#).
- Otherwise output will be distorted - - Saturation



The limiting factor of **linear amplification** is determined by the **power supply** to the amplifier


Op-Amp: VTC - Saturation

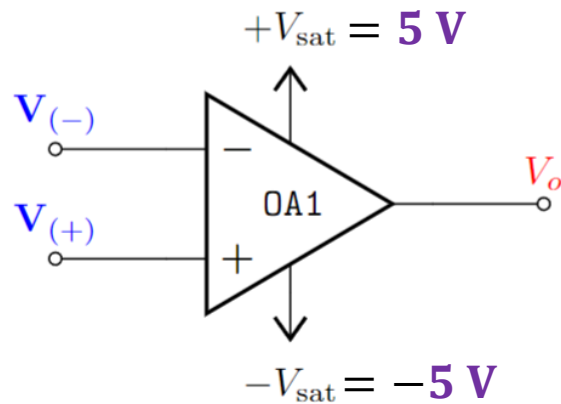

$$V_o = K \cdot V_{in} : \text{When } -5V < V_o < 5V$$

$K \rightarrow 10^5$: Gain / Amplification

Non-Linear characteristics

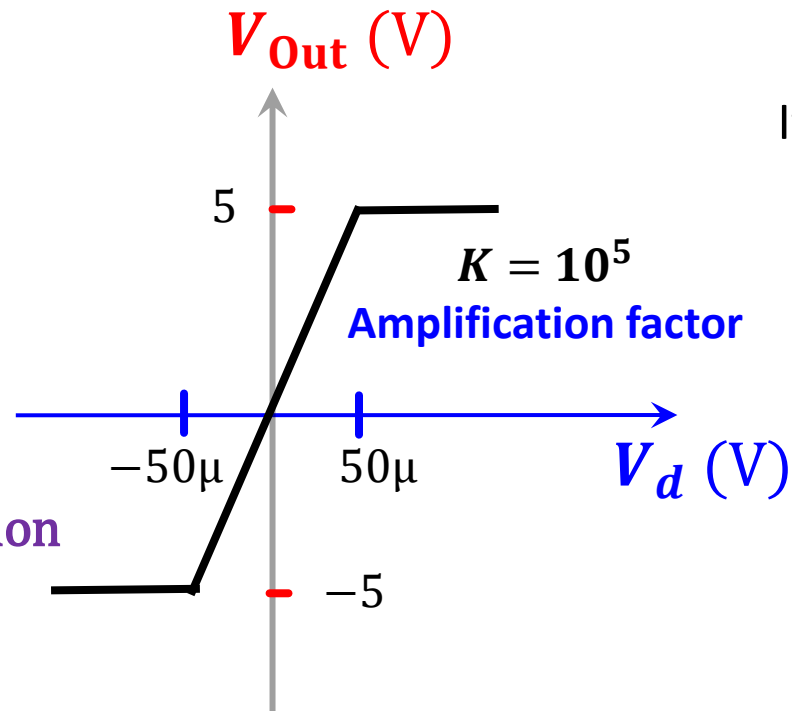



If $V_d > 50\mu$: Positive Saturation

$$\Rightarrow V_o = 5$$


If $V_d < -50\mu$: Negative Saturation

$$\Rightarrow V_o = -5$$

Op-Amp: VTC - Saturation

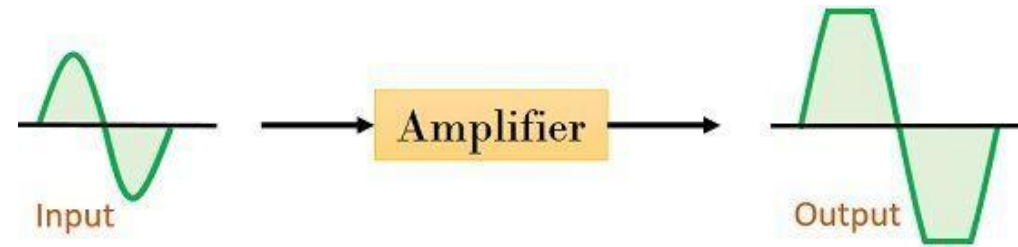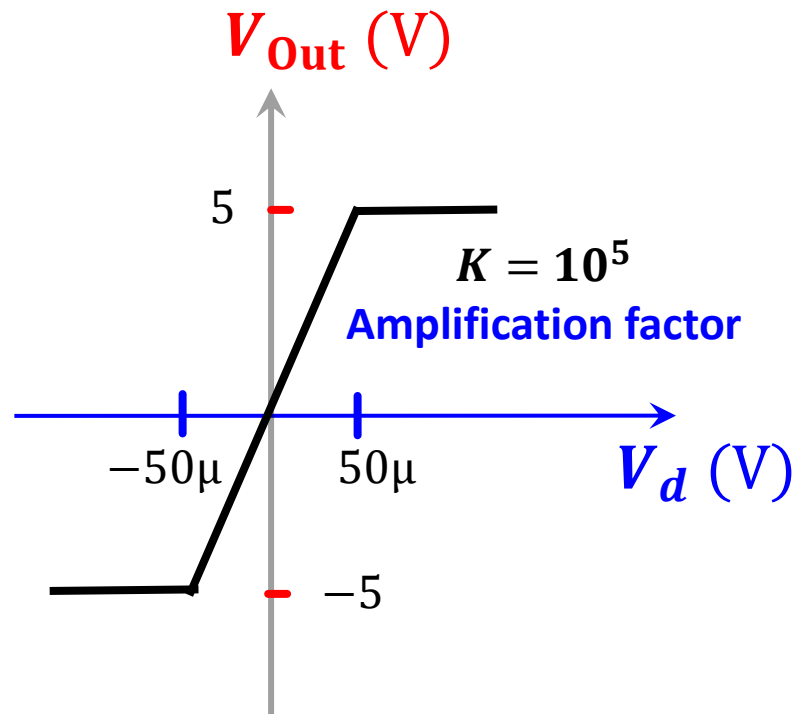

Distorted Output Of an Amplifier

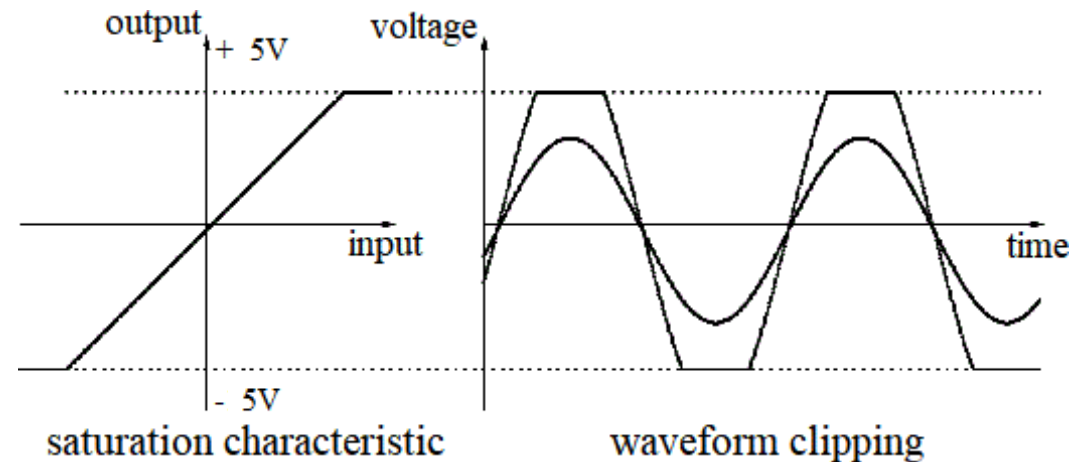

Op-Amp: VTC - Summary

Voltage Transfer Characteristics (VTC)

Positive saturation:

If $V_d > \frac{+V_{\text{sat}}}{A}$: **Positive**

$$\Rightarrow V_o = +V_{\text{sat}}$$


Linear Region

$V_o = AV_d$: When V_d is very small
 $-V_{\text{sat}} < V_o = AV_d < +V_{\text{sat}}$

Negative saturation:


If $V_d < \frac{-V_{\text{sat}}}{A}$: **Negative**

$$\Rightarrow V_o = -V_{\text{sat}}$$

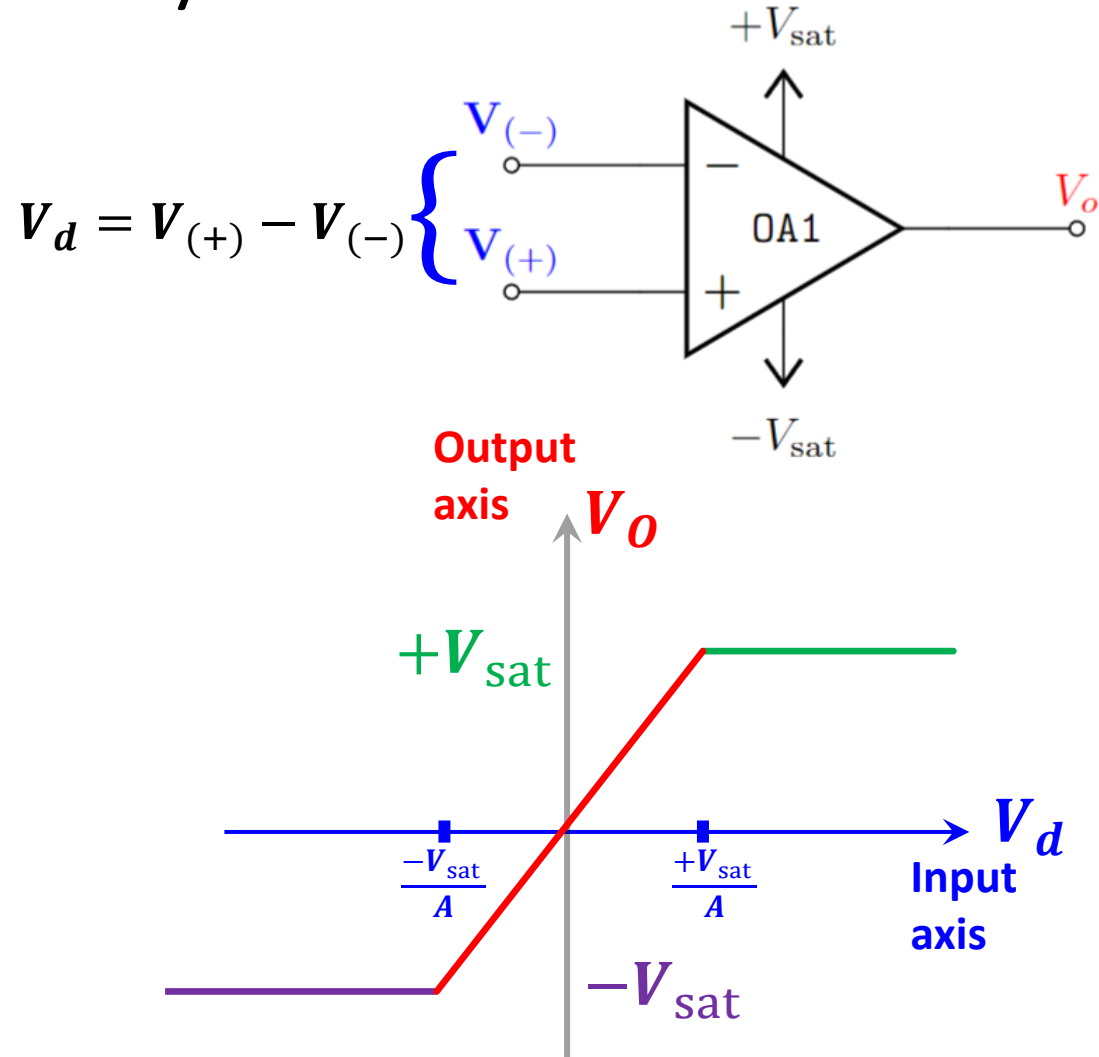


Op-Amp: Examples

Find v_o

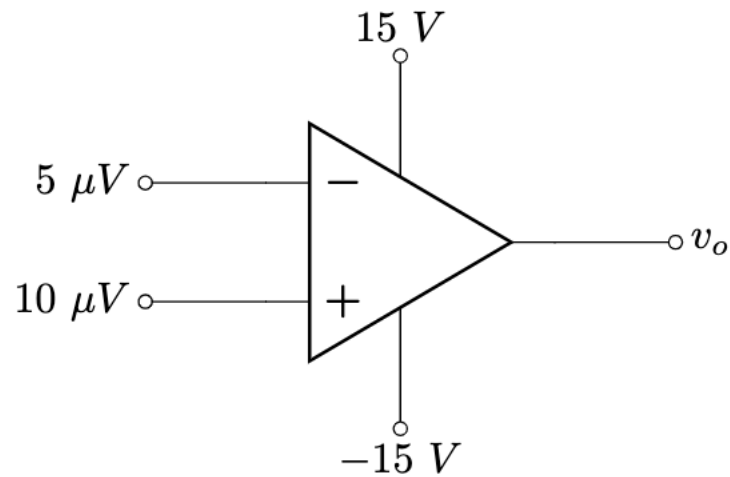

$$A = 2 \times 10^5$$

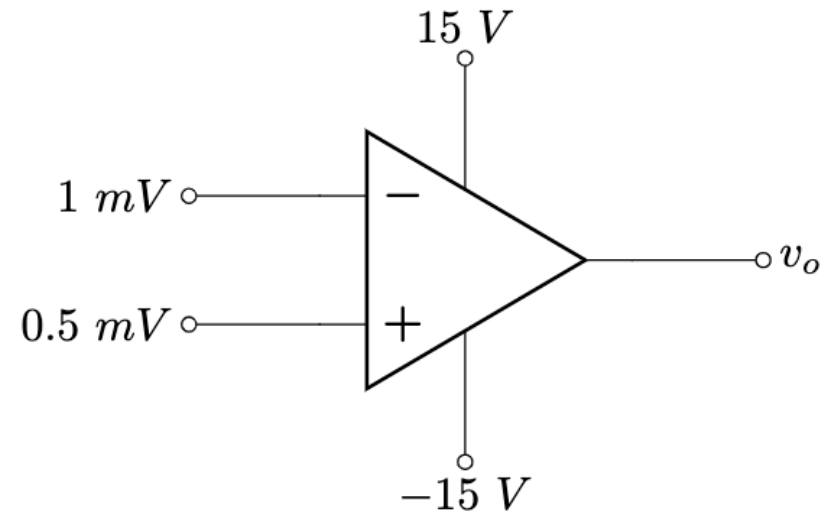


$$A = 2 \times 10^5$$

Example 1

- Find v_o

Solution:

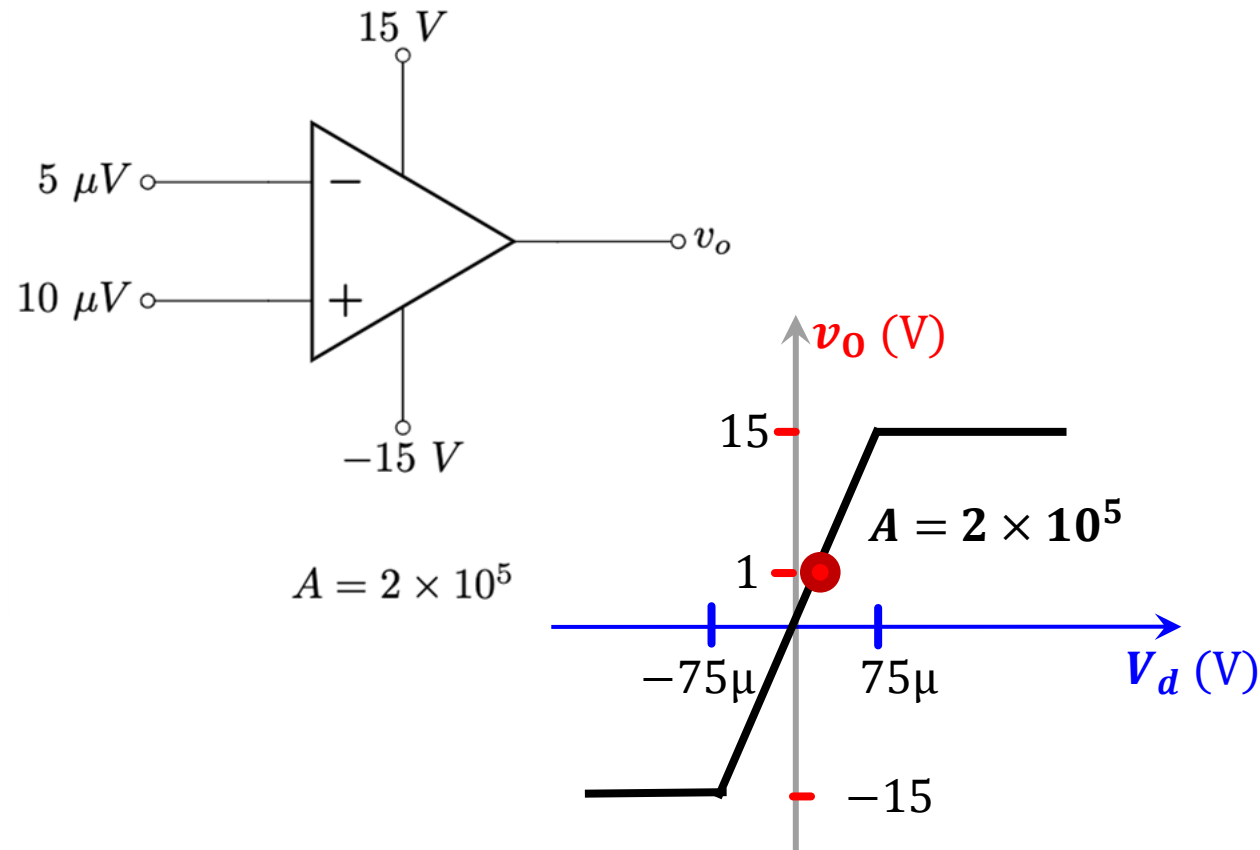

$$V_d = V_{(+)} - V_{(-)} = (10 - 5)\ \mu\text{V} = 5\ \mu\text{V}$$


$$AV_d = (2 \times 10^5) \times (5 \times 10^{-6})\ \text{V} = 1\ \text{V}$$

Since $-15\ \text{V} < AV_d < +15\ \text{V}$

$$V_o = AV_d = 1\ \text{V}$$

Example 2

- Find v_o

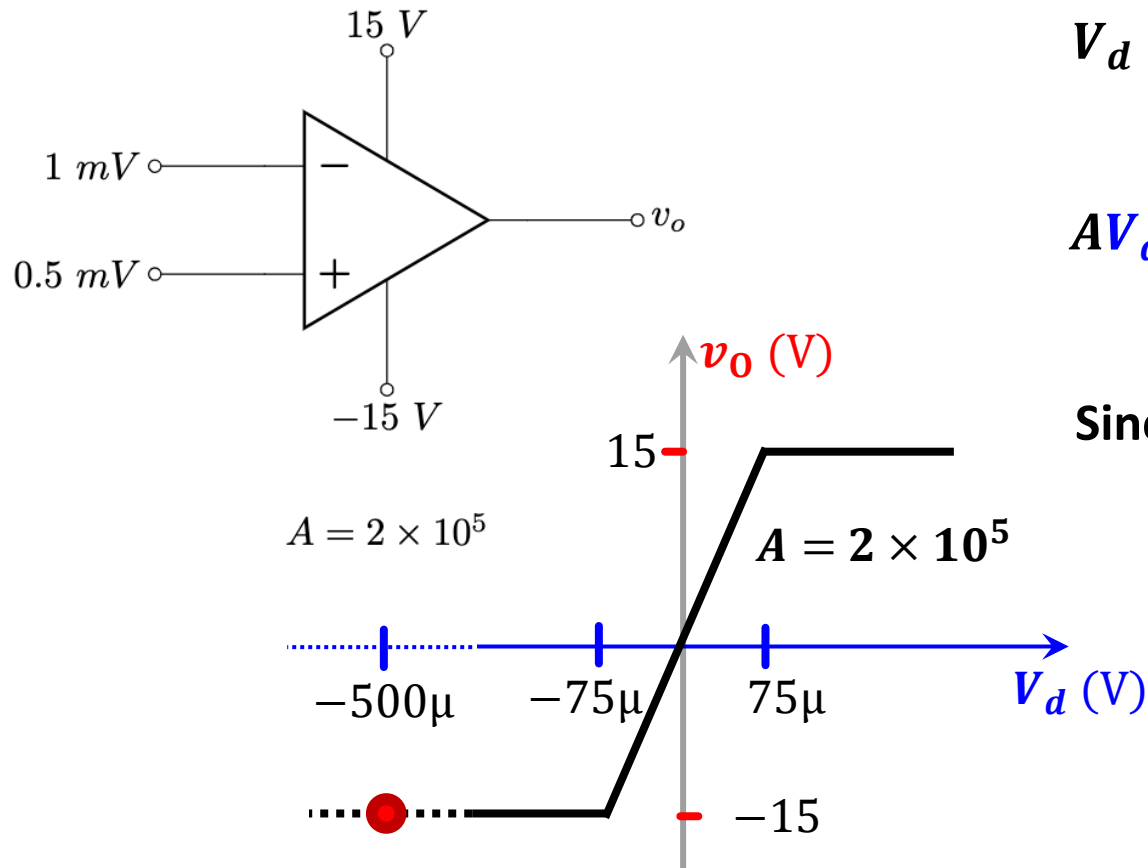

Solution:

$$V_d = V_{(+)} - V_{(-)} = (0.5 - 1) \text{ mV} = -0.5 \text{ mV}$$


$$AV_d = (2 \times 10^5) \times (-0.5 \times 10^{-3}) \text{ V} = -100 \text{ V}$$

Since $AV_d < -15 \text{ V}$ (Negative saturation)



$$V_o = AV_d = -15 \text{ V}$$

Op-Amp: Physical Entity

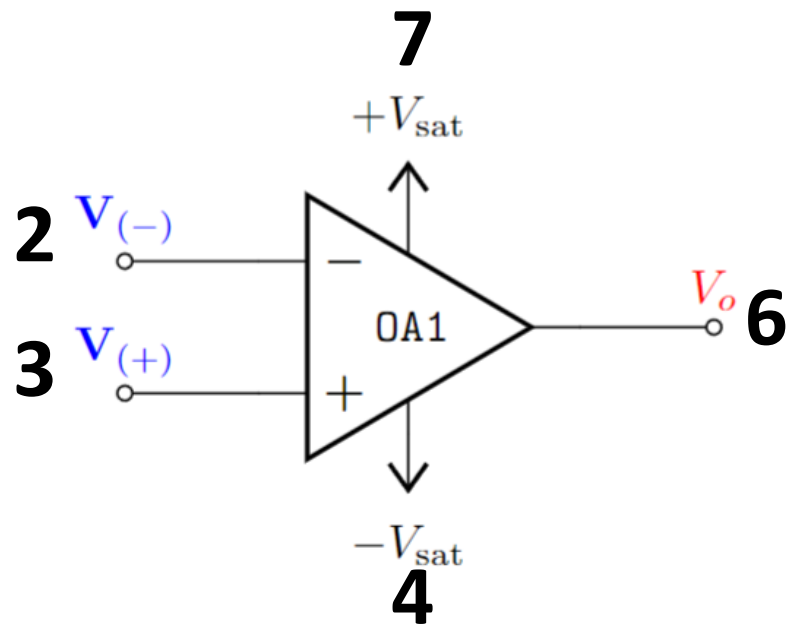Difference Amplifier – Amplifies the voltage difference between two terminals.



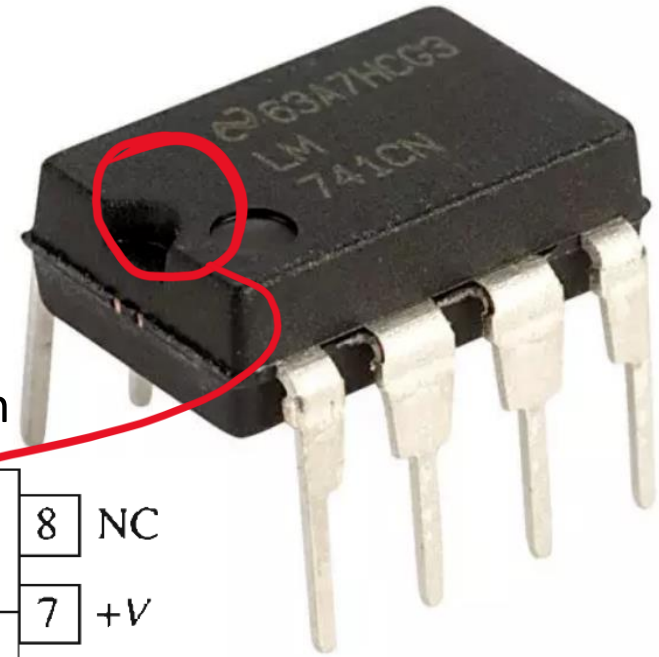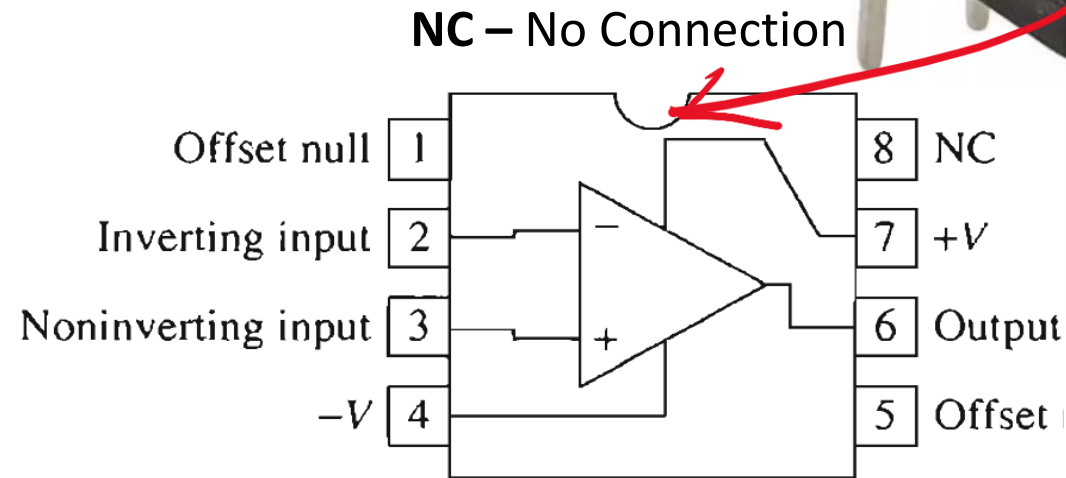Circuit symbol for the general-purpose op amp.
Pin numbering is that for an **8-pin mini-DIP package**



μ A-741C


Manufacturer ID

Part Identification Number (PIN)

C: Commercial ($0^{\circ} - 70^{\circ}\text{C}$)
I: Industrial ($-25^{\circ} - 85^{\circ}\text{C}$)
M: Military ($-55^{\circ} - 125^{\circ}\text{C}$)


Op-Amp: Summary

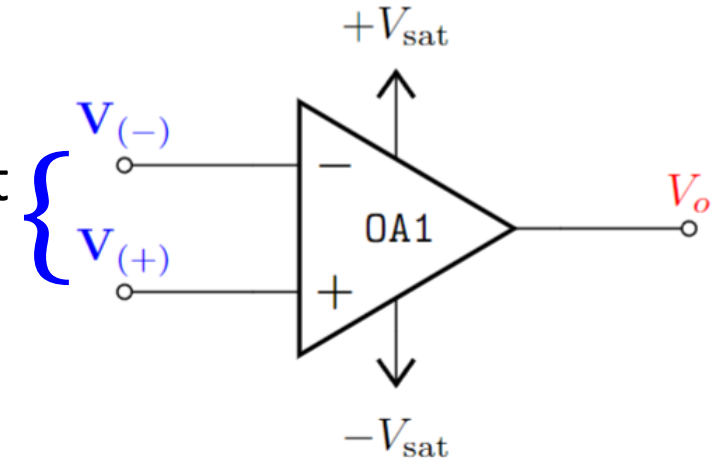Op-Amp **Amplifies** the difference between the voltages at its two input terminals - V_d



However, the **Amplification** is limited within voltage levels defined by the positive and negative saturation voltages $[-V_{sat}, +V_{sat}]$.

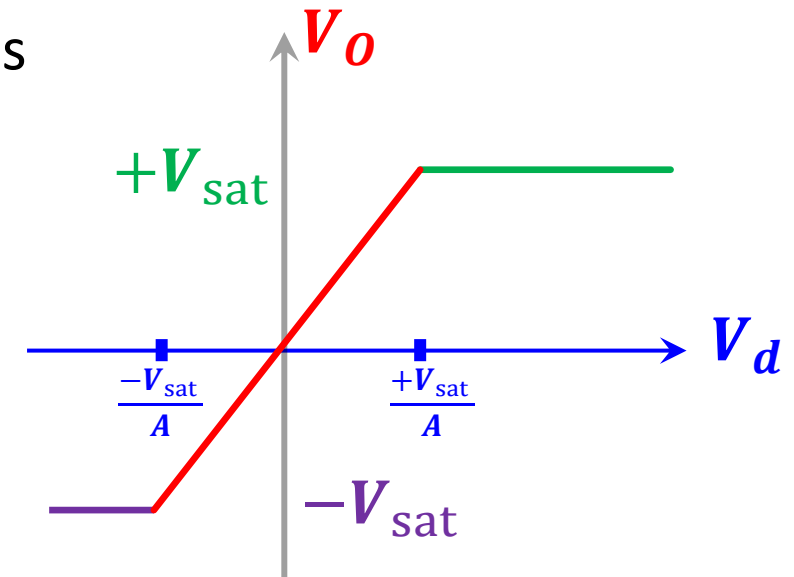The “ideal” op-amp behaves like a **voltage dependent voltage source** within the linear region.



Thank you!

Part 1 ends here


Outline

- **Op-Amp: Open Loop Configuration**
 - Op-Amp: Circuit Modelling
 - Example Problem – Op-amp model
 - Op-amp configuration – open and closed loop
 - Open Loop op-amp: Voltage Transfer Characteristics
 - Open Loop op-amp: Comparators

Op-Amp: Circuit Modelling

Voltage controlled voltage Source

“Ideal” op-amp approximation

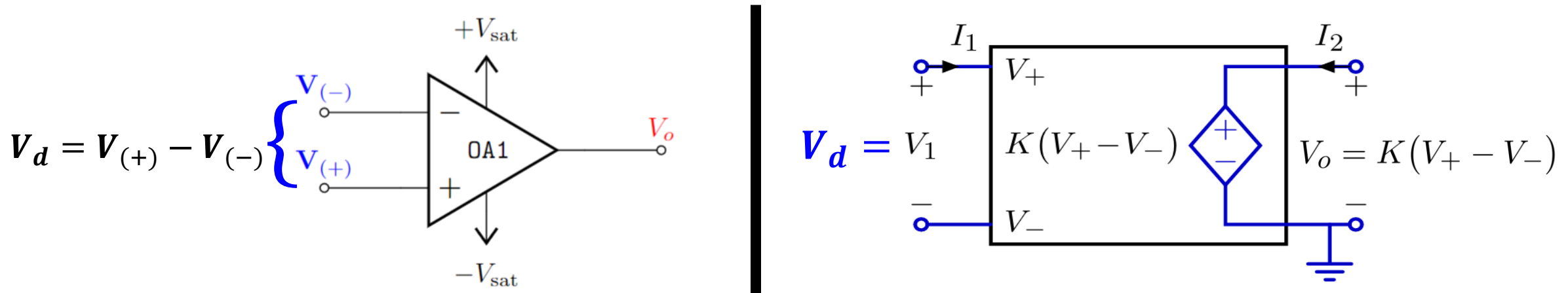



$$V_{(+)} \approx V_{(-)}$$

$$I_1 \approx 0$$

Op-amp: Circuit Model and VTC

- **Voltage (Differential/OL) Gain:** A/A_{OL} or K Slope of **VTC**
- Positive Saturation Voltage: $+V/V_{CC}/V_{sat}$
- Negative Saturation Voltage: $-V/V_{EE}/-V_{sat}$

Parameter	Typical Range	Ideally
A or K	$10^4 - 10^8$	∞

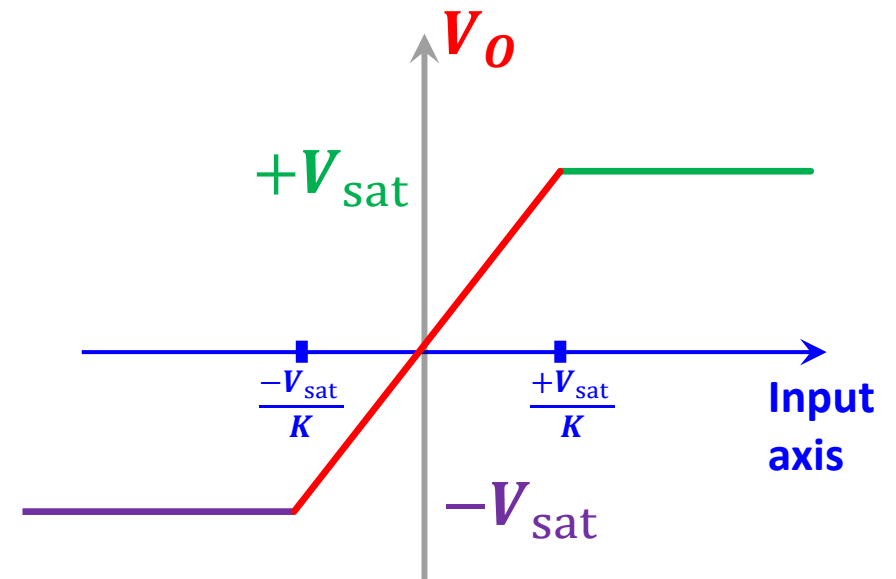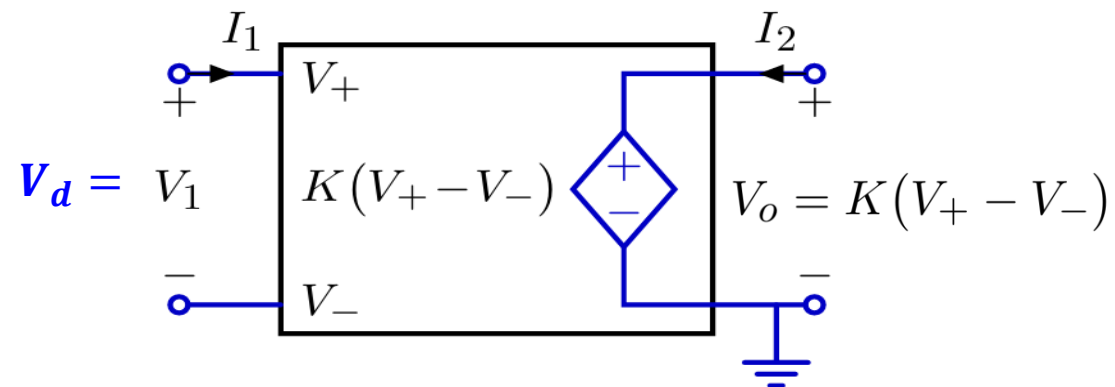

Op-amp: Circuit Model and VTC


Voltage Transfer Characteristics (VTC)

Positive saturation: $V_d > 0$
 $\Rightarrow V_o = +V_{\text{sat}}$


~~Linear Region~~

$$-V_{\text{sat}} < V_o = AV_d < +V_{\text{sat}}$$

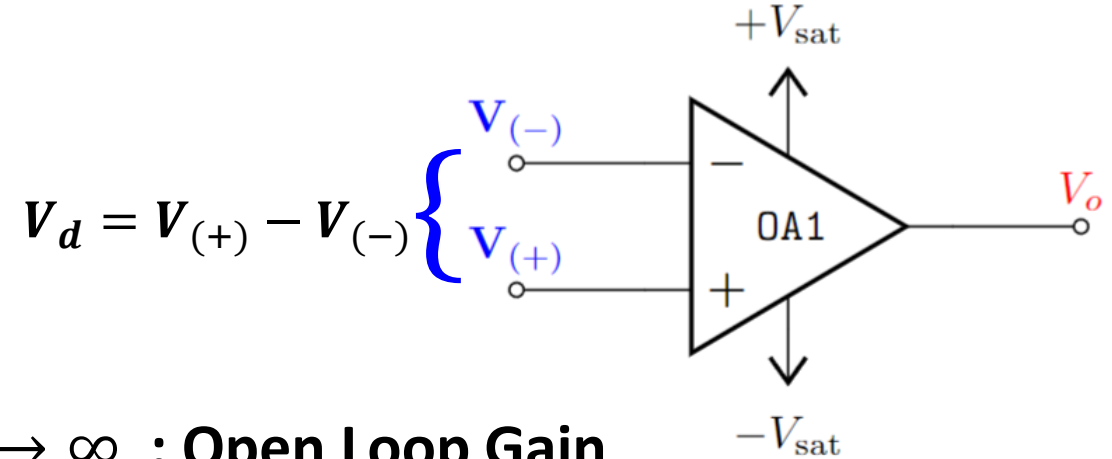Negative saturation: $V_d < 0$
 $\Rightarrow V_o = -V_{\text{sat}}$




$A \rightarrow \infty$: Open Loop Gain

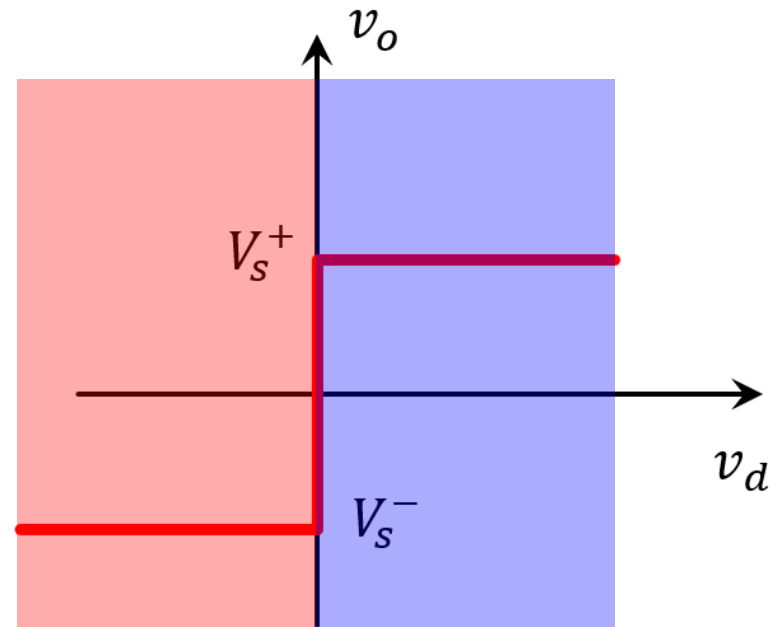

Types of Op-Amp configuration

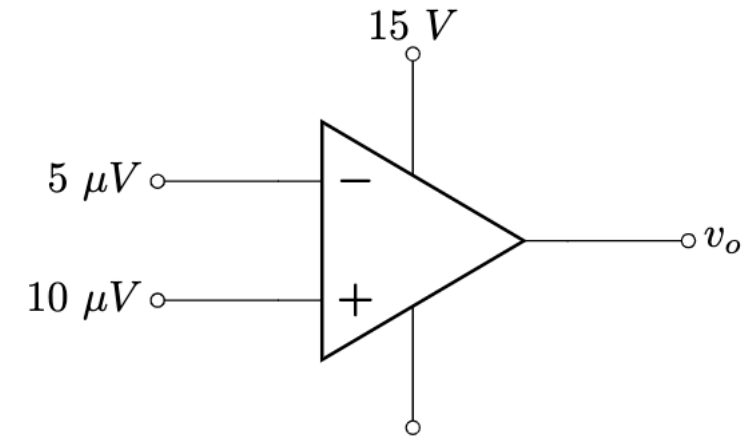
1. Open loop configuration:

No physical connection between input and output





2. Closed loop configuration:

Feedback from output terminal

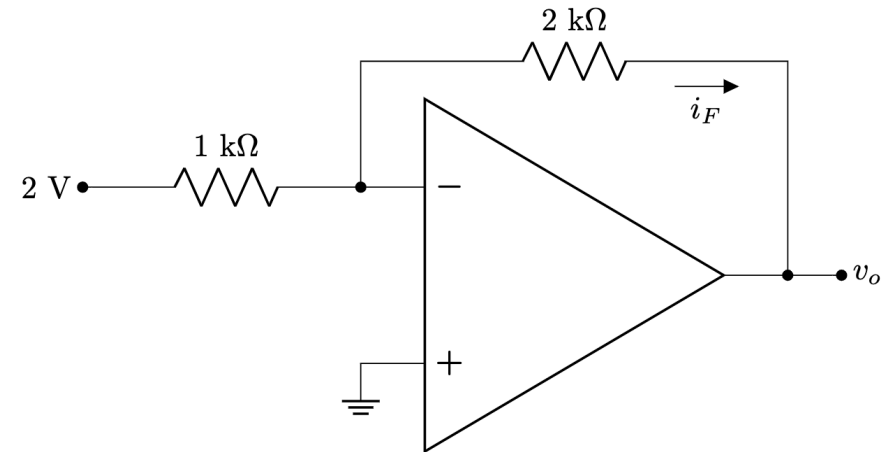

Open Loop Configuration: Comparator

Level Crossing Detector / Comparator

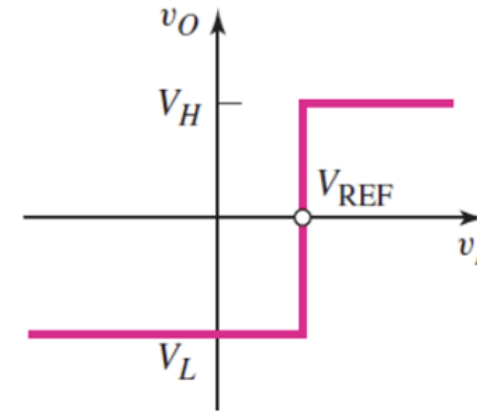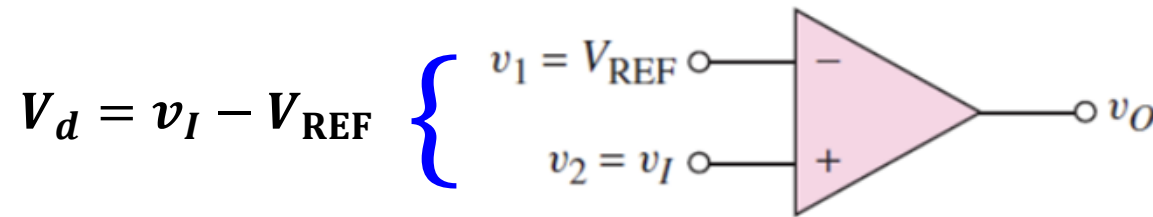

NON-INVERTING COMPARATOR



$$V_d = v_I - V_{\text{REF}} > 0 \quad \Rightarrow \quad v_O = V_H$$

$$v_I > V_{\text{REF}} \quad \Rightarrow \quad v_O = V_H$$

Open Loop Configuration: Comparator

Level Crossing Detector / Comparator

$$V_d = V_{\text{REF}} - v_I$$

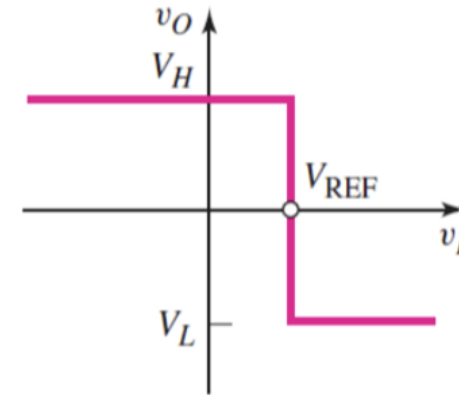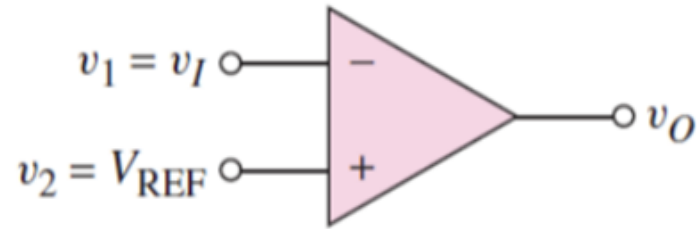

INVERTING COMPARATOR

$$V_d = V_{\text{REF}} - v_I > 0 \quad \Rightarrow \quad v_O = V_H$$




$$v_I < V_{\text{REF}} \quad \Rightarrow \quad v_O = V_H$$

Open Loop Configuration: Comparator

Zero Crossing Detector

Compare values with a reference and pin value to $+V_{sat}$ if voltage is above or to below that.

Non-inverting configuration

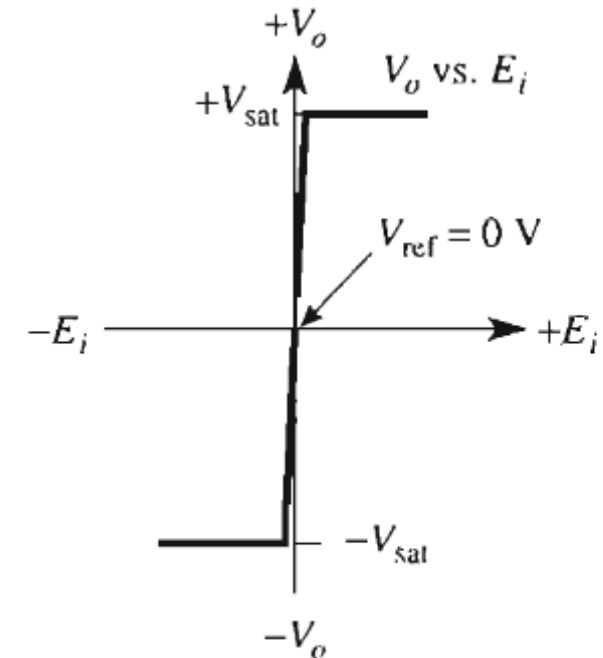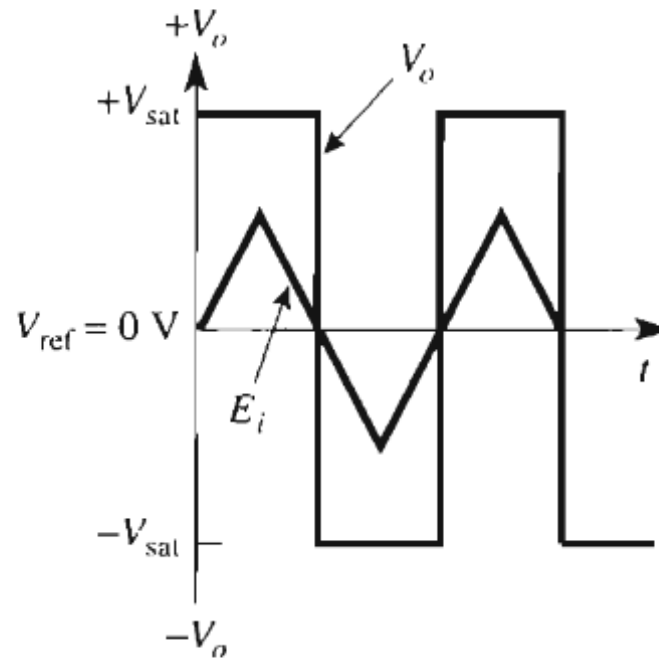
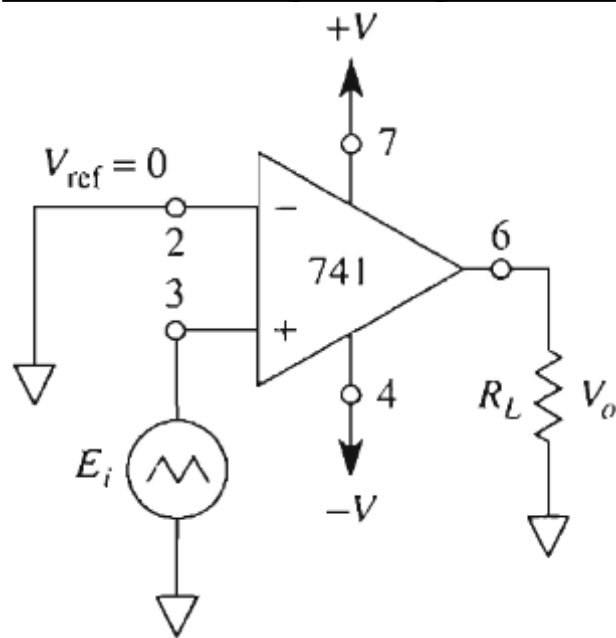


(a) Noninverting: When E_i is above V_{ref} , $V_o = +V_{sat}$.


Open Loop Configuration: Comparator

Zero Crossing Detector

Inverting configuration

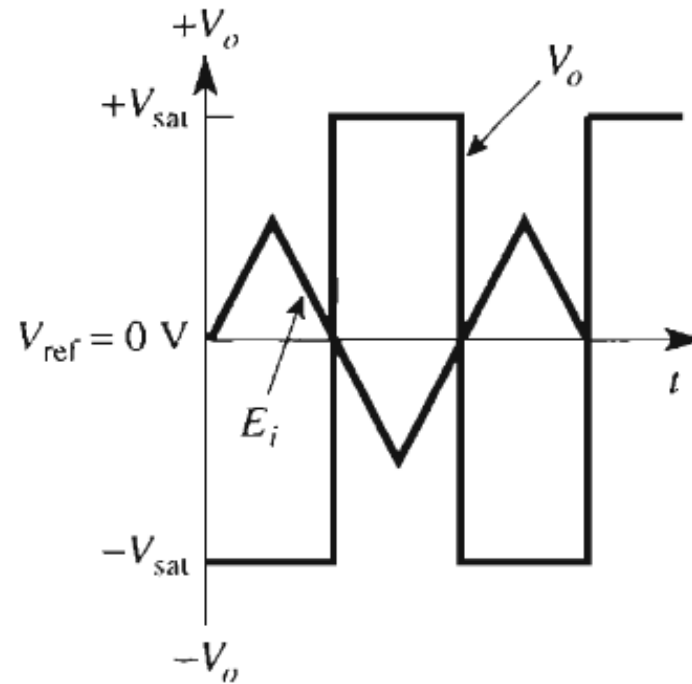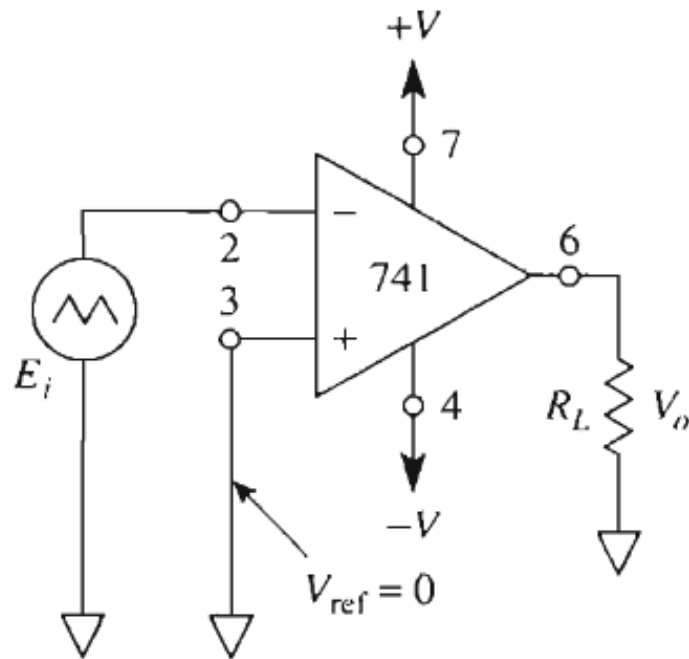

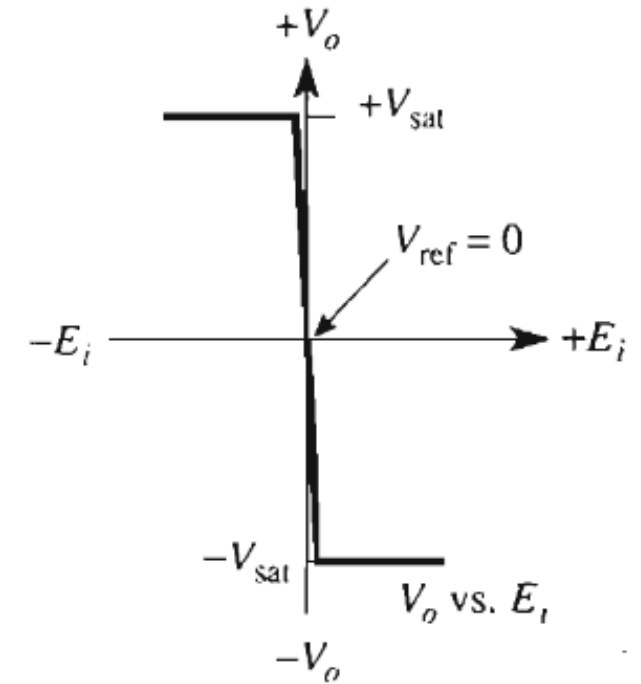(b) Inverting: When E_i is above V_{ref} , $V_o = -V_{sat}$.



Summary

Level Crossing Detector / Comparator

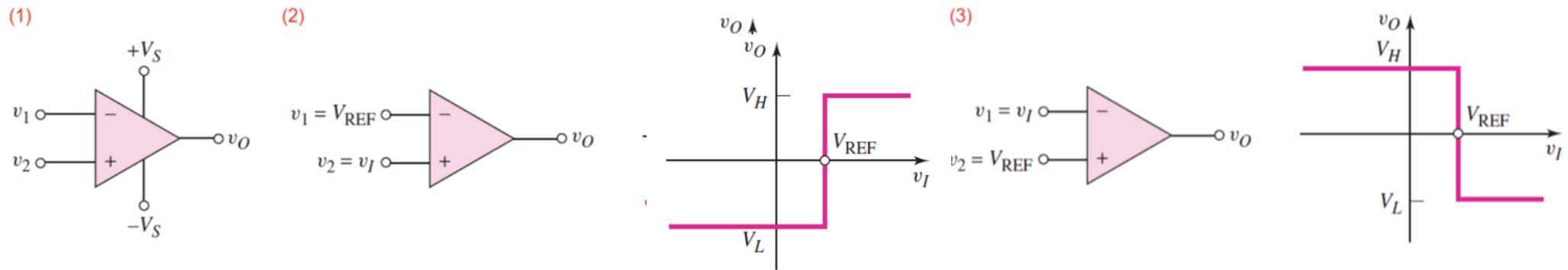


Figure 2: (1) Op-Amp Comparator (2) Noninverting Circuit (3) Inverting Circuit

Part 2 ends here


Outline

- **Op-Amp: Comparator**

- Open Loop Configuration: Example 1
- Open Loop Configuration: Example 2
- Open Loop Configuration: Example 3


Open Loop Configuration: Example 1

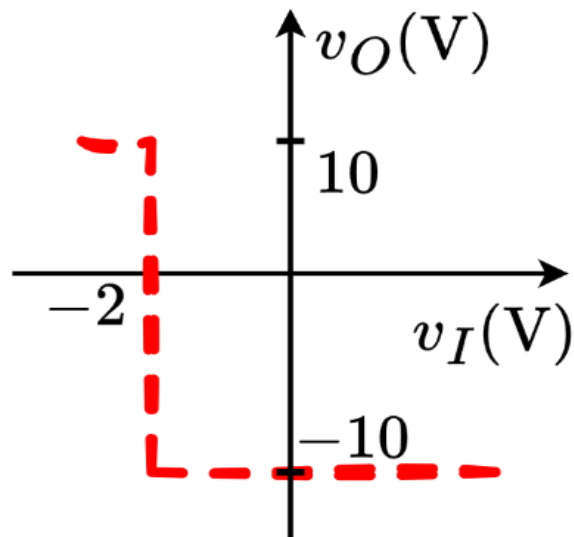- Design a circuit using **op-amp** that has the voltage transfer characteristics as shown in the figure below. $v_o(V)$ is the **output voltage** and $v_i(V)$ is the **input voltage**.



Solution:

Inverting comparator

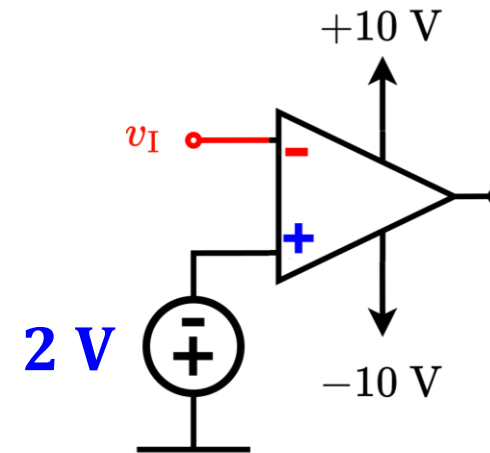


Open Loop Configuration: Example 2

- Draw the voltage transfer characteristic (VTC) curve (v_o vs v_i) from the adjacent waveform graph. Also draw the **Op-Amp Circuit** that would give rise to such a VTC.


Solution:

v_i smaller than 2 V $\Rightarrow v_o = 2.5$ V \rightarrow **Positive Saturation**

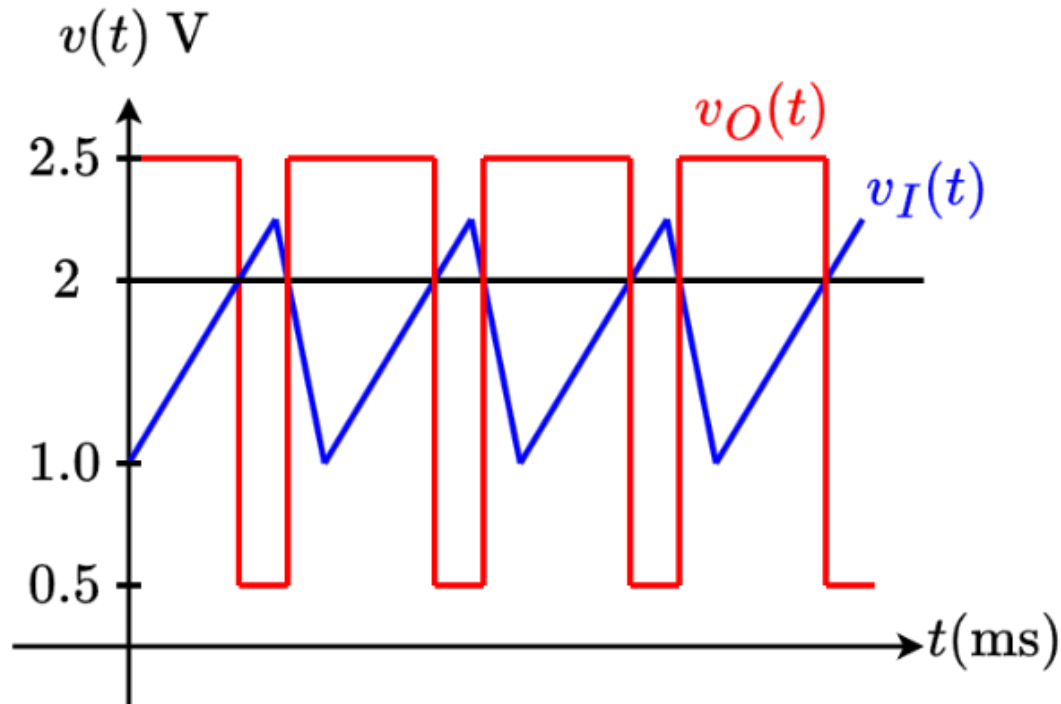v_i larger than 2 V $\Rightarrow v_o = -2.5$ V \rightarrow **Negative Saturation**





INVERTING CONFIGURATION

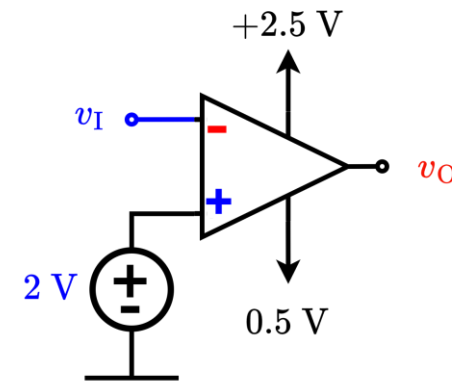

Open Loop Configuration: Example 3

Design an op-amp circuit to transform the sinusoidal voltage, $v_I = 5 \cdot \sin\left(\frac{2\pi}{5} \cdot t\right)$ (t is in units of ms , and time-period T is $5\ ms$), to: A square wave with a duty cycle of **25%**.


Solution:

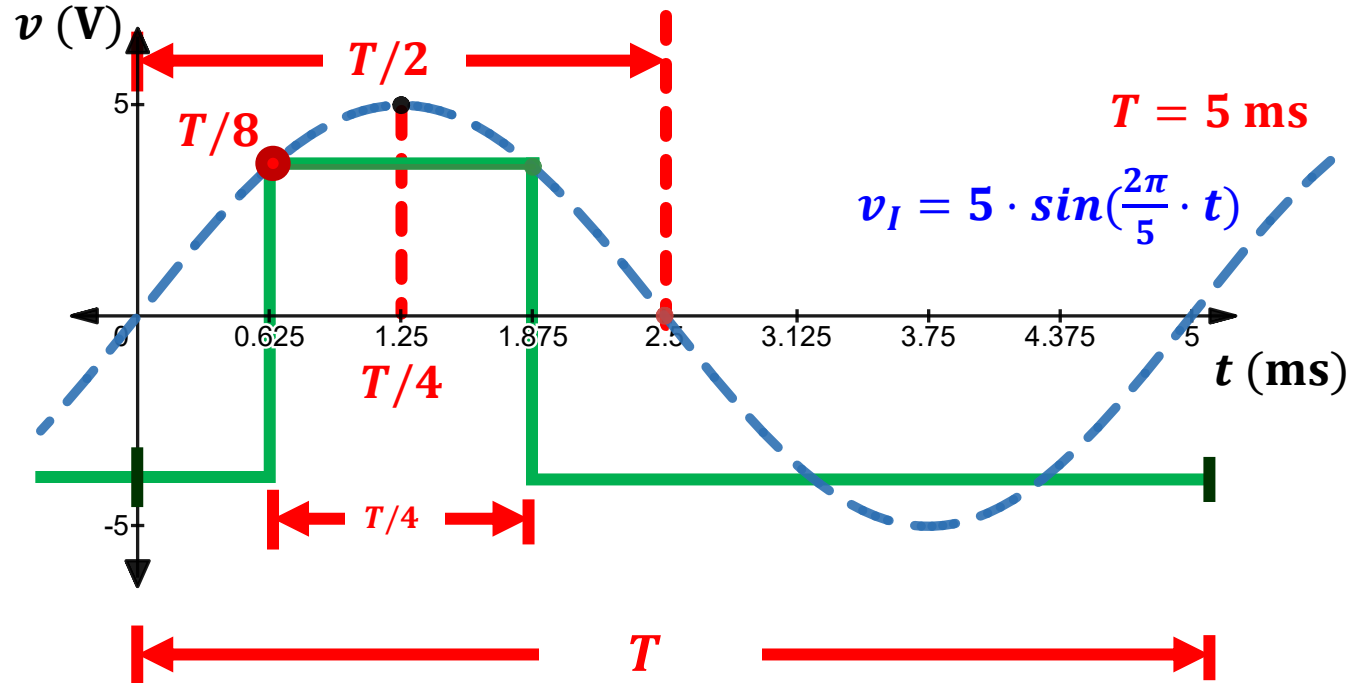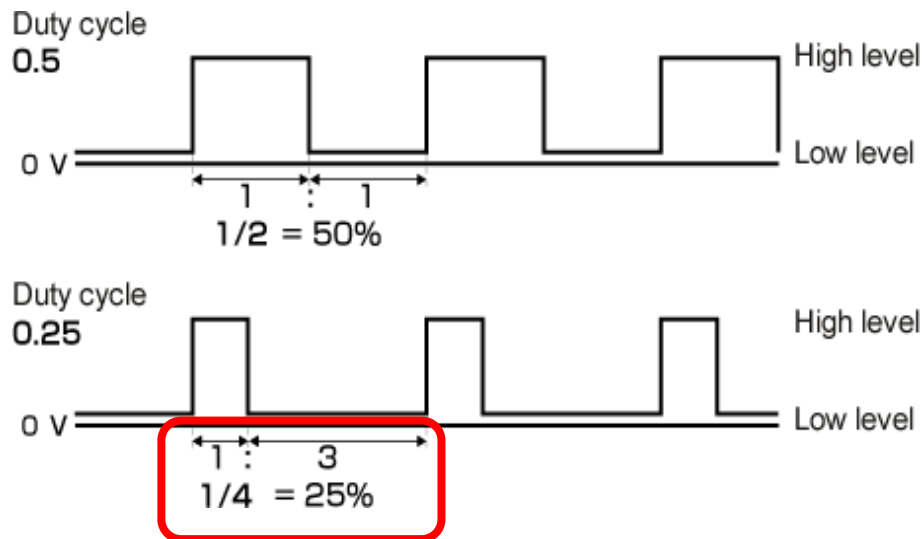

Open Loop Configuration: Example 3

Design an op-amp circuit to transform the sinusoidal voltage, $v_I = 5 \cdot \sin\left(\frac{2\pi}{5} \cdot t\right)$ (t is in units of ms , and time-period T is $5\ ms$), to: A square wave with a duty cycle of **25%**.

Solution:

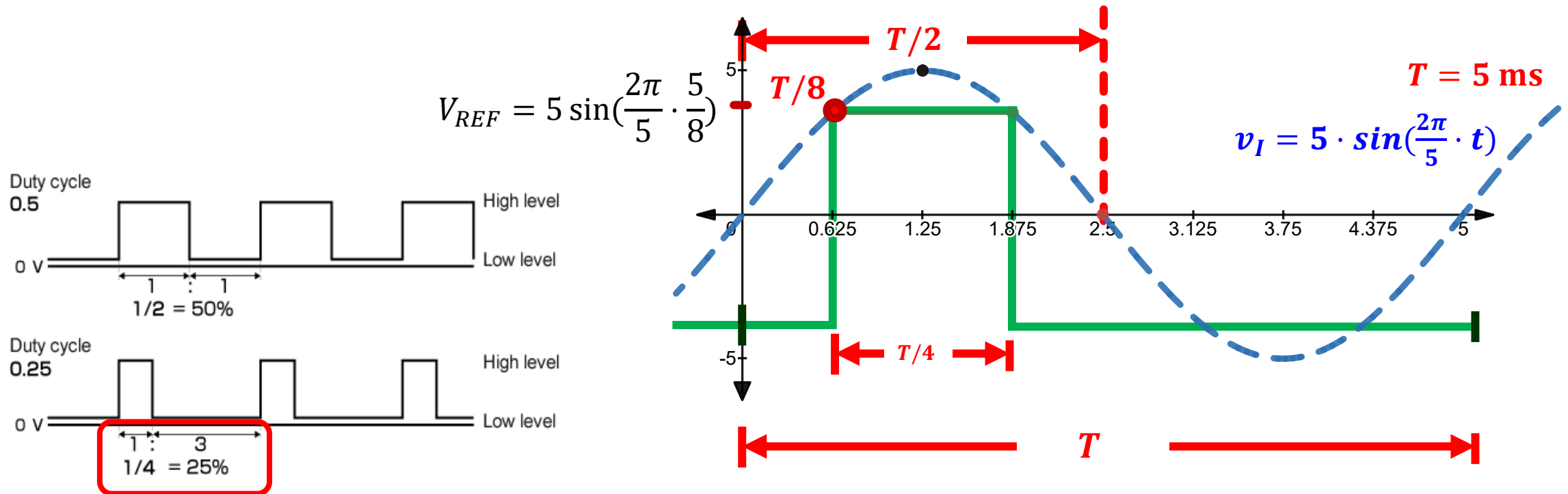

Open Loop Configuration: Example 3

Design an op-amp circuit to transform the sinusoidal voltage, $v_I = 5 \cdot \sin(\frac{2\pi}{5} \cdot t)$ (t is in units of ms , and time-period T is $5\ ms$), to: A square wave with a duty cycle of **25%**.

Solution:

$$V_{REF} = 5 \sin\left(\frac{2\pi}{5} \cdot \frac{5}{8}\right)$$



$$V_{REF} = 5 \cdot \frac{1}{\sqrt{2}}\ V$$

$$V_{REF} = 3.535\ V$$

$v_I \geq 3.535\ V : v_o \rightarrow$ **Positive Saturation**



$v_I \leq 3.535\ V : v_o \rightarrow$ **Negative Saturation**

NON-INVERTING CONFIGURATION

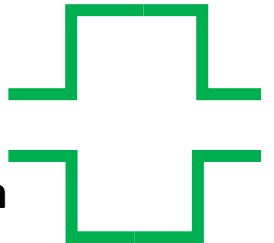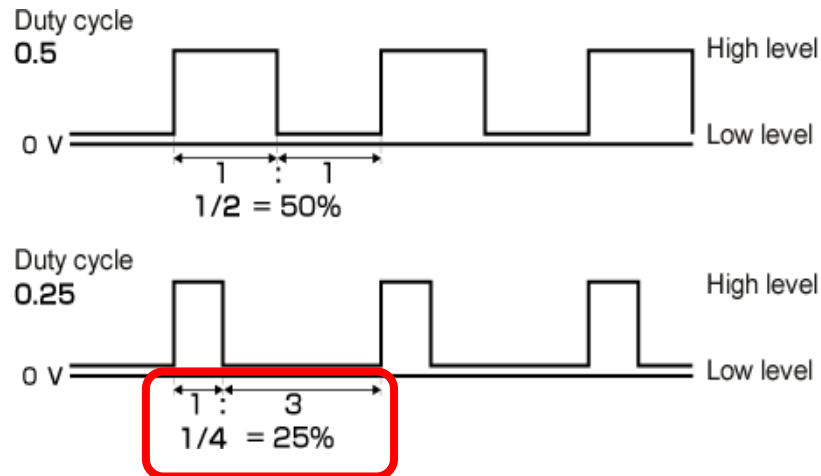

Open Loop Configuration: Example 3

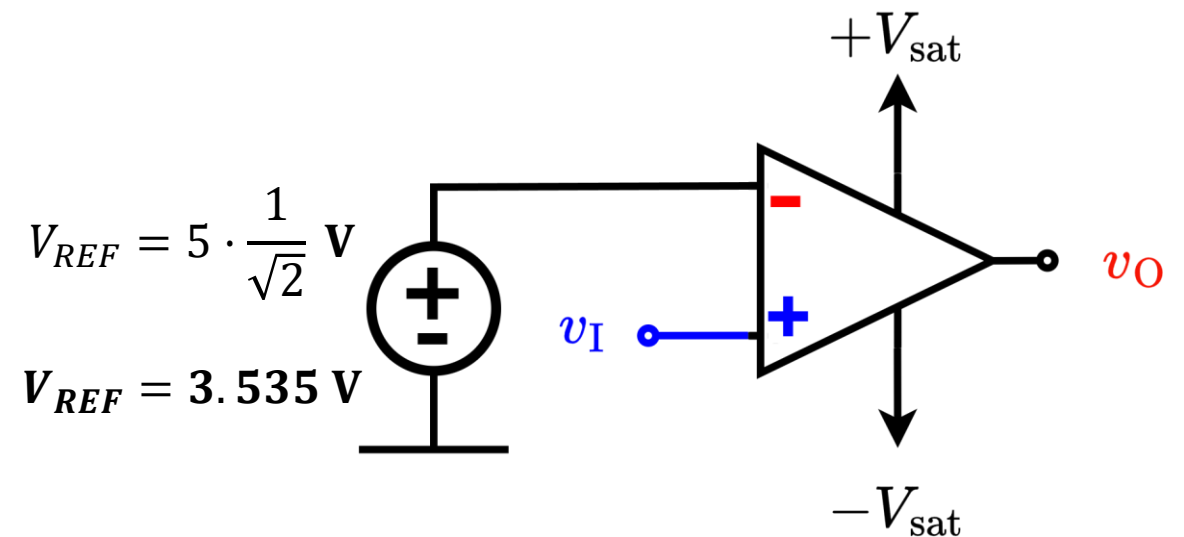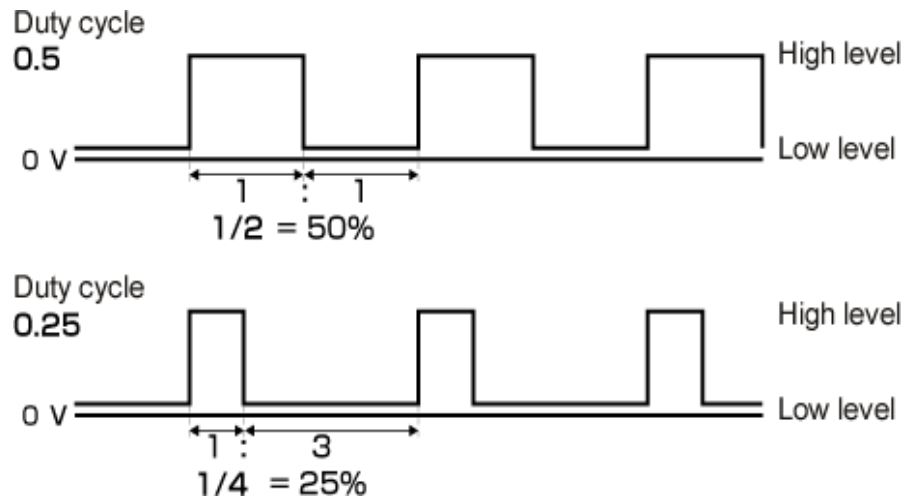Design an op-amp circuit to transform the sinusoidal voltage, $v_I = 5 \cdot \sin\left(\frac{2\pi}{5} \cdot t\right)$ (t is in units of ms , and time-period T is $5\ ms$), to: A square wave with a duty cycle of **25%**.



Part 3 ends here

Outline

- Comparator Application - Smoke Detectors
- Smoke Detector – Operation
- Comparator Application – Automatic AC
- General Principle - Comparator

Comparator Application - Smoke Detectors

Working Principle:

Smoke present → Alarm rings


No smoke present → No Alarm rings.



Since the **alarm** is an electrically driven device, we need some method to convert smoke levels to proportionate voltage.

Smoke levels → Voltage

Comparator Application - Smoke Detectors

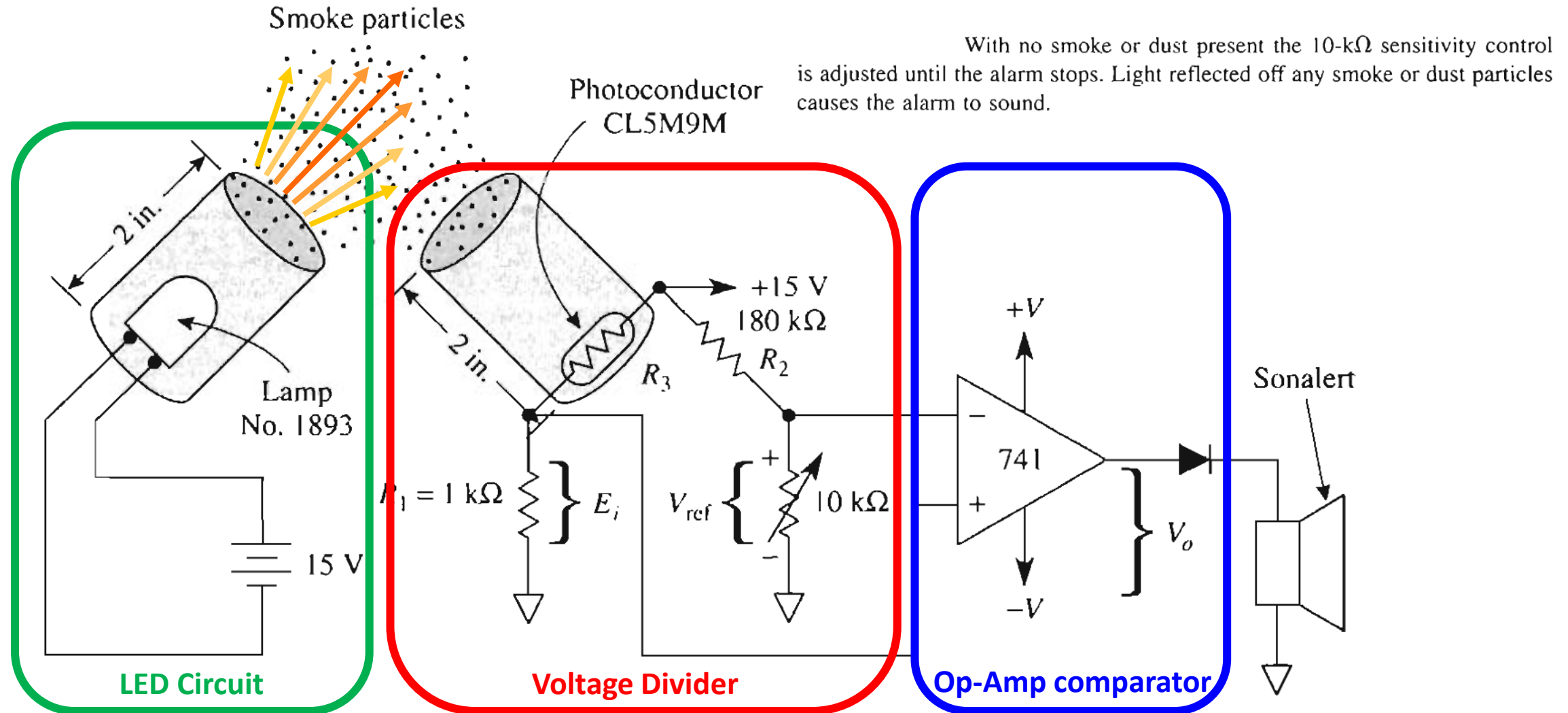

Smoke Detector - Operation

Light from the LED is reflected off the smoke particles on to the photoconductor –


Light Dependent Resistor (LDR).

No Smoke

- No scattering
- Low intensity at LDR (Dark - $I \downarrow$)

Smoke Present

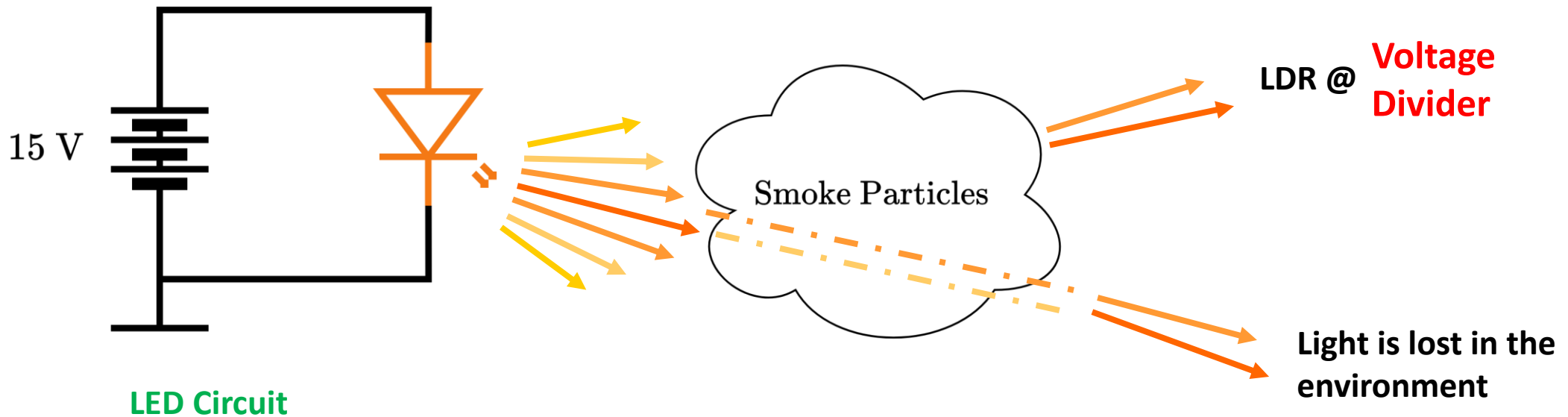- High scattering from smoke particles
- High intensity at LDR (Light - $I \uparrow$)





Smoke Detector - Operation

No Smoke

- No scattering
- Low intensity at LDR (Dark - $I \downarrow$)
- High resistance across LDR ($R_{LDR} \uparrow$)

Smoke Present

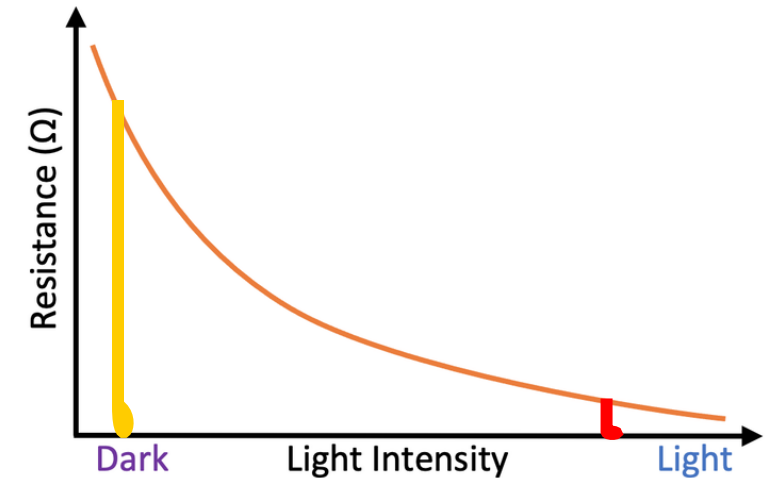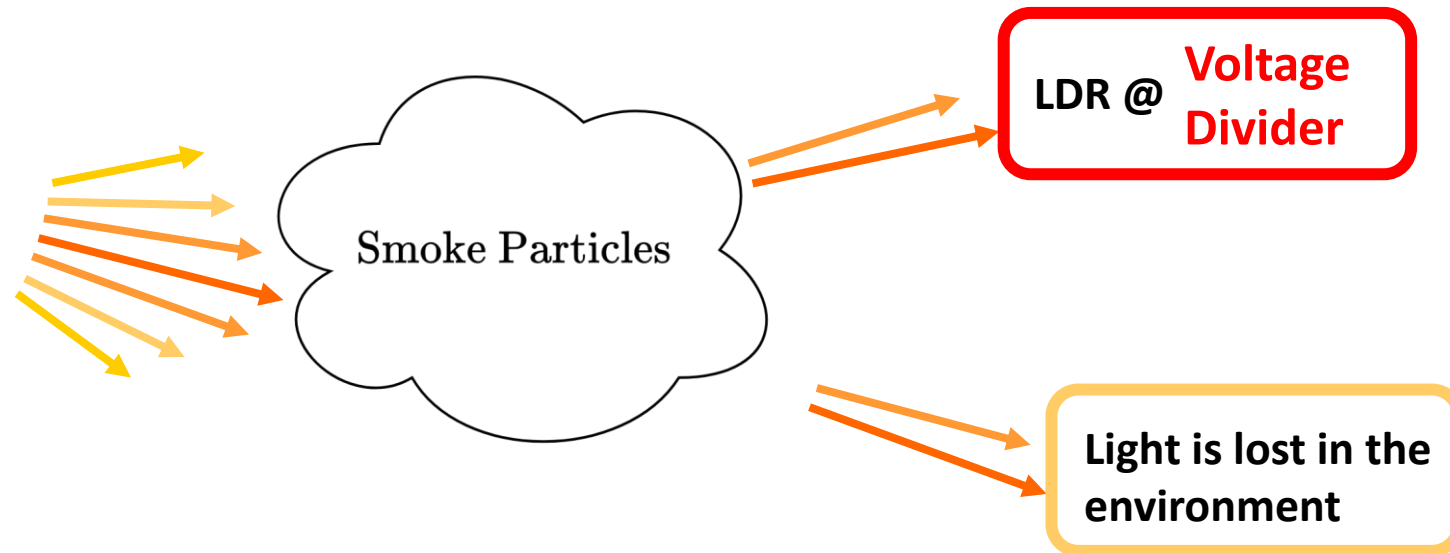
- High scattering from smoke particles
- High intensity at LDR (Light - $I \uparrow$)
- Low resistance across LDR ($R_{LDR} \downarrow$)



Smoke Detector - Operation


No Smoke

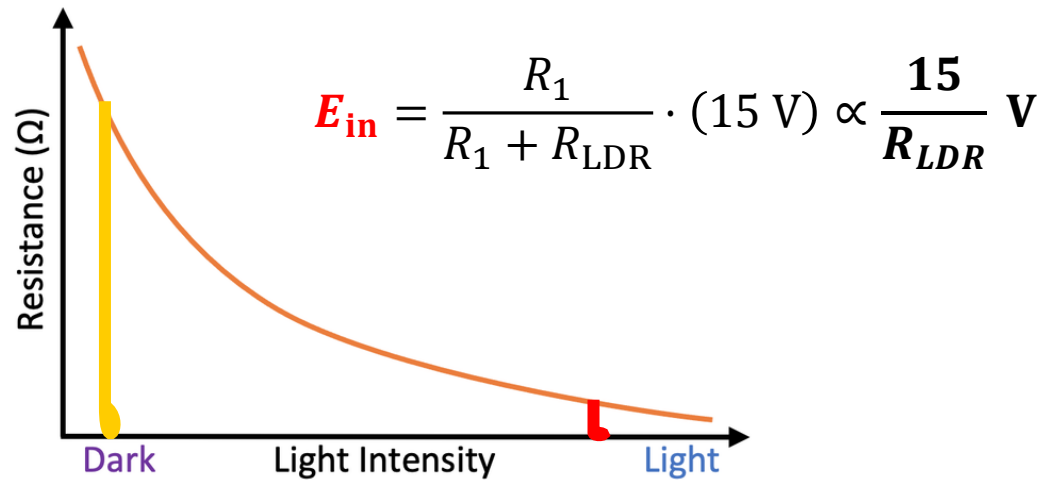- No scattering
- Low intensity at LDR (Dark - $I \downarrow$)
- High resistance across LDR ($R_{LDR} \uparrow$)
- Decrease in E_{in}



Smoke Present

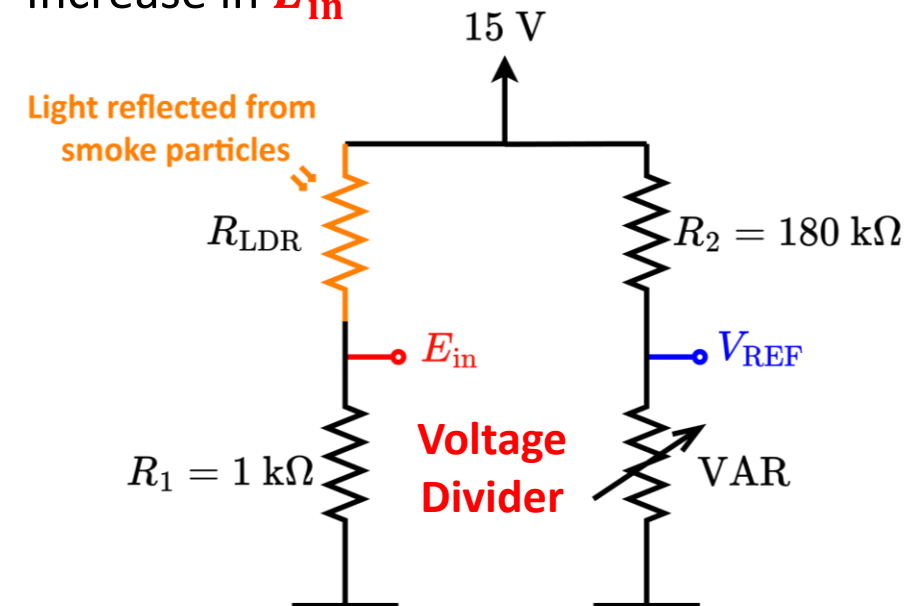- High scattering from smoke particles
- High intensity at LDR (Light - $I \uparrow$)
- Low resistance across LDR ($R_{LDR} \downarrow$)
- Increase in E_{in}




Smoke Detector - Operation

No Smoke


- No scattering
- Low intensity at LDR (Dark - $I \downarrow$)
- High resistance across LDR ($R_{\text{LDR}} \uparrow$)
- Decrease in E_{in}
- Possibility of ($E_{\text{in}} < V_{\text{REF}}$)
- $V_O = -V_{\text{sat}} \rightarrow$ No Alarm

Smoke Present

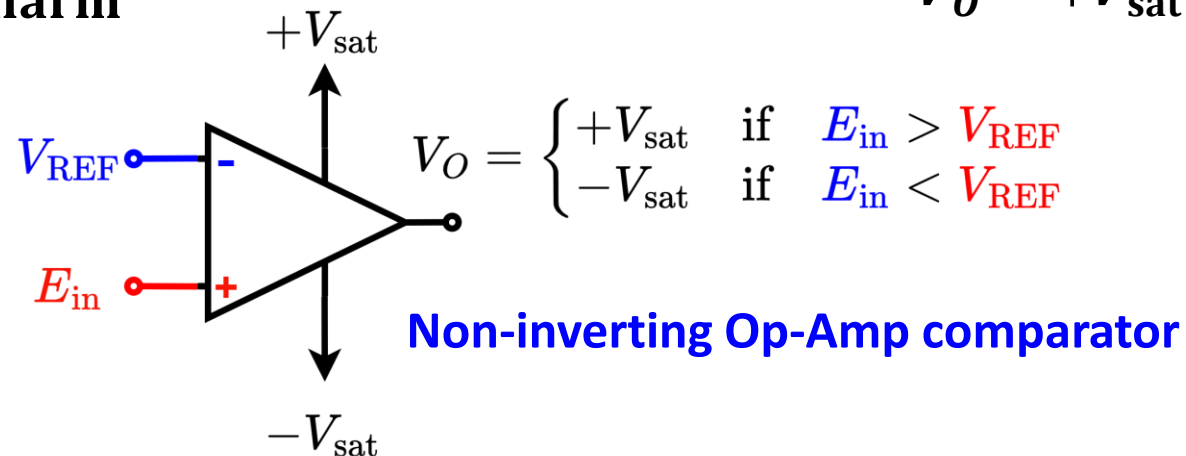
- High scattering from smoke particles
- High intensity at LDR (Light - $I \uparrow$)
- Low resistance across LDR ($R_{\text{LDR}} \downarrow$)
- Increase in E_{in}
- Possibility of ($E_{\text{in}} > V_{\text{REF}}$)
- $V_O = +V_{\text{sat}} \rightarrow$ Alarm Rings!



Smoke Detector - Operation

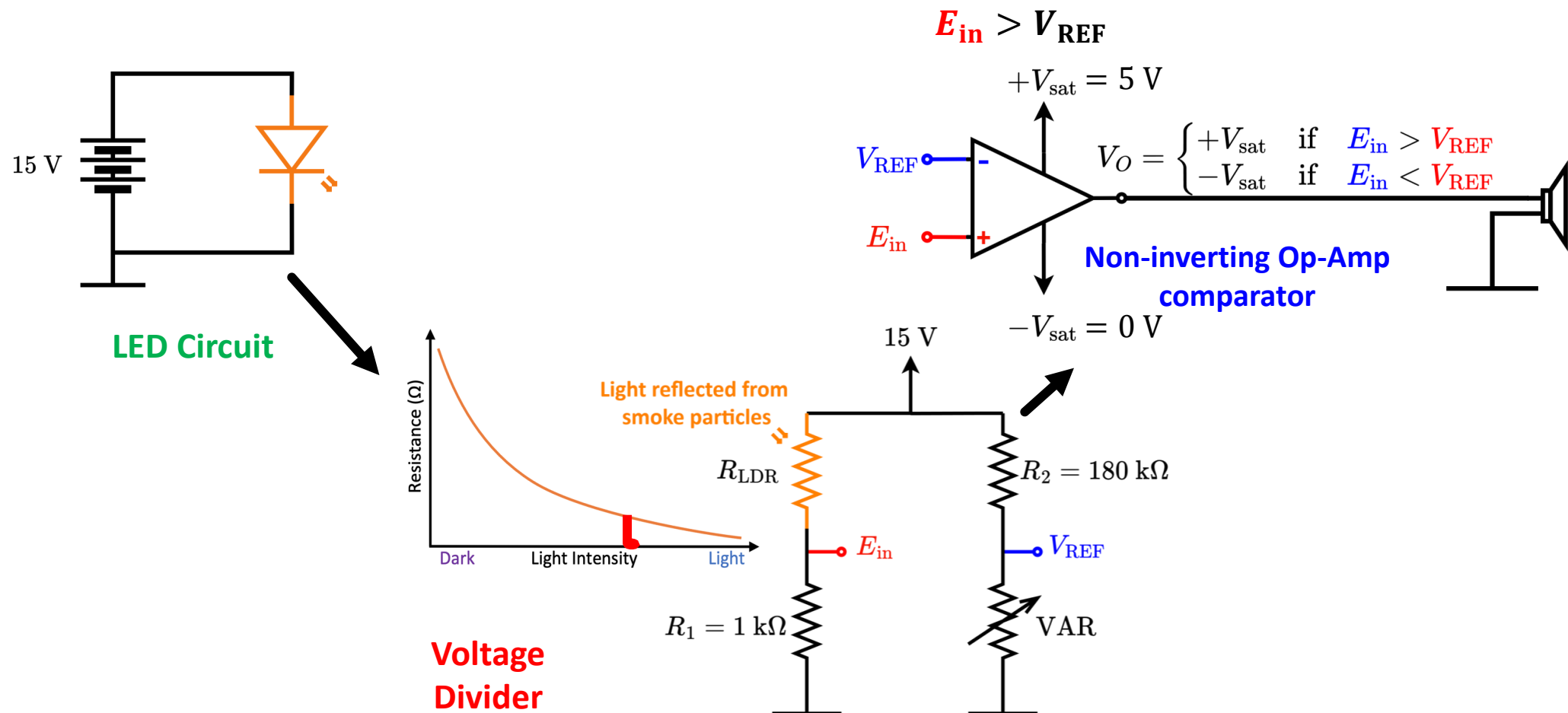


Comparator Application – Automatic AC

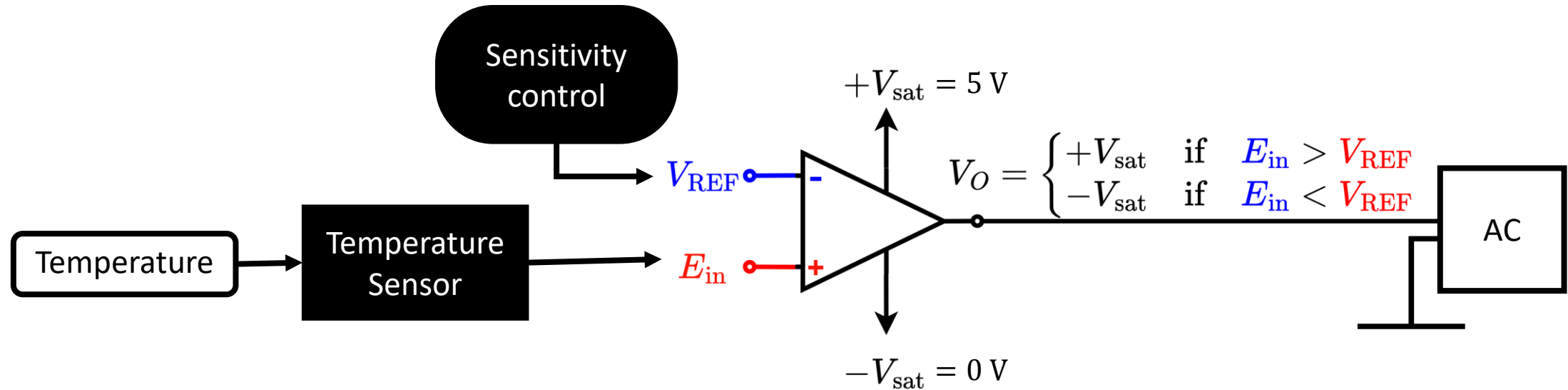

- Comparators can be used to switch on an **AC** based on a **Temperature**.
Temp. \uparrow **AC** - ON
Temp. \downarrow **AC** – OFF – Non-inverting relationship
- The sensitivity of **switching on the AC** is determined by V_{REF}

Summary

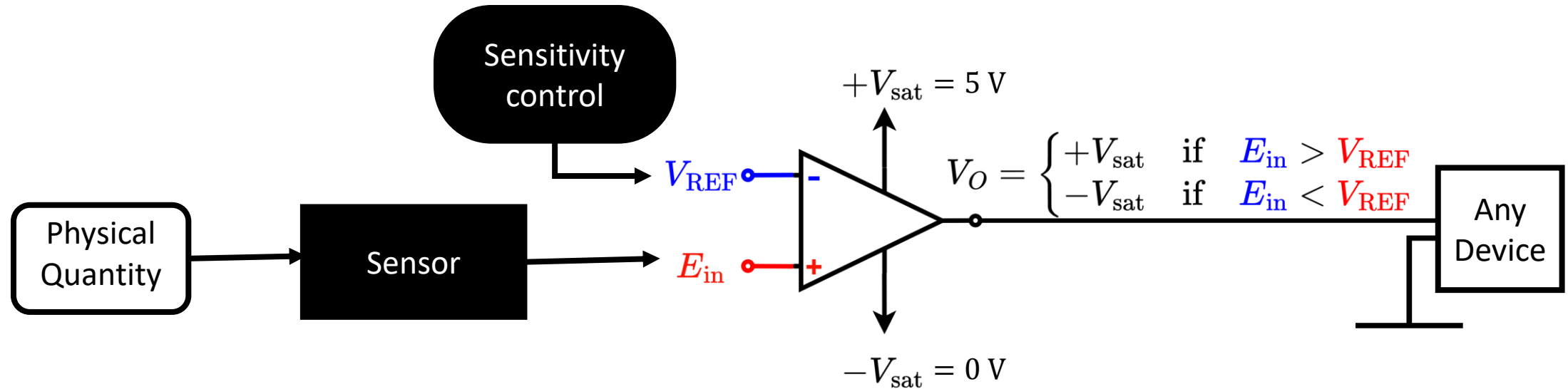

- Comparators can be used to switch on **any device** based on a **physical quantity**.
- The sensitivity of **switching** is determined by V_{REF}

Question: 01

An automatic AC switching system using an Op-Amp comparator that will turn on automatically whenever the temperature is higher than 20° Celsius. The output waveform of an Op-Amp comparator should be between the voltage range of **[-4V 5V]**. The temperature sensor used with the circuit produces a voltage signal of 1.5V for a temperature value of 20° Celsius.

- a) Design and draw the comparator circuit with the required inputs. [3]
- b) Draw the VTC curve for your designed comparator. [2]

Question: 02

Design an **automatic room heater** switching system using an Op-Amp comparator that will turn on automatically whenever the temperature is lower than **20° Celsius**. The output waveform of the comparator should be between the voltage range of **[-4V 5V]**. The temperature sensor produces a voltage signal of **2.5V** for a temperature value of **20° Celsius**.

- a) Design and draw the comparator circuit with the required inputs. [3]
- b) Draw the VTC curve for your designed comparator. [2]

Question: 03

An automated **smoke detector** system using an Op-Amp comparator that will turn on automatically whenever the particle density in the air is higher than $2.5 \times 10^{26} \text{ m}^{-3}$. The output waveform of an Op-Amp comparator should be between the voltage range of $[-6\text{V } 6\text{V}]$. The smoke particle sensor used with the circuit produces a voltage signal of 2.0V for a particle density of $2.5 \times 10^{26} \text{ m}^{-3}$.

- a) **Design** and **draw** the comparator circuit with the required inputs. [3]
- b) **Draw** the VTC curve for your designed comparator. [2]

Question: 04

Farhan, CEO of Rajshahi WASA, is building a water level indicator for an overhead tank. For this, he placed three sensors at three different levels of the tank. The voltage outputs of the three sensors are denoted as V_1 (lowest level), V_2 (mid-level), and V_3 (highest level). Farhan decided that the indicator for the water level would be,

$$V_{\text{indicator}} = \frac{1}{k} (V_1 + V_2 + V_3)$$

- (a) Assuming $k = 1$, **design** the circuit using op amps that will take V_1 , V_2 , and V_3 as *input* and will produce $V_{\text{indicator}}$ as *output*. [3]

Upon further experimentation, Farhan realized that the maximum values of V_1 , V_2 , and V_3 are 5 V . Hence, the maximum value of $V_1 + V_2 + V_3$ can be 15 V . However, Farhan only has access to $+5 \text{ V}$ and -5 V as power supplies, meaning that the $V_{\text{indicator}}$ cannot be greater than $+5 \text{ V}$ or less than -5 V .

- (b) **Choose** a value of k such that the maximum value of $V_{\text{indicator}}$ is within the given range. [1]
- (c) **Design** the circuit in part (a) again using this new value of k . [2]

Question: 05


Figure 1 shows the variation of direct solar irradiance, G (in units of kW/m^2) throughout the day in Greece. The irradiance is $0.25 \text{ kW}/\text{m}^2$ at **7:00 hours**. A photodetector generates a voltage of V_S by converting solar irradiance G (in units of kW/m^2) according to the following equation:

$$V_S(G) = 4G^2 + 9G \quad (1)$$

You have to design an automatic system with an Op-Amp comparator circuit. This system will take V_S as an input from a photodetector and control a street fan, ensuring it meets the following conditions:

- The fan has to switch ON after **7:00 hours**.
- The fan switches ON when system output is **5 V**.
- The fan switches OFF when system output is **0 V**.

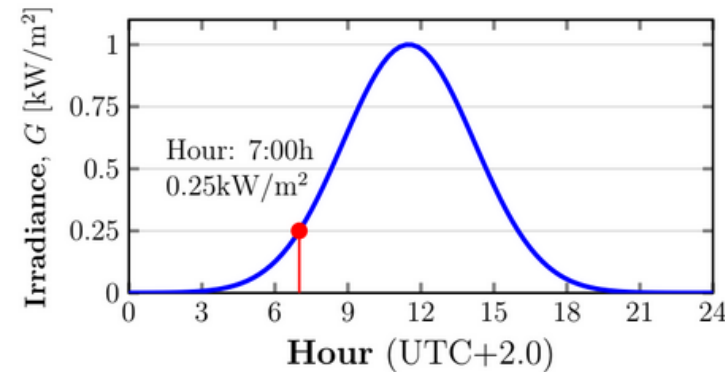Based on the above scenario, answer the following questions:



a. Calculate the photodetector voltage V_S **at 7:00 hours**. **Determine** how V_S changes before and after 7:00 hours. (2 marks)


b. Determine whether the Op-Amp comparator circuit of the system should be in an **inverting or non-inverting** configuration. **Justify** your choice by explaining briefly how this configuration meets the conditions mentioned above. (3 marks)

c. Draw the completed Op-Amp comparator circuit marking the input and output terminals and the positive and negative saturation voltages. Also clearly **indicate the reference voltage** against which the input of the comparator is compared. (5 marks)

Op-Amp: Circuit Modelling

Voltage controlled voltage Source


“Ideal” op-amp approximation

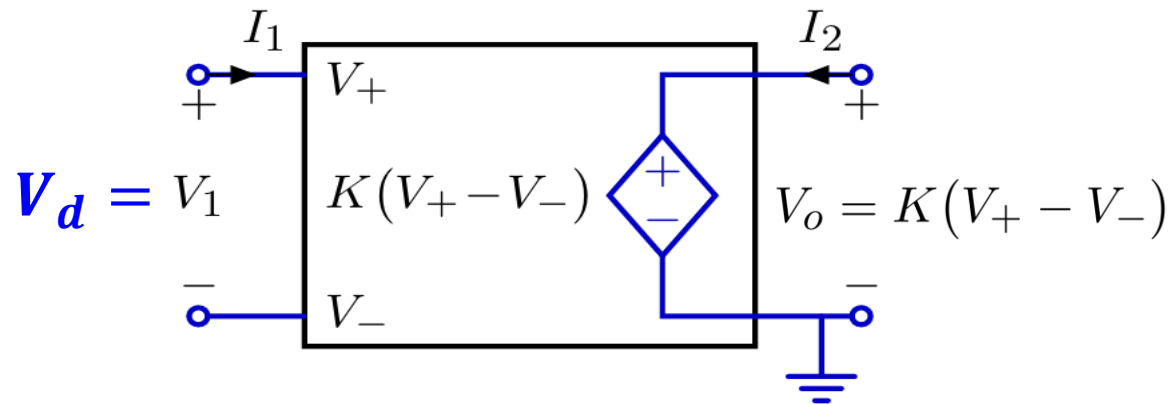

$$V_{(+)} \approx V_{(-)}$$

$$I_1 \approx 0$$

“Non-Ideal” op-amp approximation

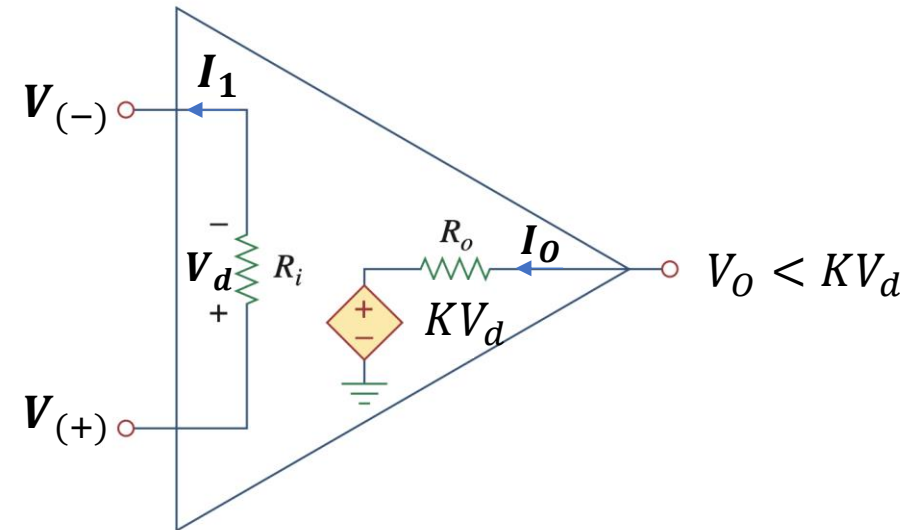


$$V_d = V_{(+)} - V_{(-)} \neq 0$$

$$I_1 > 0$$

Op-amp Model parameters

- **Input resistance:** R_i
- **Output resistance:** R_o
- **Voltage (Differential/OL) Gain:** A/A_{OL} or K
- **Positive Saturation Voltage:** $+V/V_{CC}/V_{sat}$
- **Negative Saturation Voltage:** $-V/V_{EE}/-V_{sat}$

Parameter	Typical Range	Ideally
A or K	$10^4 - 10^8$	∞
R_i	$100\text{ k}\Omega - 10^{10}\text{ k}\Omega$	∞
R_o	$0.01\text{ k}\Omega - 0.1\text{ k}\Omega$	0

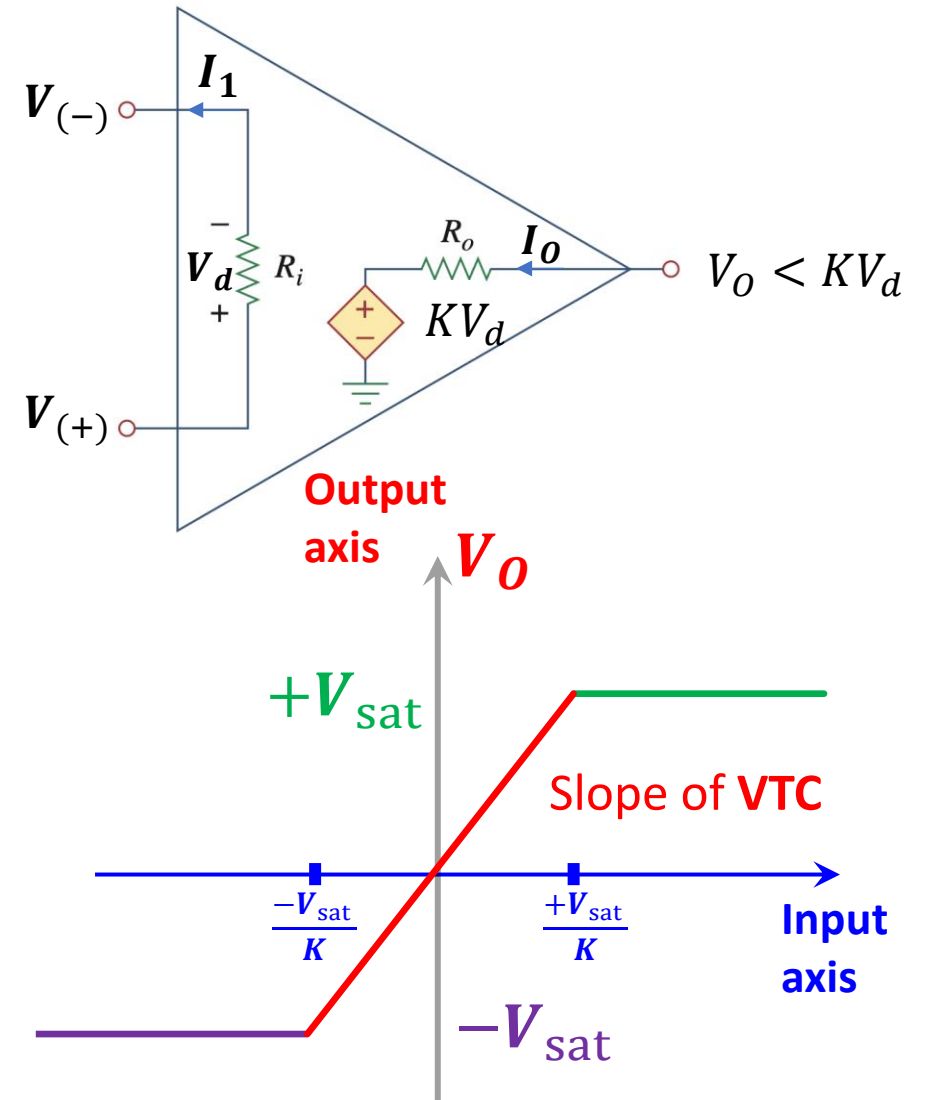

Practice Problem – op-amp


Find i_F and v_o .

Here,

$$R_i = 200 \text{ k}\Omega$$

$$R_o = 0.1 \text{ k}\Omega$$

$$A = 2 \times 10^5$$

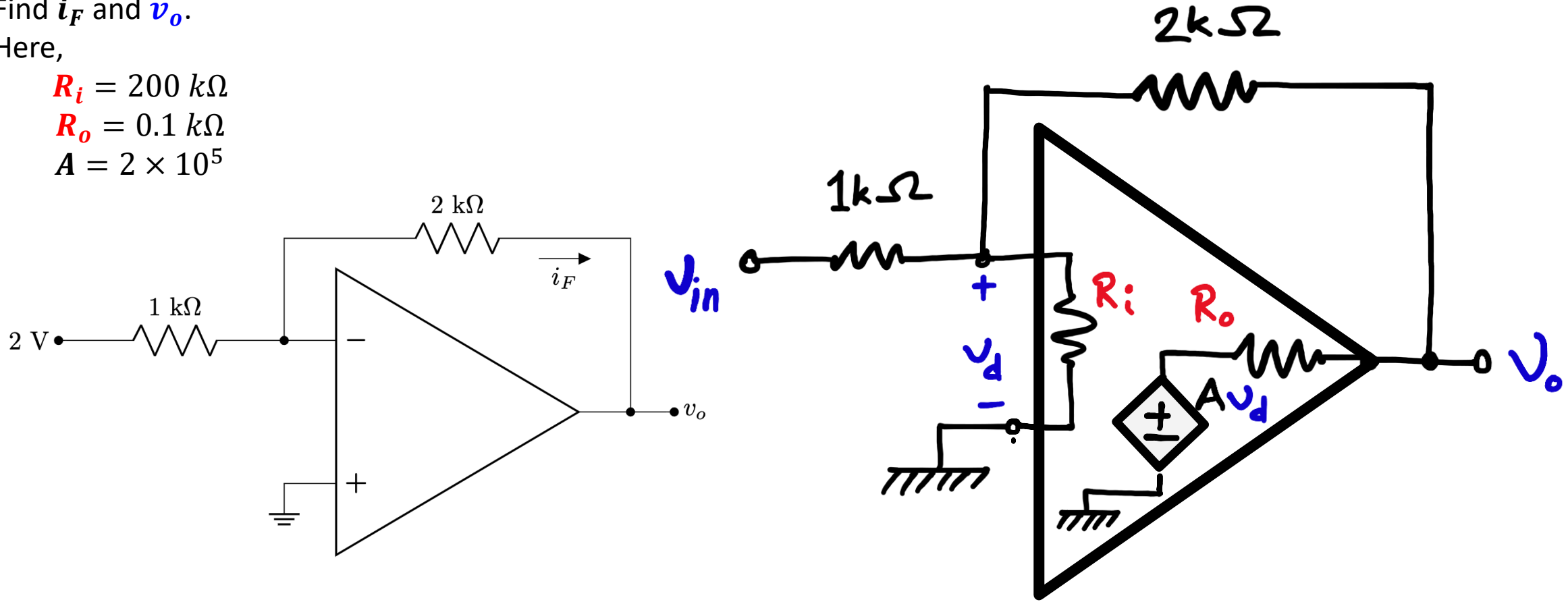

Practice Problem – op-amp


Find i_F and v_o .

Here,

$$R_i = 200 \text{ k}\Omega$$

$$R_o = 0.1 \text{ k}\Omega$$

$$A = 2 \times 10^5$$

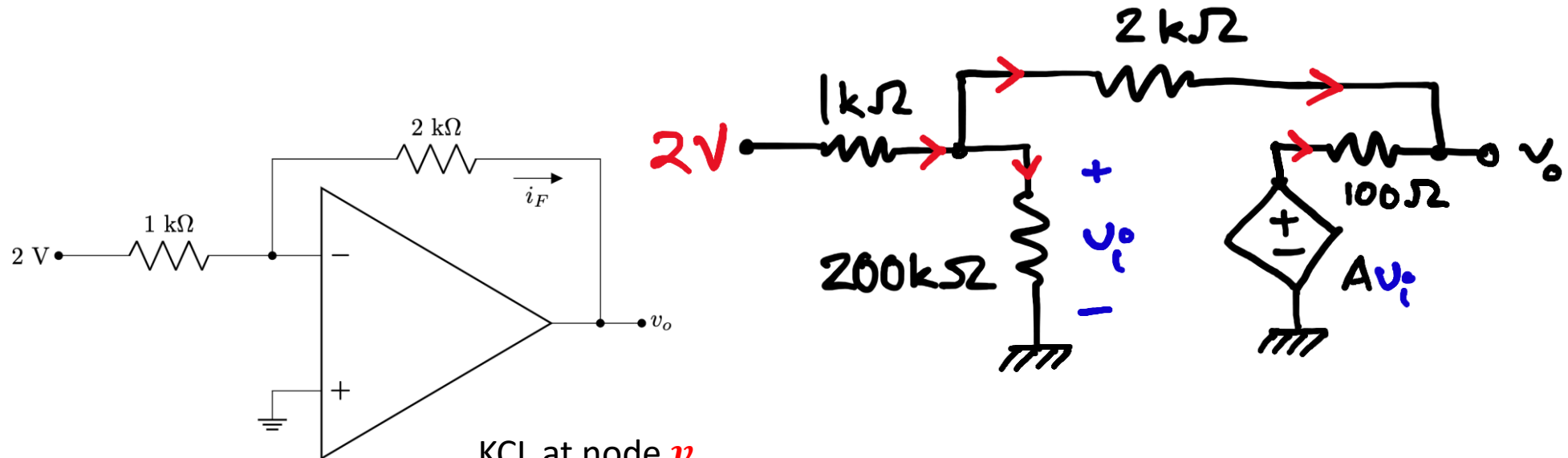

KCL at node v_i

$$\frac{2 - v_i}{1} = \frac{v_i - v_o}{2} + \frac{v_i}{200}$$

$$\frac{301}{200} v_i - \frac{1}{2} v_o = 2$$

KCL at node v_o

$$\frac{v_i - v_o}{2} + \frac{Av_i - v_o}{0.1} = 0$$

$$(2 \times 10^6 + 0.5)v_i - 10.5v_o = 0$$

$$\begin{aligned} v_i &= -21 \mu\text{V} \\ v_o &= -3.999 \text{ V} \\ i_F &= 2 \text{ mA} \end{aligned}$$

Some circuits with OP-AMP



Find i_F and v_o .

Here,

$$R_i = 200 \text{ k}\Omega$$

$$R_o = 0.1 \text{ k}\Omega$$


$$A = 2 \times 10^5$$

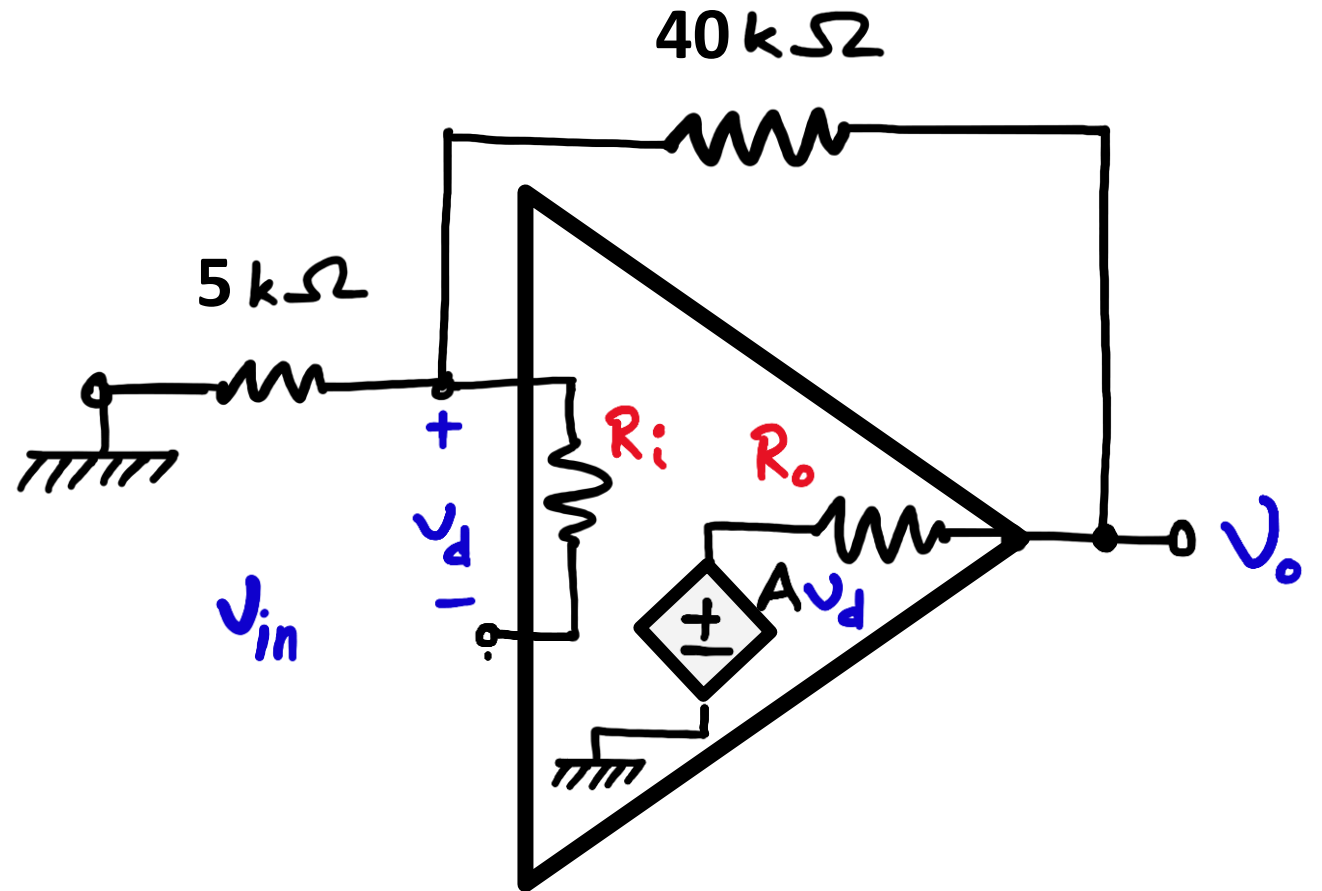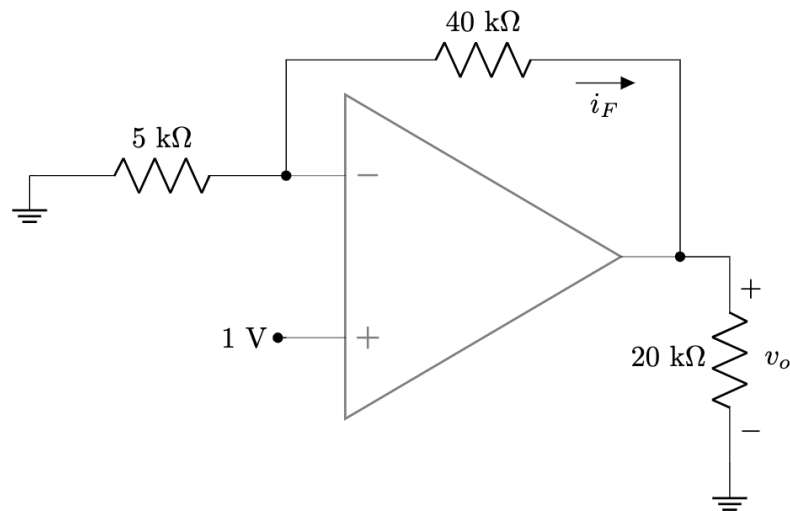

Part 5 ends here

Closed Loop Configuration

Feedback

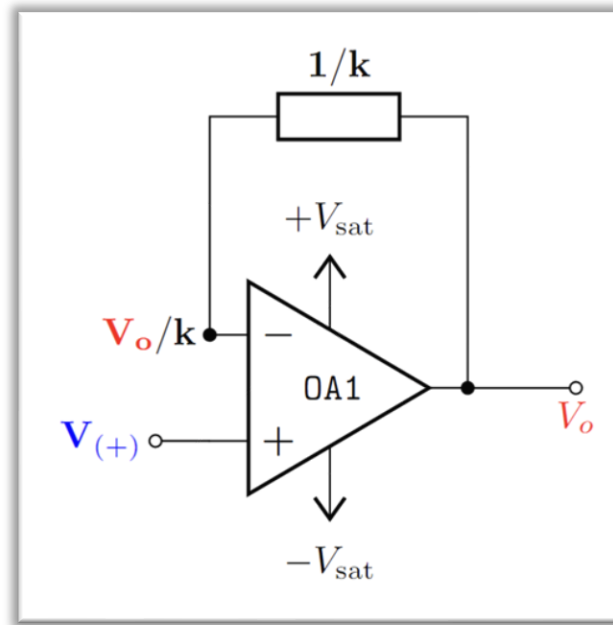

Outline

- Feedback in Op-Amp circuit
- Negative Feedback
- Open Loop VS Closed Loop Gain
- Closed Loop Configuration

Feedback in Op-Amp circuit

Two types of feedback

1. Negative Feedback:

Output voltage is fed to the inputs **negatively**

The output voltage is connected to the **inverting** terminal



$$V_o \uparrow \Rightarrow \frac{V_o}{k} \uparrow \Rightarrow V_{(-)} \uparrow \Rightarrow V_d \downarrow = V_{(+)} - V_{(-)} \uparrow \Rightarrow V_o \propto V_d \downarrow$$

2. Positive Feedback:

Output voltage is fed to the inputs **positively**

The output voltage is connected to the **non-inverting** terminal
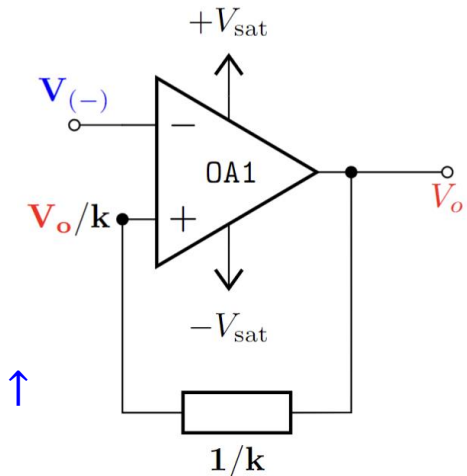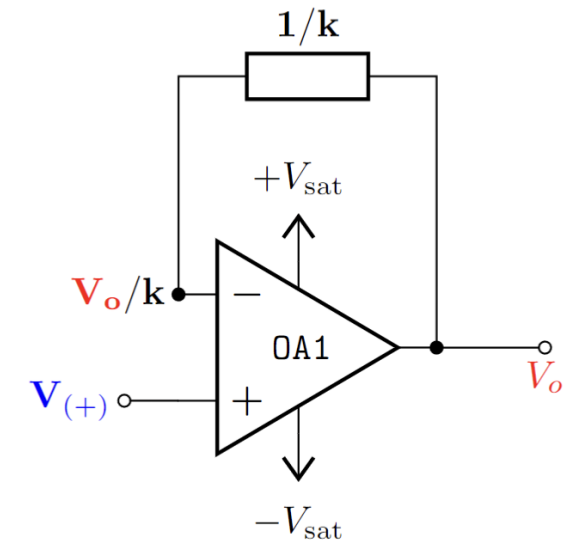
$$V_o \uparrow \Rightarrow \frac{V_o}{k} \uparrow \Rightarrow V_{(+)} \uparrow \Rightarrow V_d \uparrow = V_{(+)} \uparrow - V_{(-)} \Rightarrow V_o \propto V_d \uparrow$$



Feedback in Op-Amp circuit

Two types of feedback

1. Negative Feedback:

Output voltage is fed to the inputs **negatively**

The output voltage is connected to the **inverting** terminal



$$V_o \uparrow \Rightarrow V_o \propto V_d \downarrow$$

2. Positive Feedback:

Output voltage is fed to the inputs **positively**

The output voltage is connected to the **non-inverting** terminal
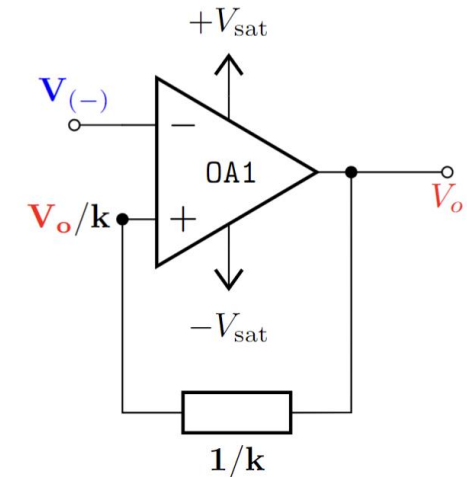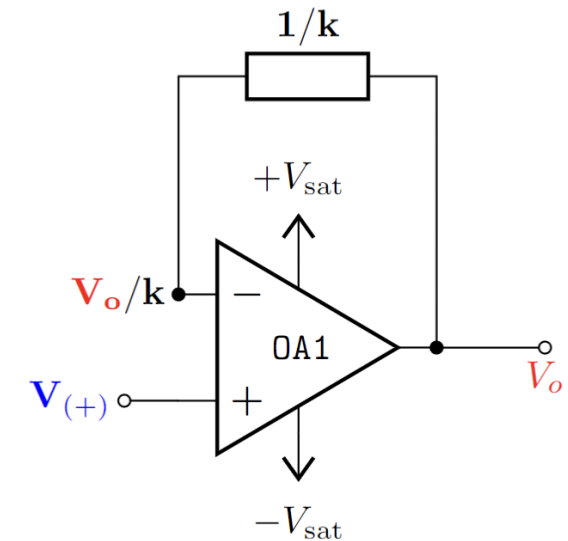
$$V_o \uparrow \Rightarrow V_o \propto V_d \uparrow$$



Negative Feedback in Op-Amp circuit

Negative Feedback:

Output voltage is fed to the inputs **negatively**

The **output voltage** is connected to the **inverting** terminal

$$\text{Here, } V_{(-)} = \frac{V_o}{k}$$

$$\text{We know, } V_o = A V_d$$

$$V_o = A(V_{(+)} - V_{(-)})$$

$$= A\left(V_{(+)} - \frac{V_o}{k}\right)$$


$$= A V_{(+)} - \frac{A}{k} V_o$$

$$\Rightarrow V_o \left(1 + \frac{A}{k}\right) = A V_{(+)}$$

$$\frac{V_o}{V_{(+)}} = \frac{A}{1 + \frac{A}{k}} = \frac{1}{\frac{1}{A} + \frac{1}{k}}$$


$$\text{If } A \rightarrow \infty \text{ then } \frac{1}{A} \rightarrow 0.$$
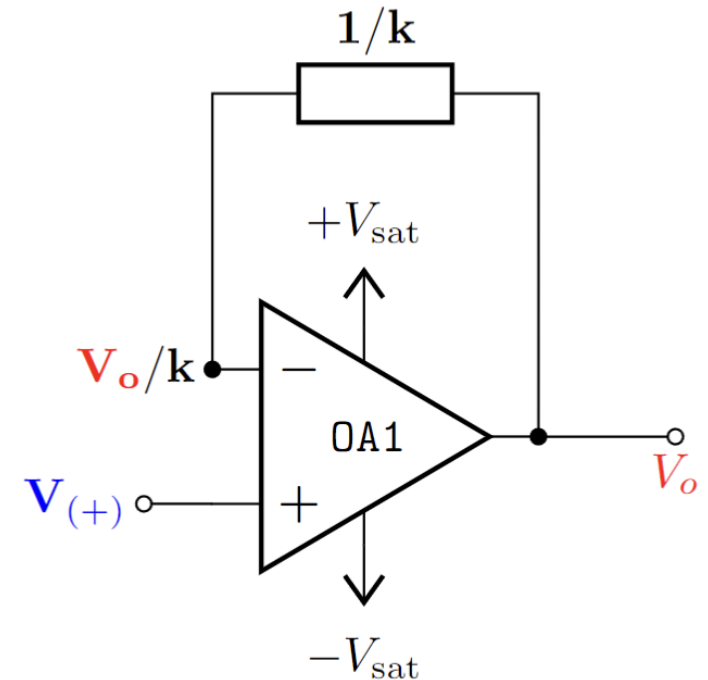
$$\therefore \frac{V_o}{V_{(+)}} = k \quad \text{This is the new amplification factor / Gain}$$



Open Loop Gain VS Closed Loop Gain

Open Loop (OL) Configuration

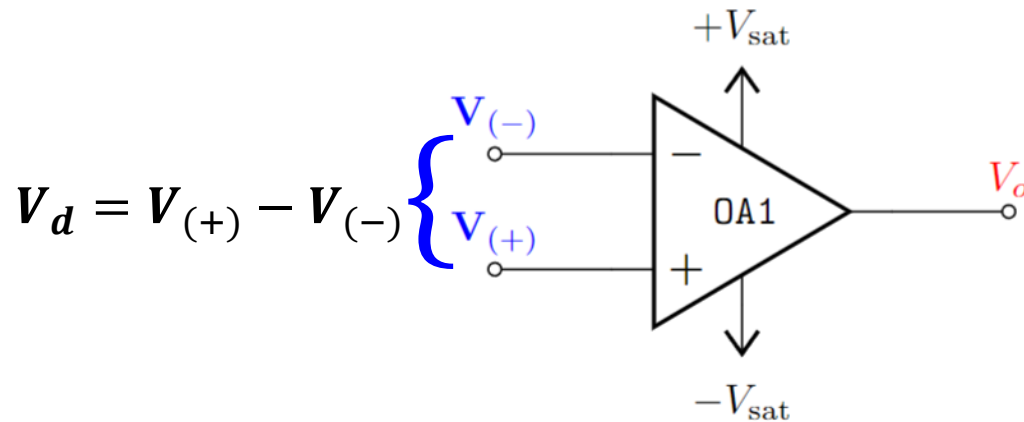


Input Voltage: V_d
Output Voltage: V_o

\therefore Voltage Gain: $\frac{V_o}{V_d} = A \text{ or } K$

OL Gain	CL Gain
$A \text{ or } K \sim 10^5$	$k \ll A$ $k < 100$

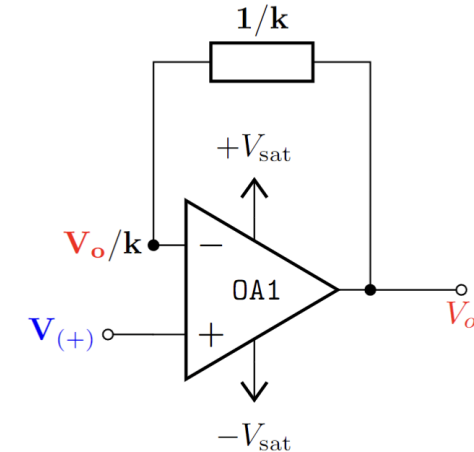With “Negative Feedback”: Closed Loop (CL) Configuration




Input Voltage: $V_{(+)}$
Output Voltage: V_o


\therefore Voltage Gain: $\frac{V_o}{V_{(+)}} = k$

Open Loop Gain VS Closed Loop Gain

Open Loop (OL) Configuration

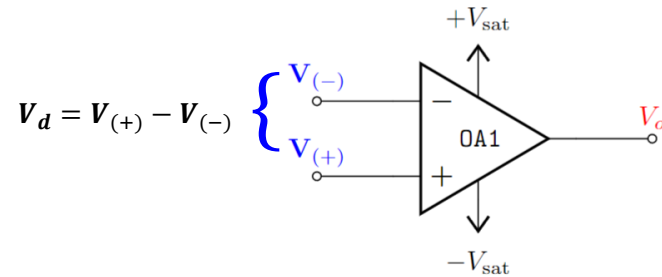

Closed Loop (CL) Configuration

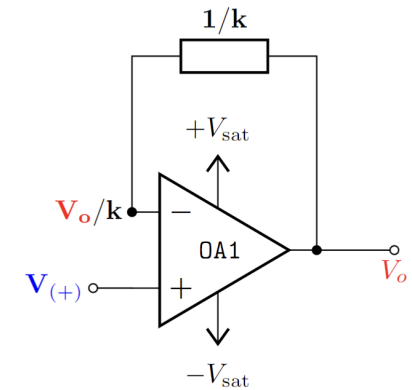


OL Gain	CL Gain
$\frac{V_o}{V_d} = A \text{ or } K \sim 10^5$	$\frac{V_o}{V_{(+)}} = k \ll A$ $k < 100$
Can't be controlled	Can be controlled by the feedback element
Used as " Comparator "	Used as " Linear Amplifier "

Negative Feedback in Op-Amp circuit


The **output voltage** is transformed in the following way:

$$V_{(-)} = \frac{1}{k} \cdot V_o$$

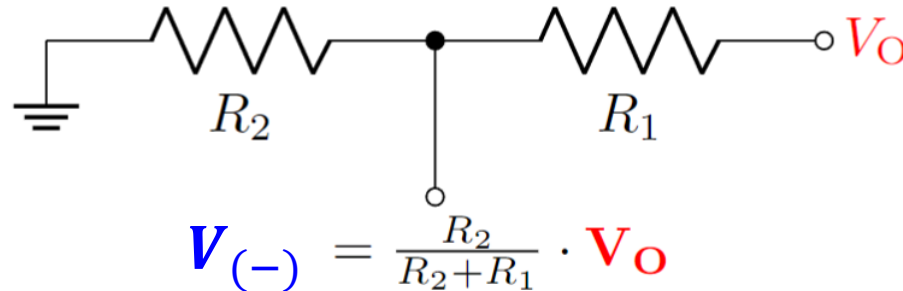This factor of $1/k$ can be achieved with a voltage divider network.




$$\frac{1}{k} = \frac{R_2}{R_1 + R_2}$$

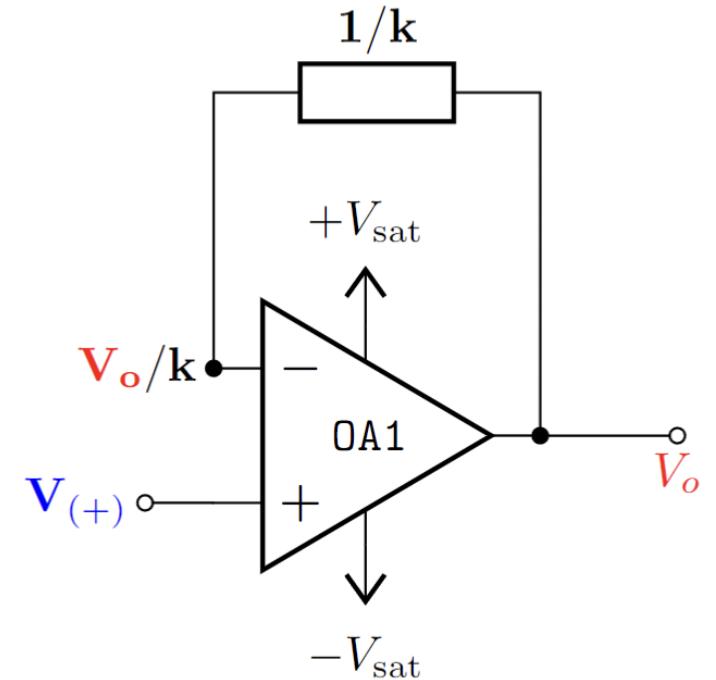

A voltage divider can act as a multiplier/factor in the **feedback** branch

Negative Feedback in Op-Amp circuit

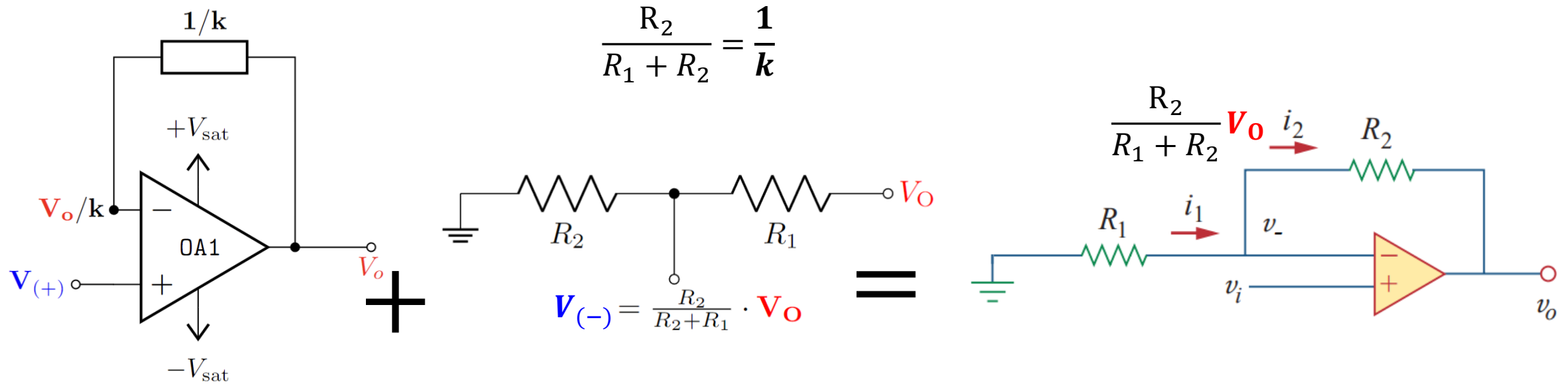
A voltage divider can act as a multiplier/factor in the **feedback** branch




If $k = 10$ (meaning we feed back one tenth of the output to negative input), we will get $v_o = 10 \cdot v_i$. that is 10-fold gain.

Solving Closed Loop Op-Amp Circuit

- For ideal op-amp
 - Infinite input resistance, $R_i = \infty = \text{open circuit}$
 - Zero output resistance, $R_o = 0 = \text{short circuit}$
 - $i_i = 0$ and $i_+ = 0$
- **When there is negative feedback**, for an ideal op-amp, " A " is infinitely high. Thus, for a finite output voltage v_o , $\frac{v_o}{A} = v_d \rightarrow 0 \Rightarrow v_+ = v_-$. This is called **virtual short circuit**
- Because of these, solving ideal op-amp circuit with negative feedback is very simple

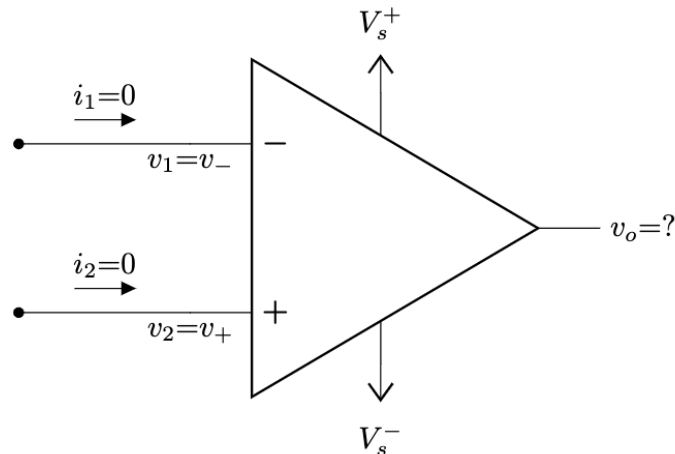

Solving Closed Loop Op-Amp Circuit

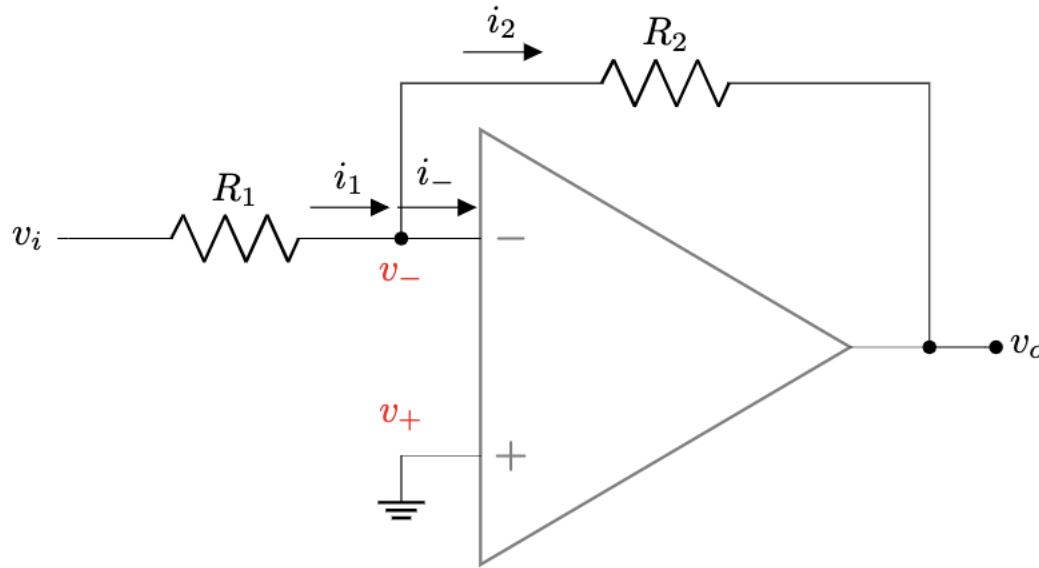

$$\text{Gain} = \frac{v_o}{v_i} = -\frac{R_2}{R_1}$$

Since v_+ is connected to ground, $v_+ = 0 \text{ V}$

Since there is negative feedback, from virtual short, $v_- = v_+ = 0 \text{ V}$

From Ohm's law for $R_1 \Rightarrow i_1 = \frac{v_i - 0}{R_1} = \frac{v_i}{R_1}$

Since ideal op-amp, $i_- = i_+ = 0$

From KCL at v_- , $i_1 = i_- + i_2 \Rightarrow i_1 = i_2 = v_i/R_1$

From Ohm's law for $R_2 \Rightarrow i_2 = \frac{v_- - v_o}{R_2} = \frac{v_i}{R_1} \Rightarrow v_o = -i_2 \times R_2 \Rightarrow v_o = -\frac{R_2}{R_1} v_i$ [ANS]