

Assignment 3  
CSE251  
Summer-25  
Total Marks: 100


1. The input of a full-wave rectifier is a cosine voltage with peak  $V_M = 5$  V and frequency 60 Hz, and output load resistance is  $R = 2$  k $\Omega$ . Silicon diodes are used in this circuit for which the forward drop is  $V_{D0} = 0.7$  V.
  - (a) Briefly explain the purpose of a rectifier and describe its operation.
  - (b) Show the input and output waveforms.
  - (c) Calculate the DC value of the output voltage. Now after connecting a capacitor in parallel with the load, the output becomes a ripple voltage  **$V_{out} = V_{DC} \pm 0.2$  V**
  - (d) Calculate the **peak-to-peak ripple voltage**, and from that, the value of the capacitor.
  - (e) Calculate the average of the output voltage  $V_{DC}$  after connecting the capacitor. Compare this with the DC value determined in 'c' and comment on the difference between these two.
  
2. The input of a **Half-wave rectifier** is a sine voltage with peak  $V_M = 10$  V and frequency 55 Hz, and output load resistance is  $R = 2.5$  k $\Omega$ . Silicon diodes are used in this circuit for which the forward drop is  $V_{D0} = 0.4$  V.
  - (a) Calculate the DC value of the output voltage.  
Now after connecting a capacitor in parallel with the load, the output becomes a ripple voltage  **$V_{out} = V_{DC} \pm 0.3$  V.**
  - (b) Calculate the **peak-to-peak ripple voltage**, and from that, the value of the capacitor.
  - (c) Draw the **Voltage Transfer Characteristic (VTC) curve**
  
3. The input of a full-wave rectifier is expressed by,  $V_s(t) = 7\sin(400\pi t)$ , and output load resistance is  $R = 5$  k $\Omega$ . Silicon diodes are used in this circuit for which the forward drop is  $V_{D0} = 0.3$  V.
  - (a) Calculate the input and output wave frequency.
  - (b) Show the input and output waveforms.

Now after connecting a capacitor,  $C = 100$   $\mu$ F in parallel with the load.

  - (c) Calculate the peak-to-peak ripple voltage,
  - (d) How can you provide better filtering for the output waves?
  - (e) What is the frequency of the Ripple voltage?
  
4. The input of a **Half-wave rectifier** is a **Square** wave voltage with peak  $V_M = 15$  V and frequency 0.5 Hz, and output load resistance is  $R = 5$  k $\Omega$ . Silicon diodes are used in this circuit for which the forward drop is  $V_{D0} = 0.7$  V.
  - i. Show the input and output waveforms.
  - ii. Draw the VTC curve

Assignment 3  
CSE251  
Summer-25  
Total Marks: 100

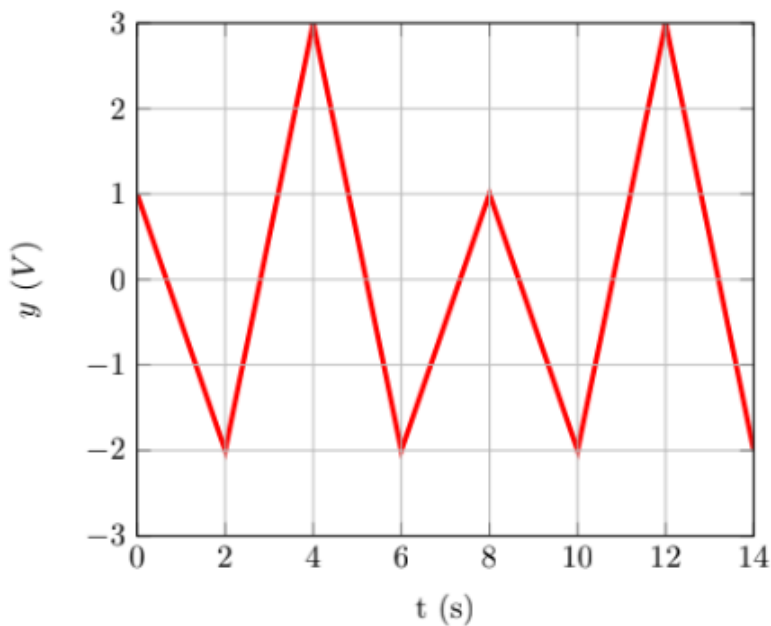5. The input of a **full-wave rectifier** is a **Square** wave voltage with peak  $V_M = 15$  V and frequency 0.5 Hz, and output load resistance is  $R = 5$  k $\Omega$ . Silicon diodes are used in this circuit for which the forward drop is  $V_{D0} = 0.7$  V.
- Show the input and output waveforms.
  - Draw the VTC curve
- 6.




(b) Input of the FW rectifier

**Part 2:** A voltage waveform  $V_i = 15 \sin(2000\pi t)$  V is fed into a Half-wave rectifier with a load resistance  $R = 5$  k $\Omega$ . Silicon diodes are used in this circuit for which the forward drop is  $V_{D0} = 0.7$  V.

- Illustrate** the input and output waveforms in separate graphs. Label the graph and **indicate** the voltage levels properly. [2]
- Calculate** the DC/Average value of the output. [1]
- A capacitor is now added to reduce the fluctuation of the output voltage, which makes the peak to peak ripple voltage 4% of the maximum output voltage  $V_P$ . **Deduce** is the value of the capacitor from the given data. [2]
- The input of a Full-wave rectifier is shown in Figure 1(b) above and output load resistance is  $R = 10$  k $\Omega$ . Germanium diodes are used in this circuit for which the forward drop is  $V_{D0} = 0.3$  V. **Show** the input and output waveforms [1]

Assignment 3  
CSE251  
Summer-25  
Total Marks: 100


7.

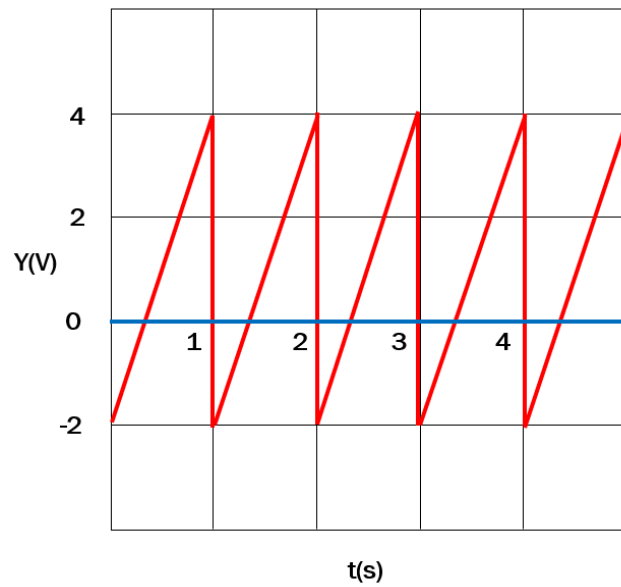

The input of a **Half-wave rectifier** is exhibited in the Figure above and output load resistance is  $R = 5 \text{ k}\Omega$ . Silicon diodes are used in this circuit for which the forward drop is  $V_{D0} = 0.7 \text{ V}$ .

- Show the input and output waveforms.
- Draw the VTC curve
- Calculate input and output frequency

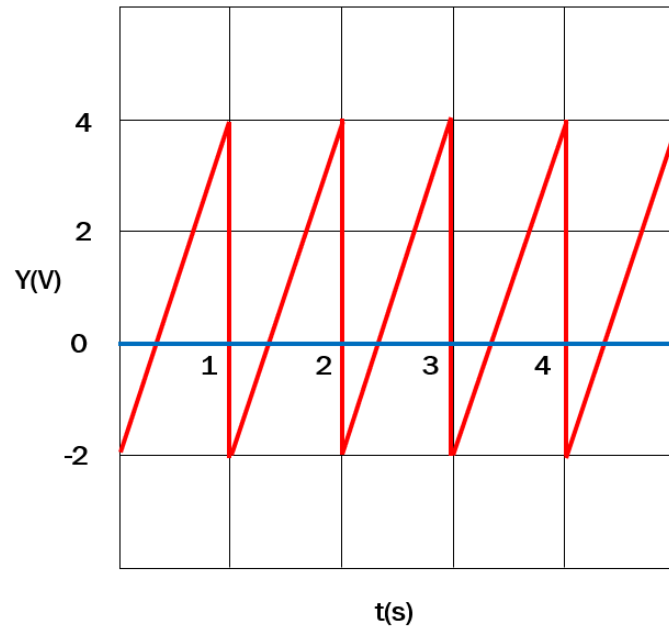Assignment 3  
CSE251  
Summer-25  
Total Marks: 100




8. The input of a **full-wave rectifier** is exhibited in the Figure above and output load resistance is  $R = 5 \text{ k}\Omega$ . Silicon diodes are used in this circuit for which the forward drop is  $V_{D0} = 0.7 \text{ V}$ .
- Show the input and output waveforms.
  - Draw the VTC curve
  - Calculate input and output frequency

Assignment 3  
CSE251  
Summer-25  
Total Marks: 100

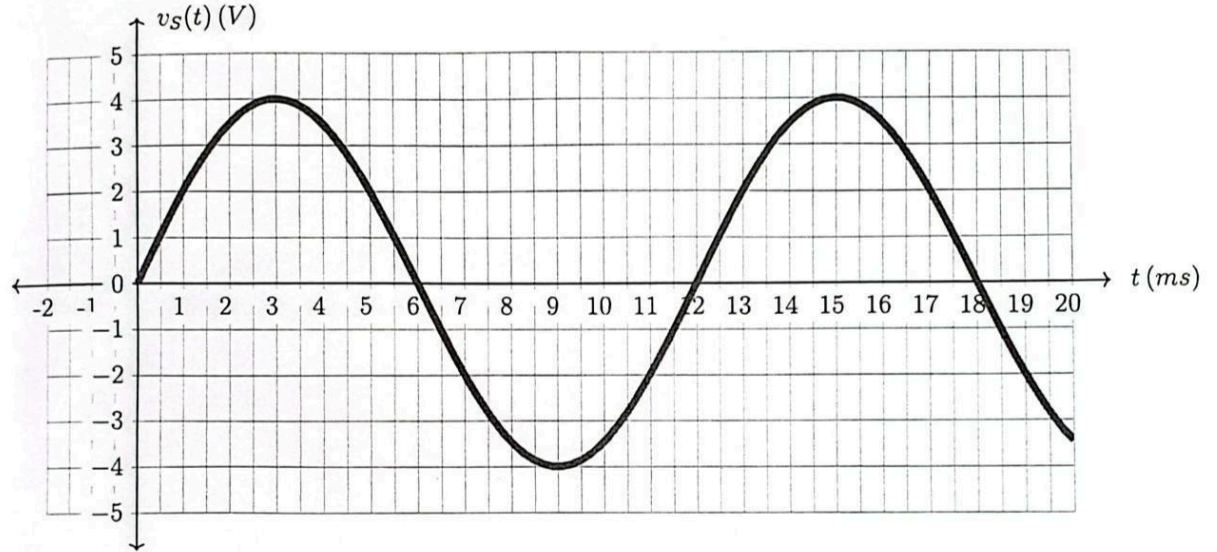9.

$v_S(t)$  is the input voltage to a half wave rectifier without filter capacitor.




- (a) [4 marks] Assuming a cut-in voltage of 1 V for the diode used in the rectifier, approximately draw the output voltage waveform on the same grid.
- (b) [2 marks] Determine the *approximate* average of the output voltage,  $V_{avg}$  or  $V_{DC}$ .
- (c) [2 marks] Determine the fraction of time within a cycle the diode is conducting.

Assignment 3  
CSE251  
Summer-25  
Total Marks: 100

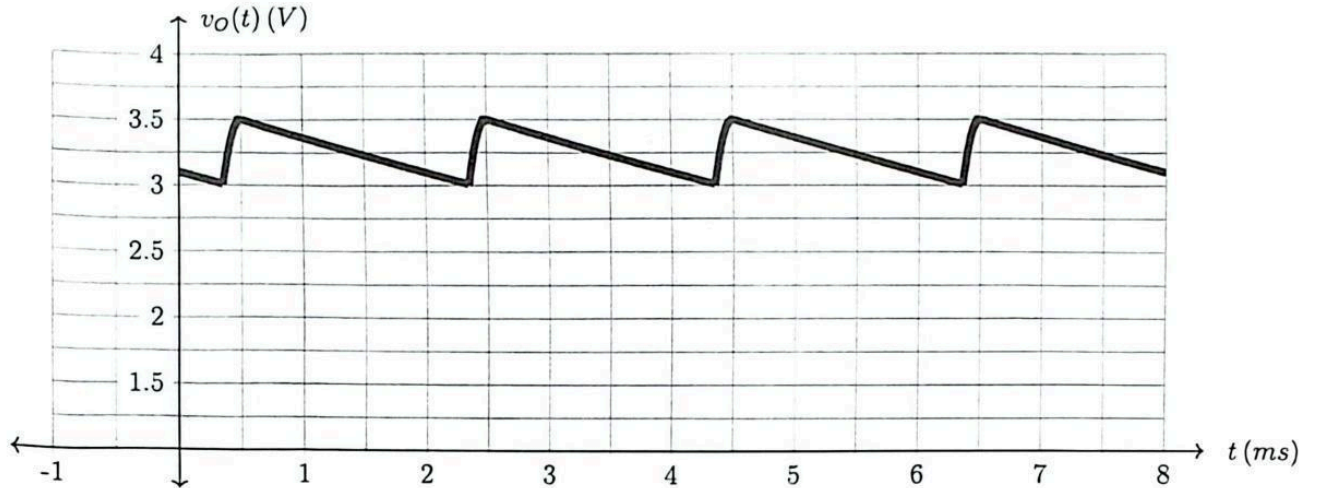10.

$v_O(t)$  is the rectified output of an ac sinusoidal voltage  $v_S(t)$  at 250 Hz frequency, provided to a load of  $4.5\text{ k}\Omega$ . The diode(s) used in the rectifier had a cut-in voltage equal to  $0.5\text{ V}$ .



- (a) [2 marks] Which rectifier was used to rectify the sinusoidal voltage? Explain in brief.
- (b) [4 marks] Determine the capacitance used in the rectifier's design.
- (c) [2 marks] Write an expression of the input voltage as a function of time.
- (d) [4 marks] Draw the circuit diagram of the rectifier. Label the input  $v_S(t)$  and output  $v_O(t)$  voltages properly on the circuit diagram.