

Lecture 3

Introduction to OpAmp

Review


- Last class: alternative representation, KCL, KVL, nodal
- Today: **review** of dependent source, introduction to amplifiers, operational amplifiers

Dependent Source

- Active sources – either voltage or current source
- Difference: voltage (or current) controlled by the voltage/current in a different branch
- Technically non-linear devices – because in real life, dependent sources are made using non-linear electronic devices (e.g. MOSFET)
- However, analysis are similar to linear circuits (CSE250), hence we will start with this


Major Difference

Independent devices:

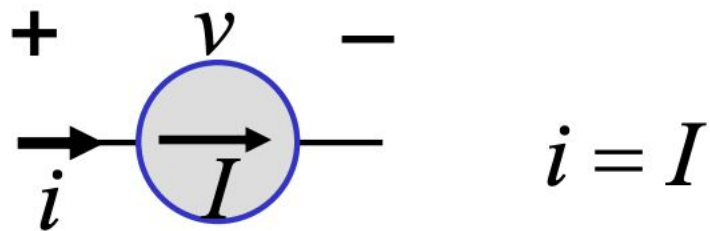


2 terminals, 1 port

Dependent devices:

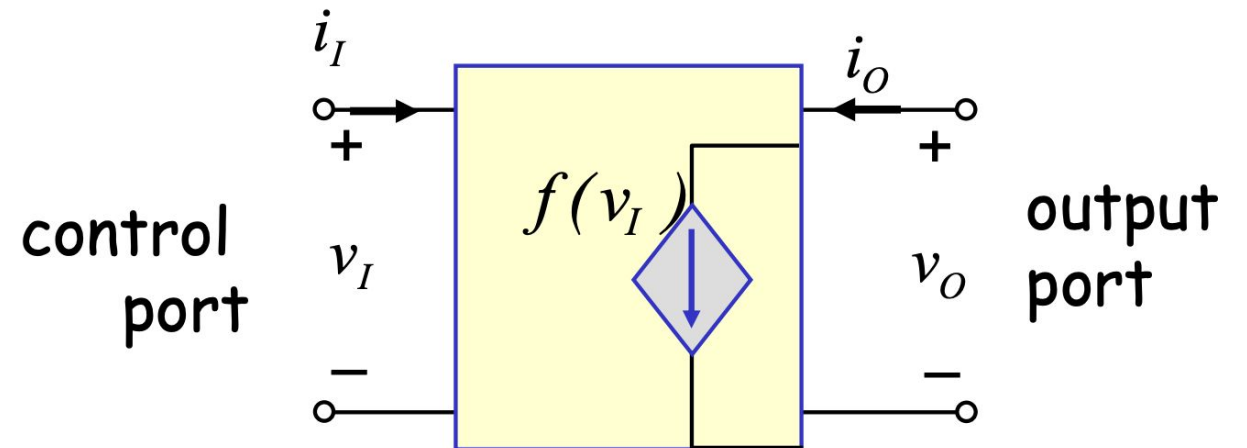

2 terminals, 2 port


Example 1

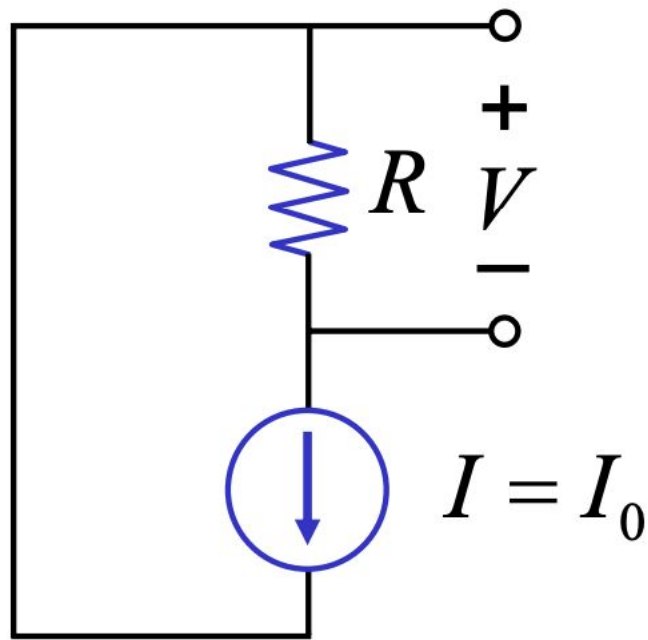


Find V

(Ans: $V = I_0 R$)

Example 2

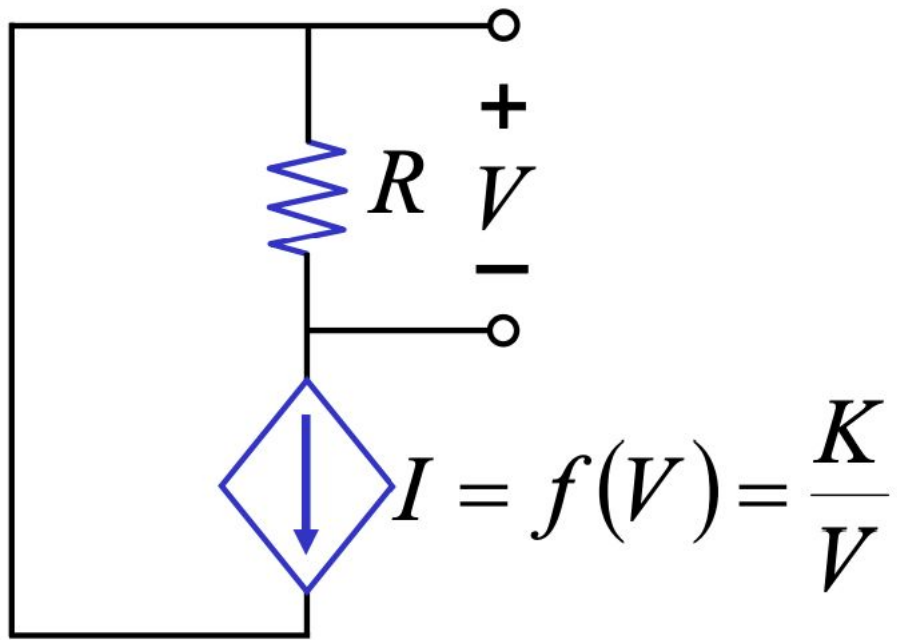

Find V


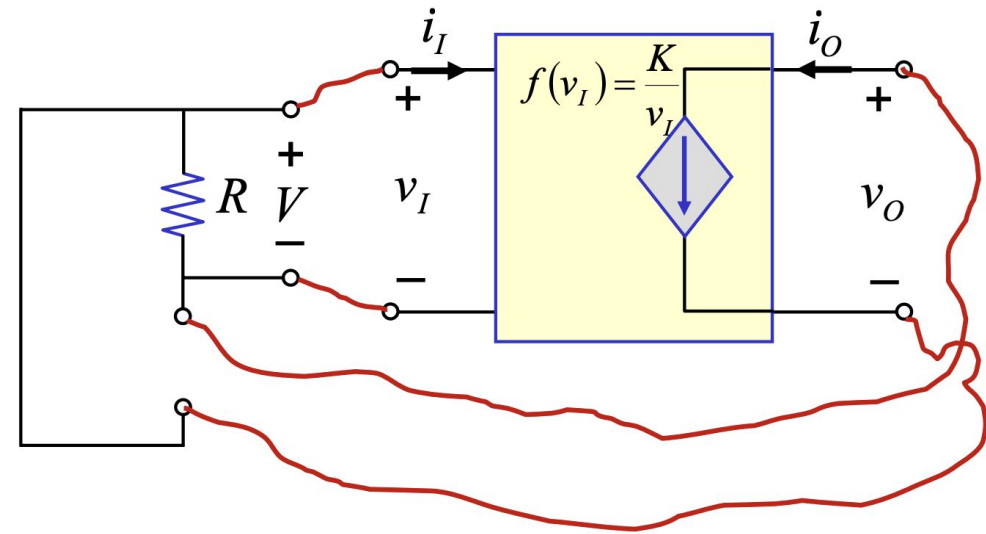


$$\begin{aligned} \text{Ans: } V &= IR \Rightarrow V = \left(\frac{K}{V}\right) R \\ &\Rightarrow V^2 = KR \Rightarrow V = \sqrt{KR} \end{aligned}$$

Application of dependent sources: amplifiers!



Amplifier

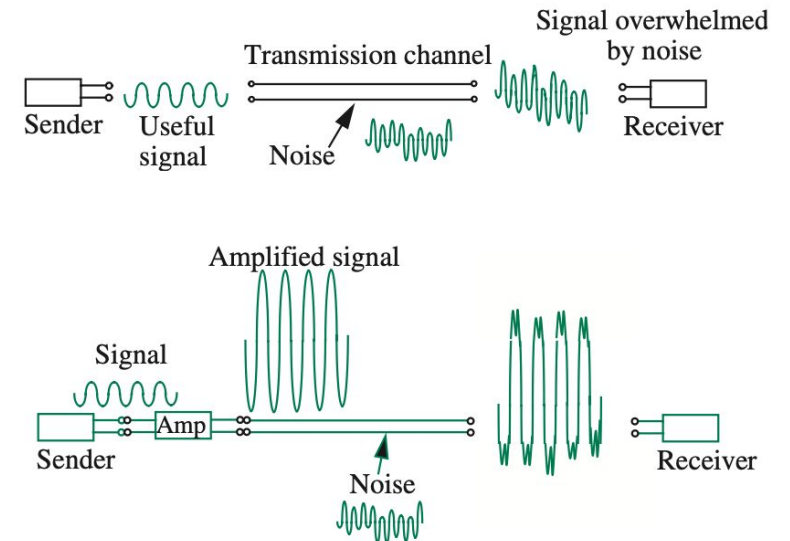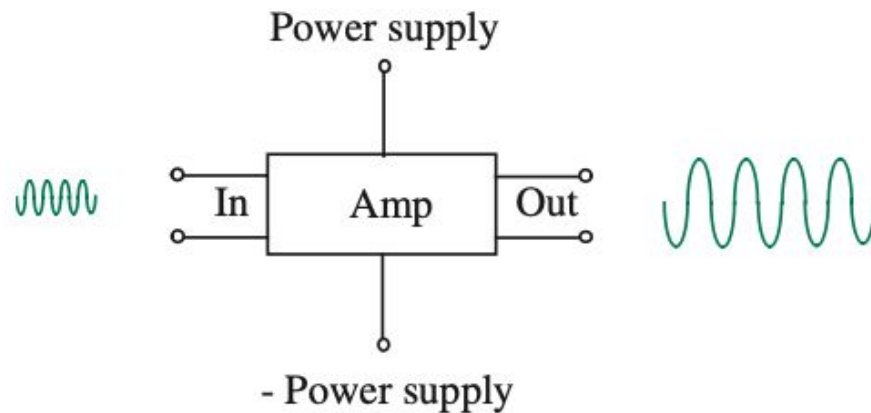- Linear amplifier $\Rightarrow OUT = k \times IN$. k is called the **gain** of the amplifier
- OUT/IN can be voltage or current
- Amplifier must provide power gain ($P_{OUT} > P_{IN}$), hence need **power supply**
- Usage: communication



Transfer Characteristics of Amplifiers

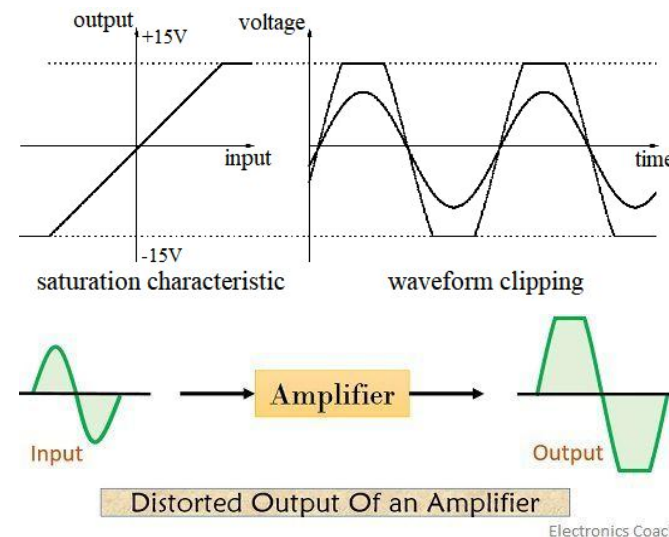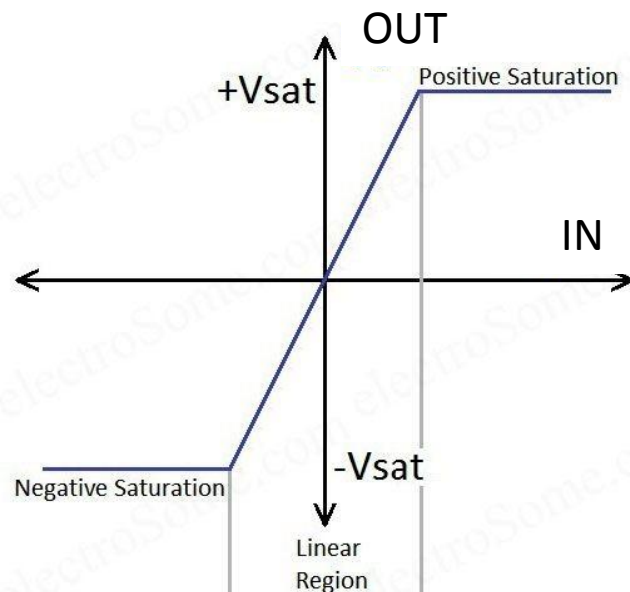- $y = mx$, hence straight line going through origin. Here, $m = k = \text{gain}$
- Saturation due to limited power supply. Output cannot be greater than P.S.
- Input must be within a **valid input range**, otherwise output will be distorted
- Amplifiers are **non-linear devices**, because they are made using dependent sources






Operational Amplifiers

- An operational amplifier, or **op-amp** for short, is a versatile and powerful integrated circuit that is widely used in a variety of electronic applications.
- An Op-Amp is designed so that it performs some mathematical operations when external components, such as resistors and capacitors, are connected to its terminals.
- The op amp is an electronic device consisting of a complex arrangement of resistors, transistors, capacitors, and diodes. A full discussion of what is inside the op amp is beyond the scope of this course. For now, it will suffice to treat the op amp as a circuit building block and simply study what takes place at its terminals.


Terminals and Circuit Symbol

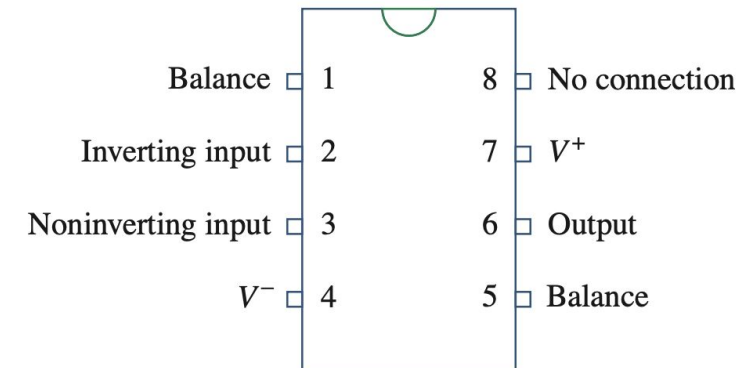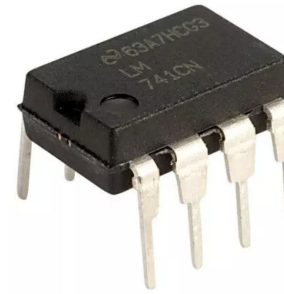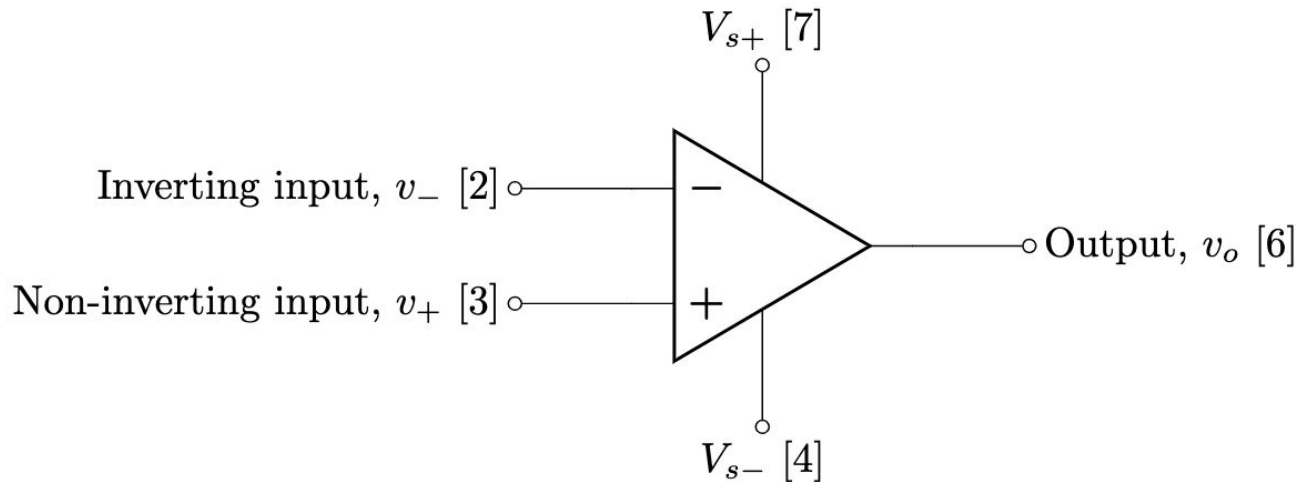- Op-amps are **differential amplifiers** – meaning it amplifies the voltage difference between two terminals. Therefore, it has two inputs
- Since this is an amplifier, there are two terminals for **power supply**



Equivalent Circuit

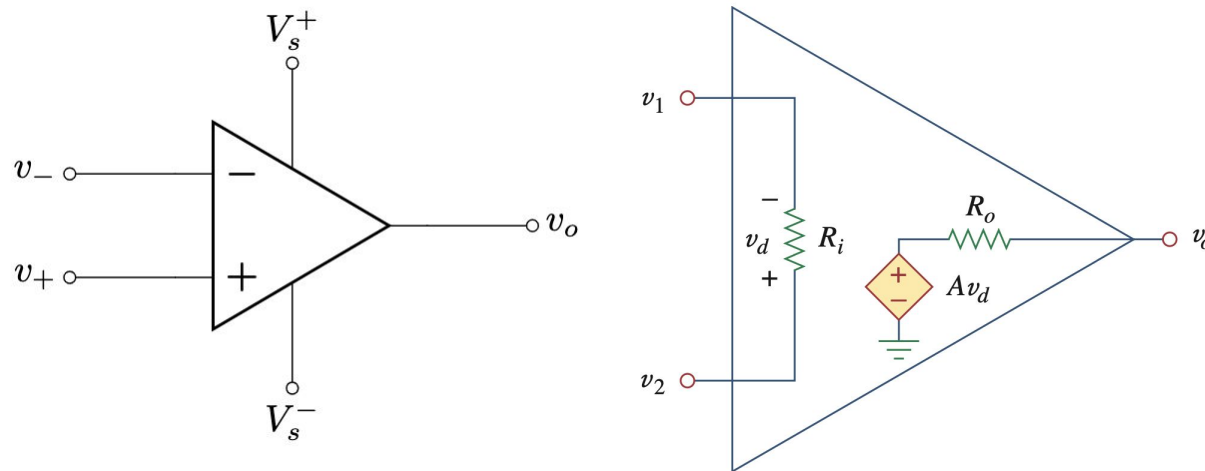Since op amp is an amplifier, the internal circuit can be modeled using a **voltage controlled voltage source** (VCVS)! (actual circuit is complicated)



$v_1 = v_- =$ voltage of inverting terminal
 $v_2 = v_+ =$ voltage of noninverting terminal

$v_d = v_+ - v_- = v_2 - v_1$
= differential input voltage for VCVS

$A =$ Open loop gain

$R_i =$ Input resistance


$R_o =$ Output resistance

The op amp senses the difference between the two inputs, multiplies it by the gain A , and causes the resulting voltage to appear at the output. Thus, the output v_o is given by

$$v_o = Av_d = A(v_2 - v_1) = A(v_+ - v_-)$$

Equivalent Circuit

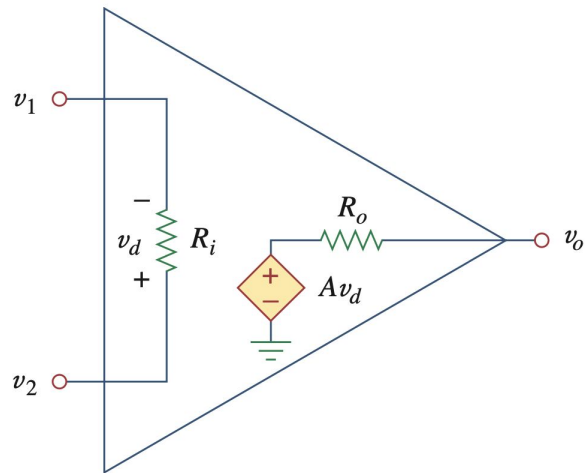Since op amp is an amplifier, the internal circuit can be modeled using a **voltage controlled voltage source** (VCVS)! (actual circuit is complicated)



$v_1 = v_-$ = voltage of inverting terminal
 $v_2 = v_+$ = voltage of noninverting terminal
 $v_d = v_+ - v_- = v_2 - v_1$
= differential input voltage for VCVS
 A = Open loop gain
 R_i = Input resistance
 R_o = Output resistance

Parameter	Typical Range


The op amp senses the difference between the two inputs, multiplies it by the gain A , and causes the resulting voltage to appear at the output. Thus, the output v_o is given by

$$v_o = Av_d = A(v_2 - v_1) = A(v_+ - v_-)$$

Practical Limitation - Saturation


- Similar to amplifiers, the output of op-amp is limited by power supply (Saturation)
- Op-amp can operate in three modes, depending on v_d :
 - Positive saturation: $v_o = V_s^+ = V_{CC}$
 - Linear region: $-V_{CC} < v_o = Av_d < V_{CC}$ [Slope = A]
 - Negative saturation: $v_o = V_s^- = -V_{CC}$
- If we attempt to increase v_d beyond the linear range, the op-amp becomes saturated and yields $v_o = V_{CC}$ or $v_o = -V_{CC}$. That is the output voltage is restricted by

$$-V_{CC} \leq v_o \leq V_{CC}$$

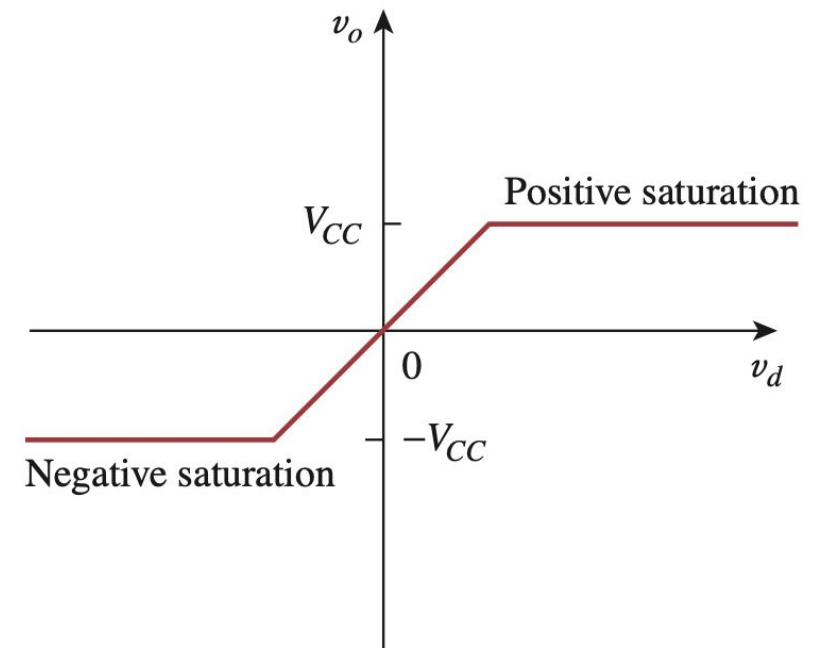

Example 3

- Find v_o

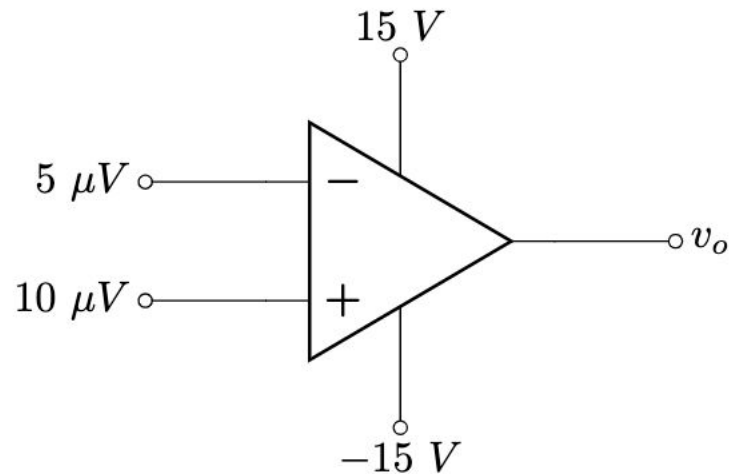

$$A = 2 \times 10^5$$

Solution:


$$v_d = v_+ - v_- = 10\ \mu V - 5\ \mu V = 5\ \mu V$$

$$\Rightarrow v_o = Av_d = (2 \times 10^5) \times (5 \times 10^{-6}) = 1\ V$$

Since this is in between $-V_{CC}$ and V_{CC} , output valid

Example 4

- Find v_o

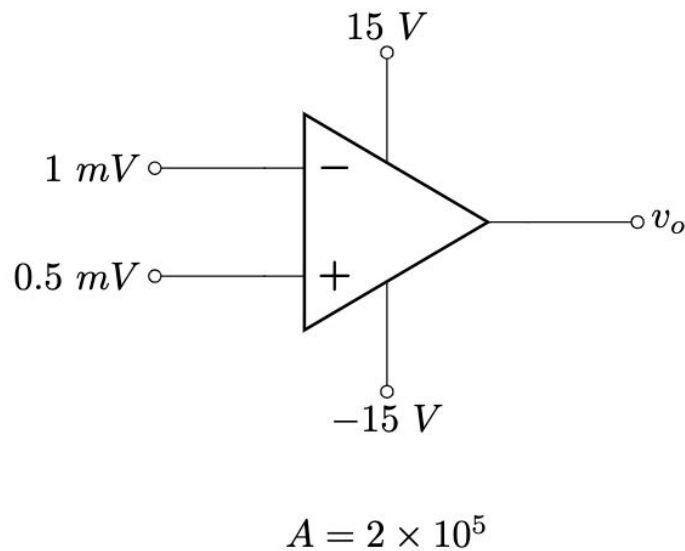

Solution:

$$v_d = v^+ - v^- = 0.5 \text{ mV} - 1 \text{ mV} = -0.5 \text{ mV}$$

$$\rightarrow v_o = Av_d = (2 \times 10^5) \times (-0.5 \times 10^{-3}) = -100 \text{ V}$$

However, the output must be limited within the range of $-V_{CC}$ to $+V_{CC}$. Therefore, the highest output voltage can be -15V.

$$\therefore v_o = -15 \text{ V}$$

Solving Circuit with Op-Amp



- Don't be scared! Circuit solving with op-amp is exactly same as the circuits you solved in CSE250
- Step 1: replace with equivalent circuit
- Step 2: solve using KCL & KVL, or nodal analysis (linear)
- In most cases, the power supply voltages are not mentioned. **Hence, we will assume the output is within the linear range in this case**

Example 5

Find i_F and v_o . Here, $R_i = 200\text{ k}\Omega$, $R_o = 0.1\text{ k}\Omega$, $A = 2 \times 10^5$


Solution:

Step 1: replace using equivalent circuit

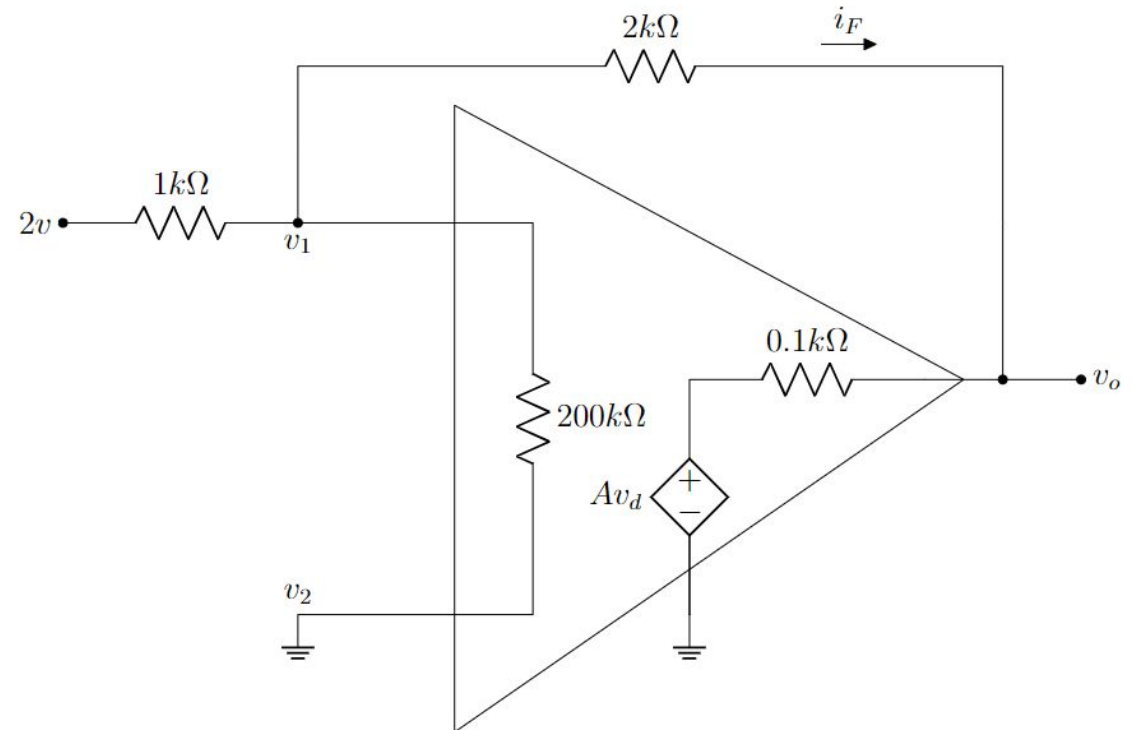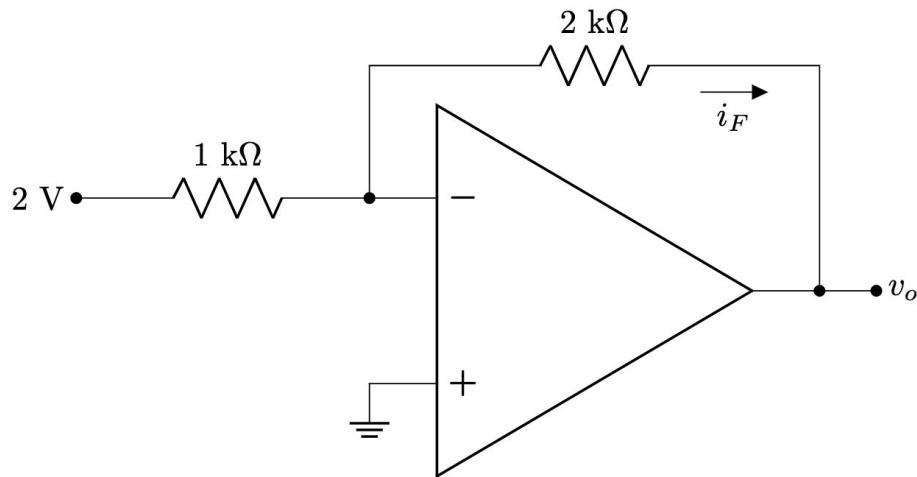

Example 5

Step 2: Solve using KCL & KVL or nodal

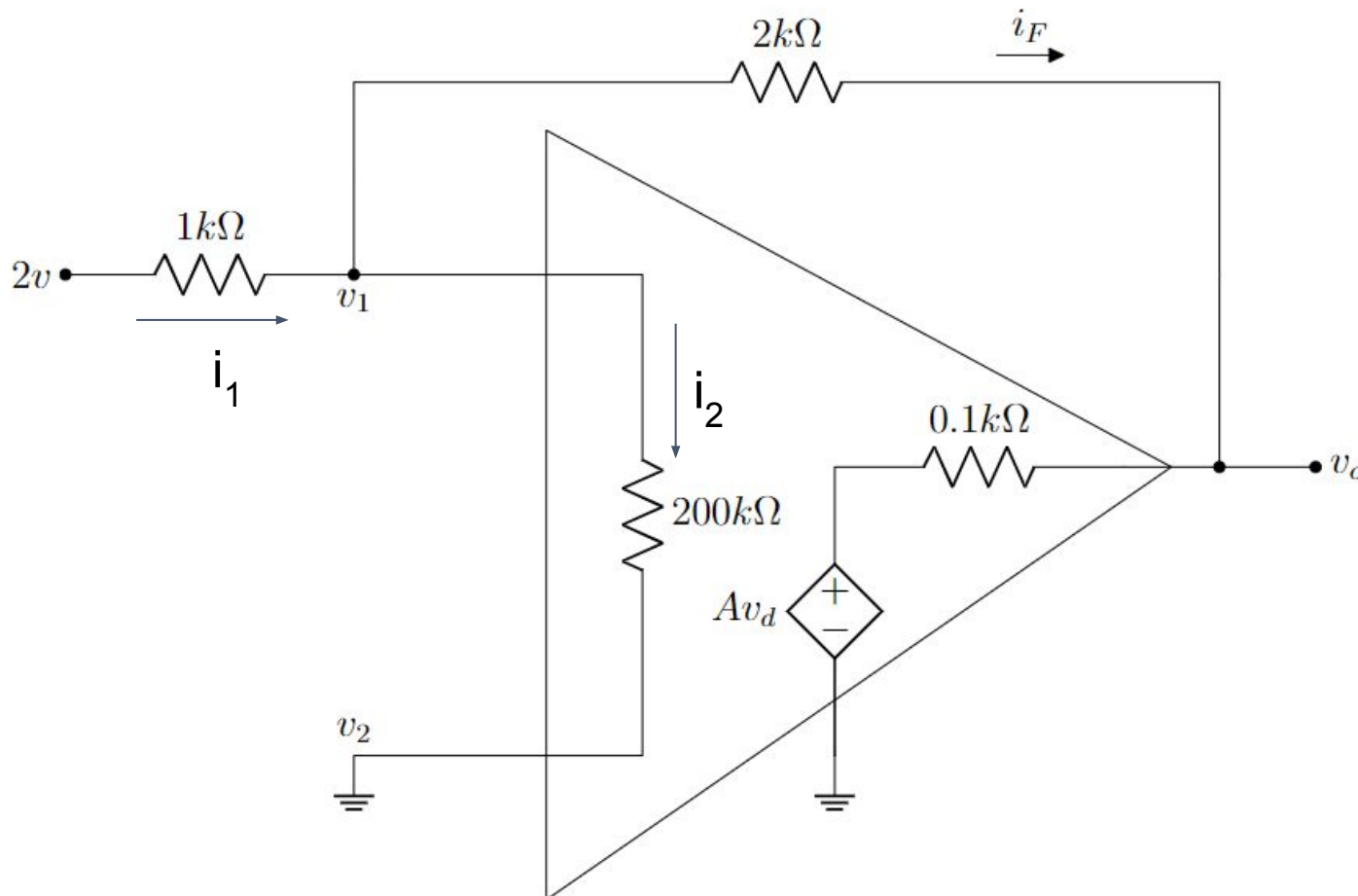

Applying KCL we get,

$$i_1 = i_2 + i_F$$

$$\rightarrow (2 - v_1)/(1k) = (v_1 - v_2)/(200k) + (v_1 - v_o)/(2k)$$

$$\rightarrow (2 - v_1)/(1k) = (v_1 - 0)/(200k) + (v_1 - v_o)/(2k)$$

$$\rightarrow (2 - v_1)/(1k) = v_1/(200k) + (v_1 - v_o)/(2k) \dots \dots (i)$$

Again, from the figure,

$$i_{0.1k} = i_F$$

$$\rightarrow (v_o - Av_d)/(0.1k) = (v_1 - v_o)/(2k)$$

$$\rightarrow (v_o - (2 \times 10^5) \times (v_2 - v_1))/(0.1k) = (v_1 - v_o)/(2k)$$


$$\rightarrow (v_o - (2 \times 10^5) \times (0 - v_1))/(0.1k) = (v_1 - v_o)/(2k)$$

$$\rightarrow (v_o - (2 \times 10^5) \times (-v_1))/(0.1k) = (v_1 - v_o)/(2k) \dots (ii)$$

We can get v_1 and v_o by solving equation (i) and (ii)


Example 5

Step 2: Solve using KCL & KVL or nodal

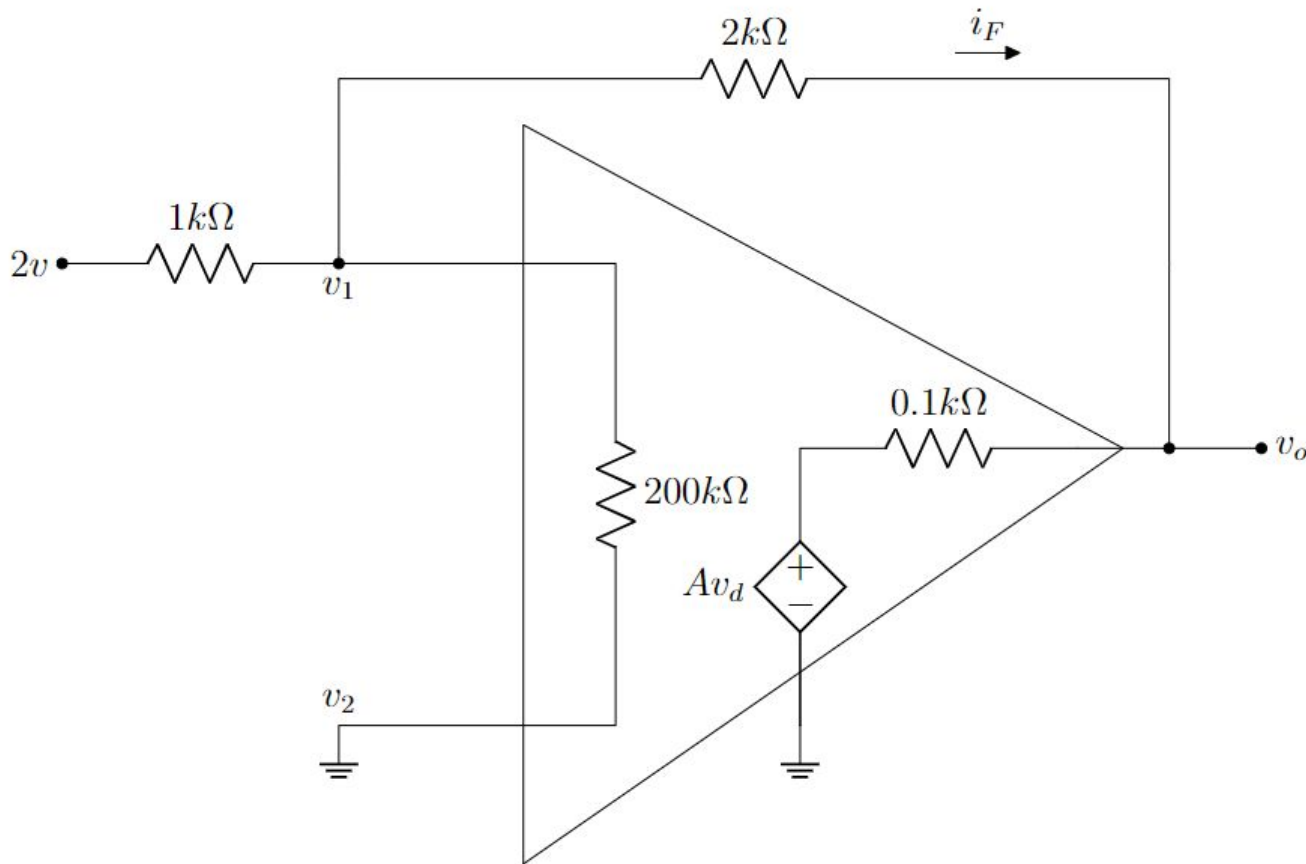

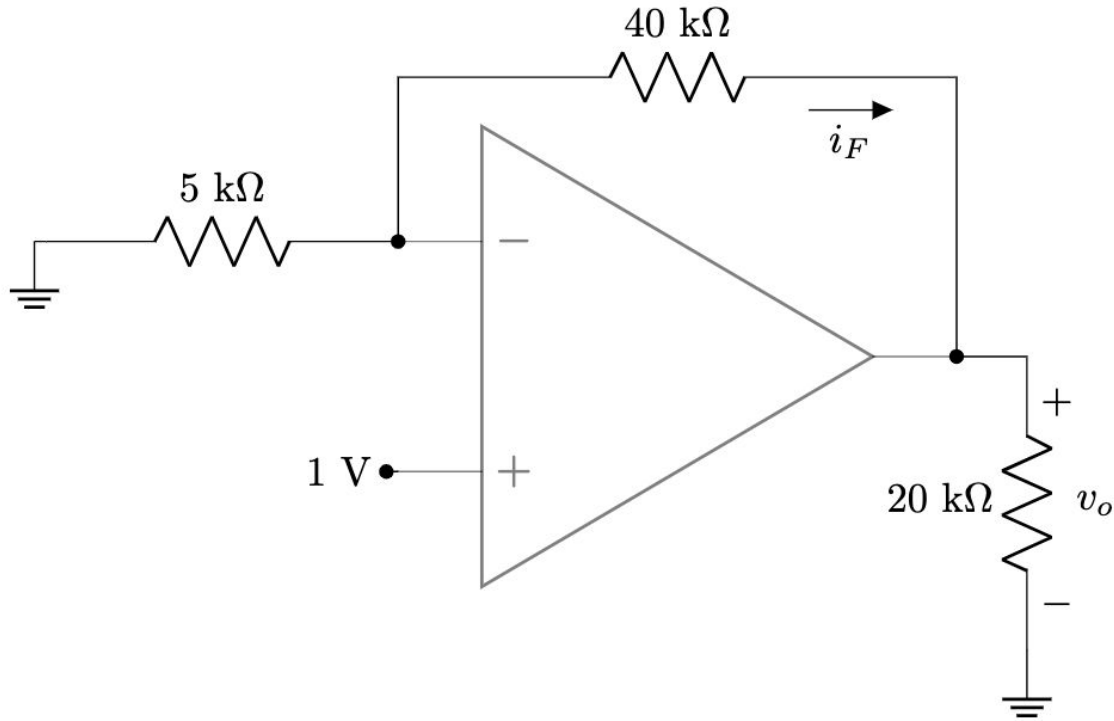Example 6

Find i_F and v_o . Here, $R_i = 200\text{ k}\Omega$, $R_o = 0.1\text{ k}\Omega$, $A = 2 \times 10^5$




The Ideal Op-Amp

- To facilitate the understanding of op amp circuits, we will assume **ideal op amps**
 - Infinite open-loop gain, $A = \infty$
 - Infinite input resistance, $R_i = \infty = \text{open circuit}$
 - Zero output resistance, $R_o = 0 = \text{short circuit}$
- Although an ideal op amp provides only an approximate analysis, most modern amplifiers have such large gains and input impedances that the approximate analysis is a good one.
- **Circuit solving become much simpler.** As $R_i = \infty, i_1 = i_2 = 0$
- Since $A = \infty$, in open-loop configuration, v_o will either be positive saturated or negative saturated (why?)

$$v_o = \begin{cases} V_s^+ & \text{if } v_d > 0 \Rightarrow v_2 > v_1 \\ V_s^- & \text{if } v_d < 0 \Rightarrow v_2 < v_1 \end{cases}$$

Reminder: $v_d = v_2 - v_1 = v_+ - v_-$

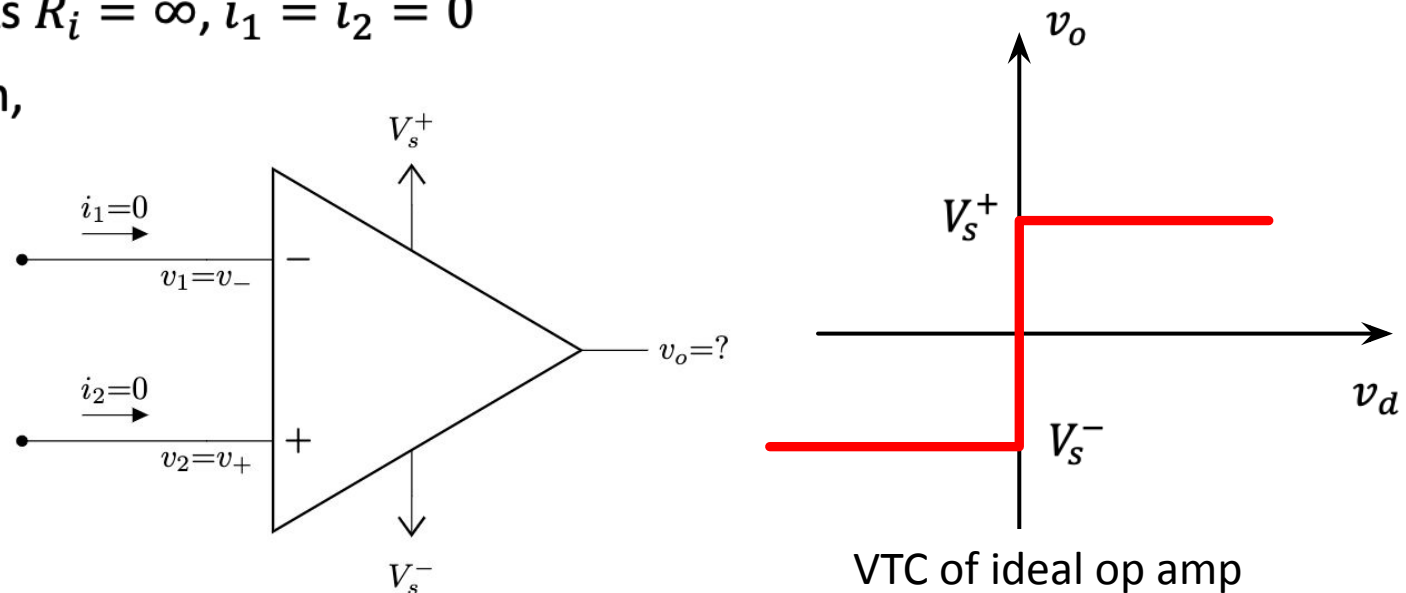

Application - Comparator

- A comparator compares two voltages to determine which is larger.
- The comparator is essentially an op-amp operated in an open-loop configuration
- Two types –
 - (1) **Non-inverting**: outputs a positive voltage ($V_H = V_S^+$) when input is greater than reference
 - (2) **Inverting**: outputs a negative voltage ($V_L = V_S^-$) when input is greater than reference
- Application – smoke detector, turning AC on/off automatically, etc (next lecture)

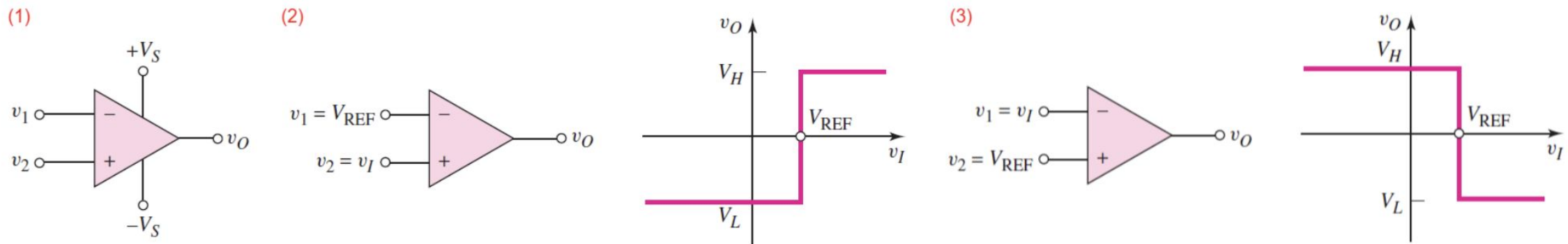


Figure 2: (1) Op-Amp Comparator (2) Noninverting Circuit (3) Inverting Circuit