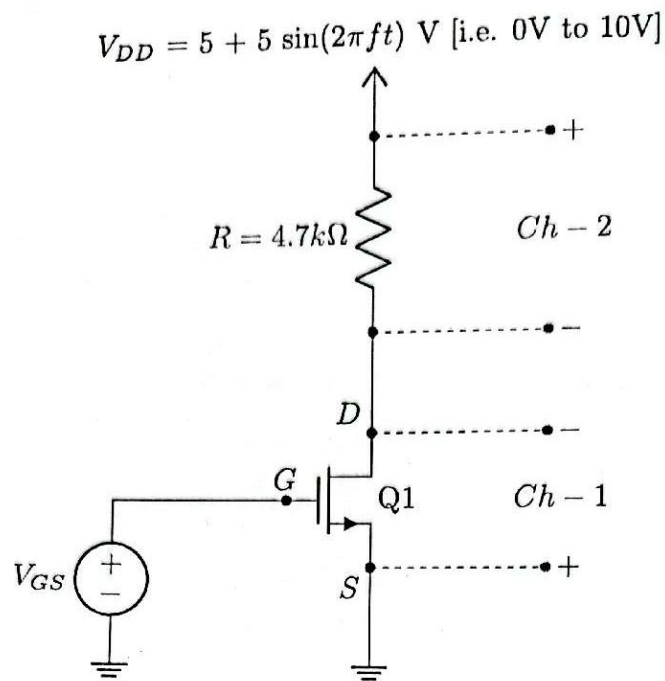


## Task-01: I-V Characteristics of a MOSFET




### Procedure

1. Construct the circuit shown above. Use a data switch and connect it to the Gate of the MOSFET which will provide necessary voltage for  $V_{GS}$ . Use the function generator for  $V_{DD} = 5 + 5 \sin(2\pi ft) \text{ V}$  [i.e. an AC voltage that varies from 0V to 10V] and set  $f = 50 \text{ Hz}$ .
2. Set the oscilloscope in X-Y mode. Invert the Channel-1.
3. Observe the plot in the oscilloscope when the data switch is ON and OFF. This plot shows the I-V characteristics of a MOSFET as a switch. Capture the plots using your mobile camera.
4. Now, disconnect the data switch from the gate of the MOSFET and connect the dc power supply to the gate terminal so that we can increase or decrease  $V_{GS}$ .
5. Rotate the voltage knob of the dc power supply slowly from 0V to 5V. You should observe the change in the I-V characteristics.
6. Use your mobile camera to capture the image of the I-V characteristics graphs for 3 different  $V_{GS}$ . Measure the values of  $V_{GS}$  of the captured images and write them in Data Table 1.

**Data Table 1: Different Values of  $V_{GS}$  to observe the change in MOSFET I-V Characteristics**

| Values of $V_{GS}$ |      |
|--------------------|------|
| 1st Value          | 2.6  |
| 2nd Value          | 01.9 |
| 3rd Value          | 1.3  |
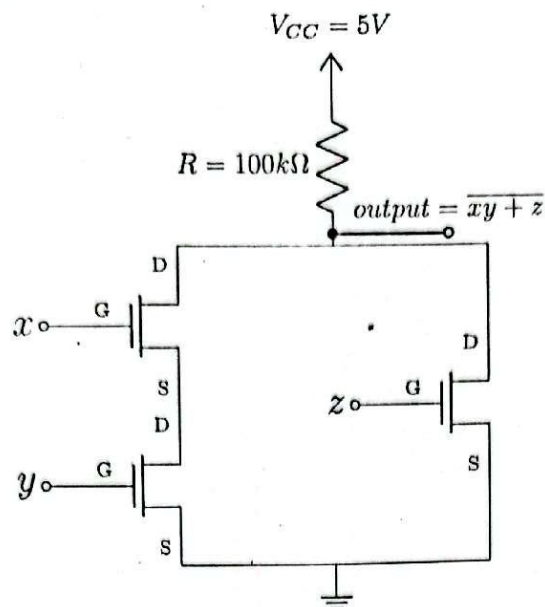
## Task-02: Logic Function Implementation



Circuit-1

Logic Function,  $f = \overline{xy} + z$  using MOSFET

### Procedure


1. On a trainer board, setup the Circuit 1.
2. Connect the gate terminals (input x, y and z) to data switches. Those switches provide 5V approximately.
3. Keeping  $V_{CC}$  constant at 5V, at first turn off the data switches connected to the gate terminal. This implies you are now applying  $V_x = 0V$ ,  $V_y = 0V$  and  $V_z = 0V$ . Measure the corresponding output voltage,  $V_{out}$  which should be approximately 5V which corresponds to boolean 1.
4. The boolean outputs can also be determined by the state of an LED. Connect  $V_{out}$  to one of the LEDs and check it. When the LED is ON, the boolean output is 1. Similarly, when the LED is OFF, the boolean output is 0.
5. Next, use the input voltage combinations of Data Table 2 and observe the state of LED again.
6. Verify the truth table of the Logic Function,  $f = \overline{xy} + z$ .

Data Table 2: Verification of the Truth Tables of Logic Function,  $f = \overline{xy} + z$


| Input Voltage,<br>$V_x$ (volt) | Input Voltage,<br>$V_y$ (volt) | Input Voltage,<br>$V_z$ (volt) | State of LED<br>(On/Off) | Boolean Output<br>(0 or 1) |
|--------------------------------|--------------------------------|--------------------------------|--------------------------|----------------------------|
| 0V                             | 0V                             | 0V                             | ON                       | 1                          |
| 0V                             | 0V                             | 5V                             | OFF                      | 0                          |
| 0V                             | 5V                             | 0V                             | ON                       | 1                          |
| 0V                             | 5V                             | 5V                             | OFF                      | 0                          |
| 5V                             | 0V                             | 0V                             | ON                       | 1                          |
| 5V                             | 0V                             | 5V                             | OFF                      | 0                          |
| 5V                             | 5V                             | 0V                             | OFF                      | 0                          |
| 5V                             | 5V                             | 5V                             | OFF                      | 0                          |





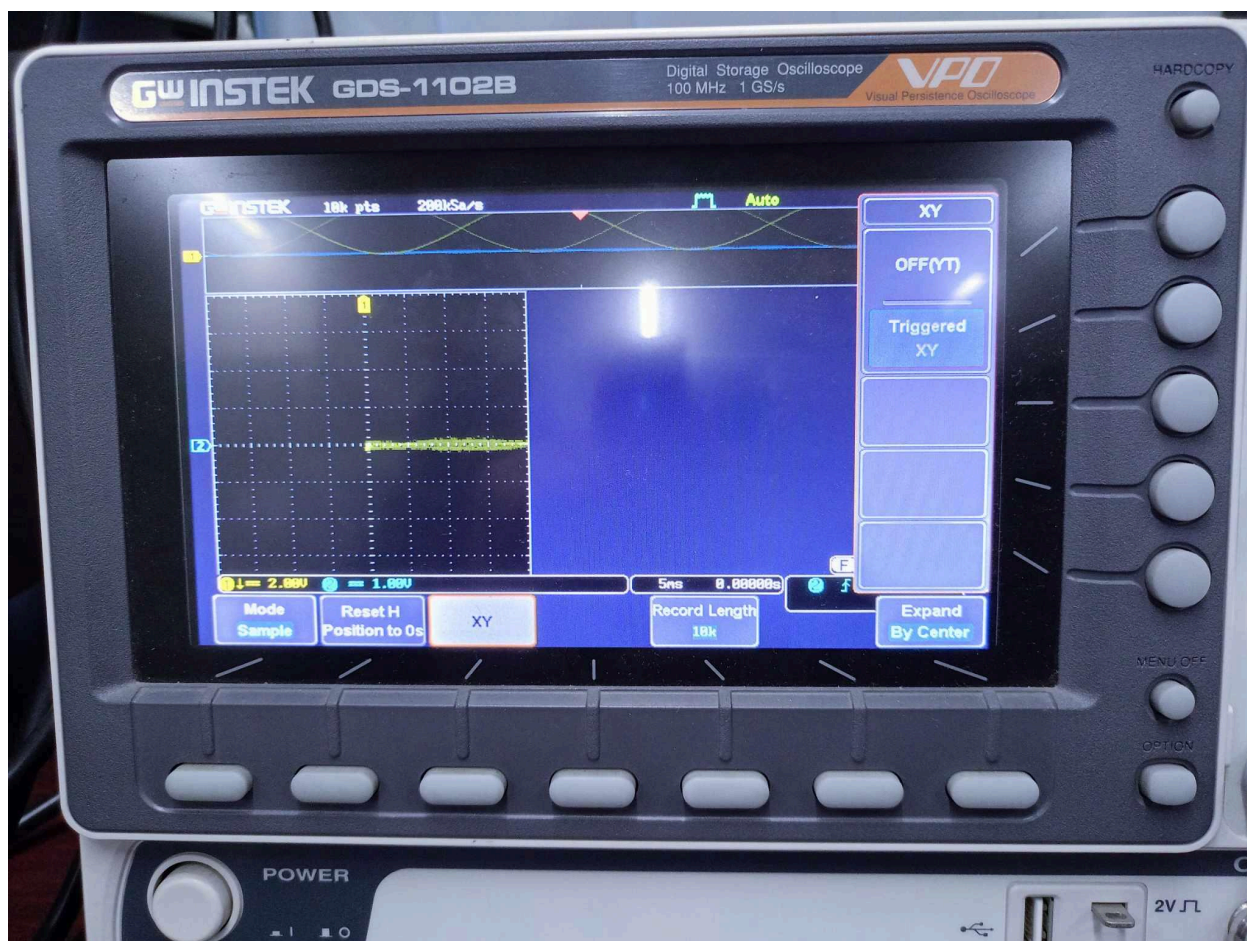




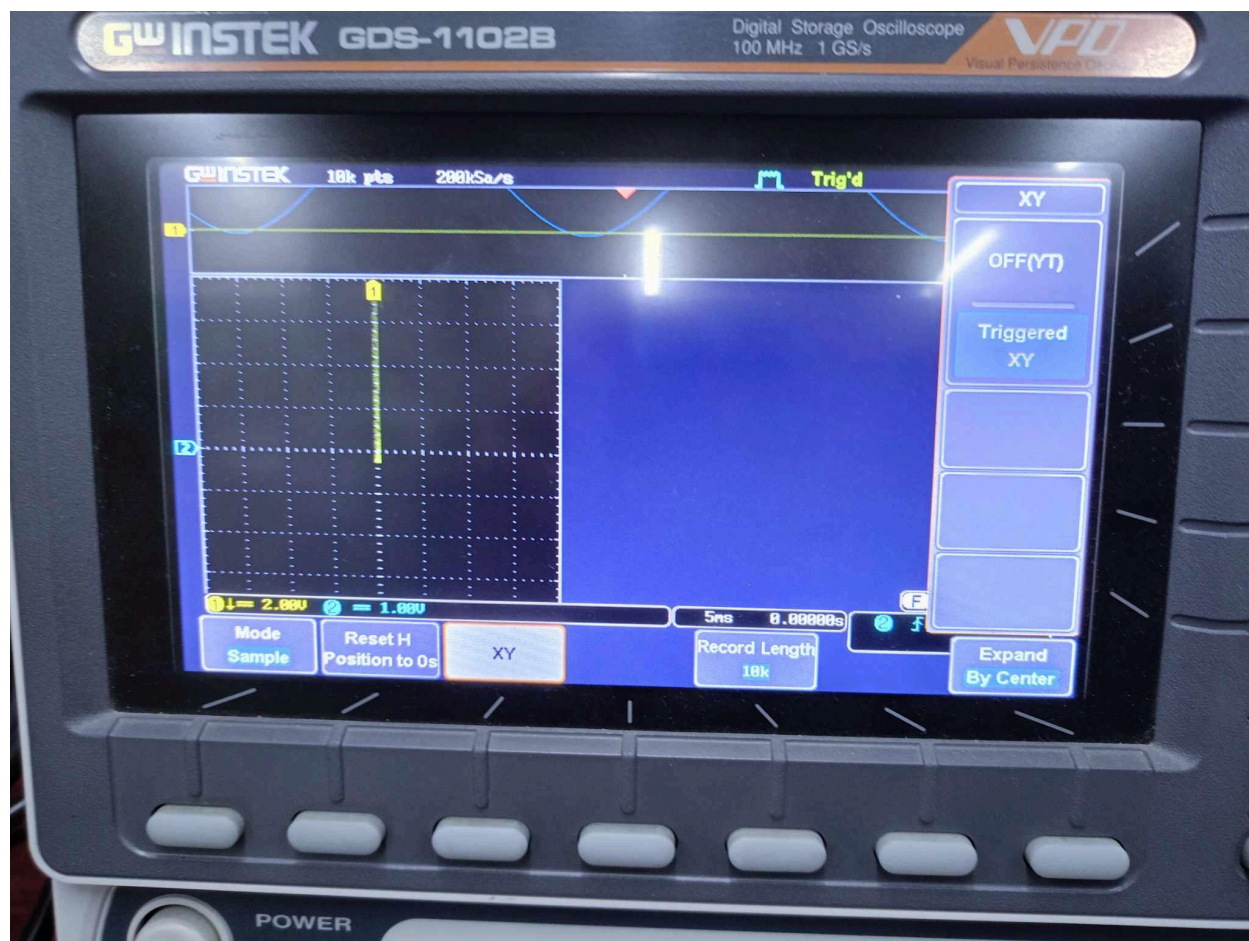
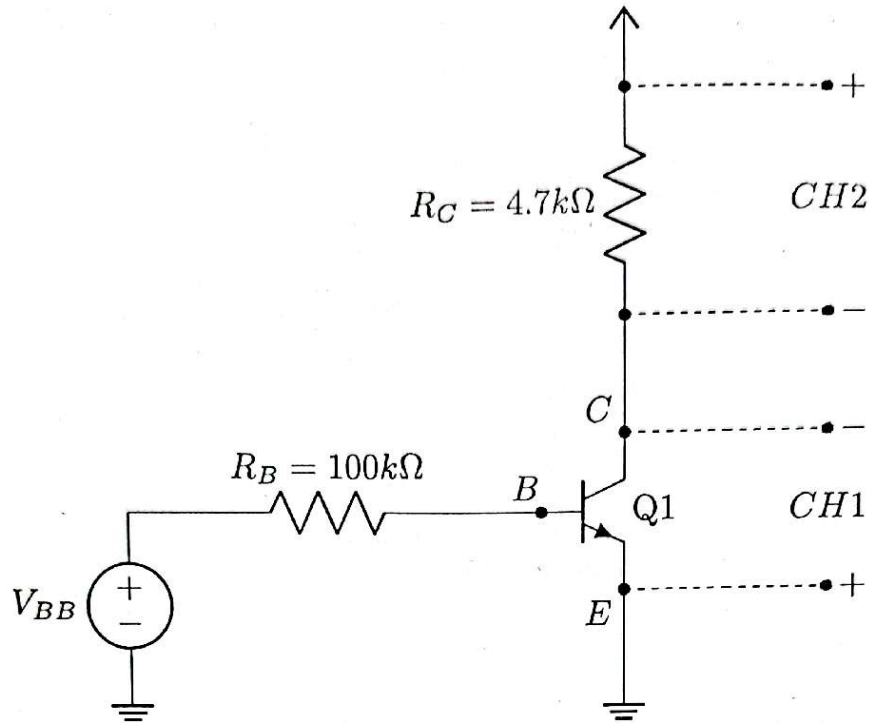
### Task-03: I-V Characteristics of a BJT

$$V_{CC} = 5 + 5 \sin(2\pi ft) \text{ V [i.e. 0V to 10V]}$$




#### Procedure

1. Construct the circuit shown above. Use the function generator for  $V_{CC} = 5 + 5 \sin(2\pi ft) \text{ V}$  [i.e. an AC voltage that varies from 0V to 10V]. Set  $f = 50 \text{ Hz}$ . Use the dc power supply for  $V_{BB}$ .
2. Invert the CH1. Set the oscilloscope in the X-Y mode.
3. Now, rotate the voltage knob of the dc power supply slowly from 0V to 5V to vary  $V_{BB}$ . You should observe the change in the I-V characteristics.
4. Use your mobile camera to capture the image of the I-V characteristics graphs for 3 different values of  $V_{BB}$ . Measure the values of  $V_{BB}$  of the captured images and write them in Data Table 3:

**Data Table 3: Different Values of  $V_{BB}$  to observe the change in BJT I-V Characteristics**

| Values of $V_{BB}$ |     |
|--------------------|-----|
| 1st Value          | 0.3 |
| 2nd Value          | 0.8 |
| 3rd Value          | 1.3 |
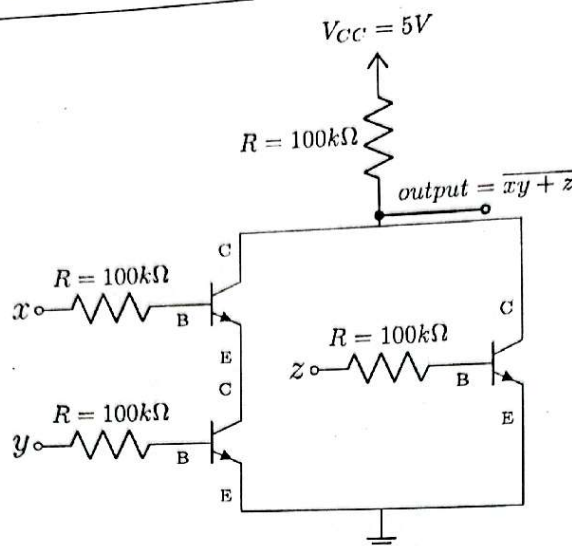
## Task-04: Logic Function Implementation



Circuit-1

Logic Function,  $f = \overline{xy} + z$  using BJT


### Procedure

1. On a trainer board, setup the Circuit 1.
2. Connect the gate terminals (input x and y) to data switches. Those switches provide 5V approximately.
3. Keeping  $V_{CC}$  constant at 5V, at first turn off the data switches connected to the gate terminal. This implies you are now applying  $V_x = 0V$ ,  $V_y = 0V$  and  $V_z = 0V$ . Measure the corresponding output voltage,  $V_{out}$  which should be approximately 5V which corresponds to boolean 1.
4. The boolean outputs can also be determined by the state of an LED. Connect  $V_{out}$  to one of the LEDs and check it. When the LED is ON, the boolean output is 1. Similarly, when the LED is OFF, the boolean output is 0.
5. Next, use the input voltage combinations of Data Table 4 and observe the state of LED again.
6. Verify the truth table of the Logic Function,  $f = \overline{xy} + z$ .

Data Table 4: Verification of the Truth Tables of Logic Function,  $f = \overline{xy} + z$

| Input Voltage,<br>$V_x$ (volt) | Input Voltage,<br>$V_y$ (volt) | Input Voltage,<br>$V_z$ (volt) | State of LED<br>(On/Off) | Boolean Output<br>(0 or 1) |
|--------------------------------|--------------------------------|--------------------------------|--------------------------|----------------------------|
| 0V                             | 0V                             | 0V                             | ON                       | 1                          |
| 0V                             | 0V                             | 5V                             | OFF                      | 0                          |
| 0V                             | 5V                             | 0V                             | ON                       | 1                          |
| 0V                             | 5V                             | 5V                             | OFF                      | 0                          |
| 5V                             | 0V                             | 0V                             | ON                       | 1                          |
| 5V                             | 0V                             | 5V                             | OFF                      | 0                          |
| 5V                             | 5V                             | 0V                             | OFF                      | 0                          |
| 5V                             | 5V                             | 5V                             | OFF                      | 0                          |



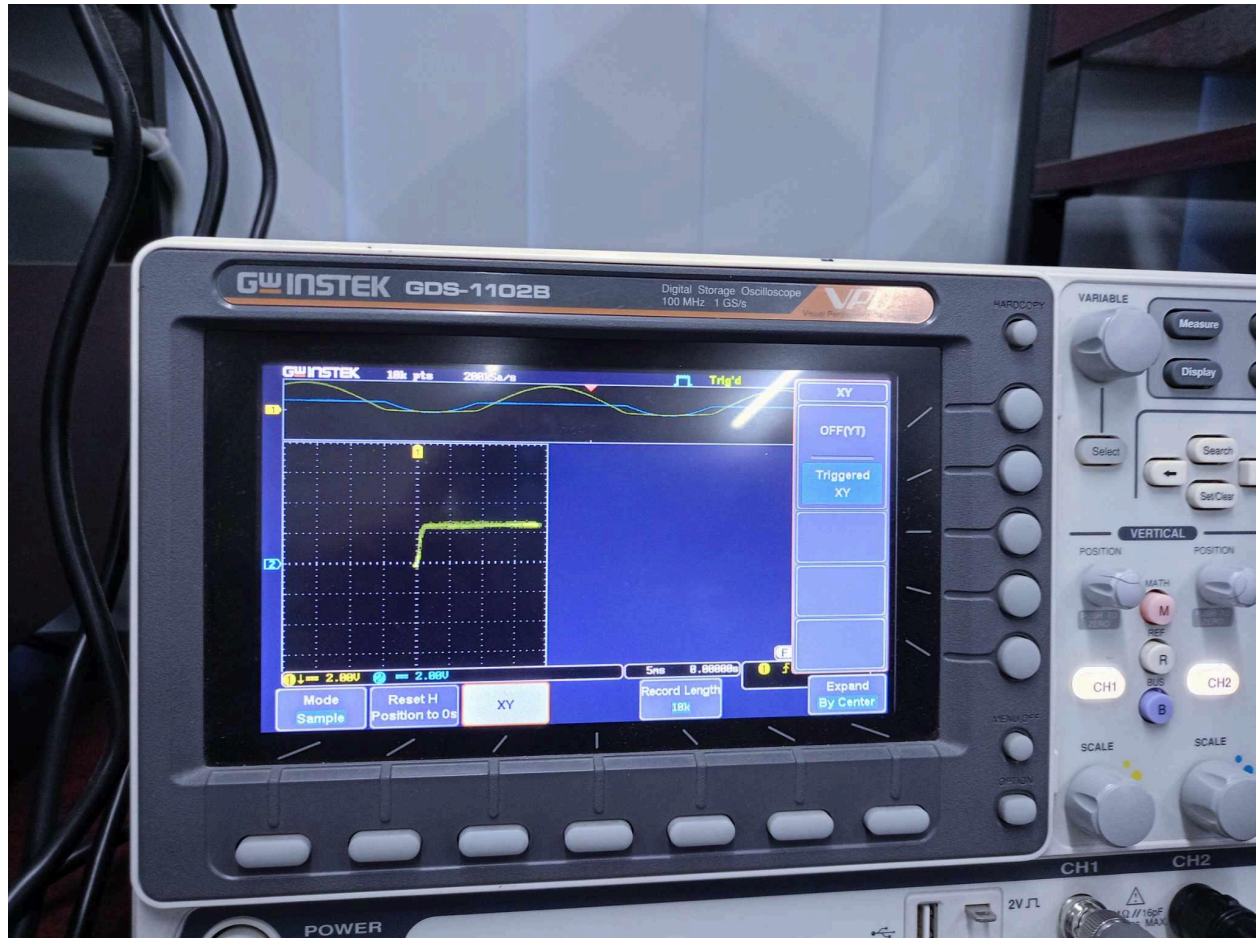







## Task-05: Report

1. Cover page [include course code, course title, name, student ID, group, semester, date of performance, date of submission]
2. Attach the signed Data Sheet.
3. Attach the captured photos of all the waveforms and measurements you have observed in the Oscilloscope. Each photo should contain necessary description.
4. Answer the questions of the Test Your Understanding section.
5. Add a brief Discussion at the end of the report. For the Discussion part of the lab report, you should include the answers of the following questions in your own words:
  - What did you learn from this experiment?
  - What challenges did you face and how did you overcome the challenges? (if any)
  - What mistakes did you make and how did you correct the mistakes? (if any)
  - How will this experiment help you in future experiments of this course?

*Teunter*

Signature of the lab faculty

### Test Your Understanding

Answer the following questions:

1. We can use the MOSFET as a switch. Which operating regions do we need for this purpose and why?

Answer:


We need linear/triode region for MOSFET to behave as a switch.

For linear region:  $V_{gs} > V_T$ ,  $V_{ds} < V_{ov}$


In this region the MOSFET allows current to flow freely between drain and source.



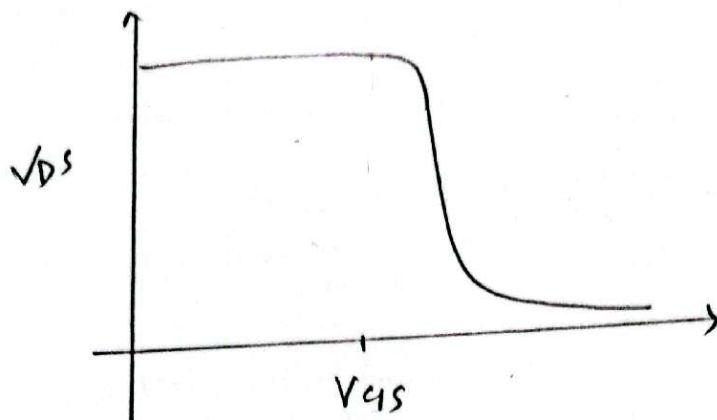2. Draw the VTC ( $V_{DS}$  vs  $V_{GS}$ ) graph of a MOSFET operating as a switch.  
Answer:



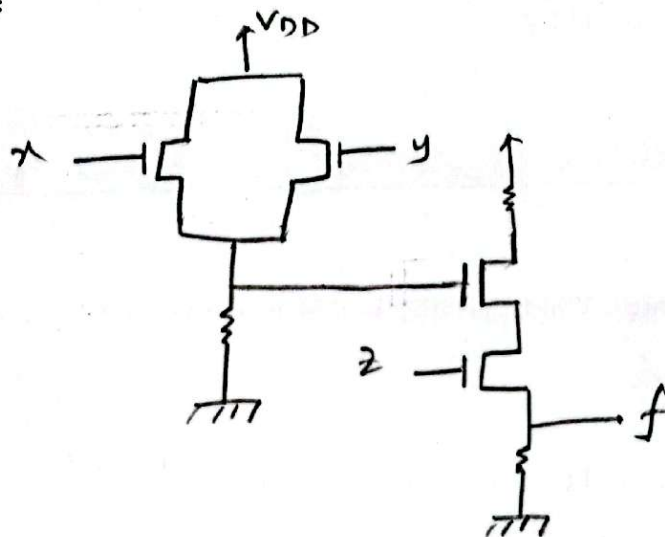3. Draw a circuit using MOSFETs that implements the following logic function,  $f = (x+y)z$   
Answer:



4. When a MOSFET is in triode mode, does it display zero, finite or infinite resistance? Justify your answer.  
Answer:


When a MOSFET is in triode mode, it displays finite resistance.

In linear mode,  $V_{GS} > V_T$  and  $V_{DS} < V_O$

$$I_D = K_n' \frac{W}{L} \left[ (V_{GS} - V_T) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

$$\therefore R_{DS} = \frac{V_{DS}}{I_D} = \frac{V_{DS}}{K_n' \frac{W}{L} \left[ (V_{GS} - V_T) V_{DS} - \frac{1}{2} V_{DS}^2 \right]}$$

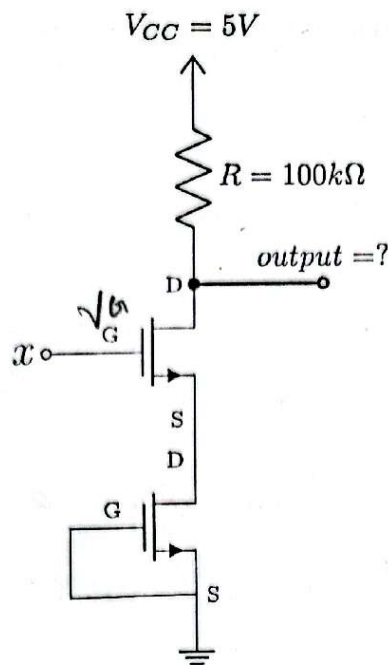So  $R_{DS}$  is not infinite nor zero. It



5. What is the value of the output of the circuit above?

Answer: Output depends on gate Voltage,  $V_G = x$

if  $x$  is 0; no current flows from drain to source,  
(OFF) output is high through resistor.

Output = 5V

if  $x$  is 1; current flows from drain to ground.  
(ON) output is pulled low.

Output = 0V

6. If  $V_{DS} = 3V$ ,  $V_{GS} = 3V$  and  $V_T = 1V$ , find the gate current, drain current and source current of a MOSFET given that  $k = 0.5mA/V^2$ .

Answer:

$$V_0 = V_{GS} - V_T = (3 - 1) = 2V$$

$$V_{DS} = 3V$$

$$V_0 < V_{DS}$$

∴ saturation

$$I_G = 0$$

$$\begin{aligned} I_D &= \frac{1}{2} k_n (V_{GS} - V_T)^2 \\ &= \frac{1}{2} \times 0.5 \times (3 - 1)^2 \\ &= 1 \text{ mA} \end{aligned}$$

$$I_S = 1 \text{ mA}$$



CamScanner

7. We can use the BJT as a switch. Which operating regions do we need for this purpose and why?

Answer:

To use BJT as a switch, we need to use  
i) cutoff & ii) saturation region.

Cutoff region for the OFF state and  
saturation region for the ON state.

We do not need to use active region because  
it's for amplification, not switching.

8. What's the primary difference between a MOSFET and a BJT when they are both acting as switches?

Answer:

MOSFET is a voltage controlled transistor  
while BJT is a current controlled transistor.

MOSFET requires voltage at the gate to turn ON.

BJT requires base current to stay ON.

MOSFET's switching speed is faster than BJT  
and its efficiency is higher at high speed compared  
to BJT


9. Suppose we want to cascade two BJT logic gates (use the output of the first logic gate as one of the inputs of the second one). Why do we need to add a resistor at the input of the second logic gate?

Answer:

The output of the first BJT is the input of the  
second BJT. The Base-emitter junction behaves like a  
diode. Without a resistor the output of the first  
gate could sink excessive current and damage logic  
levels. The resistor limits the base current to  
a safe value.



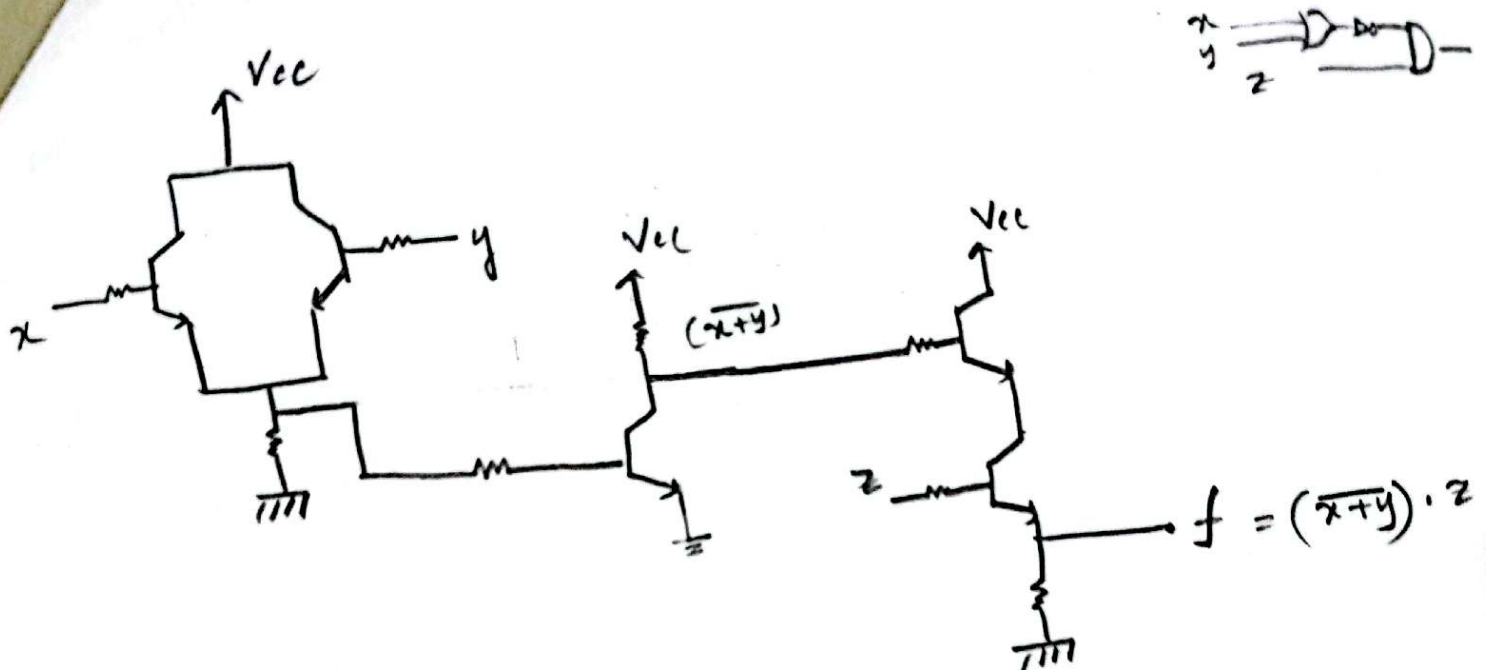10. Draw a circuit using BJTs that implements the following logic function,  $f = (\overline{x+y}).z$   
Answer:



11. Suppose, a BJT is operating in the active region where,  $I_B = 0.01\text{mA}$ . If  $\beta = 100$ , find the value of  $I_C$  and  $I_E$ .  
Answer:

$$\beta = 100$$

$$\Rightarrow \frac{I_C}{I_B} = 100$$

$$\Rightarrow I_C = (100 \times 0.01)$$

$$\therefore I_C = 1\text{mA}$$

$$\therefore I_E = I_B + I_C = (0.01 + 1) = 1.01\text{mA}$$