

set-01


① @

Region

Model

Parameter

AB

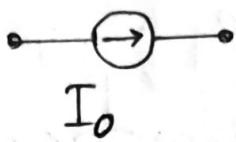

$$I_o = -4 \text{ mA. (Ans)}$$


BC



$$R = \frac{1}{m} = \frac{1}{\frac{\Delta y}{\Delta x}} = \frac{1}{\frac{(4 - (-4)) \times 10^{-3}}{2 - (-2)}}$$

$$\hookrightarrow R = 500 \Omega. \text{ (Ans)}$$

CD

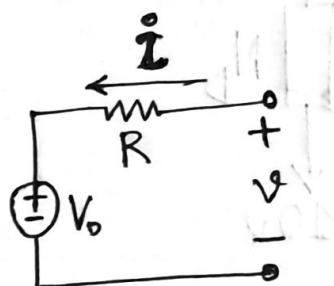

This region can be expressed by $y = mx + c$; $m = 0.3$

$$\therefore R = \frac{1}{0.3} = 3.33 \Omega$$

Again, this region goes through (2, 4) point.

$$\text{So, } 4 \times 10^{-3} = 0.3 \times 2 + c$$

$$\hookrightarrow c = 0.596.$$

We know that,

$$\frac{-V_o}{R} = c$$

$$\hookrightarrow V_o = -R \times c$$

$$\hookrightarrow V_o = -3.33 \times 0.596$$

$$\hookrightarrow V_o = -1.98468 \text{ v. (Ans)}$$


⑥ when, $V_S = 3v$, the operating region is $\rightarrow CD$
 from part-⑤, $y = mx + c$

$$\hookrightarrow i_S = mV_S + c$$


$$\hookrightarrow i_S^o = 0.3 \times 3 + 0.596$$

$$\hookrightarrow i_S^o = 1.496 \text{ A. (Ans)}$$

⑦

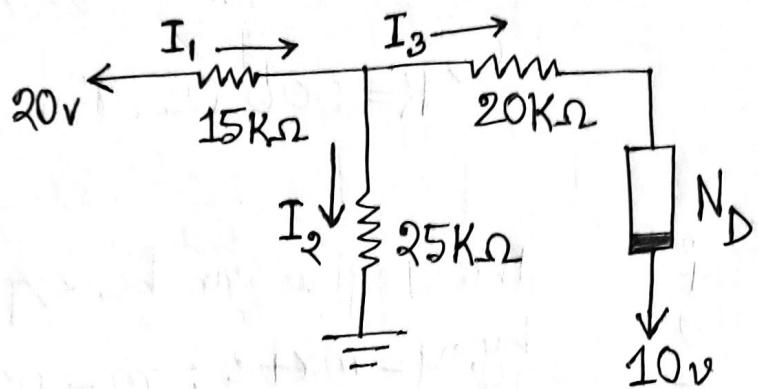

⑧

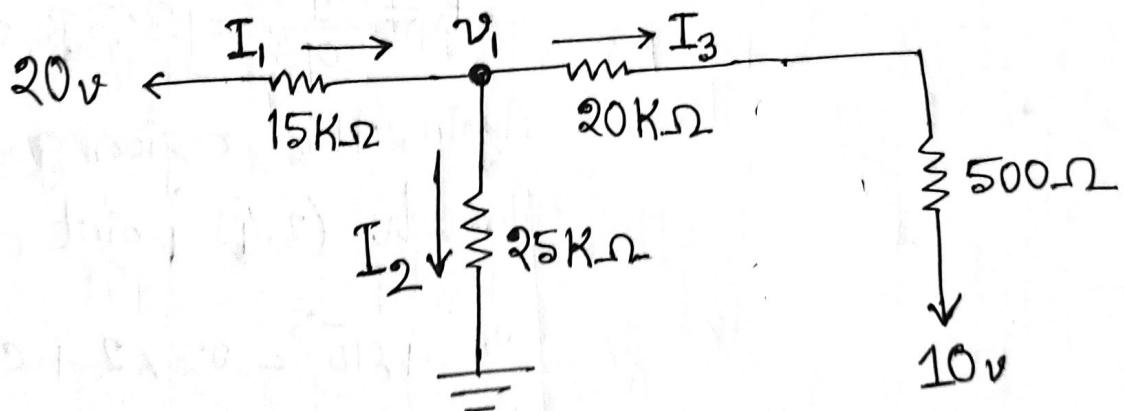

⑨ Applying KCL we get,

$$I_1 = I_2 + I_3$$

$$\hookrightarrow \frac{20 - V_1}{15\text{k}\Omega} = \frac{V_1 - 0}{25\text{k}\Omega} + \frac{V_1 - 10}{(20 + 0.5)\text{k}\Omega} \Rightarrow V_1 = 11.7155v.$$

$$\text{So, } I_1 = \frac{20 - 11.7155}{15\text{k}\Omega} = 0.5523 \text{ mA. (Ans)}$$

$$I_2 = \frac{11.7155 - 0}{25 \text{ k}\Omega} = 0.46862 \text{ mA. (Ans)}$$

$$I_3 = \frac{11.7155 - 10}{(20 + 0.5) \text{ k}\Omega} = 0.0837 \text{ mA. (Ans)}$$

②

Part-a

a) ckt-1: let, the expression be, f_1

$$\text{So, } f_1 = wx. \text{ (Ans)}$$

ckt-2: let, the expression be, f_2

$$\text{So, } f_2 = y + z. \text{ (Ans)}$$

b) from the given ckt, we get,


$$f = f_1 + f_2 = wx + y + z. \text{ (Ans)}$$

Part-b


c) let, the boolean logic function of Juber's algorithm be, J .

$$\therefore J = F \cdot R \cdot (G + N). \text{ (Ans)}$$

d)

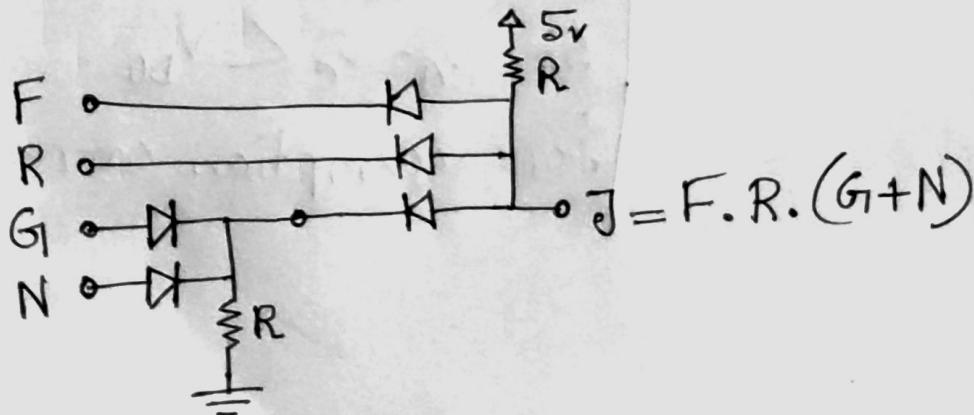

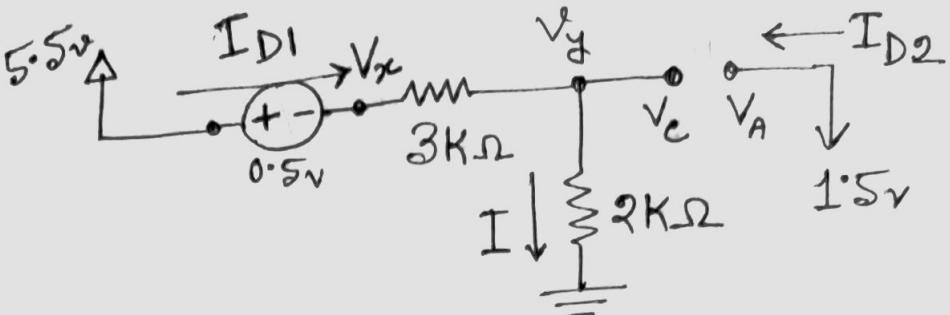③ Let, D_2 off, D_1 ON. So, the circuit will be,



$$\text{here, } V_x = (5.5 - 0.5)V = 5V; I_{D2} = 0.$$

$$\therefore I_{D1} = I$$

$$\hookrightarrow \frac{V_x - 0}{(3+2)k\Omega} = I$$

$$\hookrightarrow \frac{5}{5k\Omega} = I$$

$$\hookrightarrow I = 1mA = I_{D1}.$$

$$\text{Now, } V_c = V_y = (2k\Omega)(I) = 2k\Omega \times 1mA = 2V.$$

for D_1 ,

$$\therefore I_{D1} = 1mA > 0.$$

\therefore Assumption Correct

Again, for D_2 ,

$$V_A - V_c$$

$$= 1.5 - 2$$

$$= -0.5.$$

$$\text{So, } V_A - V_c < V_{D2}$$

So, assumption correct.

④ ① Purpose: Conversion of AC to DC is done using rectifier.

Operation:

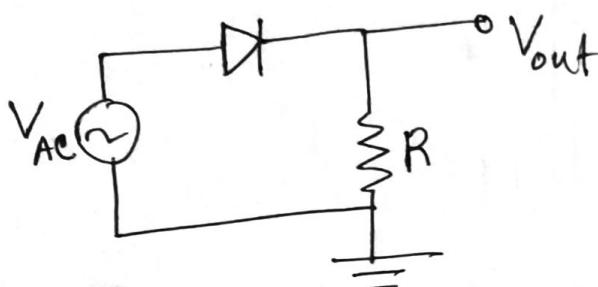


fig: Half-Wave Rectifier

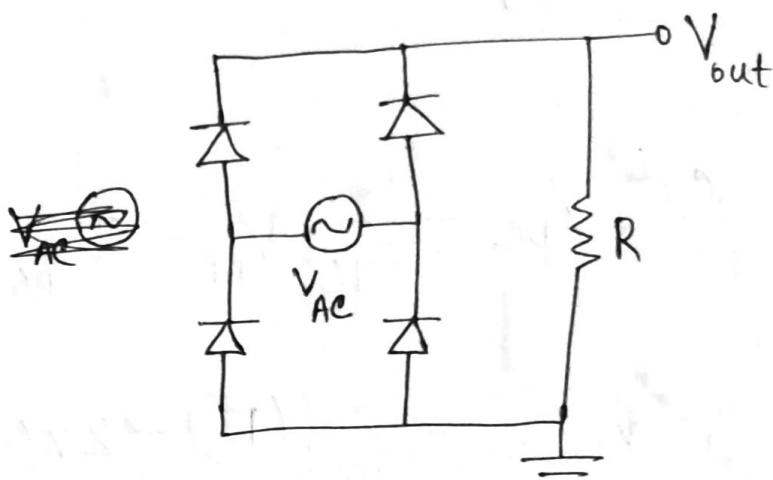


fig: Full-Wave Rectifier

Diode is used to rectify AC. In half-wave rectifier, negative half-cycle of AC voltage gets blocked by the diode. So, we get the positive half-cycle in the output. In full-wave rectifier, both half-cycles can be utilized by connecting the diodes in a smart way which can be seen in the figure above. So we get both half cycles in the output.

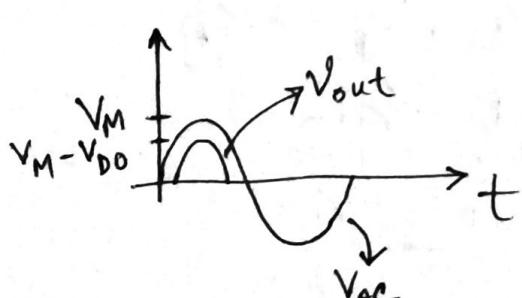


fig: Half-Wave Rectifier


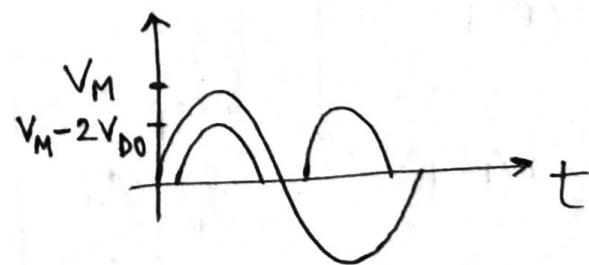


fig: Full-Wave Rectifier

(4)
(b)

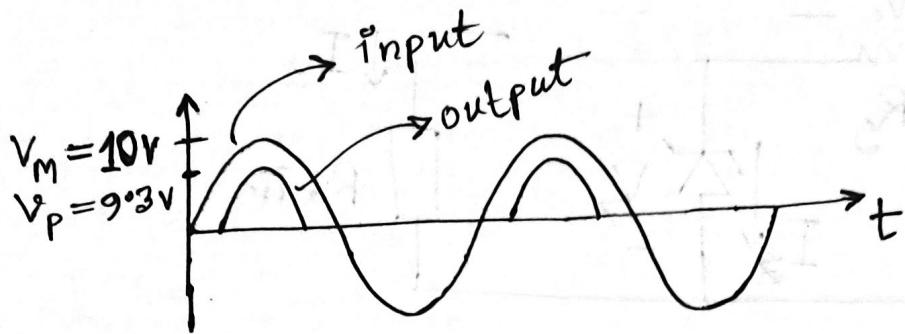

$$\begin{aligned} V_F &= V_M - V_{DO} \\ &= (10 - 0.7)V \\ &= 9.3V \end{aligned}$$

(c) $V_{DC} = \frac{1}{\pi C} V_M - \frac{1}{2} V_{DO}$

$$\hookrightarrow V_{DC} = \frac{1}{\pi C} \times 10 - \frac{1}{2} \times 0.7$$

$$\hookrightarrow V_{DC} = 2.833V. \text{ (Ans)}$$

(d) $V_{out} = (V_{DC} \pm 0.2)V$.

$$So, V_{r(p-p)} = V_{out, max} - V_{out, min} = (V_{DC} + 0.2) - (V_{DC} - 0.2)$$

$$\hookrightarrow V_{r(p-p)} = 0.4V. \text{ (Ans)}$$

~~(e)~~ Again, $V_{r(p-p)} = \frac{V_P}{f_r R C}$

$$\hookrightarrow 0.4 = \frac{9.3}{60 \times 2 \times 10^3 \times C}$$

$$\hookrightarrow C = 193.75 \mu F. \text{ (Ans)}$$


(e) $V_{DC} = V_P - \frac{1}{2} V_{r(p-p)}$

$$\hookrightarrow V_{DC} = (9.3 - \frac{1}{2} \times 0.4)V$$

$$\hookrightarrow V_{DC} = 9.1V. \text{ (Ans)}$$

here,
 $V_P = 9.3V$.
 $f_r = f_i = 60Hz$
 $R = 2K\Omega$

(5)

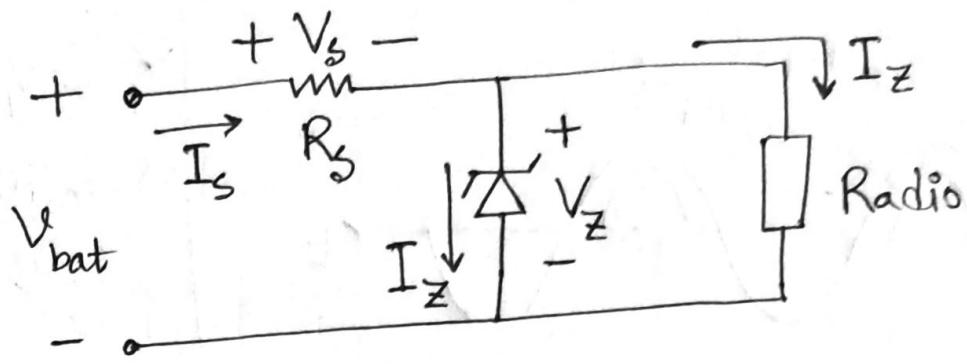

Given that, $V_{bat} = 11v \sim 13.6v$

$$I_L = 6 \sim 9 \text{ mA}$$

$$V_{z0} = 9v, r_z = 0.05 \text{ k}\Omega, I_{zK} = 1 \text{ mA}$$

a) Worst case conditions:

$$\textcircled{1} \quad V_{bat(\min)} = 11v.$$

$$\textcircled{2} \quad \cancel{I_{z(\min)}} = I_{zK} = 1 \text{ mA}.$$

$$\text{So, } I_z = 1 \text{ mA. (Ans)} \quad V_{bat} = 11v. \text{ (Ans)}$$

$$V_z = V_{z0} + I_z r_z$$

$$\hookrightarrow V_z = 9 + 1 \times 10^{-3} \times 0.05 \times 10^3$$

$$\hookrightarrow V_z = 9.05v. \text{ (Ans)}$$

$$I_L = I_{L(\max)} = 9 \text{ mA.}$$

⑤ Applying KVL we get, $V_{bat} = V_s + V_z$

$$\hookrightarrow V_s = V_{bat} - V_z$$

$$\hookrightarrow V_s = (11 - 9.05)v$$

$$\hookrightarrow V_s = 1.95v. \text{ (Ans)}$$

Applying KCL we get,

$$I_s = I_Z + I_L$$

$$\hookrightarrow I_s = (1+9)mA$$

$$\hookrightarrow I_s = 10 \text{ mA. (Ans)}$$

$$\textcircled{c} \quad R_s = \frac{V_s}{I_s} = \frac{1.95}{10 \times 10^{-3}} = 195\Omega. \text{ (Ans)}$$

Line Regulation,

$$\frac{\Delta V_L}{\Delta V_{bat}} = \frac{r}{r+R}$$

$$= \frac{0.05 \times 10^3}{0.05 \times 10^3 + 195} \text{ v/v}$$

$$= 0.20408 \text{ v/v}$$

$$= 204.08 \text{ mV/V. (Ans)}$$

here,

$$r = r_2 = 0.05 \text{ k}\Omega$$

$$R = R_s = 195\Omega$$


Set-02

① a

Region

AB

Model

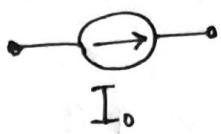

Parameter

$$I_o = -2 \text{ mA. (Ans)}$$

BC




$$R = \frac{1}{m} = \frac{1}{\frac{\Delta y}{\Delta x}}$$

$$\hookrightarrow R = \frac{1}{\frac{(-2-1) \times 10^{-3}}{-4-2}}$$

$$\hookrightarrow R = 1.67 \text{ k}\Omega. (\text{Ans})$$

CD

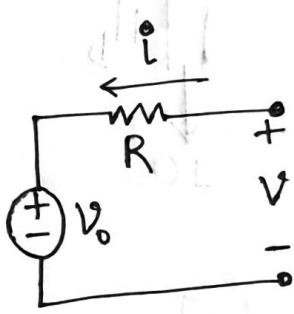

This region can be expressed by, $y = mx + c$; $m = 2$

$$\therefore R = \frac{1}{m} = 0.5 \Omega$$

Again, this region goes through $(2, 1)$ point.

$$\text{So, } 1 \times 10^{-3} = 2 \times 1 + c$$

$$\hookrightarrow c = -1.999.$$

We know that,

$$\frac{-V_o}{R} = c$$

$$\hookrightarrow V_o = -R \times c$$

$$\hookrightarrow V_o = -(0.5) \times (-1.999)$$

$$\hookrightarrow V_o = 0.9995 \text{ v. (Ans)}$$


(b) When, $v_s = 3v$, the operating region is $\rightarrow CD$
 from part-(a), $y = mx + c$

$$\hookrightarrow i_s = m v_s + c$$


$$\hookrightarrow i_s = 2 \times 3 + (-1.999)$$

$$\hookrightarrow i_s = 4.001 \text{ A. (Ans)}$$

(c)

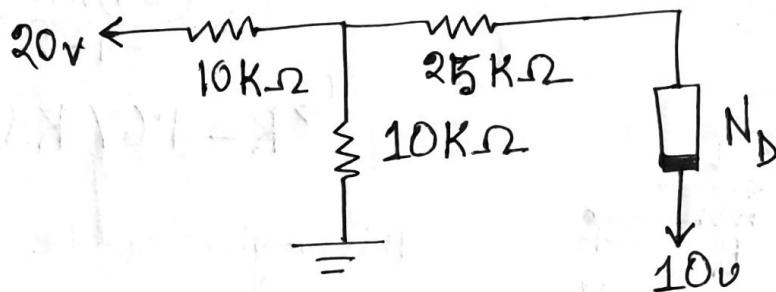

(d)

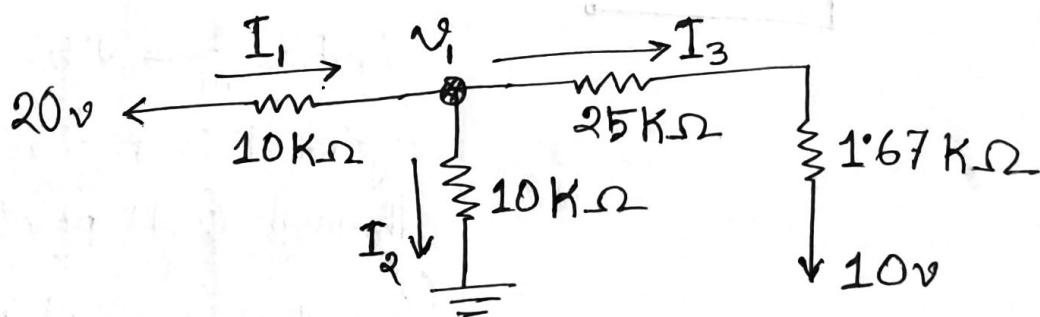

(e)

Applying KCL we get,

$$I_1 = I_2 + I_3$$

$$\hookrightarrow \frac{20 - v_i}{10 \text{ k}\Omega} = \frac{v_i - 0}{10 \text{ k}\Omega} + \frac{v_i - 10}{(25 + 1.67) \text{ k}\Omega}$$

$$\hookrightarrow v_i = 10 \text{ V.}$$

$$\text{So, } I_1 = \frac{20 - 10}{10 \text{ k}\Omega} = 1 \text{ mA. } I_2 = \frac{10 - 0}{10 \text{ k}\Omega} = 1 \text{ mA. } I_3 = \frac{10 - 10}{26.67 \text{ k}\Omega} = 0.$$

(2)

Part-a

a) ckt-1: let the expression be, f_1 .

$$\text{So, } f_1 = wx. \text{ (Ans)}$$

ckt-2: let the expression be, f_2 .

$$\text{So, } f_2 = y+z. \text{ (Ans)}$$

b) from the given ckt, we get,


$$f = f_1 f_2 = (wx)(y+z). \text{ (Ans)}$$

Part-b


c) ~~Ex~~ let, the boolean logic function of Juber's algorithm be, J .

$$\therefore J = F.R.(G+N). \text{ (Ans)}$$

(d)

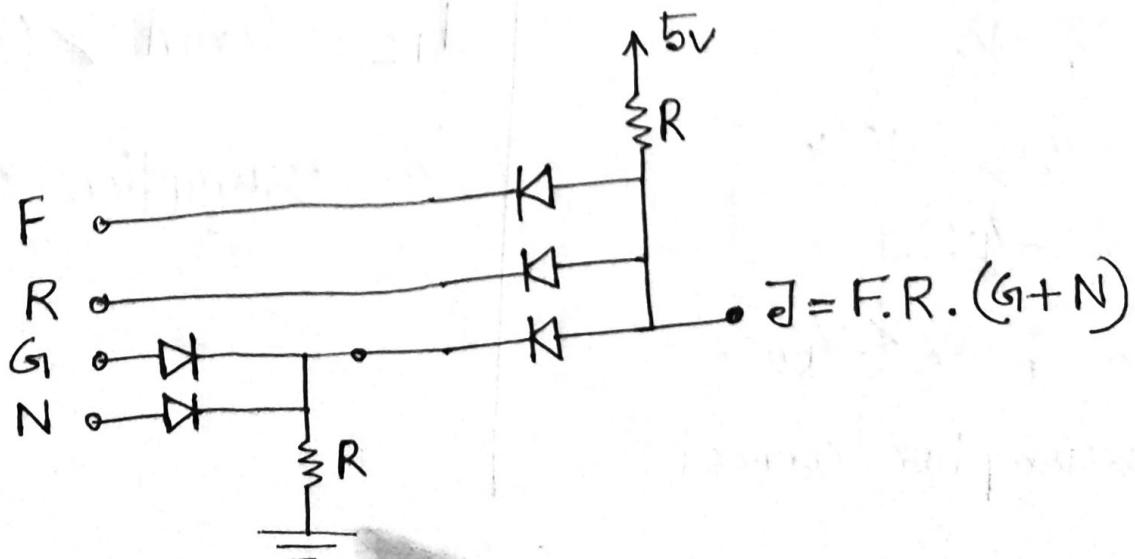

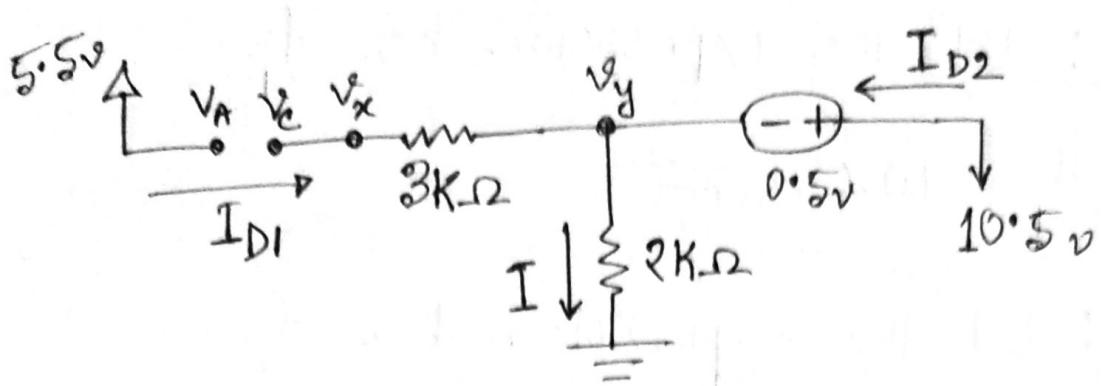③ let, D_1 off, D_2 ON. So, the circuit will be,



$$\text{here, } V_y = (10.5 - 0.5)v = 10v; I_{D1} = 0.$$

$$\therefore I = I_{D2}$$

$$\hookrightarrow \frac{V_y - 0}{2k\Omega} = I_{D2}$$

$$\hookrightarrow I_{D2} = \frac{10 - 0}{2k\Omega}$$

$$\hookrightarrow I_{D2} = 5 \text{ mA.}$$

$$V_c = V_x = V_y = 10v.$$

Now, for D_1 ,

$$\begin{aligned} & V_A - V_c \\ &= (5.5 - 10)v \\ &= -4.5v. \end{aligned}$$

$\therefore V_A - V_c < V_{D1},$
assumption correct

Again, for D_2 ,

$$I_{D2} = 5 \text{ mA} > 0.$$

So, assumption correct.

④ a) Purpose: Conversion of AC to DC is done using rectifier.

Operation:

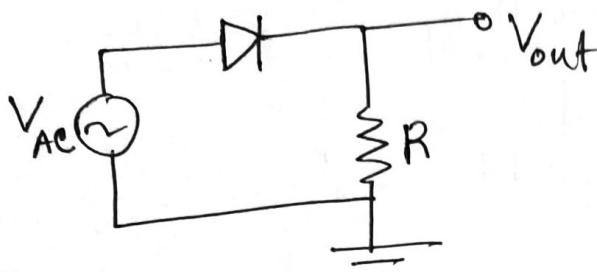


fig: Half-Wave Rectifier

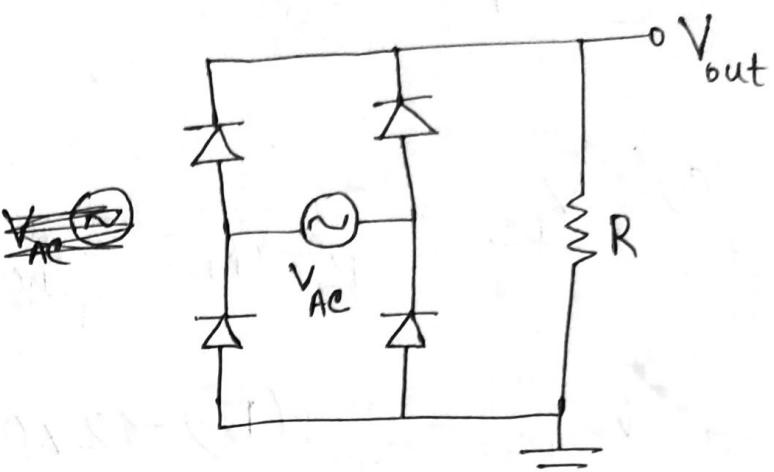


fig: Full-Wave Rectifier

Diode is used to rectify AC. In half-wave rectifier, negative half-cycle of AC voltage gets blocked by the diode. So, we get the positive half-cycle in the output. In full-wave rectifier, both half-cycles can be utilized by connecting the diodes in a smart way which can be seen in the figure above. so we get both half cycles in the output.

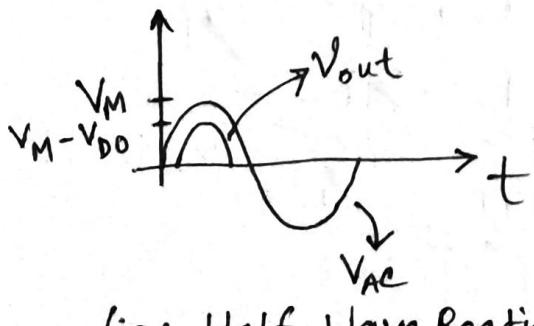


fig: Half-Wave Rectifier


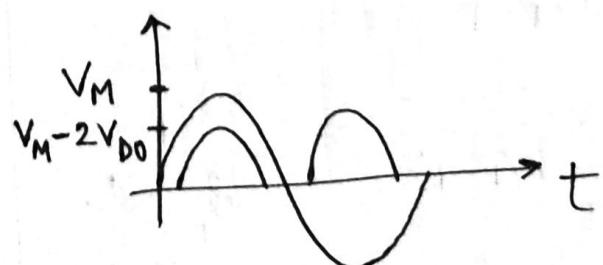


fig: Full-Wave Rectifier

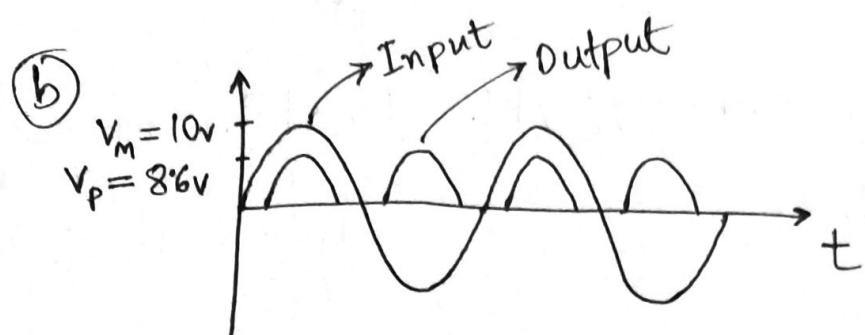

$$\begin{aligned}
 V_P &= V_M - 2V_{DO} \\
 &= (10 - 2 \times 0.7)V \\
 &= 8.6V
 \end{aligned}$$

(c) $V_{DC} = \frac{2}{TC} V_M - 2V_{DO}$

$$\hookrightarrow V_{DC} = \frac{2}{TC} (10) - 2 \times 0.7$$

$$\hookrightarrow V_{DC} = 4.9662V. \quad (\text{Ans})$$

$$④ ① V_{\text{out}} = (V_{\text{DC}} \pm 0.2)v$$

$$\therefore V_{r(\text{P-P})} = V_{\text{out, max}} - V_{\text{out, min}}$$

$$\hookrightarrow V_{r(\text{P-P})} = (V_{\text{DC}} + 0.2) - (V_{\text{DC}} - 0.2)$$

$$\hookrightarrow V_{r(\text{P-P})} = 0.4v \ . (\text{Ans})$$

Again, $V_{r(\text{P-P})} = -\frac{V_p}{f_p RC}$

$$\hookrightarrow 0.4 = \frac{8.6}{2 \times 60 \times 2 \times 10^3 \times C}$$

$$\hookrightarrow C = 89.583 \mu\text{F.} (\text{Ans})$$


here,
$V_p = 8.6 v$
$f_p = 2f_i = 2 \times 60 \text{ Hz}$
$R = 2 \text{ K}\Omega$

$$④ ② V_{\text{DC}} = V_p - \frac{1}{2} V_{r(\text{P-P})}$$

$$\hookrightarrow V_{\text{DC}} = (8.6 - \frac{1}{2} \times 0.4)v$$

$$\hookrightarrow V_{\text{DC}} = 8.4v \ . (\text{Ans})$$

Q5

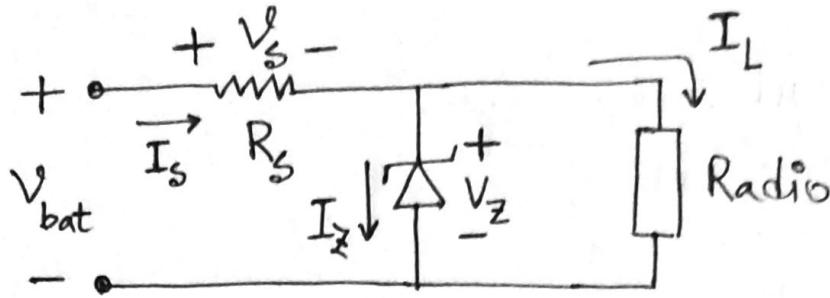

Given that, $V_{bat} = 11v \sim 13.6v$

$$I_L = 0 \sim 9 \text{ mA}$$

$$V_{z0} = 9v, r_z = 0.05 \text{ k}\Omega, I_{zK} = 1 \text{ mA}$$

~~(a)~~ @ Worst case conditions:

$$\textcircled{1} \quad V_{bat(\min)} = 11v.$$

$$\textcircled{2} \quad I_{z(\min)} = I_{zK} = 1 \text{ mA}.$$

$$\text{So, } I_z = 1 \text{ mA. (Ans)} \quad V_{bat} = 11v. \text{ (Ans)}$$

$$V_z = V_{z0} + I_z r_z$$

$$\hookrightarrow V_z = 9 + 1 \times 10^{-3} \times 0.05 \times 10^3$$

$$\hookrightarrow V_z = 9.05v. \text{ (Ans)}$$

$$I_L = I_{L(\max)} = 9 \text{ mA. (Ans)}$$

$$\textcircled{b} \quad \text{Applying KVL we get, } V_{bat} = V_s + V_z$$

$$\hookrightarrow V_s = V_{bat} - V_z$$

$$\hookrightarrow V_s = (11 - 9.05)v$$

$$\hookrightarrow V_s = 1.95v. \text{ (Ans)}$$

Applying KCL we get,

$$I_s = I_Z + I_L$$

$$\hookrightarrow I_s = (1 + g) \text{ mA}$$

$$\hookrightarrow I_s = 10 \text{ mA. (Ans)}$$

(c) $R_s = \frac{V_s}{I_s} = \frac{1.95}{10 \times 10^{-3}} = 195 \Omega. \text{ (Ans)}$

Load Regulation,

$$\frac{\Delta V_L}{\Delta I_L} = \frac{-rR}{r+R}$$

$$= \frac{-(0.05 \times 10^3 \times 195)}{(0.05 \times 10^3 + 195)} \text{ mV/mA}$$

$$= -39.796 \text{ mV/mA. (Ans)}$$

here, $r = r_Z = 0.05 \text{ k}\Omega$
 $R = R_s = 195 \Omega$