

# **CSE 251: Electronic Devices and Circuits**

## **Lecture 1**

### **Alt. Representation, CSE250 Review, IV Characteristics**

Prepared by:

Yeasin Arafat Pritom (YAP)

Lecturer, Dept. of CSE, School of Data and Sciences

Email: [yeasin.pritom@bracu.ac.bd](mailto:yeasin.pritom@bracu.ac.bd)

# Outline

- Alternative Circuit Representation – Line diagrams
- CSE250 Review
  - KCL, KVL
  - Series, Parallel resistor network – Voltage Division, Current division
  - Examples
- IV Characteristics
  - Linear IV – Resistors, Voltage Source, Current Source, SC, OC.
  - Non-Linear IV – Piecewise Linear Model


# Alternative Circuit Representation: Line diagrams

Steps to decompose circuits to line diagram



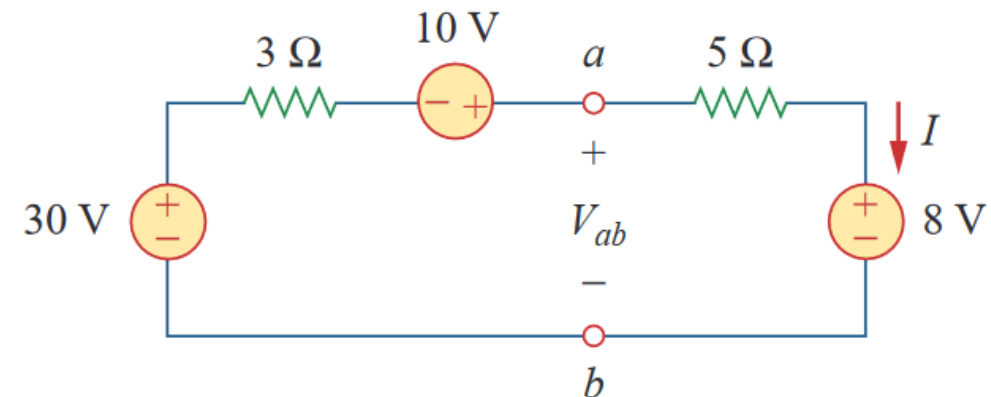
1. Set a ground so that number of **floating voltage** sources are minimized.
2. Detach the ground **from the voltage source**.
3. Convert the non-floating voltage sources (~~current sources~~) into:
  - Arrow : ( $\rightarrow$ ) **Fixed/Constant voltage source**
4. Keep passive elements as they are.

**Floating voltage** sources:




Voltage sources which are **not connected the ground** terminal. In the diagram, the **10 V** voltage source is floating



# Line diagrams: Example 1

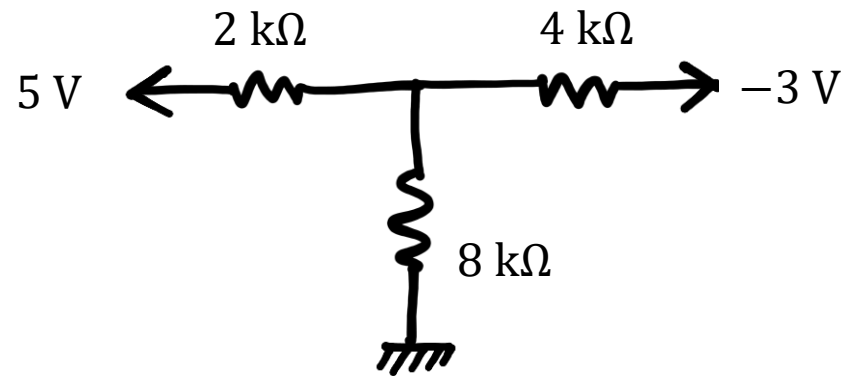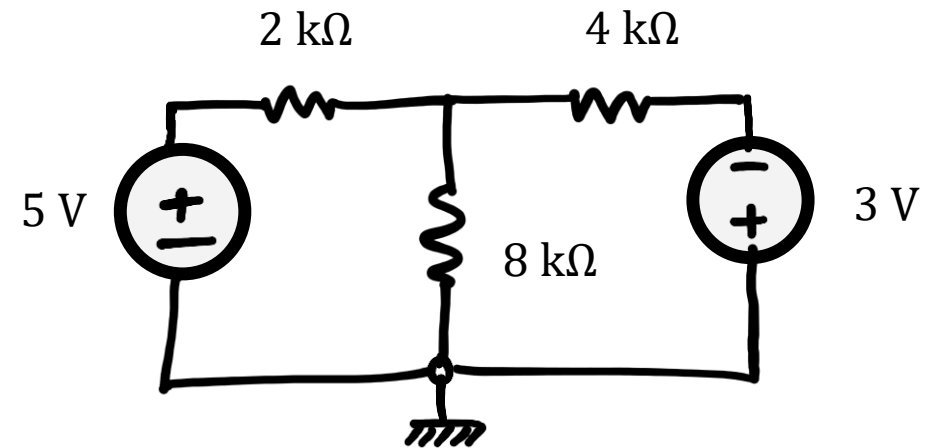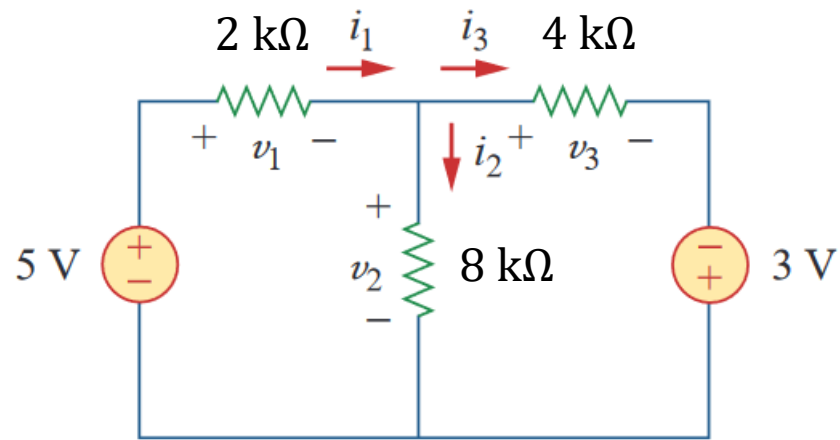


# Line diagrams: Example 2

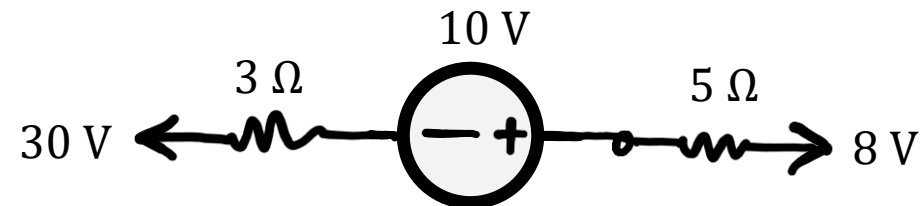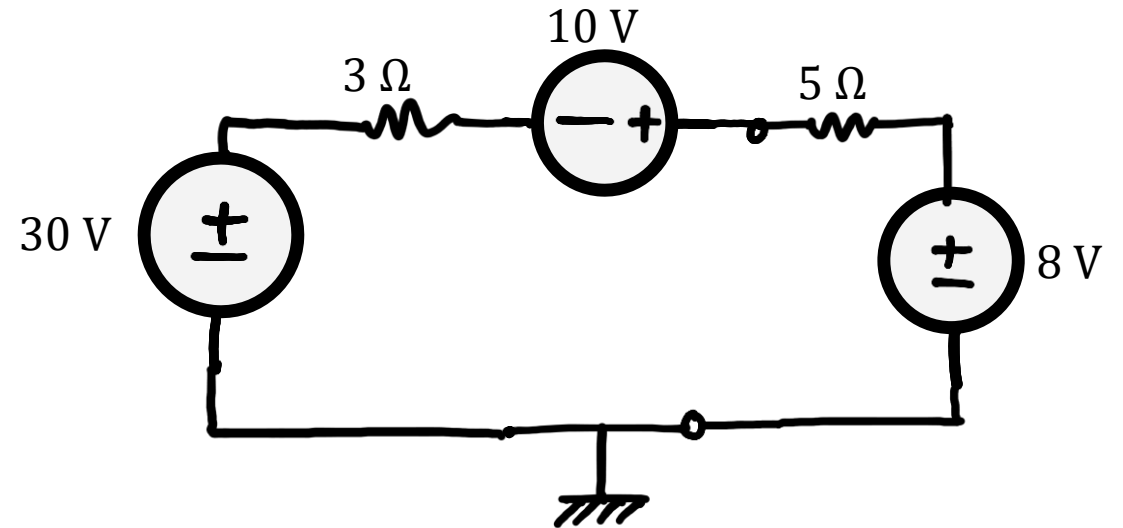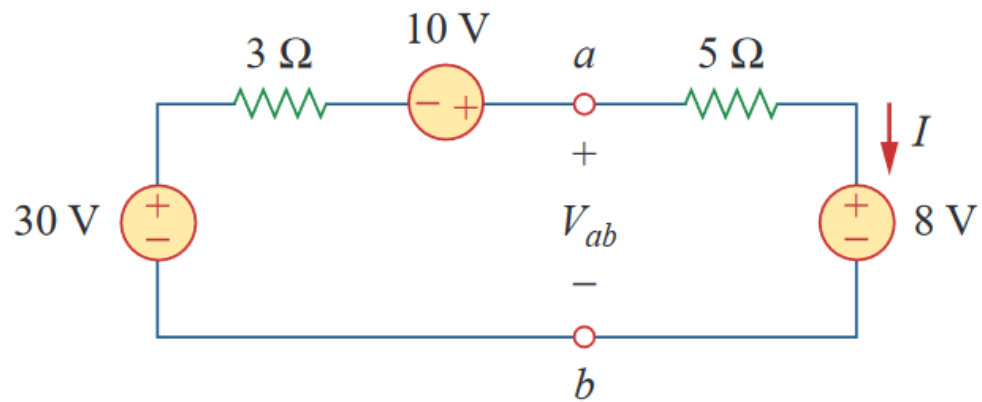


# More Examples

Difficulty : 2/5

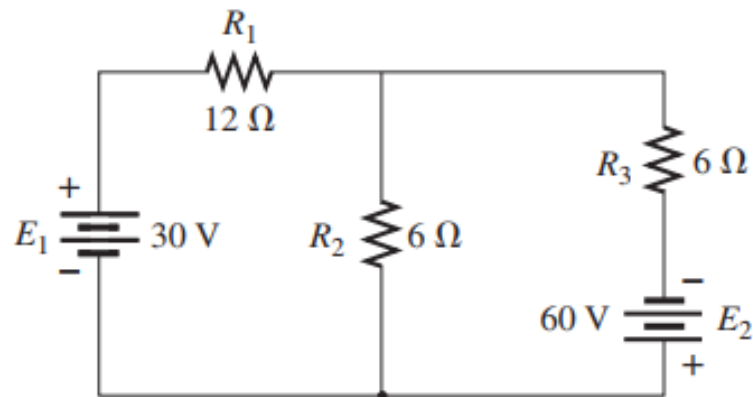

Example: 2


Difficulty : 3/5

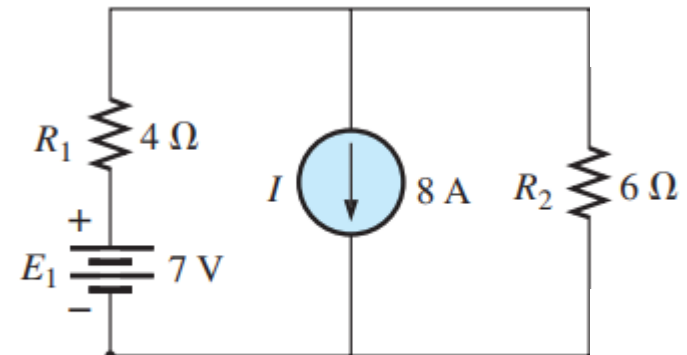

Example: 3

# More Examples

Difficulty : 4/5

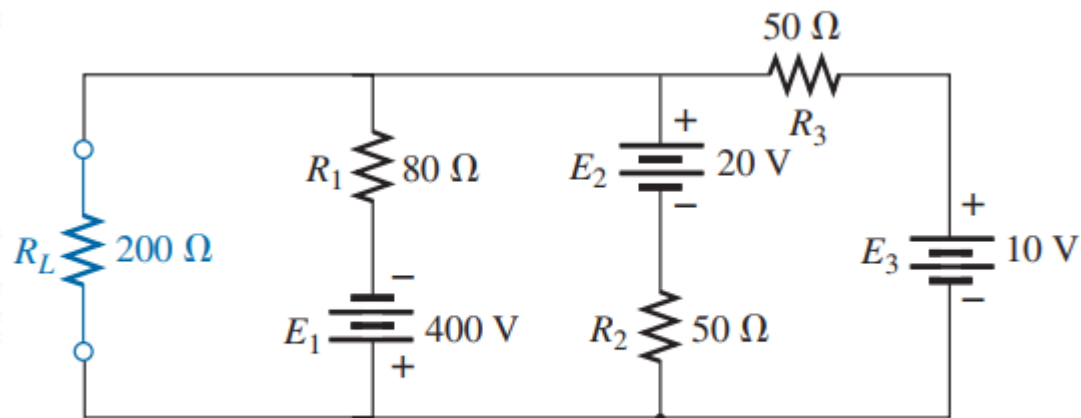

Example: 4

Step – (4) Make all the active elements (dc/ac type, voltage/~~current~~ sources) into single terminals (arrows/circles) using the voltages you wrote as much as you can **[THERE MIGHT BE CASES WHERE YOU CAN'T DO THAT]**


# The fundamentals ...

## Ohm's Law –

- the voltage  $v$  across a resistor is **directly proportional** to the current  $i$  flowing through the resistor ( $R$ )

$$v \propto i$$

$$v = iR$$

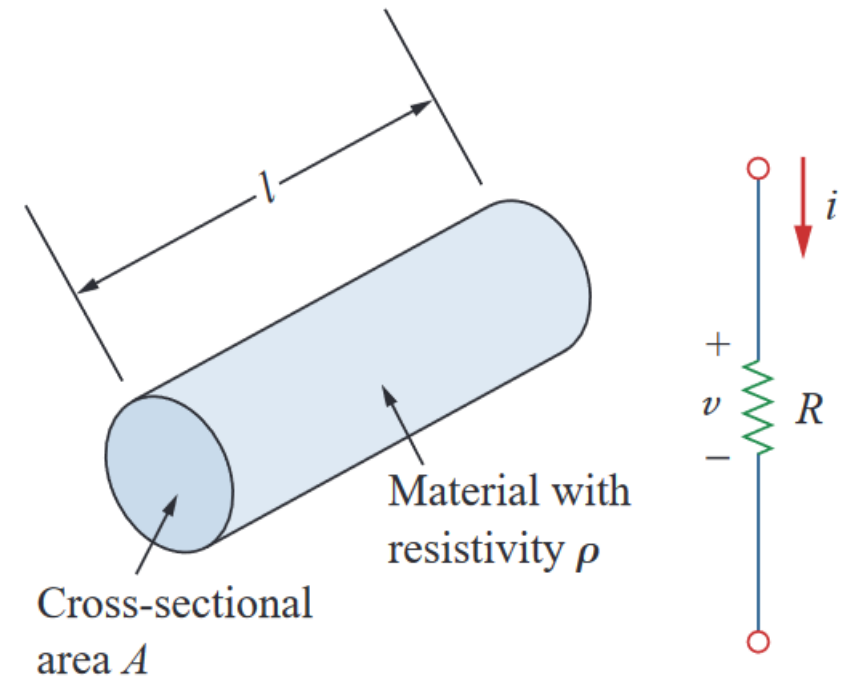




# KVL: Kirchhoff's voltage law

The algebraic sum of all **voltages** around **a closed path (or loop)** is zero.

$$-v_1 + v_2 + v_3 - v_4 + v_5 = 0$$

$$v_2 + v_3 + v_5 = v_1 + v_4$$

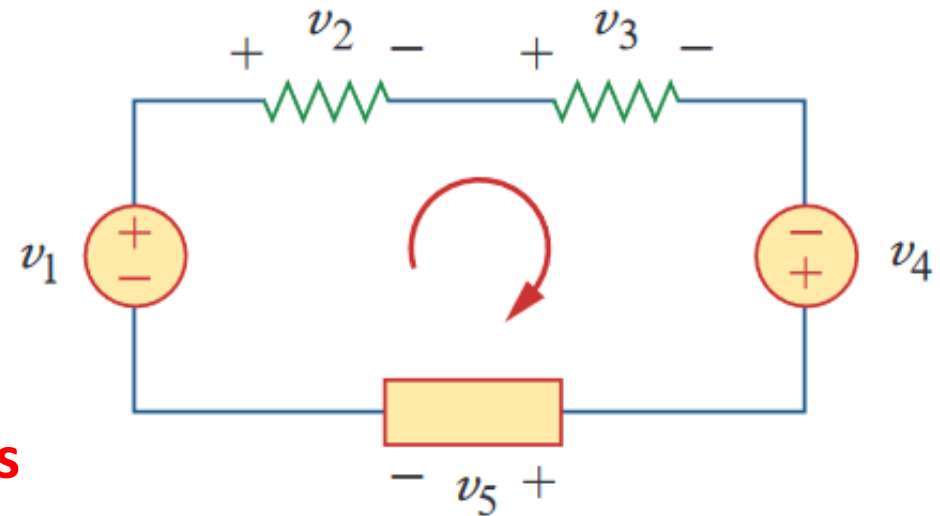
Sum of voltage drops = **Sum of voltage rises**



# KVL: Kirchhoff's voltage law

$$-V_{ab} + V_1 + V_2 - V_3 = 0$$

$$V_{ab} = V_1 + V_2 - V_3$$

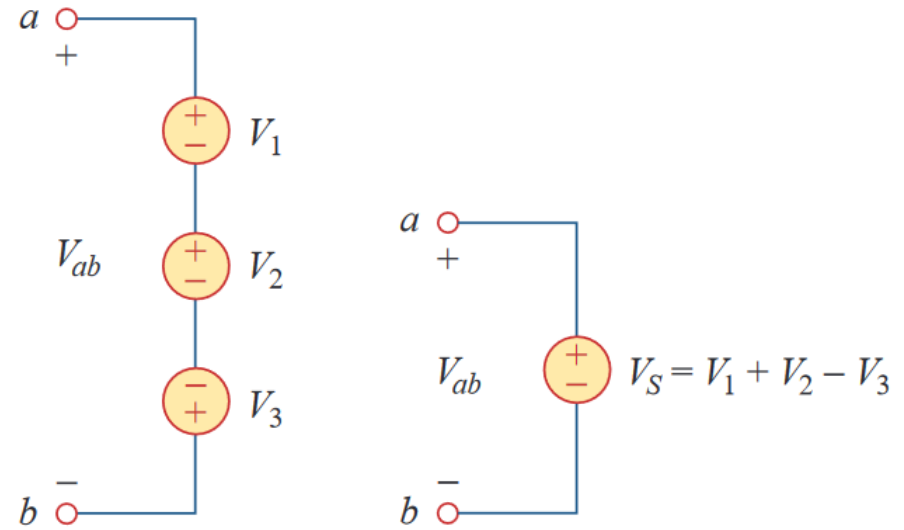

Equivalent Circuits

# KVL – Example 1

Find  $I$  and  $V_{ab}$  in the circuit

**Solution:**

KVL


$$-30 + 3I - 10 + 5I + 8 = 0$$

$$I = \frac{32}{8} \text{ A} = 4 \text{ A}$$

KVL

$$-V_{ab} + 5I + 8 = 0$$

$$V_{ab} = 28 \text{ V}$$

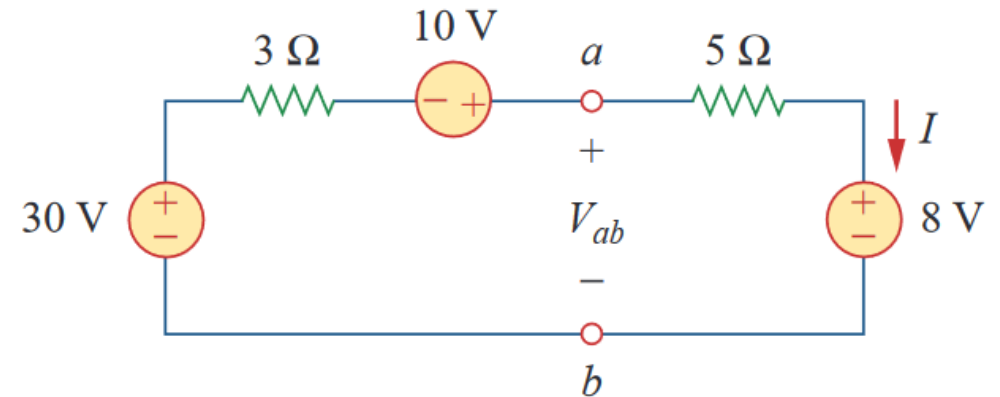

**Tip:** If you find resistance values in **kΩ** instead of **Ω**, don't convert the **kΩ** values to **Ω**. Just find currents in **mA** instead of **A**.

# KVL – Example 2

Find  $v_1, v_2, v_3, i_1, i_2$  and  $i_3$  in the circuit

## Solution:

KVL in first loop

$$-5 + 2i_1 + 8(i_1 - i_3) = 0$$

$$10i_1 - 8i_3 = 5$$

KVL in second loop

$$-8(i_1 - i_3) + 4i_3 - 3 = 0$$

$$-8i_1 + 12i_3 = 3$$

Solving:

$$i_1 = 1.5 \text{ mA}$$


$$i_3 = 1.25 \text{ mA}$$

$$i_2 = i_1 - i_3 = 0.25 \text{ mA}$$

$$v_1 = 3 \text{ V}$$

$$v_2 = 2 \text{ V}$$

$$v_3 = 5 \text{ V}$$

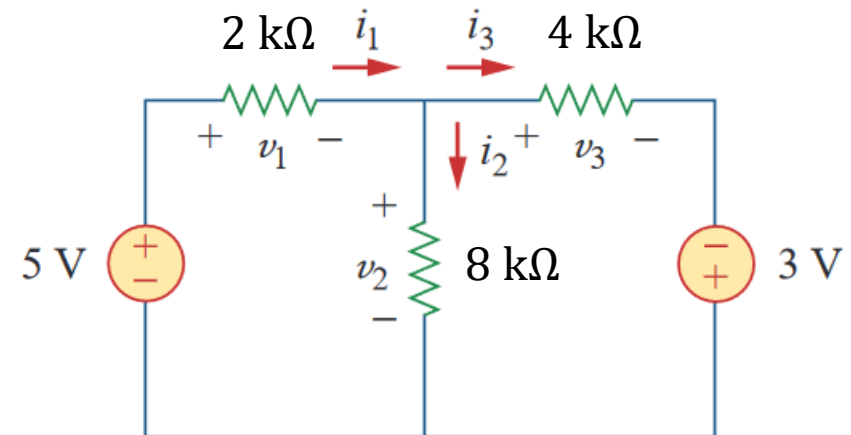

**Tip:** If you find resistance values in **kΩ** instead of **Ω**, don't convert the **kΩ** values to **Ω**. Just find currents in **mA** instead of **A**.


# KCL: Kirchhoff's Current Law

The algebraic sum of the **currents** entering a **node (closed boundary)** is equal to the sum of the currents leaving the node.

$$i_1 + (-i_2) + i_3 + i_4 + (-i_5) = 0$$

Current Entering node: **Positive**  
Current Exiting node: **Negative**

Or vice versa...

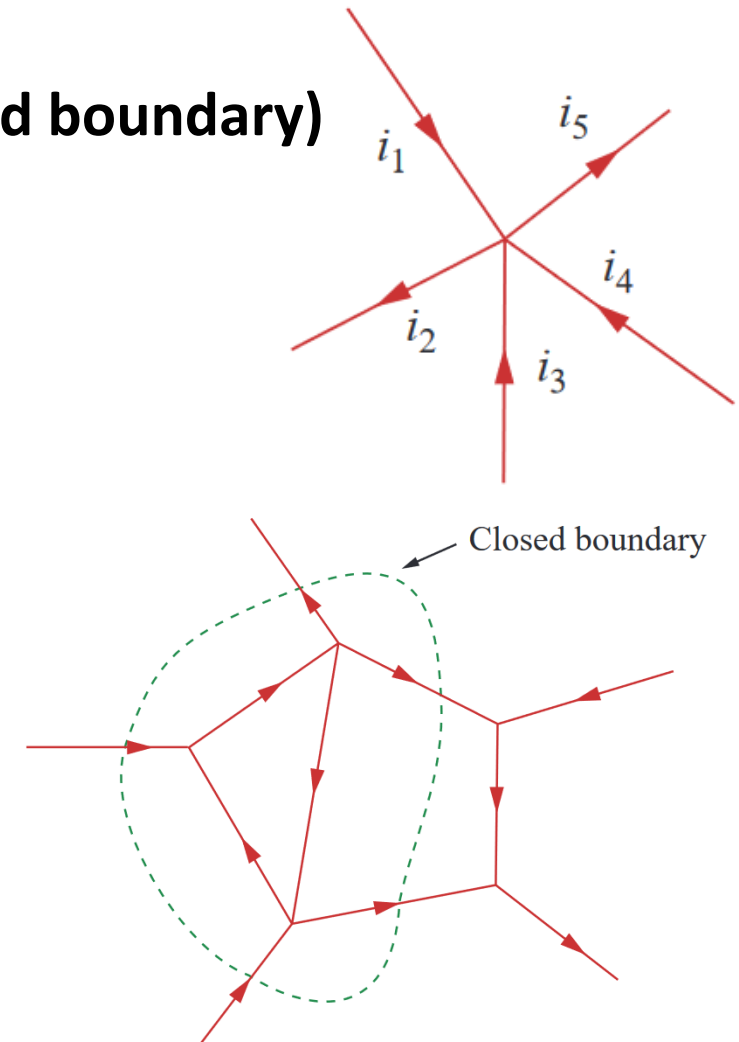

# KCL- Example 1

Find  $v_1, v_2, v_3, i_1, i_2$  and  $i_3$  in the circuit

**Solution:**

KCL in node  $v_a$ . (PS:  $v_a = v_2$ )


$$\frac{5 - v_2}{2} - \frac{v_2 - (-3)}{4} - \frac{v_2 - 0}{8} = 0$$

$$v_2 \left( -\frac{1}{2} - \frac{1}{4} - \frac{1}{8} \right) = -\left( \frac{5}{2} - \frac{3}{4} \right)$$

$$v_2 = \frac{7}{4} \cdot \frac{8}{7} \text{ V} = 2 \text{ V}$$

$$v_1 = 5 - v_2 = 3 \text{ V}$$


$$v_3 = v_2 - (-3) = 5 \text{ V}$$

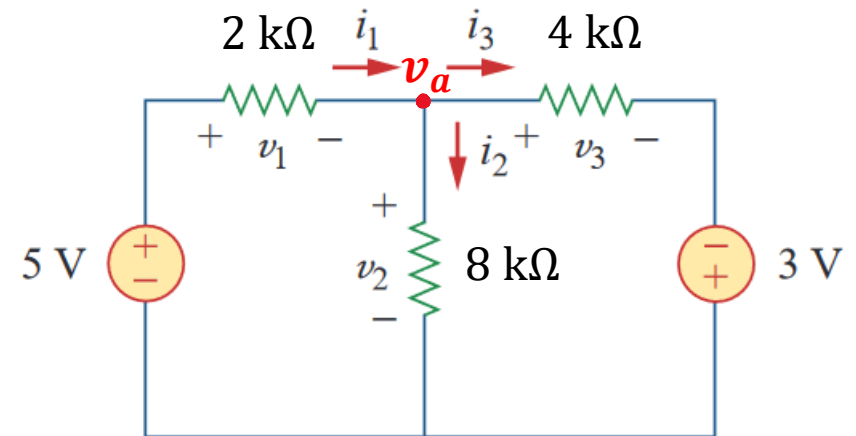


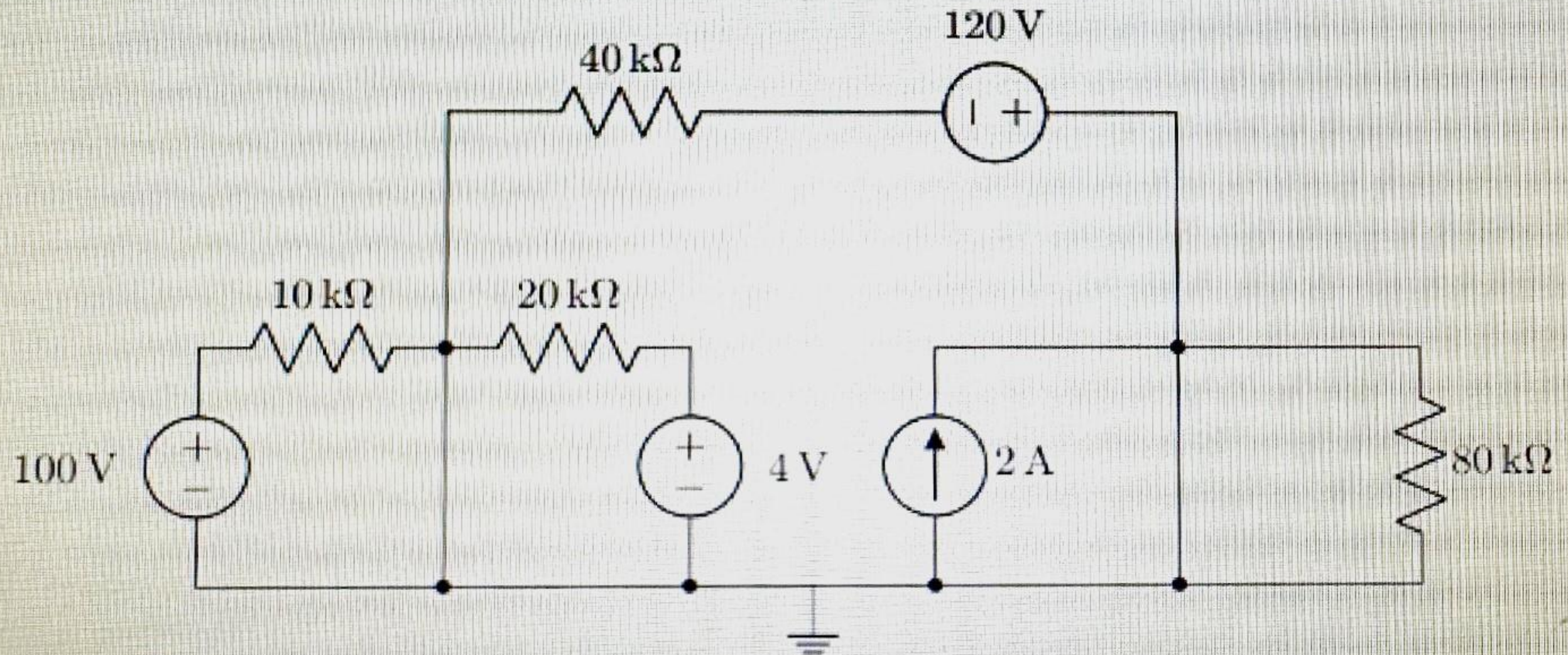
# Problem 6

- Determine the number of **nodes** and **meshes** in the following circuit.




# Series Resistors and Voltage Division

The **equivalent resistance** of any number of resistors connected in **series** is the sum of the individual resistances.
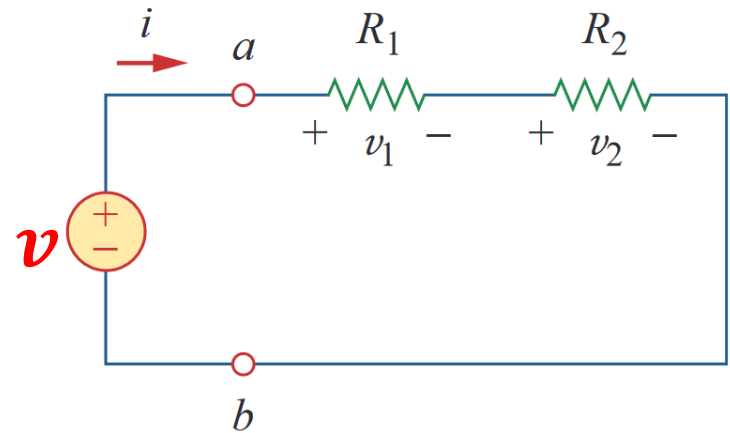
## Principle of voltage division


**Source voltage**  $v$  - is divided among the resistors in direct proportion to their resistances; the larger the resistance, the larger the voltage drop.



$$v_1 = \frac{R_1}{R_1 + R_2} v \quad v_2 = \frac{R_2}{R_1 + R_2} v$$



# Line diagram: Example 3

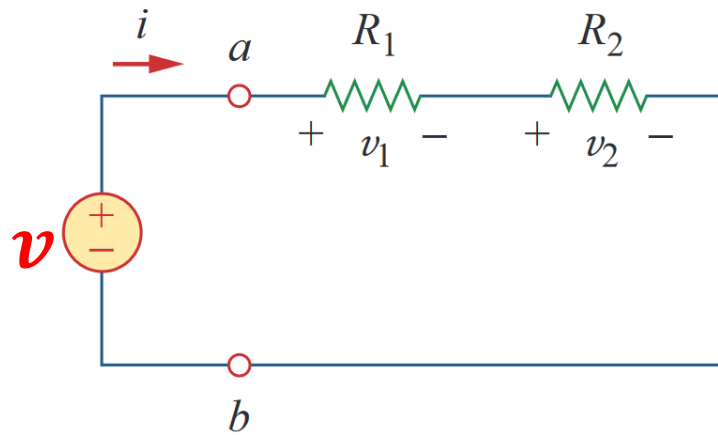

$$v_2 = \frac{R_2}{R_1 + R_2} v$$


A diagram illustrating the voltage divider principle. It shows two resistors,  $R_1$  and  $R_2$ , connected in series. The total voltage  $v$  is applied across the series combination. The voltage  $v_2$  is the voltage across  $R_2$ . The diagram shows  $R_1$  at the top and  $R_2$  at the bottom, with a ground symbol at the bottom. Brackets indicate the voltage across each resistor:  $\left\{ \frac{R_1}{R_1 + R_2} v \right\}$  for  $R_1$  and  $\left\{ \frac{R_2}{R_1 + R_2} v \right\}$  for  $R_2$ .

# Series Resistors and Voltage Division



- If there are  $N$  resistors in series, the voltage across the  $i$ –th resistor is given by,

As  $V \propto R$

$$v_i = \frac{R_i}{\sum_i R_i} v_{in}$$

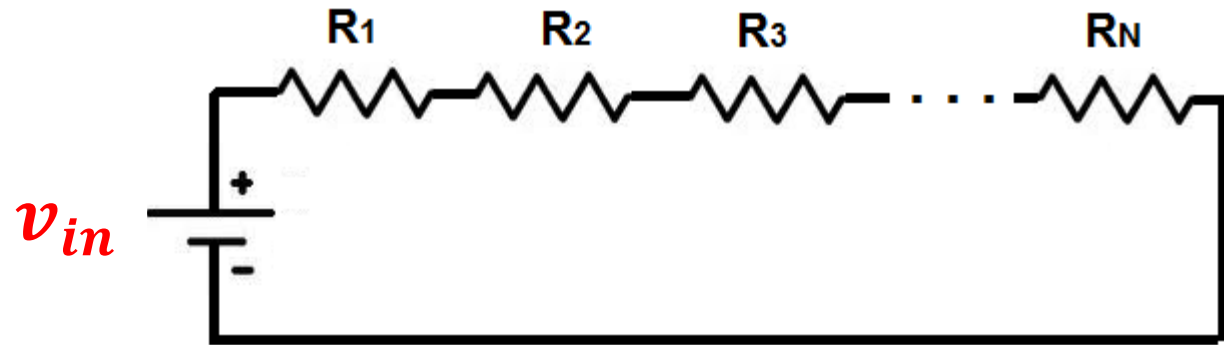

# Line diagram: Example 3

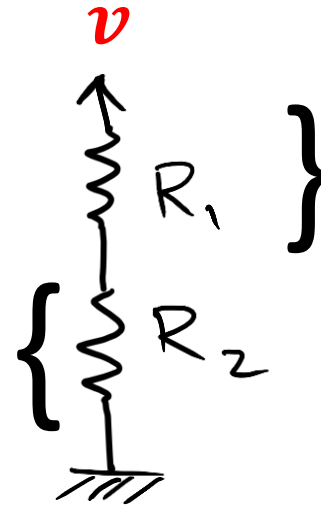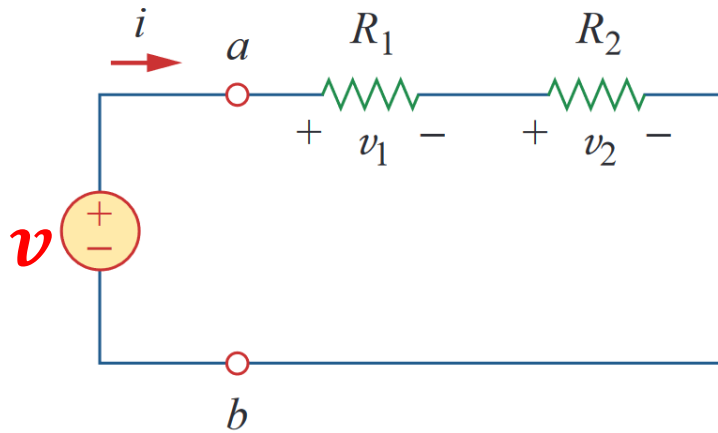


KVL (acts along a line instead of a loop)

$$v - iR_1 - iR_2 = 0$$
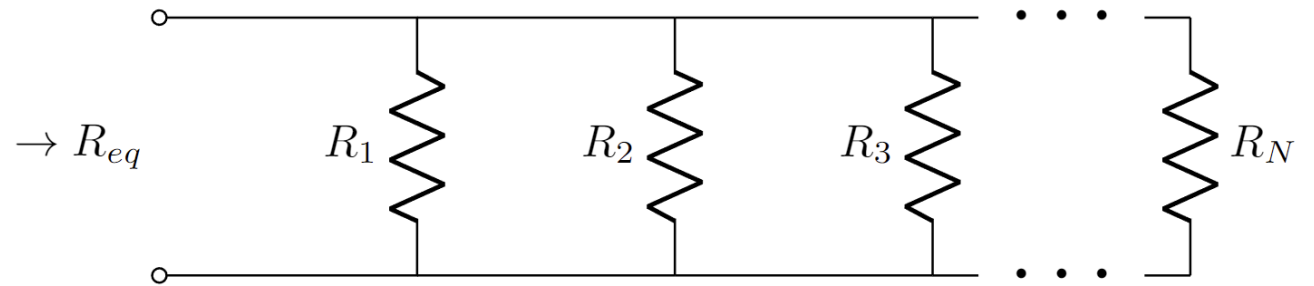
# Parallel Resistors and Current Division

The **equivalent resistance** of any number of resistors connected in **parallel** is the inverse of the sum of the individual conductances.

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \cdots \frac{1}{R_N}$$



Simplification for the case when  $R_1 = R_2 = R_3 \cdots = R_N$

$$R_{eq} = \frac{R_1}{N}$$


# Parallel Resistors and Current Division

The **equivalent resistance** of any number of resistors connected in **parallel** is the inverse of the sum of the individual conductances.

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \quad R_{eq} = R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

Simplification for the case when  $R_1 = R_2$

$$R_{eq} = \frac{R_1}{2}$$

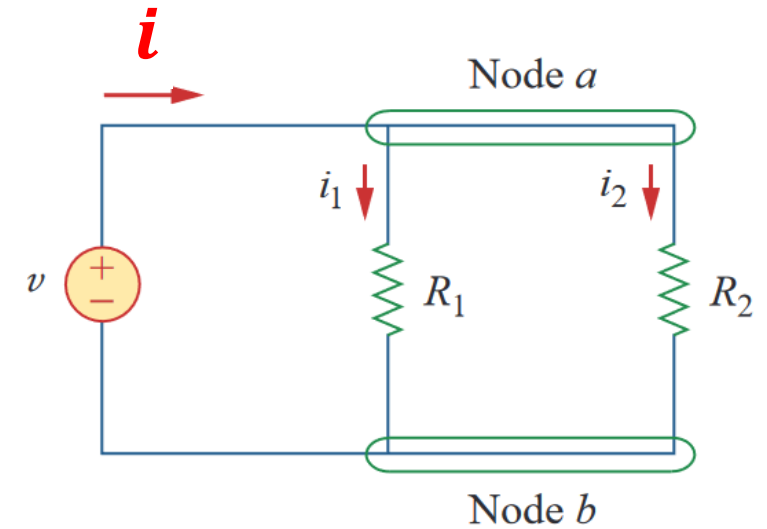


# Parallel Resistors and Current Division

The **equivalent resistance** of any number of resistors connected in **parallel** is the inverse of the sum of the individual conductances.
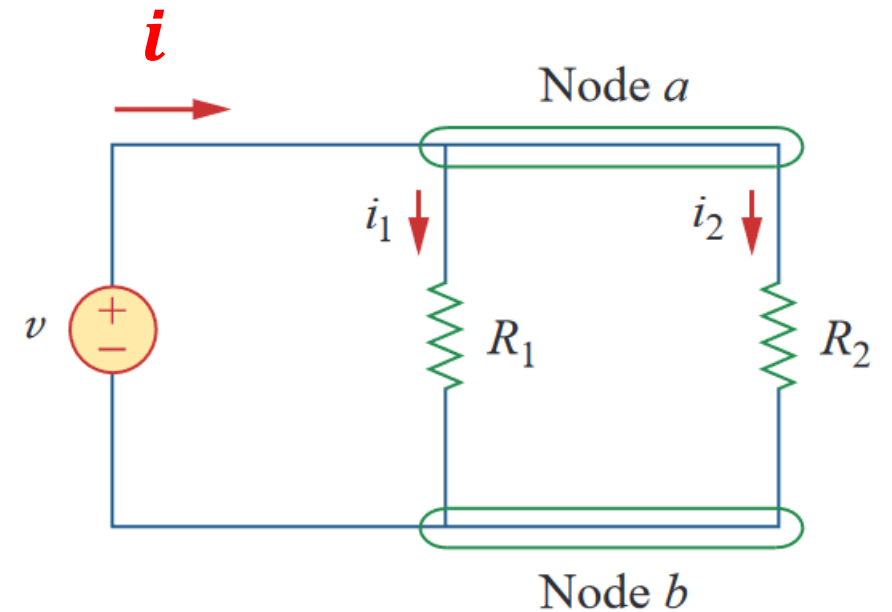
## Principle of current division

**Source current  $i$**  - is divided among the resistors in direct **inverse** proportion to their resistances; the larger the resistance, the larger the voltage drop.

$$i_1 = \frac{1/R_1}{1/R_1 + 1/R_2} i \quad i_2 = \frac{1/R_2}{1/R_1 + 1/R_2} i$$




# Parallel Resistors and Current Division



- If there are  $N$  resistors in parallel, the current through the  $i$ -th resistor is given by,  $i \in \{1, 2, 3, \dots, N\}$

$$\text{As } I \propto \frac{1}{R}$$

$$I_i = \frac{1/R_i}{\sum_i 1/R_i} I_T$$

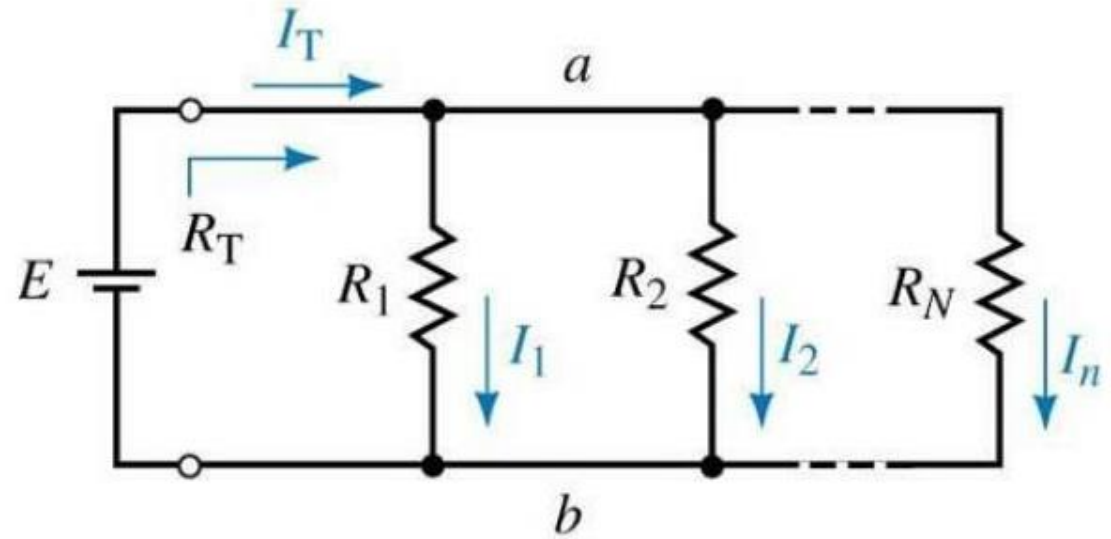

# Line diagrams: Example 4

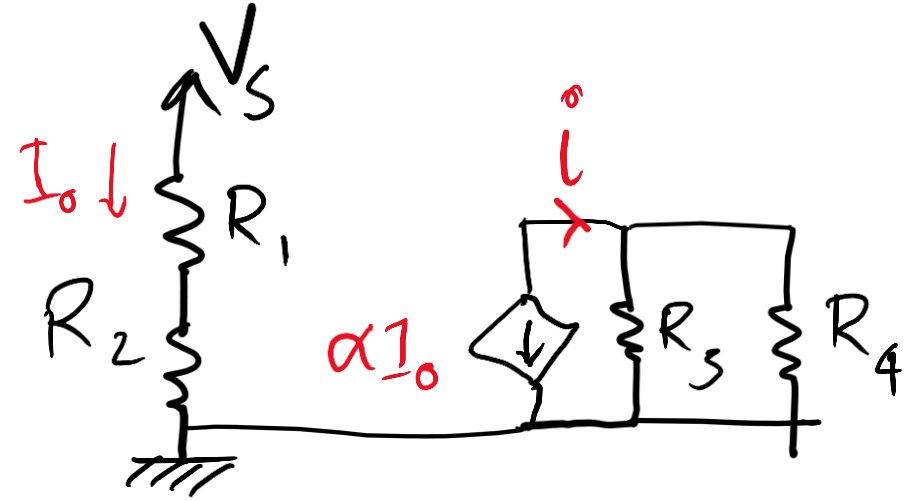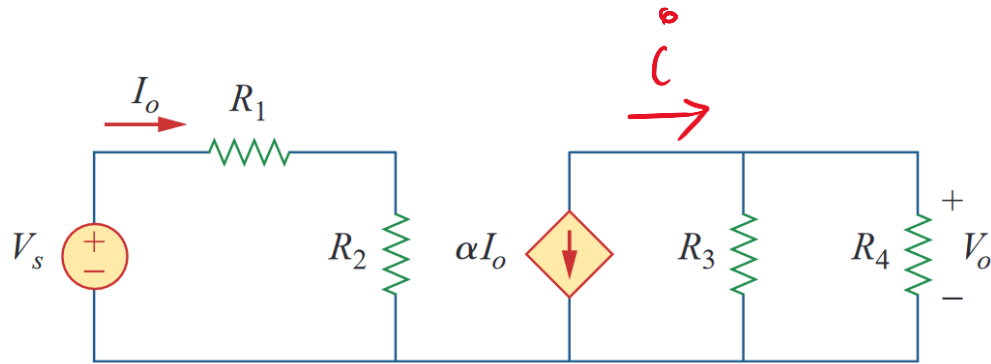



# Practice Problem 1

For the circuit, find  $\left| \frac{V_o}{V_s} \right|$  in terms of  $\alpha$ ,  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_4$ .

If  $R_1 = R_2 = R_3 = R_4$  what value of  $\alpha$  will produce  $\left| \frac{V_o}{V_s} \right| = 10$ ?

**Solution:**

Ohm's Law across  $R_1 + R_2$ .


$$I_o = \frac{V_s}{R_1 + R_2}$$

$$i = -\alpha I_o$$


Voltage across **Parallel Resistors**  $R_3, R_4$

$$V_o = i(R_3 || R_4) = -\frac{\alpha V_s}{R_1 + R_2} \cdot \frac{R_3 R_4}{R_3 + R_4}$$

$$\left| \frac{V_o}{V_s} \right| = \frac{\alpha}{R_1 + R_2} \cdot \frac{R_3 R_4}{R_3 + R_4}$$

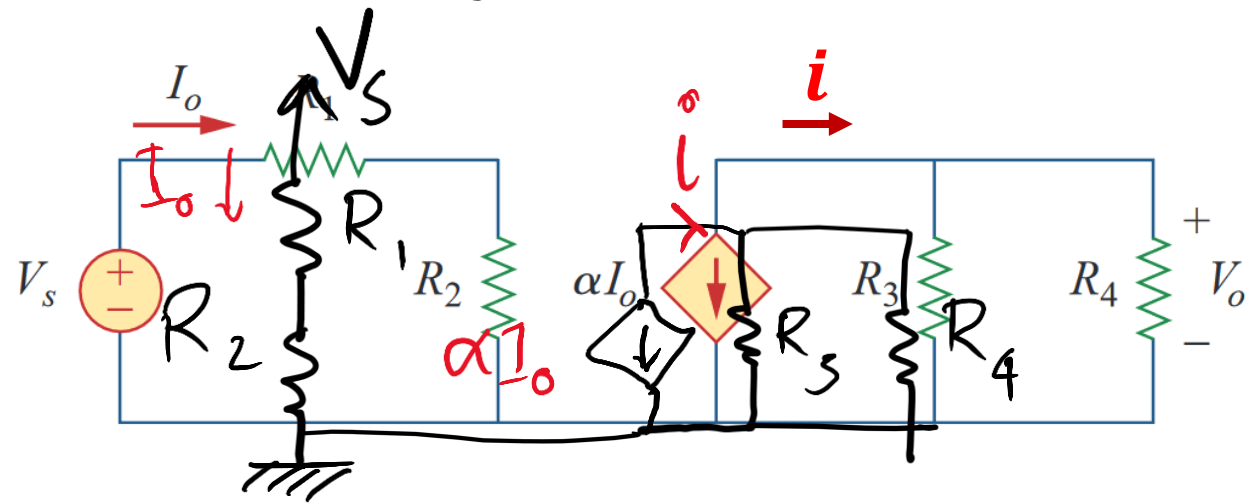

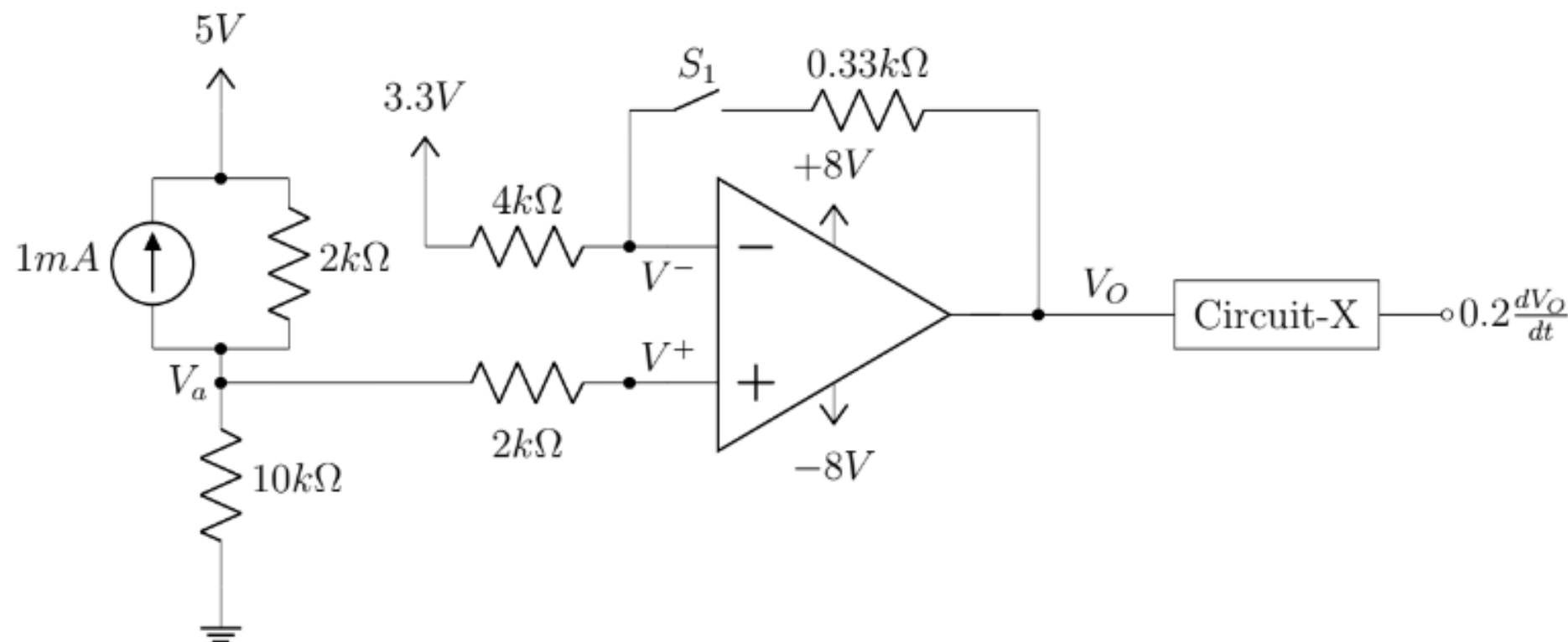The circuit diagram has a switch  $S_1$  which is shown to be 'open' in the figure. The output  $V_O$  is passed through an unknown block of 'Circuit-X' and a differentiated result is generated.



- [1 mark] **State** the equation of gain of an inverting amplifier.
- [3 marks] **Calculate** the values of  $V_a$  and  $V^+$ .
- [2 marks] **Determine**  $V_O$  when the switch  $S_1$  is closed.
- [2 marks] **Determine**  $V_O$  when the switch  $S_1$  is open.
- [2 marks] **Design** the 'Circuit-X'. **Assume** any value if necessary.

(a)  $\text{Gain} = -\frac{R_F}{R_1}$

(b) Nodal Analysis at  $V_a$  node:  $\frac{V_a - 5}{2} + \frac{V_a}{10} + 1 = 0 \Rightarrow V_a = 2.5 \text{ V}$ . Also,  $V_a = V^+ = 2.5 \text{ V}$

(c) When S1 is **closed**, the op-amp is in **closed** loop.



$$V^+ = V^- = 2.5 \text{ V.} \quad \text{Nodal Analysis at } V^- \text{ node: } \frac{V^- - 3.3}{4} + \frac{V^- - V_0}{0.33} = 0$$
$$\Rightarrow V_0 = 2.434 \text{ V}$$

(d) When S1 is **open**, the op-amp is in **open** loop.


$$V^+ = 2.5 \text{ V (from 'b')} \quad V^- = 3.3 \text{ V (from the left side of } 4k\Omega)$$

$$\text{Since, } V^+ < V^- \quad \Rightarrow V_0 = -8 \text{ V}$$

# Example 1- Nodal Analysis

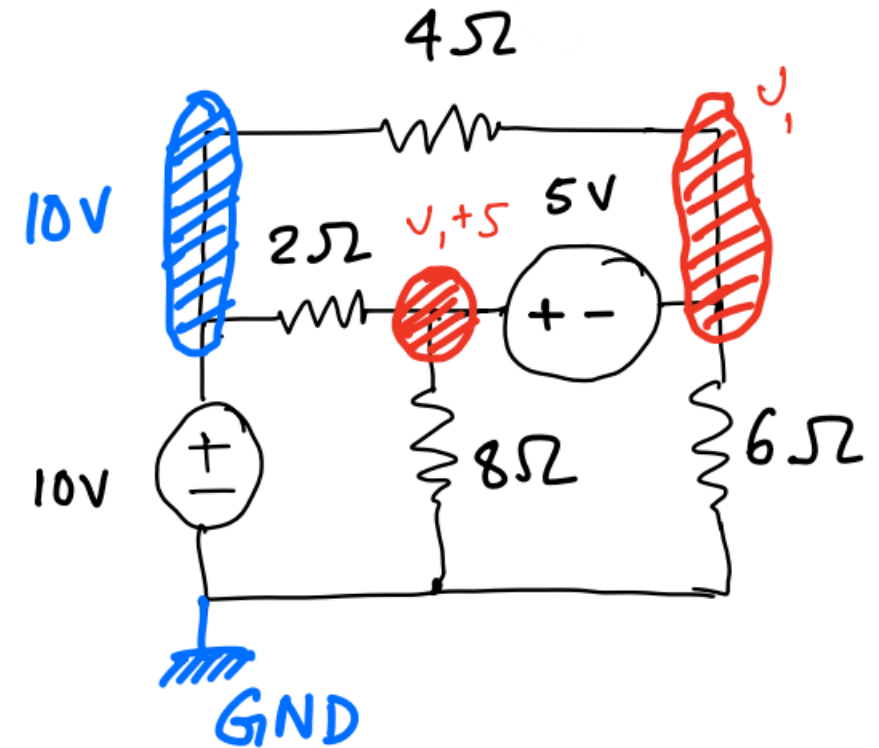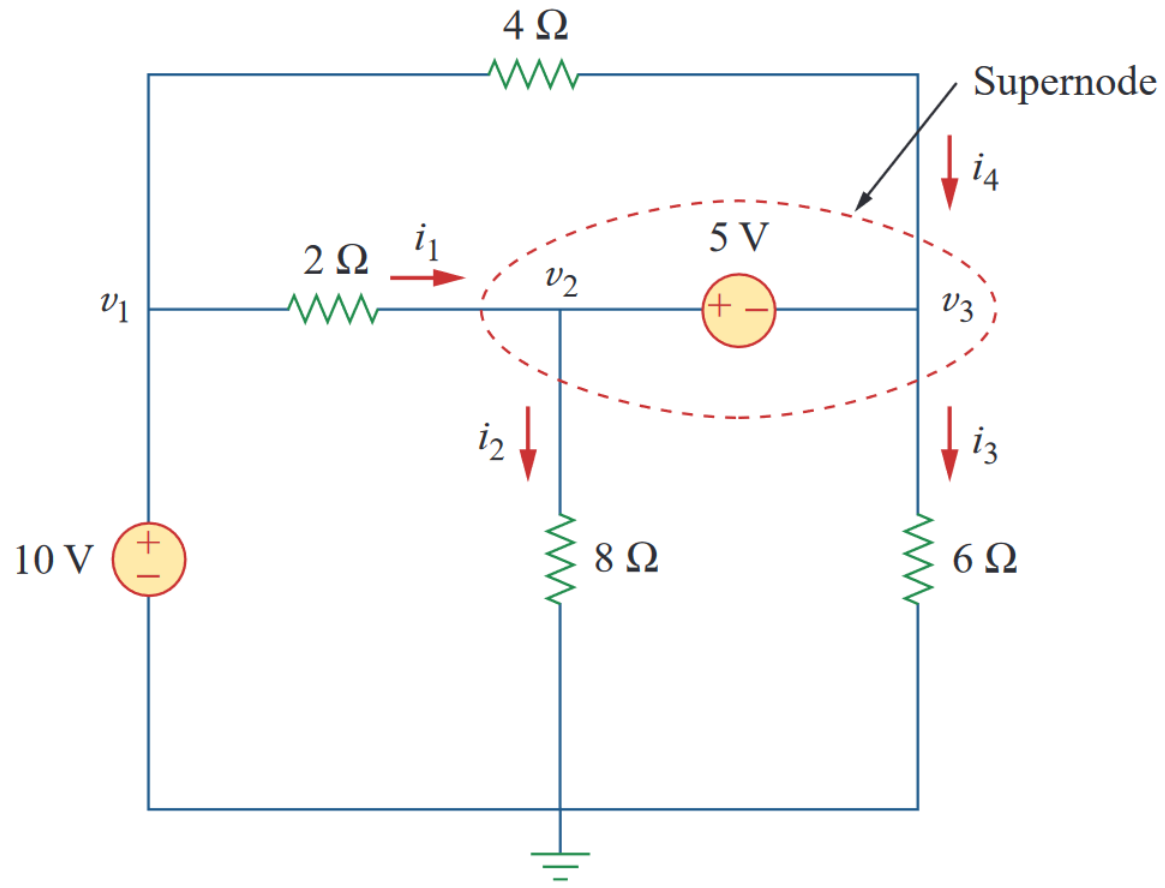

# Example 1- Nodal Analysis

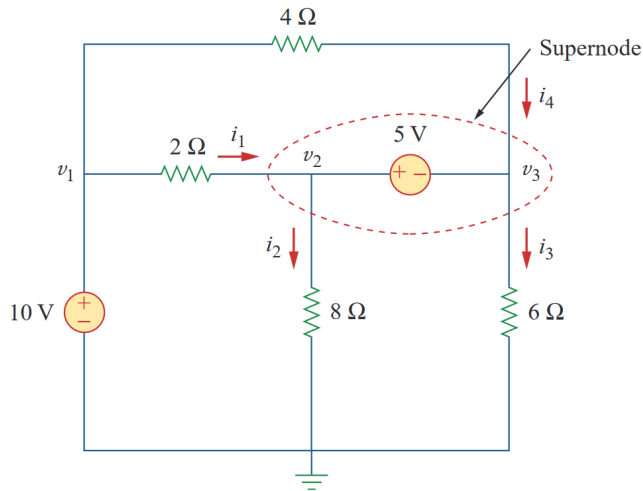


10V Node:  $10 \left( \frac{1}{4} + \frac{1}{2} \right)$

$v_1$  Node:  $v_1 \left( \frac{1}{4} + \frac{1}{6} \right)$


$v_1 + 5$  Node:  $(v_1 + 5) \left( \frac{1}{2} + \frac{1}{8} \right)$

Node equation for node  $v_1$
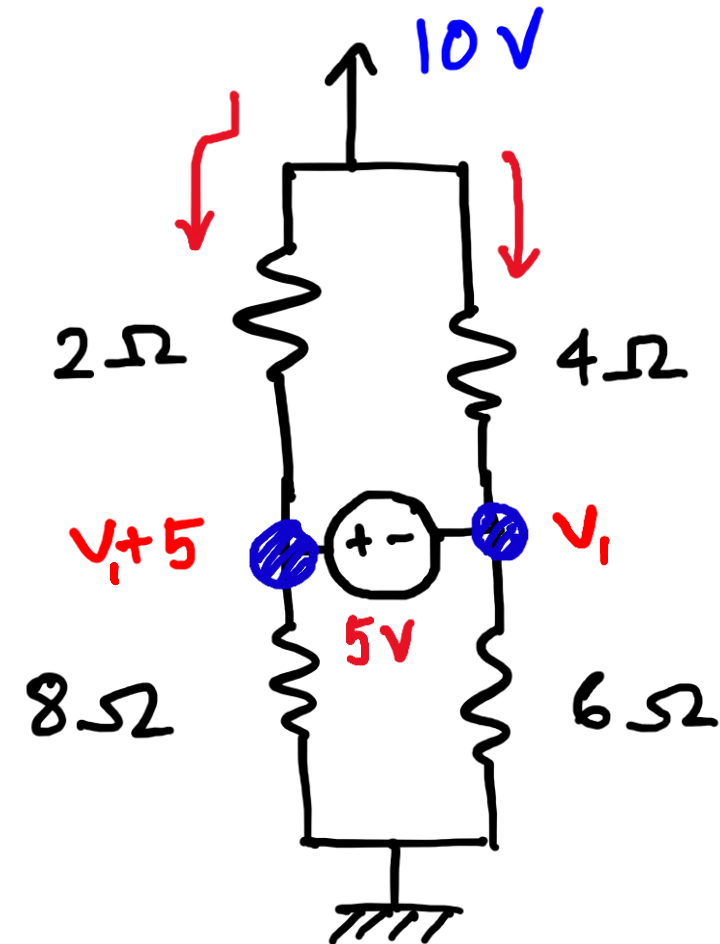
$$v_1 \left( \frac{1}{4} + \frac{1}{6} \right) + (v_1 + 5) \left( \frac{1}{2} + \frac{1}{8} \right) - 10 \left( \frac{1}{2} + \frac{1}{4} \right) = 0$$


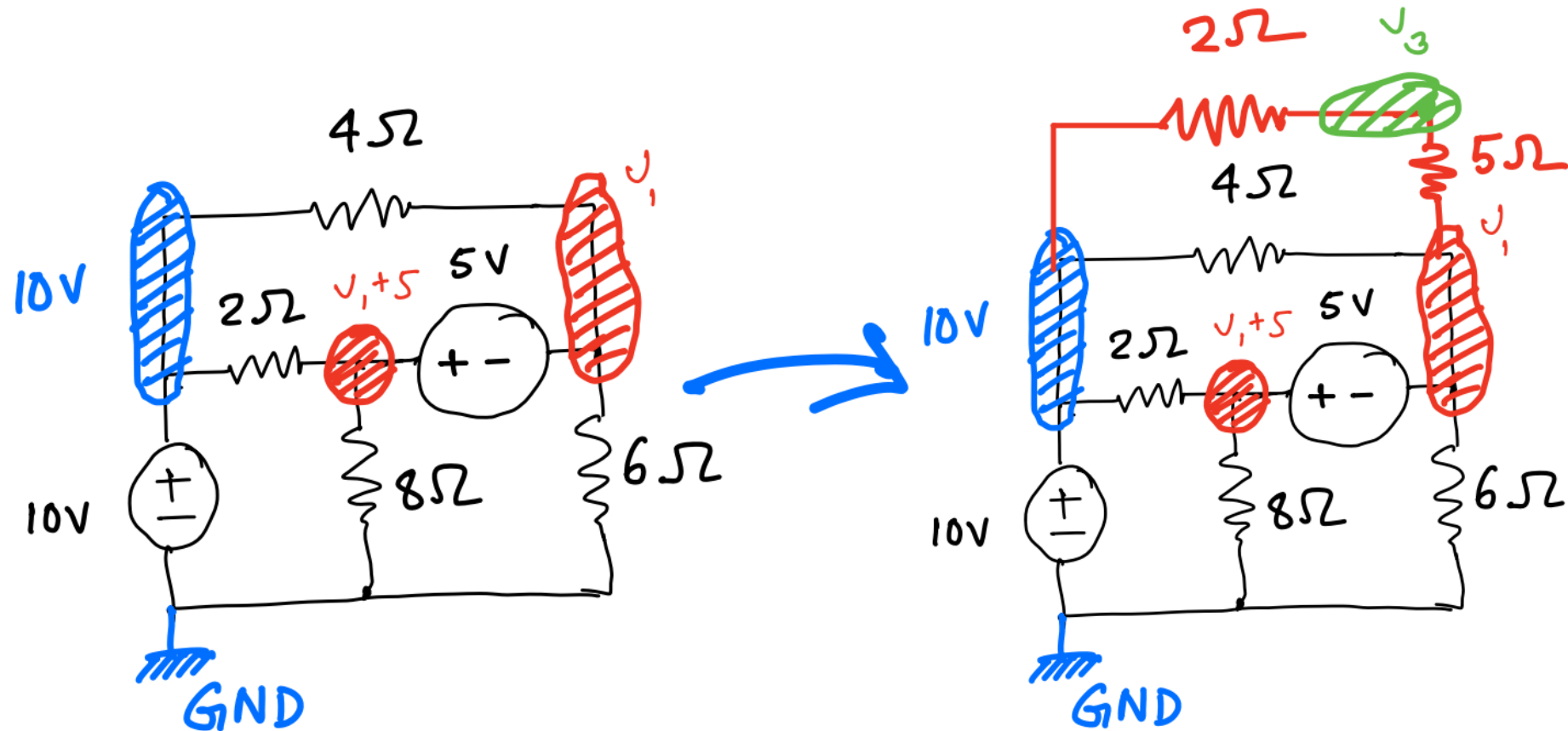
# Example 2- Nodal Analysis – Home Task 1




Find the two node  $v_1$  and  $v_3$  equations!

## Example 3

KCL at node  $v_o$

$$\frac{0.6 - 0.5}{5} = \frac{(0.5 - 0.7) - (-0.5)}{10} + I_1$$

$$I_1 = -0.01 \text{ mA}$$

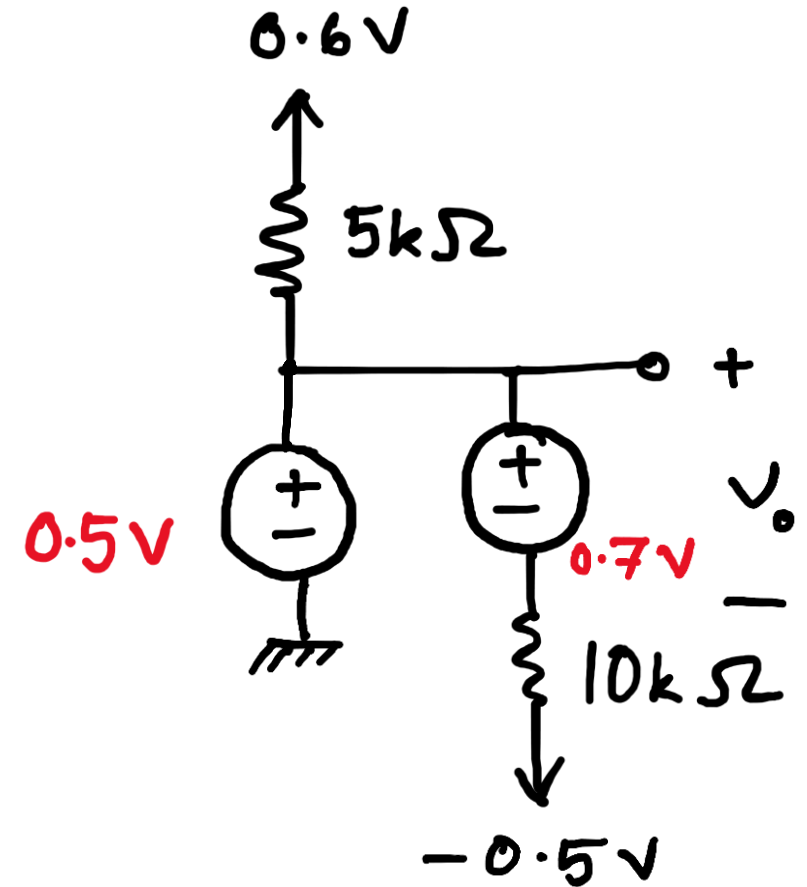

## Example 4

KCL at node  $v_i$


$$\frac{2 - v_i}{1} = \frac{v_i - v_o}{2} + \frac{v_i}{200}$$

$$\frac{301}{200}v_i - \frac{1}{2}v_o = 2$$

KCL at node  $v_o$

$$\frac{v_i - v_o}{2} + \frac{Av_i - v_o}{0.1} = 0$$
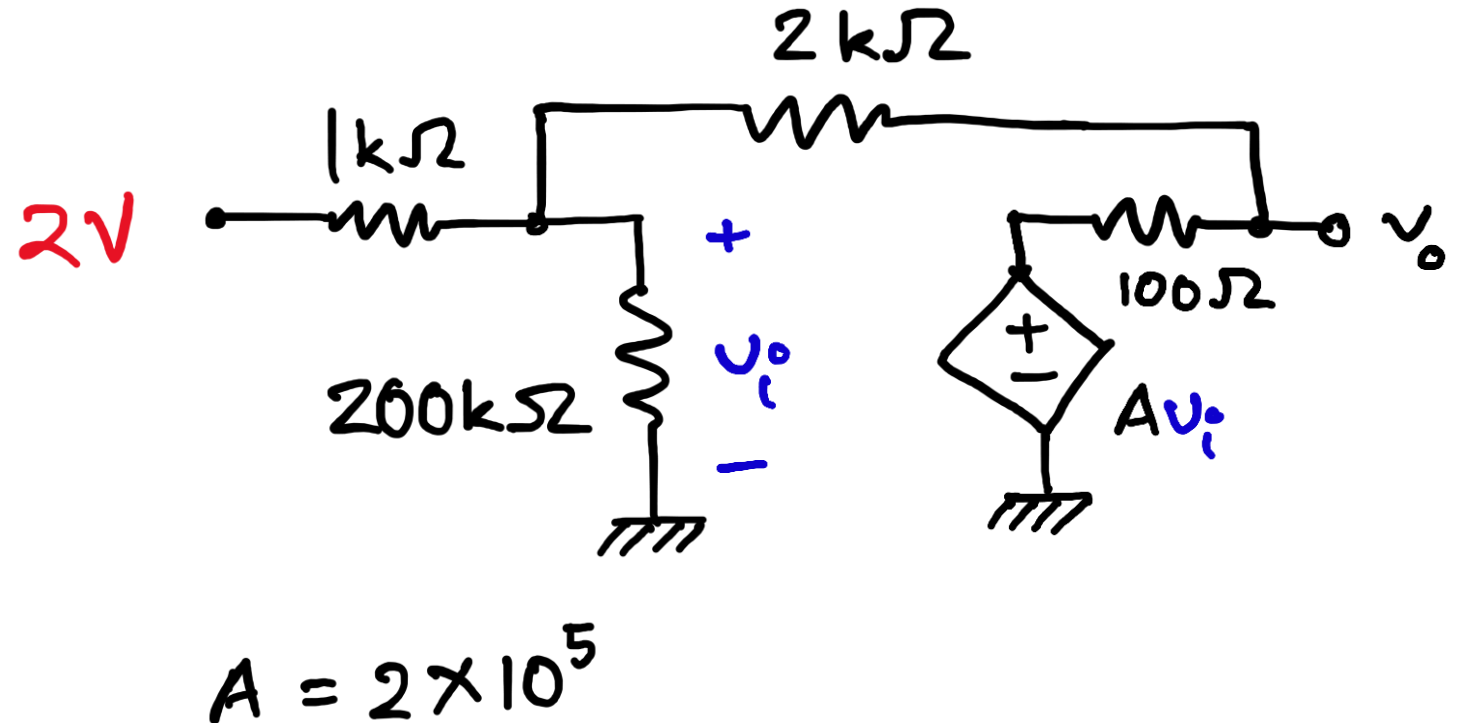
$$(2 \times 10^6 + 0.5)v_i - 10.5v_o = 0$$





# Example 5

KCL at node  $v_i$


$$\frac{0 - v_i}{5} = \frac{v_i - v_o}{40} + \frac{v_i - 1}{200}$$

$$\frac{23}{100}v_i - \frac{1}{40}v_o = \frac{1}{200}$$

KCL at node  $v_o$

$$\frac{v_i - v_o}{40} + \frac{Av_i - v_o}{0.1} = \frac{v_o}{20}$$
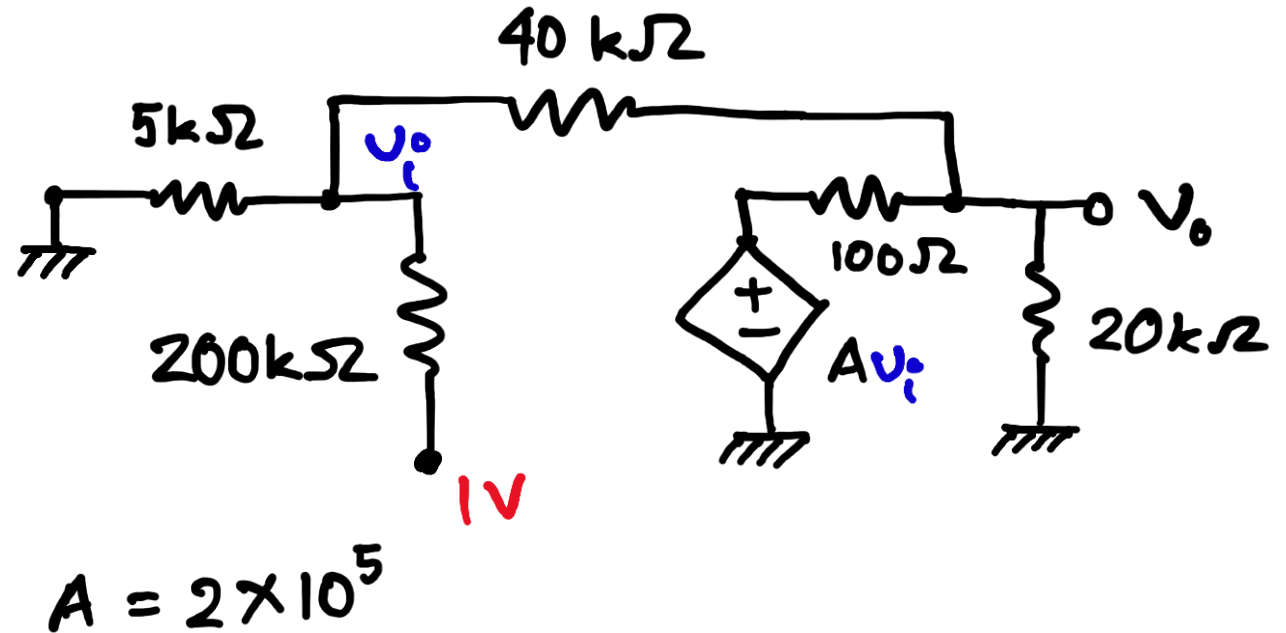
$$(2 \times 10^6 + 0.025)v_i - 10.075v_o = 0$$



# Example 6 – Home Task 2



For  $R = 100\ \Omega$ ,  $R_L = 10\ \text{k}\Omega$ ,  $r_z = 20\ \Omega$ ,  $V_{Z0} = 3\ \text{V}$ , and  $I_Z = 1\ \text{mA}$ .

a. Find  $V_O$

b. Find  $I_L$

c. Find  $I$

d. Find  $V^+$

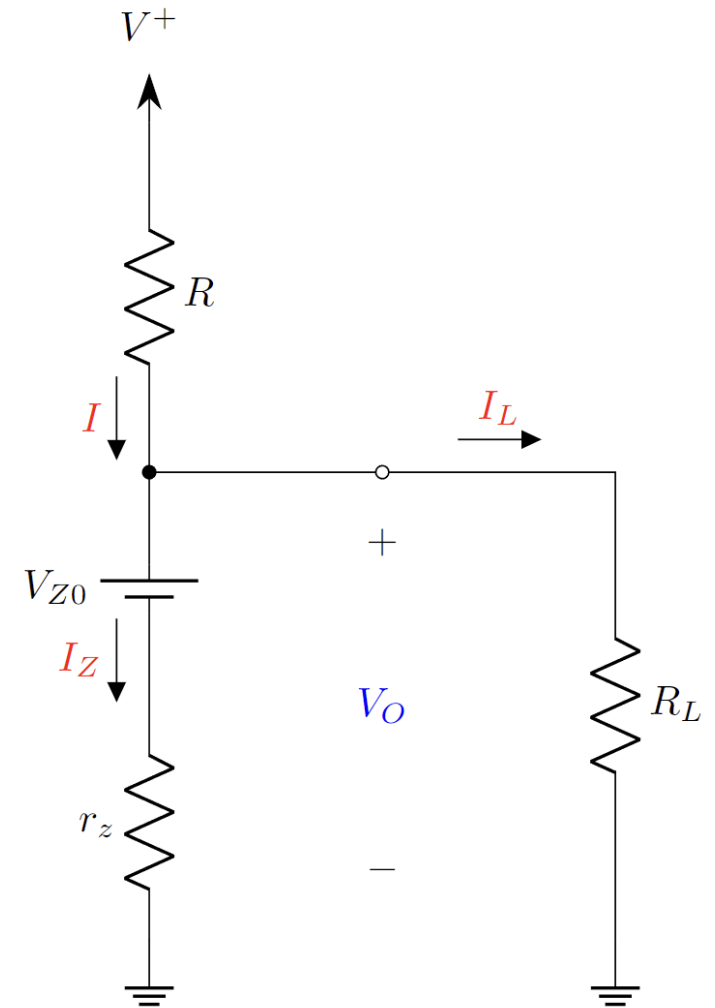
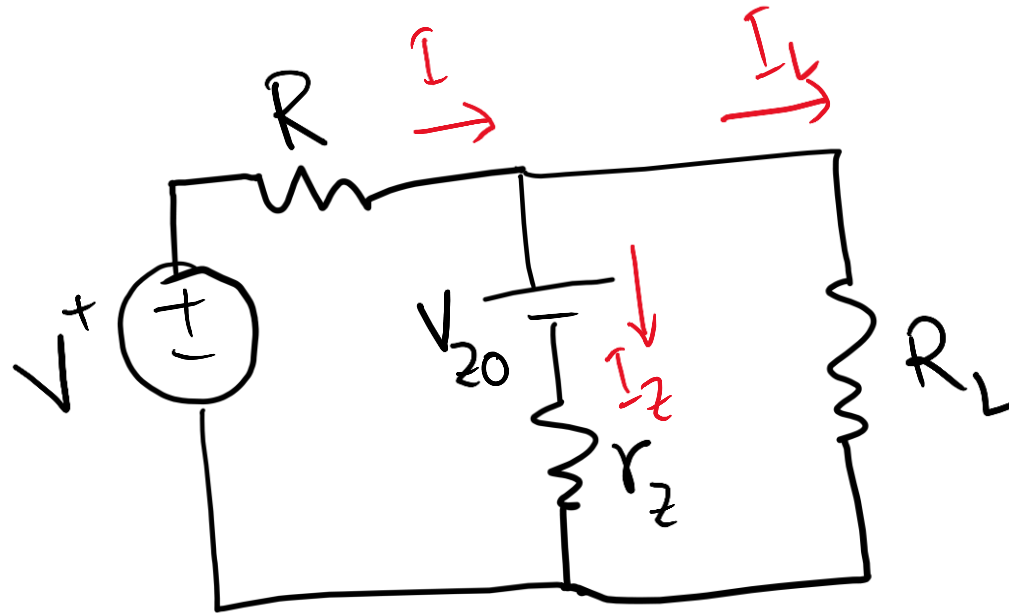


# Current-Voltage (I-V) Characteristics

- I-V characteristic defines the relationship between the **current flow (through),  $I$**  and **voltage (across),  $V$**  an electronic device or element.
- A tool for understanding the operation of the circuit.
- The Current-Voltage (I-V) characteristics are found by evaluating the **response** of a device/element under different conditions. The behavior of a device depends on the **applied excitation** and can change if the excitation changes. For example, a device may act as an “open circuit” under certain input conditions and as “current source” in another. A diode acts as an open circuit below a specific threshold voltage and acts differently after that.

# Current-Voltage (I-V) Characteristics


Example:

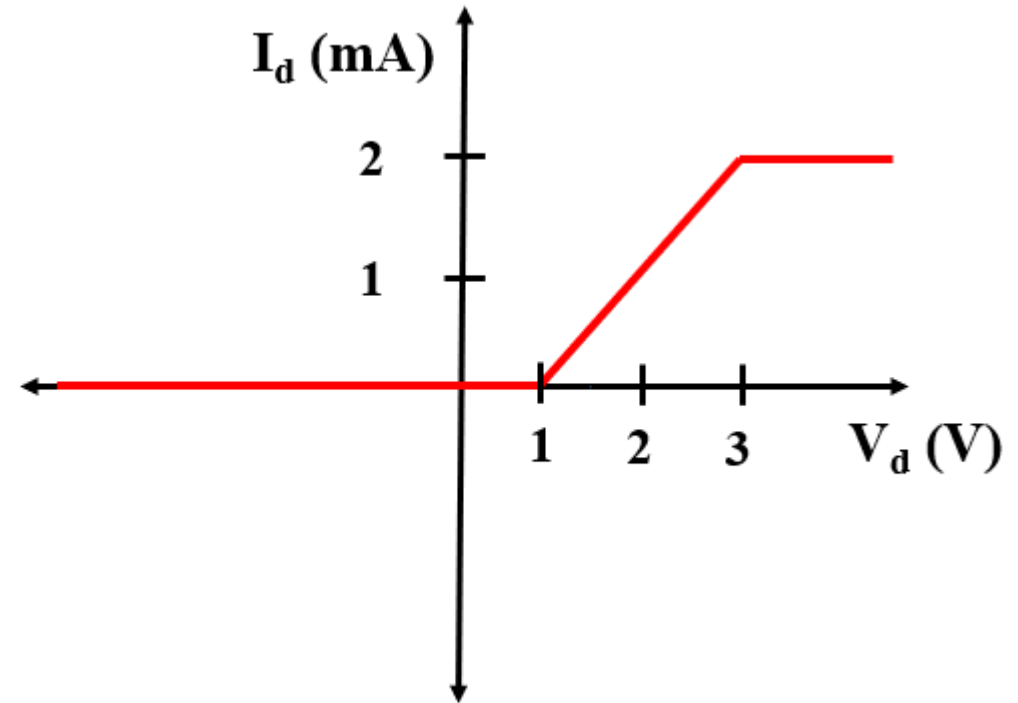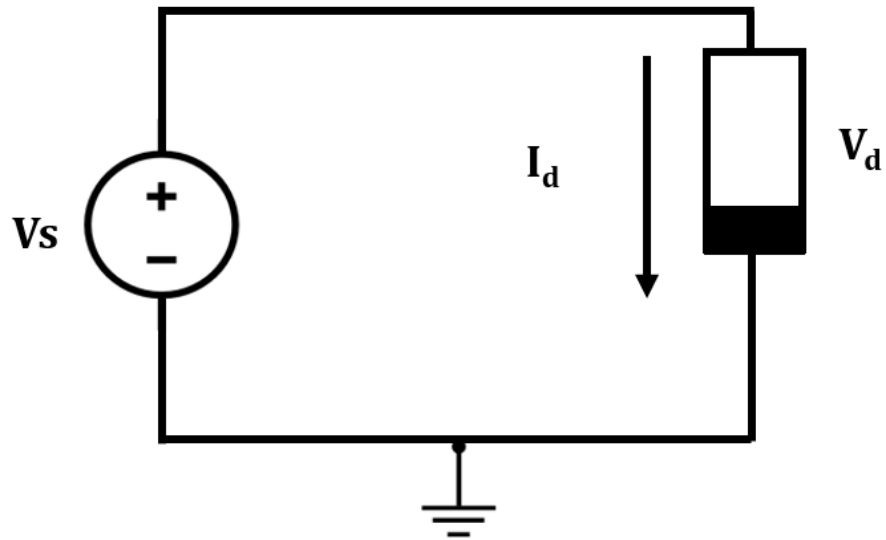
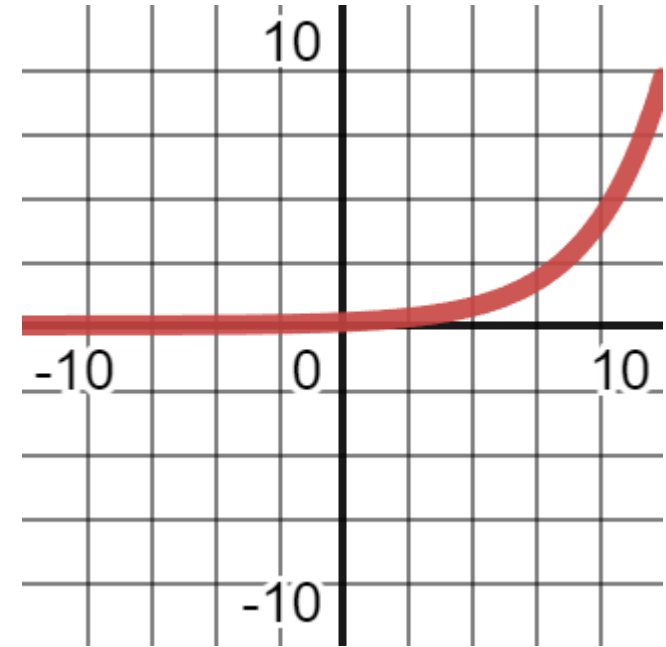
# Current-Voltage (I-V) Characteristics

$$I = kV \quad I = kV^2 \quad I = A \cdot \exp\left(\frac{V}{b}\right)$$

$$y = mx \quad y = ax^2 \quad y = A \cdot \exp\left(\frac{x}{b}\right)$$



# Type of (I-V) Characteristics

**1. Linear Devices/Elements:** The Current-Voltage relationship is linear i.e. the current through the element is a linear function of the applied voltage across it. The relationship can be characterized by:


$$I = kV$$

**2. Non-Linear Devices/Elements:** The Current-Voltage relationship is Non-linear i.e., the current through the element is a nonlinear function of the applied voltage across it.

$$I = k\sqrt{V}$$





$$I = kV^2$$

$$I = kV^3$$

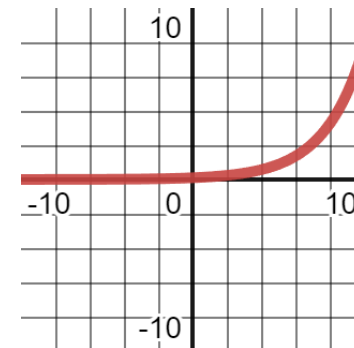

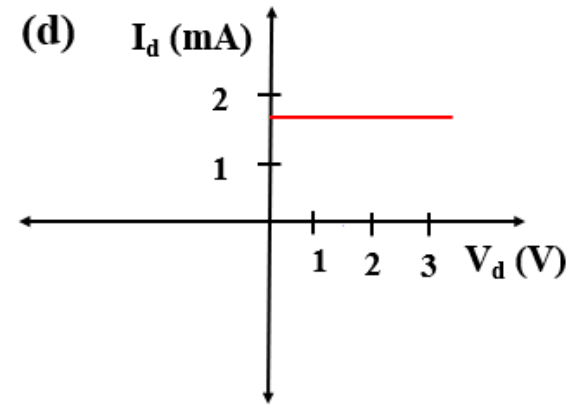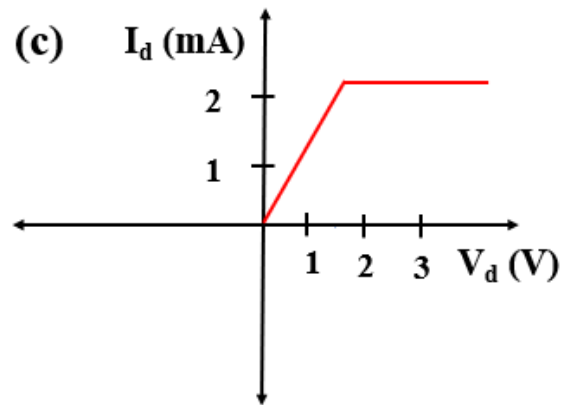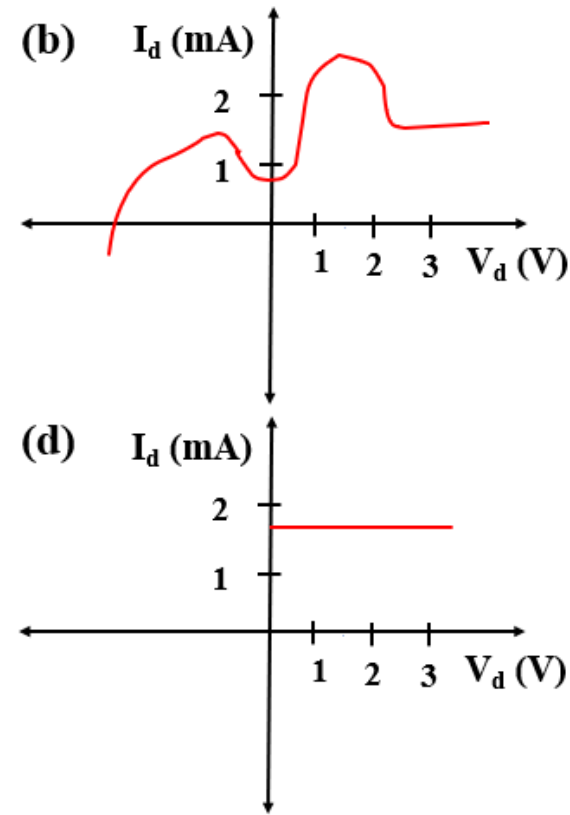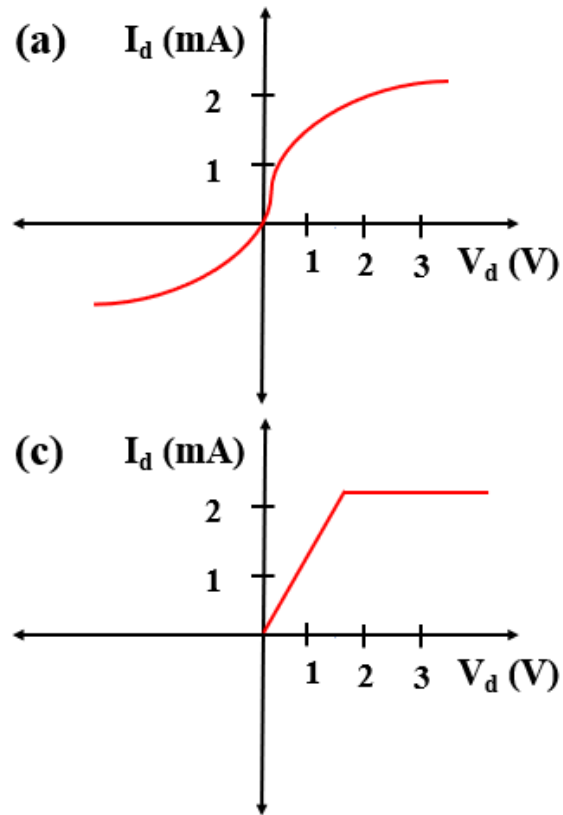
# Type of (I-V) Characteristics

- Identify which of these I-V curves are Linear and which are Nonlinear


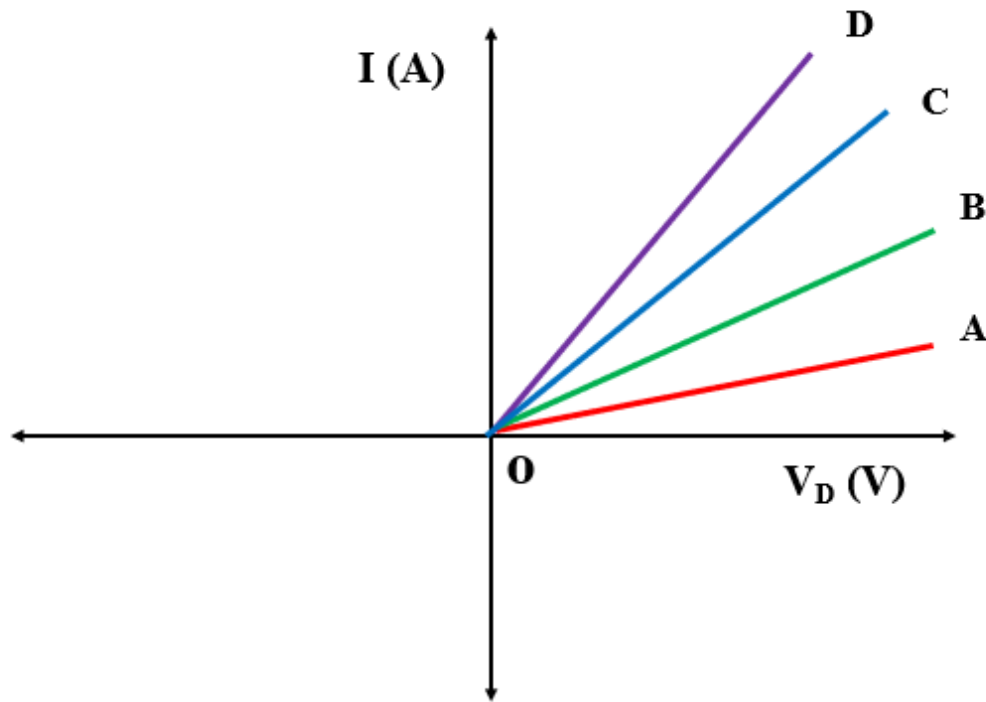
# Linear Devices/Elements


- Write down the slopes of these following regions in ascending order (you do not need to calculate the slopes)





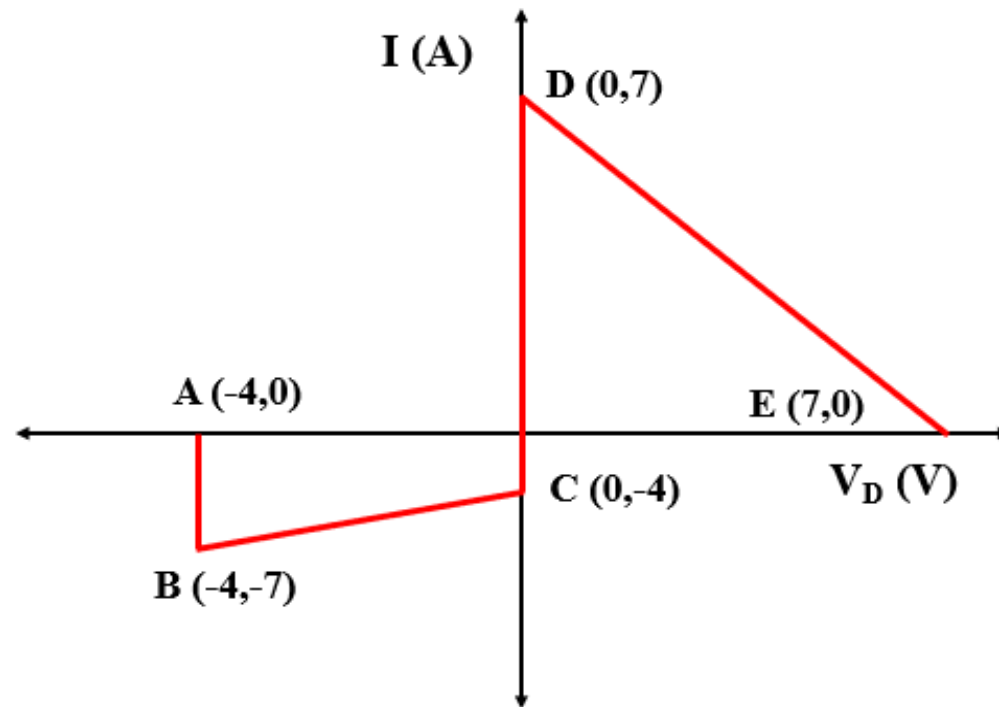
# Linear Devices/Elements

- Find out the slope of the following curves








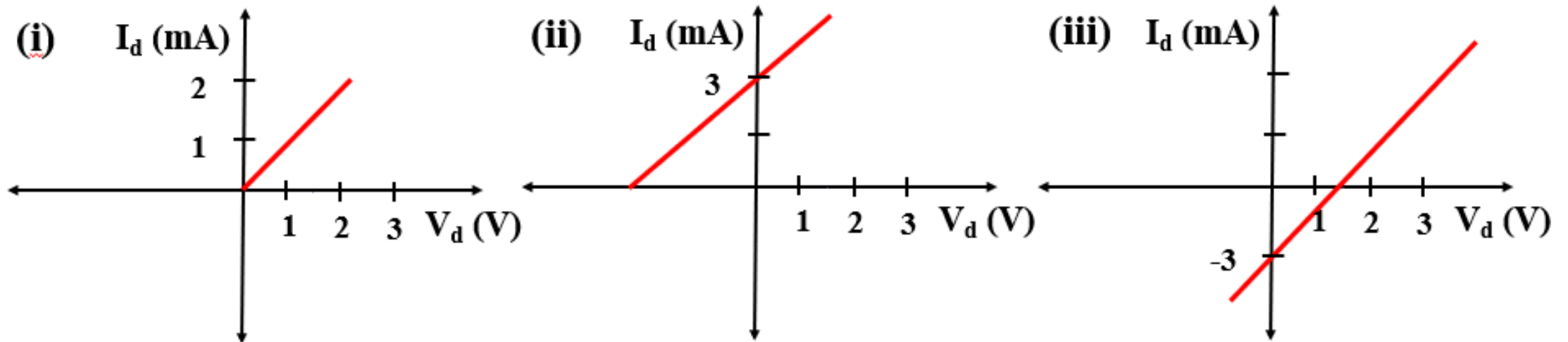
# Linear Devices/Elements

- For the lines represented by  $y = \mathbf{m}x + \mathbf{c}$  what is the value of  $\mathbf{c}$  in the following figures [Figure (i), (ii) and (iii)]



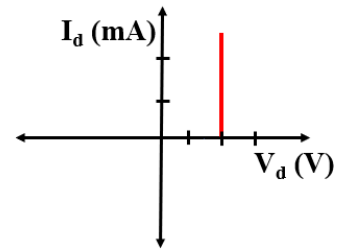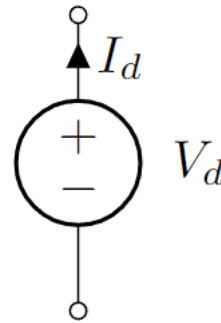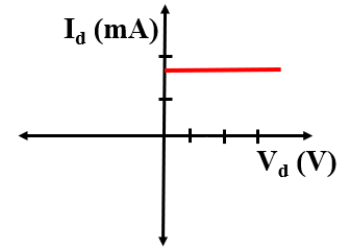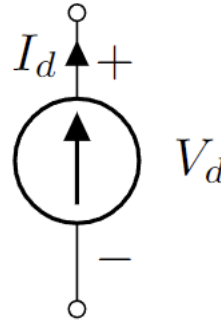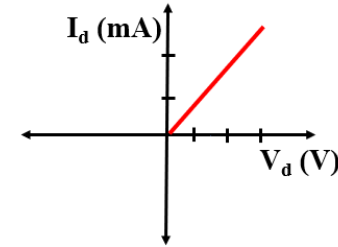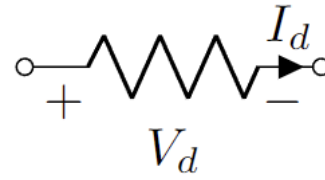
# Linear Devices/Elements:

- Resistors
- Current Source
- Voltage Source



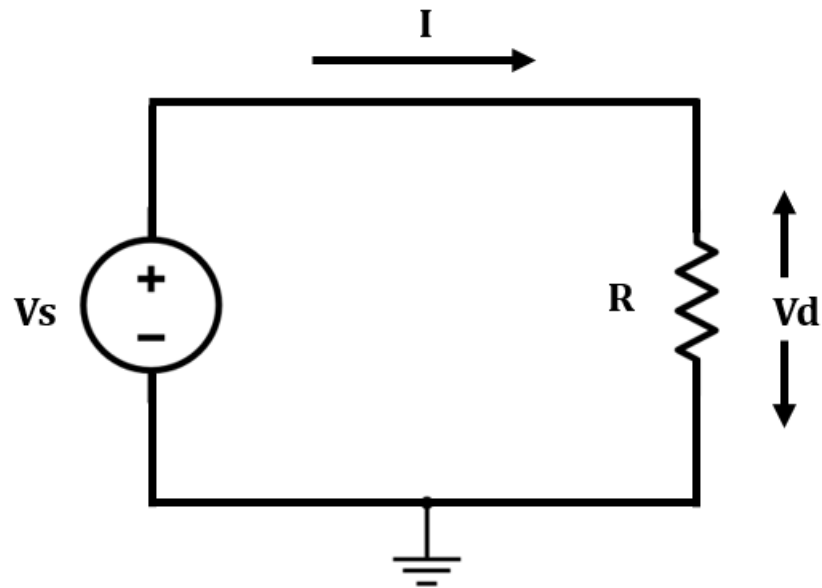
# Resistor

- The relationship between current,  $I$  and voltage,  $V_d$  in a resistor of value ' $R$ ' is defined by the "**Ohm's law**":



$$\begin{aligned} V_d &= IR \\ \Rightarrow I &= \frac{V_d}{R} \\ \Rightarrow I &= \frac{1}{R} \cdot V + 0 \end{aligned}$$


$$y = m \cdot x + c$$

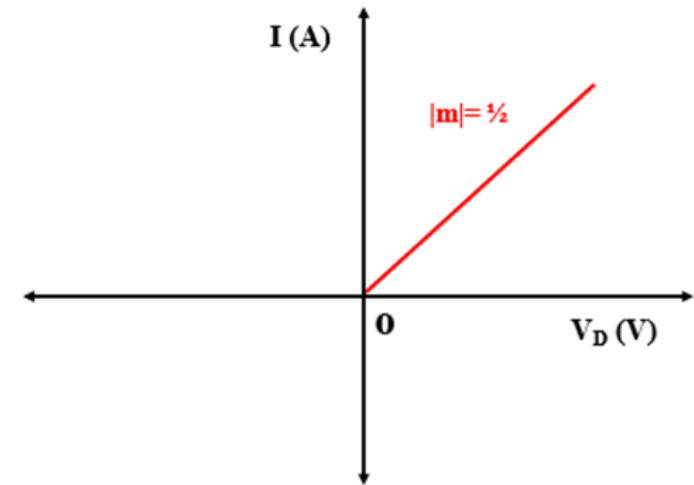

I-V curve of a  $2\Omega$  resistor
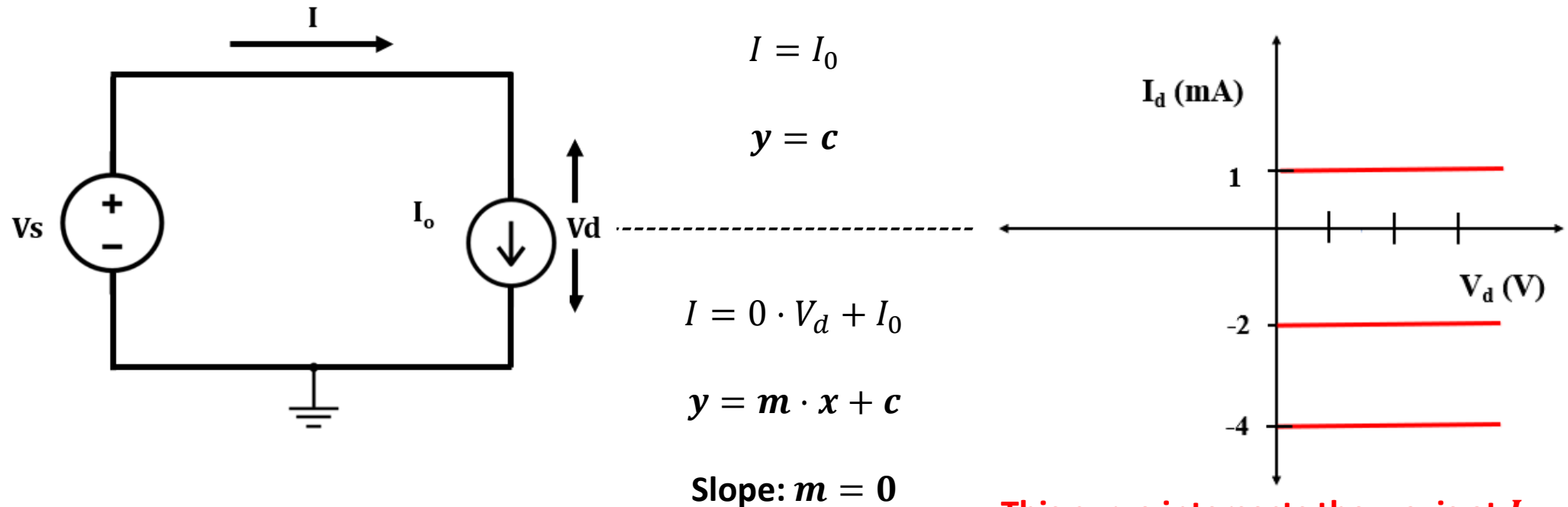
# Current Source


- The value of current flow through a current source is **FIXED** and thus does not change with voltage. The equation is as follows



This curve intersects the y axis at  $I = I_o$ .
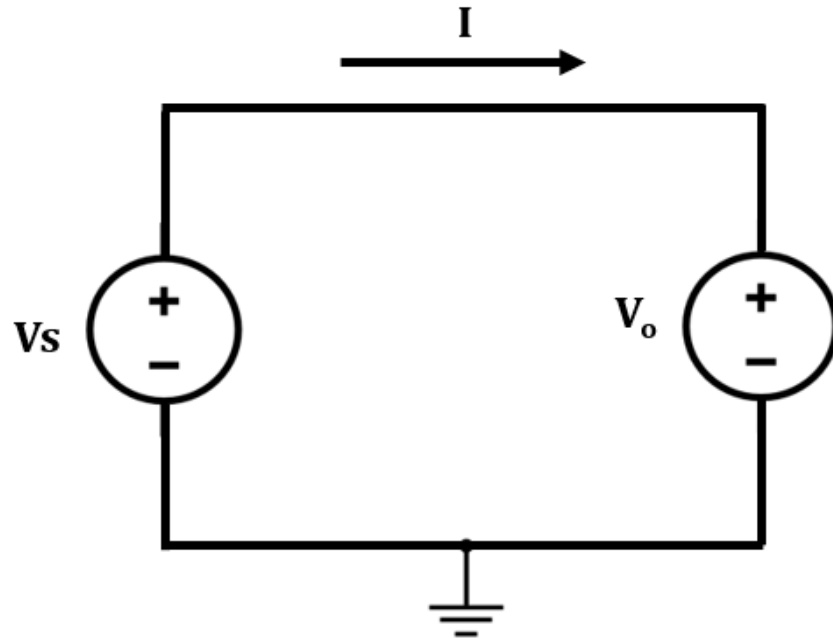
# Voltage Source


- The value of voltage across a voltage source is **FIXED** and thus does not change even if the current through the branch changes.



$$V = V_0$$

$$x = c$$

$$\text{Slope: } m = \infty$$

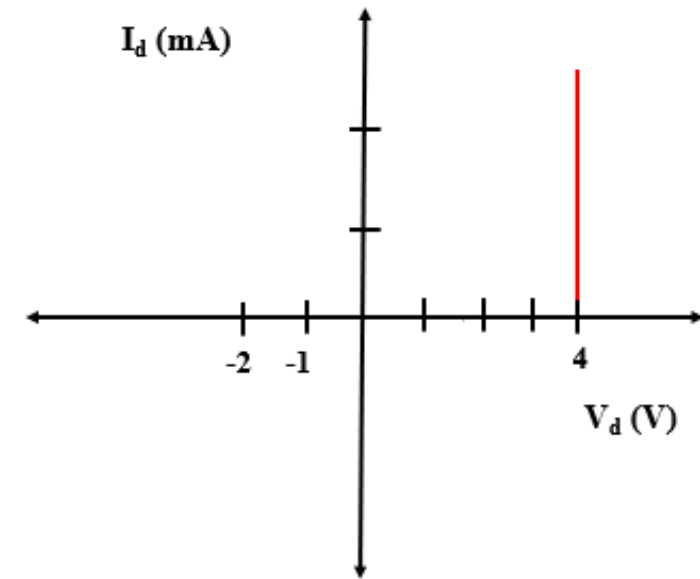


This curve intersects the x axis at  $V_d = V_o$ .



# Electrical Sources

Ideally, internal resistance of a **CURRENT SOURCE** is **infinite (undefined)**


That of a **VOLTAGE SOURCE** is **zero**

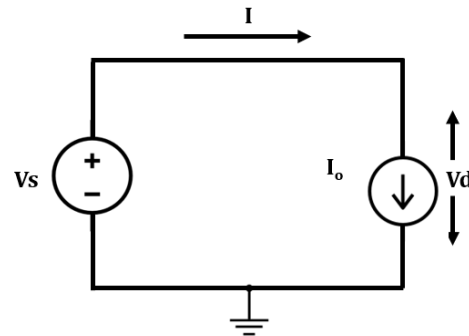

Resistance:  $\infty$

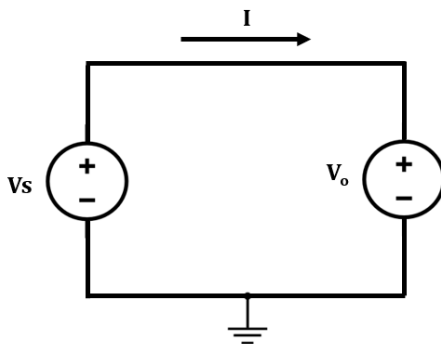
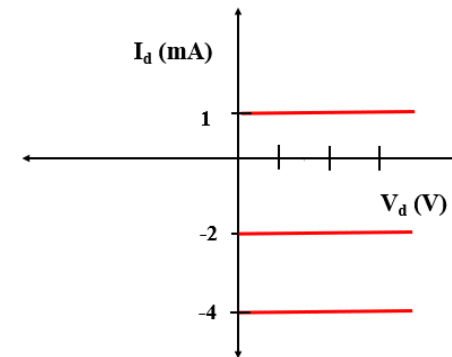


Resistance: 0

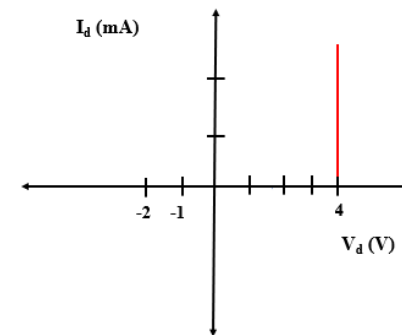

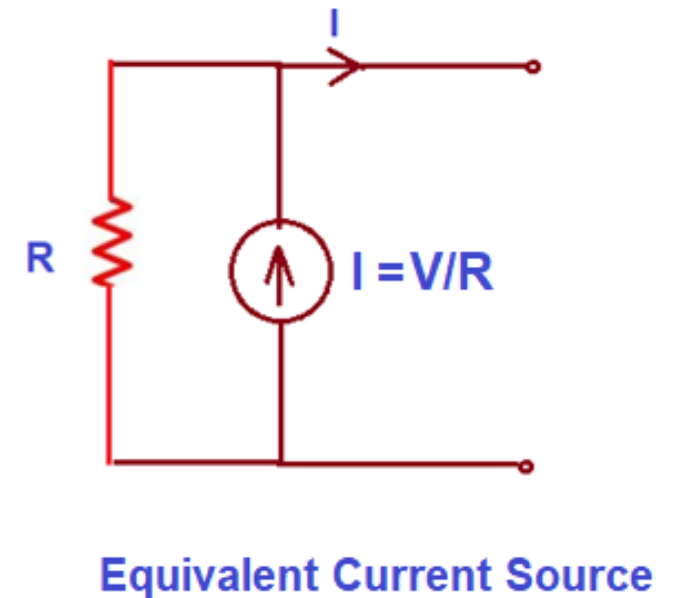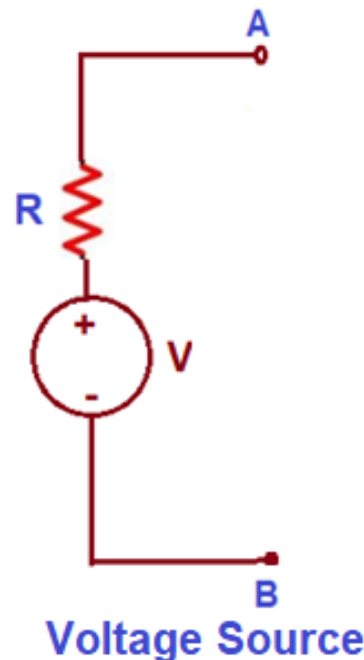
# Hybrid/ Compound Linear Circuits

- Voltage Source in Series with a Resistor
- Current source in Parallel with a Resistor





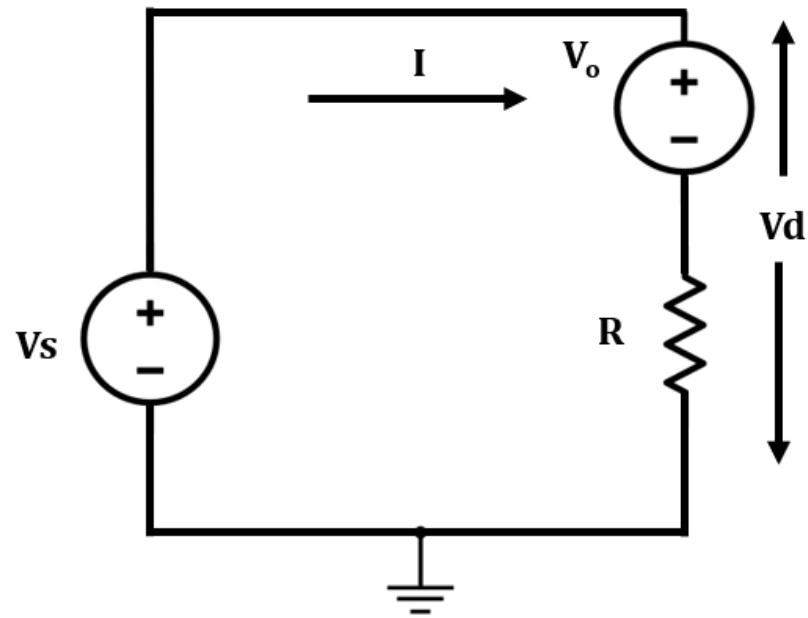
# Voltage Source in Series with a Resistor



$$\begin{aligned}V_d - V_o &= IR \\ \Rightarrow I &= \frac{V_d - V_o}{R} \\ \Rightarrow I &= \frac{1}{R} \cdot V_d - \frac{V_o}{R}\end{aligned}$$


$$y = mx + c$$
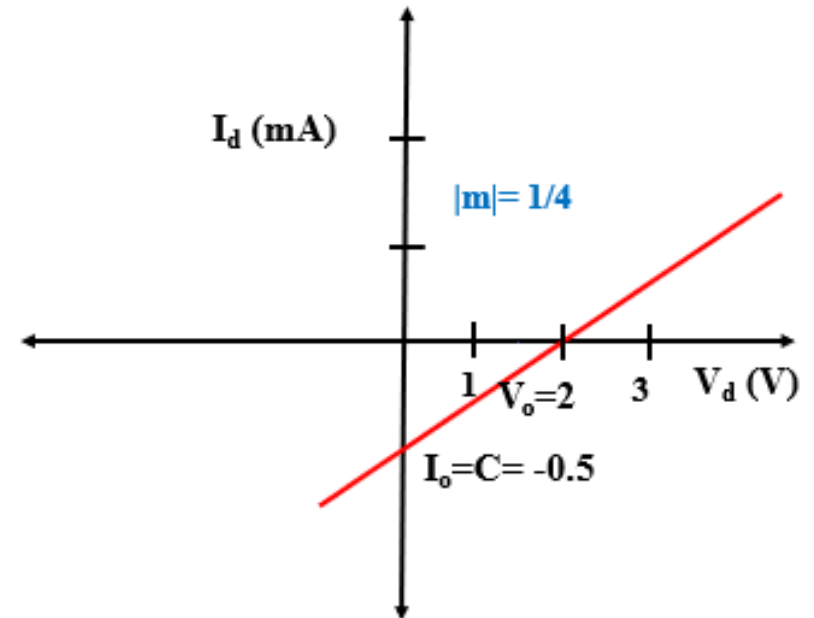
$$\begin{aligned}m &= \frac{1}{R} \\ c &= -\frac{V_o}{R}\end{aligned}$$



I-V curve of a **4 k $\Omega$**  resistor in series with a **2 V** voltage source
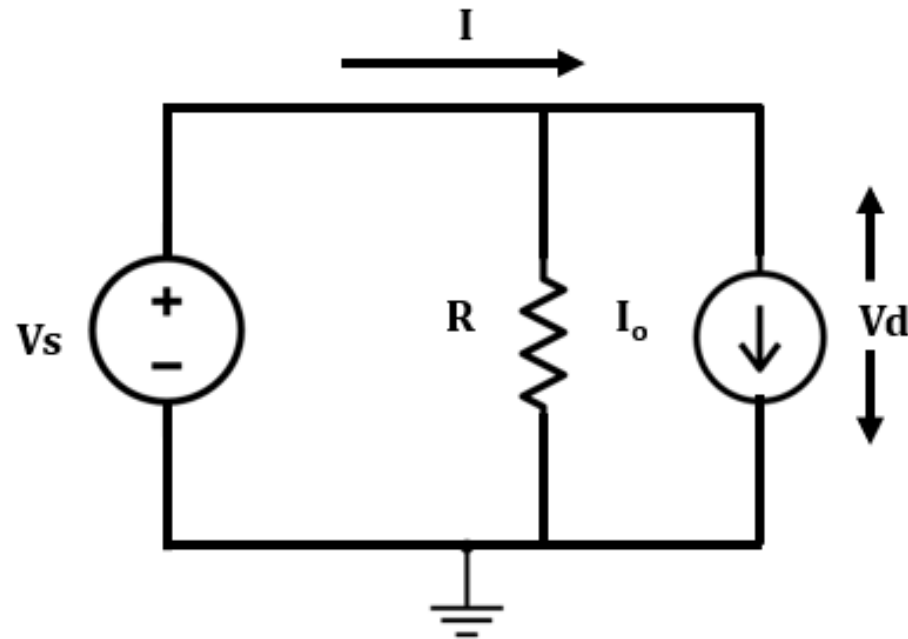
# Current source in Parallel with a Resistor




$$I = \frac{V_d}{R} + I_o$$
$$\Rightarrow I = \frac{1}{R} \cdot V_d + I_o$$

$$y = mx + c$$

$$m = \frac{1}{R}$$


$$c = I_o$$

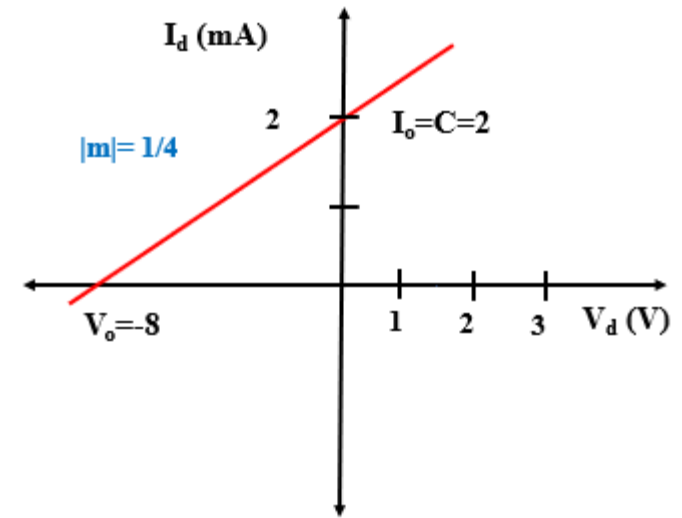

**The value of a resistor CAN NOT be Negative!**


# Degenerate Linear Elements

- Open Circuit

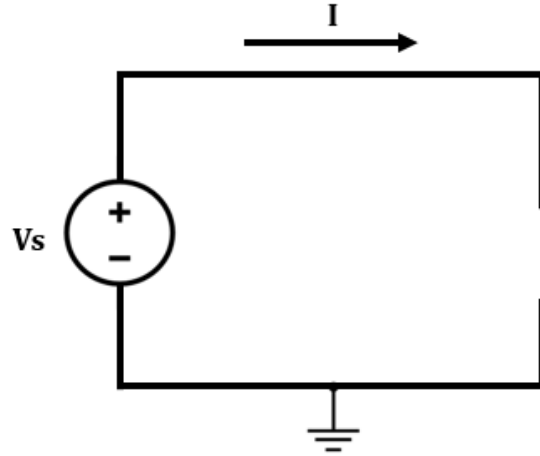


$$I_d = I_0 = 0$$

$$y = c = 0$$

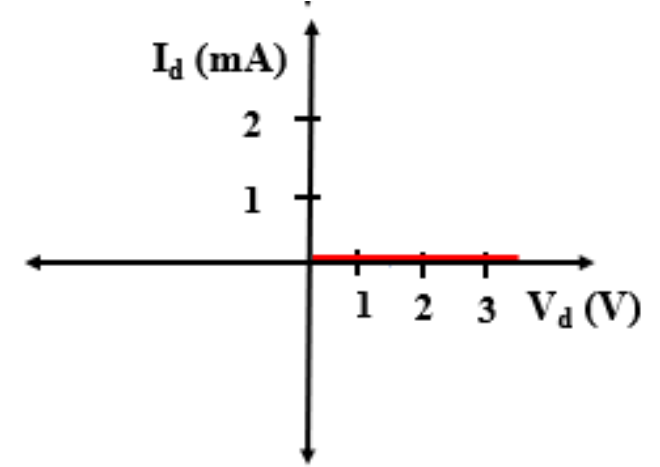


- Short Circuit

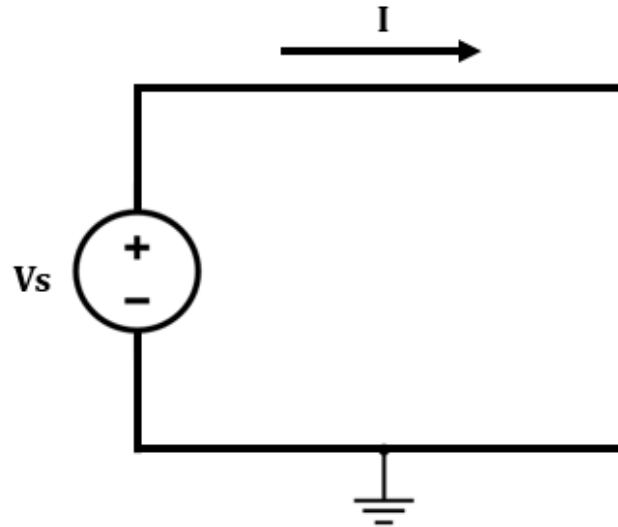






$$V = V_0 = 0$$

$$x = c = 0$$

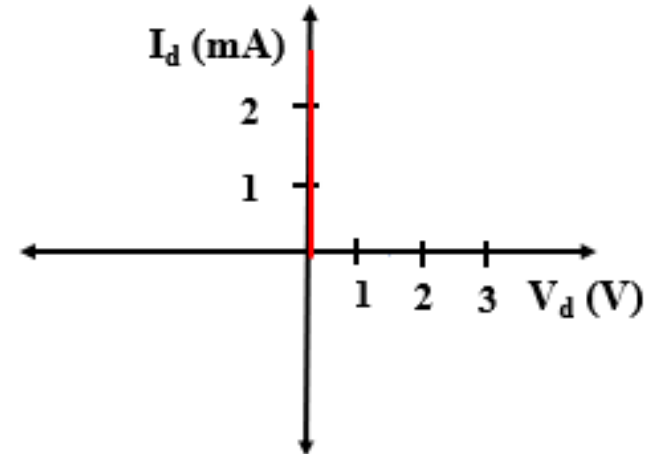


# Voltage Source in Series with a Resistor

- Find the circuit

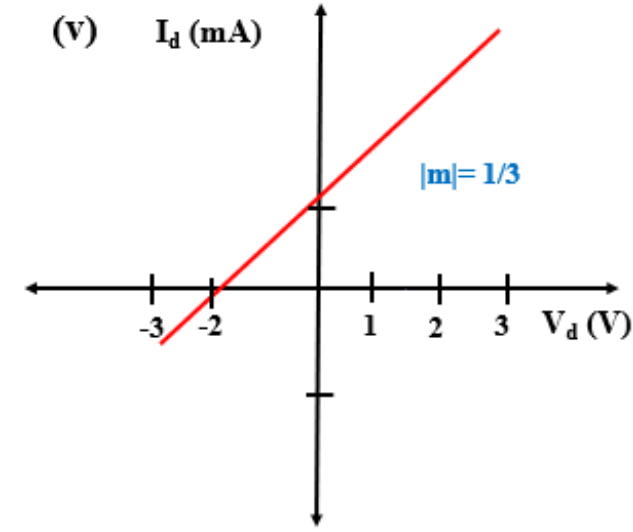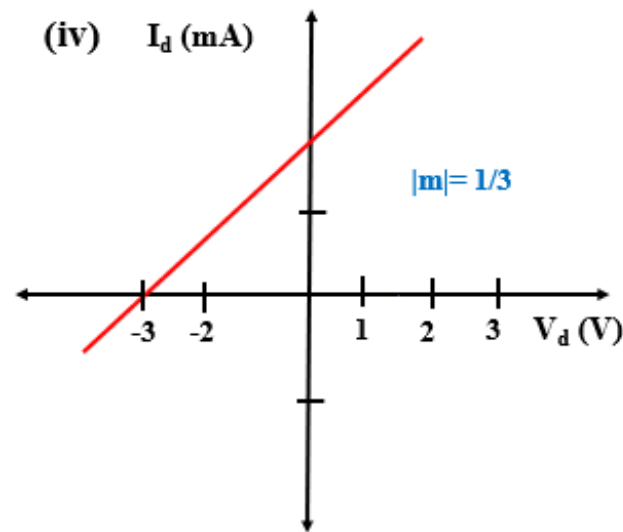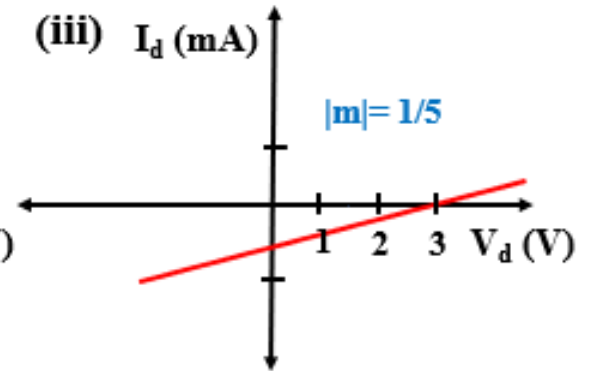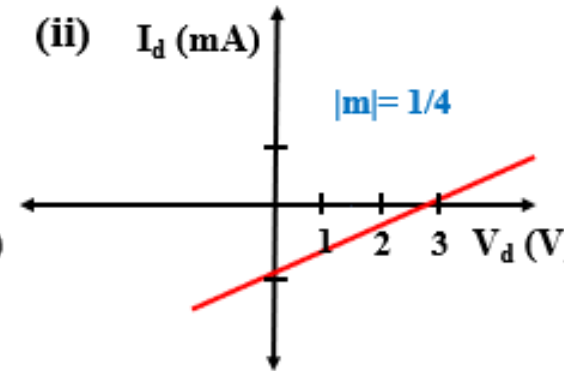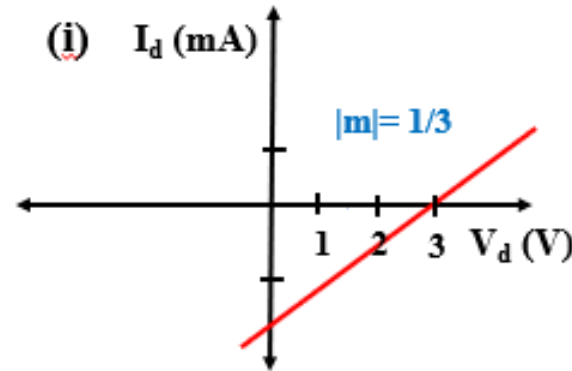

# Current source in Parallel with a Resistor

Find the circuit

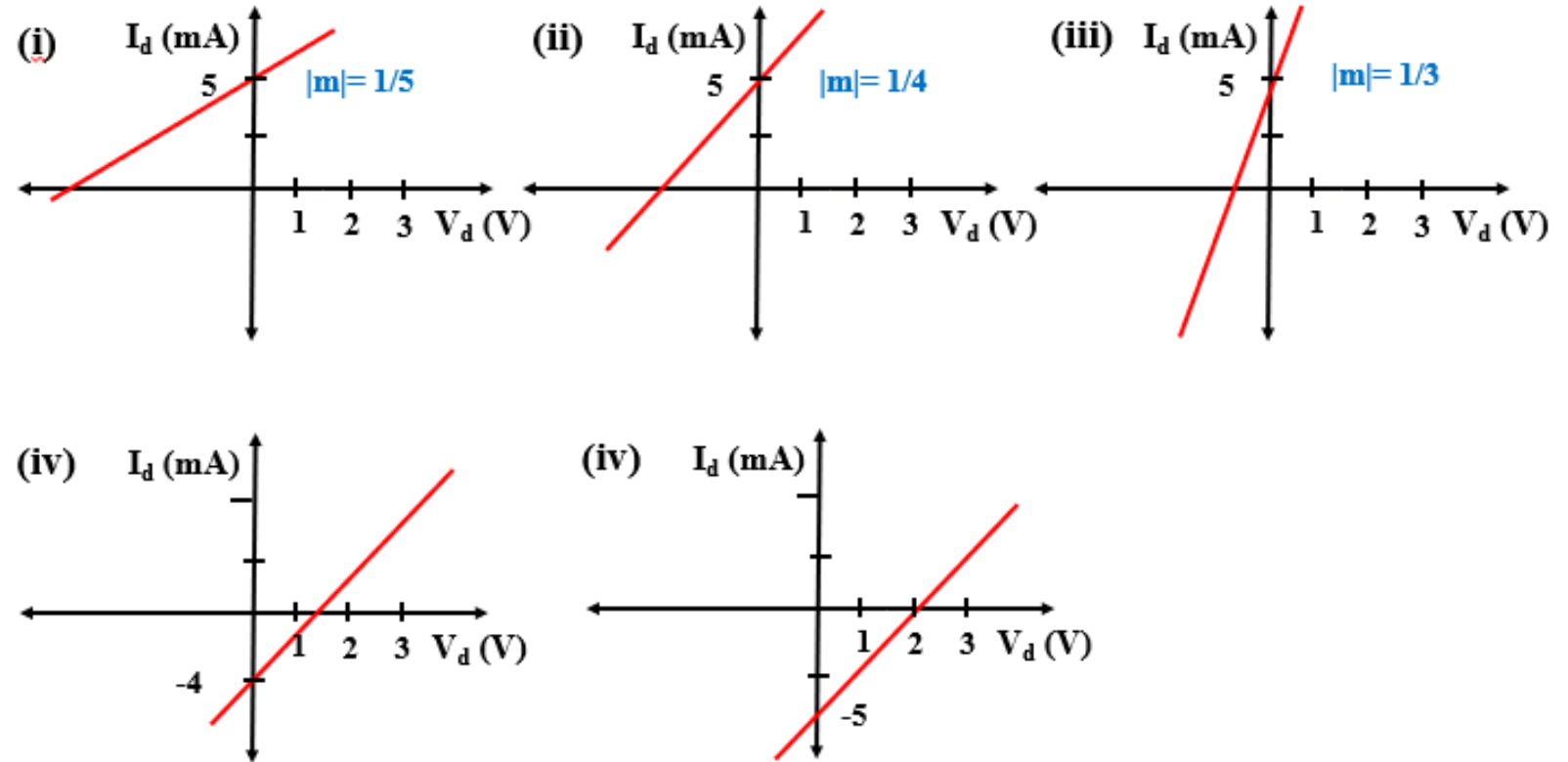


# Practice Problems


1. A Voltage Source,  $V_o = -10 \text{ V}$  in series with a resistor of  $R = 3 \text{ k}\Omega$ .
  - i. Write down the equation representing this curve
  - ii. Determine the unknown parameters
  - iii. Label the I-V curve
2. A Current Source,  $I_o = -5 \text{ mA}$  in parallel with a resistor of  $R = 5 \text{ k}\Omega$ .
  - i. Write down the equation representing this curve
  - ii. Determine the unknown parameters
  - iii. Label the I-V curve
3. A Current Source,  $I_o = 5 \text{ mA}$  in parallel with a resistor. The slope of the curve is,  $m = -5 \text{ k}\Omega^{-1}$ .
  - i. Write down the equation representing this curve
  - ii. Determine the unknown parameters
  - iii. Label the I-V curve

# Non-Linear Devices/Elements


- Diode

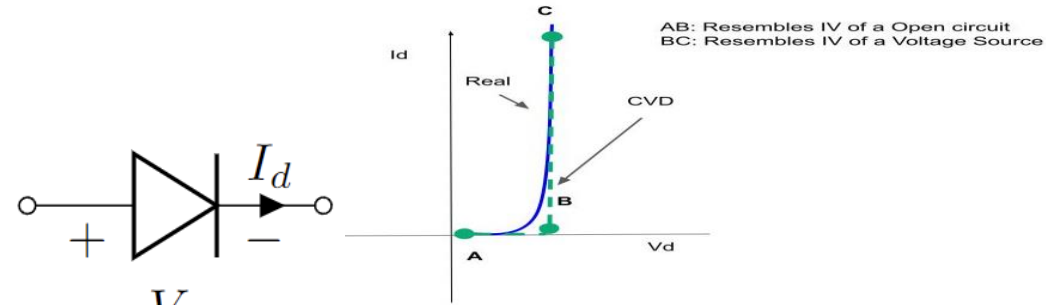

- MOSFET

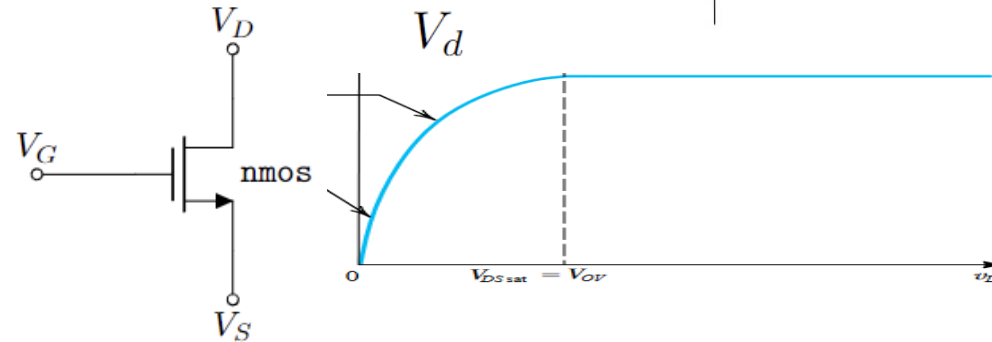


- BJT

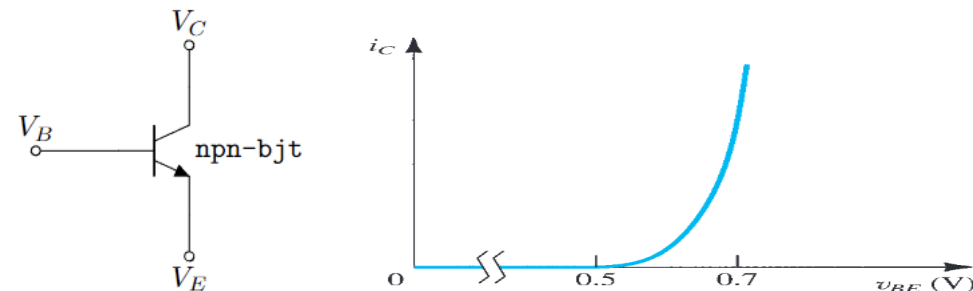
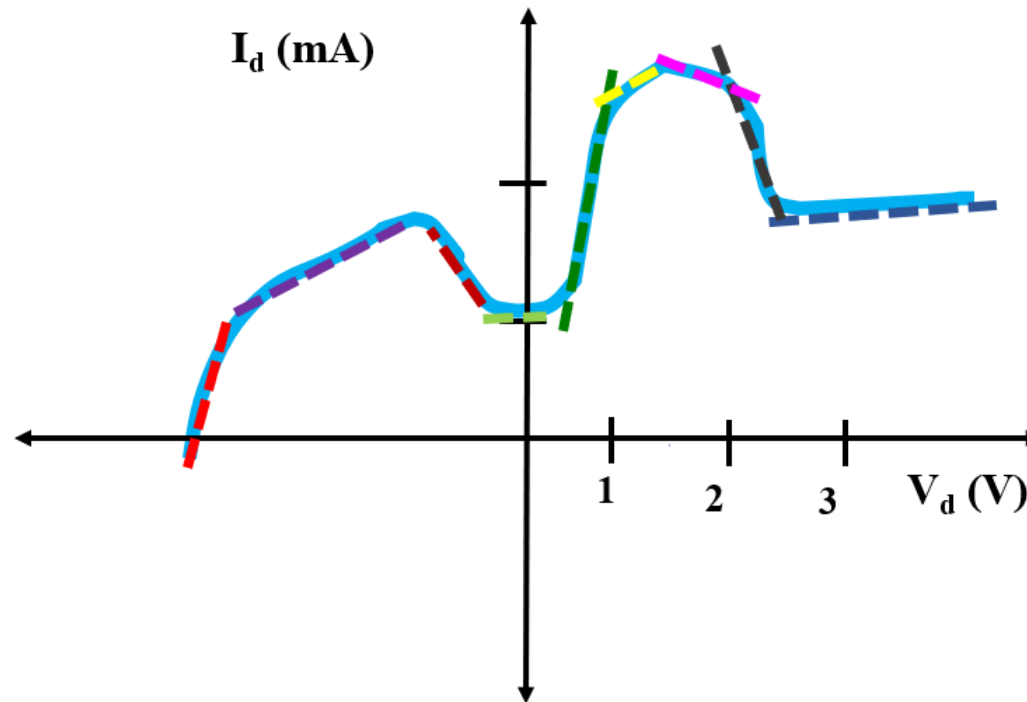
# Piecewise Linear Approximation for NL devices


- Simplifying non-linear IV characteristics by piecewise linear parts.
- Non-linear functions are usually approximated by a series of linear segments that follow the tangent of the non-linear segment as can be seen from the following figure.




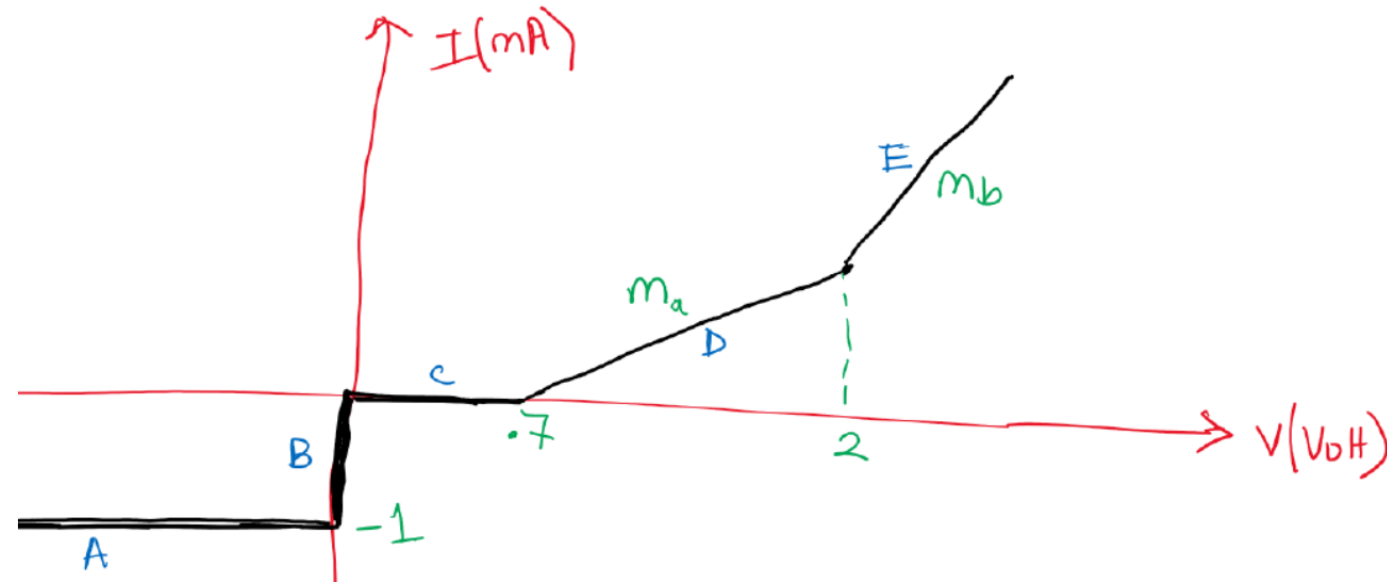
# Piecewise Linear Approximation for NL devices


I-V curve of a hypothetical piecewise linear device is shown below.




Here, P & Q that will come from your student id. For example, if the last 4 digits of your student id is 1234, then  $P=12$ ,  $Q=34$ . In the graph,  $m_a = P$  and  $m_b = Q$

What is the device model and parameter for the regions A, B, C, D, E? If the voltage across the device is 2.1v, what will be the operating region? What is the current flowing through it?
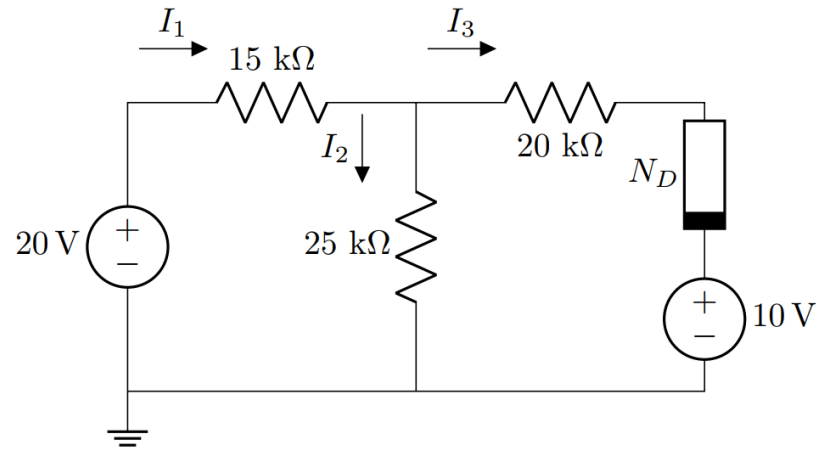
# Piecewise Linear Approximation for NL devices



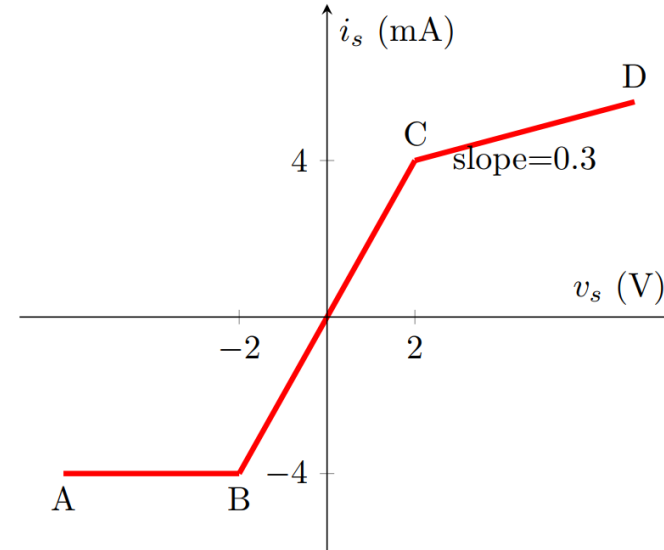(a) A circuit with a non-linear device  $N_D$



(b) IV Characteristics of the non-linear device  $N_D$

- Identify** the equivalent linear circuit models for the 3 linear regions (AB, BC, CD) shown in the IV characteristics of the non-linear device  $N_D$  (Figure (b)) and **calculate** the model parameters. [3]
- Detect** the operating region for the device when  $v_s = 3$  V and **calculate** the current through the device,  $i_s$ , for this voltage (hint: use Figure (b) and answers from previous part). [1+1]
- Show** the alternative representation of the circuit in Figure (a). [1.5]
- Assume that the non-linear device  $N_D$  has been replaced with its equivalent linear device of segment BC. **Draw** the alternative representation of the circuit again by replacing  $N_D$ . [0.5]
- Apply** KVL and KCL on the circuit of part (d) to calculate the values of  $I_1$ ,  $I_2$ , and  $I_3$ . [3]