

Assignment - 3

Name: Md. Minhazul Mowla

ID: 23201390

Section: 01

Course: CSE251

Submission Date: 23/8/25

Ans. to the ques. No. 1



a

A rectifier converts AC to DC. In a full-wave bridge, during each half-cycle a pair of diodes conducts and flips the negative half-upright, so that the load sees the absolute value of the input minus two diode drops in series.

b

$$5\cos(2\pi 60t) \text{ V} = 5\cos(377t) \text{ V} \rightarrow v_{in}$$

$$v_o = 5 - (2 \times 0.7) = 3.6$$

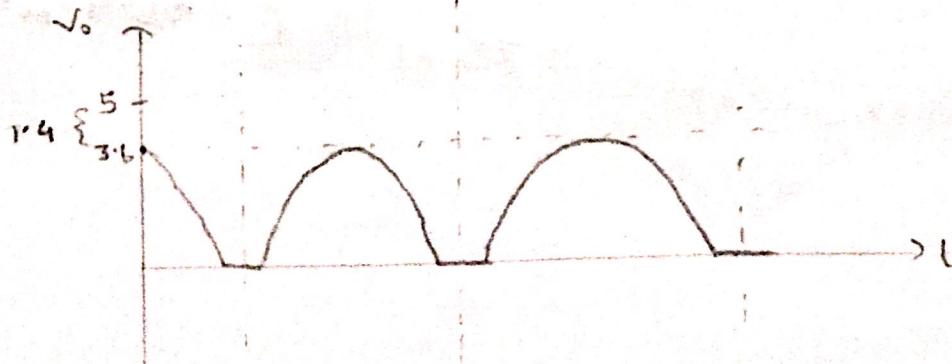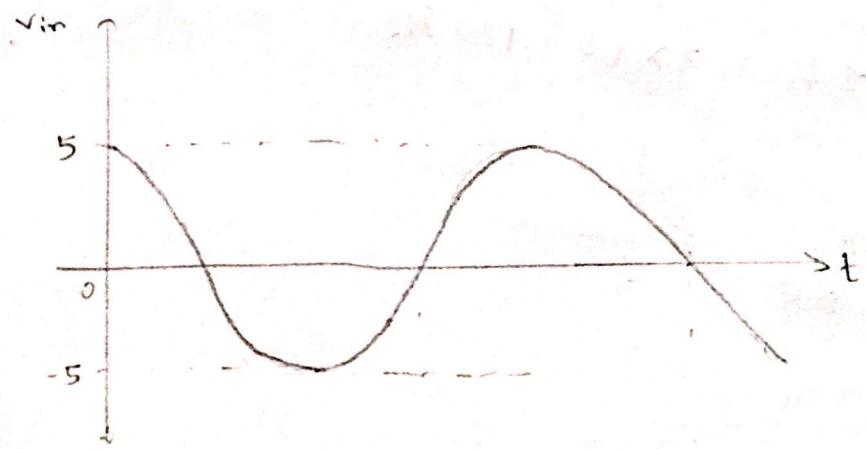

C

$$V_{DC} = \frac{2\sqrt{m}}{\pi} - 2V_{D_0} = \frac{2 \times 5}{3.1416} - 2 \times (0.7) = 1.78 \text{ V}$$

I

$$V_n = +0.2 - (-0.2) = 0.4 \text{ V}$$

$$V_p = 5 - 2 \times (0.7) \approx 3.6 \text{ V}$$

$$R = 2 \text{ k}\Omega = 2 \times 10^3 \text{ }\Omega$$

$$f_s = 60 \text{ Hz}$$

$$f_n = \cancel{23 \times} 2 f_s = 2 \times 60 = 120 \text{ Hz}$$

$$V_n = \frac{V_p}{f_n R C} \quad \cancel{\text{in}}$$

$$\Rightarrow 0.4 = \frac{3.6}{120 \times 2 \times 10^3 \times C}$$

$$\therefore C = \frac{3.6}{120 \times 2 \times 10^3 \times 0.4} = 3.75 \times 10^{-5} \text{ F} = 35.4 \text{ nF}$$

$$\underline{V_{DCe}} = V_p - \frac{V_n}{2}$$
$$= 3.6 - \frac{0.4}{2}$$
$$= 3.4$$

From eq C, $\underline{V_{DC}} = 1.78 \text{ V}$

Adding the capacitor made the N_{PC} almost twice.

Ans. to the ques. No. 2

a

$$V_p = V_m = 10 \text{ V}$$

$$V_{D_0} = 0.4 \text{ V}$$

$$V_{DC} = \frac{V_m}{\pi} - \frac{1}{2} V_{D_0} = \frac{10}{3.1416} - \frac{1}{2} (0.4) = 2.98 \text{ V}$$

b

$$V_n = 0.3 - (-0.3) = 0.6 \text{ V}$$

$$f_n = 55 \text{ Hz}$$

$$R = 2.5 \text{ k}\Omega = 2.5 \times 10^3 \Omega$$

$$V_p = V_m - V_{D_0} = 10 - 0.4 = 9.6$$

$$V_n = \frac{V_p}{f_n R C}$$

$$\Rightarrow 0.6 = \frac{9.6}{55 \times 2.5 \times 10^3 \times C}$$


$$\therefore C = \cancel{1964 \text{ F}} \times 10^{-4} \text{ F}$$

$$= \cancel{164 \text{ F}} \mu\text{F}$$

$$\therefore C = 1.164 \times 10^{-4} \text{ F}$$

$$= 116.4 \mu\text{F}$$

c

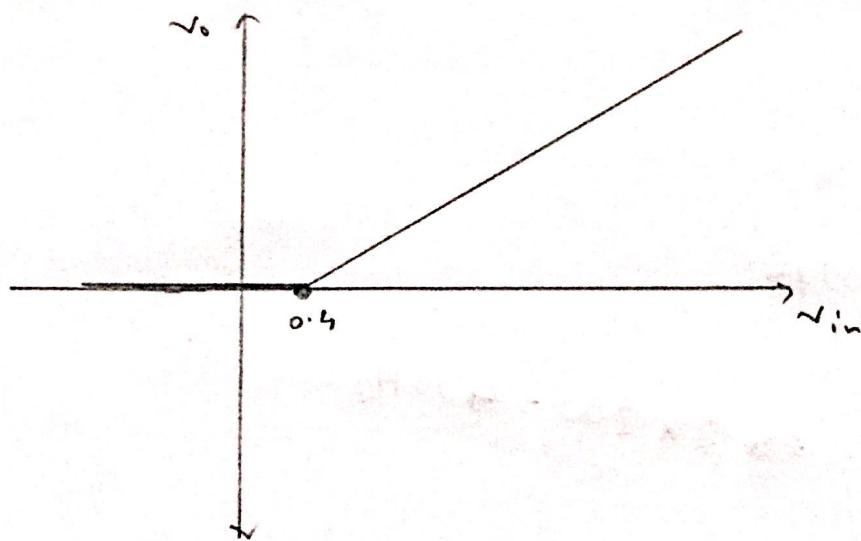

Ans. to the ques No.-3

a

$$v_s(t) = 7 \sin(400\pi t)$$



$$\therefore \omega = 400\pi$$

$$\Rightarrow 2\pi f_s = 400\pi$$

$$\therefore f_s = 200 \text{ Hz}$$

$$\therefore f_n = 2f_s = \cancel{2 \times 200} = 400 \text{ Hz}$$

b

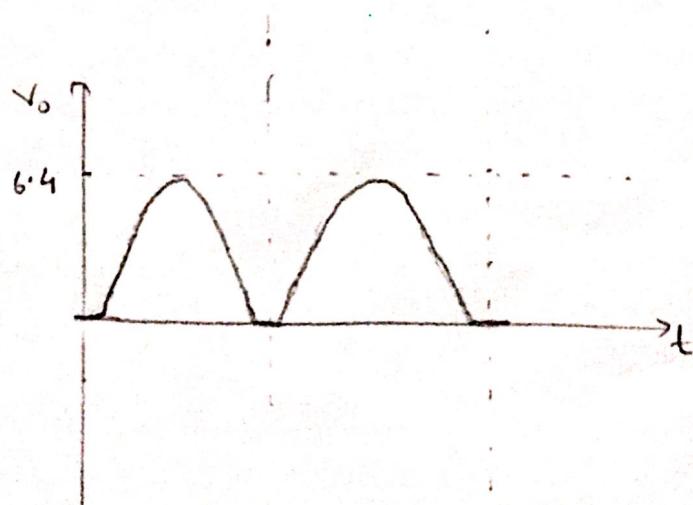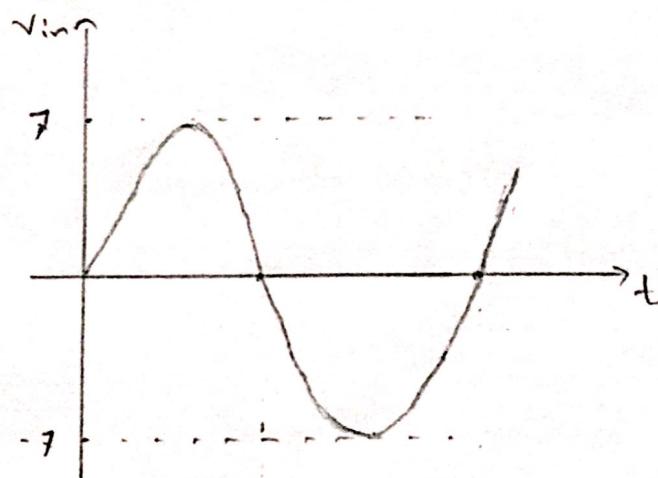

$$\begin{aligned} v_o &= 7 - (2 \times 0.3) \\ &= 6.4 \end{aligned}$$

c

$$R = 5 \text{ k}\Omega = 5 \times 10^3 \Omega$$

$$C = 100 \text{ nF} = 100 \times 10^{-9} \text{ F}$$

$$V_p = V_m - 2V_{D_0} = 7 - (2 \times 0.3) = 6.4 \text{ V}$$

$$f_n = 400 \text{ Hz}$$

$$V_n = \frac{V_p}{f_n RC} = \frac{6.4}{400 \times 5 \times 10^3 \times 100 \times 10^{-9}} = 0.032 \text{ V} = 32 \text{ mV}$$

d

i. ~~I can~~ increase C

ii. increase R

iii. increase frequency

e

$$f_n = 400 \text{ Hz}$$



Ans. to the Ques. No. 4

a i


$$V_m = 15 \text{ V}$$

$$V_{D_0} = 0.7 \text{ V}$$

$$V_p = 15 - 0.7 = 14.3 \text{ V}$$

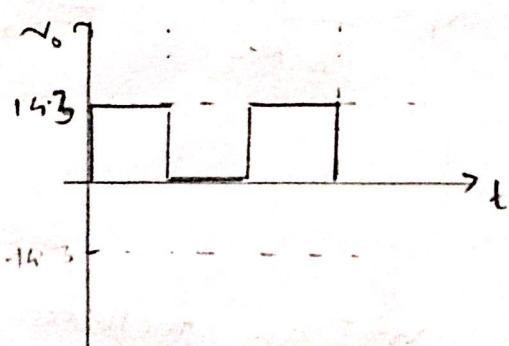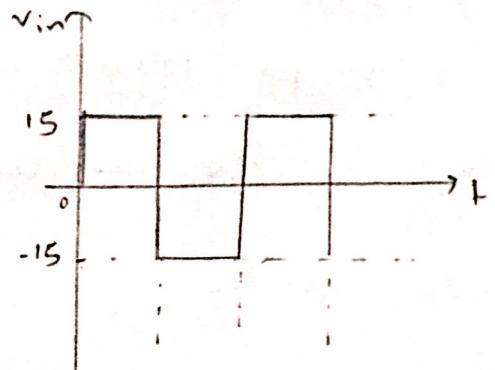

b ii

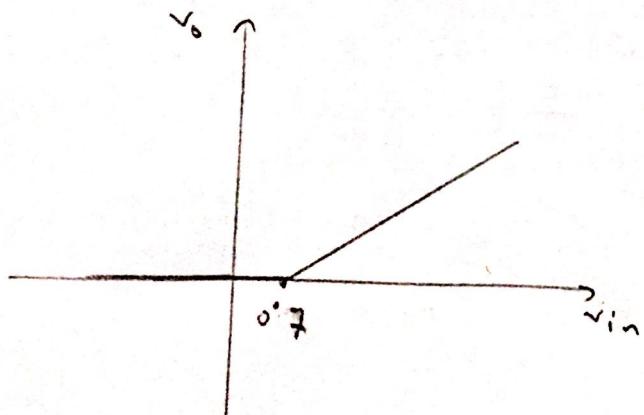

Ans. to the Ques. No. 5


i

$$V_m = 15 \text{ V}$$


$$V_{b_0} = 0.7 \text{ V}$$

$$V_p = 15 - 2 \times (0.7)$$

$$= 13.6 \text{ V}$$

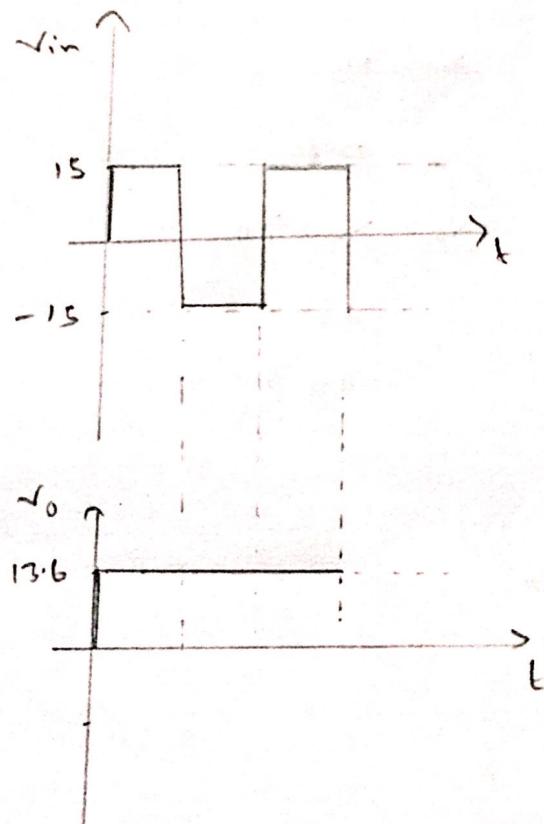

ii

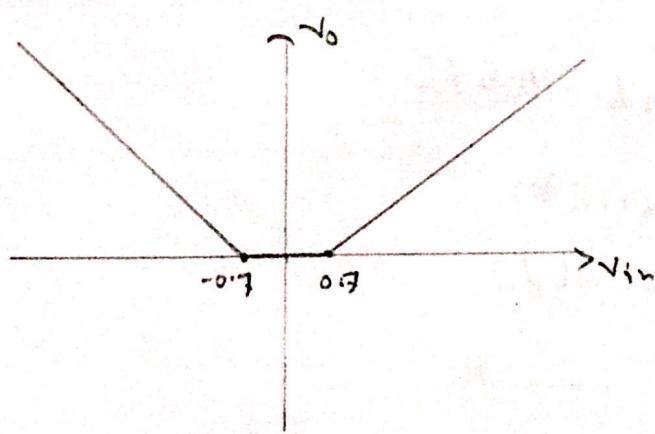


Ans. to the Ques. No. 6

a

$$V_m = 15$$

$$V_{D_0} = 0.7$$
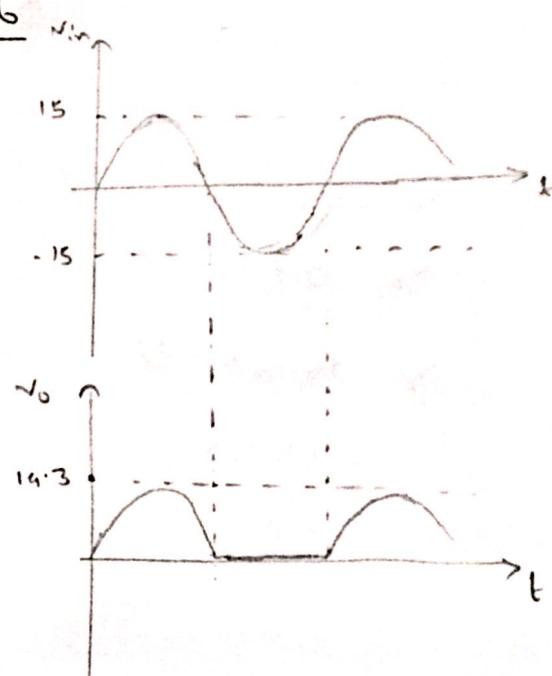
$$\begin{aligned} V_p &= V_m - V_{D_0} \\ &= 15 - 0.7 \\ &= 14.3 \end{aligned}$$



b

$$V_{DC} = \frac{V_m}{\pi} - \frac{1}{2} V_{D_0} = \frac{15}{3.1416} - (\frac{1}{2} \times 0.7) = 4.92 \text{ V}$$

c

$$V_p = 14.3$$

$$V_n = 14.3 \times 4\% = 0.572$$

$$R = 5k\Omega = 5 \times 10^3 \Omega$$

$$V_i = 15 \sin(2000\pi t)$$

$$f_s = \frac{2000\pi}{2\pi} = 1000 \text{ Hz}$$


$$f_n = 2 \times 1000 \text{ Hz}$$

$$V_o = \frac{V_p}{f_n RC}$$

$$\Rightarrow 0.572 = \frac{14.3}{1000 \times 5 \times 10^3 \times C}$$

$$\therefore C = 5 \times 10^{-6} F = 5 \mu F$$

d

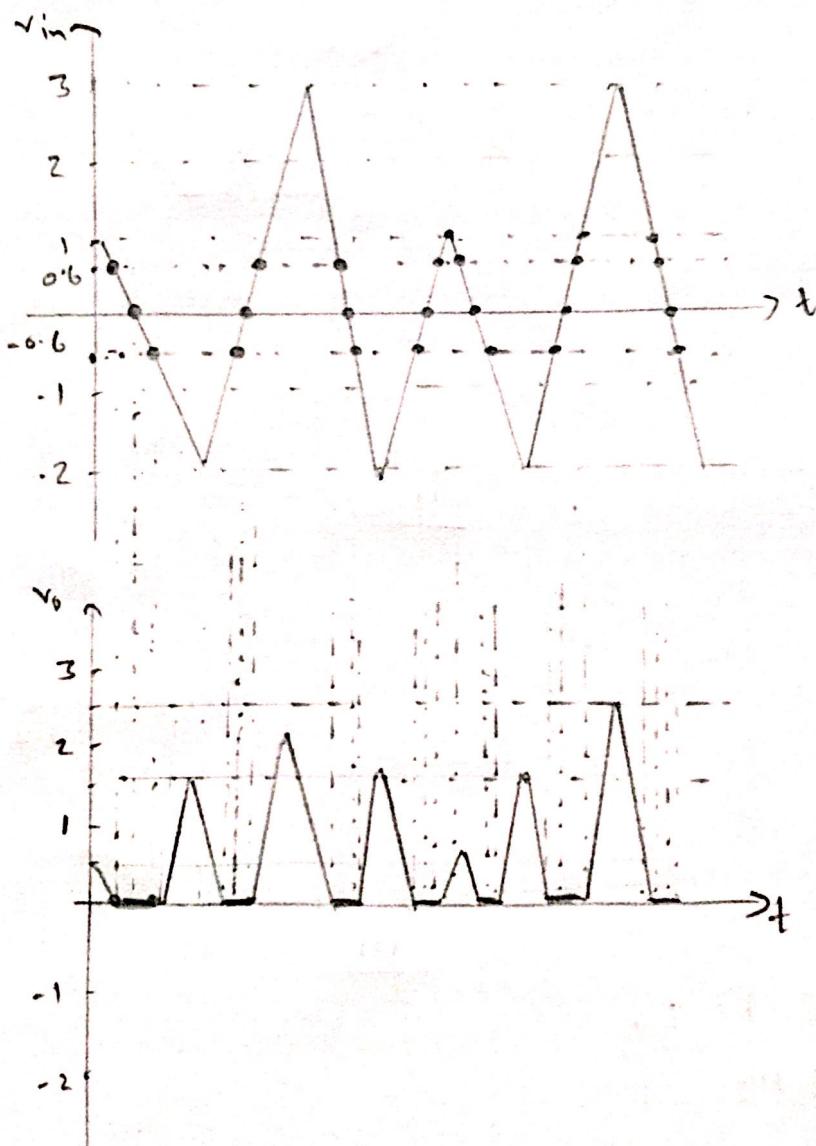


Ans. to the Ques. No. 7


$$v_m = \frac{6 - (-2)}{2} = 3$$

$$v_{D_0} = 0.7$$

$$v_D = 3 - 0.7 = 2.3$$

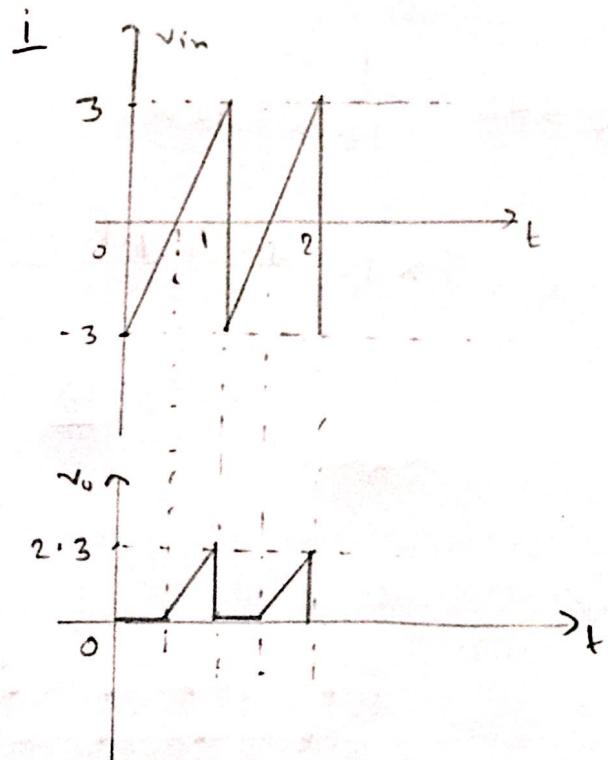

ii

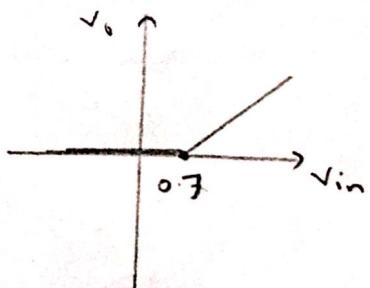

iii

$$T = 2 - 1 = 1 \text{ s}$$

$$\therefore f_s = 1 \text{ Hz}$$



$$\therefore f_n = 1 \text{ Hz}$$

Ans. to the que. No.-8

$$V_m = \frac{4-(-2)}{2} = 3$$

$$V_{D_0} = 0.7$$

$$V_p = 3 - 2 \times (0.7) = 1.6$$

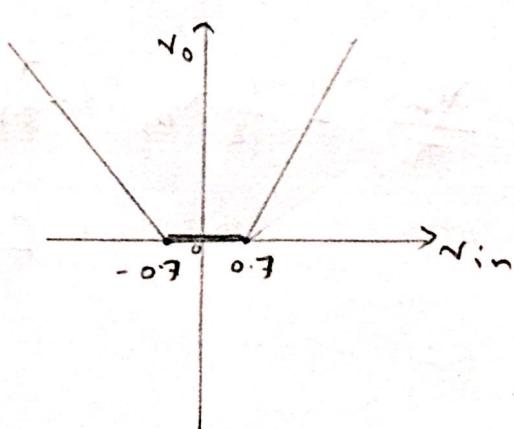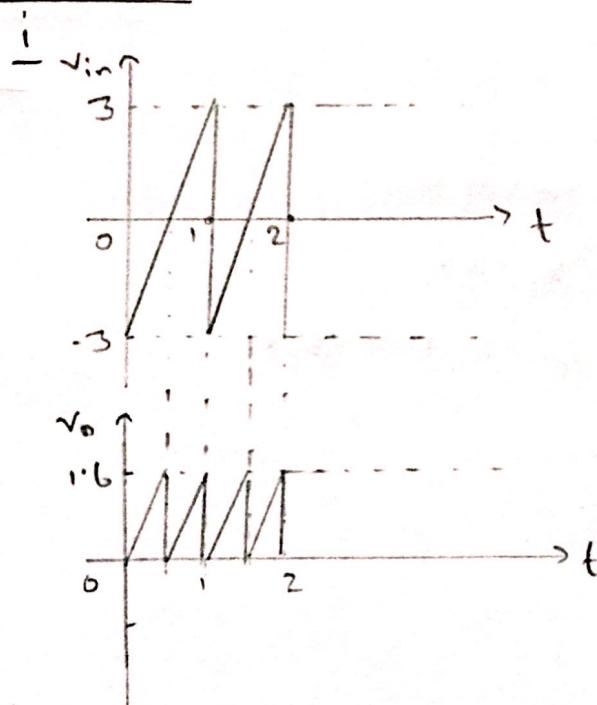

$$T = 2 - 1 = 1 \text{ s}$$

$$\therefore f_s = 1 \text{ Hz}$$

$$\therefore f_n = 2 \times f_s = 2 \times 1 = 2 \text{ Hz}$$


Ans. to the Ques. No. 3

a

$$V_m = 4 \text{ V}$$

$$V_{D_0} = 1 \text{ V}$$

$$V_p = 4 - 1 = 3 \text{ V}$$

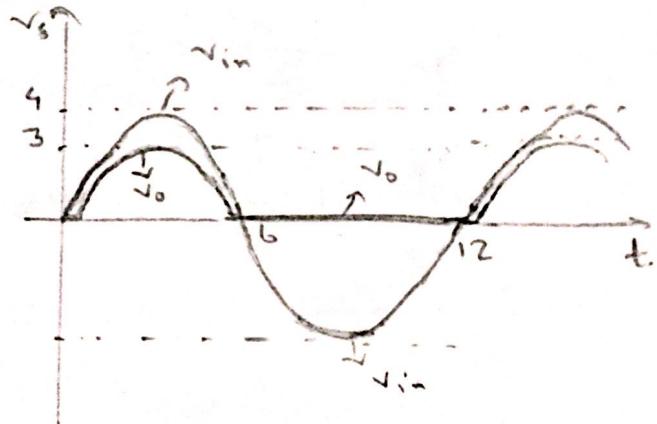

b

$$V_{DC} = \frac{V_m}{\pi} - \frac{1}{2} V_{D_0} = \frac{4}{3.1416} - \left(\frac{1}{2} \times 1 \right) = 0.77 \text{ V}$$

c

at t_1 ,

$$i = 4 \sin(\omega t_1)$$

$$\omega t_1 = \sin^{-1} \left(\frac{1}{4} \right)$$

$$\approx 14.98^\circ$$

$$; N_m = 4$$

$$\begin{aligned}
 \text{We know that, } \frac{T}{2} &\rightarrow 180^\circ \text{ on } \pi \rightarrow t_2 = \frac{T}{2} - t_1 \\
 &= 180^\circ - 14.98^\circ \\
 &= 165.52^\circ
 \end{aligned}$$

: The diode conduct from $14^{\circ}48'$ to $165^{\circ}52'$.

: Fraction of time for which diode

conducts : $\frac{165^{\circ}52' - 14^{\circ}48'}{360^{\circ}} \times 100\%$

= 48.97%

= 41.95%

Ans to the que No. - 10

Q
Full-wave rectifier was used to rectify the sinusoidal voltage.

$$T_0 = 2 \text{ ms}$$

$$T_{in} = 4 \text{ ms}$$

$$f_{in} = 250 \text{ Hz}$$

$$f_{out} = 500 \text{ Hz}$$

$$\therefore T_0 = \frac{1}{2} T_{in}$$

$$\therefore f_{out} = 2 \times f_{in}$$

\therefore Full-wave

b

$$R = 4.5 \Omega \approx 4.5 \times 10^3 \Omega$$

$$V_{b_0} = 0.5 V$$

$$f_{in} = 250 \text{ Hz}$$

~~for ka~~:

$$f_n = 250 \times 2 = 500 \text{ Hz}$$

$$V_p = 3.5$$

~~for V_n~~

$$V_n = 3.5 - 3 = 0.5$$

$$V_n = \frac{V_p}{f_n R C} \approx$$

$$\Rightarrow 0.5 = \frac{3.5}{500 \times 4.5 \times 10^3 \times C}$$

$$\therefore C = 3.11 \times 10^{-6} F$$

$$\approx 3.11 \mu F$$

c

$$V_p = V_m - 2V_{b_0}$$

$$\Rightarrow V_m = V_p + 2V_{b_0} = 3.5 + 2 \times 0.5 = 4.5 V$$

$$V_s(t) = \cancel{4.5 \sin(250\pi t)} \quad 4.5 \sin(500\pi t) \checkmark$$

