



Assignment 2
CSE251

Submitted By:

Iftekhar Hossain Rahi
22201168
Sec: 06

Submitted To :

Munshi Sanowar Raihan
Lecturer,
Brac University



BRAC UNIVERSITY

Department of Computer Science and Engineering

Assignment 02, Summer 2024

CSE 251: Electronic Devices and Circuits


1.

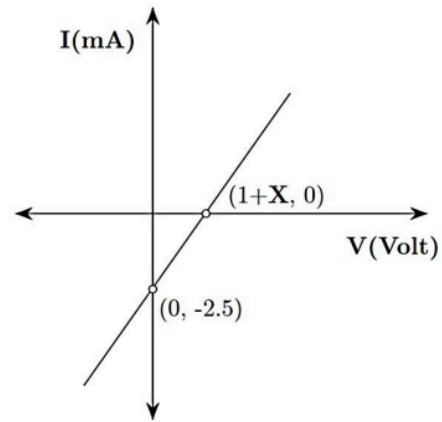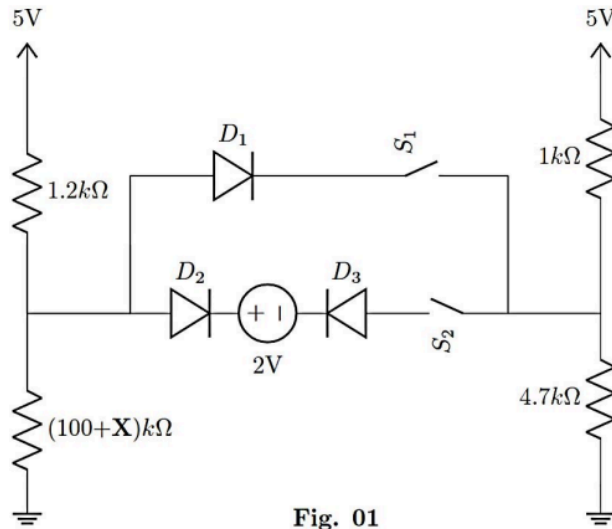

In Fig. 01, a circuit is shown with two ‘off’ switches, S1 and S2. Assume X =last digit of your ID. ($V_{D0} = 0.7V$).

- If only S1 is ‘on’, determine the current passing through the diode D1. [4]
- If only S2 is ‘on’, determine the current passing through the diode D2 and D3. [4]
- Find and draw the unknown component in Fig. 02. [2]

2.

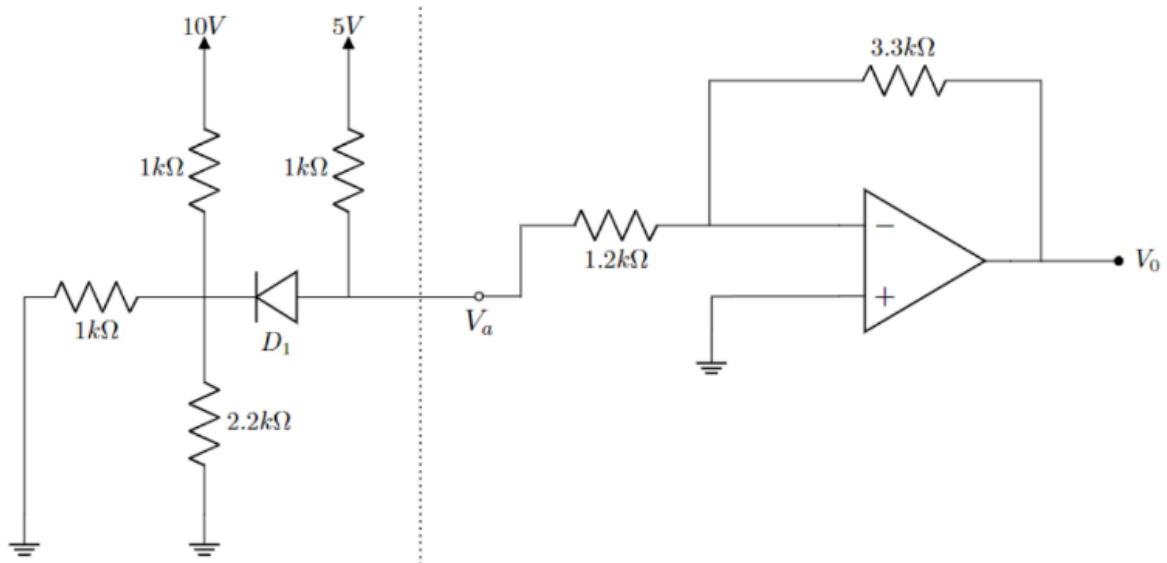


As shown in the figure, a resistor-diode network is constructed and one of its nodes V_a is fed to the ideal Op-Amp to the right side. The Op-Amp has been connected to the saturation voltages $V_{sat}^+ = +10\text{ V}$ and $V_{sat}^- = -10\text{ V}$. Assume that $V_D = 0.7\text{ V}$.

- Determine whether the diode D_1 is conducting or not. [4]
- Calculate which $1\text{ k}\Omega$ resistor (left/middle/right) dissipates the least power. [3]
- Analyze the entire circuit to find what the voltage V_0 should be. [3]

1.


My ID = 22201168

Q.

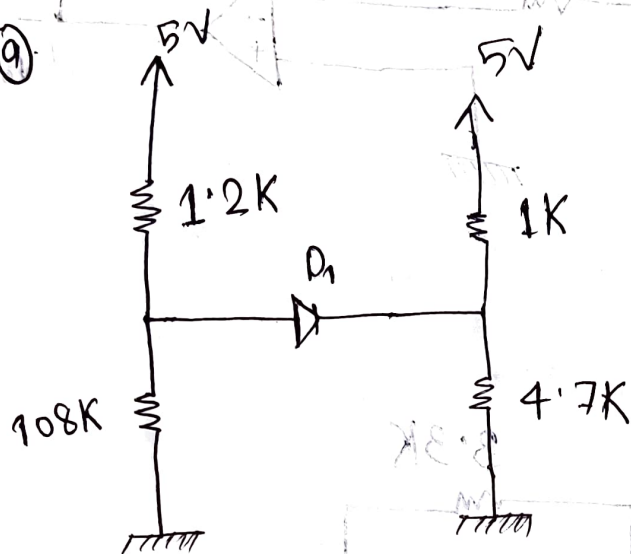

$$V_D = 0.7V$$

Lets assume the diode is ON,

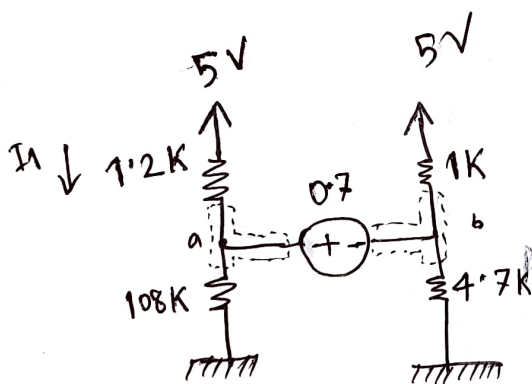

$$V_a = \left(\frac{2.8}{1.2 + 108} \right) \times 5 = 1.04V$$

$$V_b = \left(\frac{8.8}{1 + 4.7} \right) \times 5 = 8.8V$$

It's a super node, $V_a - V_b = 0.7$

$$V_a - V_b = 0.7$$

Again $\Rightarrow V_a = 0.7 + V_b$ — (1)

$$\frac{V_a - 5}{1.2} + \frac{V_a - 0}{108} + \frac{V_b - 5}{1} + \frac{V_b - 0}{4.7} = 0$$

$$\Rightarrow \frac{V_a}{1.2} - \frac{5}{1.2} + \frac{V_a}{108} + V_b - 5 + \frac{V_b}{4.7} = 0$$

$$\Rightarrow \cancel{\frac{V_a}{1.2}} + \cancel{\frac{V_a}{108}} + \cancel{\frac{V_a}{4.7}}$$

$$\Rightarrow -\frac{5}{1.2} + \frac{V_a}{108} + V_b - 5 + \frac{V_b}{4.7} = 0$$

$$\Rightarrow \frac{V_a}{1.2} + \frac{V_a}{108} + V_b + \frac{V_b}{4.7} = 5 + \frac{5}{1.2}$$

$$\Rightarrow \frac{91 V_a}{108} + \frac{57 V_b}{47} = \frac{55}{6}$$

$$\Rightarrow \frac{91(0.7 + V_b)}{108} + \frac{57 V_b}{47} = \frac{55}{6}$$

$$\Rightarrow \frac{63.7}{108} + \frac{91 V_b}{108} + \frac{57 V_b}{47} = \frac{55}{6}$$

$$\Rightarrow 2.055 V_b = 8.57$$

$$\therefore \boxed{V_b = 4.17}$$

$$\therefore V_a = 0.7 + 4.17 = 4.87$$

$$\therefore \boxed{V_a = 4.87}$$

In Va node,

$$\Rightarrow I_1 = I_D + I_L$$


$$\Rightarrow I_D = I_1 - I_L$$

$$= \frac{5 - 4.87}{1.2} - \left(\frac{4.87}{108} \right)$$



$$= 0.1083 - 0.0487$$
$$= 0.0596 \text{ mA}$$

\therefore If only S_1 is on, the current passing through the diode is 0.0596 mA
(Ans)

②

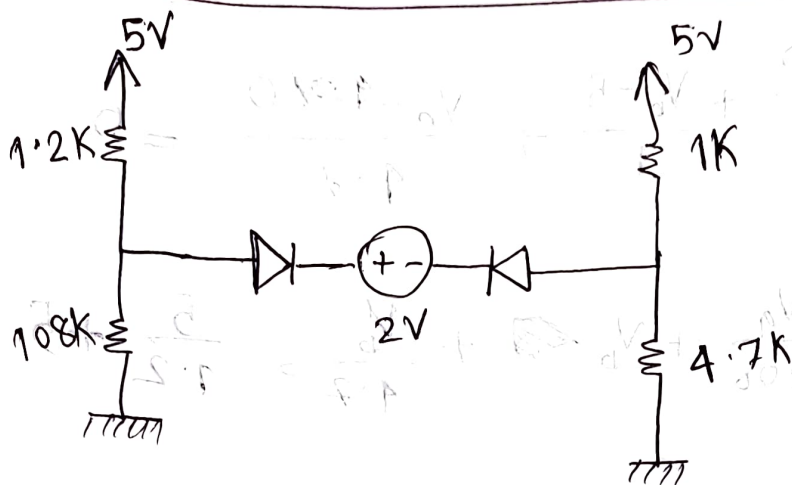

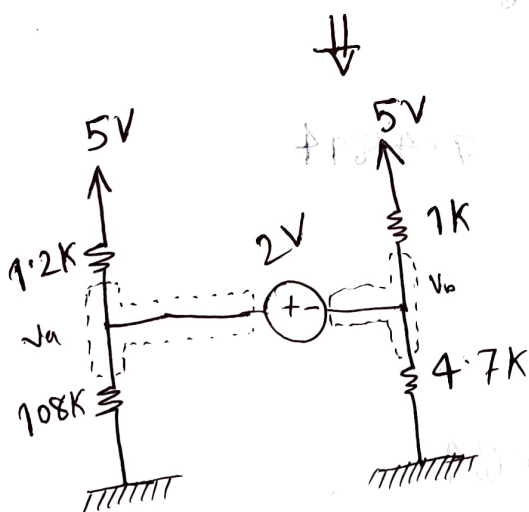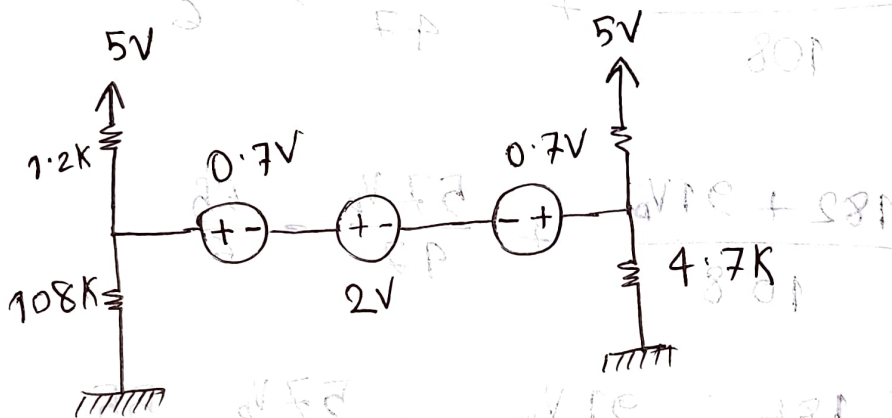Let's assume that both of the diode is on,



$$V_a - V_b = 2$$

$$\therefore V_a = 2 + V_b \quad \text{--- (1)}$$

$$\frac{V_a - 5}{1.2} + \frac{V_a - 0}{108} + \frac{V_b - 5}{1} + \frac{V_b - 0}{4.7} = 0$$

$$\Rightarrow \frac{V_a}{1.2} + \frac{V_a}{108} + V_b + \frac{V_b}{4.7} = \frac{5}{1.2} + 5 = \frac{55}{6}$$

$$\Rightarrow \frac{91V_a}{108} + \frac{57V_b}{47} = \frac{55}{6}$$

$$\Rightarrow \frac{91(2 + V_b)}{108} + \frac{57V_b}{47} = \frac{55}{6}$$

$$\Rightarrow \frac{182 + 91V_b}{108} + \frac{57V_b}{47} = \frac{55}{6}$$

$$\Rightarrow \frac{182}{108} + \frac{91V_b}{108} + \frac{57V_b}{47} = \frac{55}{6}$$

$$\Rightarrow 2.055V_b = 7.4814$$

$$\Rightarrow V_b = 3.64$$

$$\therefore V_a = 2 + V_b = 5.64$$

At node,

$$I_1 = I_D + I_2$$

$$\Rightarrow I_D = I_1 - I_2$$

$$= \frac{5 - 5.64}{1.2} - \frac{5.64 - 0}{10.8}$$


$$= -0.53 - 0.052$$

$$= -0.582 < 0$$

Assumption

Wrong!

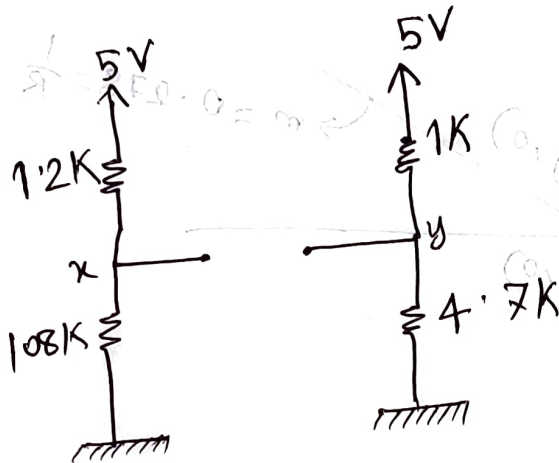Let's assume that both of the diode is off.



$$5 - 0 = 1.2 I_1 + 108 I_1$$

$$\Rightarrow I_1 = 0.045 \text{ mA}$$

$$\therefore \frac{V_x - 0}{108} = 0.045$$

$$\Rightarrow V_x = 4.86$$

$$5 - 0 = 1 I_2 + 4.7 I_2$$


$$\Rightarrow I_2 = 0.877 \text{ mA}$$

$$\frac{V_y - 0}{4.7} = 0.877$$

$$\Rightarrow V_y = 4.122$$

There will be no current flowing through D_2 and D_3 while the S_2 is on.

©

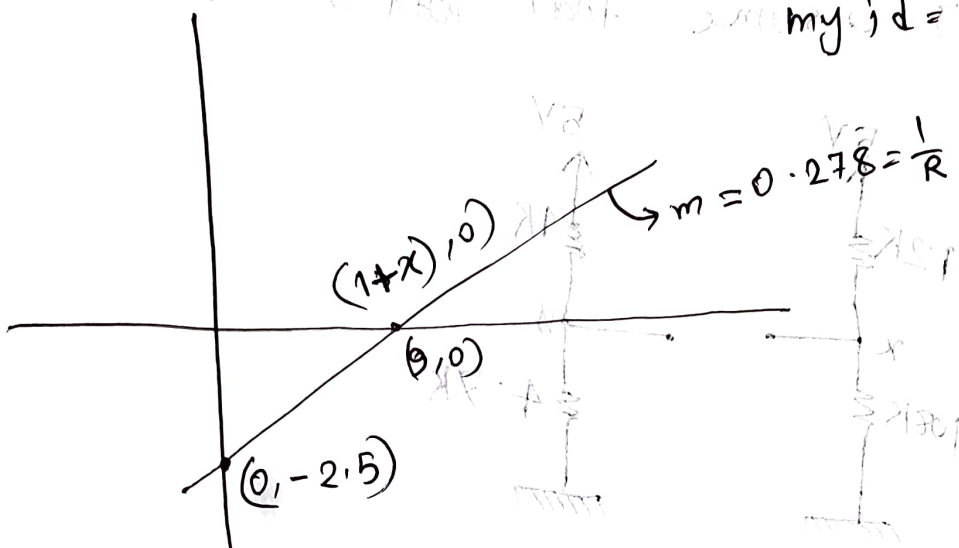

the equation

of the straight line is,

$$\underline{\underline{0 + 2.5}}$$


$$\frac{y - 0}{0 + 2.5} = \frac{x - 9}{9 - 0}$$

$$\Rightarrow 9y = 2.5x - 22.5$$

$$\Rightarrow 2.5x - 22.5$$


$$\therefore y = 0.278x - 2.5$$

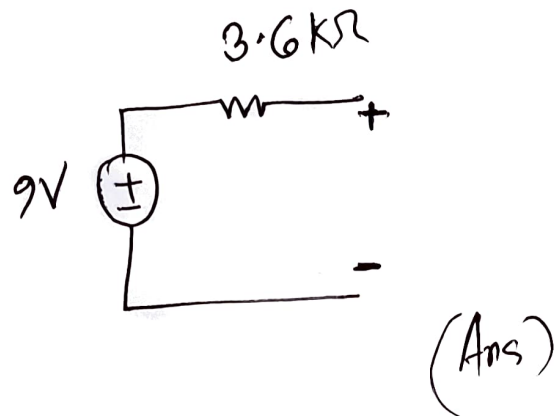The unknown component will be a voltage source with series resistance.




2.

a)

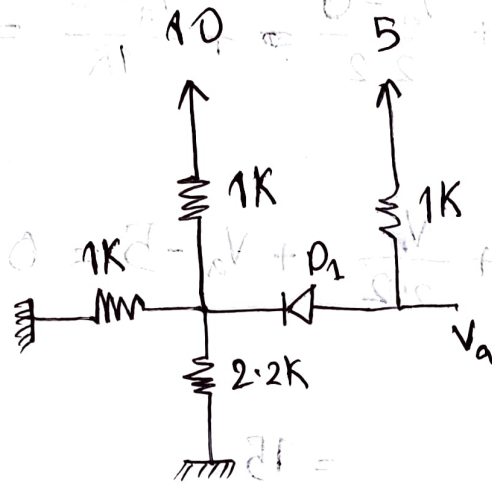

Lets assume that the diode is ON,

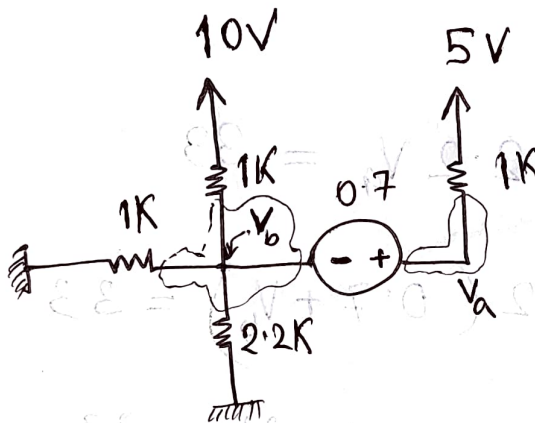

There is 3 node in this circuit. V_a , V_b and ground.
 V_a and V_b is in a supernode.

$$V_a - V_b = 0.7$$

$$\Rightarrow V_a = 0.7 + V_b \quad \text{--- ①}$$

$$\frac{V_b - 10}{1} + \frac{V_b - 0}{1} + \frac{V_b - 0}{2 \cdot 2} + \frac{V_a - 5}{1K} = 0$$

$$\Rightarrow V_b - 10 + V_b + \frac{V_b}{2 \cdot 2} + V_a - 5 = 0$$

$$\Rightarrow 2V_b + \frac{V_b}{2 \cdot 2} + V_a = 15$$

$$\Rightarrow \frac{4 \cdot 4 V_b + V_b + 2 \cdot 2 V_a}{2 \cdot 2} = 15$$

$$\Rightarrow 5.4 V_b + 2 \cdot 2 V_a = 33$$

$$\Rightarrow 5.4 V_b + 2 \cdot 2 (0.7 + V_b) = 33$$

$$\Rightarrow 5.4 V_b + 1.54 + 2 \cdot 2 V_b = 33$$

$$\Rightarrow 7.4 V_b = 31.46$$

$$\therefore V_b = 4.139 \approx 4.14$$

$$\therefore V_a = 0.7 + V_b = 4.84$$

\therefore the current passing through $D_1 = 5 - 4.84$
 $= \cancel{0.16}$
 $= 0.16 \text{ mA}$

$\therefore I_1 > 0$

\therefore The diode is conducting.
(Ans)

(b)

P_{left}

$$= \Delta V I = (V_b - 0) \frac{V_b - 0}{1000}$$

$$= \frac{(4.14)^2}{1000}$$

$$= 0.017139 \approx 0.01714 \text{ Watt}$$

P_{middle}

$$= \Delta V I$$

$$= (10 - 4.14) \frac{(10 - 4.14)}{1000}$$

$$= 0.034339 \approx 0.03434 \text{ Watt}$$

P_{right}



$$= \Delta V I$$

$$= (5 - 4.84) \frac{(5 - 4.84)}{1000}$$

$$= 0.0000256 \text{ watt}$$

\therefore The right $1K$ resistance will ~~dis~~ dissipates the least power. (Ans)

©

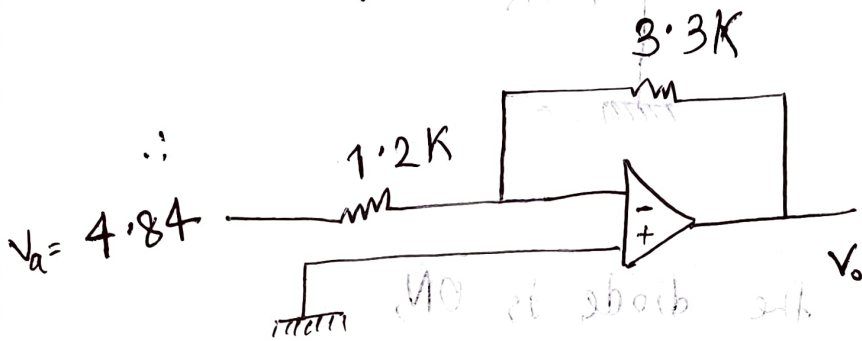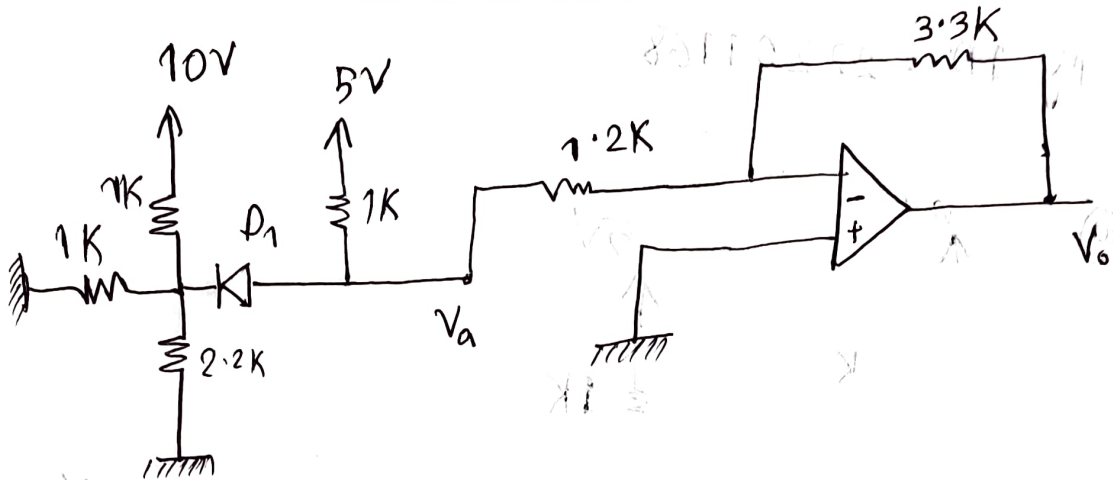

$$\therefore V_{out} = -\left(\frac{R_f}{R_i}\right) V_{in}$$

$$= -\left(\frac{3.3}{1.2}\right) \times 4.84$$

$$= -13.31V$$

(Ans)