

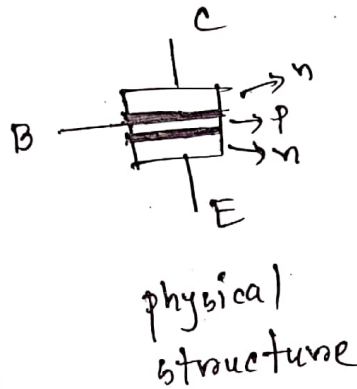


#

physical structure of BJT

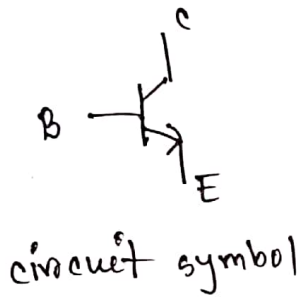

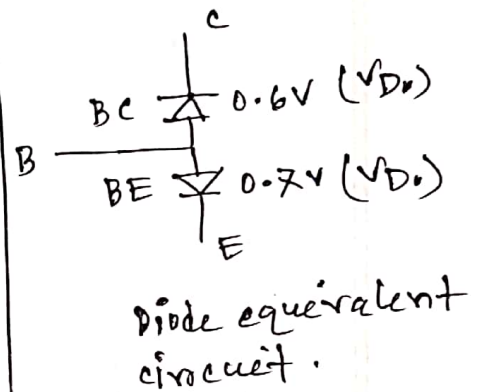Here,
Base is very thin. Emitter is heavily doped, base is lightly doped.



Now will it work like BJT if we put two simple diode like the diode equivalent ckt. configuration?

⇒ No. Because in BJT base is lighter than emitter and collector and emitter is heavily doped and base is lightly doped.


Topic Name : _____

Day : _____

Time : _____

Date : / /

#(Overs) Simplified operation of BJT

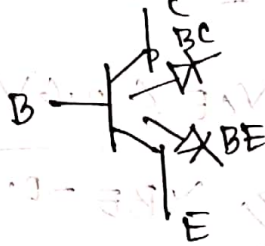


BE → ON, OFF
BC → ON, OFF } 4 combinations so BJT has 4 modes of operation

BE	BC	operation mode / region of BJT
OFF	OFF	cut off
ON	ON	Saturation
ON	OFF	Active
OFF	ON	Reverse Active

→ This 3 modes we will mainly study.

→ very near in practical application.

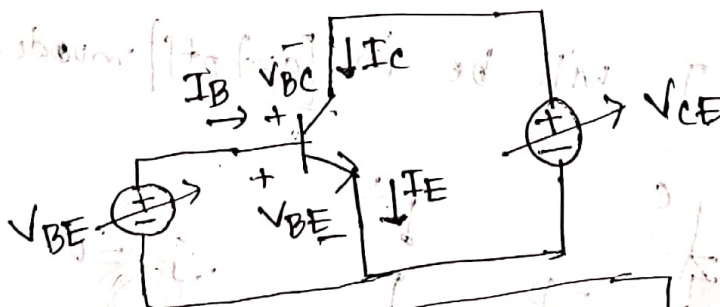For study of BJT we will use this circuit. that is want see how I_B controls I_C vs V_{CE}



$$I_E = I_B + I_C$$

$$V_{BC} = V_{BE} - V_{CE}$$

$$V_{BC} = V_B - V_C$$

$$= (V_B - V_E) - (V_C - V_E)$$

$$= V_{BE} - V_{CE}$$

Topic Name : _____

Day : _____

Time : _____

Date : / /

condition for $BC \Rightarrow OFF$

$$V_{BC} \leq 0.6V$$

$$V_{BE} - V_{CE} \leq 0.6V$$

$$V_{CE} \geq V_{BE} - 0.6V$$

the Base-collector will be off for this condition.

$BE \Rightarrow OFF$

$$V_{BE} \leq 0.7V$$

Case 1: $V_{BE} \leq 0.7$ and $V_{CE} \geq V_{BE} - 0.6$



\Downarrow

$BE \rightarrow OFF$
(diode)

\Downarrow

$BC \rightarrow OFF$
(diode)

BJT will be in cutoff mode.

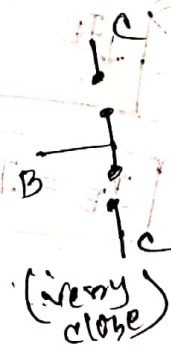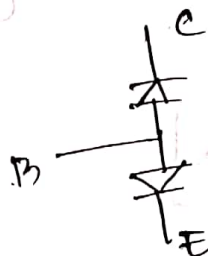

$$\therefore I_C = 0$$

$$I_E = 0$$

$$\therefore I_B = 0 \quad \text{equation}$$


Topic Name : _____

Day : _____

Time : _____


Date : / /

IV will be like this for cutoff:

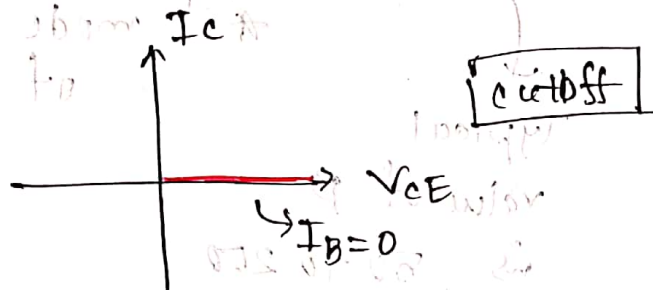


Case 2: $I_B > 0$ and $V_{CE} > V_{BE} - 0.6$
 \Rightarrow $BE \Rightarrow ON$ (diode)
 $BC \Rightarrow OFF$ (diode)

So, Active region.

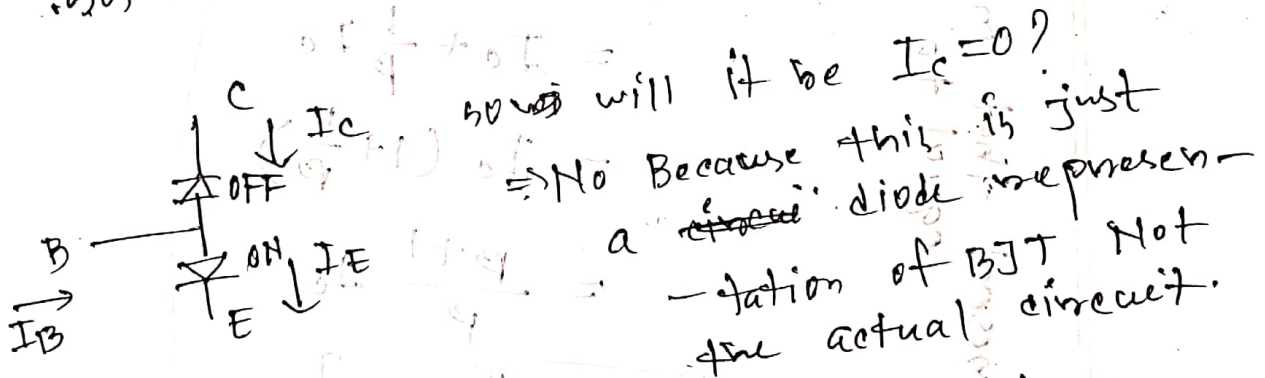

Due to their structure

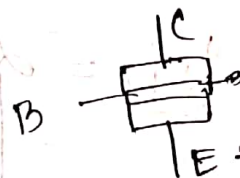

in this active mode huge current starts flowing from collector to emitter.

And this current \propto Base current that is $I_C \propto I_B$

this represent that in active mode I_E is almost equal to I_C

$$\therefore I_C = \beta I_B$$

Typical
value of β
is 50 to 200

* We use this Active
mode for creation
of amplifier

$$\therefore I_C = \beta I_B$$

$$V_{BE} = 0.7V$$

equation

$$I_E = I_C + I_B$$

$$= I_C + \frac{1}{\beta} I_C$$

$$= I_C \left(1 + \frac{1}{\beta}\right)$$

$$= \frac{\beta + 1}{\beta} I_C$$

$$I_C = \frac{\beta}{\beta + 1} I_E$$

$$\therefore I_C = \alpha I_E$$

alpha, this is also a constant
typical value is 0.99

Topic Name : _____

Day : _____

Time : _____ Date : / /

$$V_{CE} \geq V_{BE} - 0.6$$

$$= 0.7 - 0.6$$


$$V_{CE} \geq 0.1 \text{ V}$$

Active Mode


$$I_C = \beta I_B$$

$$V_{BE} = 0.7 \text{ V}$$

Model the BJT with

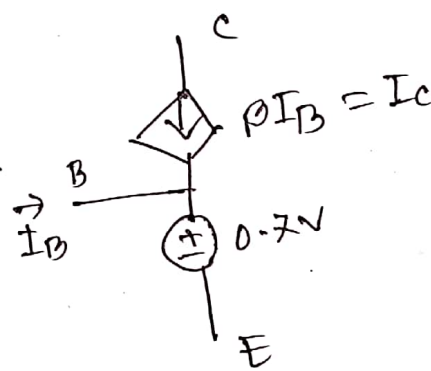

IV of I_C vs V_{CE}

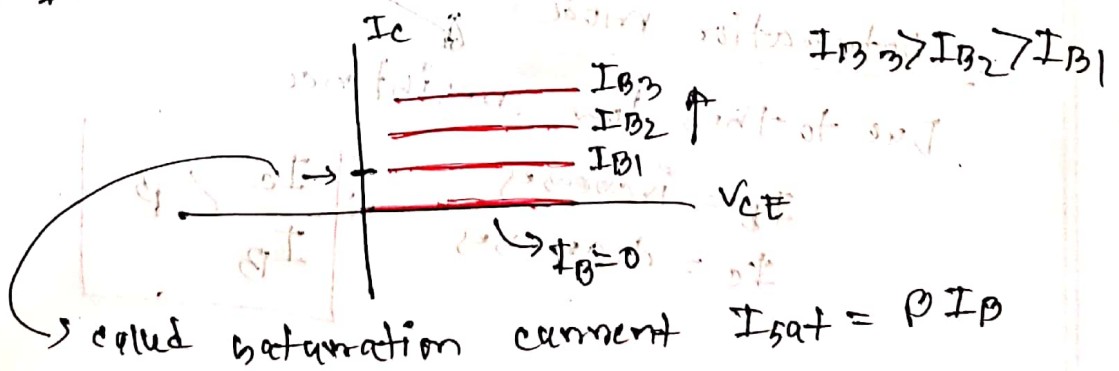

Topic Name : _____

Day : _____

Time : _____

Date : / /

Case 3 :

$$I_B > 0$$



and

$$V_{CE} < V_{BE} = 0.6$$

$B \rightarrow E$ ON
(diode)

$B \rightarrow C$ ON
(diode)

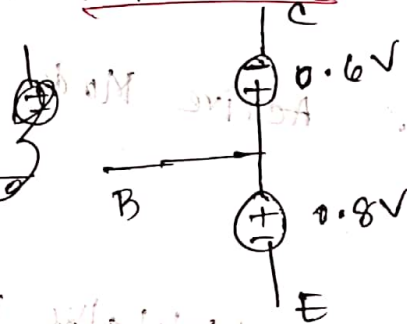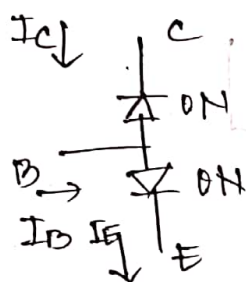\therefore BJT will be in saturation mode.



[using CVD model]

[But in Forward bias mode diode has small resistance]
 \therefore these collector and emitter terminal will have small resistance.

Saturation mode

Due to this low resistance

I_B = increases
 I_C = decreases

$$\frac{I_C}{I_B} < \beta$$

Topic Name : _____

Day : _____

Time : _____ Date : / /


$$V_{CE} = V_{DE} - V_{DE}$$

$$= 0.8 - 0.6$$


$$\boxed{V_{CE} = 0.2 \text{ V}}$$

BJT works like a voltage source of 0.2 V in saturation region.

IV of I_C vs V_{CE} will be like this

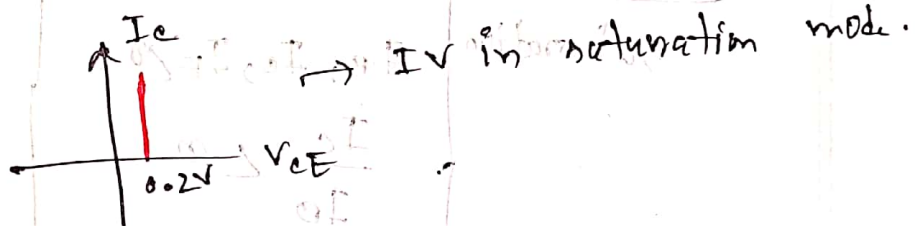

⑧ simplified IV of BJT will be like this

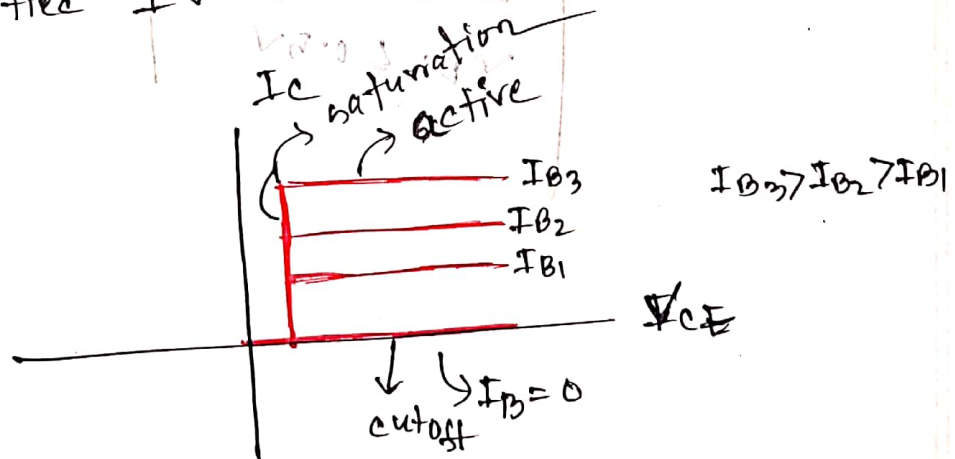

Topic Name : _____

Day : _____

Time : _____ Date : / /

Summary condition and Model :

State	Condition	Equation
Active	$I_B, I_C, I_E > 0$ $V_{CE} > 0.2V$	$V_{BE} = 0.7V$ $I_C = \beta I_B$ $I_C = \alpha I_E$ <div style="display: inline-block; vertical-align: middle; border-left: 1px solid black; padding-left: 5px;"> $\alpha = \frac{\beta}{1+\beta}$ </div>
Saturation	$I_B, I_C, I_E > 0$ $\frac{I_C}{I_B} < \beta$	$V_{BE} = 0.8V$ $V_{CE(sat)} = 0.2V$
Cut off	$V_{BE} \leq 0.7V$ $V_{BC} \leq 0.6V$ $V_{CE} \leq 0.5V$ [some cases]	$I_B = I_C = I_E = 0$


BJT

[Method of 'Assumed state']

Steps:

- ① Assume
- Active $[V_{BE} = 0.7V, I_C = \beta I_B, I_C = \alpha I_E]$ $\alpha = \frac{\beta}{1+\beta}$
 - Saturation $[V_{BE} = 0.8V, V_{CE} = 0.2V]$
 - cut off $[I_B = I_C = I_E = 0]$
- ② solve [KVL, KCL, nodal]
- ③ verify
- Active $[V_{CE} > 0.2V]$
 - Saturation $[\frac{I_C}{I_B} < \beta]$
 - cutoff $[V_{BE} \leq 0.7V \text{ and } V_{BC} \leq 0.6V]$
- $\hookrightarrow \leq 0.5V$
↓
[some cases]

Ex 4 :

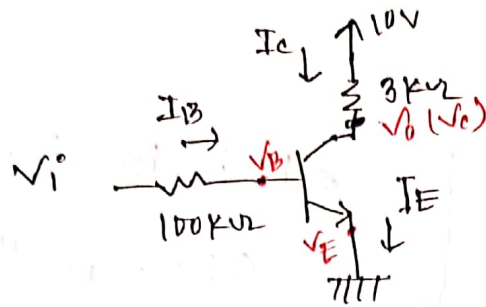

* Find V_o for $V_i = 1V$

Given, $\beta = 100$

Assumption: Active Mode

$$\therefore V_{BE} = 0.7V \quad \text{and} \quad I_C = \beta I_B$$

$$\therefore V_{BE} = V_B - V_E = 0.7$$

$$\Rightarrow V_B - 0 = 0.7$$

$$\therefore V_B = 0.7V$$

$$I_B = \frac{V_i - V_B}{R_B} = \frac{1 - 0.7}{100} = 0.003 \text{ mA}$$

$$\therefore I_C = \beta I_B = 100 * 0.003 = 0.3 \text{ mA}$$

$$\text{now, } 10 - V_C = I_C * 3$$

$$\Rightarrow V_C = 10 - 3I_C = 10 - 3 * 0.3 = 9.1V$$

Verification:


$$V_{CE} = V_C - V_E = 9.1 - 0 = 9.1V$$

$$\therefore V_{CE} > 0.2$$

\therefore Assumption is correct.

$$\therefore \boxed{V_o = V_C = 9.1V} \quad \text{Answer}$$

EX2:

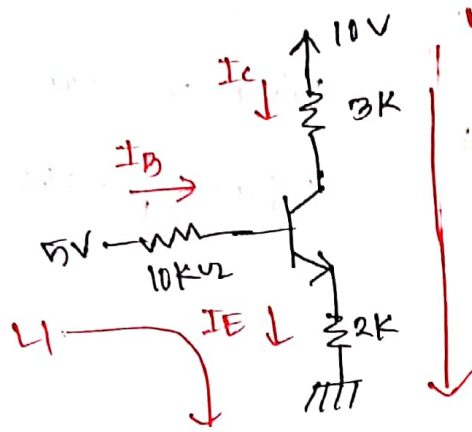

* Find I_B , I_C , I_E , V_{CE}

Given, $\beta = 100$

Assumption 1: Active Mode

$$\therefore V_{BE} = 0.7V \quad \text{and} \quad \begin{matrix} I_C = \beta I_B \\ I_C = \alpha I_E \end{matrix} \quad \left. \vphantom{\begin{matrix} I_C = \beta I_B \\ I_C = \alpha I_E \end{matrix}} \right\} \rightarrow I_E = \frac{\beta}{\alpha} I_B$$

~~$\therefore I_E = \frac{\beta}{\alpha} I_B$~~

$$I_E = I_B + I_C$$

$$\alpha = \frac{\beta}{1+\beta} = \frac{100}{100+1} = 0.999$$

KVL along L1:

$$10I_B + V_{BE} + 2I_E = 5 - 0$$

$$\Rightarrow 5V = 10I_B + 0.7 + 2 \frac{\beta}{\alpha} I_B$$

$$\Rightarrow I_B = 0.02 \text{ mA}$$

$$\therefore I_C = 100 \times I_B = 100 \times 0.02 = 2 \text{ mA}$$

$$I_E = I_C + I_B = 2.02 \text{ mA}$$

~~V_{CE}~~

$$I_E = \frac{V_E - 0}{2}$$

$$\Rightarrow V_E = 4.04V$$

$$I_C = \frac{10 - V_C}{3}$$

$$\Rightarrow V_C = 4V$$

$$\therefore V_{CE} = V_C - V_E = 4 - 4.04V = -0.04V$$

Verification:

$$V_{CE} = -0.04V < 0.2V$$

\therefore Assumption 1. wrong.

Assumption 2: Saturation Mode

$$\therefore V_{BE} = 0.8V$$

$$V_{CE} = 0.2V$$

$$\text{KCL: } I_E = I_C + I_B \quad \therefore I_E - I_C - I_B = 0 \quad \text{--- (1)}$$

$$\text{KVL along L1: } 10I_B + V_{BE} + 2I_E = 5 - 0$$

$$\Rightarrow 10I_B + 0.8 + 2I_E = 5 = 0 \quad \text{--- (2)}$$

KVL along L2:

$$3I_C + V_{CE} + 2I_E = 10 - 0$$

$$\Rightarrow 3I_C + 0.2 + 2I_E - 10 = 0 \quad \text{--- (3)}$$

$$\text{From (1), (2) and (3), } I_E = 1.975, I_C = 1.95, I_B = 0.025$$

Verification:

$$\frac{I_c}{I_B} = \frac{1.075}{0.025} = 78$$

$$\therefore \frac{I_c}{I_B} < \beta$$

\therefore Assumption 2 correct.

$$\begin{aligned} \therefore I_E &= 1.075 \\ I_c &= 1.075 \\ I_B &= 0.025 \end{aligned} \quad \left. \vphantom{\begin{aligned} I_E &= 1.075 \\ I_c &= 1.075 \\ I_B &= 0.025 \end{aligned}} \right\} \text{(Answer)}$$