



Inspiring Excellence

**Course Code:** CSE251

**Course Title:** Electronic Devices and Circuits

**Semester:** Spring-2023

**STUDENT NAME**

**ID**

**Md. Mahir Faisal**

**21301371**

Tajwar Al Haque Robin

21101312

Mansura Akhter

21201329

Anika Islam

21101298

**Experiment Number:** 04

**Experiment Name:** Study of Half-Wave and Full-Wave rectifiers

**Group No:** 03

**Section:** 12

**Submitted by:** Md. Mahir Faisal, **ID:** 21301371

# Data Sheet

## Data Sheet

### Experimental Observation: HW Rectifier

#### 1. HW Rectifier without Capacitor:

Peak output voltage,  $V_p$  (oscilloscope) = **4.24V**

Average or DC output voltage,  $V_{dc}$  (multimeter in DC mode) = **1.24 V**

RMS or AC output voltage,  $V_{r-rms}$  (multimeter in AC mode) = **1.699 V**

#### 2. HW Rectifier with $1\mu F$ Capacitor: $C = 0.97 \mu F$

Peak output voltage,  $V_p$  (oscilloscope) = **4.24 V**

Peak to peak ripple voltage,  $V_{r(p-p)}$  (oscilloscope) = **3.14 V**

Average or DC value of the ripple voltage,  $V_{dc}$  (multimeter in DC mode) = **2.23**

RMS or AC value of the ripple voltage,  $V_{r-rms}$  (multimeter in AC mode) = **1.062**

Ripple factor,  $r = V_{r-rms}/V_{dc}$  = **0.476**

#### 3. HW Rectifier with $4.7\mu F$ Capacitor: $C = 4.86 \mu F$

Peak output voltage,  $V_p$  (oscilloscope) = **4.08 V**

Peak to peak ripple voltage,  $V_{r(p-p)}$  (oscilloscope) = **1.28 V**

Average or DC value of the ripple voltage,  $V_{dc}$  (multimeter in DC mode) = **3.387 V**

RMS or AC value of the ripple voltage,  $V_{r-rms}$  (multimeter in AC mode) = **0.378**

Ripple factor,  $r = V_{r-rms}/V_{dc}$  = **0.116**

### Theoretical Calculation: HW Rectifier

#### 1. HW Rectifier Without Capacitor:

Peak output voltage,  $V_p$  (see the experimental observation) = **4.24**

Peak input voltage,  $V_m$  = **5 V**

Diode voltage,  $V_{D0} = 0.7 V$

DC output voltage of the rectifier,  $V_{dc} = \frac{V_m}{\pi} - \frac{V_{D0}}{2} = 1.24 V$

RMS or AC output voltage,  $V_{r-rms} = \frac{V_p}{2} = 2.12$

#### 2. HW Rectifier With $1\mu F$ Capacitor:

Peak output voltage,  $V_p$  (see the experimental observation) = **4.24**

Peak to peak ripple voltage,  $V_{r(p-p)}$  (see the experimental observation) = **3.44**

DC value of the ripple voltage,  $V_{dc} = V_p - \frac{V_{r(p-p)}}{2} = 2.52$

RMS value of the ripple voltage,  $V_{r-rms} = \frac{V_{r(p-p)}}{2\sqrt{3}} = 0.993$

Ripple factor,  $r = V_{r-rms}/V_{dc}$  = **0.394**

#### 3. HW Rectifier with $4.7\mu F$ Capacitor:

Peak output voltage,  $V_p$  (see the experimental observation) = **4.08**

Peak to peak ripple voltage,  $V_{r(p-p)}$  (see the experimental observation) = **1.28**

DC value of the ripple voltage,  $V_{dc} = V_p - \frac{V_{r(p-p)}}{2} = 3.44$

RMS value of the ripple voltage,  $V_{r-rms} = \frac{V_{r(p-p)}}{2\sqrt{3}} = 0.3695$

Ripple factor,  $r = V_{r-rms}/V_{dc}$  = **0.1074**

### Experimental Observation: FW Rectifier

#### 1. FW Rectifier without Capacitor:

Peak output voltage,  $V_p$  (oscilloscope) = **3.68 V**

Average or DC output voltage,  $V_{dc}$  (multimeter in DC mode) = **2.061**

RMS or AC output voltage,  $V_{r-rms}$  (multimeter in AC mode) = **1.281**

#### 2. FW Rectifier with $1\mu F$ Capacitor:

Peak output voltage,  $V_p$  (oscilloscope) = **3.52 V**

Peak to peak ripple voltage,  $V_{r(p-p)}$  (oscilloscope) = **1.76**

Average or DC value of the ripple voltage,  $V_{dc}$  (multimeter in DC mode) = **2.621**

RMS or AC value of the ripple voltage,  $V_{r-rms}$  (multimeter in AC mode) = **0.540**

Ripple factor,  $r = V_{r-rms}/V_{dc}$  = **0.206028**

#### 3. FW Rectifier with $4.7\mu F$ Capacitor:

Peak output voltage,  $V_p$  (oscilloscope) = **3.44 V**

Peak to peak ripple voltage,  $V_{r(p-p)}$  (oscilloscope) = **0.64 V**

Average or DC value of the ripple voltage,  $V_{dc}$  (multimeter in DC mode) = **3.069**

RMS or AC value of the ripple voltage,  $V_{r-rms}$  (multimeter in AC mode) = **0.148**

Ripple factor,  $r = V_{r-rms}/V_{dc} = \underline{0.0182}$

### Theoretical Calculation: FW Rectifier

#### 1. FW Rectifier without Capacitor:

Peak output voltage,  $V_p$  (see the experimental observation) = **3.68 V** *28/02/23*

Peak input voltage,  $V_m = 5 V$

Diode voltage,  $V_{D0} = 0.7 V$

DC output voltage of the rectifier,  $V_{dc} = \frac{2V_m}{\pi} - 2V_{D0} =$

RMS or AC output voltage,  $V_{r-rms} = \frac{V_p}{\sqrt{2}} =$

#### 2. FW Rectifier with $1\mu F$ Capacitor:

Peak output voltage,  $V_p$  (see the experimental observation) = **3.52**

Peak to peak ripple voltage,  $V_{r(p-p)}$  (see the experimental observation) = **1.76**

DC value of the ripple voltage,  $V_{dc} = V_p - \frac{V_{r(p-p)}}{2} = \underline{2.64}$

RMS value of the ripple voltage,  $V_{r-rms} = \frac{V_{r(p-p)}}{2\sqrt{3}} = \underline{0.508}$

Ripple factor,  $r = V_{r-rms}/V_{dc} = \underline{0.192}$

#### 3. FW Rectifier with $4.7\mu F$ Capacitor:

Peak output voltage,  $V_p$  (see the experimental observation) = **3.44**

Peak to peak ripple voltage,  $V_{r(p-p)}$  (see the experimental observation) = **0.64**

DC value of the ripple voltage,  $V_{dc} = V_p - \frac{V_{r(p-p)}}{2} = \underline{3.12}$

RMS value of the ripple voltage,  $V_{r-rms} = \frac{V_{r(p-p)}}{2\sqrt{3}} = \underline{0.184}$

Ripple factor,  $r = V_{r-rms}/V_{dc} = \underline{0.058}$

### Table for Comparison


Use the experimental and theoretical data for comparison.

	C(uF)	Experimental Observation			Theoretical Calculation		
		Vr-rms (V)	Vdc (V)	Ripple Factor	Vr-rms (V)	Vdc (V)	Ripple Factor
HW	1	1.062	2.23	0.476	0.993	2.52	0.394
	4.7	0.578	3.381	0.116	0.3695	3.49	0.1079
FW	1	0.590	2.621	0.206028	0.508	2.64	0.192
	4.7	0.148	3.069	0.0482	0.184	3.12	0.058


*✓*  
28/02/23
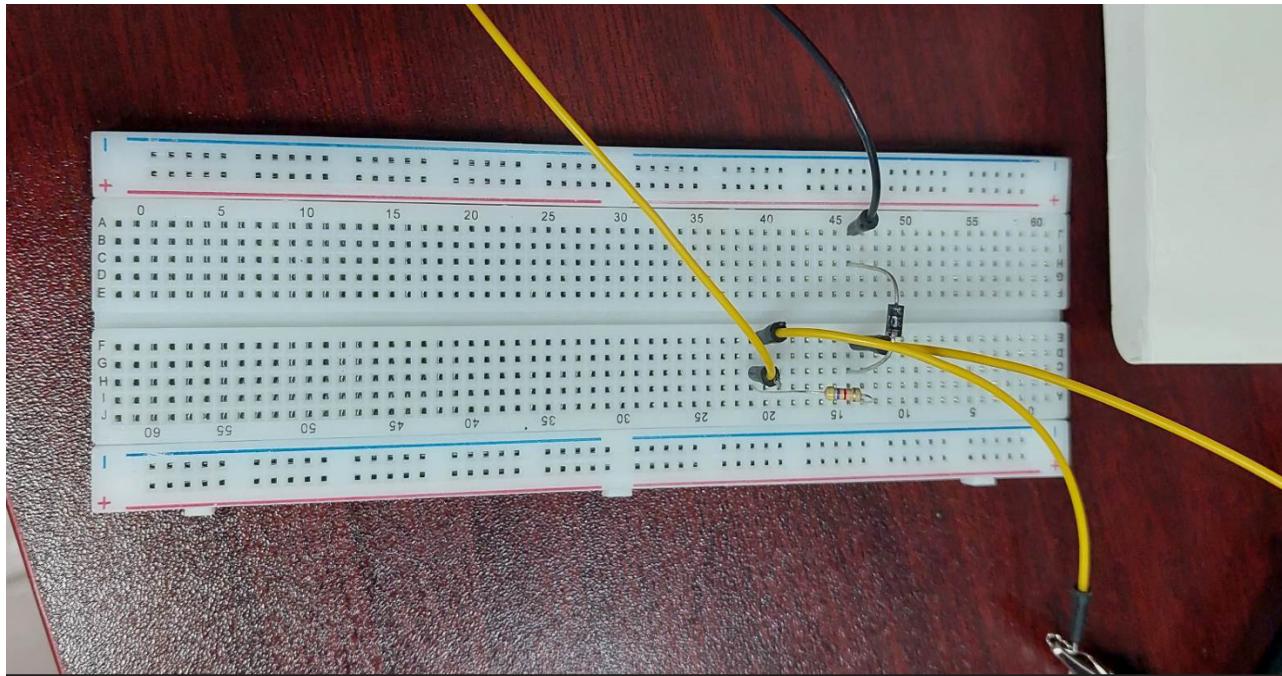
## Half-Wave rectifier


Circuit: Half-Wave rectifier (Without capacitor)



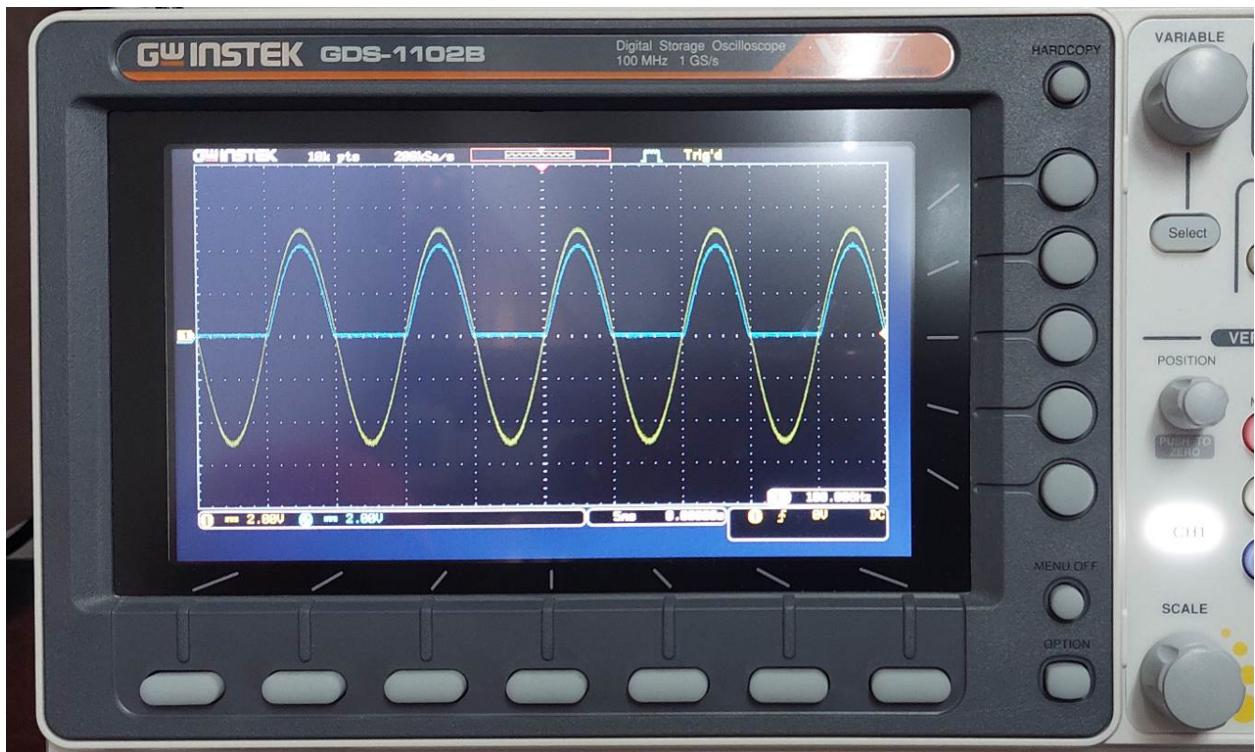
Graph: Input & output for Half-wave rectifier (Without capacitor)



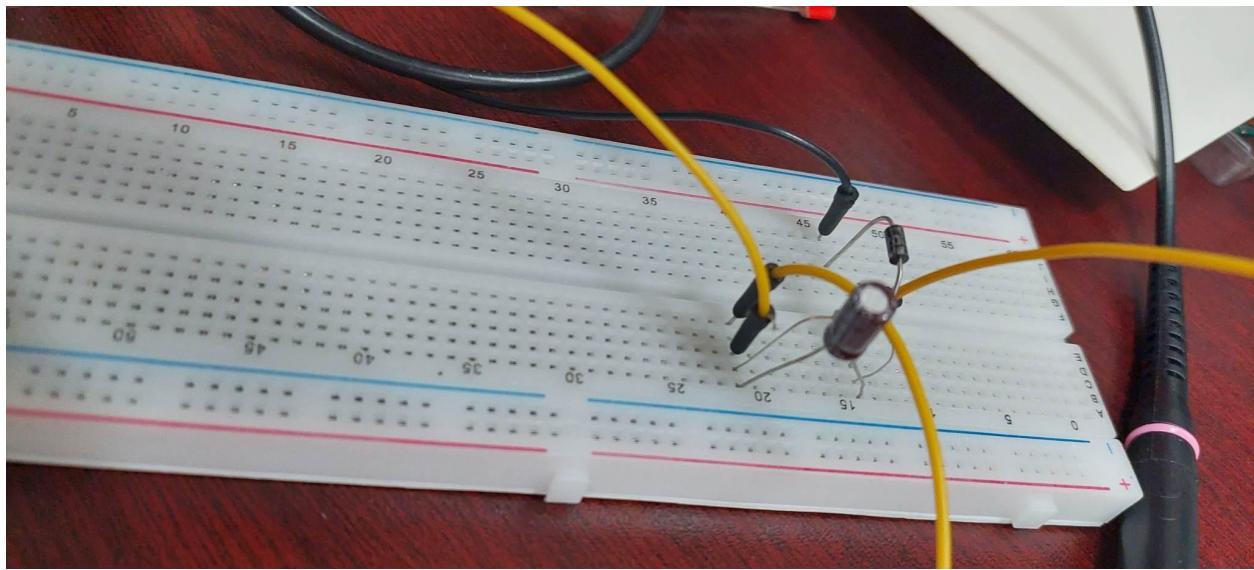
**Circuit: Half-Wave rectifier (Using 1uF capacitor)**



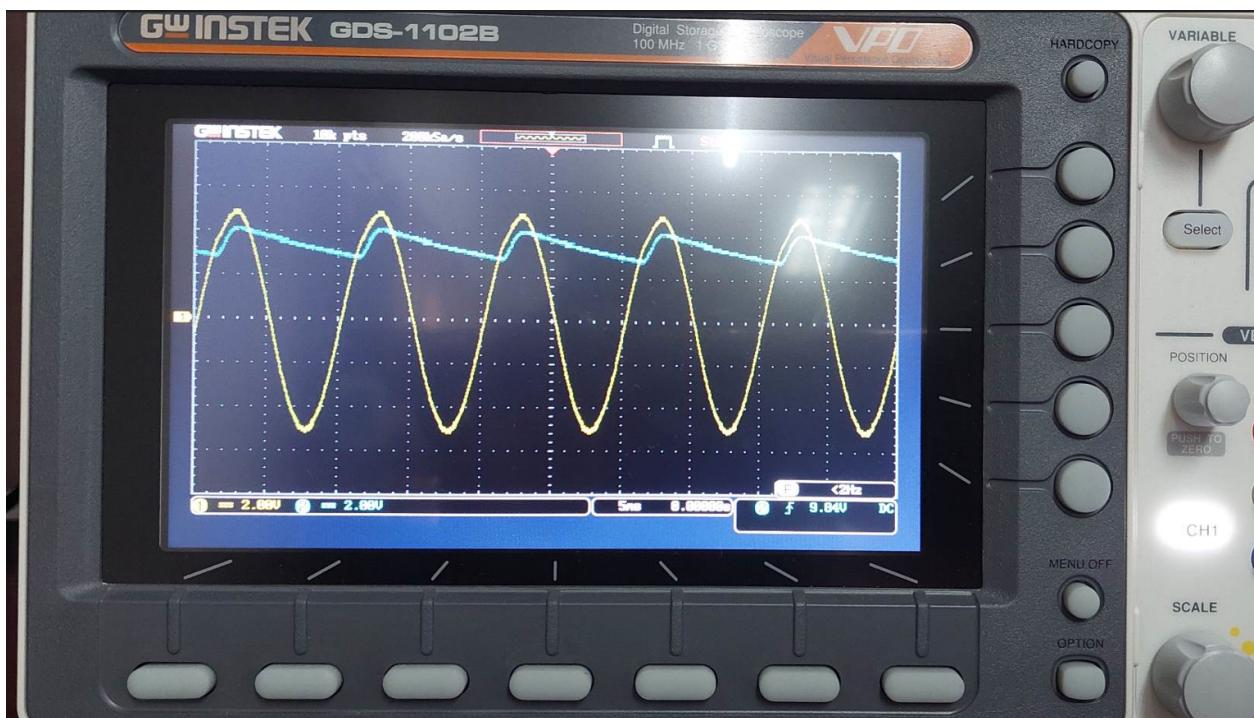
**Graph: Input & output for Half-Wave rectifier (Using 1 uF capacitor)**


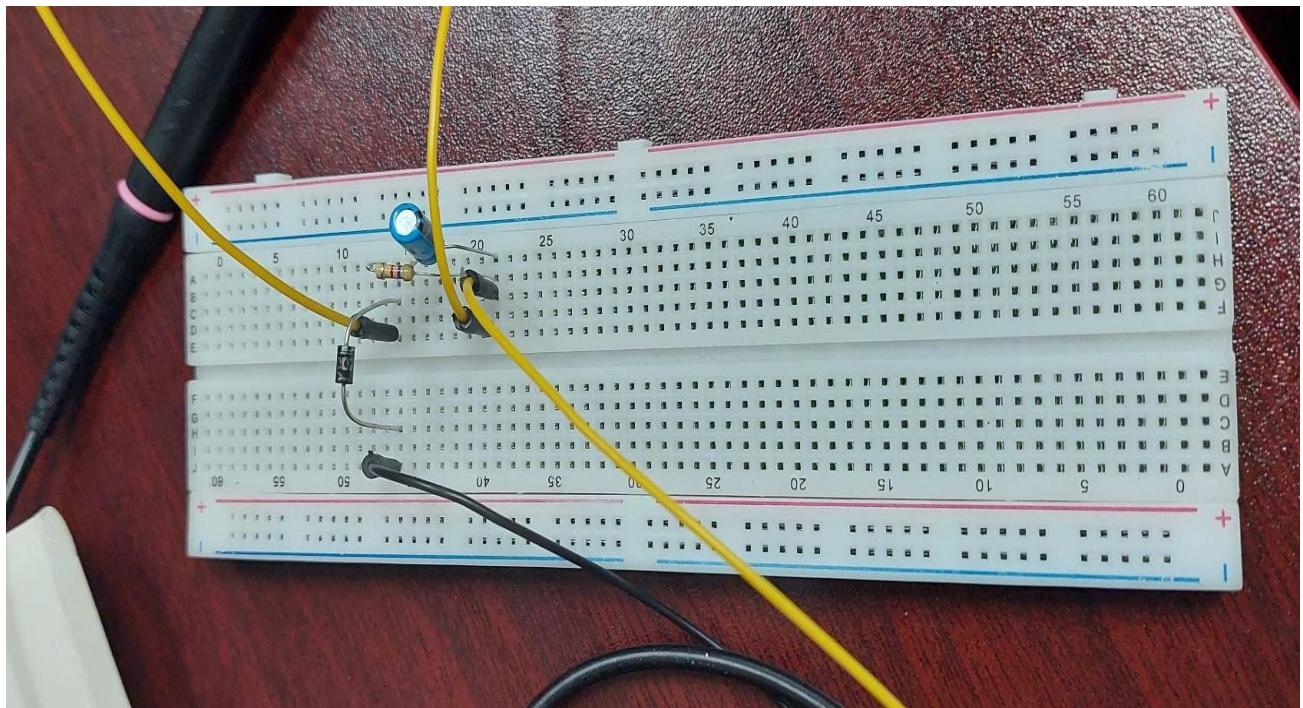
## Circuit: Half-wave rectifier (Using 4.7 uF capacitor)



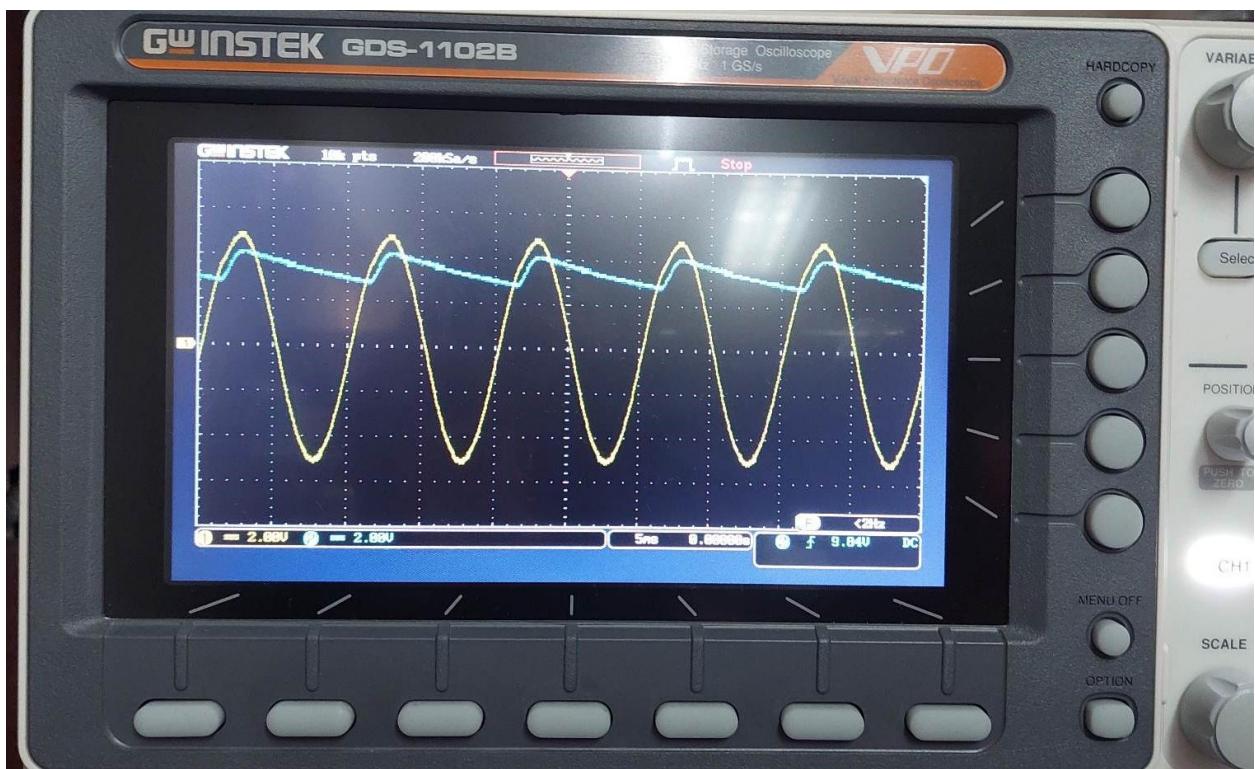
## Graph: Input & output for Half-Wave rectifier (Using 4.7 uF capacitor)



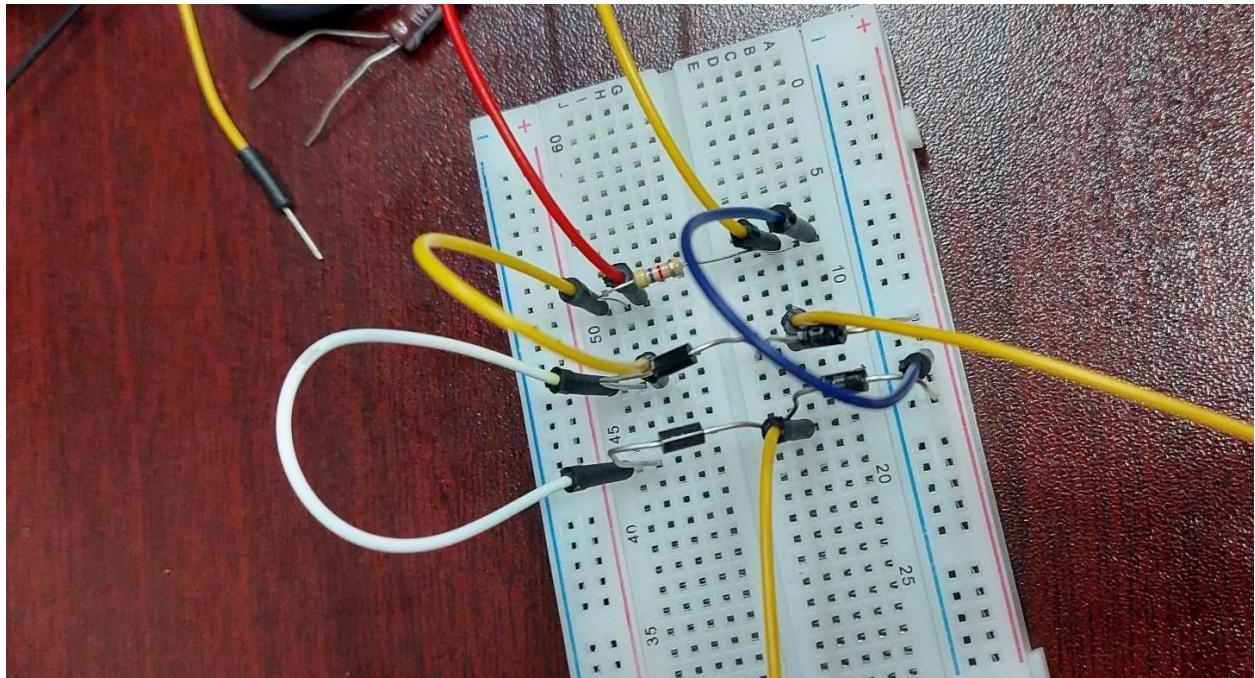
## Full-Wave rectifier


Circuit: Full-Wave rectifier (without capacitor)



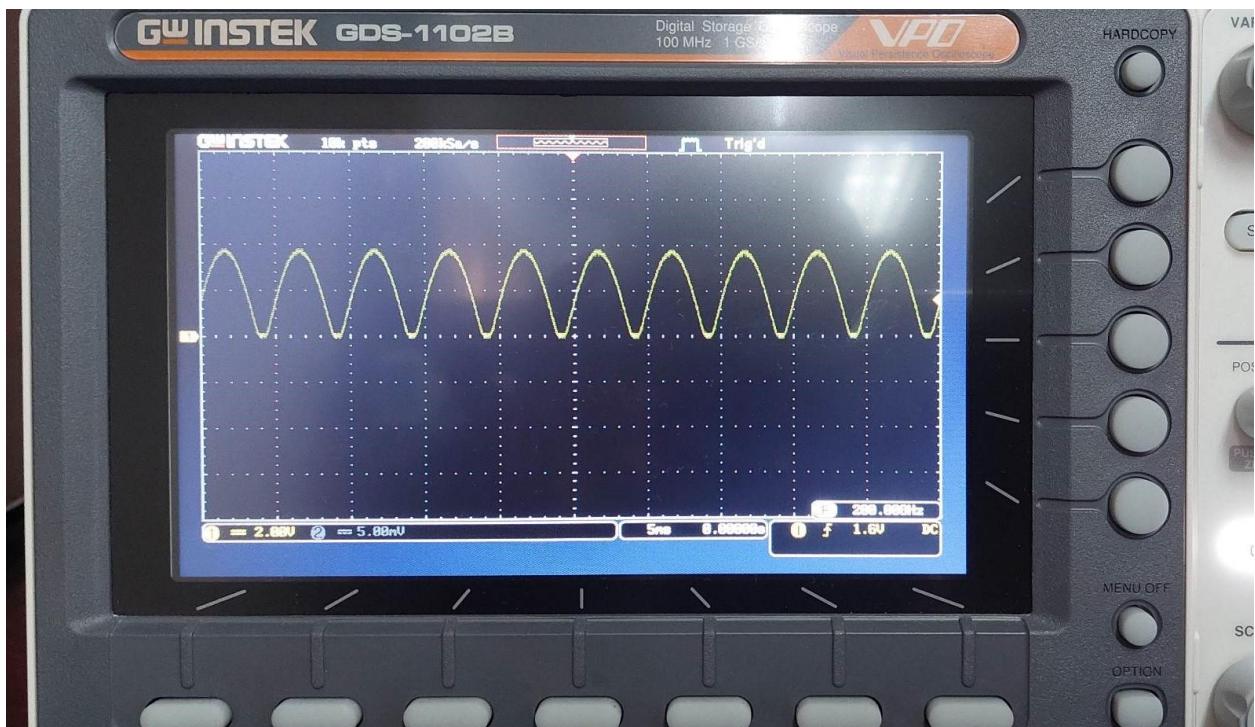
Graph: Output for Full-Wave rectifier (Without capacitor)



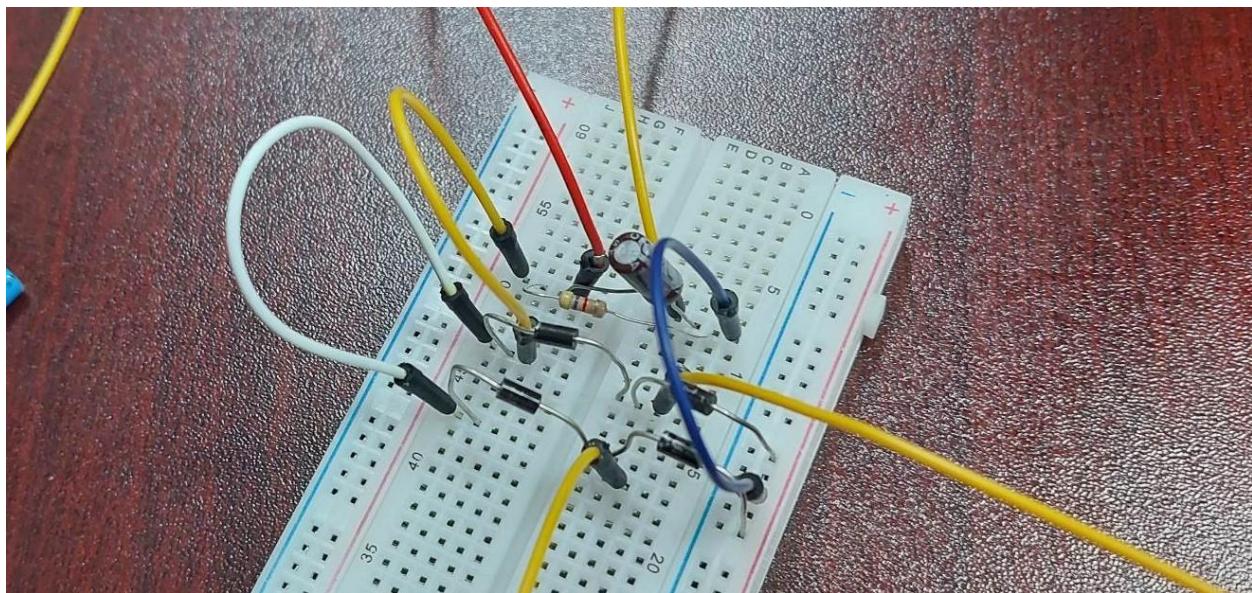
**Circuit: Full-Wave rectifier (Using 1 uF capacitor)**



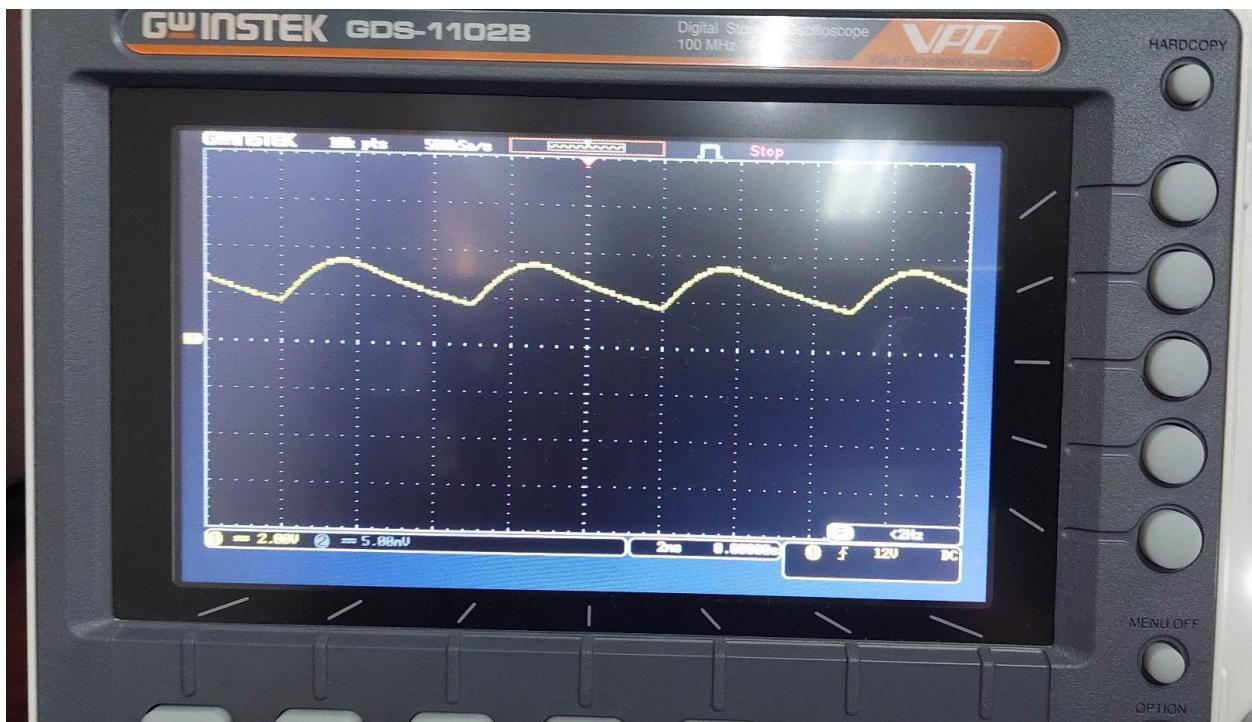
**Graph: Output for Full-Wave rectifier (Using 1 uF capacitor)**



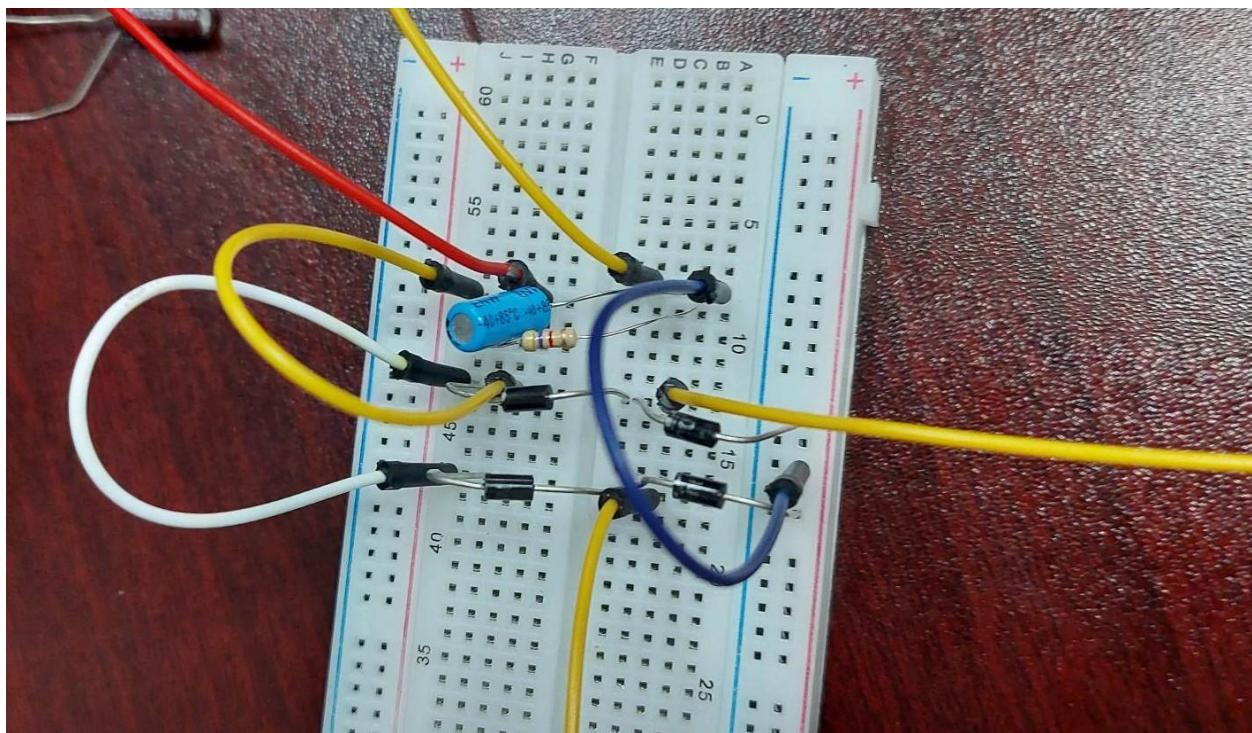**Circuit: Full-Wave rectifier (Using 4.7 uF capacitor)**



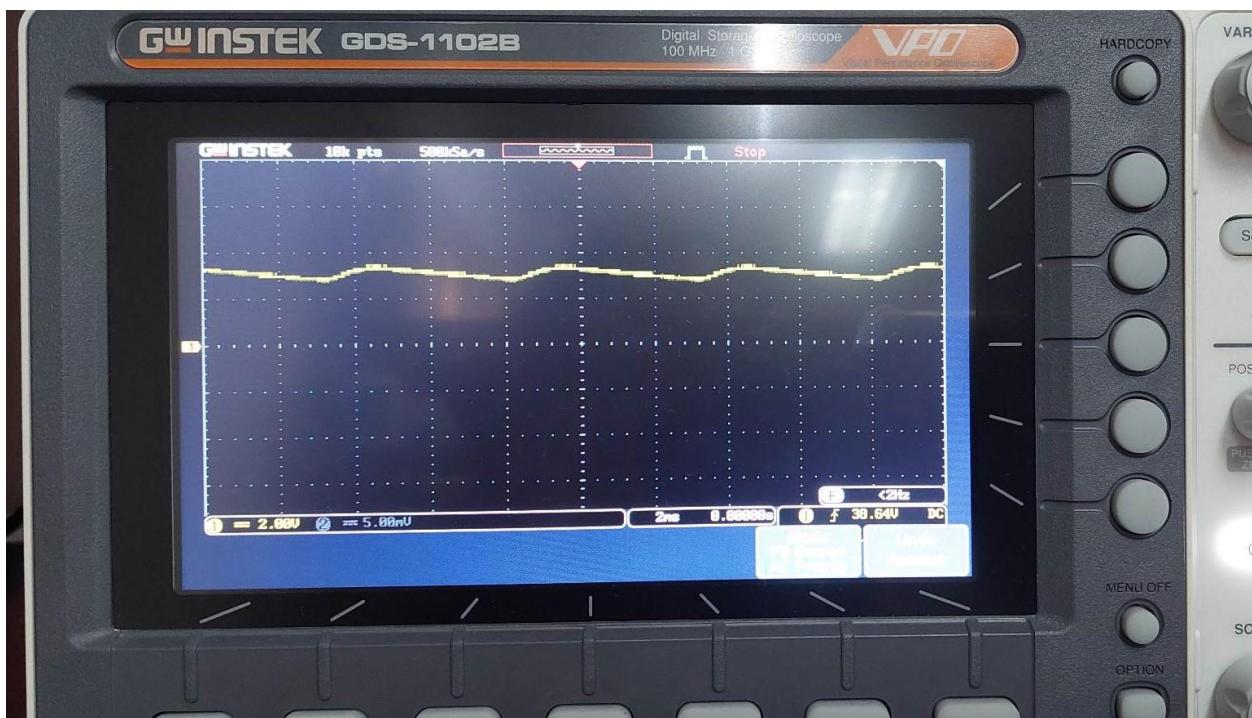**Graph: Output for Full-Wave rectifier (Using 4.7 uF capacitor)**



## Discussion

Initially, for the half-wave rectifier, a function generator set at 5V with a  $100k\Omega$  resistor and diode connected in series and connected to channel 1 of the oscilloscope at 100Hz, and channel 2 connected to the resistor. Channel 1 and channel 2 of the oscilloscope are used to view the input and output. Here,  $1\mu F$  and  $4.7\mu F$  capacitors are used to observe the smoothness of the resulting curves. Otherwise, for a full-wave rectifier, it is put together through connecting two diodes in series with another two diodes in series. Series diodes are connected in parallel. To find the output, a  $100k$  resistor is connected in parallel to the diodes other hand channel 2 is connected to the resistor. Here,  $1\mu F$  and  $4.7\mu F$  capacitors are used to observe the smoothness of the resulting curves.

If considering between half and full-wave rectifiers, in this case full-wave rectifier is better because diode does not turn off in -ve half cycle and current is not likely to flow in the circuit as it is forward-biased.

The problem I encountered while doing the experiment was that the output curve of the full-wave rectifier was not correct. To solve this problem, the capacitor was attached to one of the wires tied to the resistor, which was connected to channel 2.