



Assignment 3
CSE251

Submitted By:

Iftekhar Hossain Rahi
22201168
Sec: 06

Submitted To :

Munshi Sanowar Raihan
Lecturer,
Brac University


BRAC UNIVERSITY
Department of Computer Science and Engineering
 Assignment 03, Summer 2024
 CSE 251: Electronic Devices and Circuits

1.

Relevant information for the circuit configuration on the right is given in the tables below:

Resistor values in ($k\Omega$)			
R_1	R_2	R_3	R_4
4	6	3	4

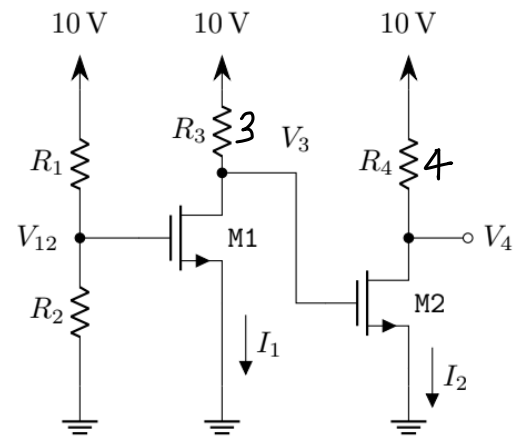
Transistor Parameters
$k_n = 2 \text{ mA/V}^2$
$V_T = 1 \text{ V}$



- Explain, in short, which of the two models (S and SR) of MOSFET is a better approximation? [1]
- Determine the value of V_{12} . [1]
- Calculate the value of drain-to-source voltage of the transistor $M1$. In the process, determine the operating mode of $M1$. [3]
- Determine which one of the four resistors will consume the least amount of power. [Hint, Power = $I^2 R$] [3]
- Determine how the operating mode of $M2$ would change if R_2 were set to zero. [2]

⑨ The SR-model of is generally a better approximation for compared to the S model. This is because the model includes more detailed effects like the body effect and velocity saturation, making it more accurate in representing real-world MOSFET characteristics.

(b)

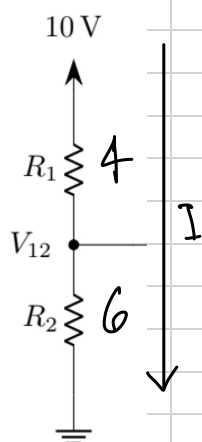

$$I_{n\ M1}, I_{G1} = 0$$

$$\therefore 10 - 0 = 4I + 6I$$


$$\Rightarrow 10I = 10$$

$$\Rightarrow I = 1\text{mA}$$

$$\therefore \frac{V_{12} - 0}{6k} = 1\text{mA}$$

$$\Rightarrow V_{12} = 6\text{V} \quad (\text{Ans})$$

(c)

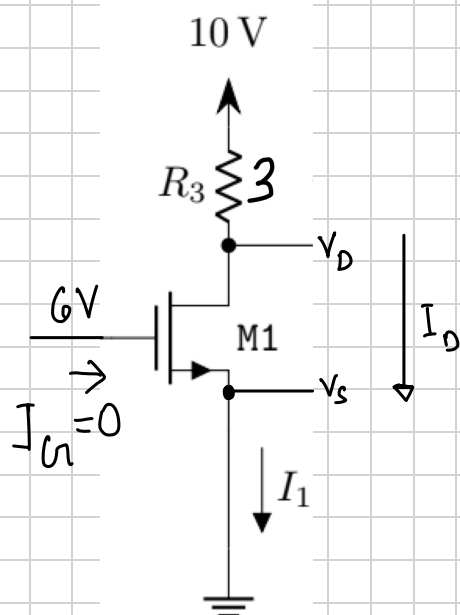

$$\begin{aligned} V_{GS} &= V_G - V_S \\ &= 6 - 0 \\ &= 6\text{V} \end{aligned}$$

$$\begin{aligned} V_{OV} &= V_{GS} - V_T \\ &= 6 - 1 \\ &= 5\text{V} \end{aligned}$$

mode.

As $V_{GS} \geq V_T$, So, M_1 would be in triode or saturation.
Let's assume that the operating mode is saturation,

$$\begin{aligned}
 \therefore I_D &= \frac{K_n}{2} \times V_{ov}^2 \\
 &= \frac{2}{2} \times 5^2 \\
 &= 25 \text{ mA}
 \end{aligned}$$

Again,

$$\frac{10 - V_D}{3} = I_D$$

$$\Rightarrow 10 - V_D = 3 \times 25$$

$$\Rightarrow 10 - V_D = 75$$

$$\Rightarrow V_D = 10 - 75 = -65$$

$$\Rightarrow V_D = -65 \text{ V}$$

$$\begin{aligned}
 \therefore V_{DS} &= V_D - V_S \\
 &= -65 - 0 \\
 &= -65 \text{ V}
 \end{aligned}$$

$$V_{GS} > V_T$$

$$V_{DS} > V_{ov}$$

$$\therefore V_{GS} > V_T \quad \text{but}$$

$$V_{DS} = -65 \not> V_{ov} = 5 \text{ V}$$

\therefore Assumption wrong.

Let's assume that the operating mode is triode,

$$I_D = k_n \left[V_{ov} V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

$$\Rightarrow \frac{10 - V_D}{3} = 2 \left[5 V_D - \frac{1}{2} V_D^2 \right]$$

$$\Rightarrow \frac{10 - V_D}{3} = 10 V_D - V_D^2$$

$$\Rightarrow 10 - V_D = 30 V_D - 3 V_D^2$$

$$\Rightarrow 3 V_D^2 - 31 V_D + 10 = 0$$

$$\therefore V_D = 10, \frac{1}{3}$$

$\therefore V_D \neq 10$ as the voltage drop would be 0.


$$\therefore V_D = \frac{1}{3}$$

$$\therefore V_{DS} < V_{ov}$$

\therefore So, the assumption is true, M_1 is in triode mode.

(Ans)

(d)

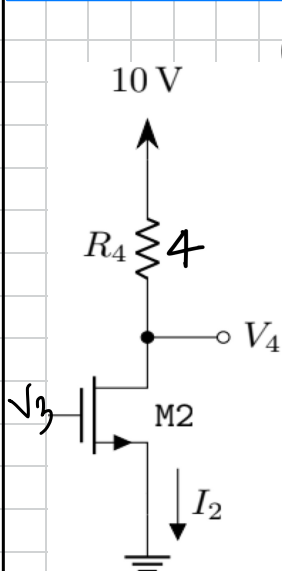

$$I_n M_2, \\ V_3 = \frac{1}{3} = 0.33$$

$$\Rightarrow V_3 < V_T$$


So, the M_2 will remain off.

There will be no current flow.

$\therefore R_4$ will consume least power.

(Ans)


c)

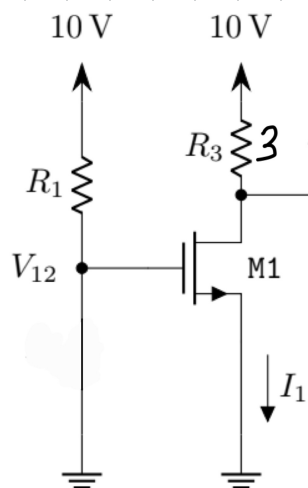

When $R_2 = 0$,

the M1 MOSFET is in the cutoff mode, because $V_{GS} < V_T$

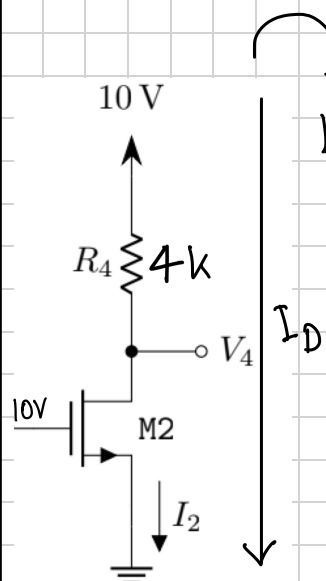So, the gate voltage for M2 is $V_G = 10V$,



Let's assume that
M2 is in Triode mode.

$$\begin{aligned} \therefore V_{OV} &= V_{GS} - V_T \\ &= V_G - V_S - V_T \\ &= 10 - 0 - 1 \\ &= 9V \end{aligned}$$

$$I_D = K_n \left[V_{OV} V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

$$\Rightarrow \frac{10 - V_D}{4} = 2 \left(9V_D - \frac{1}{2} V_D^2 \right)$$

$$\Rightarrow \frac{10 - V_D}{4} = 18V_D - V_D^2$$

$$\Rightarrow 10 - V_D = 72 V_D - 4 V_D^2$$

$$\Rightarrow 4 V_D^2 - 73 V_D + 10 = 0$$

$$\therefore V_D \neq 18.11$$

$$V_D = 0.138$$

$$\begin{aligned}\therefore V_{DS} &= V_D - V_S \\ &= 0.138 - 0 \\ &= 0.138\end{aligned}$$

$$\therefore V_{DS} < V_{ov}$$

\therefore Assumption Correct. M2 is in Triode Mode. (Ans)