
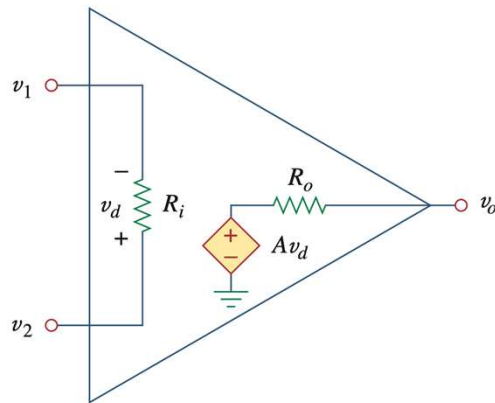


# Lecture 4 & 5

Op Amp – Part 2 & 3

# Review – Operational Amplifier

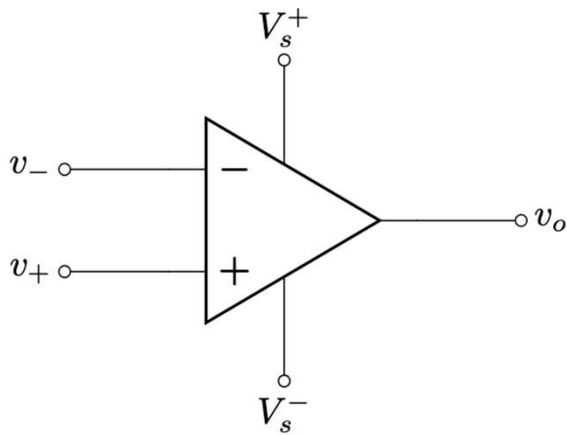

$v_1 = v_-$  = voltage of inverting terminal  
 $v_2 = v_+$  = voltage of noninverting terminal

$v_d = v_+ - v_- = v_2 - v_1$   
= differential input voltage for VCVS

$A$  = Open loop gain

$R_i$  = Input resistance


$R_o$  = Output resistance

Differential amplifier  $\Rightarrow$  amplifies the difference

$$v_o = A v_d = A(v_2 - v_1) = A(v_+ - v_-)$$
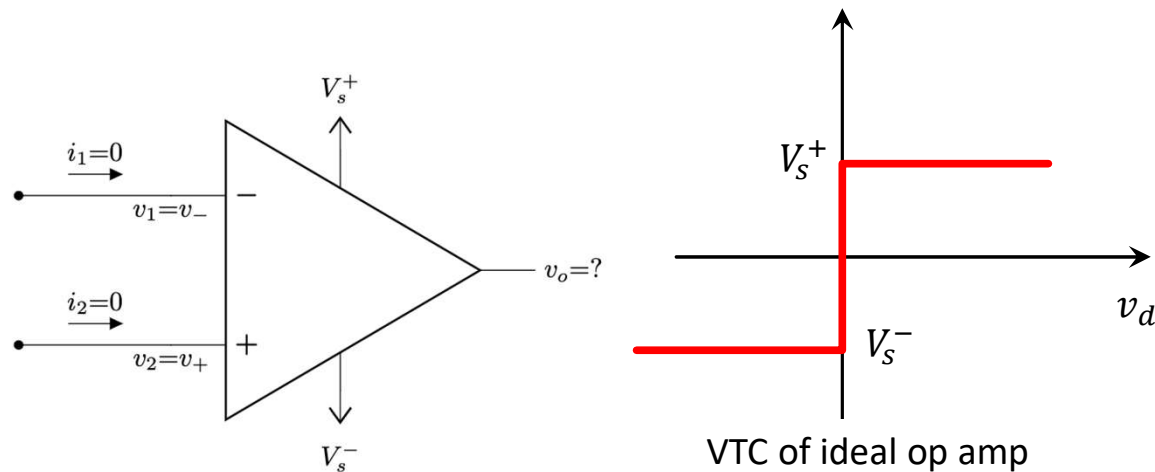
# Review – Ideal Op Amp

- Infinite open-loop gain,  $A = \infty$
- Infinite input resistance,  $R_i = \infty = \text{open circuit}$
- Zero output resistance,  $R_o = 0 = \text{short circuit}$
- As  $R_i = \infty$  (open circuit),  $i_1 = i_2 = 0$ . Therefore, circuit solving become much simpler



$$v_o = \begin{cases} V_s^+ & \text{if } v_d > 0 \Rightarrow v_2 > v_1 \\ V_s^- & \text{if } v_d < 0 \Rightarrow v_2 < v_1 \end{cases}$$

# Application of Ideal Op Amp - Comparator

- A comparator compares two voltages to determine which is larger.
- The comparator is essentially an op-amp operated in an open-loop configuration
- Two types –
  - (1) **Non-inverting**: outputs a positive voltage ( $V_H = V_S^+$ ) when input is greater than reference
  - (2) **Inverting**: outputs a negative voltage ( $V_L = V_S^-$ ) when input is greater than reference
- Application – smoke detector, turning AC on/off automatically, etc


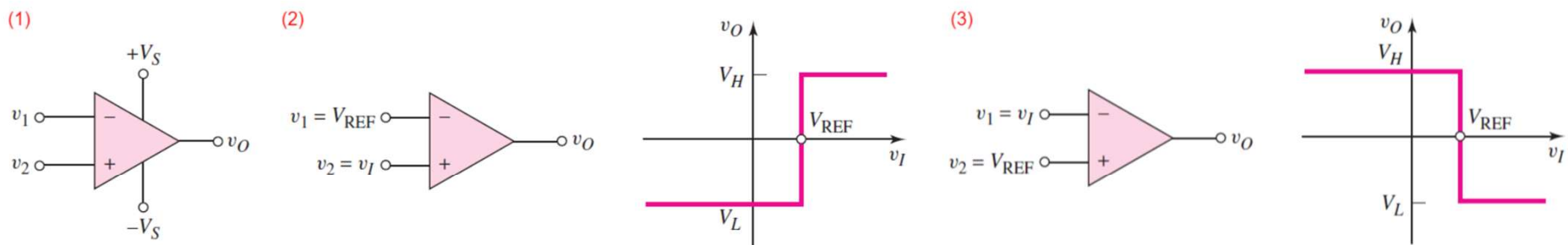




Figure 2: (1) Op-Amp Comparator (2) Noninverting Circuit (3) Inverting Circuit

# Comparator: Pulse Generator

Pulse generator

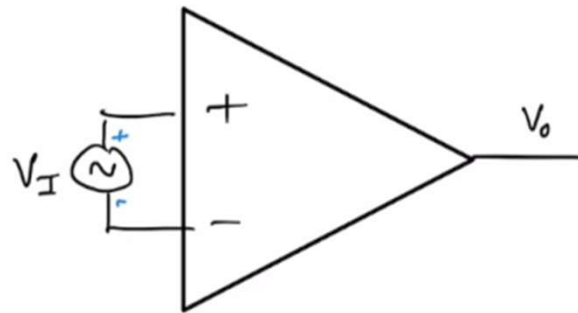
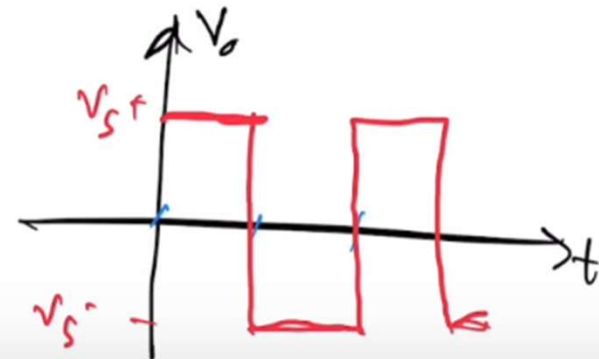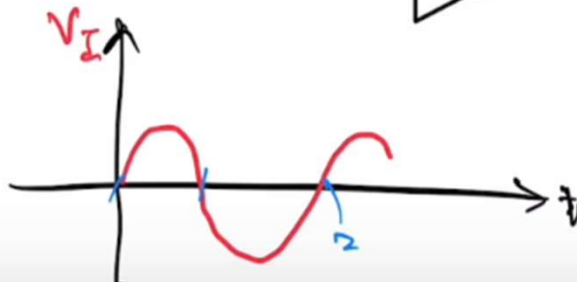
$$V_{I,+} = V_+, \quad V_{I,-} = V_-$$
$$\Rightarrow V_d = V_+ - V_- = V_I$$



# Comparator Application – Automatic AC

Auto AC ON/OFF

Sensor




$$V_T \propto T$$

$$23^\circ, V_T = 1.2V$$

$$24^\circ, V_T = 1.4V$$

$$25^\circ, V_T = 1.6V$$


AC should be on if  
 $T > 24^\circ C$

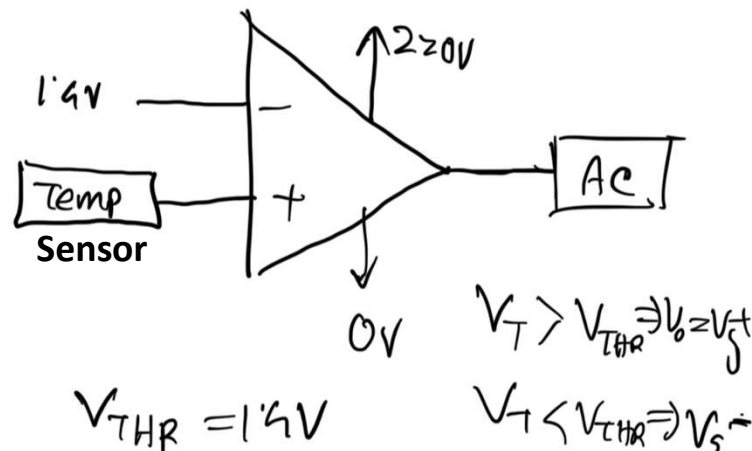


# Smoke Detector

## ③ Smoke Detector

Smoke sensor

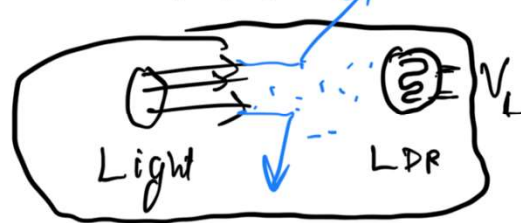


$$V_L \propto R$$

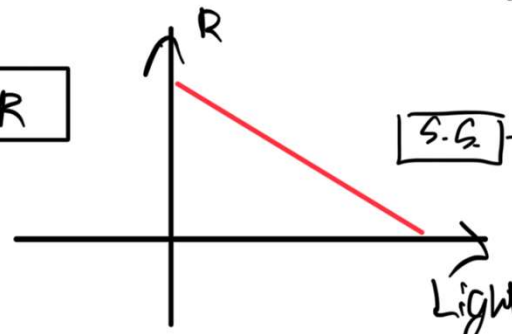

No smoke,  $V_L = \text{small} = 2V$


Smoke,  $V_L = \text{high} = 4V$

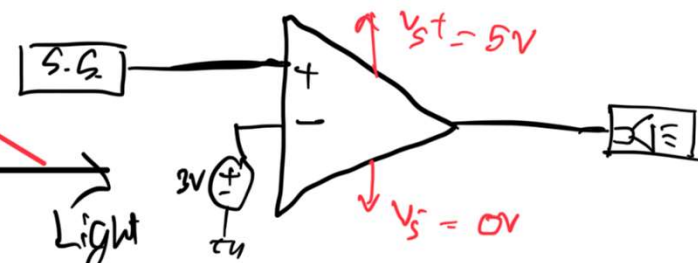$V_L > 3V \Rightarrow \text{Alarm ON}$   
 $V_L < 3V \Rightarrow \sim \text{OFF}$


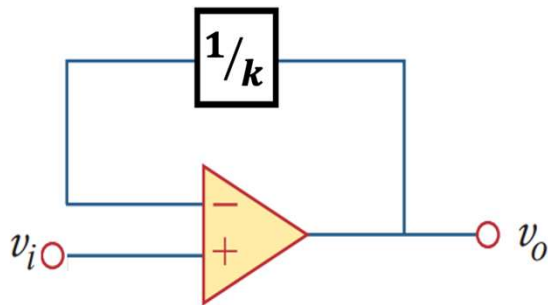
# Introducing Negative Feedback

- The gain ( $A$ ) of an ideal op amp is infinity, practically extremely large.
- The power supply ( $+V_s$  and  $-V_s$ ) limits the op amp's output.
- We require a method to have a finite gain. That is what negative feedback does.
- Negative feedback: feeding back **a portion** of output to inverting input
- Idea – the output will become stable due to a self-correcting mechanism




For example, here,  $v_- = \text{one } k'\text{th part of output} = \frac{1}{k} v_o$

If  $v_o$  increases,  $v_-$  will increase, hence  $v_d$  will decrease, eventually  $v_o$  decreases


If  $v_o$  decreases,  $v_-$  will decrease, hence  $v_d$  will increase, eventually  $v_o$  increases



# Negative Feedback – Numerical Example

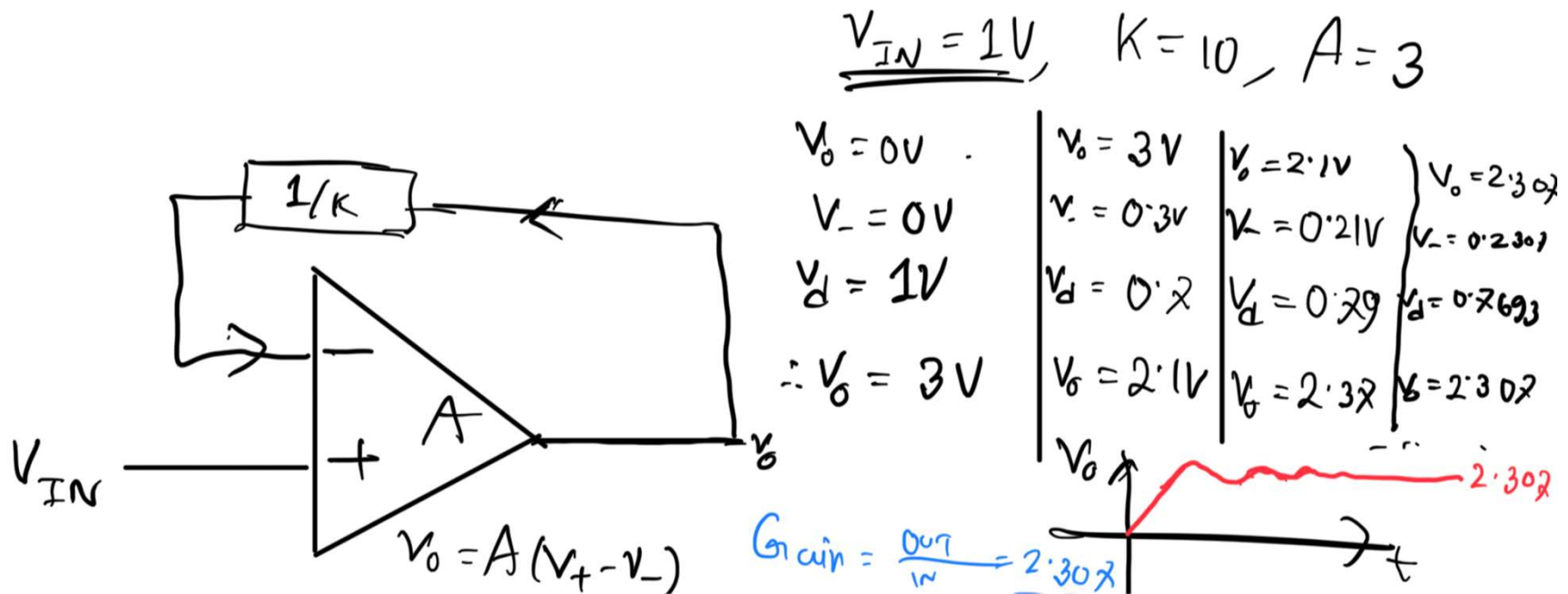

# Negative Feedback – Derivation of Gain

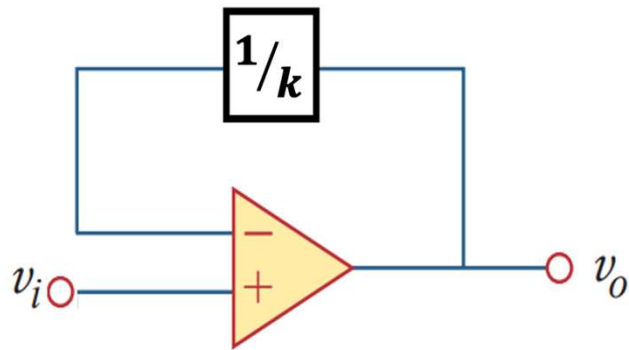

Here,  $v_- = \frac{v_o}{k}$

We know,  $v_o = A v_d$

or,  $v_o = A(v_+ - v_-)$

$$= A\left(v_i - \frac{v_o}{k}\right)$$

$$= A v_i - \frac{A}{k} v_o$$

or,  $v_o\left(1 + \frac{A}{k}\right) = A v_i$

So,  $v_o = \frac{A v_i}{1 + \frac{A}{k}}$

or,  $v_o = \frac{v_i}{\frac{1}{A} + \frac{1}{k}}$


$A$  is extremely large,

so,  $\frac{1}{A} \approx 0$

$$v_o = \frac{v_i}{\frac{1}{k}} = k v_i$$


If  $k = 10$  (meaning we feed back one tenth of the output to negative input), we will get  $v_o = 10 * v_i$ . that is 10 fold gain.

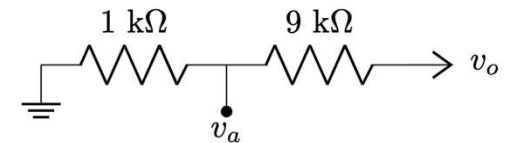How to get  $1/k$  of output to input? Voltage dividers!




$$v_a = \frac{1 \text{ k}\Omega}{1 \text{ k}\Omega + 9 \text{ k}\Omega} \times v_o = \frac{v_o}{10}$$

# Inverting Amplifier

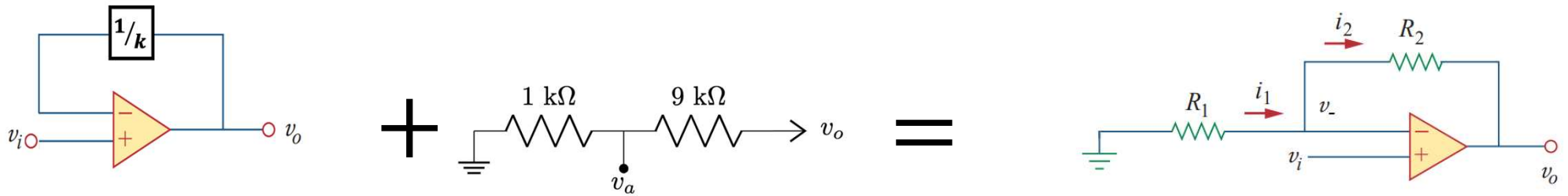

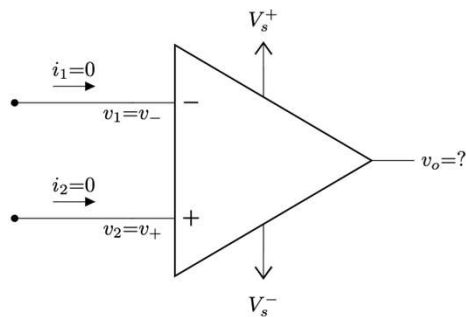
# Solving Circuit with Ideal Op Amp + NF

- For ideal op-amp
  - Infinite input resistance,  $R_i = \infty = \text{open circuit}$
  - Zero output resistance,  $R_o = 0 = \text{short circuit}$
  - $i_i = 0$  and  $i_+ = 0$
- **When there is negative feedback**, For ideal A as is infinitely high, for a finite output voltage  $v_o$ ,  $\frac{v_o}{A} = v_d = 0 \Rightarrow v_+ = v_-$ . This is called **virtual short circuit**
- Because of these, solving ideal op-amp circuit with negative feedback is very simple



# Inverting Amplifier-General

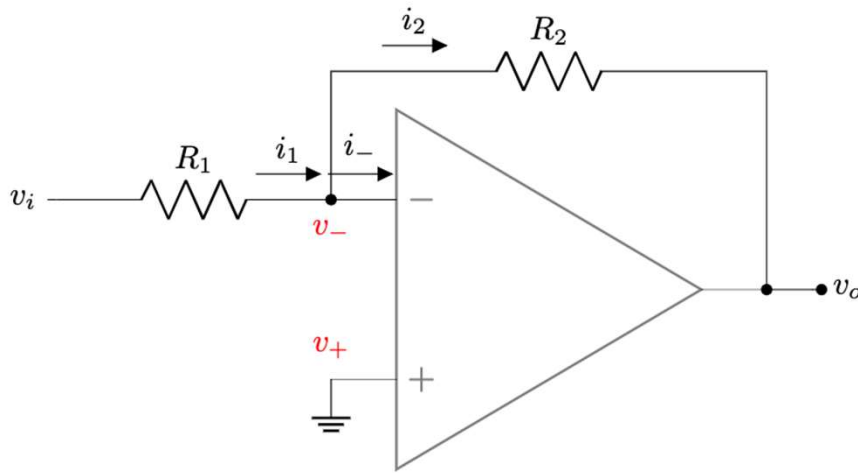

Since  $v_+$  is connected to ground,  $v_+ = 0V$

Since there is negative feedback, from virtual short,  $v_- = v_+ = 0V$

From Ohm's law for  $R_1 \Rightarrow i_1 = \frac{v_i - 0V}{R_1} = v_i/R_1$

Since ideal op-amp,  $i_- = i_+ = 0$


From KCL at  $v_-$ ,  $i_1 = i_- + i_2 \Rightarrow i_1 = i_2 = v_i/R_1$

From Ohm's law for  $R_2 \Rightarrow i_2 = \frac{v_- - v_o}{R_2} = \frac{v_i}{R_1} \Rightarrow v_o = -i_2 \times R_2 \Rightarrow v_o = -\frac{R_2}{R_1} v_i$  [ANS]

$$\text{Gain} = -\frac{R_2}{R_1}$$

# Example – Inverting Amplifier

Solve the circuit to find  $v_o$

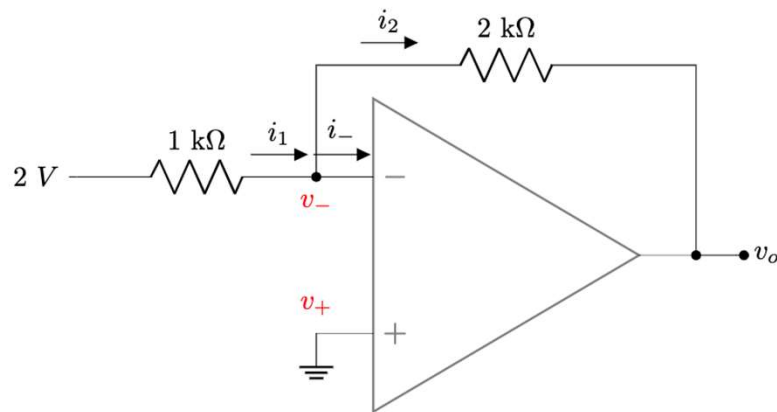

Since  $v_+$  is connected to ground,  $v_+ = 0V$

Since there is negative feedback, from virtual short,  $v_- = v_+ = 0V$

From Ohm's law for 1 kΩ  $\Rightarrow i_1 = \frac{2V - 0V}{1 \text{ k}\Omega} = 2mA$

$$\text{Gain} = -\frac{4V}{2V} = -2 \text{ (hence **inverting**)}$$

Since ideal op-amp,  $i_- = i_+ = 0$


From KCL at  $v_-$ ,  $i_1 = i_- + i_2 \Rightarrow i_1 = i_2 = 2mA$

From Ohm's law for 2 kΩ  $\Rightarrow i_2 = \frac{v_- - v_o}{2 \text{ k}\Omega} = 2mA \Rightarrow v_o = -i_2 \times 2 = -4V$  [ANS]

# Example – Inverting Amplifier

If  $v_i = 0.5$  V, calculate:

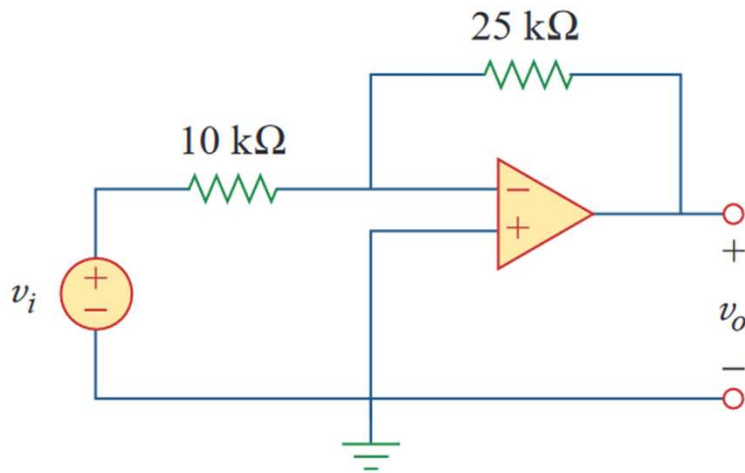- (a) Output voltage  $v_o$ .
- (b) Current in the **10 k $\Omega$**  resistor.





(a)

$$v_o = -\frac{R_f}{R_i} \cdot v_i = -2.5v_i = -1.25 \text{ V}$$

(b) Current through the **10 k $\Omega$**  resistor is

$$i = \frac{v_i}{R_i} = \frac{0.5}{10} \text{ mA} = \mathbf{50 \mu\text{A}}$$


# Example

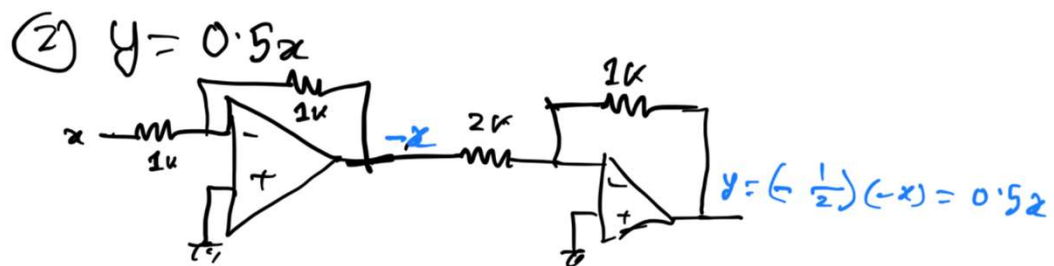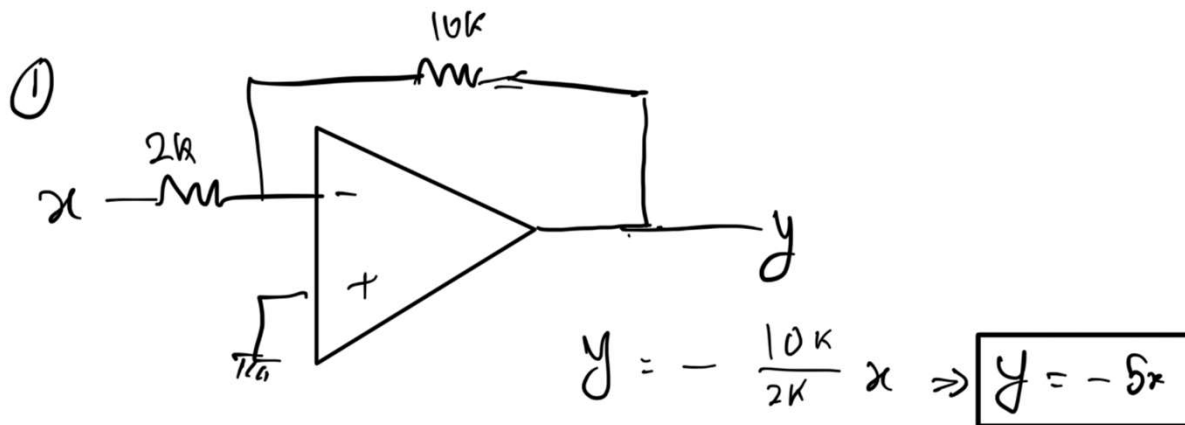



# Non-Inverting Amplifier


Gain  $> 1$

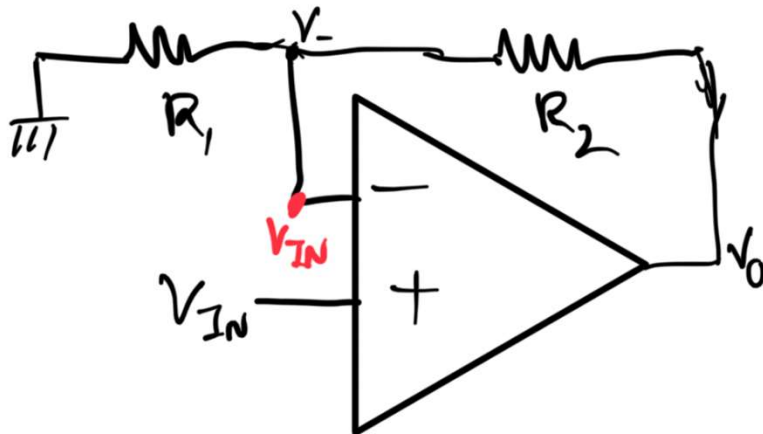

$$\therefore V_O = \left(1 + \frac{R_2}{R_1}\right) V_{IN}$$

$$V_- = \frac{R_1}{R_1 + R_2} V_O = \frac{1}{1 + \frac{R_2}{R_1}} V_O$$

K

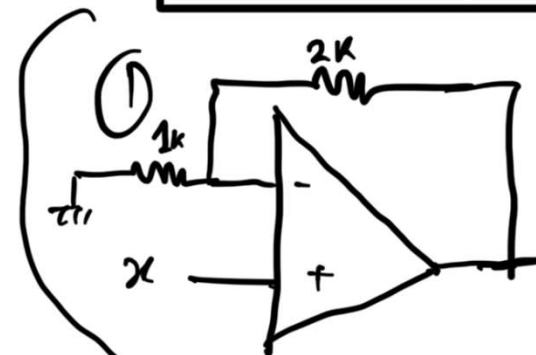


$$y = \left(1 + \frac{2}{1}\right) x$$

$$\Rightarrow y = 3x$$

② Design  $y = 4x$
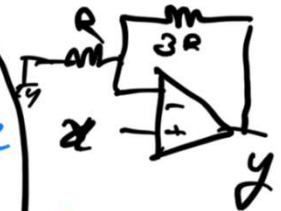
$$1 + \frac{R_2}{R_1} = 4 \Rightarrow \frac{R_2}{R_1} = 3$$



$$y = 4x$$

# Inverting Adder

Consider  $v_1$  first, and deactivate other ( $v_2, v_3, v_4$ ) sources.

It is nothing but an inverting amplifier.

$$\text{So, } v_{o1} = -\frac{R_f}{R_1} v_1$$

Similarly, if we active one source and deactivate others, we will get:

$$v_{o2} = -\frac{R_f}{R_2} v_2, v_{o3} = -\frac{R_f}{R_3} v_3, v_{o4} = -\frac{R_f}{R_4} v_4$$


Now, using **superposition principle**,

$$v_o = v_{o1} + v_{o2} + v_{o3} + v_{o4}$$

$$\text{So, } v_o = -\frac{R_f}{R_1} v_1 - \frac{R_f}{R_2} v_2 - \frac{R_f}{R_3} v_3 - \frac{R_f}{R_4} v_4$$

$$\text{Or, } v_o = -\left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3 + \frac{R_f}{R_4} v_4\right)$$

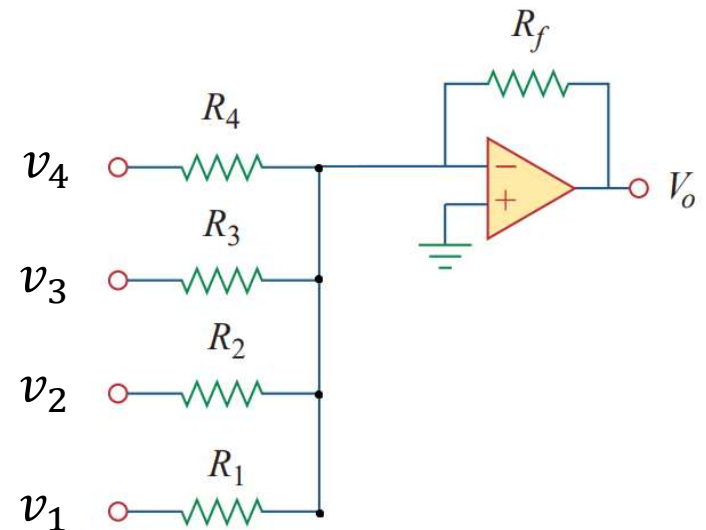**We can use this circuit to add any 'n' number of inputs!**



# Example

**Implement the following function using op-amps:**

$$v_0 = -(v_1 + 0.5v_2 + v_3)$$

**Solution:**


Here,  $R_f/R_1 = 1$ ,  $R_f/R_2 = 0.5$ ,  $R_f/R_3 = 1$

If  $R_f = 1 \text{ k}\Omega$ ,  $R_2 = 2 \text{ k}\Omega$ ,  $R_3 = 1 \text{ k}\Omega$

# Example-Inverting Adder

Calculate:

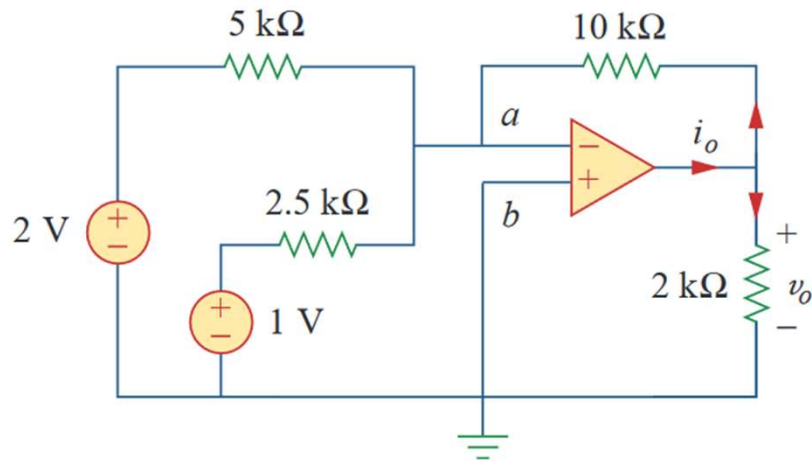- (a) Output voltage  $v_o$ .
- (b) Output current  $i_o$ .




(a)

$$v_o = -\left(\frac{10}{5} \cdot 2 + \frac{10}{2.5} \cdot 1\right) = -8 \text{ V}$$

(b)

$$i = \frac{v_o}{10} + \frac{v_o}{2} = (-0.8 - 4) \text{ mA} = -4.8 \text{ mA}$$

# Op Amp as Differentiator

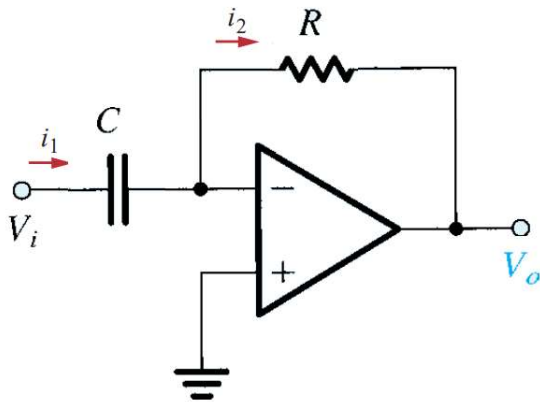

Since  $v_+$  is connected to ground,  $v_+ = 0V$

Since there is negative feedback, from virtual short,  $v_- = v_+ = 0V$

For the capacitor  $C$ ,  $\Rightarrow i_1 = C \frac{dv_C}{dt} = C \frac{d(v_i - v_-)}{dt} = C \frac{dv_i}{dt}$

From Ohm's law for  $R \Rightarrow i_2 = \frac{v_- - v_o}{R} = -\frac{v_o}{R}$


Since ideal op-amp,  $i_- = i_+ = 0$ , so  $i_1 = i_2$

$$\Rightarrow -\frac{v_o}{R} = C \frac{dv_i}{dt} \Rightarrow v_o = -RC \frac{dv_i}{dt} \text{ [Ans.]}$$


Review – Capacitor

$$i_1 = C \frac{dv_C}{dt} = C \frac{d(v_1 - v_2)}{dt}$$

# Example

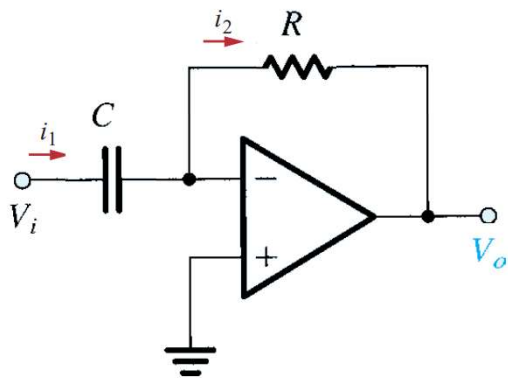

$$\text{Slope: } \left| \frac{dv}{dt} \right| = \frac{V_M - (-V_M)}{T/2} = \frac{4V_M}{T}$$

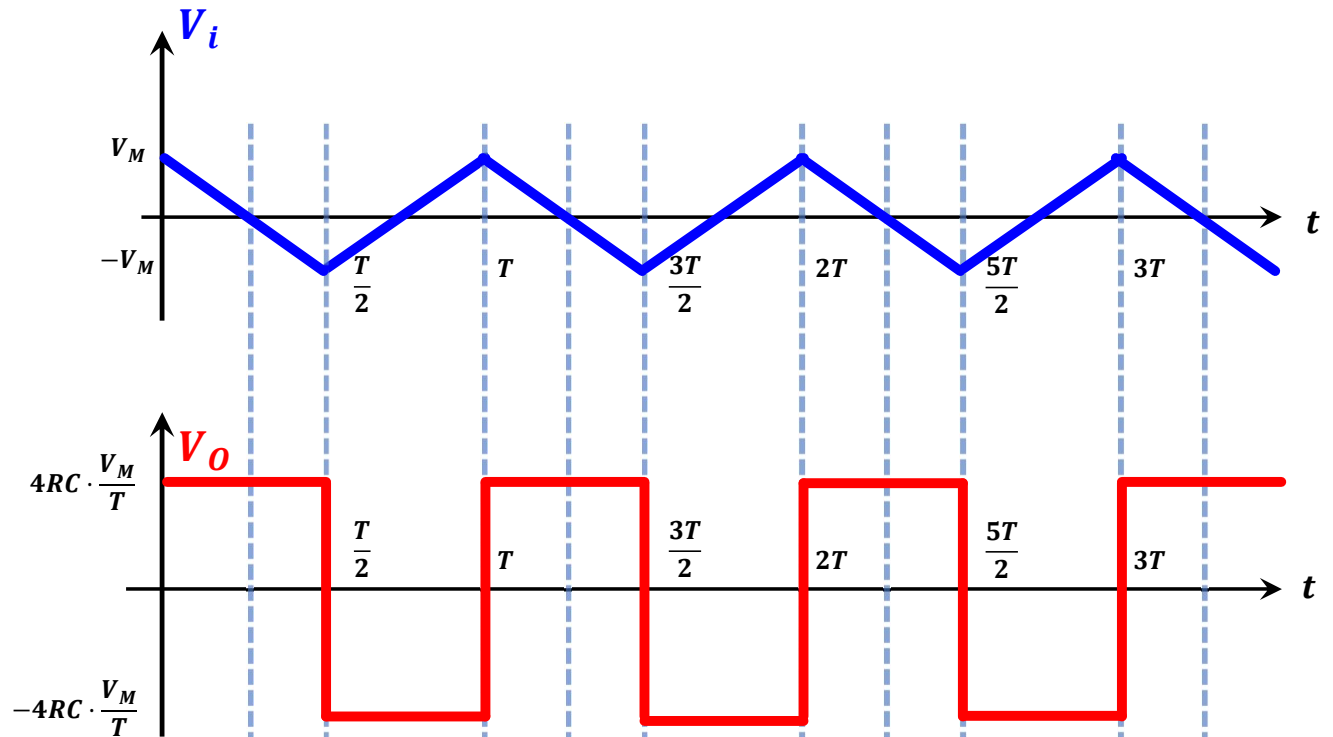

# Op Amp as Integrator

Since  $v_+$  is connected to ground,  $v_+ = 0V$


Since there is negative feedback, from virtual short,  $v_- = v_+ = 0V$

From Ohm's law for  $R \Rightarrow i_1 = \frac{v_i - v_-}{R} = \frac{v_i}{R}$

For the capacitor  $C$ ,  $\Rightarrow i_2 = C \frac{dv_C}{dt} = C \frac{d(v_- - v_o)}{dt} = -C \frac{dv_o}{dt}$


Since ideal op-amp,  $i_- = i_+ = 0$ , so  $i_1 = i_2$
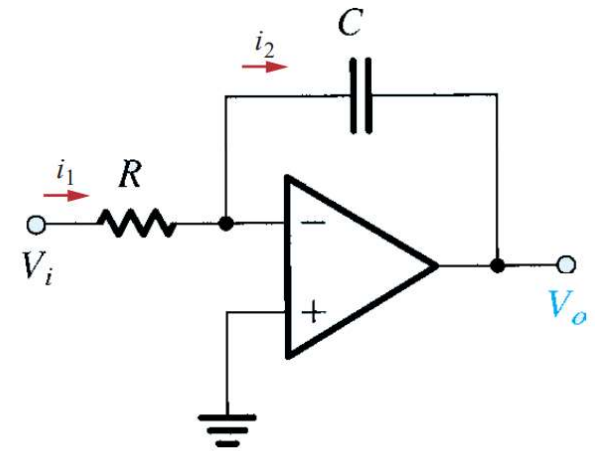
$$\begin{aligned}\Rightarrow \frac{v_i}{R} &= -C \frac{dv_o}{dt} \\ &= -RC \frac{dv_o}{dt} \\ \Rightarrow v_o &= -\frac{1}{RC} \int v_i dt\end{aligned}$$


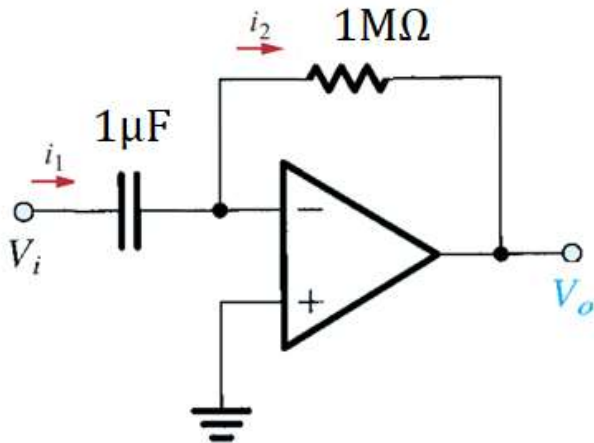
# Example

**Observe** the following Figure. If  $v_i = 5\sin 6t$ , Find the value of  $v_o$ .



**Solution:**



This is a **differentiator**.

$$\text{So, } v_o = -RC \frac{dv_i}{dt} = -1 \times 10^6 \times 1 \times 10^{-6} \times \frac{d(5\sin 6t)}{dt}$$

$$\Rightarrow v_o = -1 \times (5 \times 6 \cos 6t) = -30 \cos 6t \text{ [Ans.]}$$




# Example

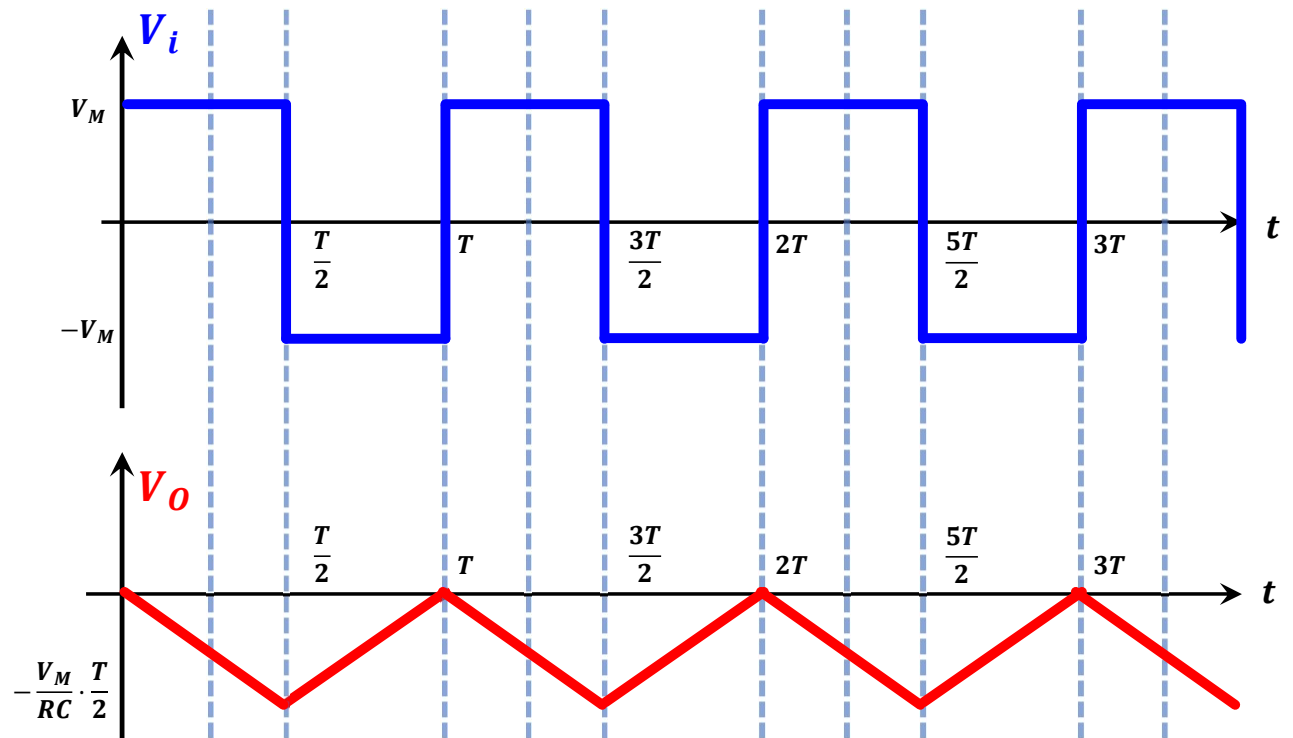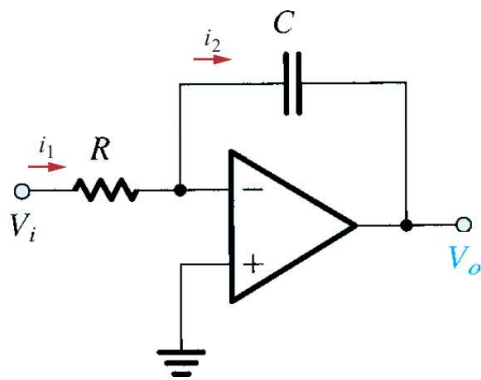
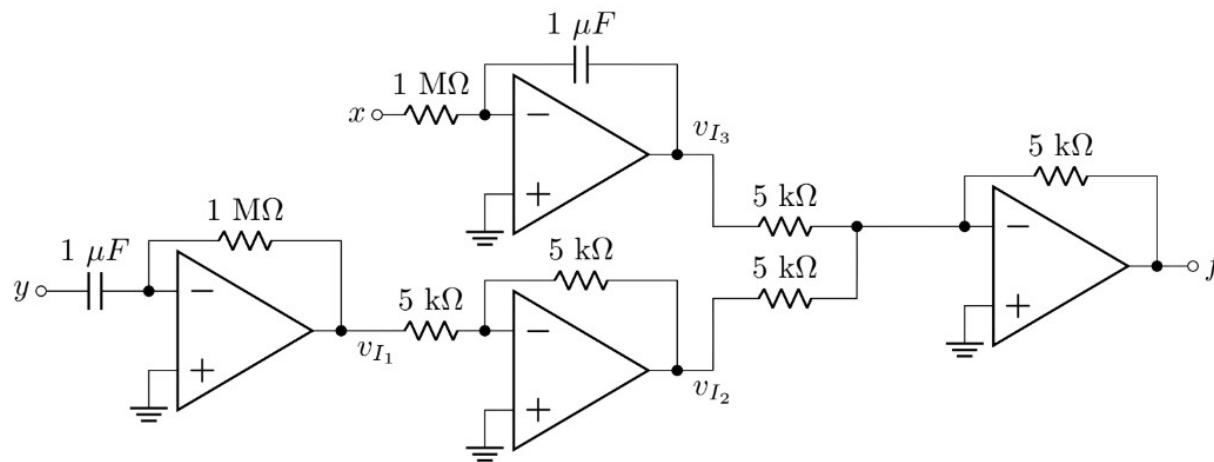
# Example

**Analyze** the circuit below to **find** an expression of  $f$  in terms of inputs  $x$  and  $y$ .



**Solution:**

$$v_{I1} = -\frac{dy}{dt}; v_{I3} = -\frac{1}{RC} \int x \, dt; v_{I2} = -v_{I1} = \frac{dy}{dt}; v_o = f = -(v_{I2} + v_{I3})$$

## Exponential Amplifier

$$V_+ = V_- = 0V$$

$$i_1 = i_2$$


$$\Rightarrow I_s e^{v_d/V_T} = (0 - V_{out})/R$$

$$\Rightarrow V_{out} = -I_s R e^{v_d/V_T}$$


$$V_d = V_{in} - 0 = V_{in}$$

$$\text{Considering } I_s R = 1, V_T = 1$$

$$V_{out} = -e^{V_{in}}$$

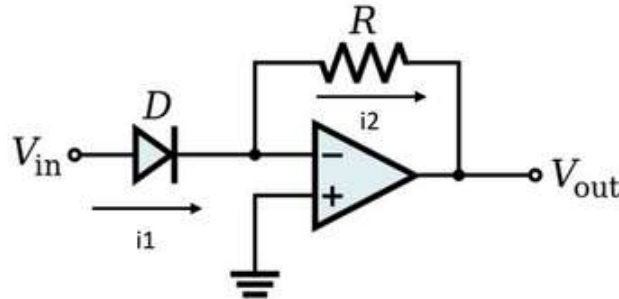

## Real diode

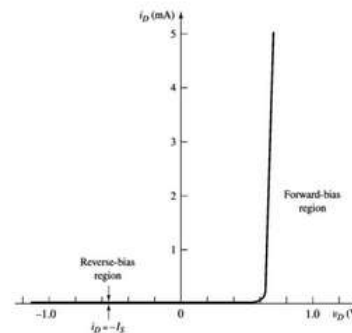

I-V characteristics of a real diode

Relation between diode current and diode voltage:

$$i_D = I_s \left( e^{\frac{v_D}{\eta V_T}} - 1 \right)$$

where  $v_D (= v_A - v_C)$  is the voltage across the diode,  $i_D$  is the current through the diode (from anode to cathode) and  $V_T$ , called the thermal voltage, is a temperature dependent constant. For temperature  $T = 300K$ ,  $V_T = 25 mV$ .

$\eta$  is called the ideality factor (try to recall, you measured this in the lab!)

## Logarithmic Amplifier

$$V_+ = V_- = 0V$$

$$i_1 = i_f$$

$$\Rightarrow (V_i - 0)/R = I_s e^{V_d/V_T}$$

$$\Rightarrow V_i = -I_s R e^{V_d/V_T}$$


$$V_d = 0 - V_o = -V_o$$

$$\text{Considering } I_s R = 1, V_T = 1$$

$$V_i = e^{-V_o}$$

$$\Rightarrow -V_o = \ln(V_i)$$

$$\Rightarrow V_o = -\ln(V_i)$$

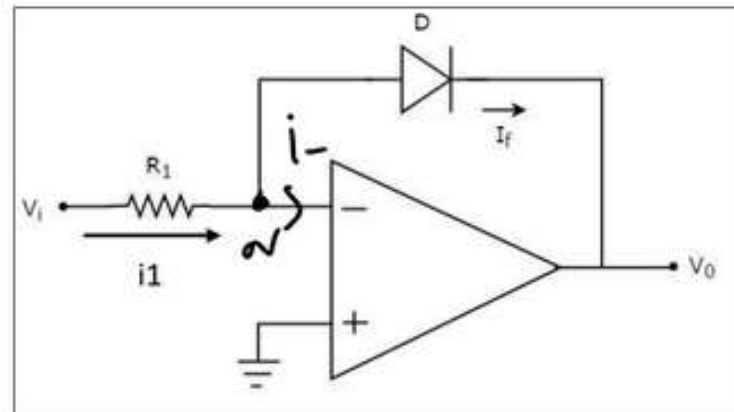

## Example Problem

Design the following function using op-amps:

- $f = -\frac{1}{3} \int x \cdot dt + 2 \ln y + 4z$


## Example Problem

Design the following function using op-amps:

- $f = -3 \frac{dx}{dt} + 2 \exp(y) + 4z$
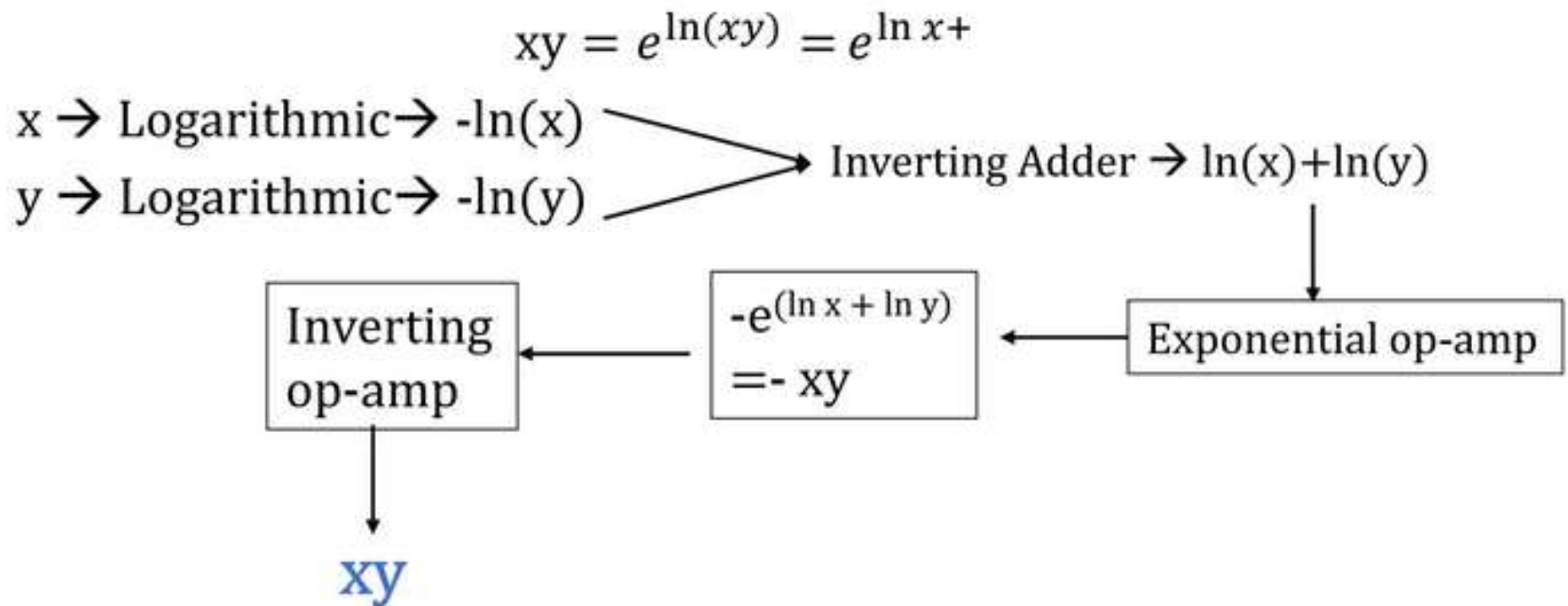
## Example Problems


- Design  $f = x \cdot y$  by using op-amps


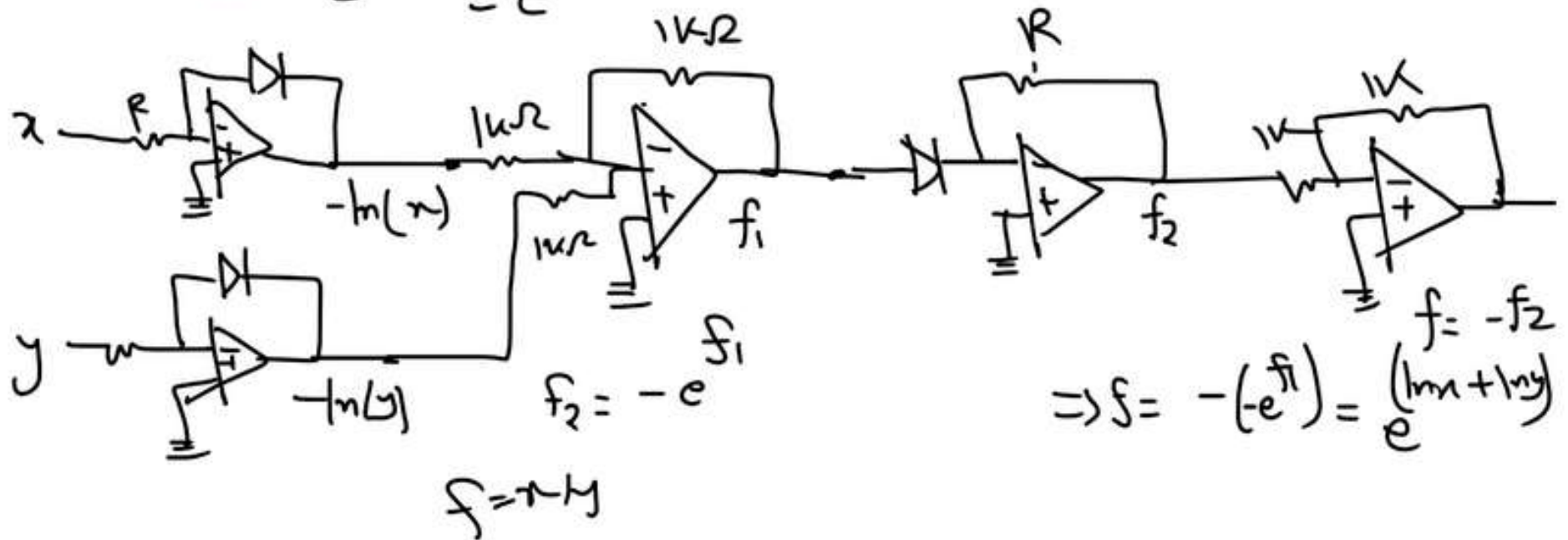
## Example Problems

•  $f = x \cdot y = e^{\ln(xy)} = e^{\ln x + \ln y}$

$$f_1 = -(-\ln x - \ln y) = \ln x + \ln y$$





## Practice Problem:

Design the following function using op-amps:

- $f = xy/z$

**Hint:**  $f = xy/z$

$$\ln(f) = \ln(xy/z) = \ln(x) + \ln(y) - \ln(z)$$


$$f = \exp(\ln(x) + \ln(y) - \ln(z))$$

So,

$$f = \exp(z) \text{ where } z = \ln(x) + \ln(y) - \ln(z)$$


# Voltage follower or Buffer amplifier

By **virtual short circuit**

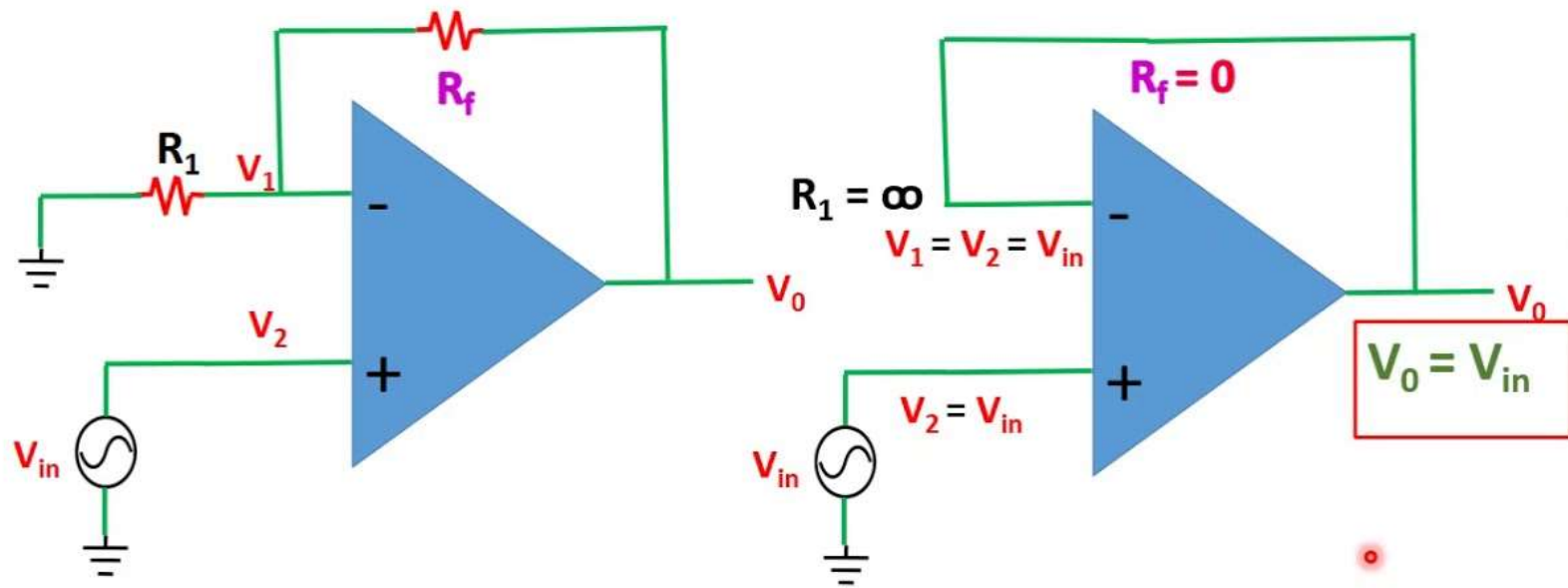


The output of the op-amp follows the input signal. In this configuration, the **gain of the op-amp is unity**.

# Buffer Amplifier

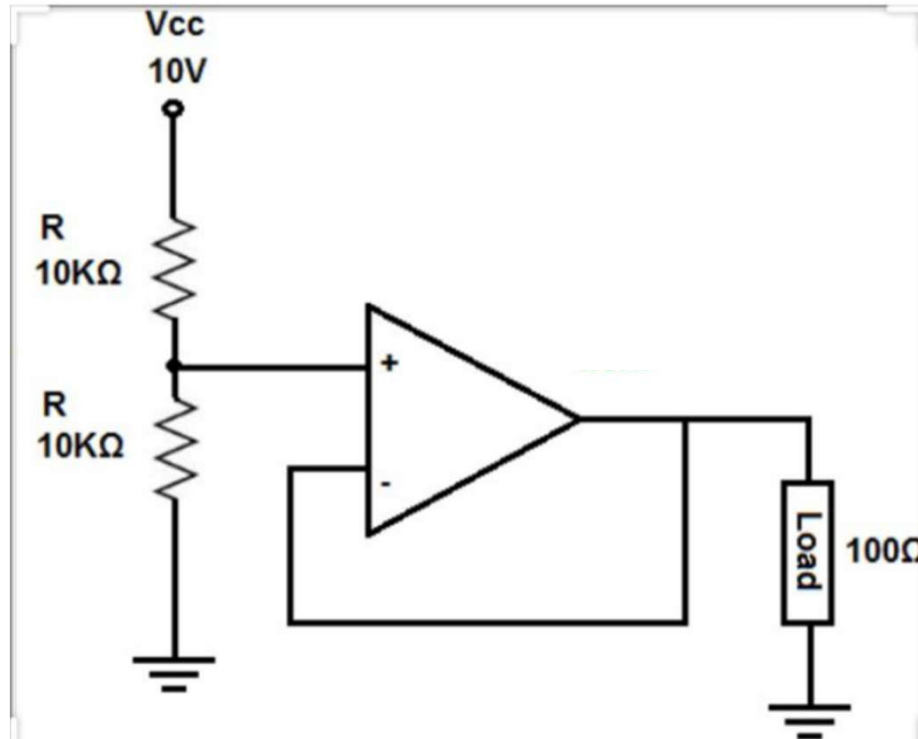

As we use the op amp buffer between , we can isolate the two stages completely , thus ensuring that we get  $10/2 = 5\text{V}$  at our  $100\Omega$  load which won't be the case if we connect it directly in parallel

# Example Problems

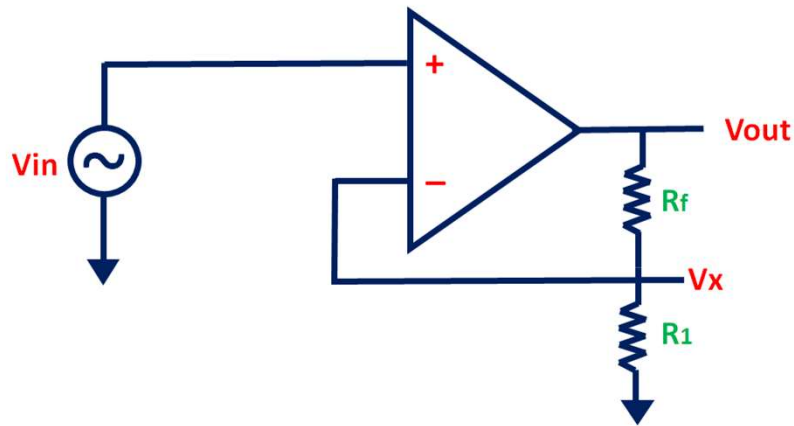

What type of amplifier is this?


❖ Find out  $V_o$

$$I_+ = 0 \text{ mA}$$

$$(1 - V_+)/2 + (1 - V_+)/3 = I_+ = 0$$

$$V_+ = V_- = 1.4 \text{ V}$$

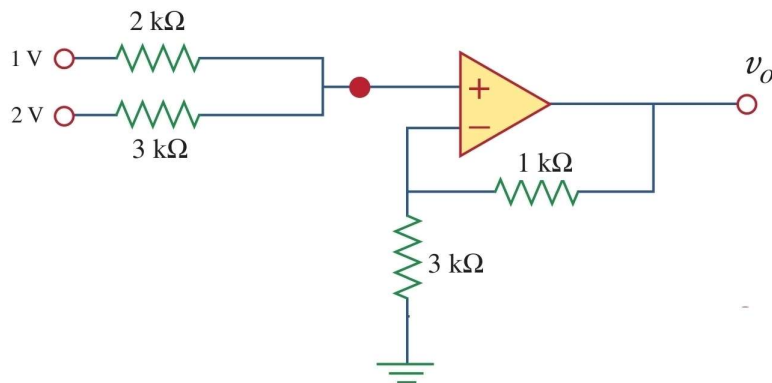
$$V_o = (1 + 1/3) * V_+ \\ = 1.8667 \text{ V}$$



# Example Problems

## ❖ Find output

Subtractor circuit

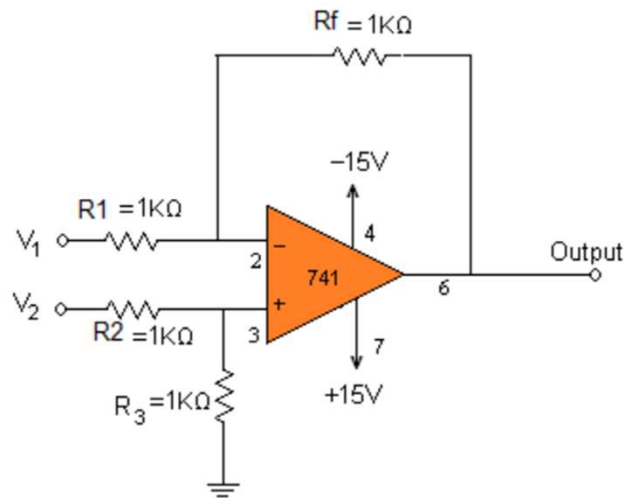

$$V_+ = V_2 \cdot R_3 / (R_3 + R_2) = V_2 / 2$$

Superposition theorem,

$$V_{o1} = -(R_f / R_1) \cdot V_1 = -V_1$$

$$V_{o2} = (1 + R_f / R_1) \cdot V_+ = 2 \cdot V_2 / 2 = V_2$$

$$V_o = V_{o1} + V_{o2} = -V_1 + V_2 = V_2 - V_1$$


# Example Problems

**Design** a circuit using Op-Amps to implement the following expression:

$$f = \frac{1}{4}x + 7y - \frac{dz}{dt}$$


$$f = \frac{1}{4}x + 7y - \frac{dz}{dt}$$
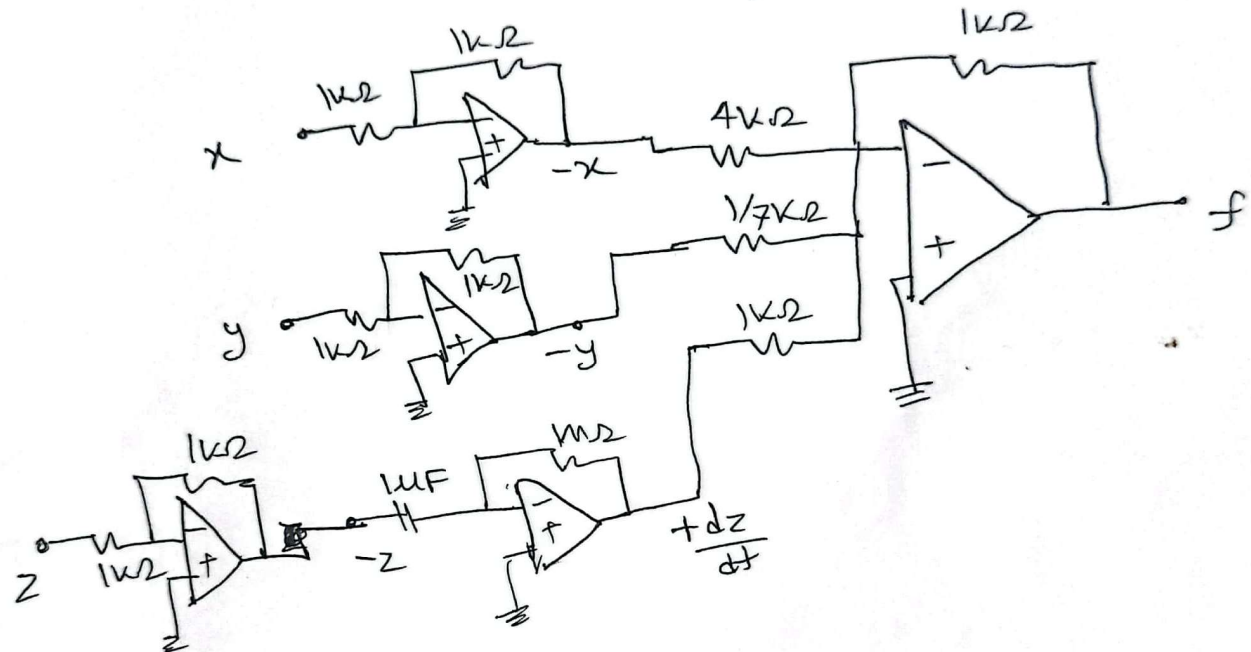
$$\Rightarrow f = - \left( -\frac{1}{4}x - 7y + \frac{dz}{dt} \right)$$



# Example Problems

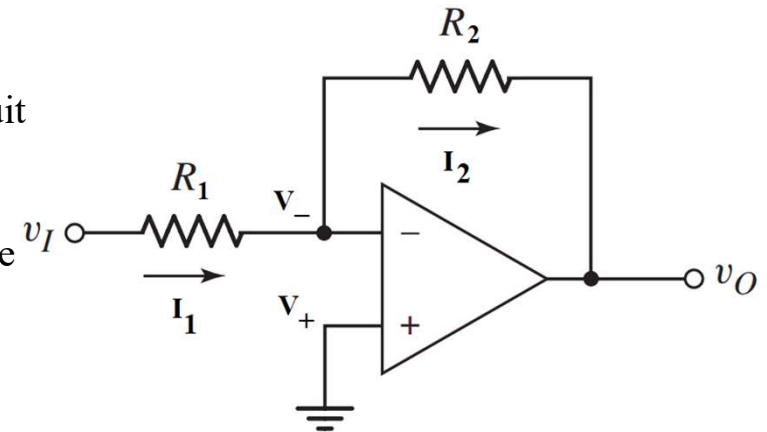- A. Design** an inverting amplifier (i.e., find the values of  $R_1$  and  $R_2$  of the circuit shown in the Figure above) in such a way that the voltage gain is  $-5$ .
- B.** Consider the circuit you drew in (a) again. Assume the input  $v_i = 0.1 \sin \omega t$  (V) has a maximum current rating of  $5 \mu\text{A}$ . What design changes, if any, are required for this input, if the voltage gain remains the same?
- C. Draw** the input and output waveforms of the circuit.



A.  $-R_2/R_1 = -5$

Assuming  $R_1 = 1 \text{ k}\Omega$  so,  $R_2 = 5 \text{ k}\Omega$

B.  $I_{1, \max} = 5 \mu\text{A}$



So,  $R_{1, \min} = |v_i| / I_{1, \max} = 0.1 \text{ V} / 5 \mu\text{A} = 20 \text{ k}\Omega$

But in A we assumed  $R_1 = 1 \text{ k}\Omega (< R_{1, \min})$


Now, assuming new value of  $R_1 = 25 \text{ k}\Omega$

Therefore,  $R_2 = 5 * 25 \text{ k}\Omega = 100 \text{ k}\Omega$

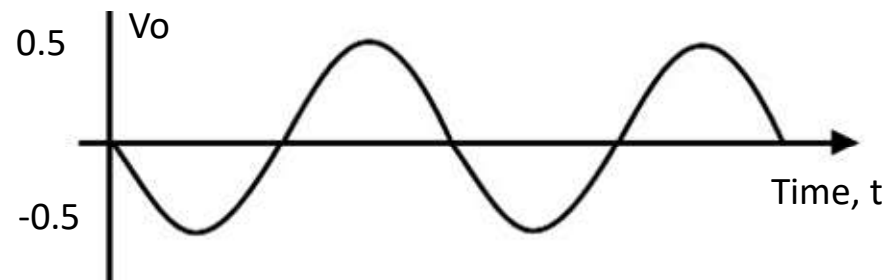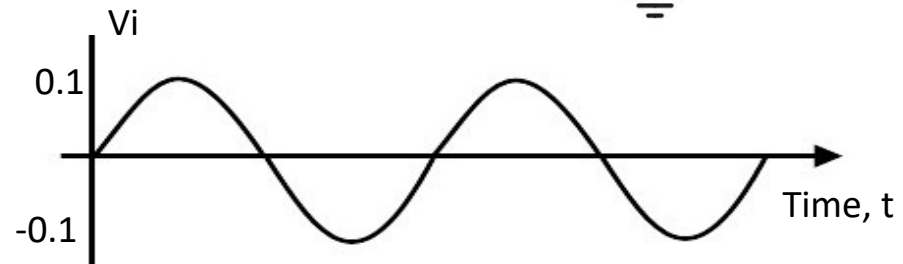C.  $V_o = \text{gain} * V_i = -5 * 0.1 \sin \omega t = -0.5 \sin \omega t$



# Example

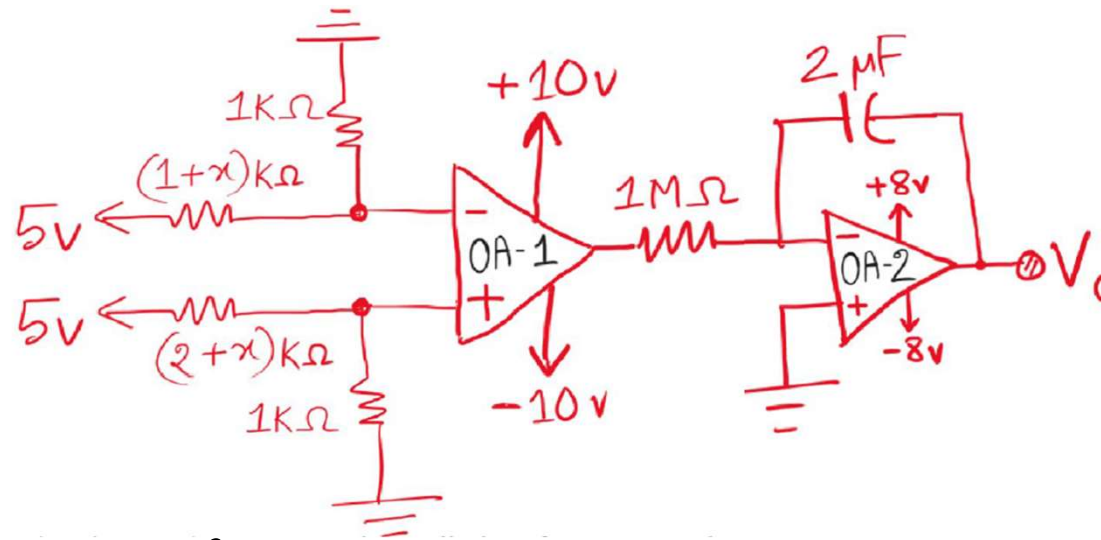


In the circuit given above,  $x = 0$


- (a) **Analyze** the circuit and **determine** the voltage at the inverting, non-inverting terminals and the output of OA-1.
- (b) **Determine** the highest  $V_O$  you can get from this circuit. **Explain** briefly.
- (c) **Analyze** the circuit to **determine** the output voltage,  $V_O$  of OA-2 and **plot**  $V_O$  vs. time. **Label** the plot appropriately. [at  $t = 0$ ,  $V_O = 0$ ]




# Voltage Follower – VTC

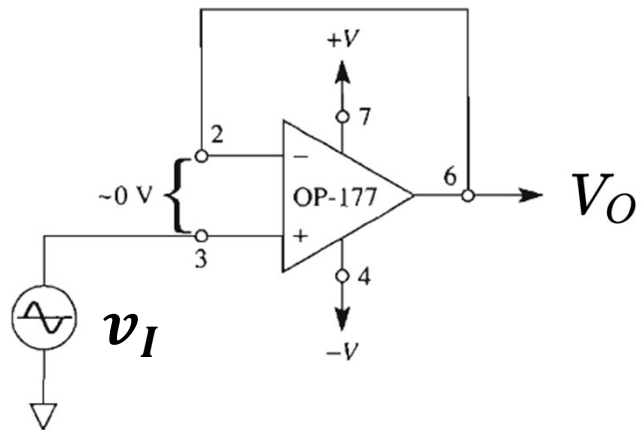

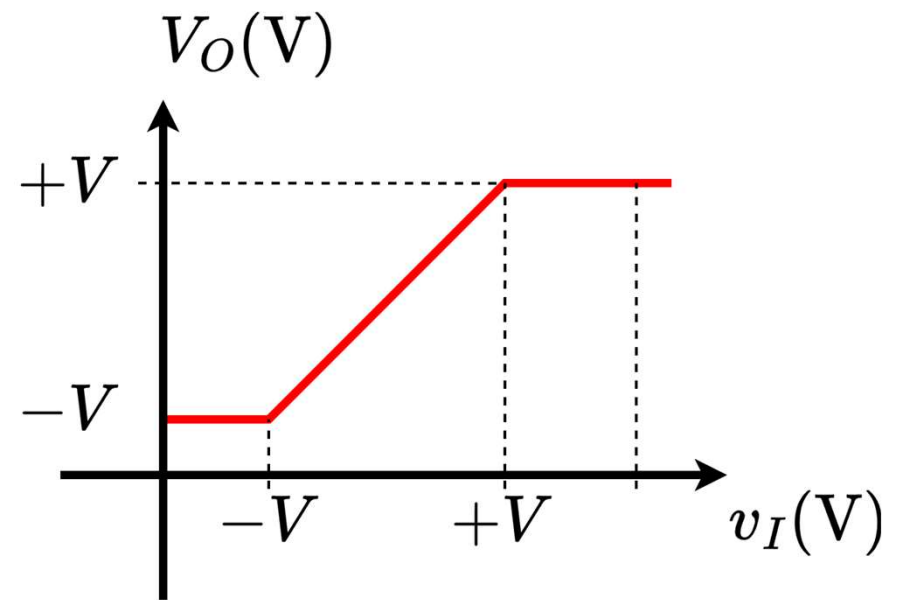
$$V_O = \begin{cases} +V, & \text{if } v_I \geq +V \\ v_I, & \text{if } -V \leq v_I \leq +V \\ -V, & \text{if } v_I \leq -V \end{cases}$$





# Inverting Amplifier – VTC

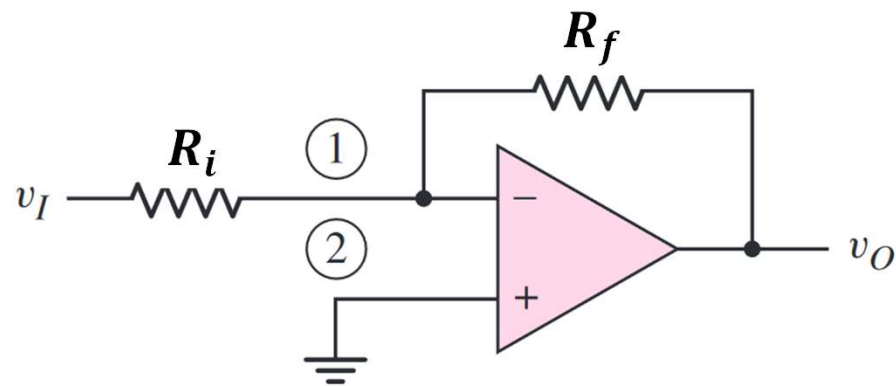
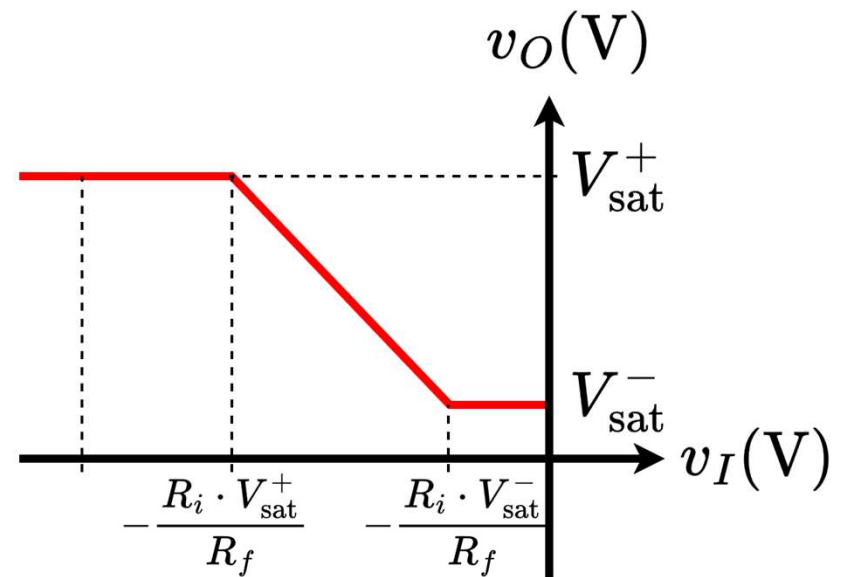
$$v_O = \begin{cases} V_{\text{sat}}^+, & \text{if } v_O \geq V_{\text{sat}}^+ \\ -v_I \cdot \frac{R_f}{R_i}, & \text{if } V_{\text{sat}}^- \leq v_O \leq V_{\text{sat}}^+ \\ V_{\text{sat}}^-, & \text{if } v_O \leq V_{\text{sat}}^- \end{cases}$$




# Non-Inverting Amplifier – VTC

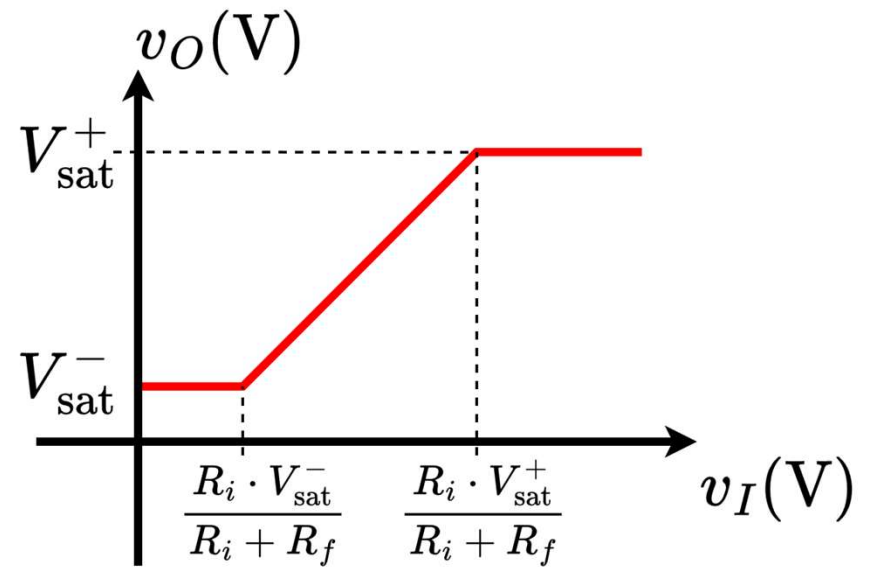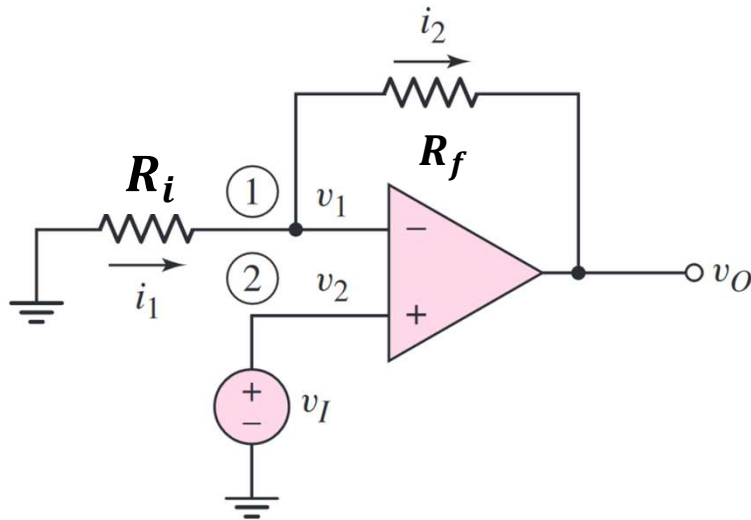

$$v_O = \begin{cases} V_{\text{sat}}^+, & \text{if } v_O \geq V_{\text{sat}}^+ \\ v_I \cdot \left(1 + \frac{R_f}{R_i}\right), & \text{if } V_{\text{sat}}^- \leq v_O \leq V_{\text{sat}}^+ \\ V_{\text{sat}}^-, & \text{if } v_O \leq V_{\text{sat}}^- \end{cases}$$

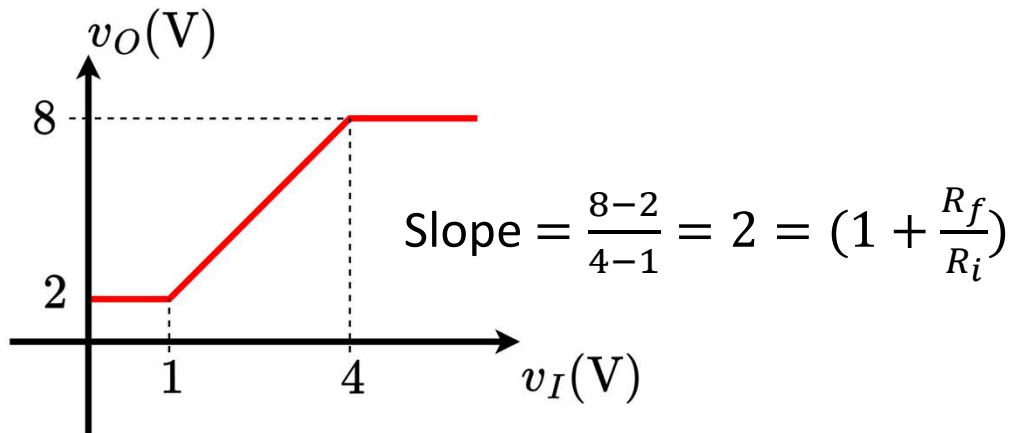
# Non-Inverting Amplifier – VTC

Draw an Op-Amp Circuit with the following VTC




$$\left(1 + \frac{R_f}{R_i}\right) = 2$$

$$\Rightarrow \frac{R_f}{R_i} = 1$$

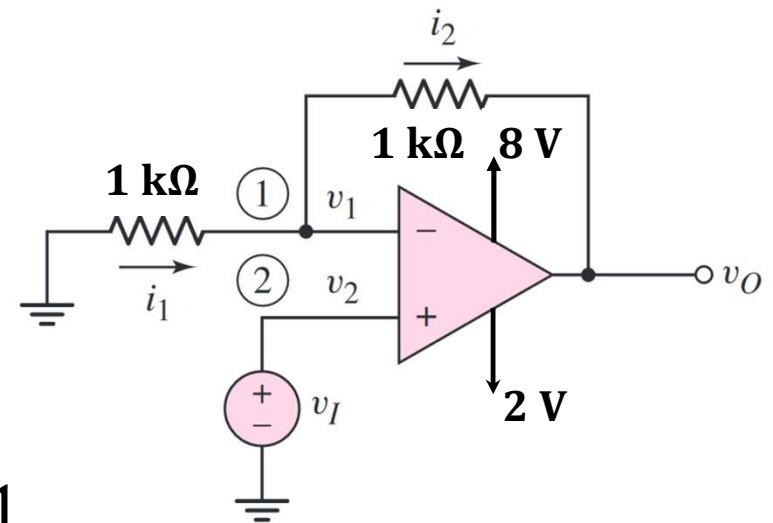


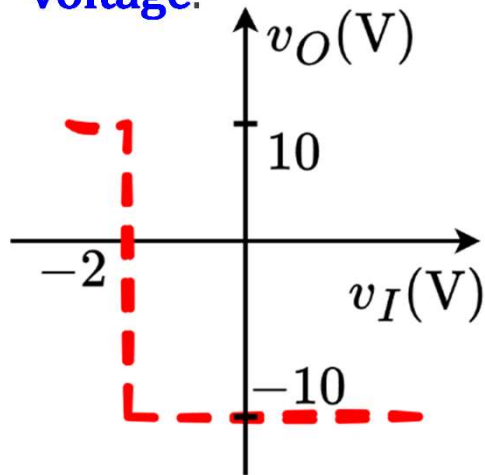
# VTC Problems

Design a circuit using **op-amp** that has the voltage transfer characteristics as shown in the figure below.  $v_O(\text{V})$  is the **output voltage** and  $v_I(\text{V})$  is the **input voltage**.



# VTC Examples

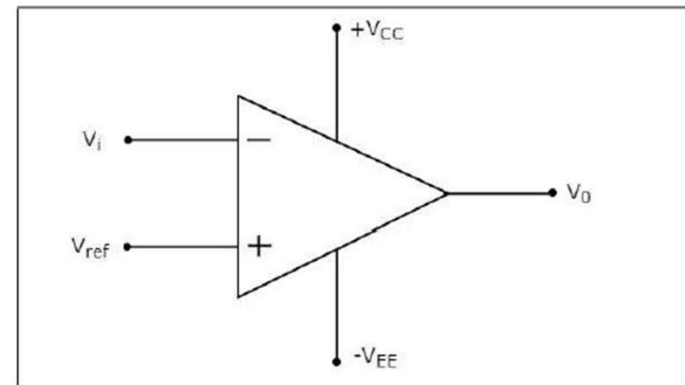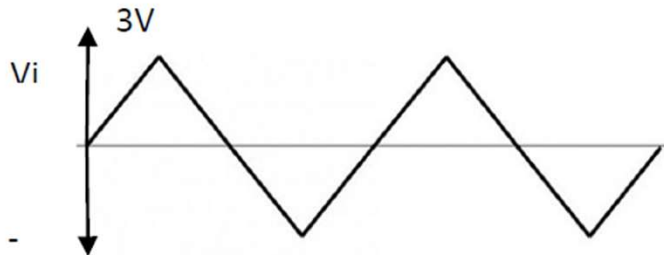**Q1:**  $V_{CC} = 15V = V_{EE}$ ,  $V_{ref} = 1V$ ,  $V_i$  is a 6V p-p triangular signal as shown below  
Draw output  $V_o$  for the following op-amp circuit.



**Thank You**