
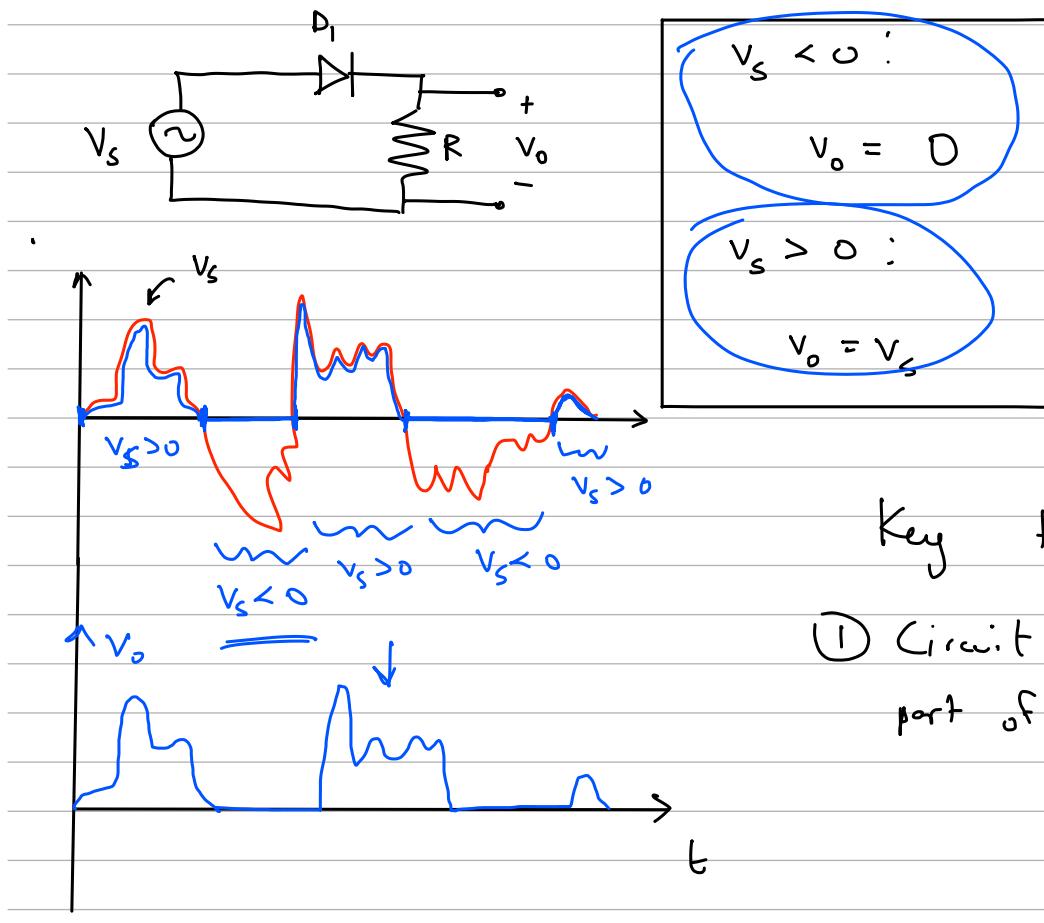


Half wave rectifier:

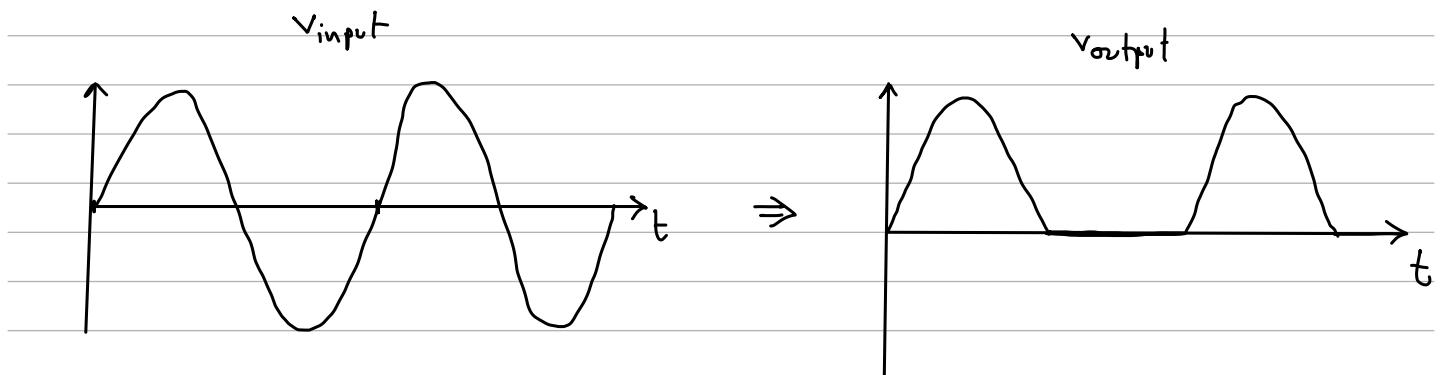

Key takeaway :

- ① Circuit keeps only +ve part of input.



5 10 12 7 2

$$\text{Avg : } \frac{(5+10+12+7+2)}{\# \text{ points}} = \frac{36}{5} = 7.2$$

5 10 12 7 2 5 10 12 7 2 5 10 12 7 2


$$\text{Avg : } \frac{(5+10+12+7+2)+(5+10+12+7+2)+(5+10+12+7+2)}{3 \times 5}$$

$\hookrightarrow \# \text{ points in duration}$

$$= \frac{\beta \times (5+10+12+7+2)}{\beta \times 5} = \frac{(5+10+12+7+2)}{5}$$

$$= 7.2$$

$f(t)$

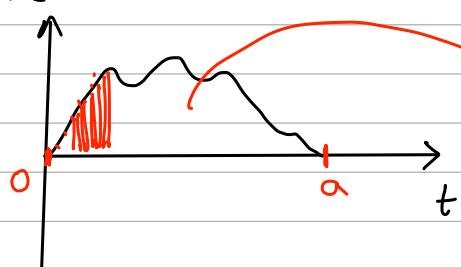


Average value :

$$\frac{\int_0^a f(t) dt}{a}$$

the equivalent
of cutting data
points

$$\frac{1}{n} \sum_{i=1}^n \Delta t \Rightarrow \int$$

$f(t)$

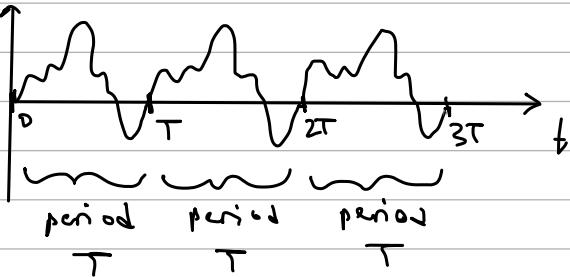


Average :

$$\frac{\int_0^{3T} f(t) dt}{3T}$$


$$= \frac{\int_0^T f(t) dt}{T}$$

$$A \sin(\omega t) \rightarrow A \sin(\omega t)$$

1 period

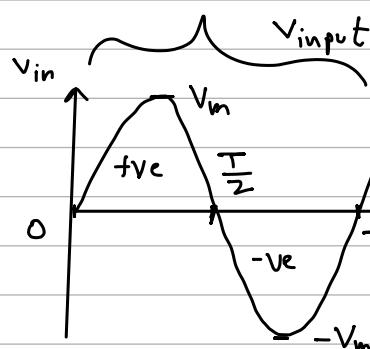

v_{out}

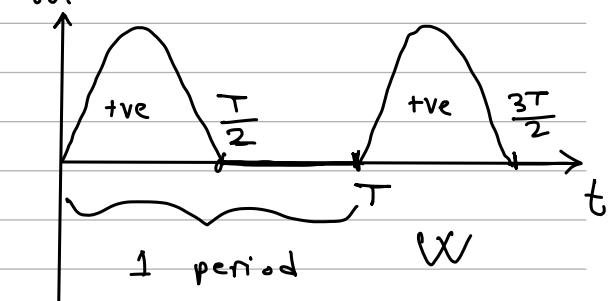

Input :

$$V_{avg} = \frac{\int_0^T v_{in} dt}{T}$$

$$\omega = \frac{2\pi}{T}$$

Output :

$$V_{avg} = \frac{\int_0^T v_{out} dt}{T}$$

$$= \int_0^{\frac{T}{2}} V_m \sin(\omega t) dt + \int_{\frac{T}{2}}^T V_m \sin(\omega t) dt$$



$$= \frac{1}{T} \int_0^{\frac{T}{2}} V_m \sin(\omega t) dt$$

$$= \frac{1}{\pi} V_m$$

$$= \frac{1}{T} \int_0^{\frac{T}{2}} V_m \sin(\omega t) dt$$

$$= 0$$

Full wave :

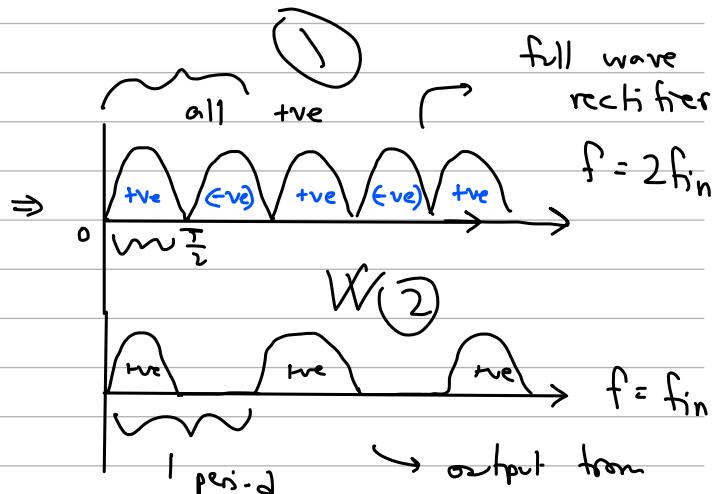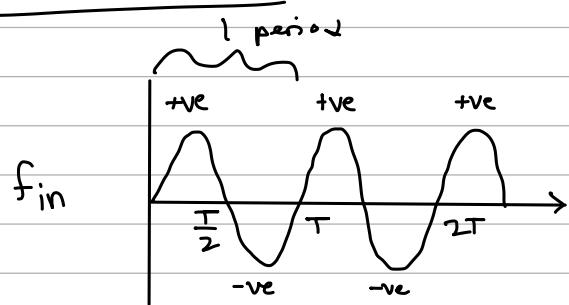


(1) → has higher avg. value


∴ has higher DC characteristic

$f = f_{in}$



→ output from half wave rectifier

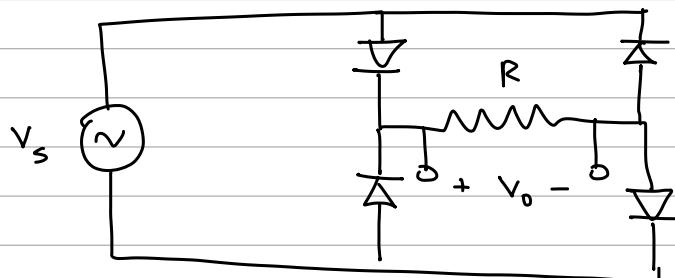

tve cycle :

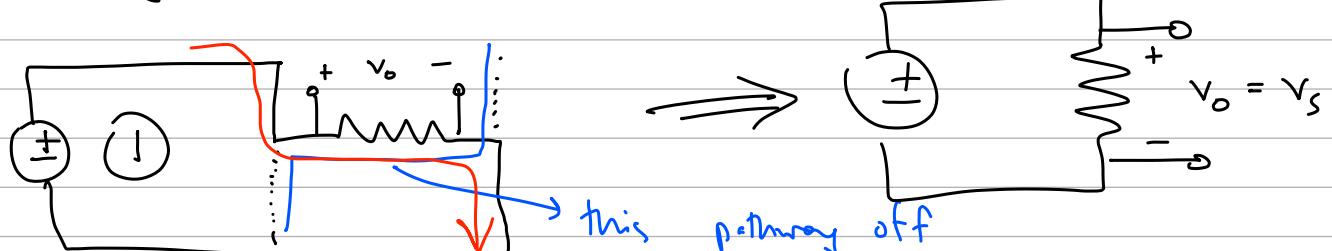


-ve cycle :

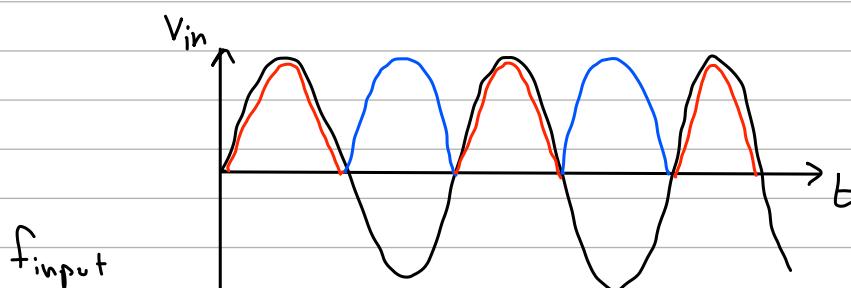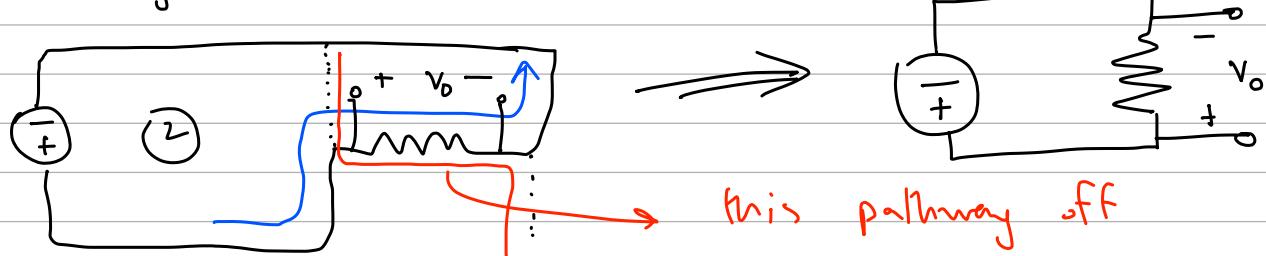


absolute value :

$$|a| = \begin{cases} a & ; a > 0 \\ -a & ; a < 0 \end{cases}$$

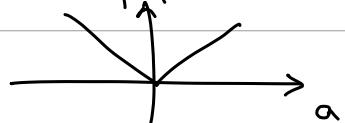


Half wave:

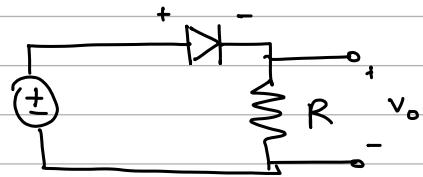

$$V_p = V_m - V_D$$

$$f = f_{\text{input}}$$
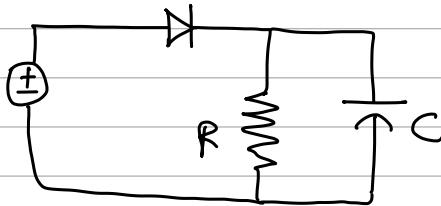
$$\begin{aligned} V_{DC} &= \frac{1}{T} \int_0^{\frac{T}{2}} (V_m \sin \omega t - V_D) dt \\ &= \frac{1}{\pi} V_m - \frac{V_D}{2} \end{aligned}$$





$$V_r(p-p) = \frac{V_p}{f \cdot RC}$$

$$V_r(\text{rms}) = \frac{V_p}{2\sqrt{3} f \cdot RC}$$

RMS \rightarrow equivalent DC value
of an AC waveform

Full wave:

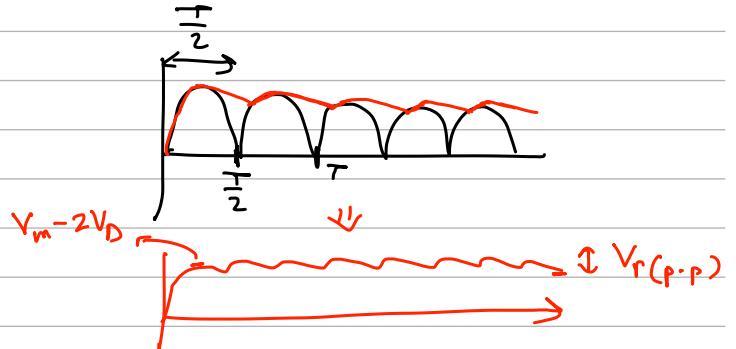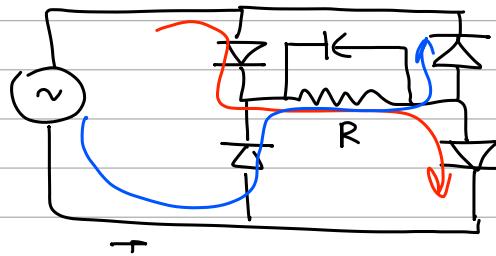

$$V_p = V_m - 2V_D$$

$$f = 2f_{\text{input}}$$

$$\begin{aligned} V_{DC} &= \frac{1}{(\frac{T}{2})} \int_0^{\frac{T}{2}} (V_m \sin \omega t - 2V_D) dt \\ &= \frac{2}{\pi} V_m - 2V_D \end{aligned}$$

$$V_r(p-p) = \frac{V_p}{f \cdot RC}$$

$$V_r(\text{rms}) = \frac{V_p}{2\sqrt{3} f \cdot RC}$$

Monday : 9:00 pm

Without capacitor, Fullwave + halfwave:

HW:

$$f = f_{in}$$

$$V_{dc} / V_{avg} = \frac{V_m}{\pi} - \frac{V_D}{2}$$

$$V_p = V_m - V_D$$



FW:

$$f = 2f_{in}$$

$$V_{dc} / V_{avg} = \frac{2}{\pi} V_m - 2V_D$$


$$V_p = V_m - 2V_D$$

With capacitor [HW+FW formula same]:

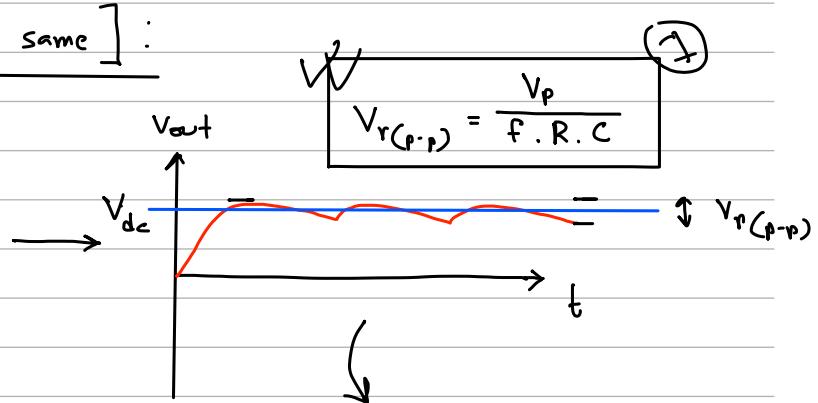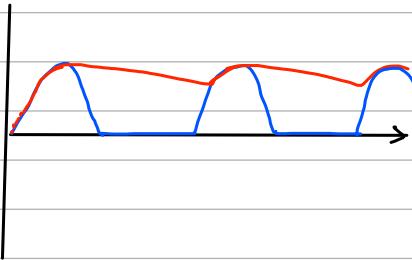

In general:
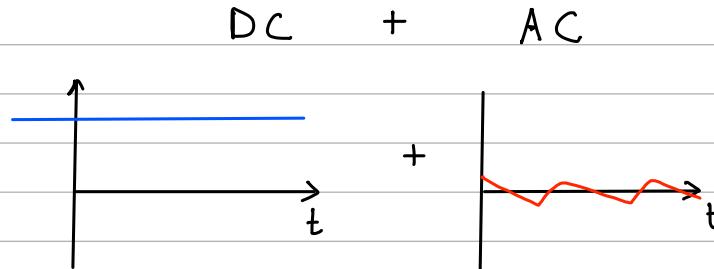
$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V_{AC}^2 dt}$$



→ rms is a characteristic of an AC wave form

Multimeter DC $\rightarrow V_{dc} / V_{avg}$

" AC $\rightarrow V_{rms}$

$$V_{dc} / V_{avg}$$

$$V_{dc} = V_p - \frac{V_{r(pp)}}{2}$$

$$V_{r(rms)}$$

$$V_{r(rms)} = \frac{V_p}{2\sqrt{3} f \cdot R \cdot C}$$

For rectifiers: $V_{ac} \downarrow \downarrow \downarrow = V_{r(rms)} \downarrow \downarrow \downarrow$

$$(3) \rightarrow V_{r(rms)} = \frac{V_p}{2\sqrt{3} f \cdot R \cdot C} = \frac{1}{2\sqrt{3}} V_{r(pp)}$$

Summarise table :

Without Capacitor

	HW	FW
Peak, V_p	$V_m - V_D$	$V_m - 2V_D$
Avg., V_{dc} / V_{avg}	$\frac{V_m}{\pi} - \frac{V_D}{2}$	$\frac{2V_m}{\pi} - 2V_D$
output freq., f	f_{in}	$2f_{in}$

With Capacitor

	HW	FW
Peak, V_p	$V_m - V_D$	$V_m - 2V_D$
ripple freq., f_R	f_{in}	$2f_{in}$
Peak to peak ripple, $V_{r(p-p)}$		$\frac{V_p}{f R C}$
RMS ripple, $V_{r(rms)}$		$\frac{1}{2\sqrt{3}} V_{r(p-p)}$
Output avg., V_{dc} / V_{avg}		$V_p - \frac{V_{r(p-p)}}{2}$



Q. We have a FW rectifier.

$$V_i = V_m \sin(\omega t)$$

↳ amp. ↳ $\omega = 2\pi f$




(a) Draw FW circuit.

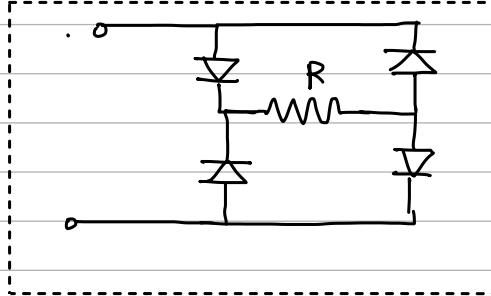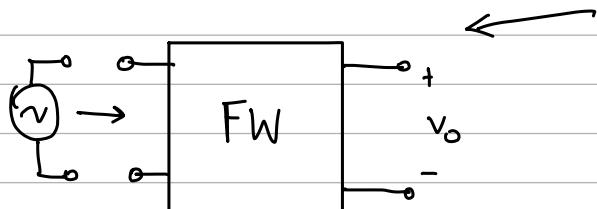

(b)

(b) Draw input, output voltage.

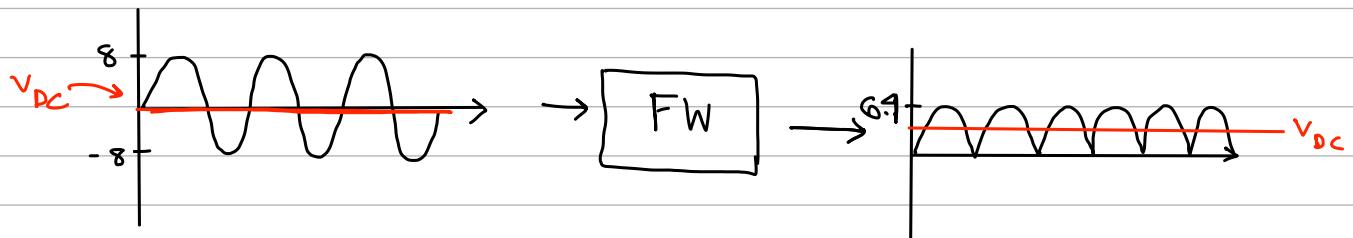

(c) $R = 50k\Omega$
 $V_D = 0.8V$ } find peak of input, output. Also DC value.

Input,

$$V_p = 8V$$

$$V_{DC} = 0V$$

Output,

$$V_p = V_m - 2V_D$$


$$= 8 - 2 \times 0.8 = 6.4V$$

$$V_{DC} = \frac{2}{\pi} V_m - 2V_D$$

$$= \frac{2}{\pi} \times 8 - 2 \times 0.8$$

$$= 3.49V$$


- (d) 10MF capacitor added in FW.

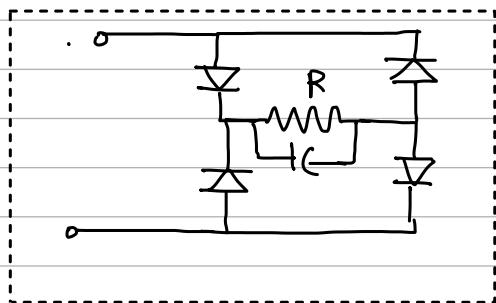

$$R = 50k\Omega$$


$$V_D = 0.8V$$

$$C = 10\mu F$$

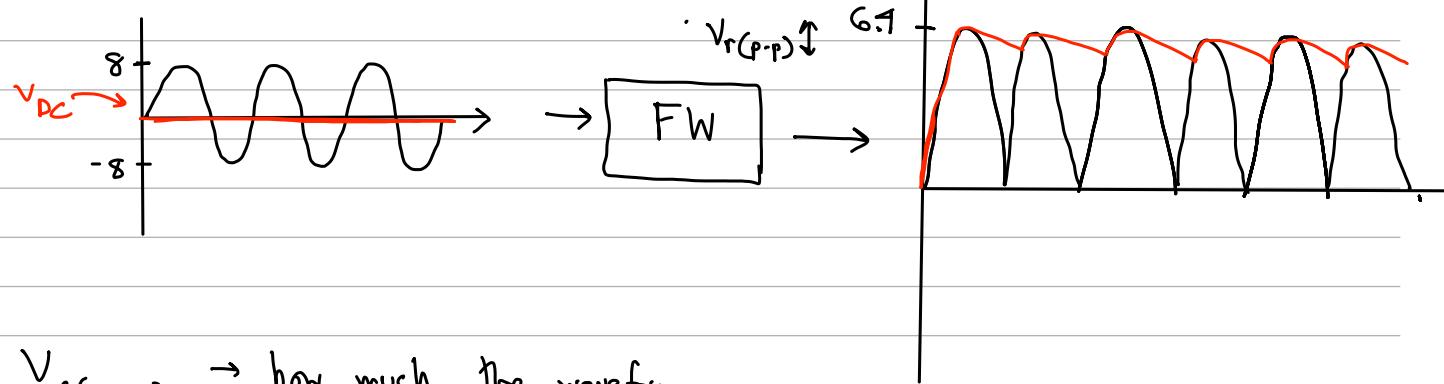

$V_r(p-p)$ → how much the waveform drops from V_p .

$$V_i = 8 \sin(2000\pi t)$$

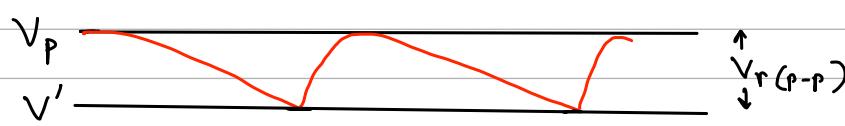

$$\omega = 2000\pi$$

$$f_{in} = \frac{\omega}{2\pi}$$

$$= \frac{2000\pi}{2\pi}$$

$$= 1000 Hz$$

$$V_r(p-p) = \frac{V_p}{fRC} = \frac{6.4}{2000 \times (50 \times 10^3) \times (10 \times 10^{-6})}$$

$$= 6.4 \times 10^{-3} V$$

$$f = 2f_{in} = 2 \times 1000$$

$$= 2000 Hz$$

$$V_{DC} = V_p - \frac{V_r(p-p)}{2} = 6.4 - (3.2 \times 10^{-3})$$

$$= 6.3968 V$$

$$V_p \rightarrow V_{r(p-p)} \downarrow \downarrow$$

ripple,

(f) Suppose, we want a 1% of input peak. Value of C?



$$V_{r(p-p)} = 1\% \text{ of } V_{\text{input peak}} = \frac{1}{100} \times 8 = 0.08$$

$$V_{r(p-p)} = \frac{6.1}{f R C} = 0.08 \rightarrow$$


$$\Rightarrow \frac{6.1}{f \times R \times 0.08} = C \quad \therefore C = \frac{6.1}{2000 \times 50 \times 10^3 \times 0.08}$$

$$= 0.8 \text{ nF}$$

$$= 8 \times 10^{-7} \text{ F}$$

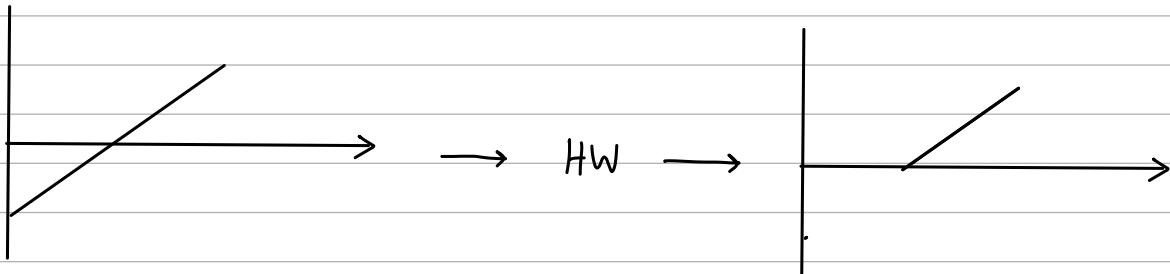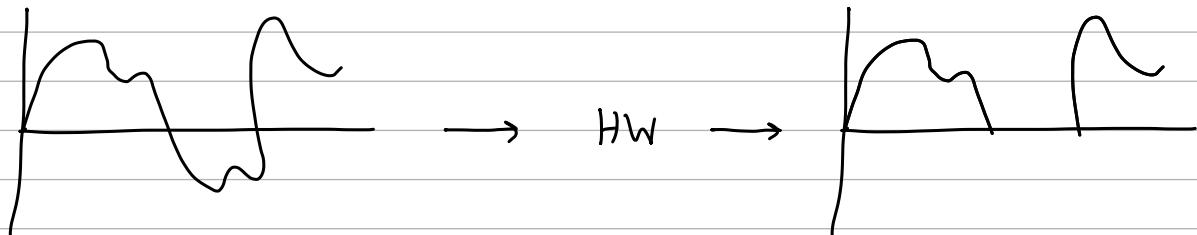

$$V_{dc} = \frac{1}{T} \int_0^T V dt$$

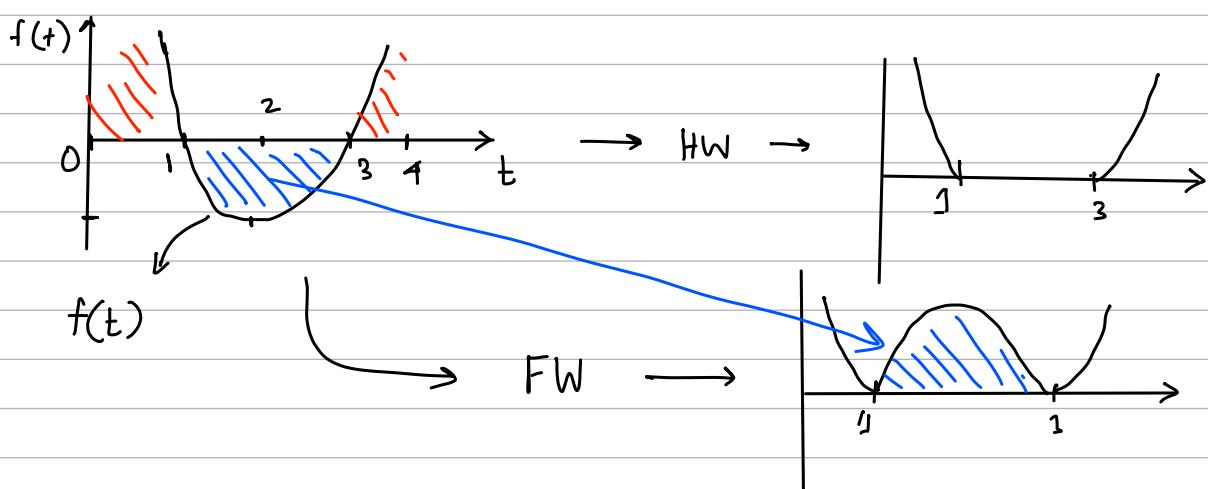

$$V_{dc} = \frac{1}{4} \int_0^4 f(t) dt = \frac{1}{4} \left[\int_0^1 f(t) dt + \underbrace{\int_1^3 f(t) dt}_{\text{blue part}} + \int_3^4 f(t) dt \right]$$

blue part

For FW:

$$V_{dc} = \frac{1}{4} \left[\int_0^1 f(t) dt + \left| \int_1^3 f(t) dt \right| + \int_3^4 f(t) dt \right]$$