

# Lecture 5

Op Amp – Part 3

# Inverting Adder

Consider  $v_1$  first, and deactivate other ( $v_2, v_3, v_4$ ) sources.

It is nothing but a non-inverting amplifier.

$$\text{So, } v_{o1} = -\frac{R_f}{R_1} v_1$$

Similarly, if we active one source and deactivate others, we will get:

$$v_{o2} = -\frac{R_f}{R_2} v_2, v_{o3} = -\frac{R_f}{R_3} v_3, v_{o4} = -\frac{R_f}{R_4} v_4$$


Now, using **superposition principle**,

$$v_o = v_{o1} + v_{o2} + v_{o3} + v_{o4}$$

$$\text{So, } v_o = -\frac{R_f}{R_1} v_1 - \frac{R_f}{R_2} v_2 - \frac{R_f}{R_3} v_3 - \frac{R_f}{R_4} v_4$$

$$\text{Or, } v_o = -\left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3 + \frac{R_f}{R_4} v_4\right)$$

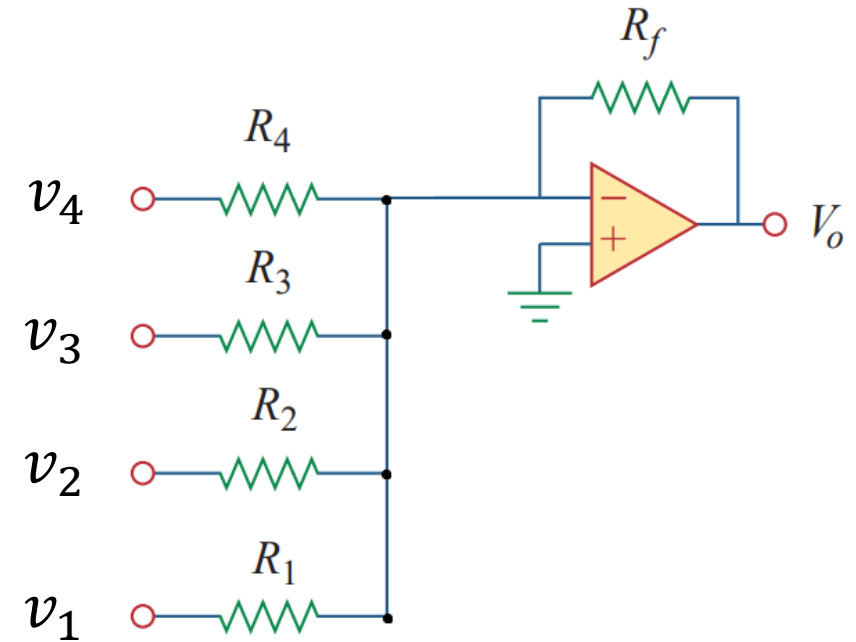**We can use this circuit to add any 'n' number of inputs!**



# Example

**Implement the following function using op-amps:**


$$v_0 = -(v_1 + 0.5v_2 + v_3)$$

**Solution:**

Here,  $R_f/R_1 = 1$ ,  $R_f/R_2 = 0.5$ ,  $R_f/R_3 = 1$

If  $R_f = 1 \text{ k}\Omega$ ,  $R_2 = 2 \text{ k}\Omega$ ,  $R_3 = 1 \text{ k}\Omega$

# Op Amp as Differentiator

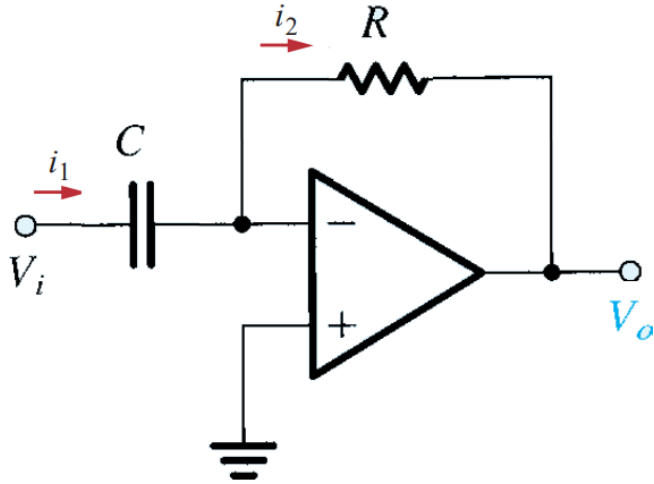

Since  $v_+$  is connected to ground,  $v_+ = 0V$

Since there is negative feedback, from virtual short,  $v_- = v_+ = 0V$


For the capacitor  $C$ ,  $\Rightarrow i_1 = C \frac{dv_C}{dt} = C \frac{d(v_i - v_-)}{dt} = C \frac{dv_i}{dt}$

From Ohm's law for  $R \Rightarrow i_2 = \frac{v_- - v_o}{R} = -\frac{v_o}{R}$

Since ideal op-amp,  $i_- = i_+ = 0$ , so  $i_1 = i_2$

$$\Rightarrow -\frac{v_o}{R} = C \frac{dv_i}{dt} \Rightarrow v_o = -RC \frac{dv_i}{dt} \text{ [Ans.]}$$

## Review – Capacitor

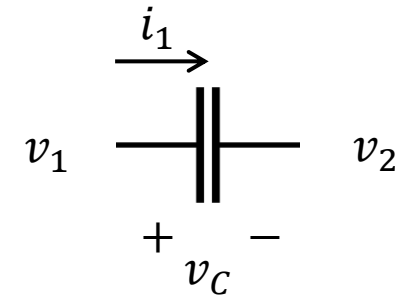

$$i_1 = C \frac{dv_C}{dt} = C \frac{d(v_1 - v_2)}{dt}$$

# Op Amp as Integrator

Since  $v_+$  is connected to ground,  $v_+ = 0V$

Since there is negative feedback, from virtual short,  $v_- = v_+ = 0V$

From Ohm's law for  $R \Rightarrow i_1 = \frac{v_i - v_-}{R} = \frac{v_i}{R}$


For the capacitor  $C$ ,  $\Rightarrow i_2 = C \frac{dv_C}{dt} = C \frac{d(v_- - v_o)}{dt} = -C \frac{dv_o}{dt}$

Since ideal op-amp,  $i_- = i_+ = 0$ , so  $i_1 = i_2$

$$\Rightarrow \frac{v_i}{R} = -C \frac{dv_o}{dt}$$


$$= -RC \frac{dv_o}{dt}$$
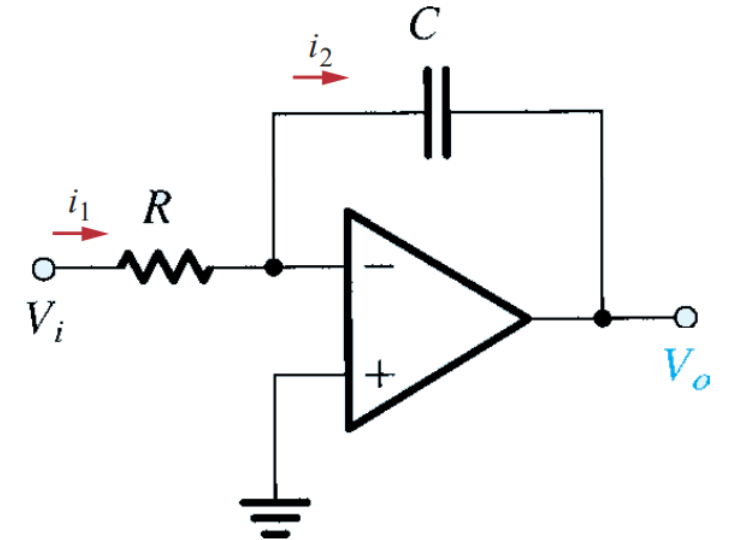
$$\Rightarrow v_o = -\frac{1}{RC} \int v_i dt$$


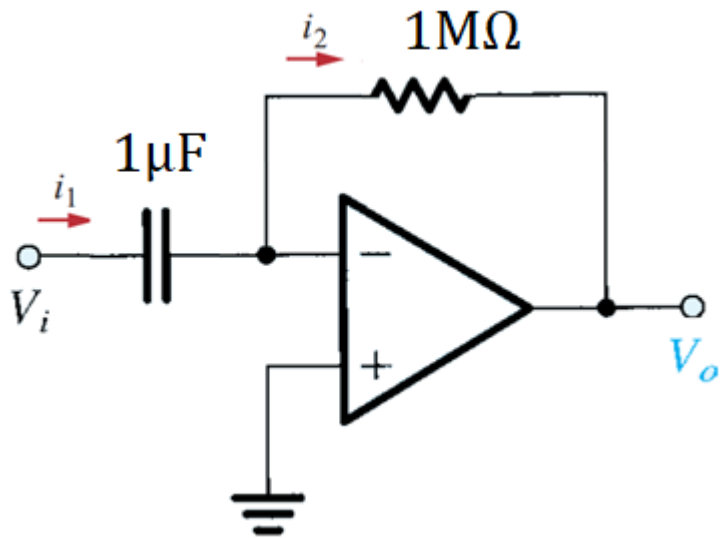
# Example

**Observe** the following Figure. If  $v_i = 5\sin 6t$ , Find the value of  $v_o$ .




**Solution:**

This is a **differentiator**.

$$\text{So, } v_o = -RC \frac{dv_i}{dt} = -1 \times 10^6 \times 1 \times 10^{-6} \times \frac{d(5\sin 6t)}{dt}$$
$$\Rightarrow v_o = -1 \times (5 \times 6 \cos 6t) = -30 \cos 6t \text{ [Ans.]}$$
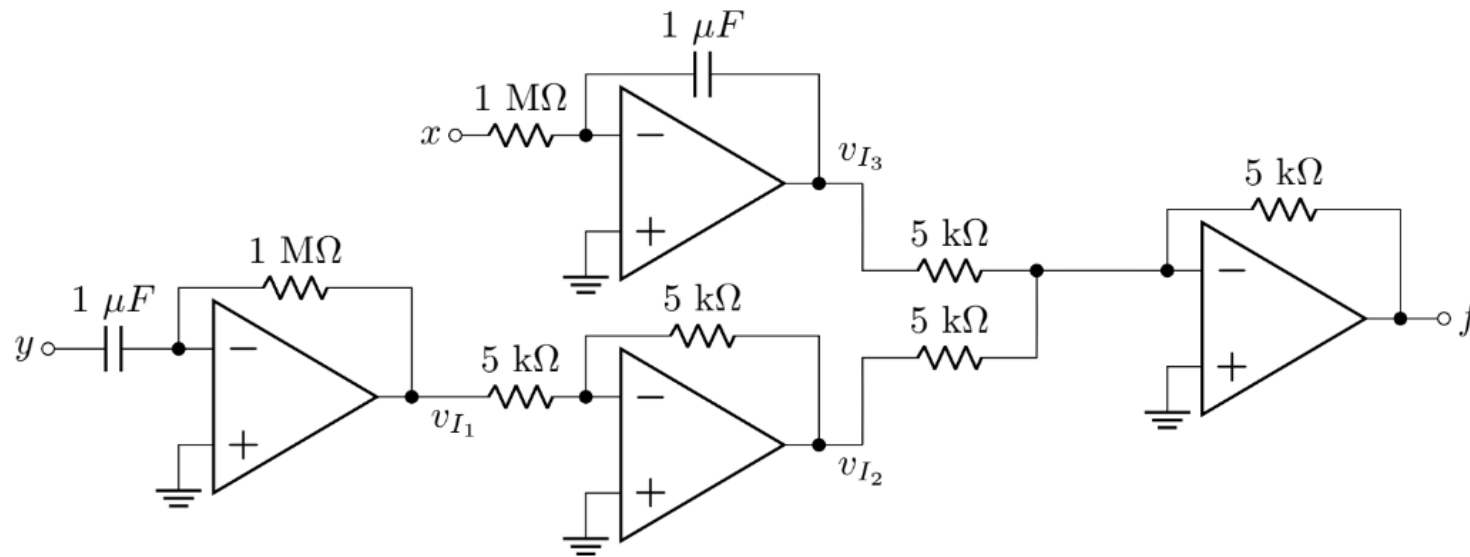
# Example

**Analyze** the circuit below to **find** an expression of  $f$  in terms of inputs  $x$  and  $y$ .



**Solution:**

$$v_{I1} = -\frac{dy}{dt}; v_{I3} = -\frac{1}{RC} \int x\ dt; v_{I2} = -v_{I1} = \frac{dy}{dt}; f = -(v_{I2} + v_{I3})$$