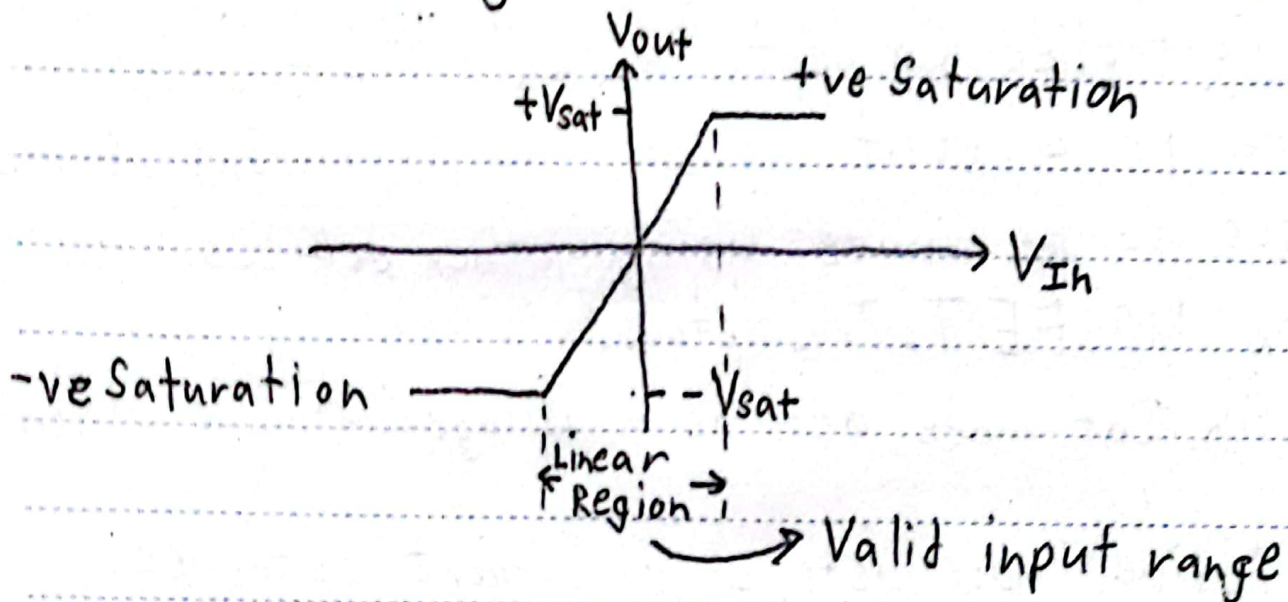



- * Linear Amplifier \Rightarrow Output = $k \times$ Input [$k = \text{gain}$]
- * Input/Output can be voltage or current.
- * $P_{out} > P_{in}$, so power supply is needed.
- * Usage: Communication

Transfer characteristics of Amps:

- * Acts as a straight line going through the origin,
 $y = mX$ [$m = k = \text{gain}$]



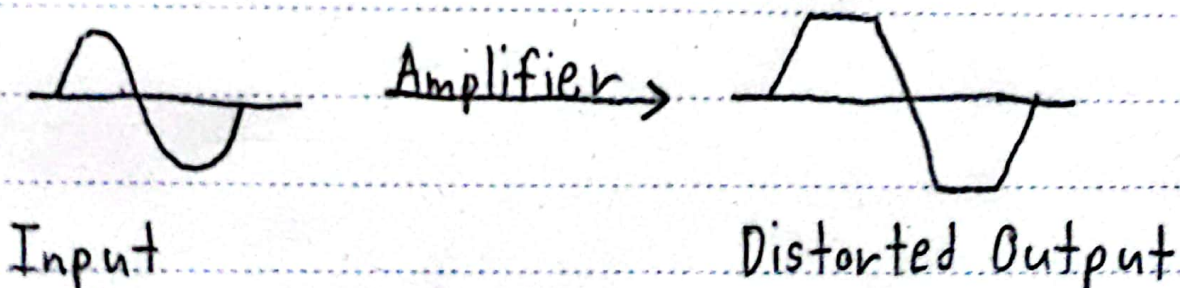- * Saturation due to limited power supply
- * Input must be in valid input range or the output will be distorted.



* Inverting amps have negative gain, $y = -m x$.
* Depending on input (V/I) and output (V/I) there can be 4 types of amps:

- 1) Voltage amplifier ($I_{in} = V, O_{ut} = V$)
- 2) Current " ($I_{in} = I, O_{ut} = I$)
- 3) Transconductance amplifier ($I_{in} = V, O_{ut} = I$)
- 4) Transresistance " ($I_{in} = I, O_{ut} = V$)


* Dependent Sources can be used to make amplifiers.

* E.g., for transconductance amp, $I_{out} = g_m \times V_{in} \Rightarrow$
Voltage Controlled Current Source (VCCS).

* There are no current sources or dependent sources they need to be made using other devices. Like BJT and MOSFET, Transistors.


- MOSFET in Sat mode acts as a Voltage Controlled Current Source.
- BJT in Active mode acts as a Current controlled Current Source.
- BJT ~~is~~ in Active mode is preferred as the relation is linear of I/O.

*BJT Common Emitter Amplifier:

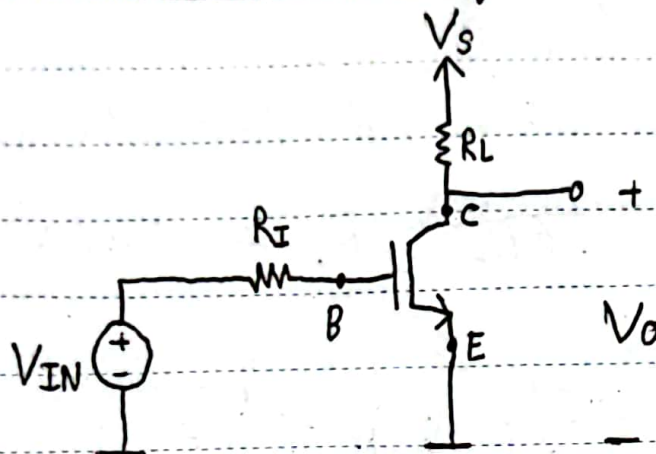

• This circuit is same as BJT inverter.

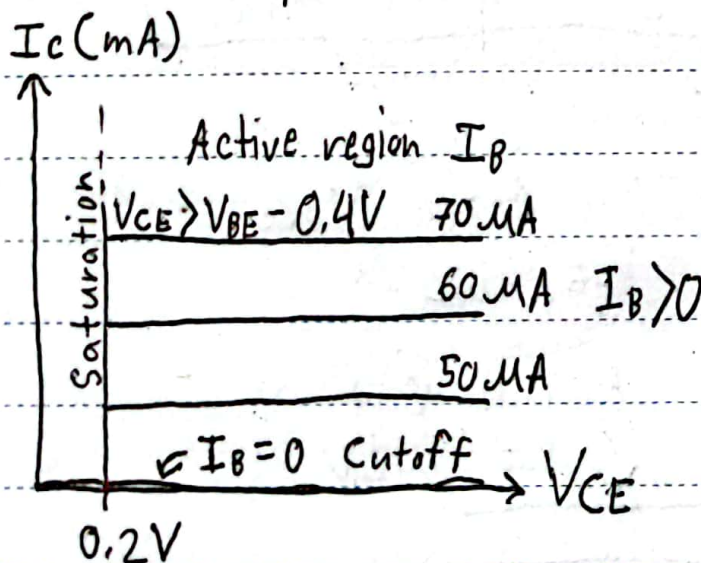- In Active Mode, $I_{out} = \beta I_{in}$ [$I_{in} = I_B$ and $I_{out} = I_C$]
- R_I converts input voltage (V_{IN}) to I_B .
- R_L " output current I_C to V_O (Output Voltage).



* KVL: $V_O = V_{CE} = V_S - I_C \times R_L$ (True for any mode)

* Cutoff: $I_B = 0 \Rightarrow V_{BE} \leq 0.7V \Rightarrow V_{IN} \leq 0.7V$

$$V_O = V_S - 0 \times R_L = V_S \text{ (since in cutoff } I_B = 0)$$

* Active: $V_{CE} = V_O > 0.2V$, $0.7 < V_{IN} < 0.7 + \left(\frac{V_S - 0.2}{\beta R_L}\right) R_I$

$$V_O = \left(V_S + \frac{0.7 \beta R_L}{R_I}\right) - \frac{\beta R_L}{R_I} V_{IN}$$

* Saturation: $V_{IN} > 0.7 + \left(\frac{V_s - 0.2}{\beta R_L} \right) R_I$
 $V_o = V_{CE} = 0.2V$


VTC of BJT/CE Amplifier:

Let $R_I = 100k\Omega$, $R_L = 10k\Omega$, $\beta = 100$, $V_s = 10V$

Threshold Voltage $= 0.7 + \left(\frac{V_s - 0.2}{\beta R_L} \right) R_I = 0.7 + \left(\frac{10 - 0.2}{100 \times 10} \right) 100$
 $= 1.68V$

$$V_o = \left(V_s + \frac{0.7 \beta R_L}{R_I} \right) - \frac{\beta R_L}{R_I} V_{IN} \Rightarrow \boxed{V_o = 17 - 10V_{IN}}$$

$V_{IN} \leq 0.7$	$V_o = 10$	Cutoff
$0.7 < V_{IN} < 1.68$	$V_o = 17 - 10V_{IN}$	Active
$V_{IN} \geq 1.68$	$V_o = 0.2$	Saturation

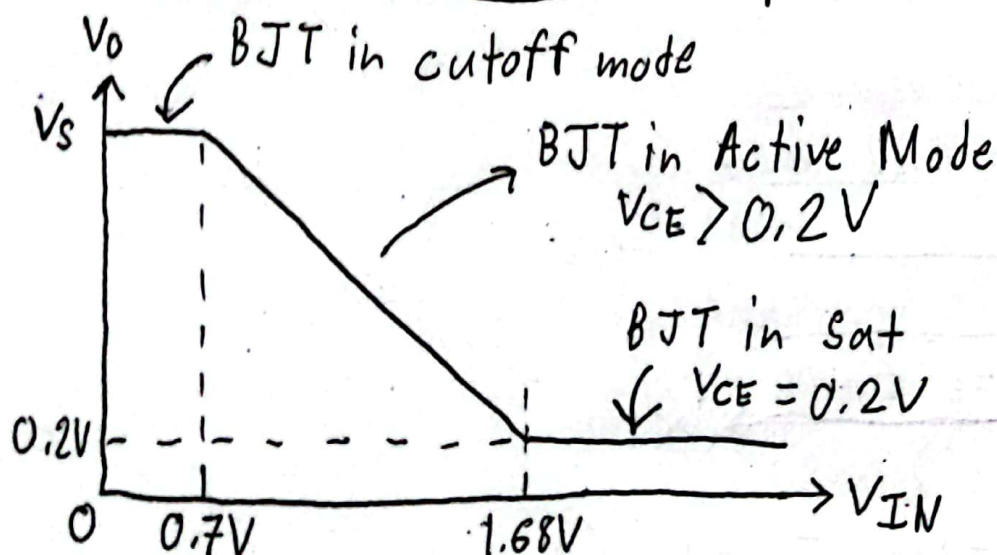

* If $V_{IN} = 1 \sin \omega t$, output will be distorted since for $V_{IN} \leq 0.7V$ in cutoff and $0.7 < V_{IN} < 1.68$ in active, Hence does not amplify "Large" Signals.

Small Signal Amplification:

V_{IN}	V_O
0.5	10
0.7	10
1	7
1.3	4
1.4	3
1.5	2
1.6	1
1.7	0.2
1.8	0.2

• Overall gain, $1.3V \Delta$ in in, $9.8V \Delta$ in out.


• But non-linear overall.

• Linear in Active Region.

• $0.1V$ change in in $\Rightarrow 1V$ change in out

• ~~Output~~ 10-fold change \Rightarrow Amplification!

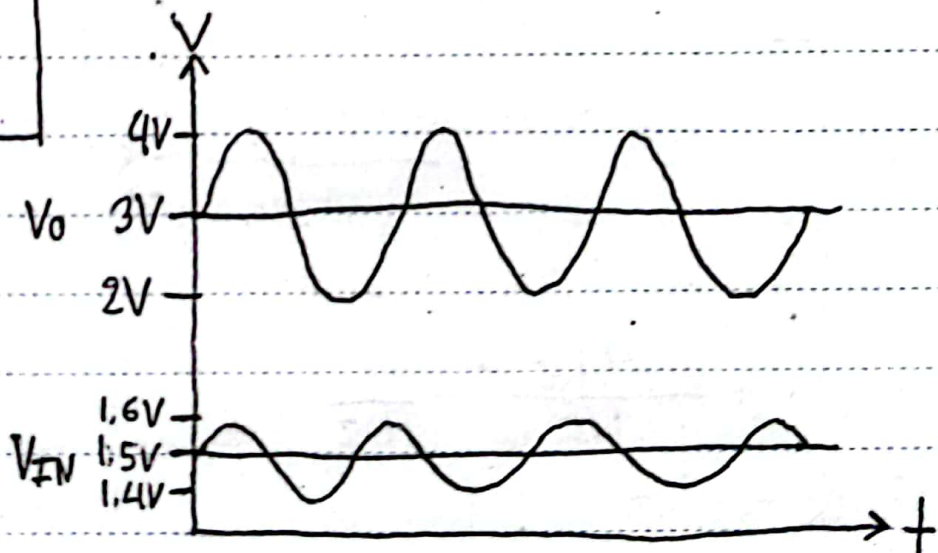
* Say $V_{IN} = 1.5 \pm 0.1V$, then $V_O = 2 \mp 1V$



* Here a 'small' signal of $0.1V$ amp with input offset $1.5V$ will have a $1V$ amp for the small signal output with an output offset $2V$, and gain $k = -10$.

* Small signal = an AC signal with small amplitude.

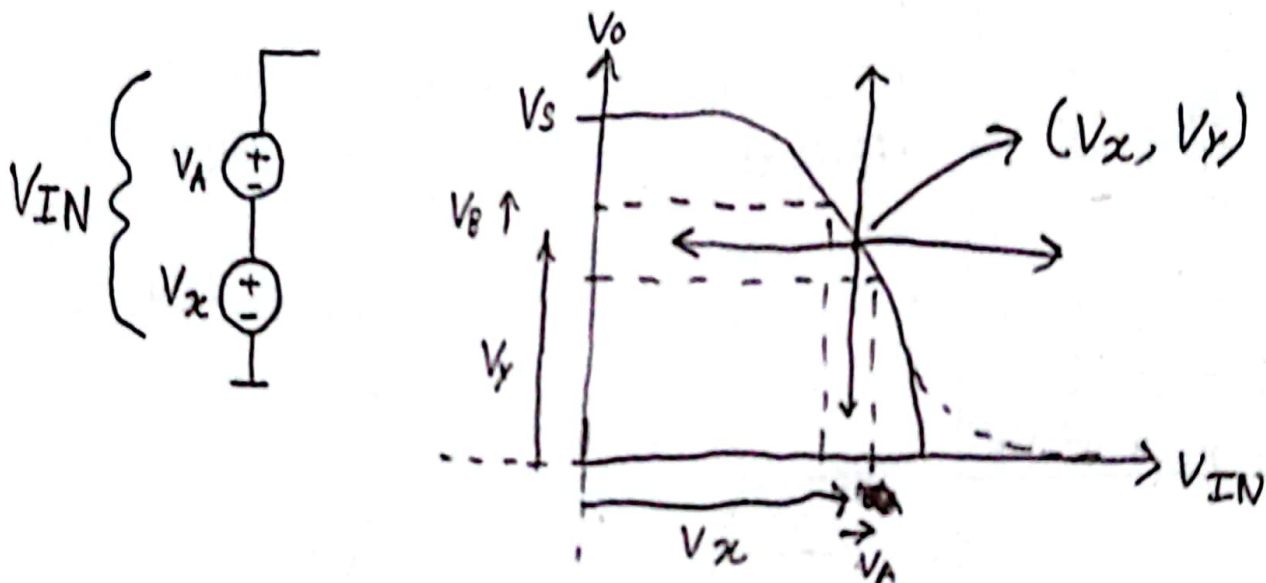- In general $V_{IN} = V_x + V_A \Rightarrow V_o = V_y + V_B$
- V_A and V_B are I/O small signals of interest and $V_B = k V_A$, where $k = -\frac{\beta R_L}{R_I} = \text{gain}$.
- V_x and V_y are I/O bias, called the operating bias or bias point or Q-point.
- Biasing is used to ensure BJT stays in Active region.



TC of amp with Bias point

- * $V_y = \left(V_s + \frac{0.7 \beta R_L}{R_I} \right) - \frac{\beta R_L}{R_I} V_x$
- * Select Q-point in such a way that input is within Valid voltage range.
- * Valid voltage range: $0.7 < V_{IN} < 0.7 + \left(\frac{V_s - 0.7}{\beta R_L} \right) R_I$
- * Best Q-point is middle of active region, which gives max swing (peak-to-peak) for V_A .