

Lec 3

Lecture 3


Sub.:

SAT ☐ SUN ☐ MON ☐ TUE ☐ WED ☐ THU ☐ FRI ☐

DATE: / /


(op-amp) Rough

operational amplifiers:

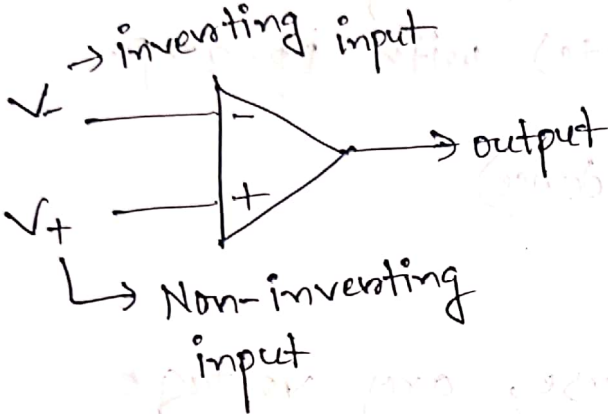

Differential amplifiers \Rightarrow amplifiers difference.
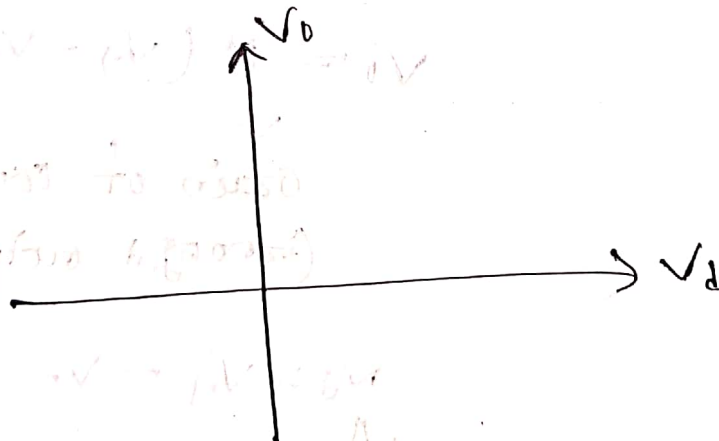
$$V_o = A(V_+ - V_-)$$
$$\boxed{V_o = A V_d} \quad \text{where } [V_d = V_+ - V_-]$$



Sub.: _____

SAT ☐ SUN ☐ MON ☐ TUE ☐ WED ☐ THU ☐ FRI ☐

DATE: / /

why operational?

→ cause if we can perform any mathematical operation (+, -, *, / etc) with op-amp.

op-amp (3 terminal device)

inverting input cause, any voltage provide in V_- terminal will be multiplied by -1.

why differential? because it doesn't amplify particular voltage rather it amplifies voltage difference. $(V_+ - V_-)$

$$V_o = A (V_+ - V_-)$$

↓
gain of amplifier.

(correct output & voltage)

$$V_d = V_+ - V_-$$

↑
voltage difference.

$$\boxed{V_o = A V_d}$$


Sub.: _____

SAT ☐ SUN ☐ MON ☐ TUE ☐ WED ☐ THU ☐ FRI ☐

DATE: / /

Now from: where this output amplification

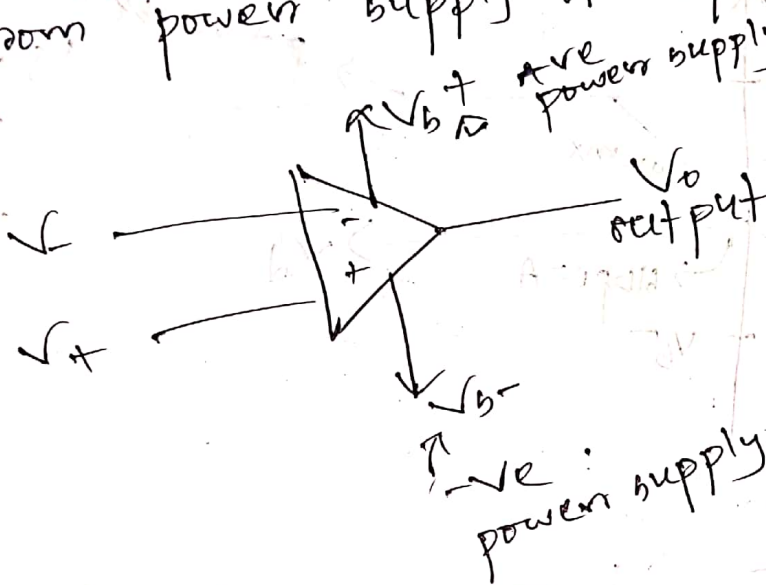come?
from power supply of op-amp. $[V_6^+$ and $V_6^-]$



we need power supply because output
voltage ~~difference~~ should be higher than
input voltage difference.

LB

* lab's op-amp usually


$V_{b+} = 15V$ and $V_{b-} = -15V$

Sub.: _____


SUN MON TUE WED THU FRI

DATE: / /

Transfer characteristics: of op-amp:

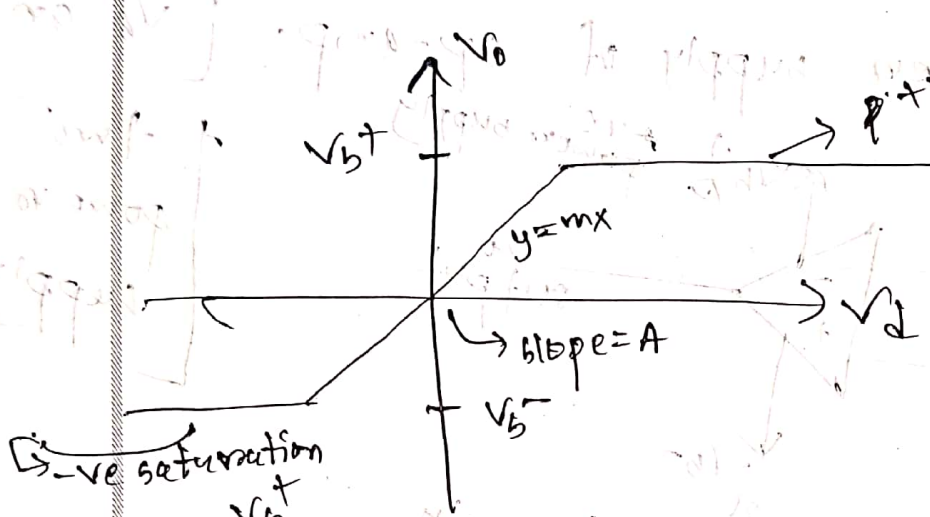

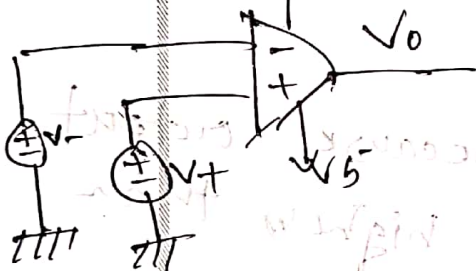when V_d crosses valid input range then V_o saturation



Example:

$$A = 100$$

$$V_+ = 10V$$

$$V_- = -10V$$

$$① V_+ = 1.01V, V_- = 1V$$

$$V_d = ? \quad V_o = ?$$

$$V_d = V_+ - V_- = 0.01V$$

$$V_o = 100 \times 0.01 = 1V$$

$$② V_d = 0.02V$$

$$\therefore V_o = 2V$$

$$③ V_d = 0.1V$$

$$V_o = 10V$$

$$④ V_d = 0.2V$$

$$[V_o = 20V? \text{ No}]$$

$$\therefore V_o = 10V$$

Opm - contains of BJT

Sub.: _____


SAT ☐ SUN ☐ MON ☐ TUE ☐ WED ☐ THU ☐ FRI ☐

DATE: / /

∴ For this case valid input range is

$$-0.1 < V_d < 0.1$$

Ideal op-amp

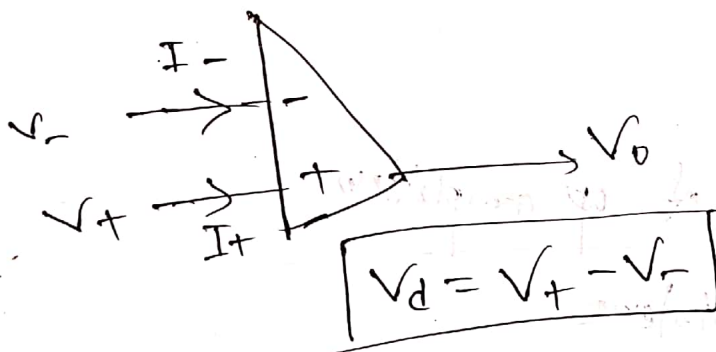


Normal op-amp

Gain $A = 100, 200$

but practical
real life &
ideal op-amp
has $A = \infty$
(too
large)

∴ $A = \infty$

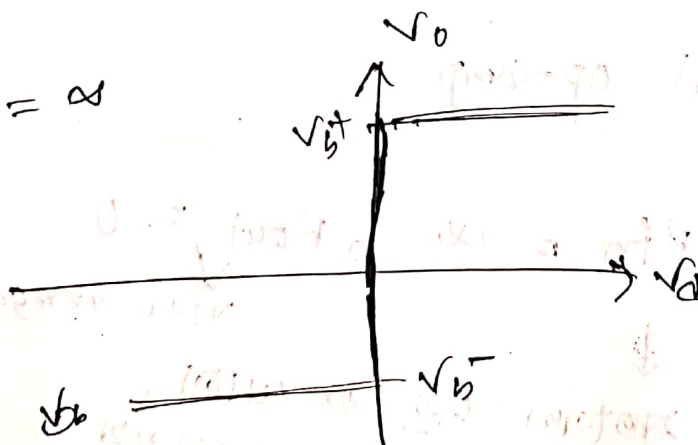

practical
op-amp
 $A = 10^6 \sim 10^7$

Sub.: _____

SAT ☐ SUN ☐ MON ☐ TUE ☐ WED ☐ THU ☐ FRI ☐

DATE: / /

Now what's the valid input range for ideal op-amp? (from transfer characteristic)

$V_d = 0V$

$\therefore A = \infty$ $\left[\begin{array}{l} \text{if } V_d > 0 \Rightarrow V_o = V_{s+} \\ \text{and } V_d < 0 \Rightarrow V_o = V_{s-} \end{array} \right.$

properties of ideal op-amp \Rightarrow

Other properties of op amplifiers:

1. input resistance
2. output "

For ideal op-amp

$R_{in} = \infty$

$R_{out} = 0$

prohara

vice versa



loading effect

Sub: _____

SAT ☐ SUN ☐ MON ☐ TUE ☐ WED ☐ THU ☐ FRI ☐

DATE: / /

∴ For this case $I_- = 0$
 $I_+ = 0$ } ideal op-amp.

Note that **

For ideal op-amp:

1. $A = \infty$
2. $R_{in} = \infty$, $R_o = 0$
3. $I_- = 0$, $I_+ = 0$

but the

behaviour

$$V_d > 0$$

$$\Rightarrow V_o = V_{s+}$$

$$V_d < 0$$

$$\Rightarrow V_o = V_{s-}$$

like comparator.

that is

$$V_+ > V_- \Rightarrow V_o = V_{s+}$$

$$\text{and } V_+ < V_- \Rightarrow V_o = V_{s-}$$

by which is greater

so we can measure two voltage without measuring the voltage.

Sub.: _____


L3

Exam question use case to

SAT ☐ SUN ☐ MON ☐ TUE ☐ WED ☐ THU ☐ FRI ☐
 design circuit
 DATE: / /

go use case of ideal op-amp.

① comparators

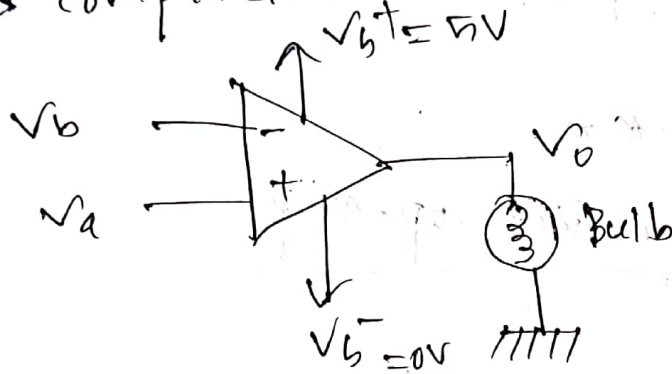

$$V_d = V_a - V_b$$

$\therefore V_d > 0$ means $V_a > V_b$

and $V_d < 0$ " $V_a < V_b$

if $V_a > V_b \Rightarrow V_o = 5V$ no bulb on

and if $V_a < V_b \Rightarrow V_o = 0V$ " " OFF


* if multiple voltage then compare
for ~~two~~ voltage pairs and pick one
from them for next test.

Sub.: _____

SAT ☐ SUN ☐ MON ☐ TUE ☐ WED ☐ THU ☐ FRI ☐

DATE: / /

② Turn ON AC automatically.

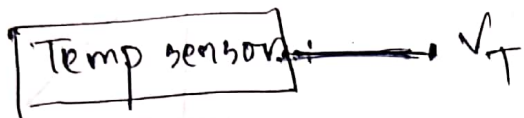


$V_T \propto \text{Temp}$

if $\text{Temp} = 23^\circ, V_T = 1V$
 if $\text{Temp} = 24^\circ, V_T = 2V$
 if $\text{Temp} = 25^\circ, V_T = 3V$

if $\text{Temp} > 24^\circ$ AC ON
 if $\text{Temp} < 24^\circ$ AC OFF

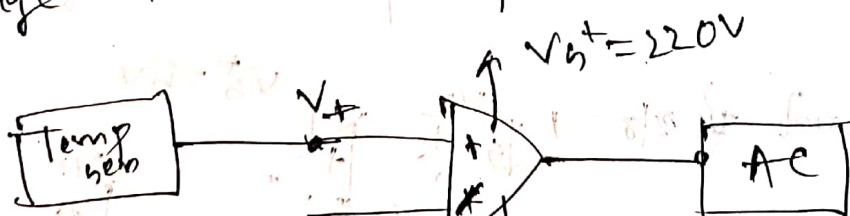So here we can't measure temperature, we can compare the voltage only. So we compare the voltage with ideal temp. So



$V_T > 2 \Rightarrow V_O = 220V$
 $V_T < 2 \Rightarrow V_O = 0V$

set voltage




Design error is
 because positive & negative
 voltage

Sub.: _____


SAT ☐ SUN ☐ MON ☐ TUE ☐ WED ☐ THU ☐ FRI ☐

DATE: / /

③ smoke detector :

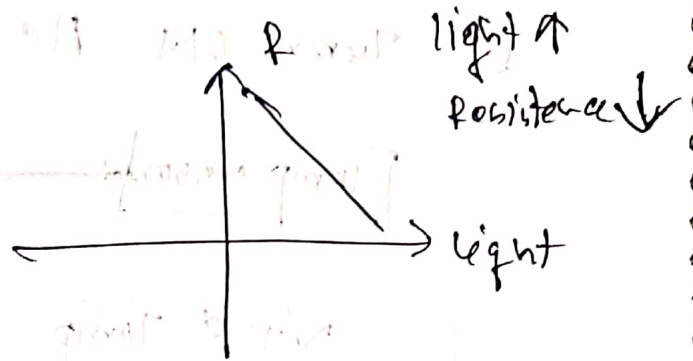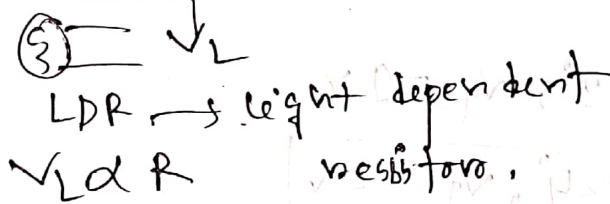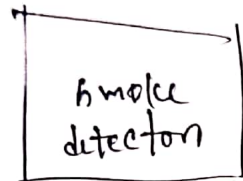

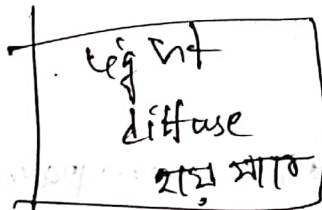No smoke $V_L = \text{small} = 2V$ (assume) \rightarrow intermittent voltage
 smoke $V_L = \text{high} = 4V$ (assume)




so we want

if $V_L > 3V \Rightarrow$ Alarm ON

$V_L < 3V \Rightarrow$ OFF

positive negative

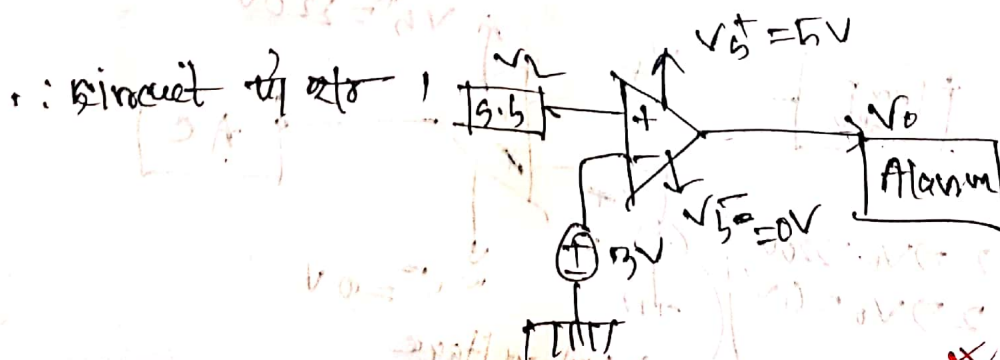

④ Op-amp (here using open loop configuration)

Sub.: _____

SAT ☐ SUN ☐ MON ☐ TUE ☐ WED ☐ THU ☐ FRI ☐

DATE: / /

LB

④ Because here no physical connection between ~~input~~ output and input.

So if it is said that you have to use to solve the use case using open loop configuration of op-amp. Then it ~~is~~ ~~us~~ should be comparator problem.

So it should think ~~where~~ which voltage should be V_+ and which voltage should be V_- .

Sub.: _____

SAT ☐ SUN ☐ MON ☐ TUE ☐ WED ☐ THU ☐ FRI ☐

DATE: / /




① Pulse generator:



$$V_{I+} = V_+ \quad | \quad V_{I-} = V_-$$

$$V_d = V_+ - V_-$$

$$V_d = V_I$$

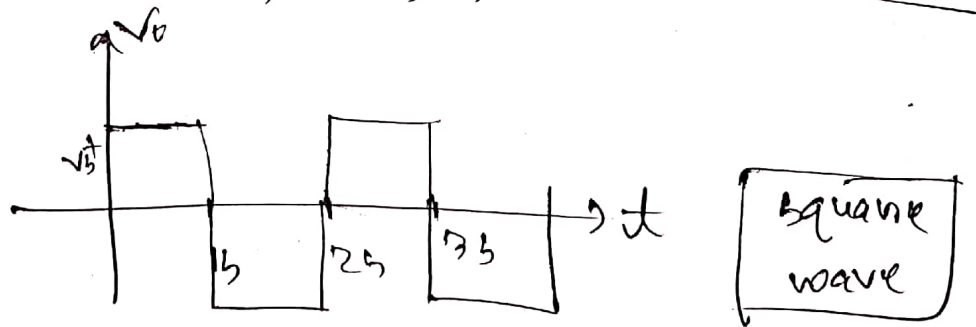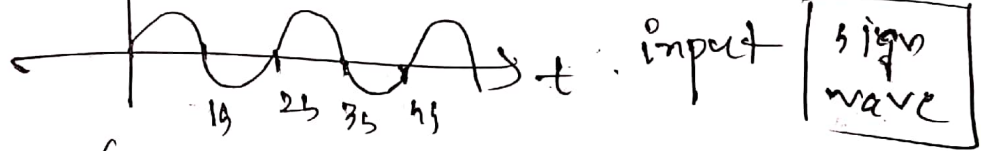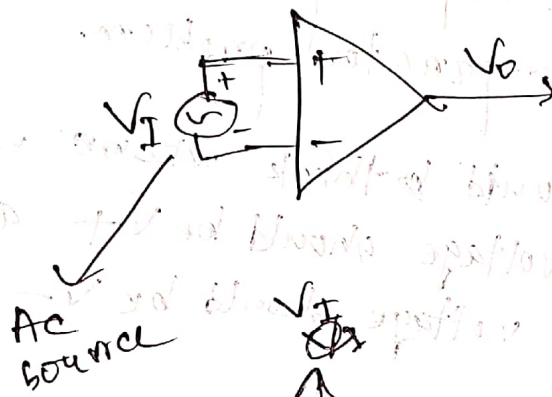


Sub.: _____

SAT ☐ SUN ☐ MON ☐ TUE ☐ WED ☐ THU ☐ FRI ☐


DATE: / /

now if input:

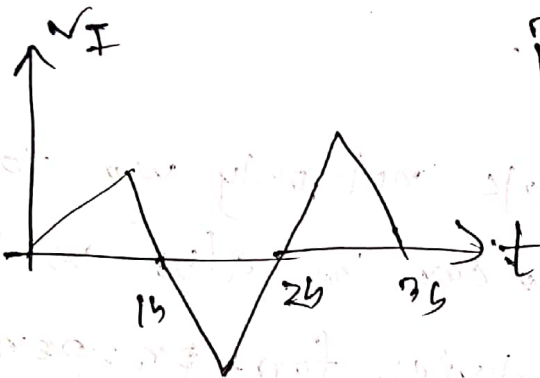

input triangle

output:

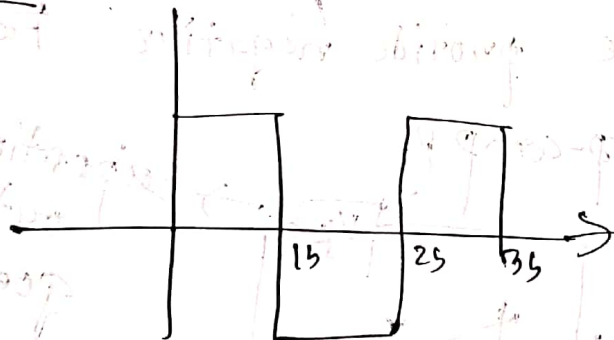

output square wave

Q11: now everything is op-amp's open loop configuration.

[No connection between output and input] Hence output is unstable.
 is because of ~~an~~ ideal op-amp has infinity gain.

Sub.:


Nodal analysis

/ KCL / KVL / on op-amp

DATE: / /




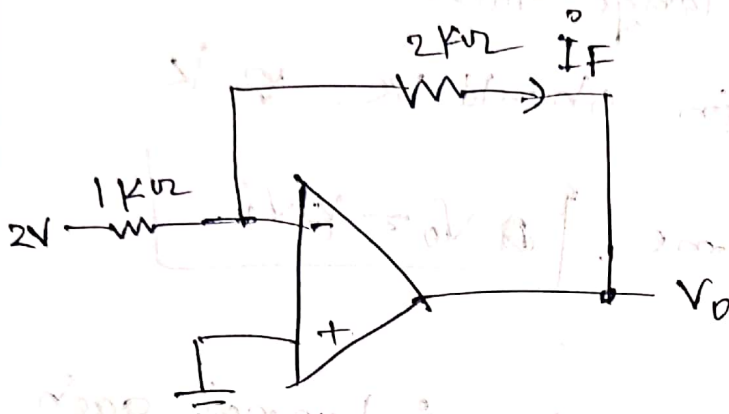SAT ☐ SUN ☐ MON ☐ TUE ☐ WED ☐ THU ☐ FRI ☐



Question find I_F and V_o


Solⁿ: The equivalent circuit:

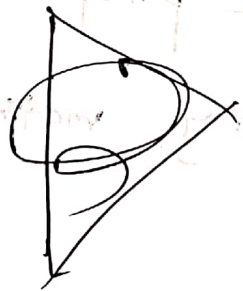

Sub.: _____

SAT ☐ SUN ☐ MON ☐ TUE ☐ WED ☐ THU ☐ FRI ☐

DATE: / /

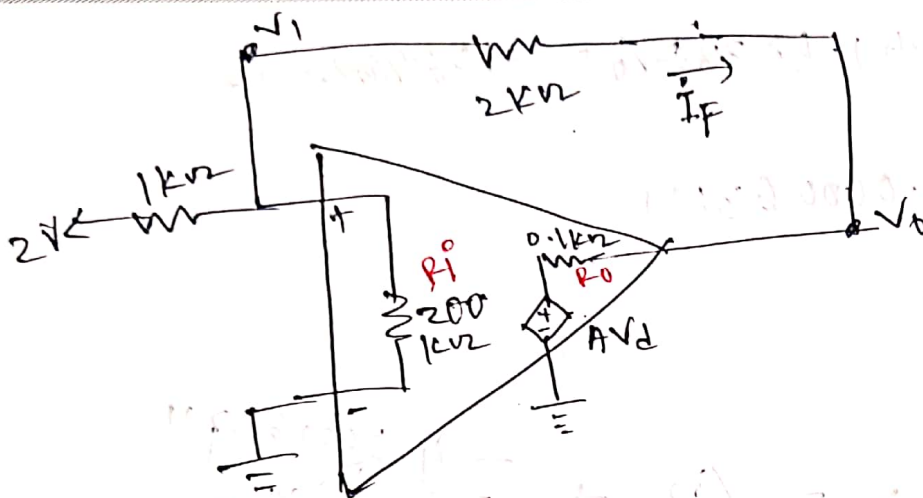

Here,

$$V_d = V_+ - V_-$$

$$= V_1 - 0$$

$$\therefore A V_d = A V_1$$

Using node analysis.

$$V_1 \left(\frac{1}{2} + \frac{1}{200} + \frac{1}{2} \right) - \frac{2}{1} - \frac{V_0}{200} - \frac{V_0}{2} = 0$$

$$\Rightarrow V_1 \times 1.505 - 2 - \frac{V_0}{2} = 0 \quad \text{--- (1)}$$

$$\Rightarrow V_1 = \left(2 + \frac{V_0}{2} \right) \times \frac{1}{1.505}$$

$$V_0 \left(\frac{1}{2} + \frac{1}{0.1} \right) - \frac{V_1}{2} - \frac{A V_d}{0.1} = 0$$

$$\Rightarrow -V_0 \times 10.5 - \frac{V_1}{2} - \frac{2 \times 10^5 V_1}{0.1} = 0$$

$$\Rightarrow 10.5 V_0 - \frac{V_1}{2} - 2 \times 10^6 \times V_1 = 0 \quad \text{--- (2)}$$

$$\Rightarrow 10.5 V_0 - \frac{1}{2} \left(\frac{2}{1.505} + \frac{V_0}{2 \times 1.505} \right) - 2 \times 10^6 \times \left(\frac{2}{1.505} + \frac{V_0}{2 \times 1.505} \right) = 0$$

$$\Rightarrow 10.5 V_0 - \frac{1}{1.505} - \frac{V_0 \times 50.}{301} = 0$$

$$- 265280 \times 309 - 664451.8272 V_0 = 0$$

Sub.: _____

SAT ☐ SUN ☐ MON ☐ TUE ☐ WED ☐ THU ☐ FRI ☐

DATE: / /

$$\Rightarrow -664441 \cdot 4233 \div 6 = 2652802.973$$

$$\Rightarrow V_0 = 4.000063211$$

$$= -4 \text{ V}$$

$$\text{Now, } V_1 = \left(2 + \frac{-4.000063211}{2} \right) \times \frac{1}{1.505}$$

$$= -6.2545 \times 10^{-8} \text{ V}$$

$$\approx 0$$

$$\therefore A \quad 2 \times I_F = 4 \text{ V}$$

$$\Rightarrow 2 I_F = V_1 - V_0$$

$$\Rightarrow 2 I_F = 0 - (-4)$$


$$\Rightarrow 2 I_F = 4$$

$$\therefore I_F = 2 \text{ mA (Ans)}$$

Sub: _____

SAT	SUN	MON	TUE	WED	THU	FRI
<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>

DATE: / /

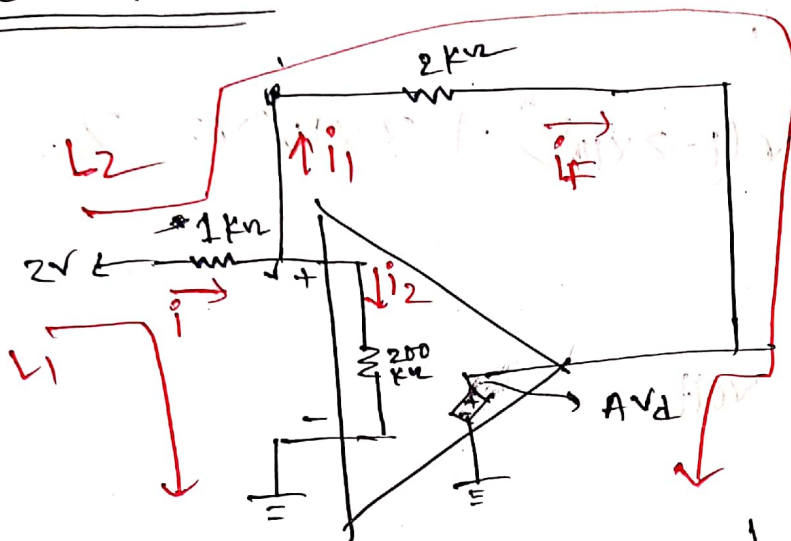KCL KVLKCL

$$i = i_1 + i_2$$

$$= i_2 + i_F$$

KVL along L1:

$$i + 200i_2 = 2 - 0$$

$$\Rightarrow 2 = i + 200i_2 \quad \text{--- (1)}$$

KVL along L2:

$$i + 2i_F + AV_d = 2 - 0$$

$$\Rightarrow i + 2i_F + 2 \times 10^5 V_d = 2 \quad \text{--- (2)}$$

Ohm's law
~~Now find~~

Ohm's law

$$V - 0 = i_2 \times 200$$

$$\Rightarrow V = 200 \times i_2$$

Again

$$V - AV_d = 2i_F$$

$$\Rightarrow V(1 - 2 \times 10^5) = 2i_F$$

$$\Rightarrow i_F = \frac{V(1 - 2 \times 10^5)}{2}$$

\therefore From (1)

$$2 = i + 2i_F$$

$$i = 2 - 200i_2$$

$$= 2 - 200 \times \frac{V}{200}$$

$$= 2 - V$$

Sub.: _____

SAT ☐ SUN ☐ MON ☐ TUE ☐ WED ☐ THU ☐ FRI ☐

DATE: / /

Now from (2),

$$2-V + 2 \times 10^5 V (1 - 2 \times 10^5) + 2 \times 10^5 V = 2$$

⇒ ~~OR~~

$$2) V = 0 \text{ Volt}$$