

CSE251: Electronic Devices and Circuits

Lecture 5:
Closed Loop Op-amp configurations

Prepared By:
Shadman Shahid (SHD)
Lecturer, Department of Computer Science and Engineering, School of Data and Sciences, BRAC University


Email: shadman9085@gmail.com

Outline

- **Closed Loop Operational Amplifier: Introduction**
 - Open Loop VS Closed Loop Gain
 - Closed Loop Configuration: Negative Feedback
 - Solving Closed Loop Circuit

Open Loop Gain VS Closed Loop Gain

Open Loop (OL) Configuration

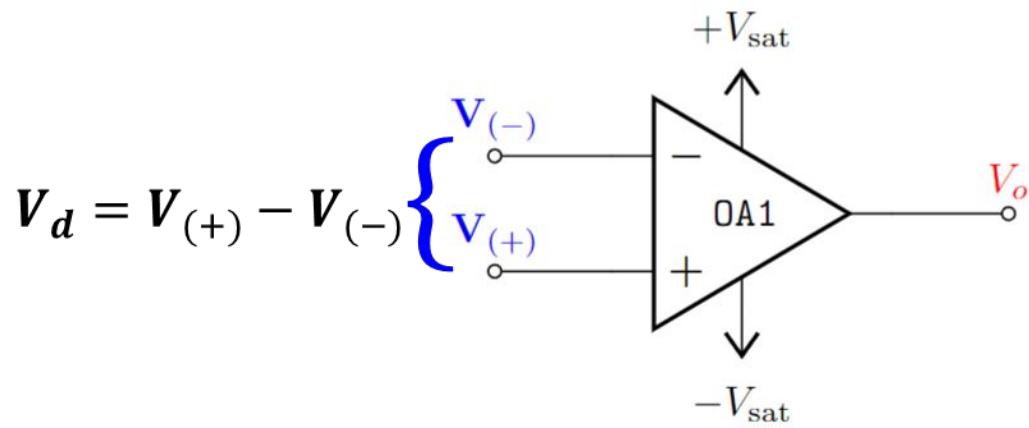


Input Voltage: V_d
Output Voltage: V_o

$$\therefore \text{Voltage Gain: } \frac{V_o}{V_d} = A \text{ or } K$$

OL Gain	CL Gain

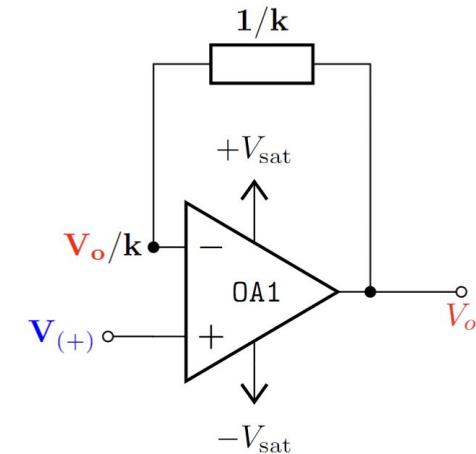With “Negative Feedback”: Closed Loop (CL) Configuration




Input Voltage: $V_{(+)}$
Output Voltage: V_o


$$\therefore \text{Voltage Gain: } \frac{V_o}{V_{(+)}} = k$$

Open Loop Gain VS Closed Loop Gain

Open Loop (OL) Configuration

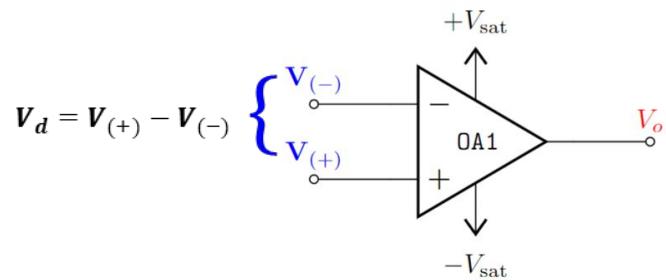

Closed Loop (CL) Configuration

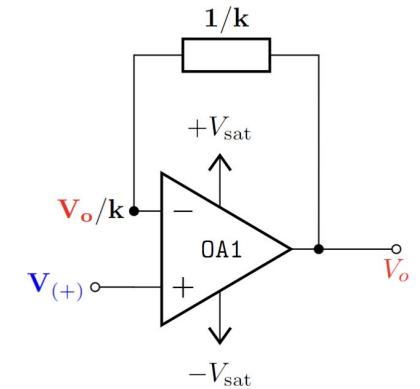


OL Gain	CL Gain
Can't be controlled	Can be controlled by the feedback element
<i>Used as “Comparator”</i>	<i>Used as “Linear Amplifier”</i>

Negative Feedback in Op-Amp circuit

The **output voltage** is transformed in the following way:


$$V_{(-)} = \frac{1}{k} \cdot V_O$$

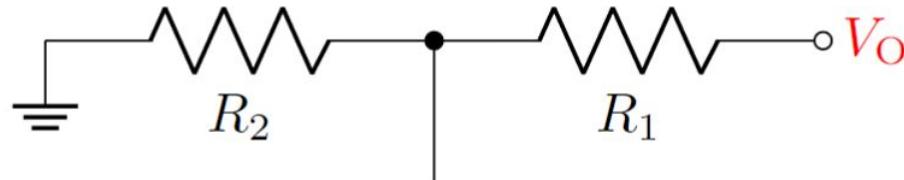This factor of **1/k** can be achieved with a voltage divider network.



$$\underline{V_{(-)}} = \frac{R_2}{R_2 + R_1} \cdot V_O$$

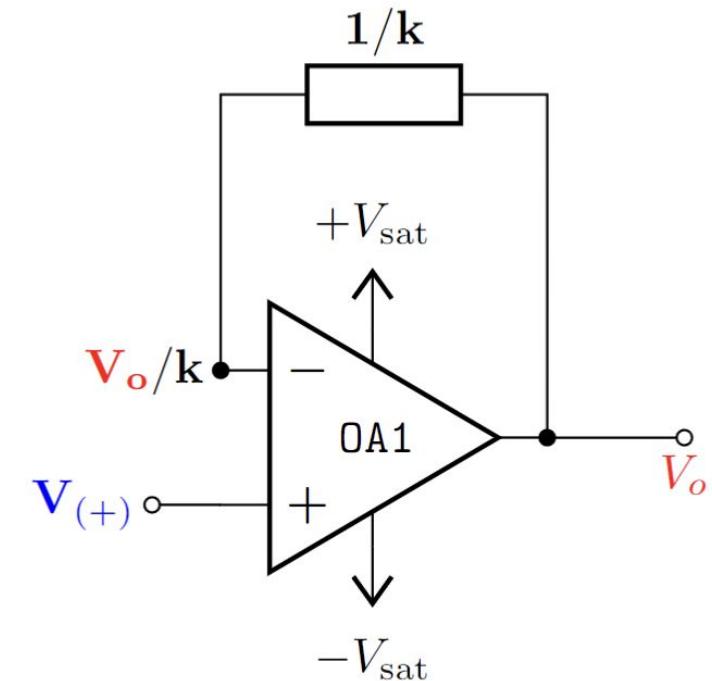
$$\boxed{\frac{1}{k} = \frac{R_2}{R_1 + R_2}}$$



A voltage divider can act as a multiplier/factor in the **feedback branch**

Negative Feedback in Op-Amp circuit

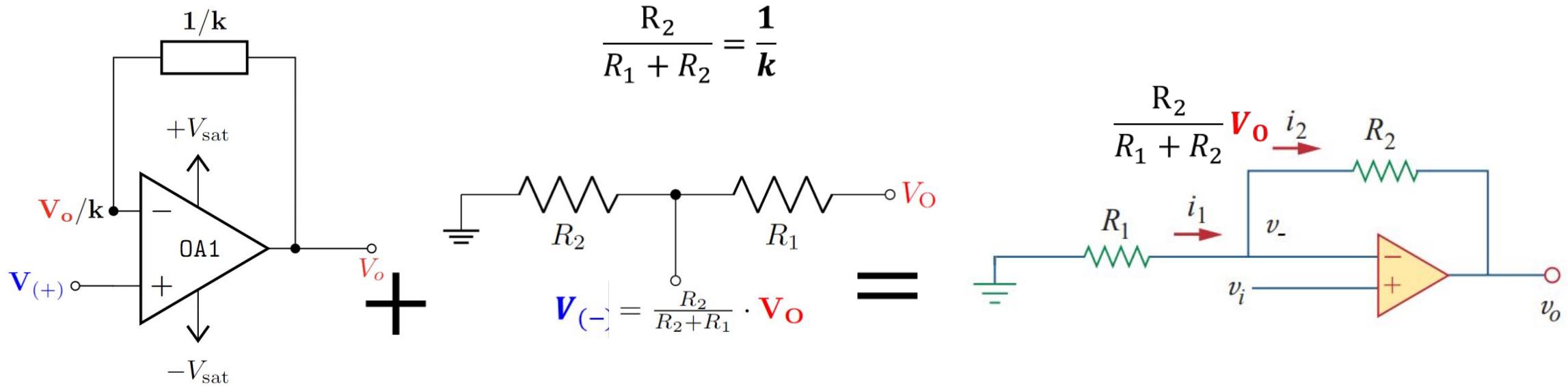A voltage divider can act as a multiplier/factor in the **feedback** branch



If $k = 10$ (meaning we feed back one tenth of the output to negative input), we will get $v_o = 10 * v_i$. that is 10-fold gain.

Solving Closed Loop Op-Amp Circuit

- For “ideal” op-amp


- Infinite input resistance, $R_i = \infty$ = open circuit
- Zero output resistance, $R_o = 0$ = short circuit
- $i_i = 0$ and $i_+ = 0$

- When there is negative feedback,



- In an ideal op-amp, “ A ” (or K) is infinitely high. Thus, for a finite output voltage v_o :

$$\frac{v_o}{A} = v_d \rightarrow 0 \Rightarrow v_+ = v_-.$$

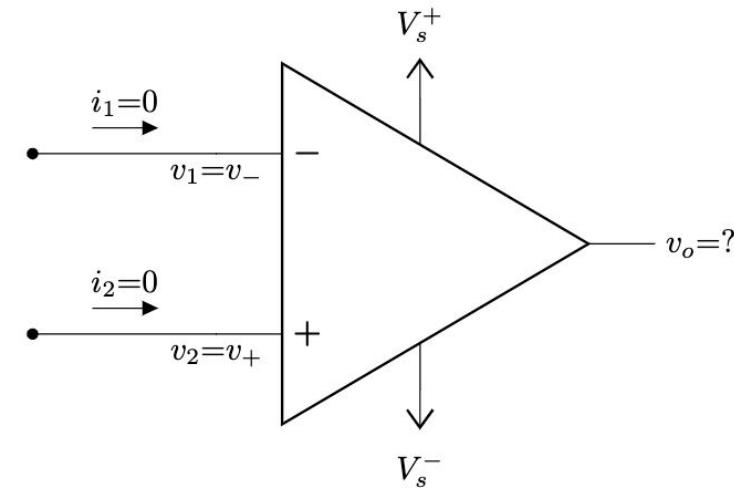- This is called **virtual short circuit**



Solving Closed Loop Op-Amp Circuit

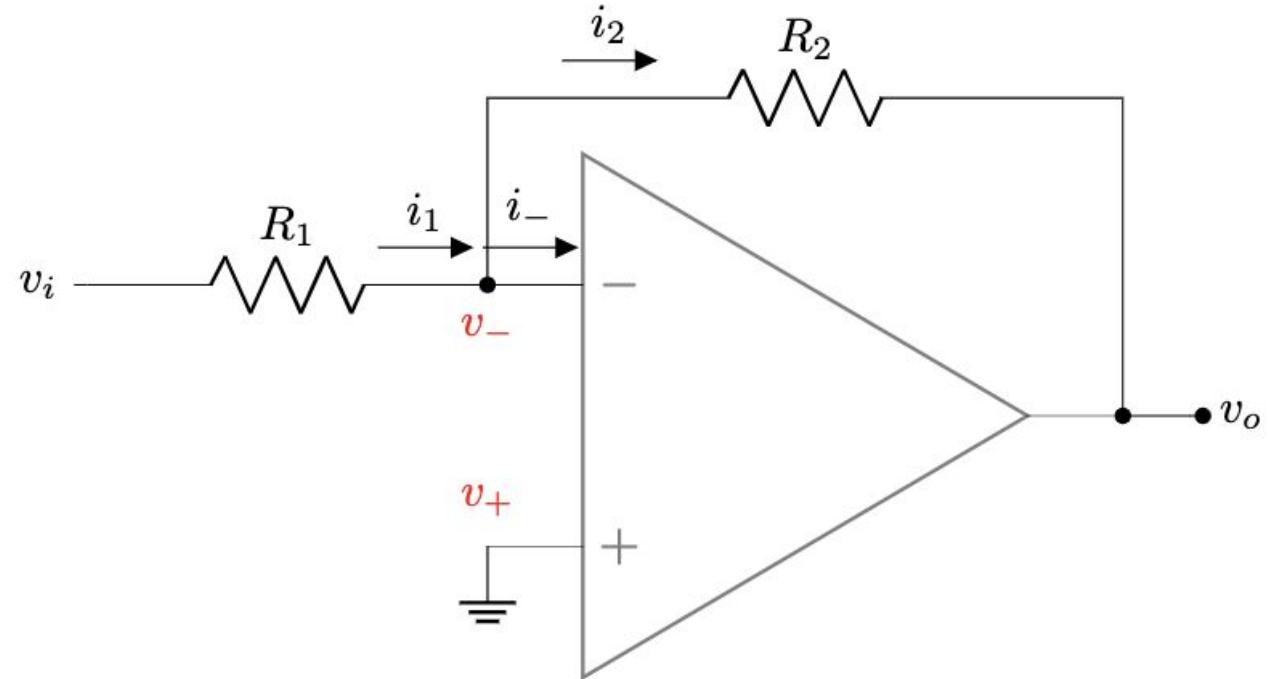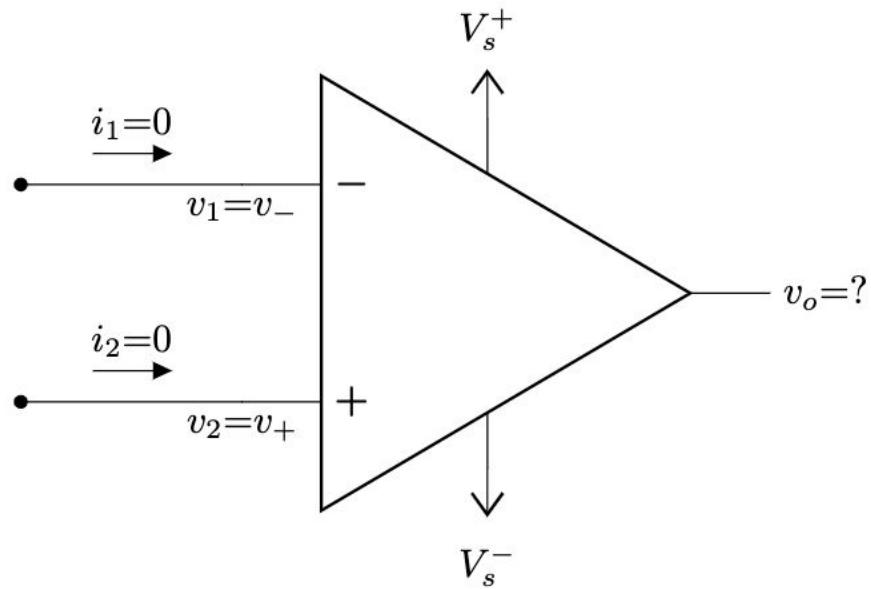


Two Rules:

1. Virtual Shorting:
2. Zero input bias current:

$$v_+ = v_-$$

$$i_- = i_+ = 0$$

Solving Closed Loop Op-Amp Circuit

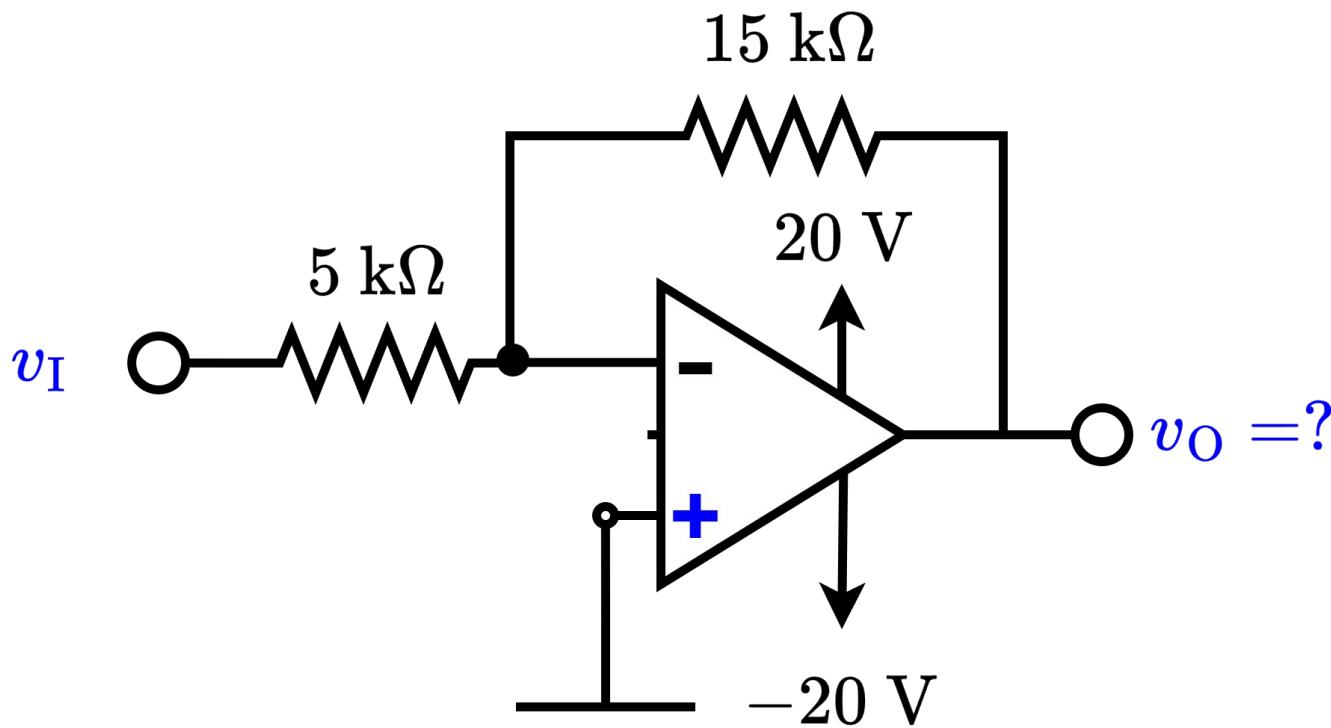

Solving Closed Loop Op-Amp Circuit

1. Since v_+ is connected to ground,

$$v_+ = 0 \text{ V}$$

2. Since there is negative feedback,
from virtual short,


$$v_- = v_+ = 0 \text{ V}$$

3. Ohm's law for $5 \text{ k}\Omega$:

$$I_{\text{in}} = \frac{v_I - 0}{5} = \frac{v_I}{5}$$

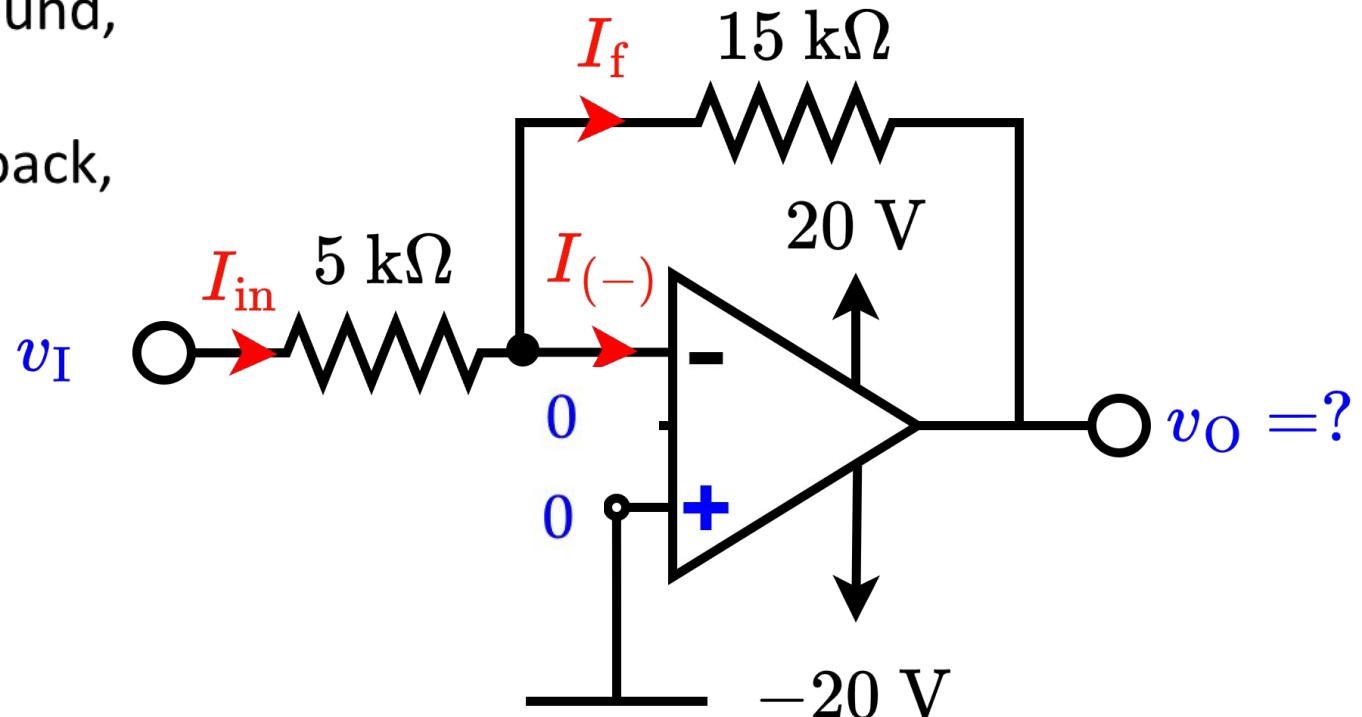4. Ohm's law for $15 \text{ k}\Omega$:

$$I_f = \frac{0 - v_O}{15} = -\frac{v_O}{15}$$



Solving Closed Loop Op-Amp Circuit

3. Ohm's law for $5 \text{ k}\Omega$:

$$I_{\text{in}} = \frac{v_I - 0}{5} = \frac{v_I}{5}$$

4. Ohm's law for $15 \text{ k}\Omega$:

$$I_f = \frac{0 - v_O}{15} = -\frac{v_O}{15}$$


5. For “ideal” op-amp,

$$I_{(-)} = I_{(+)} = 0$$

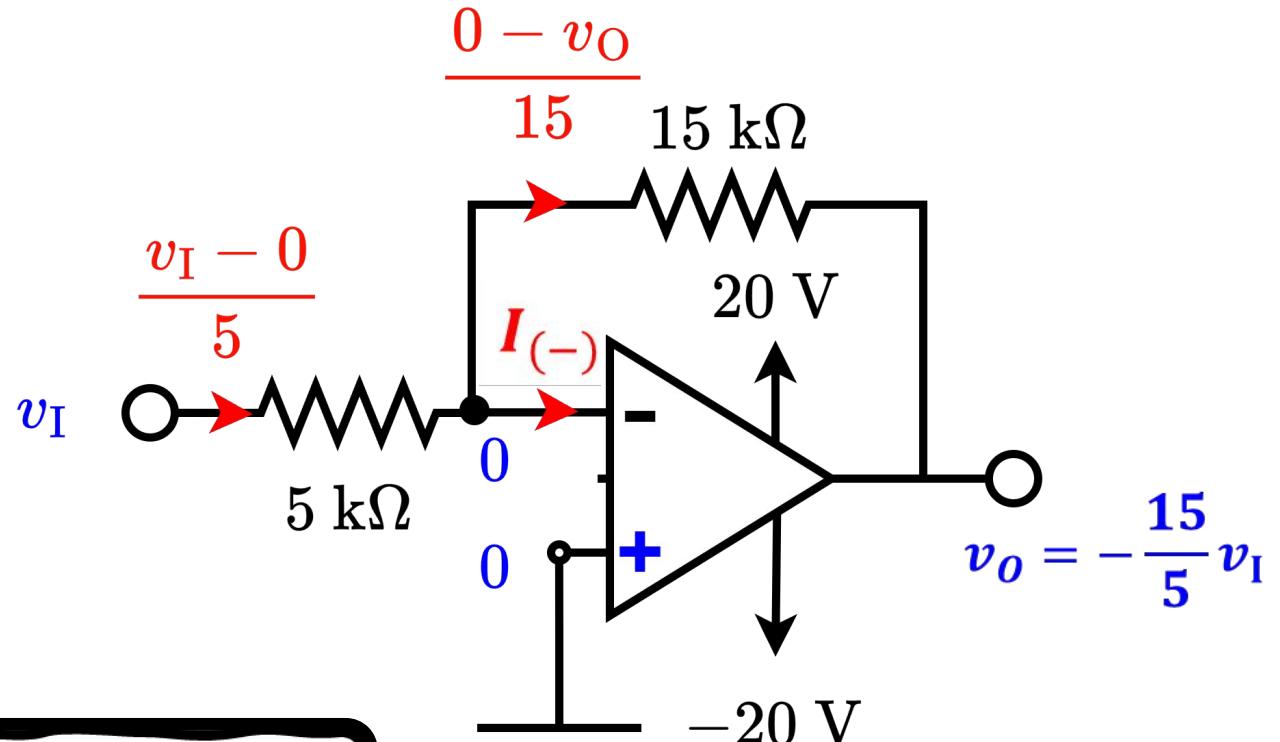6. So, $I_{\text{in}} = I_f$

$$-\frac{v_O}{15} = \frac{v_I}{5}$$

$$\Rightarrow \frac{v_O}{v_I} = -\frac{15}{5}$$



Solving Closed Loop Op-Amp Circuit

3. Ohm's law for $5 \text{ k}\Omega$:

$$I_{\text{in}} = \frac{v_I - 0}{R_I} = \frac{v_I}{R_I}$$

4. Ohm's law for $15 \text{ k}\Omega$:

$$I_f = \frac{0 - v_O}{R_f} = -\frac{v_O}{R_f}$$


5. For “ideal” op-amp,

$$I_{(-)} = I_{(+)} = 0$$

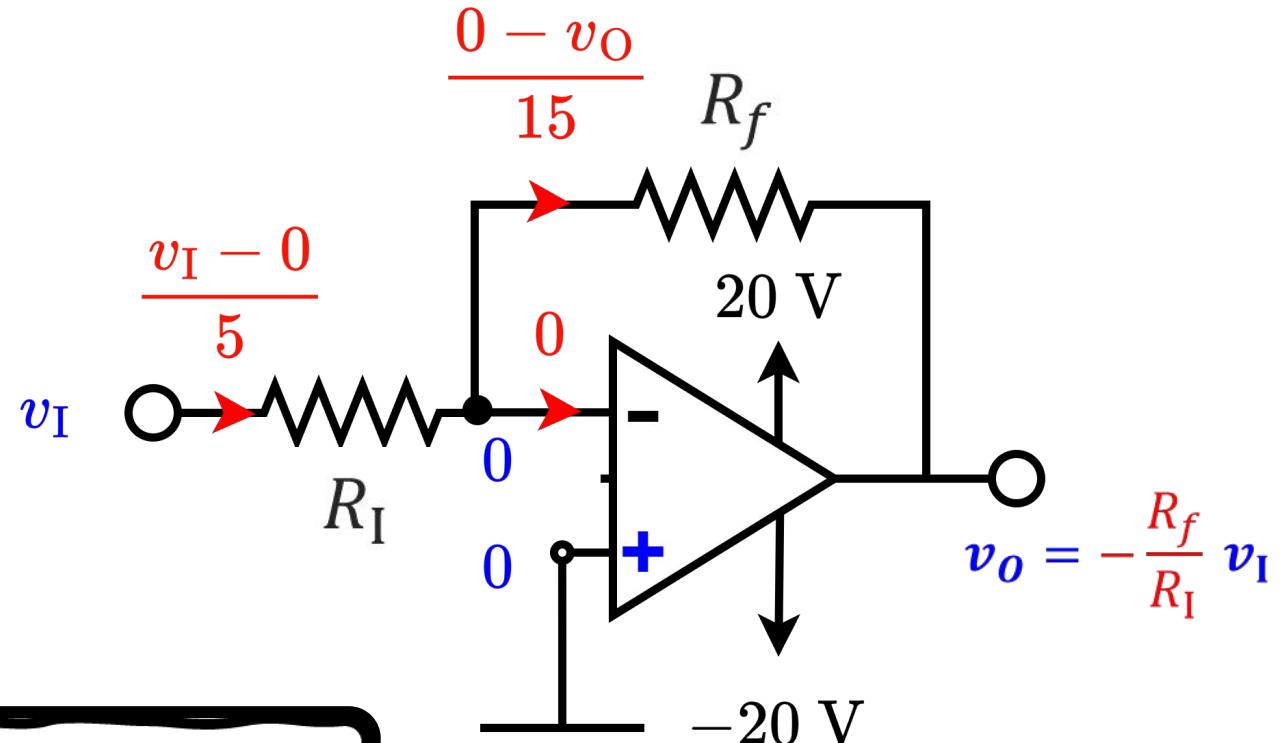6. So, $I_{\text{in}} = I_f$

$$-\frac{v_O}{R_f} = \frac{v_I}{R_I}$$

$$\Rightarrow \frac{v_O}{v_I} = -\frac{R_f}{R_I}$$



Solving Closed Loop Op-Amp Circuit

7. Check whether the amplified voltage exceeds **saturation limit**.

$$-\frac{R_f}{R_I} v_I = -\frac{15}{5} v_I = -3v_I$$

If $v_I = 3 \text{ V}$:


$$-3v_I = -3 \times 3 > -20 \text{ V}$$

$$\therefore v_O = -9 \text{ V}$$

If $|v_I| > 6.67 \text{ V}$:

Op-amp goes into saturation as $-3v_I = -3 \times 6.67 < -20$

$$\therefore v_O = -20 \text{ V}$$

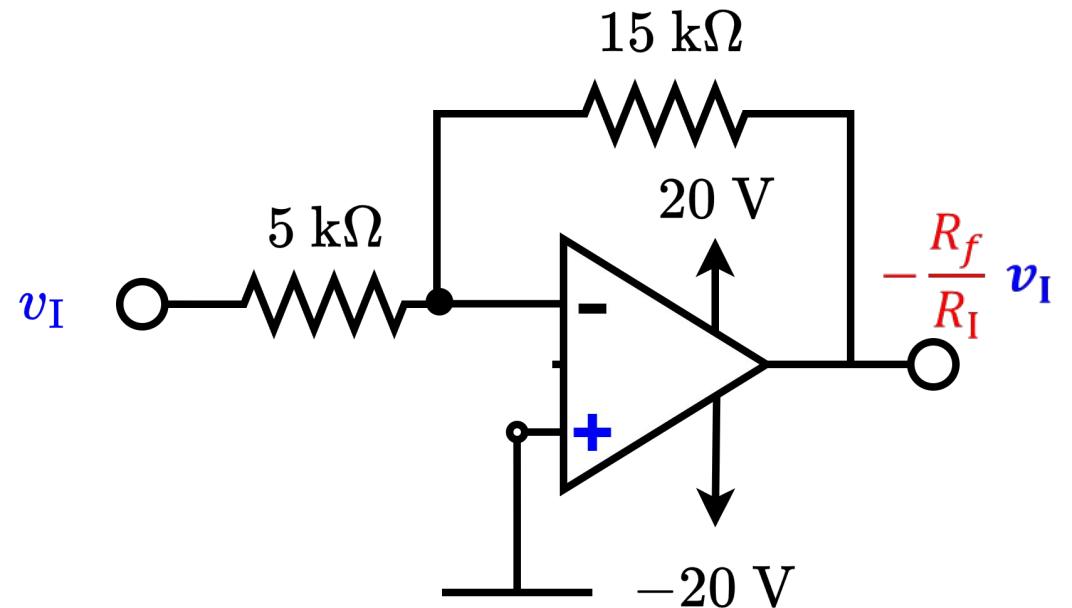

Part 1 ends here


Outline

- **Closed Loop Operational Amplifier: Configurations**
 - Basic Op-Amp Configurations: OL vs CL
 - Closed Loop Configurations: Formulas and Examples

Basic Op-Amp Configurations

- **Open-loop Configurations**

1. Comparator / Voltage Level Detectors

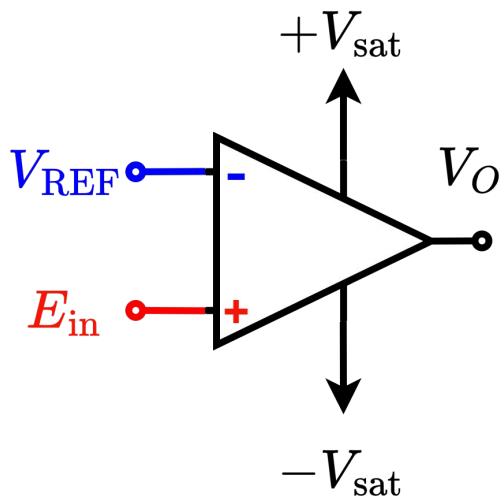


- **Closed Loop Configurations**

1. Voltage Follower
2. Inverting Amplifier
3. Inverting Summer
4. Non-Inverting Amplifier
5. Weighted Subtractor
6. Inverting Integrator
7. Inverting Differentiator
8. Exponential Converter
9. Logarithmic Converter
10. Multiplier
11. Divider

Basic Op-Amp Configurations

- **Open-loop Configurations**


1. Comparator / Voltage Level Detectors

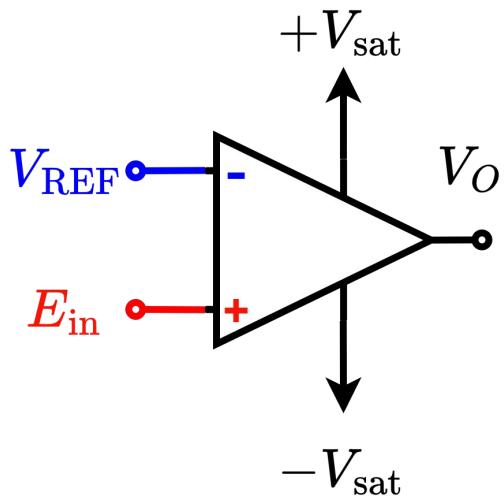

- **Closed Loop Configurations**

1. Voltage Follower
2. Inverting Amplifier
3. Inverting Summer
4. Non-Inverting Amplifier
5. Weighted Subtractor
6. Integrator
7. Differentiator
8. Exponential Converter
9. Logarithmic Converter
10. Multiplier
11. Divider


Voltage Follower / Buffer:

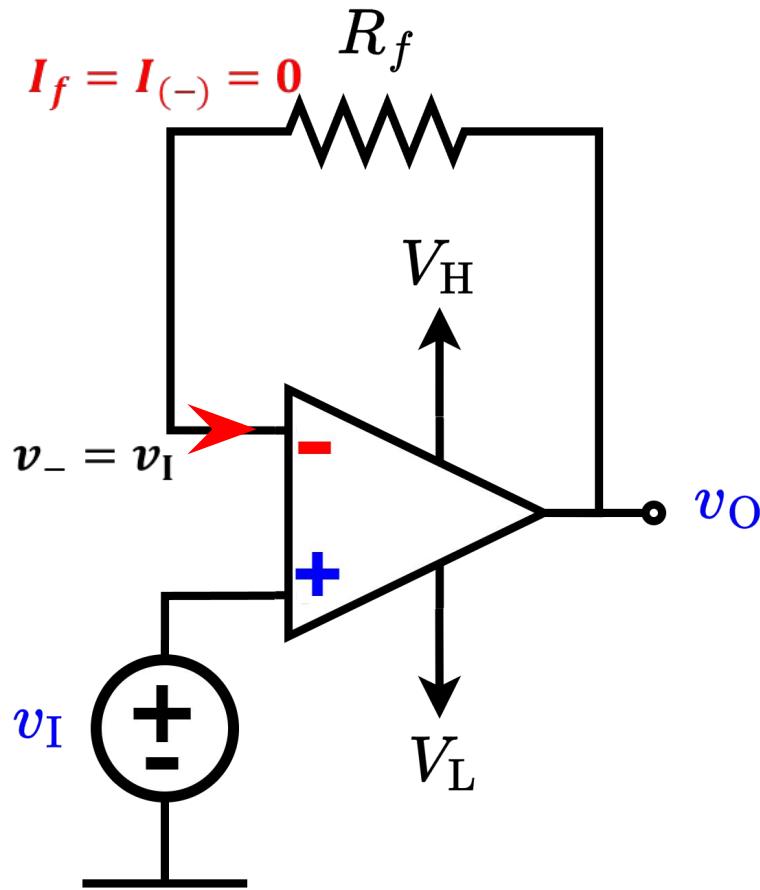

$$v_O = v_I$$

Regardless of the value of R_f

Inverting Amplifier

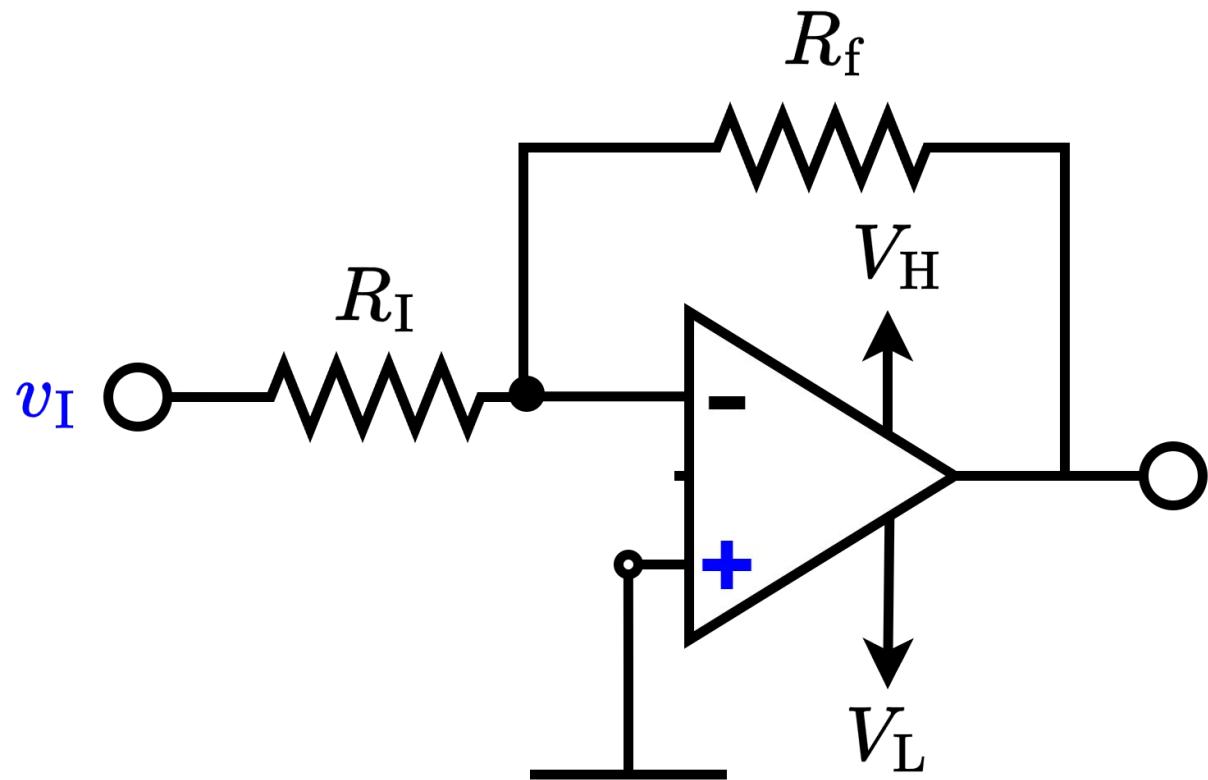


$$v_O = \begin{cases} V_H, & \text{if } v_O \geq V_H \\ -v_I \cdot \frac{R_f}{R_i}, & \text{if } V_L \leq v_O \leq V_H \\ V_L, & \text{if } v_O \leq V_L \end{cases}$$

Example - 1

If $v_i = 0.5$ V, calculate:

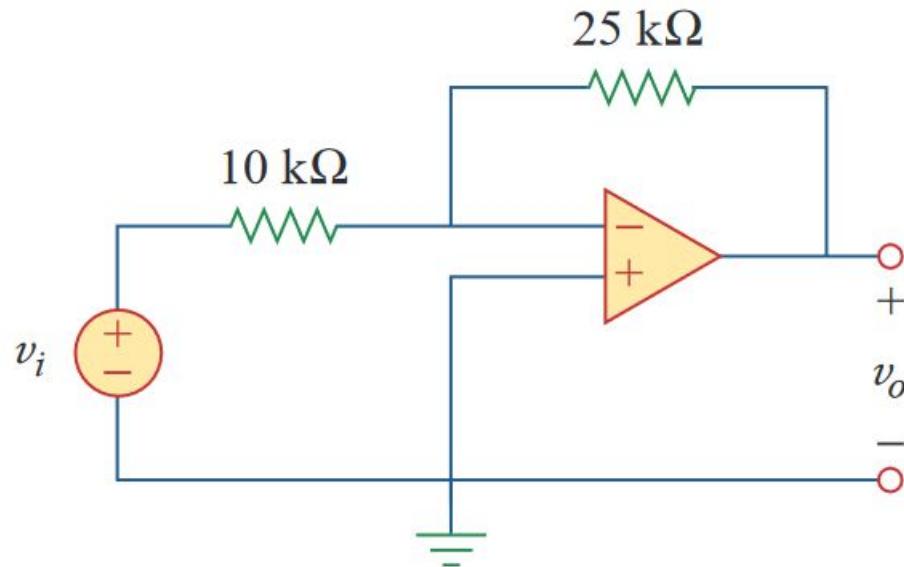- (a) Output voltage v_o .
- (b) Current in the **10 k Ω** resistor.



(a)


$$v_o = -\frac{R_f}{R_i} \cdot v_i = -2.5v_i = -1.25 \text{ V}$$

(b) Current through the **10 k Ω** resistor is

$$i = \frac{v_i}{R_i} = \frac{0.5}{10} \text{ mA} = 50 \mu\text{A}$$

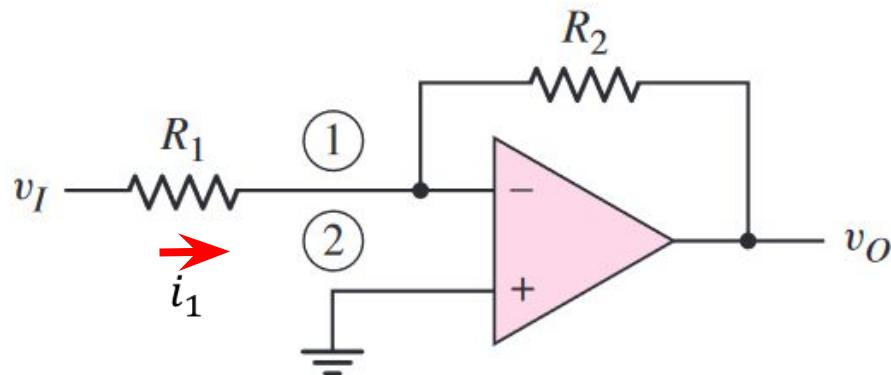Example - 2

Design the circuit such that the closed loop voltage gain is $A_{CL} = -5$. Assume the op-amp is driven by an ideal sinusoidal source, $v_I = 0.1 \sin(\omega t) (V)$, that can supply a maximum current of $5 \mu\text{A}$.





$$i_1 = \frac{v_I}{R_1}$$

$$R_1 = \frac{v_I(\max)}{i_1(\max)} = \frac{0.1}{5 \times 10^{-3}} = 20 \text{ k}\Omega$$

$$R_2 = -A_{CL} \cdot R_1 = 5 \times 20 = 100 \text{ k}\Omega$$

Inverting Summer

- Multichannel Amplifier

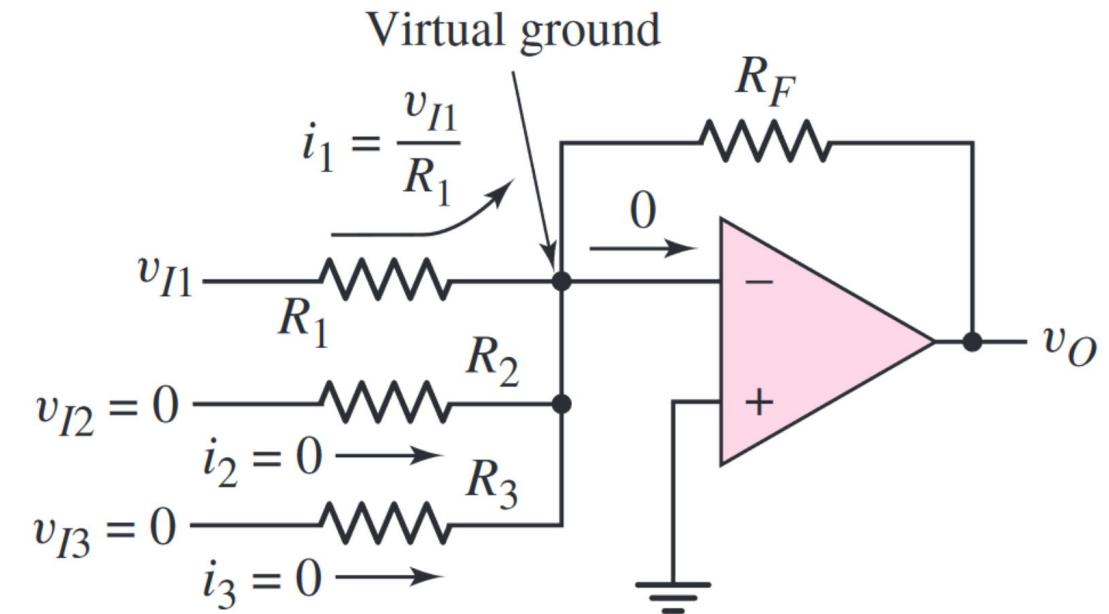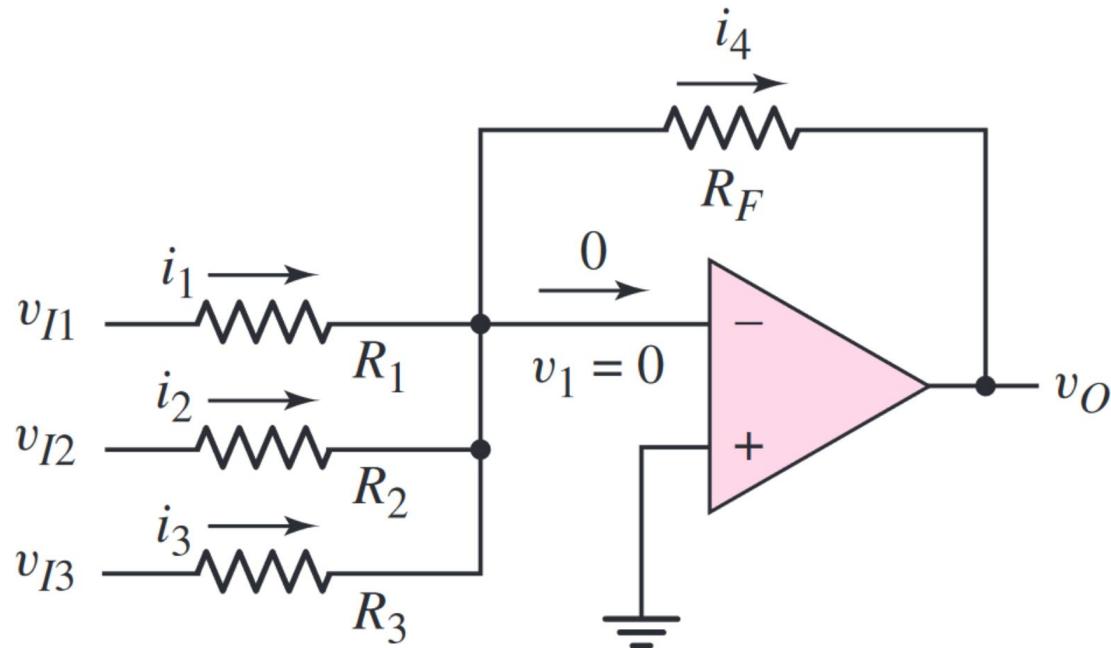


$$v_O(v_{I1}) = -i_1 R_F = -\left(\frac{R_F}{R_1}\right) v_{I1}$$

$$v_O = -\left(\frac{R_F}{R_1}v_{I1} + \frac{R_F}{R_2}v_{I2} + \frac{R_F}{R_3}v_{I3}\right)$$

Example - 3

Calculate:

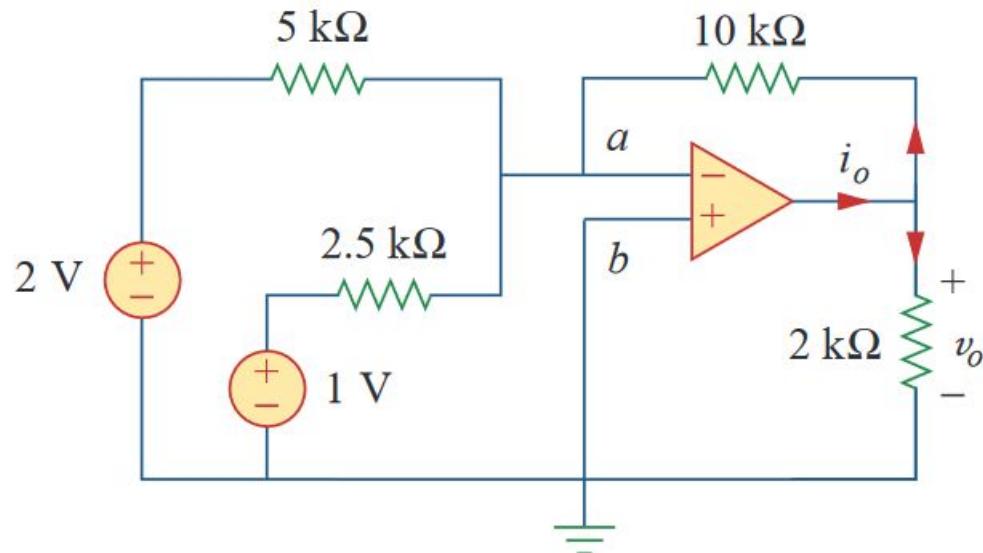- (a) Output voltage v_o .
- (b) Output current i_o .



(a)

$$v_o = -\left(\frac{10}{5} \cdot 2 + \frac{10}{2.5} \cdot 1\right) = -8 \text{ V}$$

(b)


$$i = \frac{v_o}{10} + \frac{v_o}{2} = (-0.8 - 4) \text{ mA} = -4.8 \text{ mA}$$

Part 2 ends here

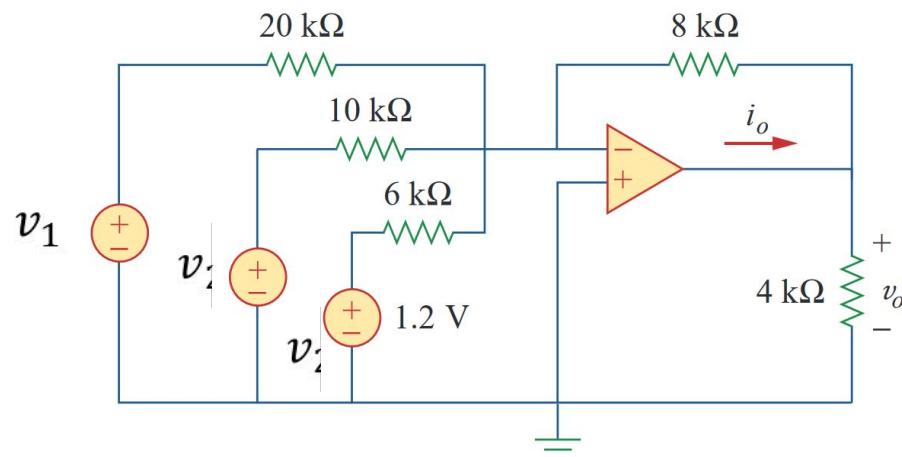Example 4

Design an op-amp circuit with inputs v_1 , v_2 and v_3 such that, output voltage v_o :

$$v_o = -\frac{2}{5}v_1 - \frac{4}{5}v_2 - \frac{4}{3}v_3$$



Solution:

The given function can be achieved by an **inverting summing amplifier**. Having the voltage transfer formula as:

$$v_o = \left(-\frac{R_f}{R_1} v_1 - \frac{R_f}{R_2} v_2 - \dots - \frac{R_f}{R_n} v_n \right)$$

Here, the numerators of all the coefficients of input voltages are same (R_f). As per the given problem, this can be achieved by setting the numerator to the LCM of 2 and 4 (i.e., to 8).

$$\begin{aligned} v_o &= -\frac{2}{5}v_1 - \frac{4}{5}v_2 - \frac{4}{3}v_3 \\ &= -\frac{8}{20}v_1 - \frac{8}{10}v_2 - \frac{8}{6}v_3 \end{aligned}$$

Example 4

Design an op-amp circuit with inputs v_1 , v_2 and v_3 such that, output voltage v_o :


$$v_o = -\frac{2}{5}v_1 - \frac{4}{5}v_2 - \frac{4}{3}v_3$$

Easier Solution:

$$v_o = -\frac{2}{5}v_1 - \frac{4}{5}v_2 - \frac{4}{3}v_3$$

$$= -\frac{8}{20}v_1 - \frac{8}{10}v_2 - \frac{8}{6}v_3$$

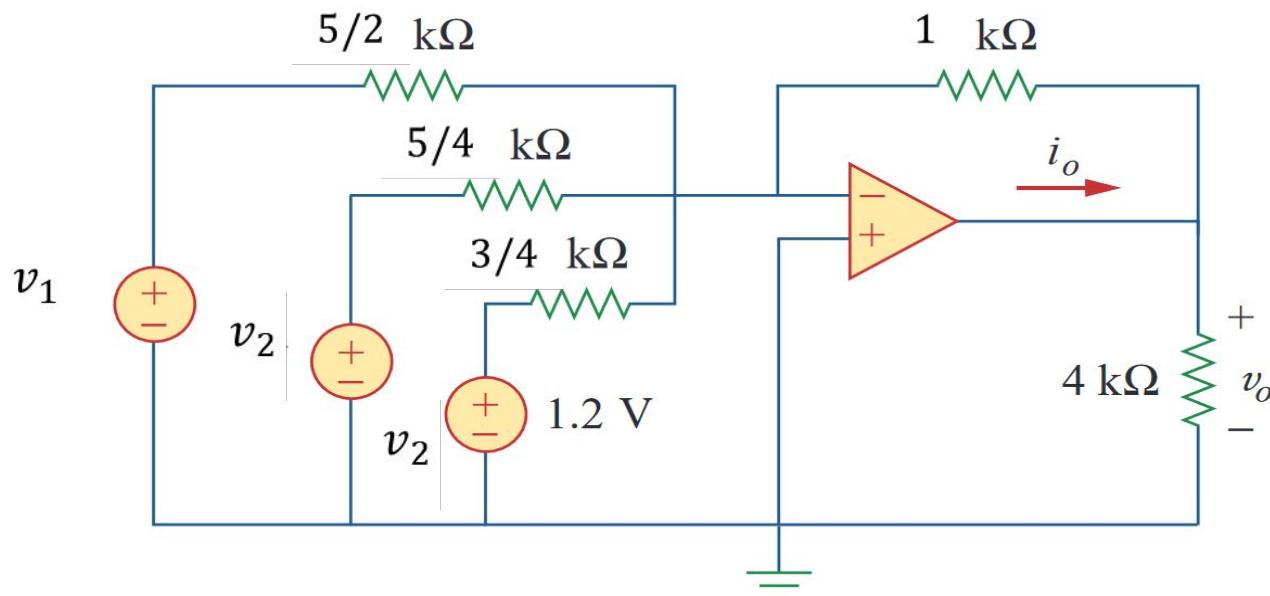
$$= -\frac{1}{5/2}v_1 - \frac{1}{5/4}v_2 - \frac{1}{3/4}v_3$$



Example - 5

$v_I = 0.5 \text{ V}$. Calculate:

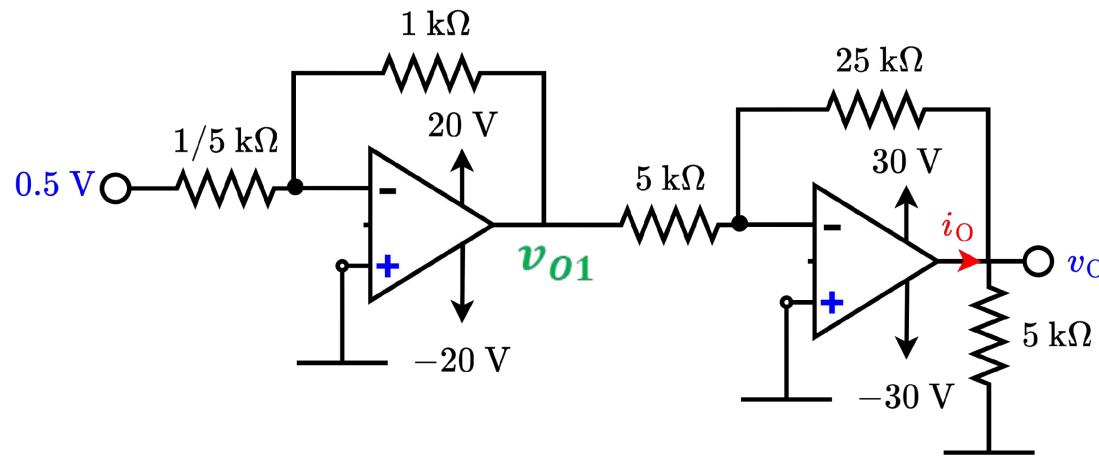- (a) Output voltage v_o .
- (b) Output current i_o .



(a)

$$v_{o1} = -\frac{1}{1/5} \times 0.5 \text{ V} = -2.5 \text{ V}$$

$$v_o = -\frac{25}{5} \cdot v_{o1} = 12.5 \text{ V}$$

$$v_o = \left(-\frac{1}{1/5}\right) \cdot \left(-\frac{25}{5}\right) \cdot 0.5 = 12.5 \text{ V}$$

(b)


$$i = \frac{v_o}{5} + \frac{v_o}{25} = (2.5 + 0.5) \text{ mA} = 3 \text{ mA}$$

Example - 6


Calculate:

- (a) Voltages v_{o1} and v_o .
- (b) Output current i_o .

$$v_I = 0.5 \sin(120\pi t)$$

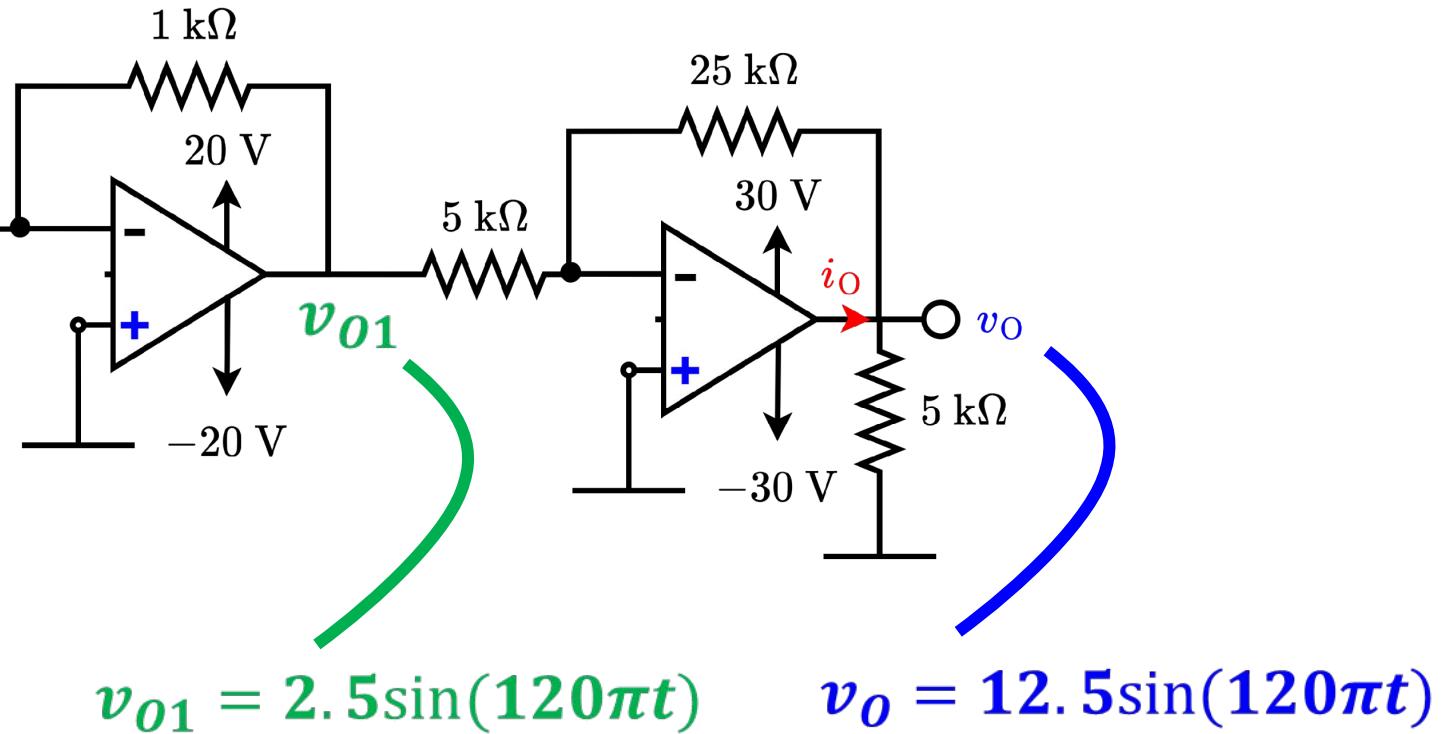

Non-Inverting Amplifier

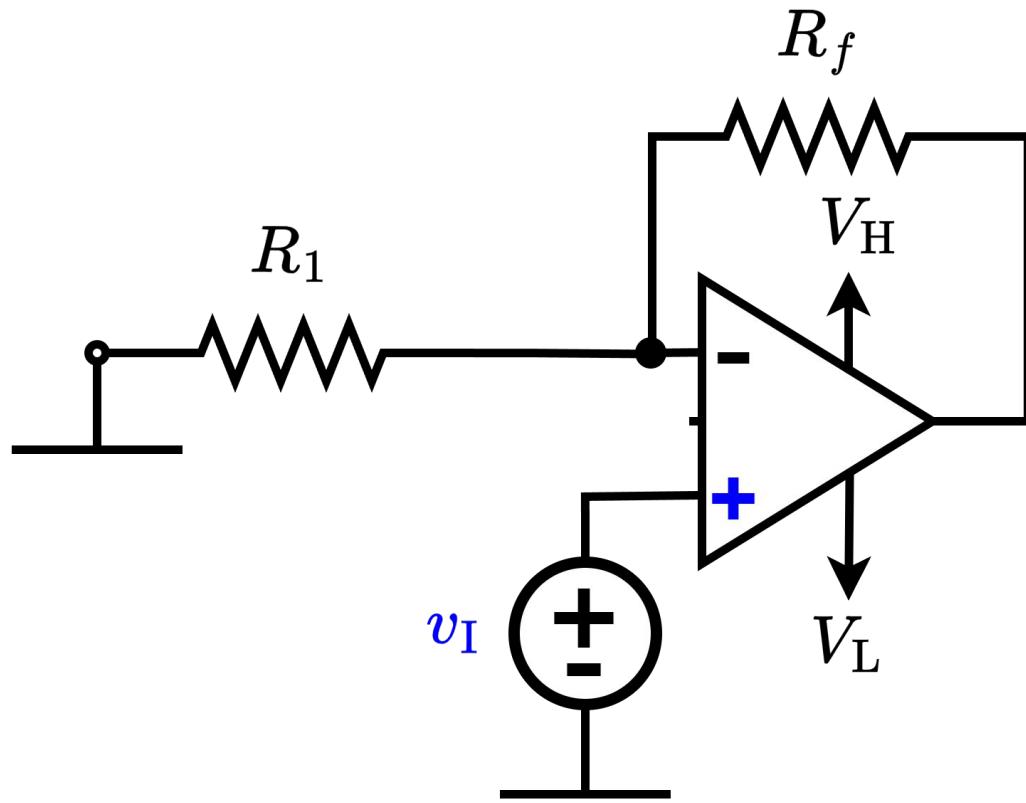


$$v_O = \begin{cases} V_H, & \text{if } v_O \geq V_H \\ v_I \cdot \left(1 + \frac{R_f}{R_I}\right), & \text{if } V_L \leq v_O \leq V_H \\ V_L, & \text{if } v_O \leq V_L \end{cases}$$

$$\mathbf{v}_O > \mathbf{v}_I$$

Non-Inverting Amplifier: Example 7

Calculate:

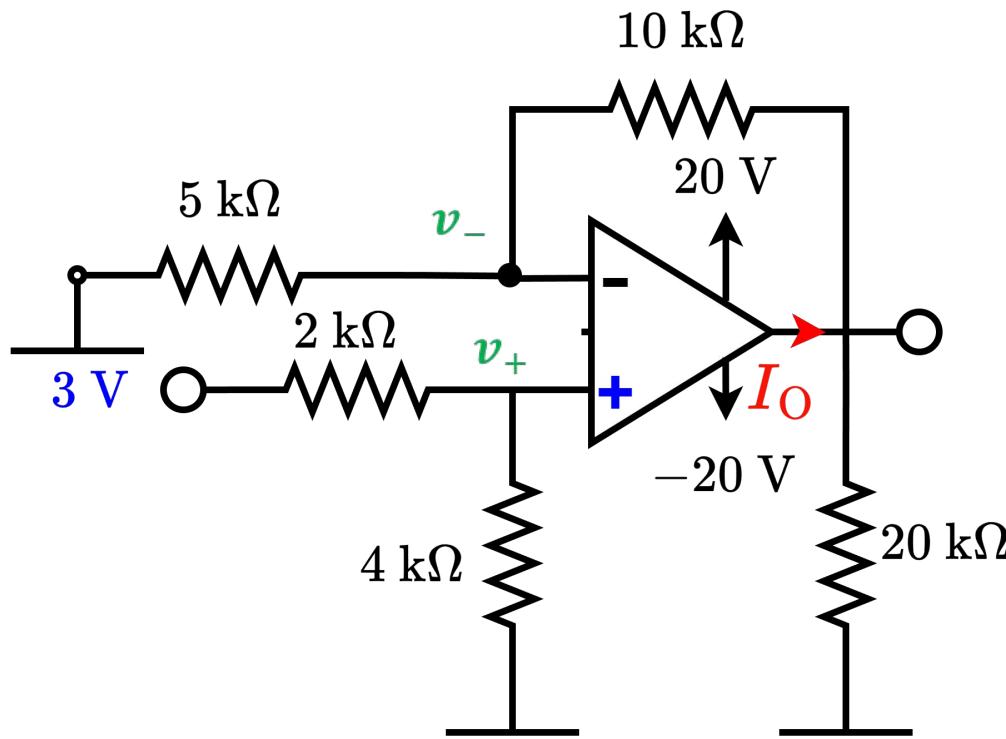- (a) Output voltage v_o .
- (b) Output current I_o .



(a)



$$v_+ = \frac{4}{2+4} \times 3\text{ V} = 2\text{ V}$$

$$v_o = \left(1 + \frac{10}{5}\right) \cdot v_+ = 6\text{ V}$$



(b)

$$i = \frac{v_o}{20} + \frac{v_o}{10} = (0.3 + 0.6) \text{ mA} = 0.9 \text{ mA}$$



Summary so far

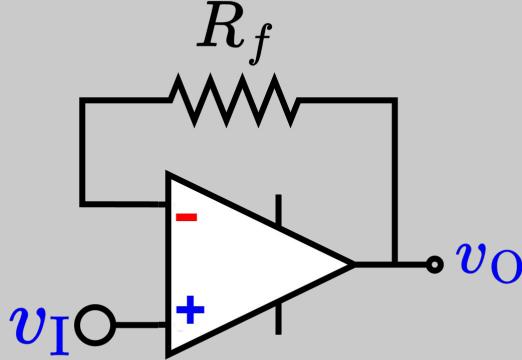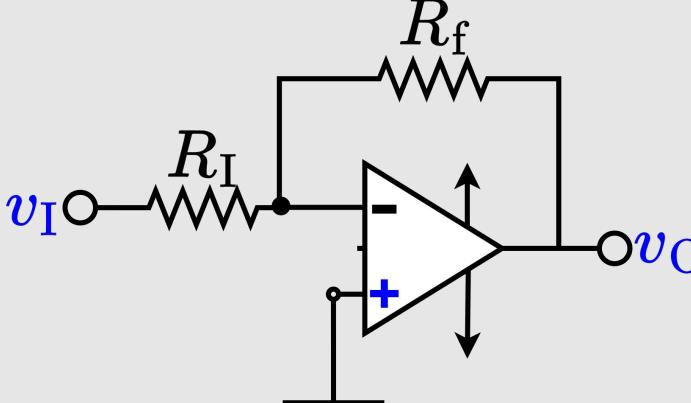Configuration	Circuit diagram	Amplification Formula
Voltage Follower		
Inverting Amplifier		

Summary so far

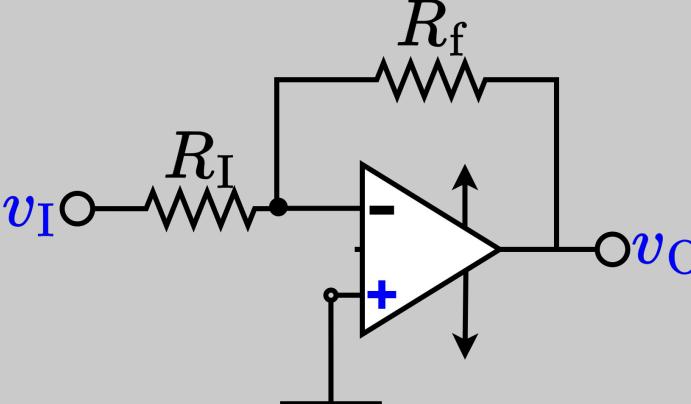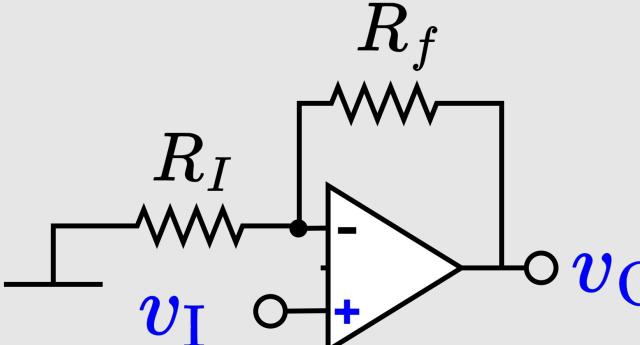
Configuration	Circuit diagram	Amplification Formula
Inverting Amplifier		
Non-Inverting Amplifier		

Summary so far

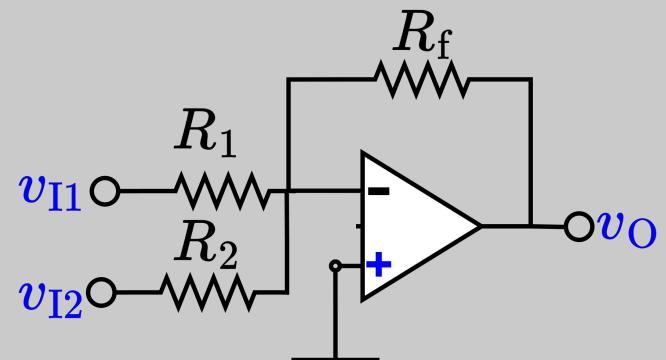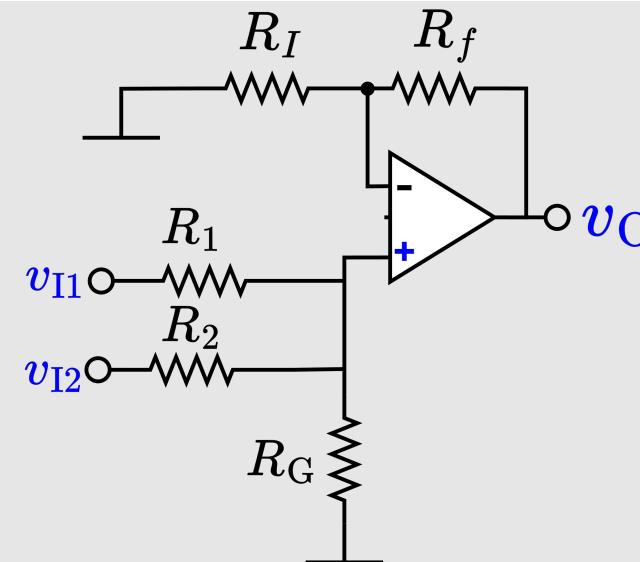
Configuration	Circuit diagram	Formula
Inverting Amplifier Adder		
Non-Inverting Amplifier Adder		

Part 3 ends here

Difference Amplifier

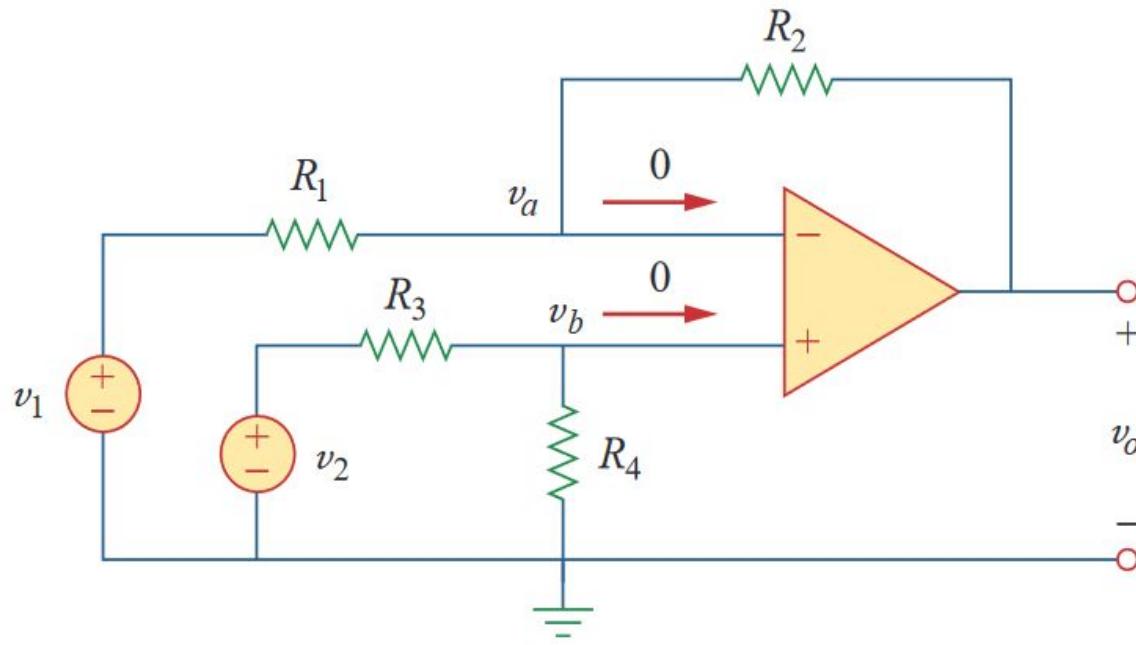

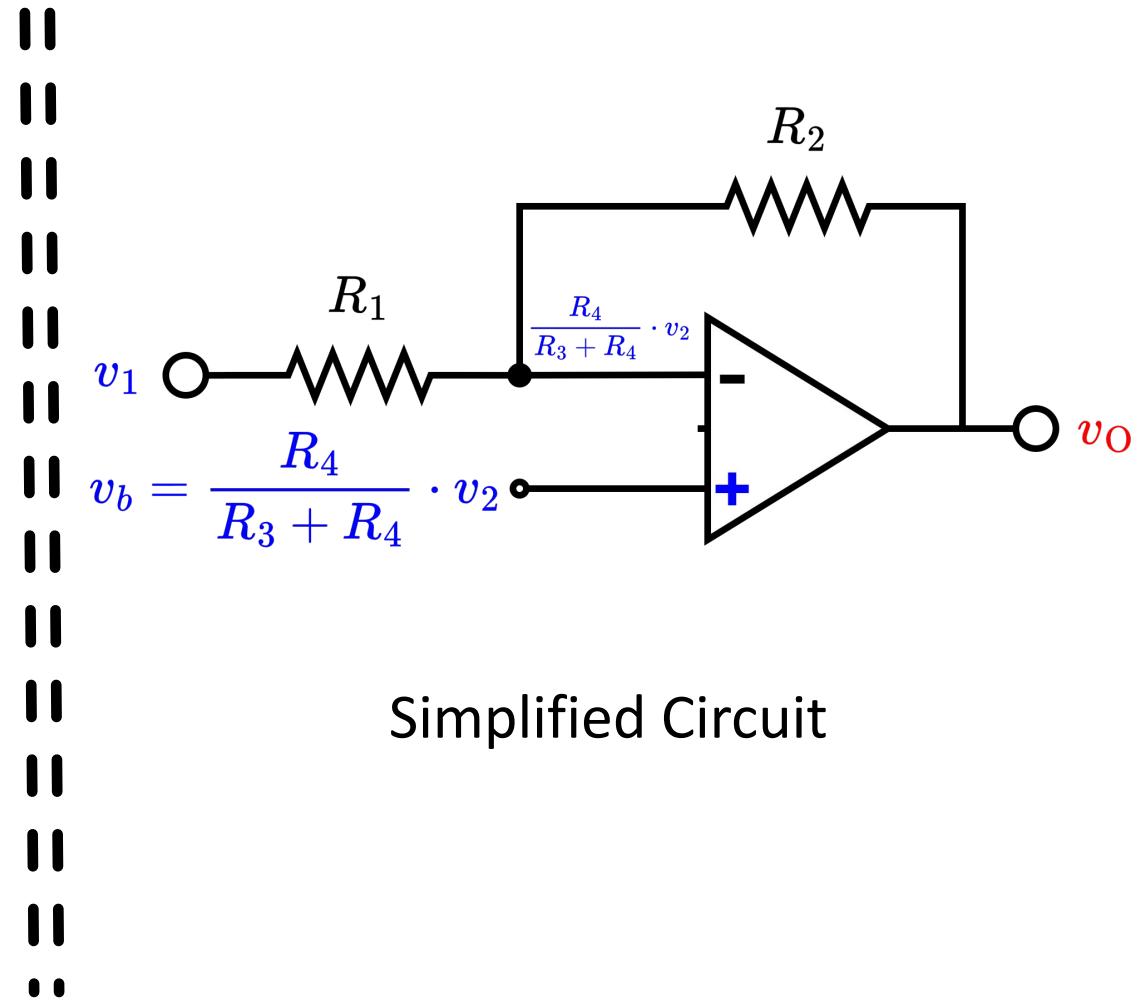
$$v_b = v_a = \frac{R_4}{R_3 + R_4} v_2$$



Difference Amplifier

Apply superposition principle:

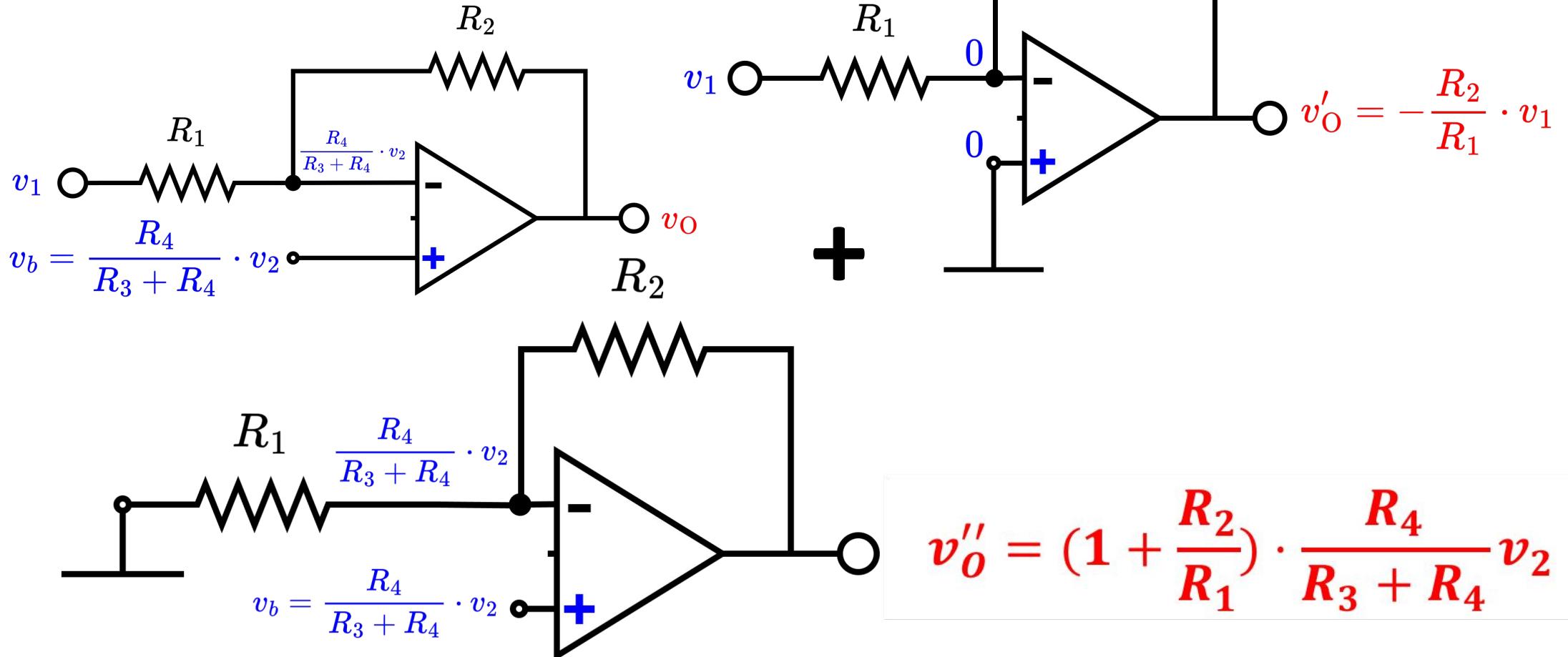


Difference Amplifier

$$v_b = v_a = \frac{R_4}{R_3 + R_4} v_2$$

$$v_o = v_o'' + v_o'$$
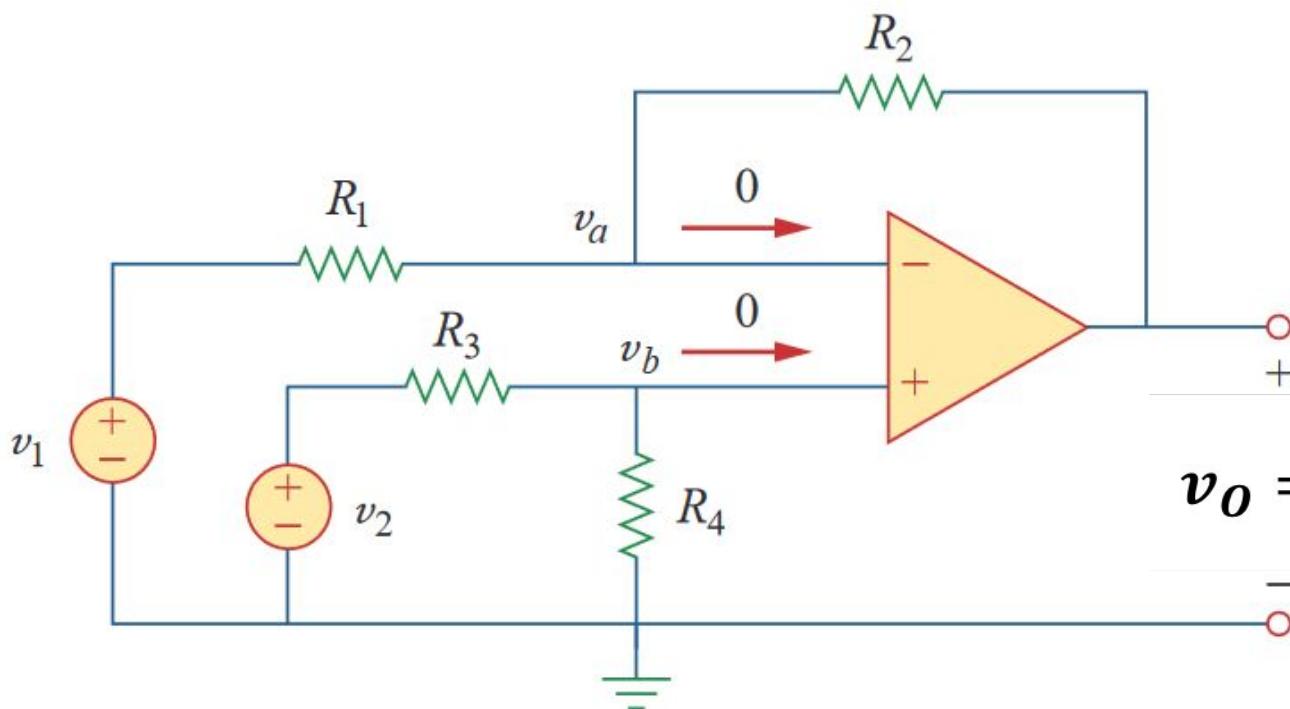
$$v_o = \left(1 + \frac{R_2}{R_1}\right) v_b - \frac{R_2}{R_1} \cdot v_1$$




$$v_o = \left(1 + \frac{R_2}{R_1}\right) \cdot \frac{R_4}{R_3 + R_4} v_2 - \frac{R_2}{R_1} \cdot v_1$$

Difference Amplifier – Example 8

Design an op amp circuit with inputs v_1 and v_2 such that

$$v_o = -5v_1 + 3v_2.$$

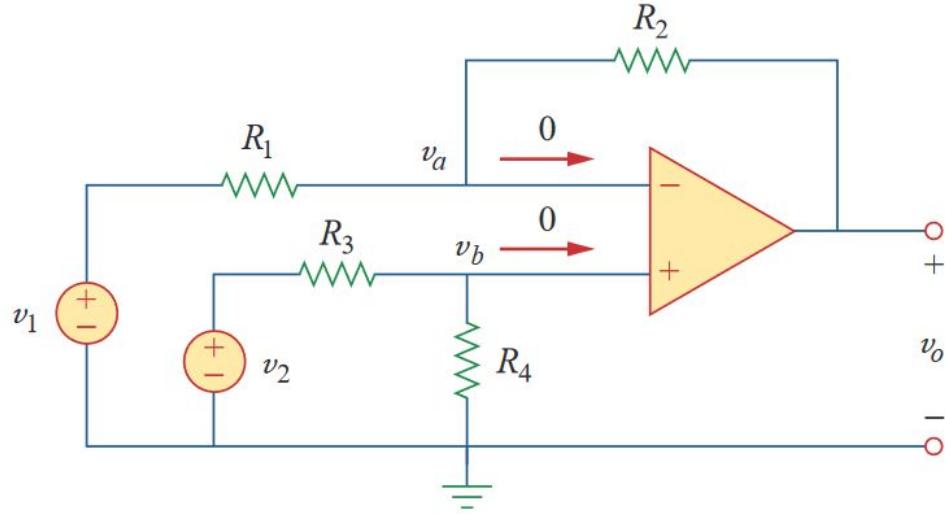

Solution: Method 1

$$v_o = -\frac{R_2}{R_1} \cdot v_1 + (1 + \frac{R_2}{R_1}) \cdot \frac{R_4}{R_3 + R_4} v_2$$

$$\therefore \frac{R_2}{R_1} = 5$$

$$\therefore (1 + 5) \cdot \frac{R_4}{R_3 + R_4} = 3$$

$$\Rightarrow R_3 = R_4$$

* To implement functions of the form $v_o = -Av_1 + Bv_2$, with difference amplifiers, **B must be less than $A + 1$**

Difference Amplifier – Example 9


Design an op amp circuit with inputs v_1 and v_2 such that

$$v_o = -3v_1 + 5v_2.$$

Solution: Method 2

Two stages amplifiers must be , we can implement this function.

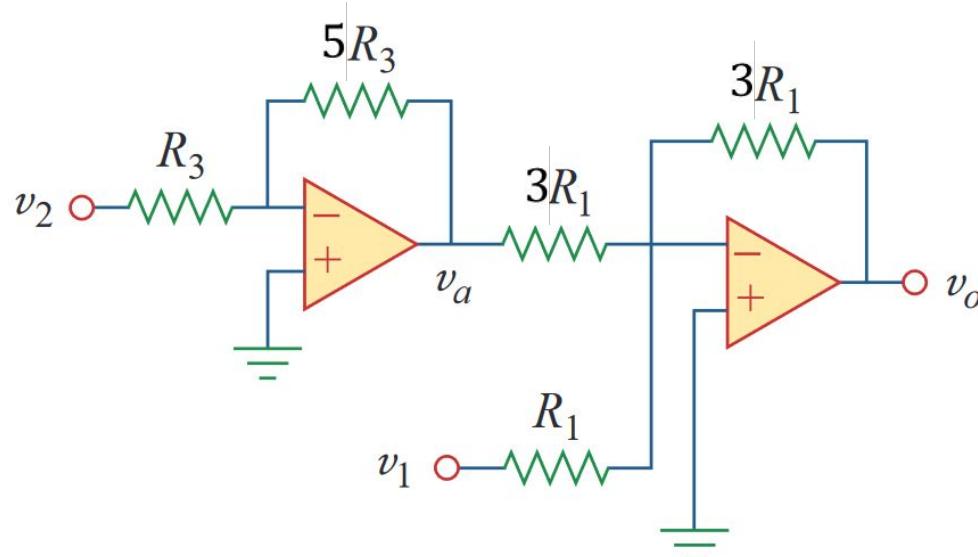$-3v_1$: Can be achieved with one stage inverting amplifier




$+5v_2$: Can be achieved by cascading two inverting amplifiers $\rightarrow (- \times - = +)$

* Here, in the expression of the form $v_o = -Av_1 + Bv_2$ given in the question $B > A + 1$. So, single stage difference amplifier cannot be used.

Subtractor ($v_1 - v_2$)

Design an op amp circuit with inputs v_1 and v_2 such that

$$v_o = v_1 - v_2.$$

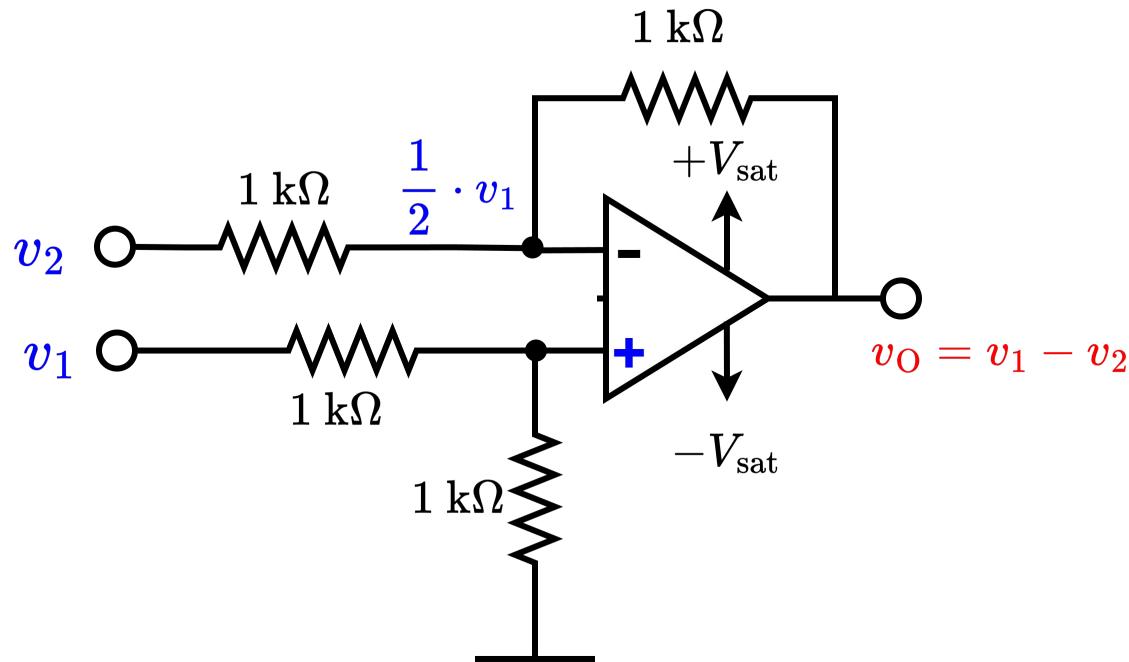

Solution: Method 1

$$\text{Inverting ratio} = 1$$

$$\text{Non-inverting ratio} = 1$$

$$\text{So, } \frac{R_2}{R_1} = 1 \text{ and } \left(1 + \frac{R_2}{R_1}\right) = 2.$$


$$\therefore R_1 = R_2$$

$$\text{So, to get } \left(1 + \frac{R_2}{R_1}\right) \cdot \frac{R_4}{R_3 + R_4} = 1,$$


$$\therefore R_4 = R_3$$

Op Amp as Inverting Differentiator

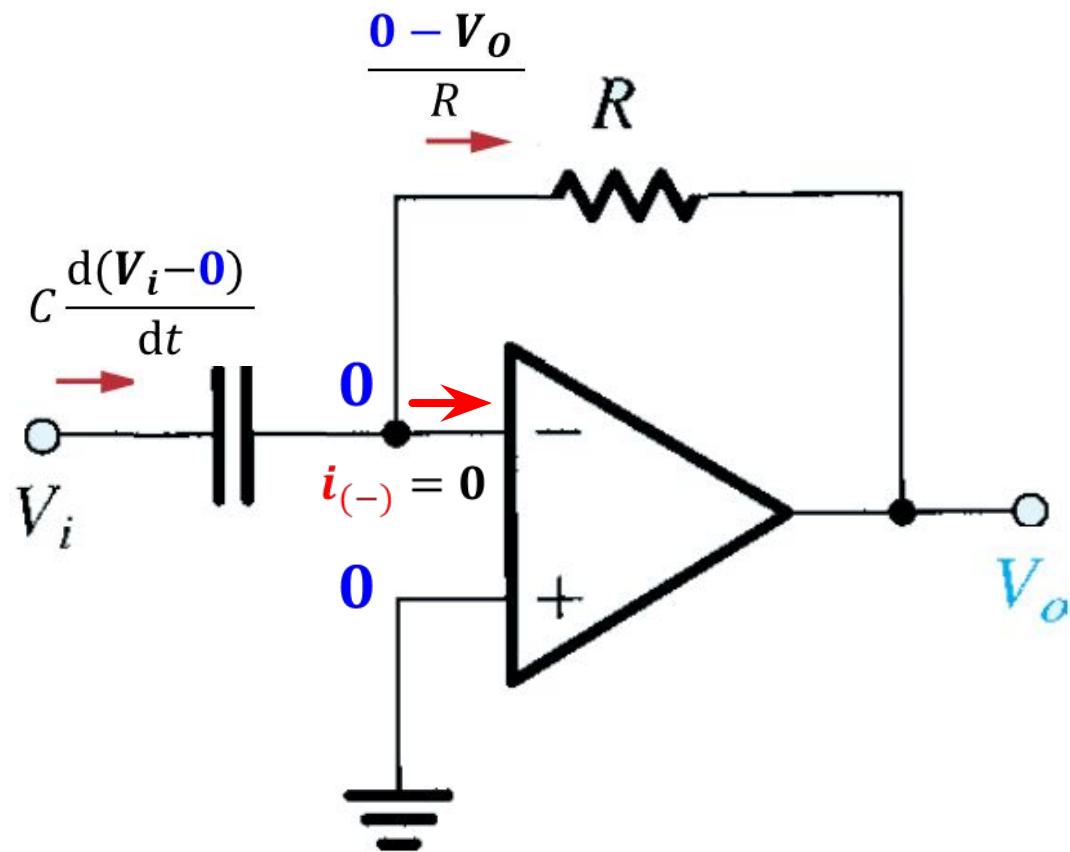Since ideal op-amp, $i_- = i_+ = 0$, so $i_1 = i_2$



Review – Capacitor

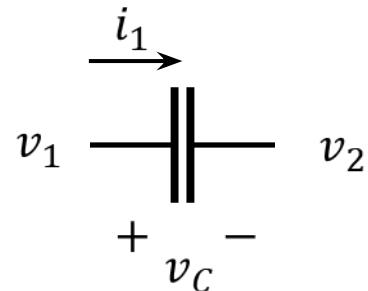


$$i_1 = C \frac{dv_C}{dt} = C \frac{d(v_1 - v_2)}{dt}$$

$$\Rightarrow -\frac{V_o}{R} = C \frac{dV_i}{dt}$$


$$\Rightarrow V_o = -RC \frac{dV_i}{dt}$$

Op Amp as Inverting Integrator

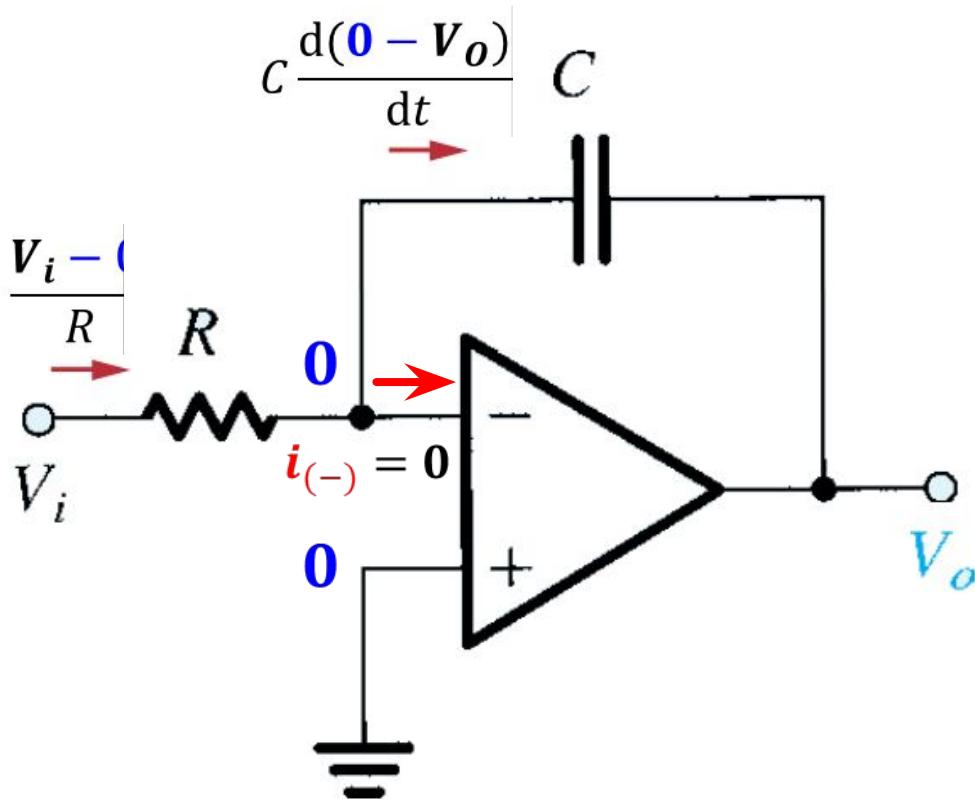Since ideal op-amp, $i_- = i_+ = 0$, so $i_1 = i_2$



Review – Capacitor

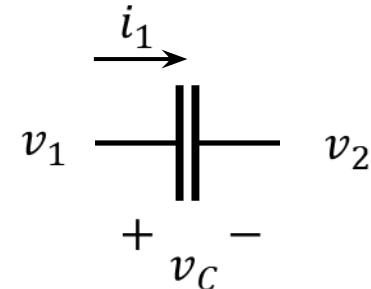


$$i_1 = C \frac{dv_C}{dt} = C \frac{d(v_1 - v_2)}{dt}$$

$$\Rightarrow \frac{V_i}{R} = -C \frac{dV_o}{dt}$$

$$\Rightarrow V_o = -\frac{1}{RC} \int V_i(t) dt$$

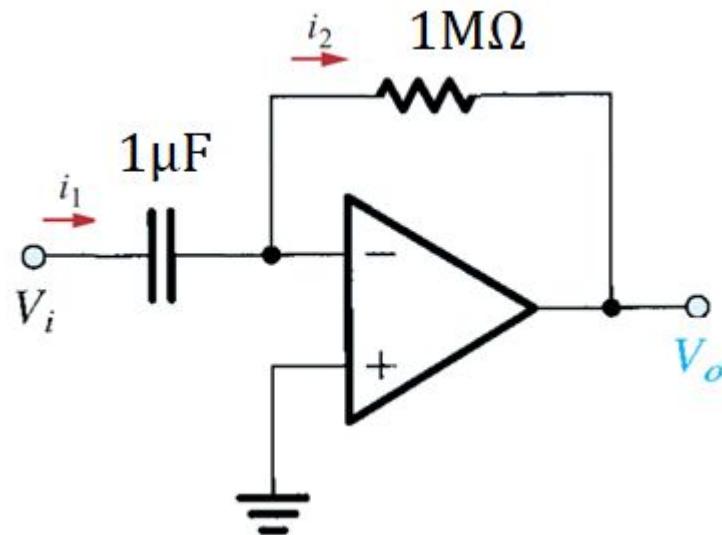Example 10

Observe the following Figure. If $V_i = 5 \cdot \sin(6t)$, Find the value of V_o



Solution:

This is a **differentiator**.


$$v_o = -RC \frac{dV_i}{dt}$$

$$= -(1 \times 10^6) \cdot (1 \times 10^{-6}) \times \frac{d(5 \cdot \sin(6t))}{dt}$$


$$= -1 \times (5 \times 6 \cos(6t))$$

$$= -30 \cos(6t)$$


Example 11

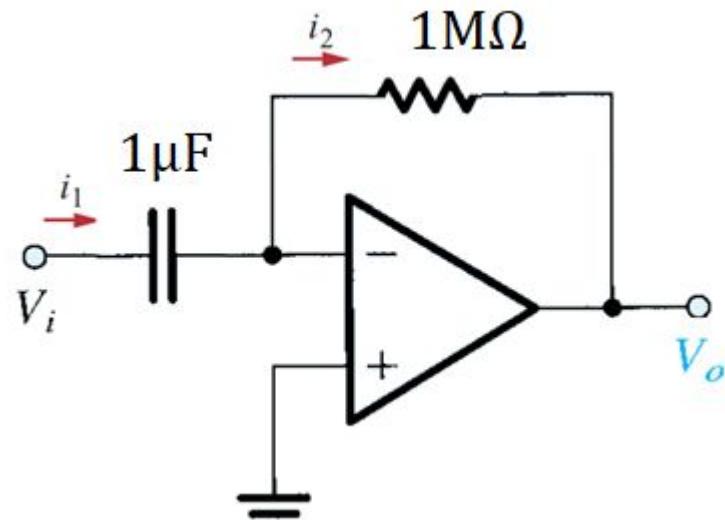


$$\text{Slope: } \left| \frac{dv}{dt} \right| = \frac{V_M - (-V_M)}{T/2} = \frac{4V_M}{T}$$

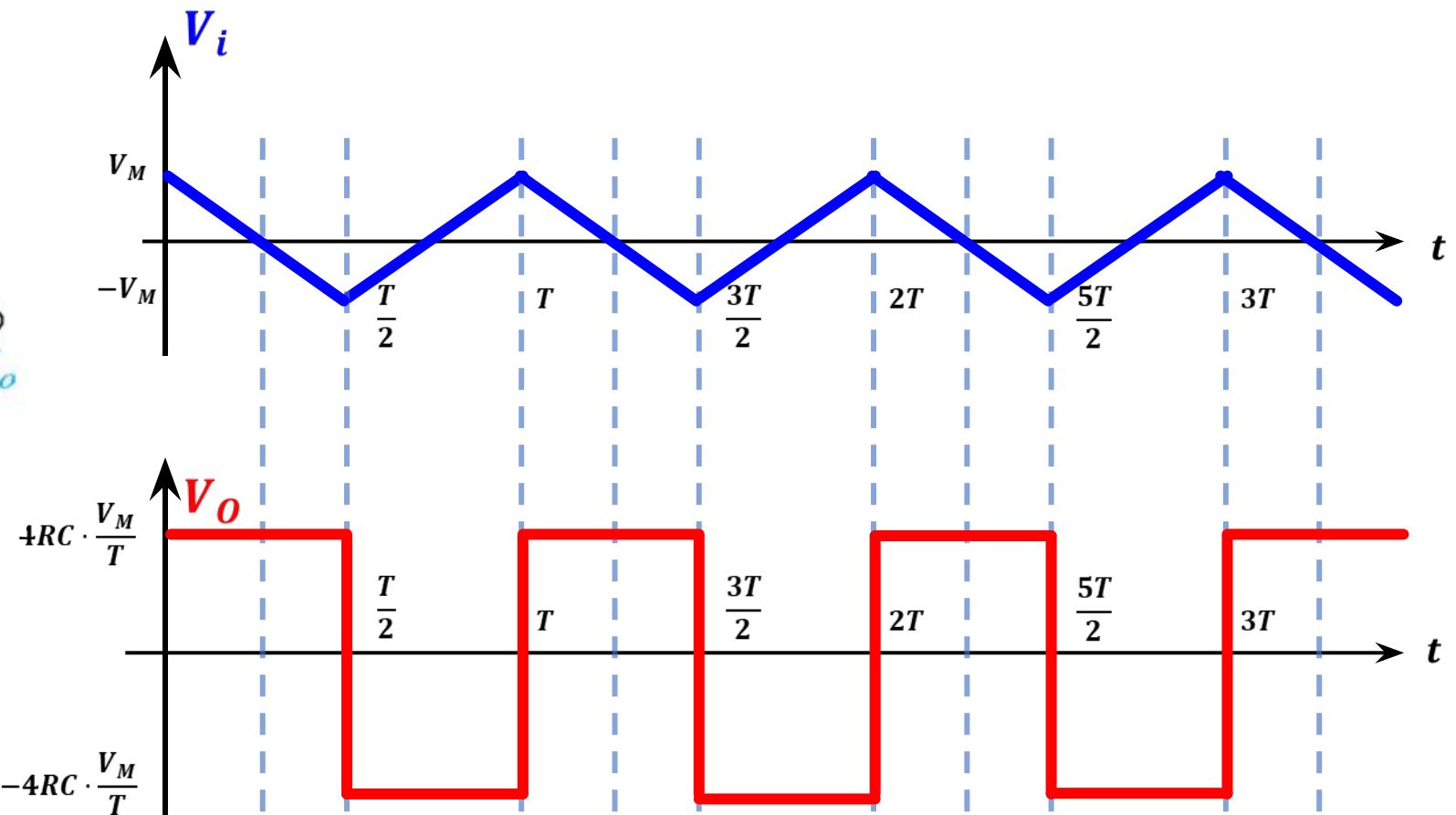


Example 12

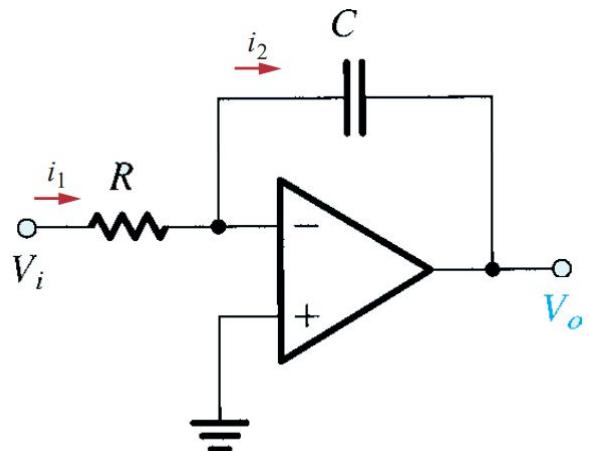


$$\int_0^t v_I dt = V_M \cdot t$$

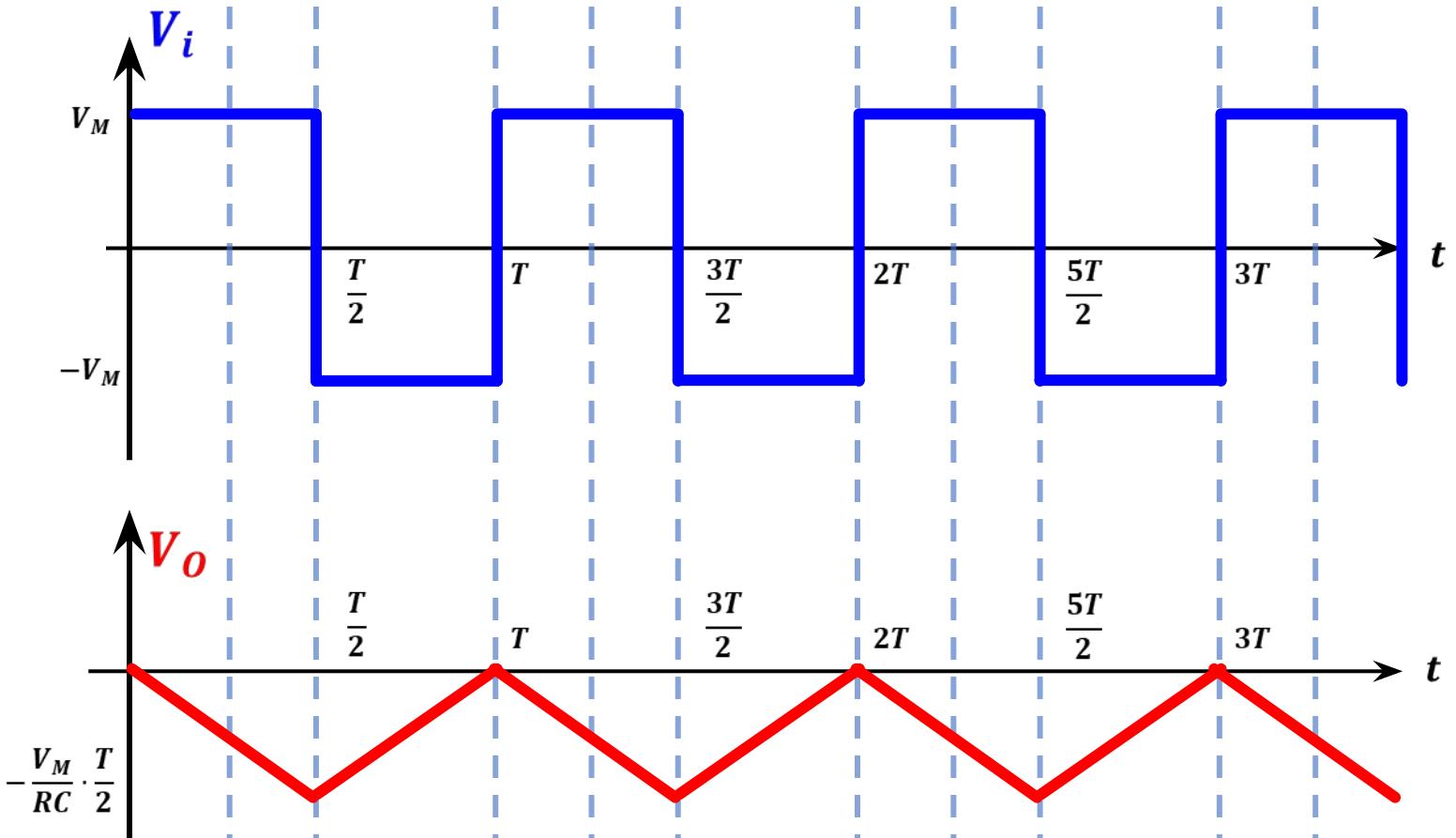

Example 12

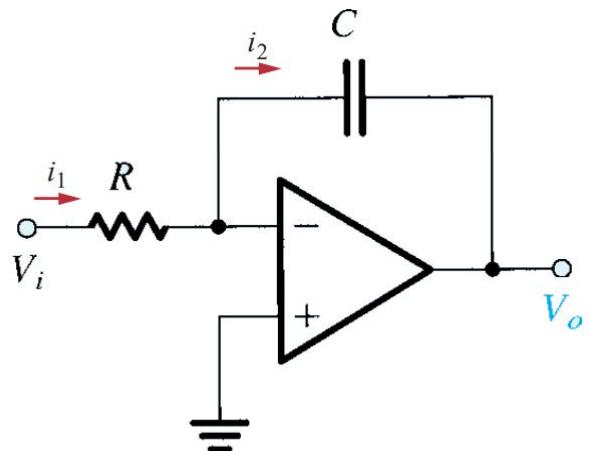

$$\int_0^t v_I dt = V_M \cdot t$$

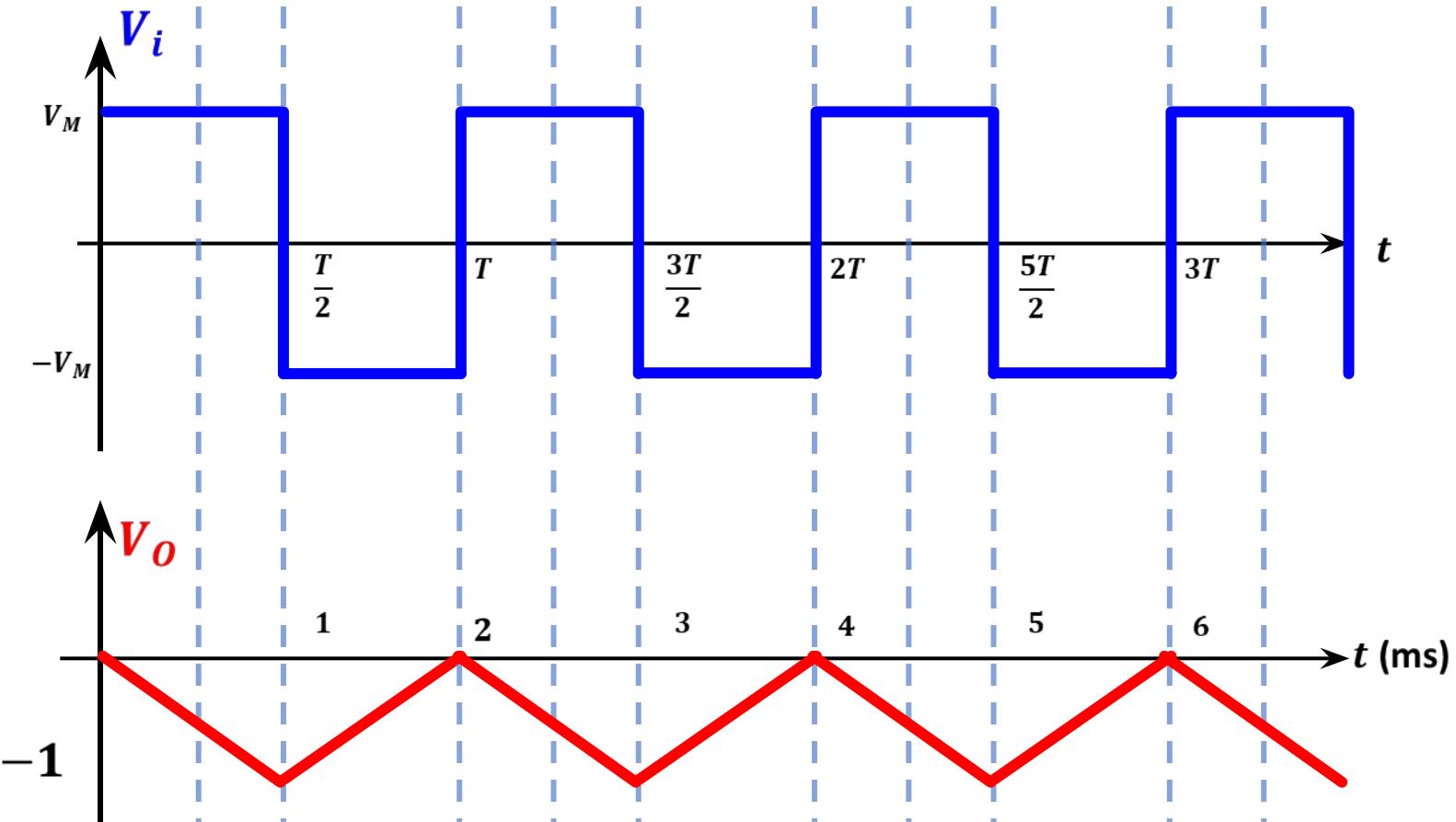

APPLICATIONS:

Implementing operational functions

- $f = -2x - 3y$
- $f = -4x + 5y$
- $f = -7x + \frac{d}{dt}y$
- $f = -\frac{1}{3} \int x \cdot dt + 2 \ln y + 4z$
- $f = -3 \frac{dx}{dt} + 2 \exp(y) + 4z$
- $f = xy/z$

APPLICATIONS:

Implementing operational functions

- $f = -2x - 3y$

APPLICATIONS:

Implementing operational functions

- $f = -4x + 5y$


APPLICATIONS:

Implementing operational functions

- $f = -7x + \frac{d}{dt}y$

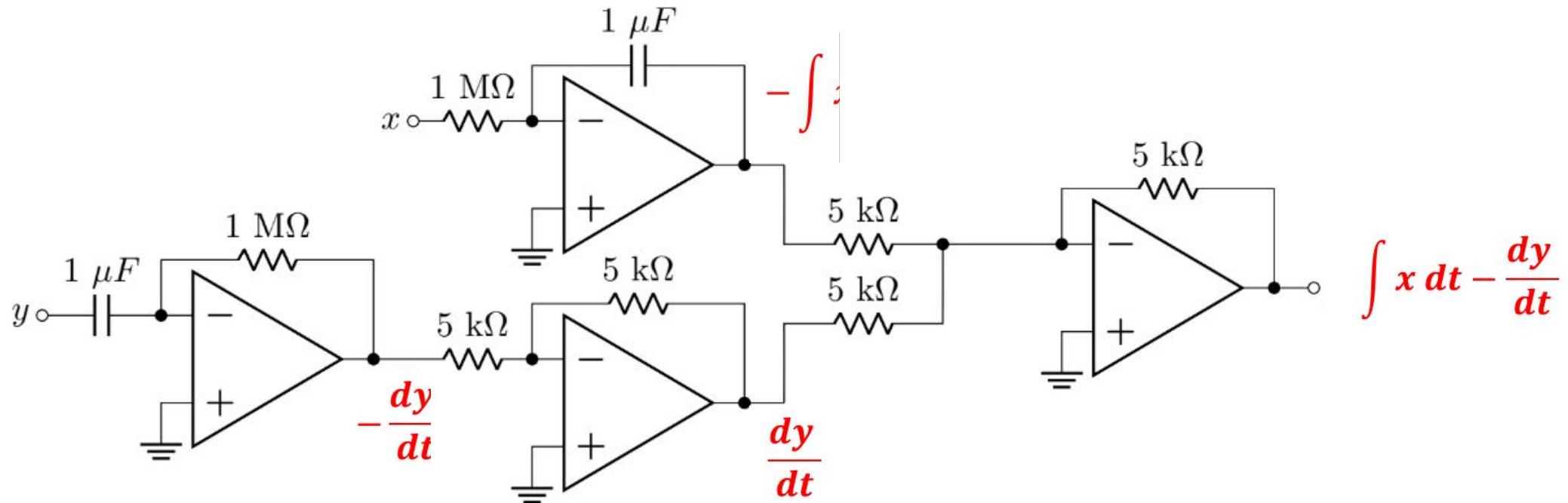Example

Analyze the circuit below to find an expression of f in terms of inputs x and y .




Solution:

$$v_{I_1} = -\frac{dy}{dt}; v_{I_2} = -\frac{1}{RC} \int x dt; v_{I_3} = -v_{I_1} = \frac{dy}{dt}; v_o = -(v_{I_2} + v_{I_3})$$

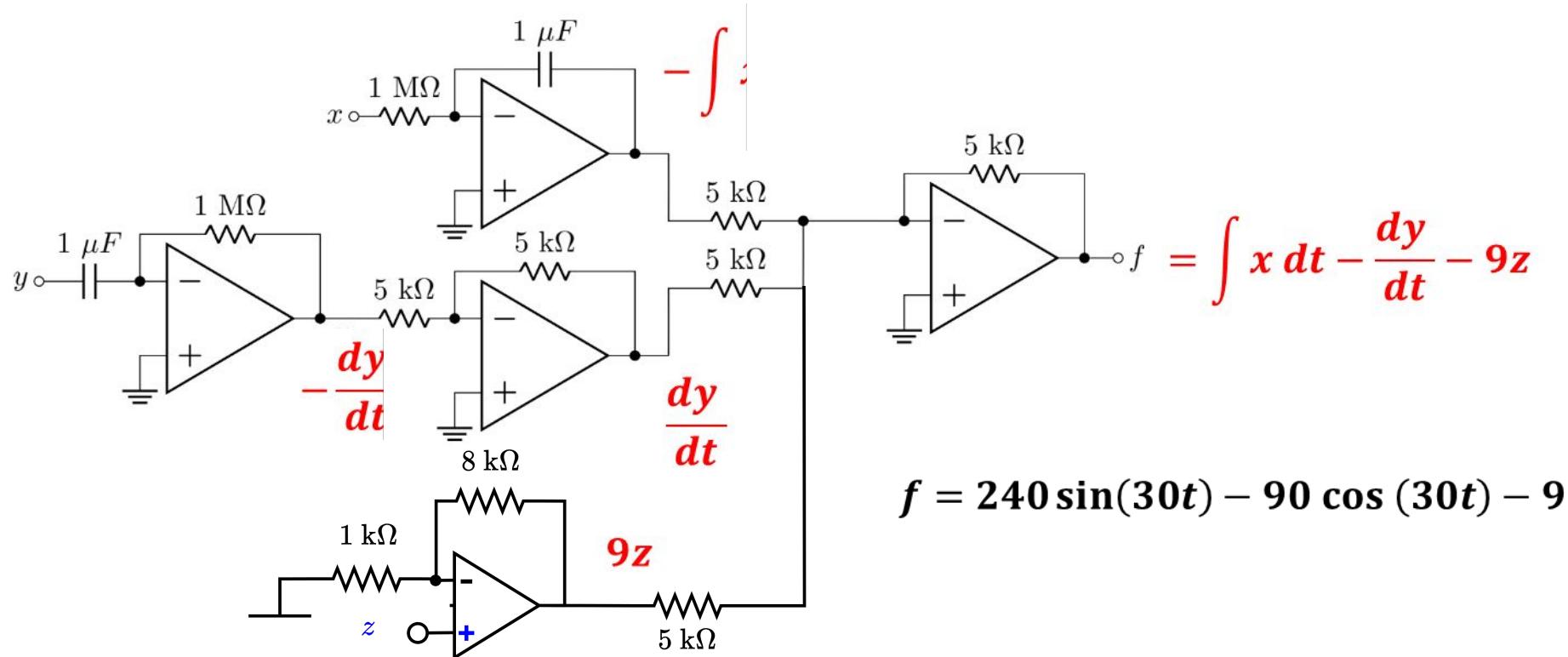Example

Analyze the circuit below to find an expression of f in terms of inputs x and y .

If $x = 8 \cos(30t)$ V and $y = 3 \sin(30t)$ V and $z = 1$ V



Thank You!