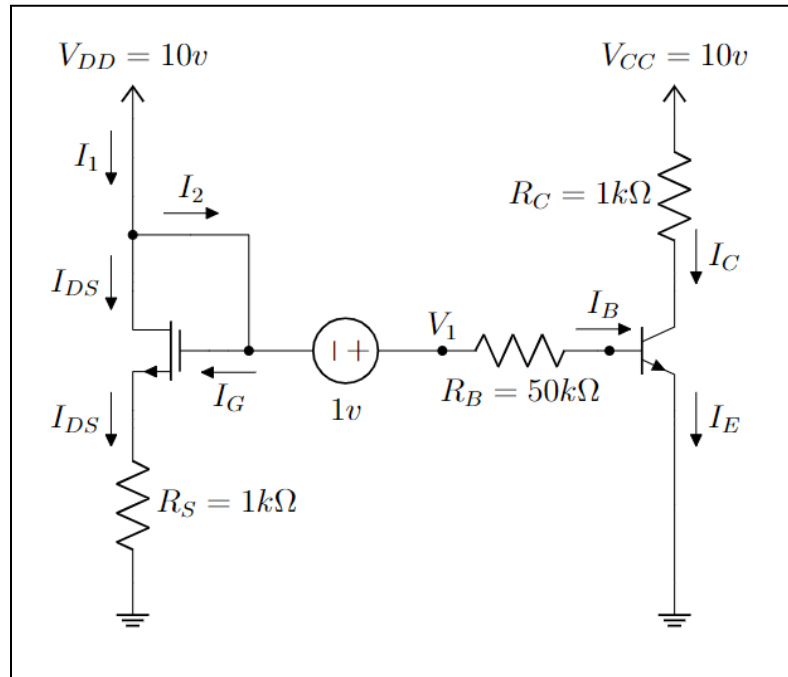


Assignment 4
CSE251
Total Marks: 40

1.




In the circuit above, the MOSFET and BJT have the following parameters,

$$K = 4 \text{ mA/V}^2, V_T = 0.9 \text{ V}, \beta = 100, V_{BE(\text{active})} = 0.7 \text{ V}, V_{BE(\text{sat})} = 0.8 \text{ V}$$

- Find out the gate voltage of the MOSFET.
- Calculate V_1 .
- Find out the expression for V_{GS} , V_{DS} and V_{OV} .
- Find the operating mode of the MOSFET using the expressions from ©. [Hint: You don't need any assumption]
- Calculate I_{DS} and V_{DS} using the given parameters.
- Assume that the BJT is in the saturation mode. Now, **calculate** I_B , I_C , I_E . You must **validate** the given assumption.

Assignment 4
CSE251
Total Marks: 40

2.

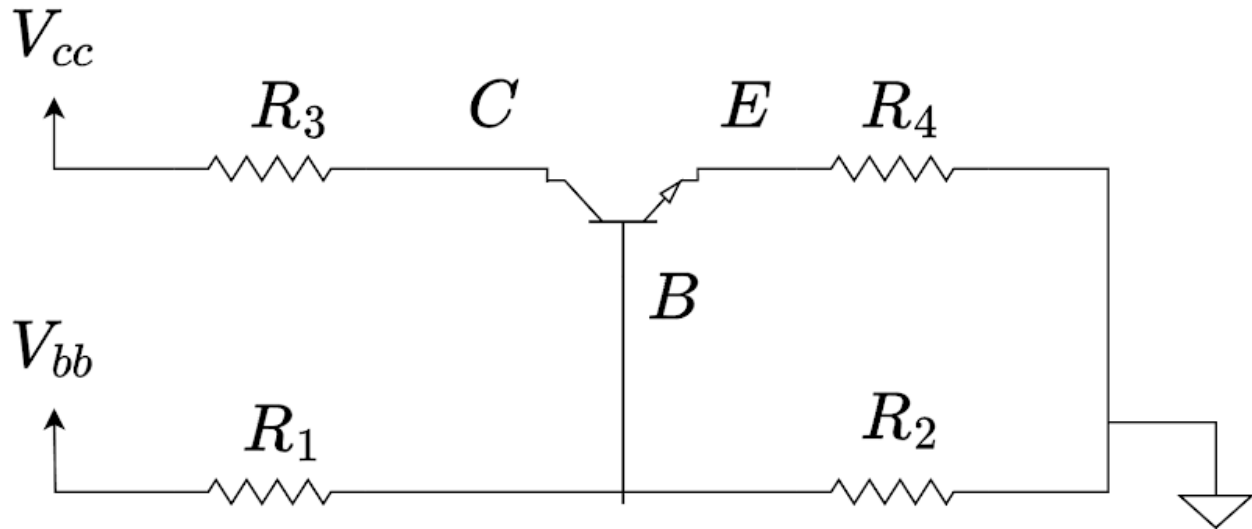


In the above circuit, $V_{bb} = 5V$, $V_{cc} = 15V$, $R_1 = 20k\Omega(40k\Omega)$, $R_2 = 80k\Omega(60k\Omega)$, $R_3 = 2k\Omega$ and $R_4 = 1k\Omega$. Also, assume current gain, $I_c/I_b = 100$.

- Draw the equivalent circuit of BJT during saturation and active modes. [2]
- Solve the above circuit and calculate I_B , I_C , I_E , V_{CE} and V_C using the method of assumed states. [Hint: try to find the Thevenin equivalent of the left hand side circuit from the B terminal and ground] [3]
- If V_{bb} is changed from 5V to 5.1V, what happens to the outputs of the circuits? Calculate I_B , I_C , I_E , V_{CE} and V_C again. Now for a 0.1V increase in input V_{bb} , what is the change of I_C ? Use $\Delta I_C = I_{C,new} - I_{C,old}$. [3+1]
- Explain any use case of the differences in voltage increase between input and output. What could the use case be to such a phenomenon? [1]

Assignment 4
CSE251
Total Marks: 40

3.

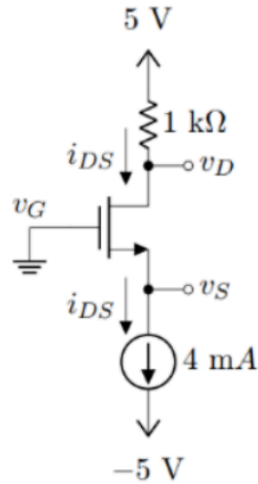


Circuit 1

Refer to the **Circuit** above. For the MOSFET, $V_T = 1\text{ V}$ and $k = k'_n \frac{W}{L} = 4\text{ mA/V}^2$.

- (a) **Identify** the value of the gate voltage v_G and the drain-source current i_{DS} .
- (b) **Calculate** the value of the drain voltage v_D using the $1\text{ k}\Omega$ resistor.
- (c) **Analyze** the circuit to find v_S . Here, **use** the Method of Assumed State. You must **validate** your assumptions. [Hint: assume $v_S = x$]

Assignment 4
CSE251
Total Marks: 40

4.

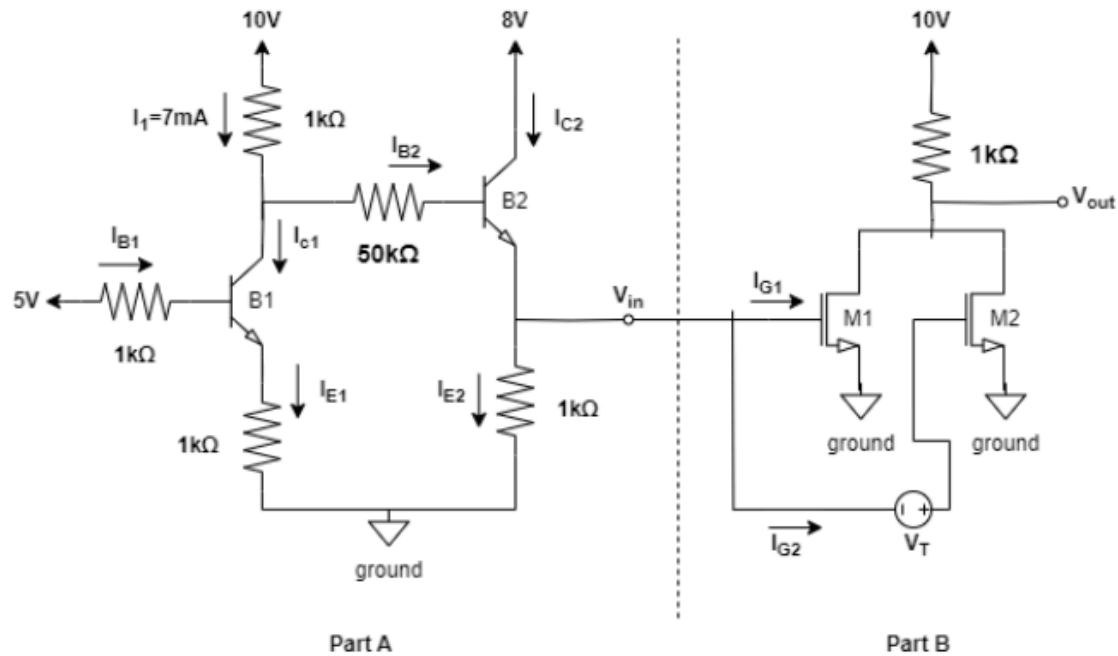

In the circuit above, the BJTs have the following specification: $\beta=100$, Forward Active Region: $V_{BE} = 0.7\text{ V}$, $I_C = \beta I_B$, Saturation Region: $V_{BE} = 0.8\text{ V}$, $V_{CE} = 0.2\text{ V}$, or the MOSFETs: $V_T = \text{Threshold Voltage of M1 and M2}$.

- (a) Determine i_{g1} and i_{g2}
- (b) **Justify** why the SR model of MOSFET is more efficient than the S model ? [1]
- (c) Assume, B1 and B2 are in the **Saturation region**. Calculate i_{c2} .
- (d) Assume, B1 is in the **Forward Active region**. Calculate V_{in} .
- (e) **Draw the VTC** of Part- B assuming, $V_T = 8\text{ V}$. [Use S model of MOSFETs]