
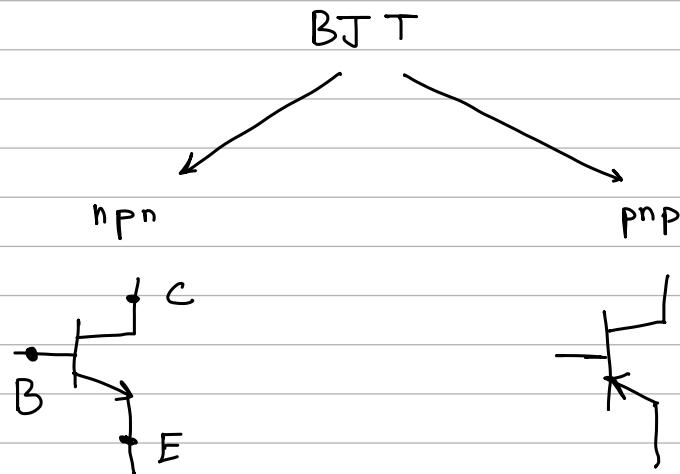


# BJT (Bipolar Junction transistor) :

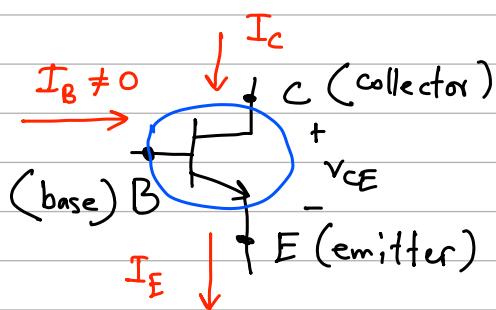

→ mainly will deal with npn.

## BJT



$$I_B + I_C = I_E$$


$$I_C \neq I_E$$

IV characteristics ( $I_C$  vs.  $V_{CE}$ ):

→  $I_B$  controls this graph

→ current controlled

## MOSFET

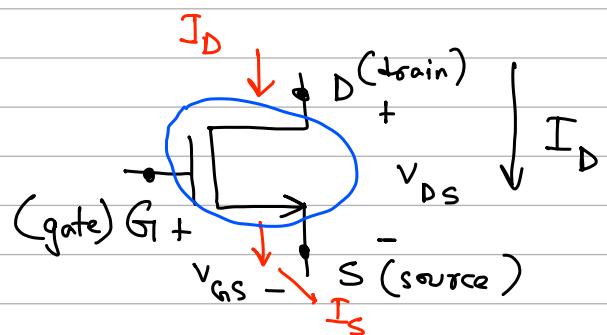

$$V_{GS} < V_T : \text{cutoff}$$

$$V_{GS} > V_T : \text{triode or saturation}$$

$$V_{DS} \leq V_{ov}$$

$$V_{DS} > V_{ov}$$


$$V_{ov} = V_{GS} - V_T$$

$$I_G = 0, I_D = I_S$$

IV characteristics ( $I_D$  vs  $V_{DS}$ ) :

→  $V_{GS}$  controls this graph

→ voltage controlled

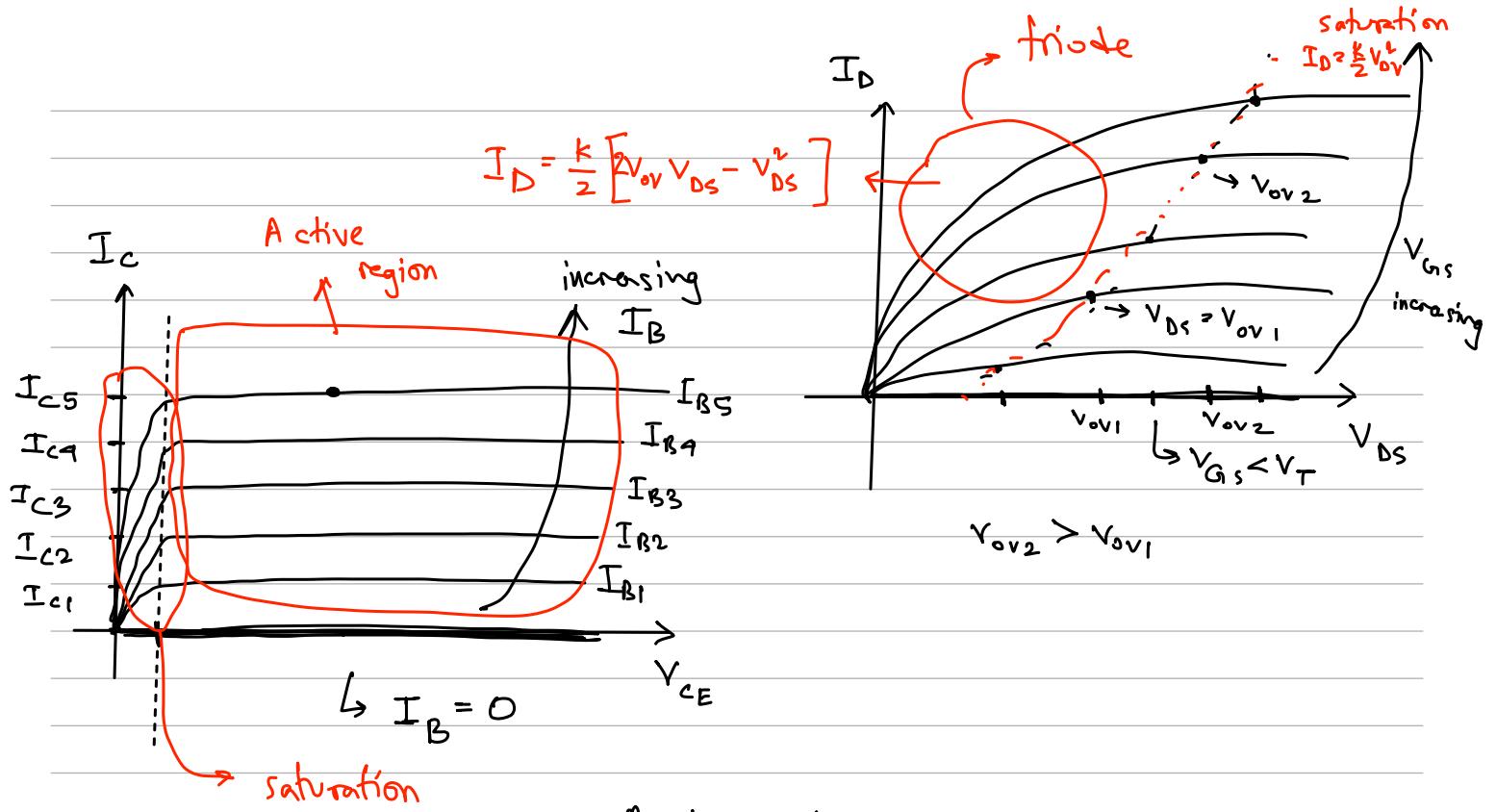

Analogue :

BJT


cutoff  
(much easier)  
than MOSFET saturation

active

MOSFET

cutoff  
triode  
saturation

S-model of BJT :

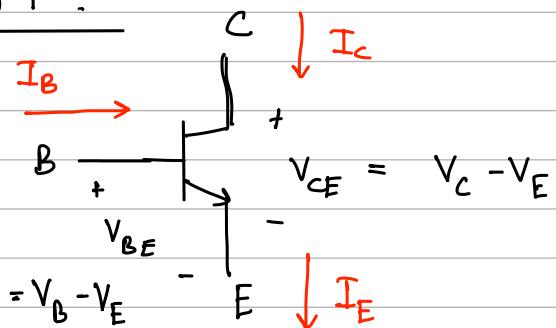


$$I_E = I_B + I_C$$


\* Current controlled ( $I_B$ ) switch.

\* Interested in  $I_C$ ,  $V_{CE}$

$$I_B = 0$$




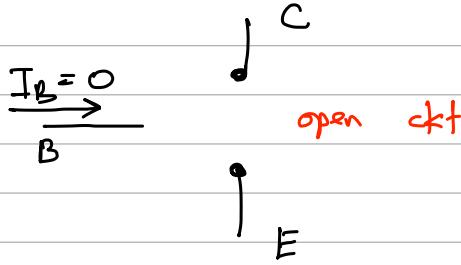


$$I_B \geq I_{th}$$

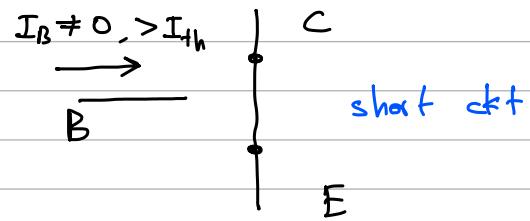

OFF ( logic state 0 )

ON ( logic state 1 )

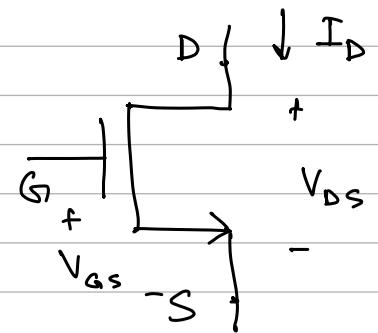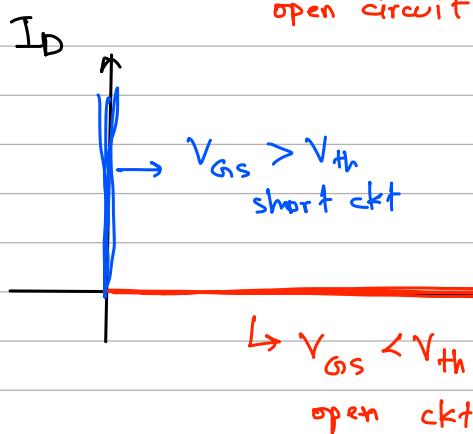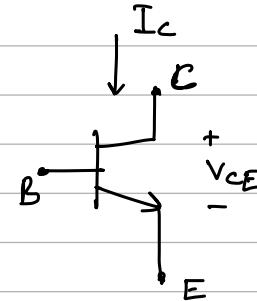
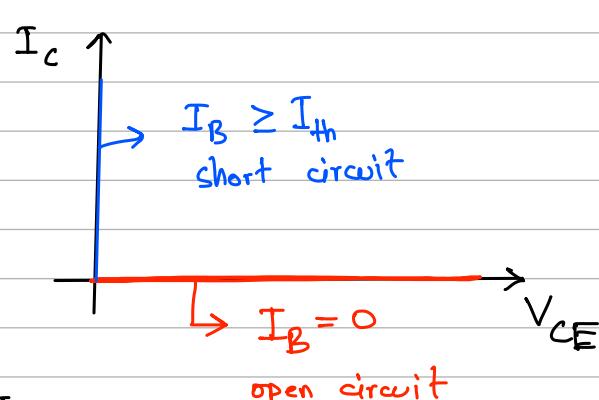


\* What if  $0 < I_B$  and  $I_B < I_{th}$  ?

→ Invalid in S-model


→  $0 < I_B < I_{th}$  : actually 'active mode' in BJT

NOT inverter :

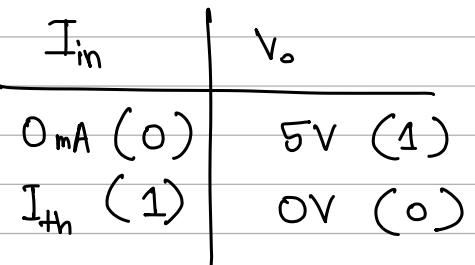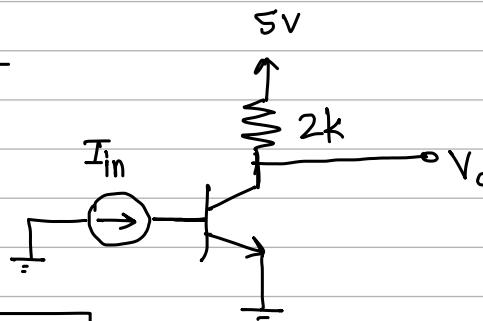

Output = Input


NAND :

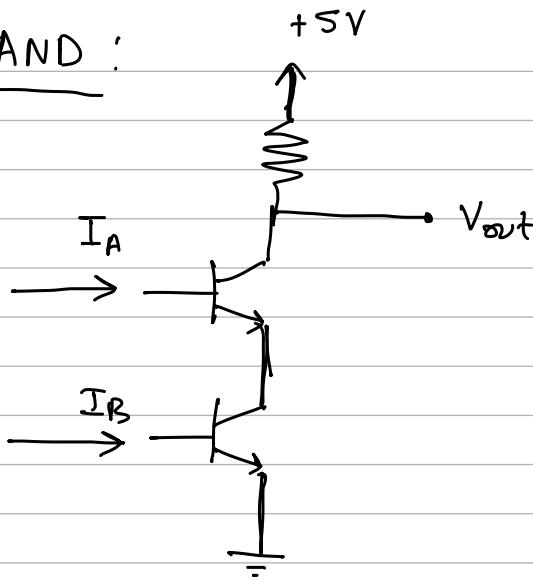

$$out = \overline{AB}$$


$I_A$	$I_B$	$V_{out}$
0mA(0)	0mA(0)	5V(1)
0mA(0)	$I_{th}(1)$	5V(1)
$I_{th}(1)$	0mA(0)	5V(1)
$I_{th}(1)$	$I_{th}(1)$	0V(0)

NOR :

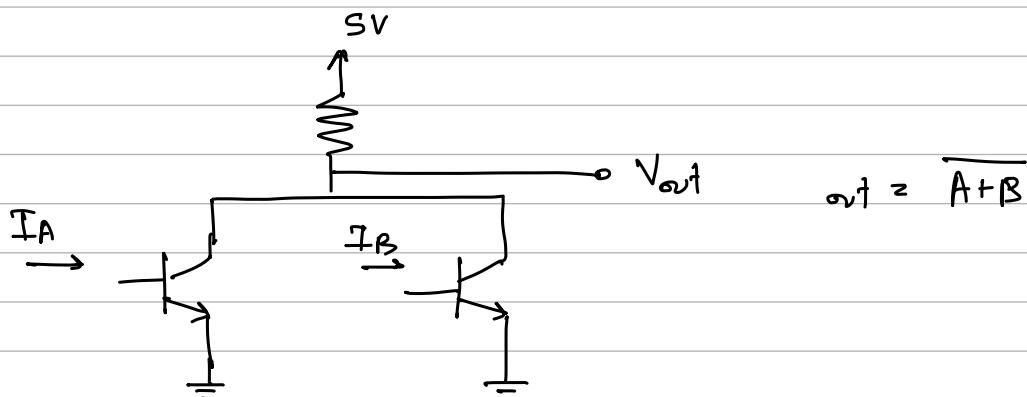

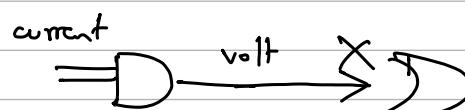
Problem :

- ① Cascading issue [ gate output voltage, but input current ]



\* Can be addressed by using voltage source to

create base current,

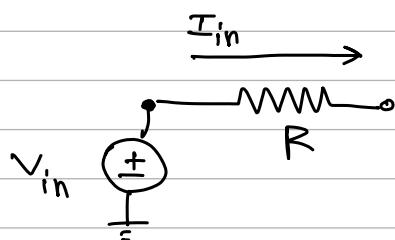


- ② Current source ?


- ③ current setting to zero is tough

[ for mosfet :  
 $V_{GS} < V_{th} \rightarrow \text{logic 0}$   
 for BJT :  
 $I_B = 0 \rightarrow \text{logic 0}$  ]

## Voltage control :

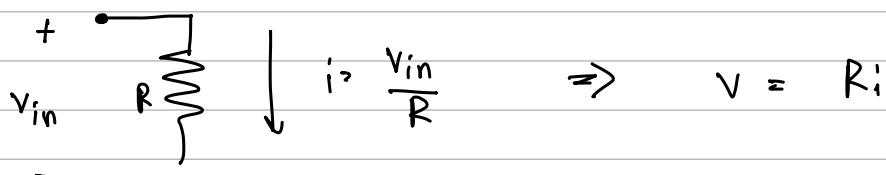


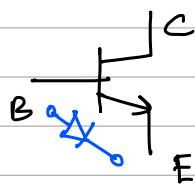→ we use resistors to convert from voltage to current




$\begin{matrix} n & \rightarrow & n\text{-type semiconductor} \\ P & \rightarrow & P\text{-type semiconductor} \\ n & \rightarrow & n\text{-type semiconductor} \end{matrix}$


bef" Base and Emitter :

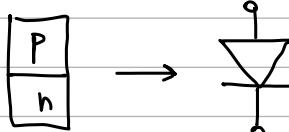

E.g : Inverter :

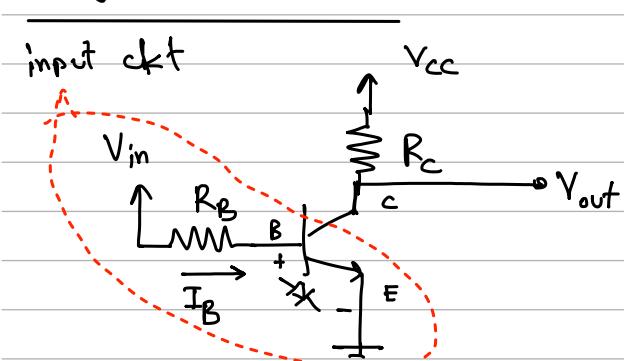

input (control) circuit :

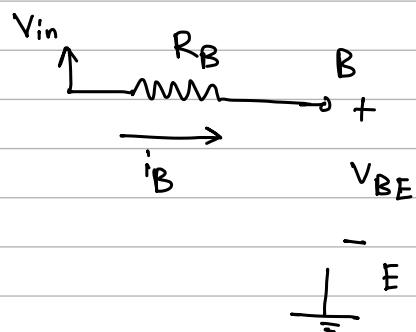

$I_B$	$V_{in}$	$V_{out}$
$I_B = 0 \text{ mA (0)}$	$V_{in} < 0.7V$	5V (1)
$I_B \geq I_{th} (1)$	$V_{in} > V_{th}$	0V (0)

$V_{in} < 0.7$  :

→ BE is not forward biased


$\left[ \text{B} \times \text{E} \text{ is 'OFF'} \right]$

→  $I_B = 0$ .

$V_{in} \geq 0.7$  :

BE forward biased

$I_B > 0$ .

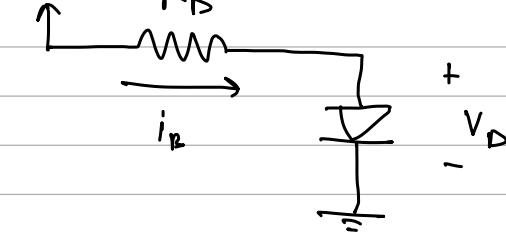

when diode ON : KVL :

$$i_B R_B + 0.7 = V_{in} - 0$$

or,


$$i_B = \frac{V_{in} - 0.7}{R_B}$$

When  $i_B = I_{th}$ :


$$I_{th} = \frac{V_{th} - 0.7}{R_B} \Rightarrow V_{th} = (I_{th} R_B + 0.7) V$$

When,  $I_B = I_{th}$ ,  $V_{in} = V_{th}$ .

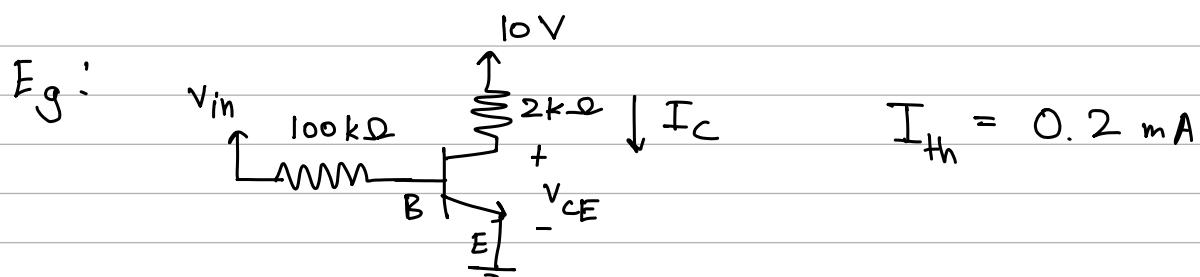$\therefore V_{in} \geq V_{th}$ ,  $I_B \geq I_{th}$ .



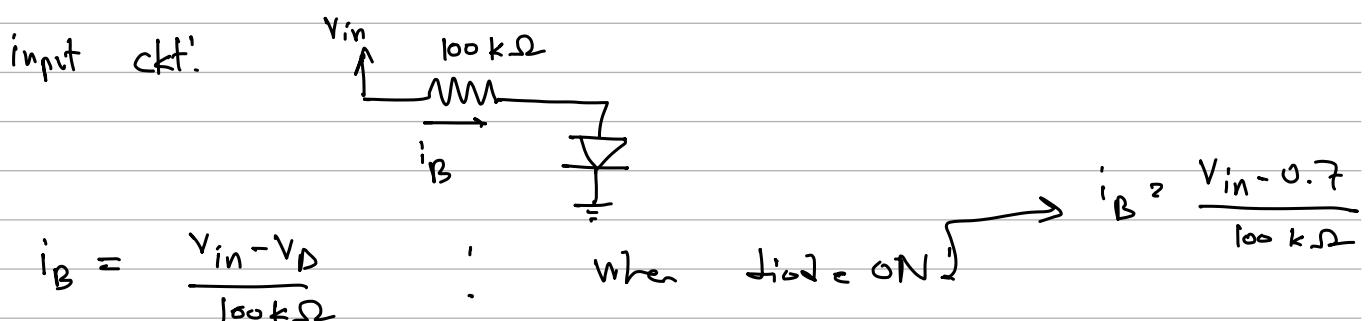
find threshold of  $V_{in}$  for which  $I_B \geq I_{th}$ .



$\therefore V_{in} < 0.7 \text{ V}$  : Diode OFF, BE junction reverse biased.

$\therefore I_B = 0$  when  $V_{in} < 0.7 \text{ V}$

$I_B = I_{th} = 0.2 \text{ mA}$ :

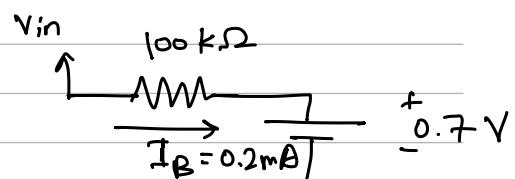



$$0.2 \text{ mA} \times 100 \text{ k}\Omega = V_{in} - 0.8 \text{ V}$$

$$V_{th} = 20 + 0.8 = 20.8 \text{ V}$$

$$V_{in} = 20.8 \text{ V}, I_B = 0.2 \text{ mA} \Rightarrow V_{in} \geq \underline{\underline{20.8 \text{ V}}}, I_B \geq I_{th}.$$

$V_{th}$



Slight correction:

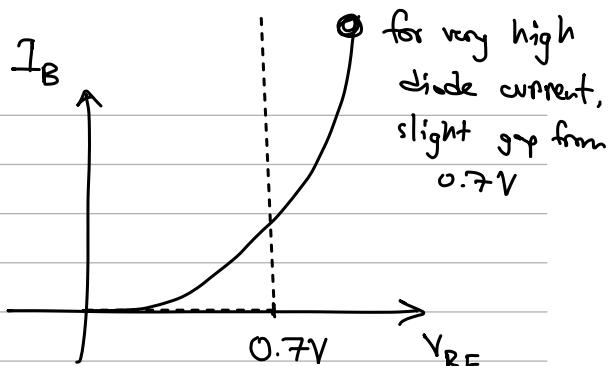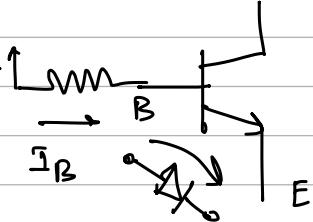

then for  $I_B \geq I_{th}$ :


→ very high current, so diode loop assumed slightly more than 0.7V.  $\Rightarrow 0.8V$

Physical structure:

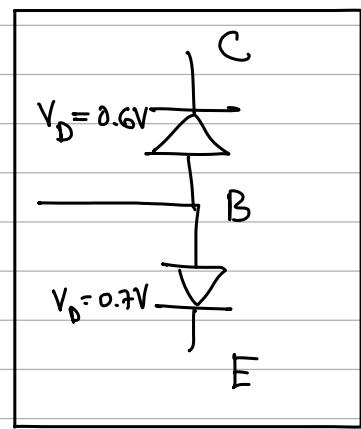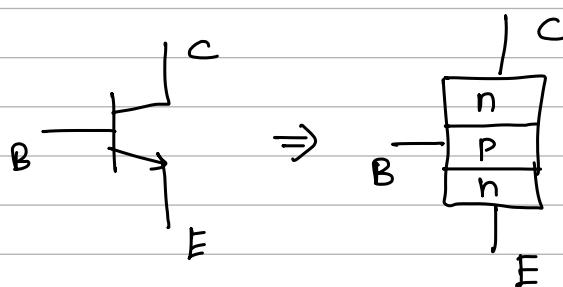


→ not actual BJT structure

→ only used for analysis simplification

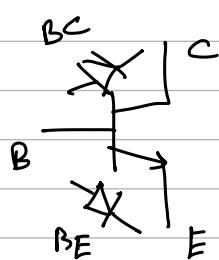

$BE \rightarrow ON, OFF$       } 4 combinations  
 $BC \rightarrow ON, OFF$       } 4 modes of operation


[cutoff]

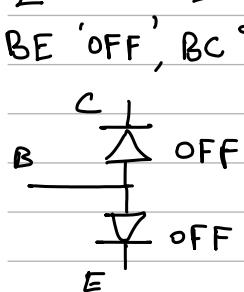

$$\rightarrow I_B \approx 0.$$


$$\rightarrow I_C = 0$$

$BE 'OFF', BC 'ON'$  (reverse active)

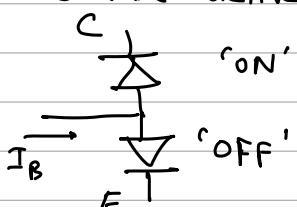

→ similar to 'active'  
→ will not deal  
with this much


[saturation]

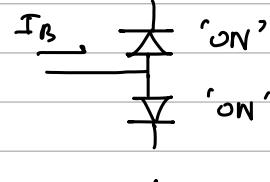


$$\rightarrow I_C \propto I_B$$

$$\frac{0.6}{I_B} + \frac{V_{CE}}{I_B} = 0.8 - 0.6 \\ \frac{0.8}{I_B} - \frac{V_{CE}}{I_B} = 0.2V$$

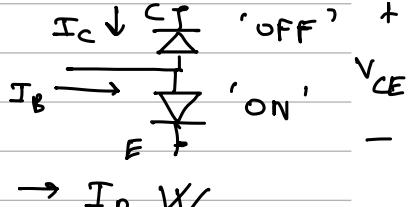$BE 'ON', BC 'OFF'$  (active)  
 $I_C \downarrow$  'OFF'


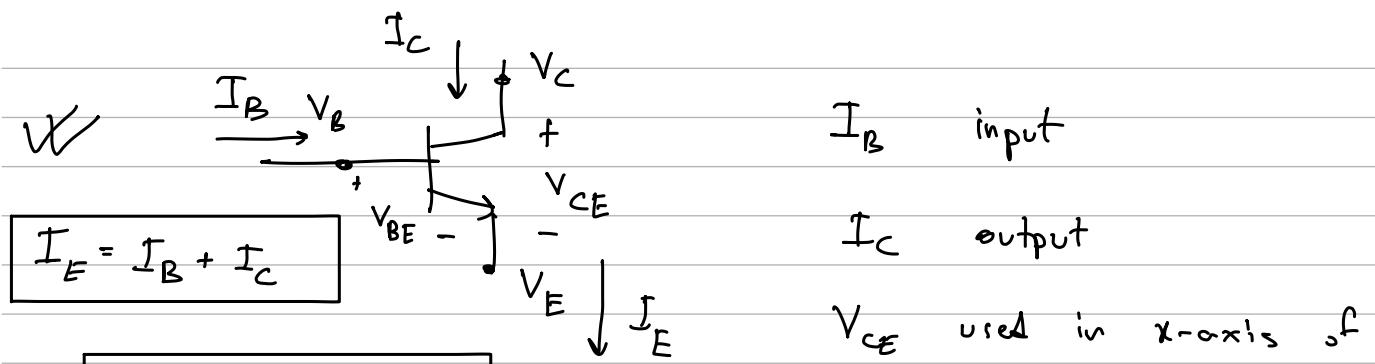
$$\rightarrow I_C \text{ const.}, \propto I_B$$



$$V_{BE} = V_B - V_E$$

$$V_{BC} = V_B - V_C$$

$$V_{CE} = V_C - V_E$$



(output characteristics graph)

$$V_{BC} = V_B - V_E + V_E - V_C$$

$$= (V_B - V_E) - (V_C - V_E)$$

$$V_{BC} = V_{BE} - V_{CE}$$

## ① Cut-off :

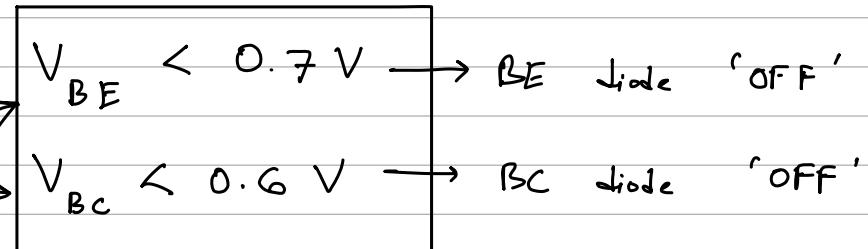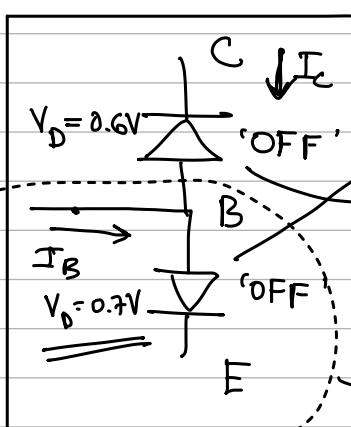


Consequence :

Input circuit current cannot be nonzero

if BE OFF.


$$\therefore I_B = 0, I_C = 0, I_E = 0$$

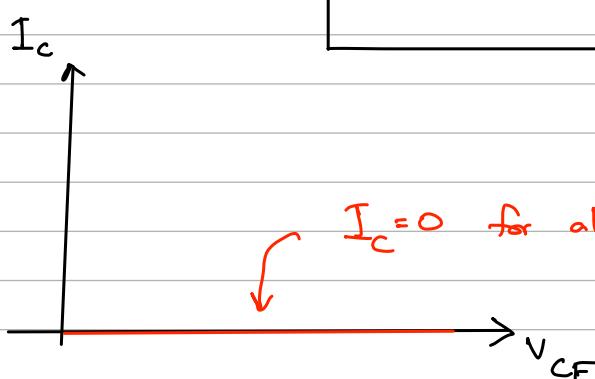

$I_c = 0$  for all  $V_{CE}$  in this mode

'open ckt'

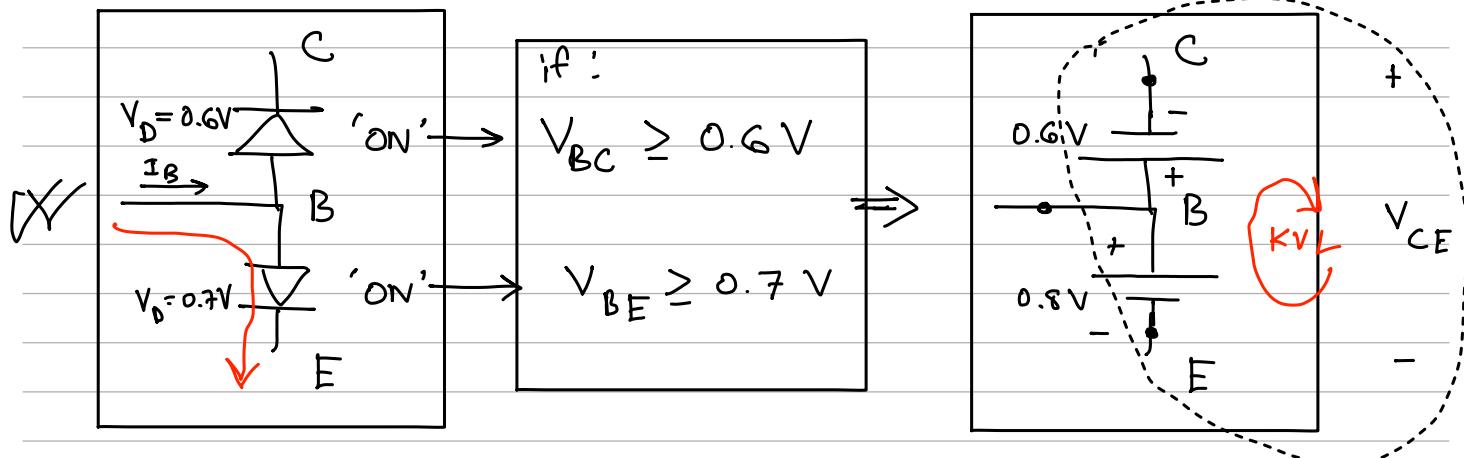
② Saturation : BE and BC junction forward biased and  $I_B$  very high, so consider  $V_{BE} \approx 0.8V$



If in saturation, then :

$$\rightarrow V_{CE} = 0.2V$$

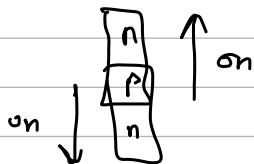$\rightarrow$  Both junction forward biased




$$-V_{BE} + V_{BC} + V_{CE} = 0$$


$$\text{or, } V_{CE} = V_{BE} - V_{BC}$$

$$= 0.8 - 0.6$$

$$= 0.2V$$

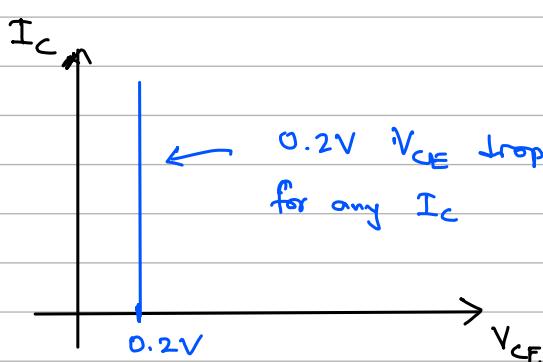

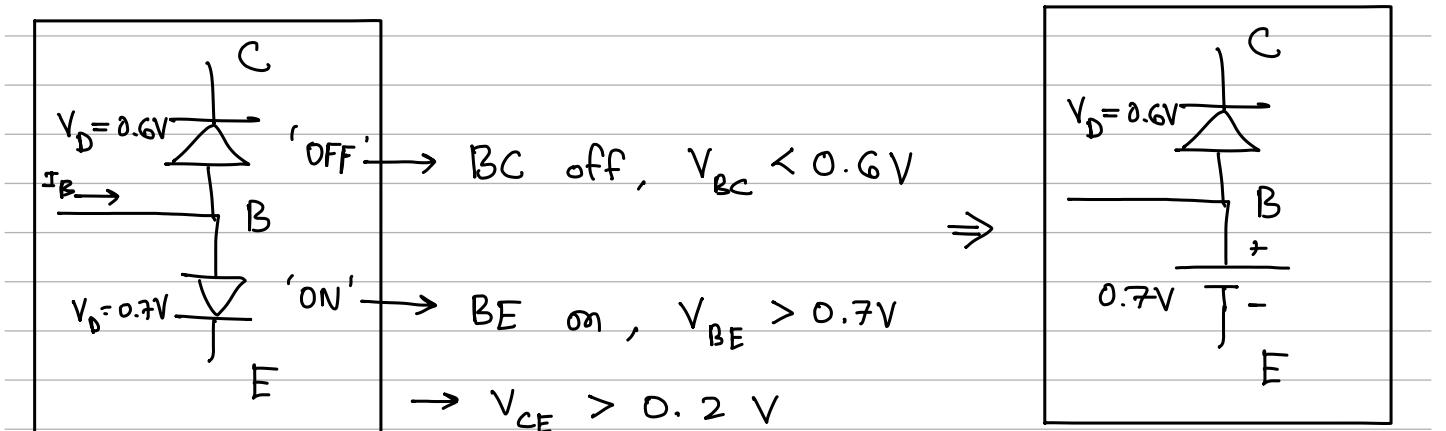③ Active :  $I_C$  current saturates (and only depends on  $I_B$ ).



BC is not 'open ckt'-ed. In this config., huge  $I_C$  flows from C to B that depends only on  $I_B$ .

W

$$I_C = \beta I_B \quad \text{where } \beta = \text{constant that is commonly called current gain} \quad \text{common values}$$

$$\begin{aligned} I_E &= I_B + I_C \quad \text{②} \\ &= I_B + \beta I_B \\ &= (\beta + 1) I_B \end{aligned}$$

100 150

W

$$I_B = \frac{1}{\beta} I_C \quad \text{③} \Rightarrow I_E = \frac{1}{\beta} I_C + I_C = I_C \left( \frac{1}{\beta} + 1 \right) = I_C \left( \frac{\beta + 1}{\beta} \right)$$

∴  $I_C = \left( \frac{\beta}{\beta + 1} \right) I_E$

W



$$\Rightarrow I_C = \alpha I_E$$

$$I_C = \beta I_B$$


current gain [ collector-base ]

current gain [ collector-emitter ]

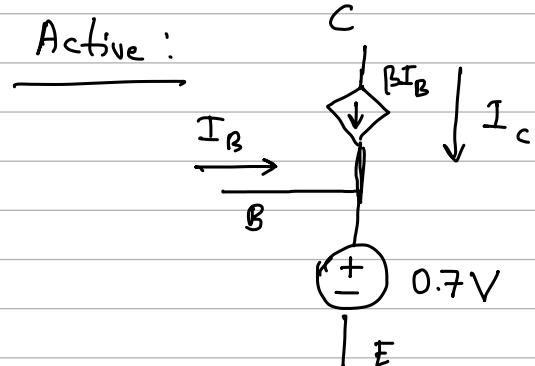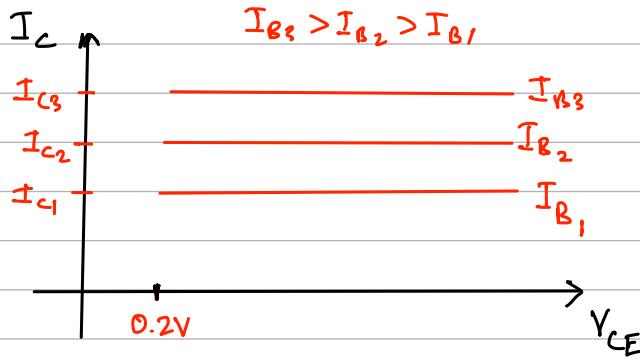
→ Behaves like a current source depending on input current  $I_B$ .



Cutoff :

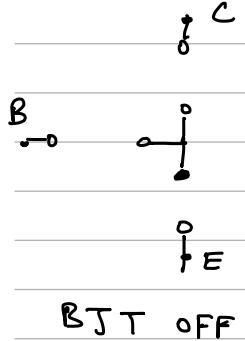


Saturation :

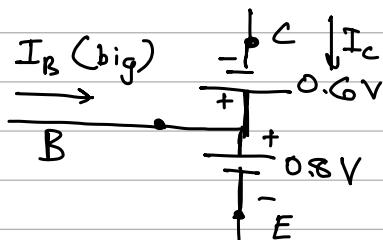

W

Active :

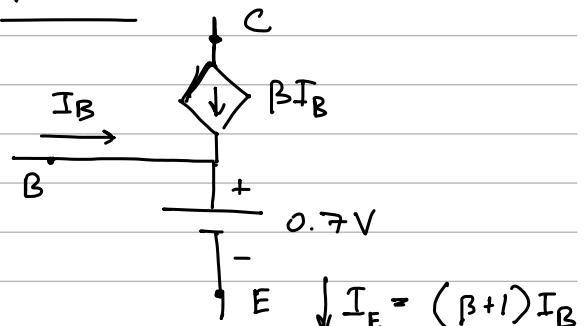


## Method of Assumed State :

- ① Assume  $\begin{cases} \text{Active } [V_{BE} = 0.7V, I_c = \beta I_B] \\ \text{Saturation } [V_{BE} = 0.8V, V_{BC} = 0.6V, V_{CE} = 0.2V] \\ \text{Cutoff } [I_B = I_c = I_E = 0] \end{cases}$

- ② Solve  $[KCL, KVL, \text{node}]$

- ③ Verify  $\begin{cases} \text{Active } [V_{CE} > 0.2V] \\ \text{Saturation } \left[ \frac{I_c}{I_B} < \beta \right] \\ \text{Cutoff } [V_{BE} < 0.7V, \text{ and } V_{BC} < 0.6V] \end{cases}$

Ex - 1 :

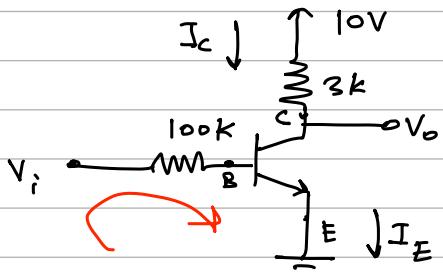


Find  $V_o$  for  $V_i = 1V$

$$\beta = 100$$

Assume : Active - ①  $V_{BE} = 0.7V$

$$② I_c = \beta I_B$$

Solve :

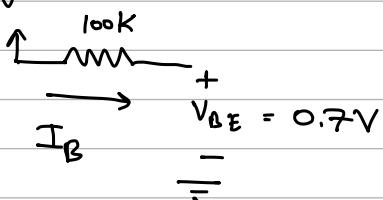

$$I_c = \beta I_B$$

$$= 100 \times 0.003 \text{ mA}$$

$$= 0.3 \text{ mA}$$

$$I_E = I_B + I_c = (\beta + 1) I_B$$

$$= 0.303 \text{ mA}$$


$$\Rightarrow I_B = \frac{1 - 0.7}{100k} = 0.003 \text{ mA}$$

$V_o = V_C$  here.

KCL

$$I_c \times 3k = 10 - V_c$$

$$\text{or, } V_c = 10 - I_c \times 3k$$

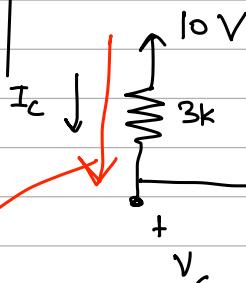

$$V_o = 10 - I_c \times 3k$$

$$= 10 - 0.3 \times 3$$

$$= 10 - 0.9$$

$$= 9.1 \text{ V}$$


$$V_C = 9.1 \text{ V}, V_E = 0, V_B = V_{BE} + V_E = 0.7 \text{ V}$$

Verify :

$$V_{CE} = V_C - V_E = 9.1 - 0 = 9.1 \text{ V} > 0.2 \text{ V}.$$

∴ Correct assumption


Ex - 2 :

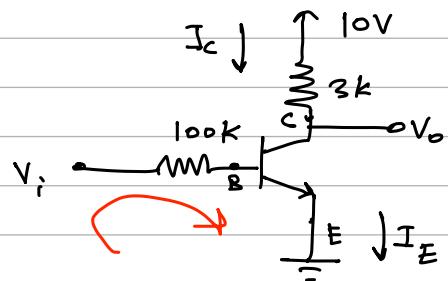

Find  $V_o$  for  $v_i = 5 \text{ V}$

$$\beta = 100$$

Assume : Active

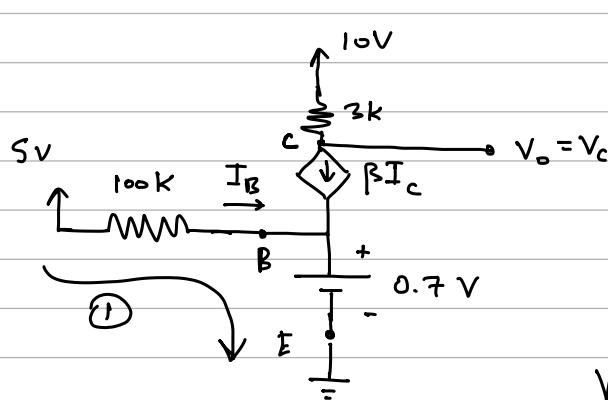

$$\textcircled{1} \rightarrow 100 \times I_B + 0.7 = 5 - 0$$

$$I_B = \frac{5 - 0.7}{100} = 0.013 \text{ mA}$$

$$I_C = \beta \times I_B = 100 \times 0.013 = 1.3 \text{ mA}$$


$$V_C = 10 - I_C \times 3k = -2.9 \text{ V}$$

$$V_E = 0 \text{ V}$$

$$V_{CE} = V_C - V_E = -2.9 < 0.2 \text{ V}$$

∴ Assumption wrong! Not in active state

Saturation :

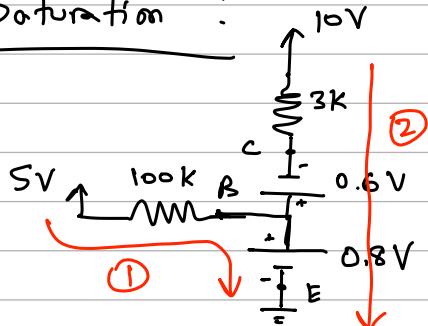

$$\textcircled{1} \rightarrow 100 I_B + 0.8 = 5 - 0$$


$$I_B = \frac{5 - 0.8}{100} = 0.012 \text{ mA}$$

$$\textcircled{2} \rightarrow 3 I_C - (0.6 + 0.8) = 10 - 0$$

$$I_C = \frac{10 - 0.8 + 0.6}{3}$$


$$= \frac{9.8}{3} = 3.29 \text{ mA}$$

Example 2 :

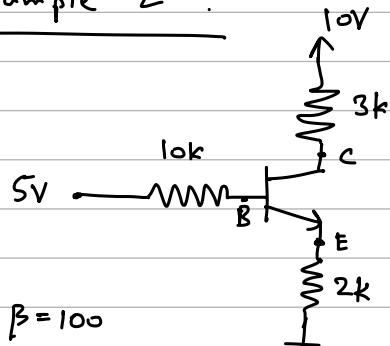

Find  $I_B$ ,  $I_C$ ,  $I_E$ ,  $V_{CE}$

① Assume : Active

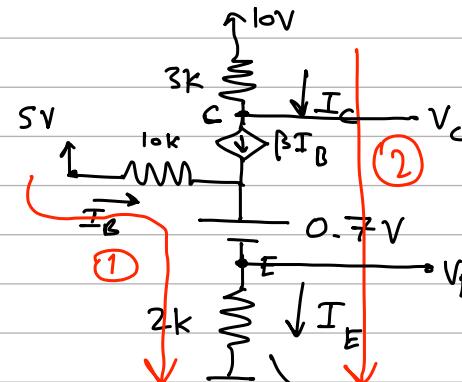

$$I_E = I_B + I_C = I_B + \beta I_B$$

$$I_E = (\beta + 1) I_B$$

$$I_C = \beta I_B$$

$$\textcircled{1} \rightarrow 10I_B + 0.7 + 2I_E = 5 - 0$$


$$\Rightarrow 10I_B + 2 \times 100I_B = 5 - 0.7$$

$$\Rightarrow I_B (210) = 4.3$$

$$I_B = 0.0205 \text{ mA}$$

$$I_C = \beta I_B = 2.05 \text{ mA}$$


$$I_E = I_B + I_C = 2.0705 \text{ mA}$$

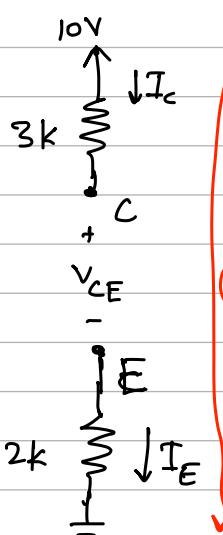

$$3I_C + V_{CE} + 2I_E = 10 - 0$$

$$\begin{aligned} V_{CE} &= 10 - 6.15 - 4.14 \\ &= 10 - 10.3 \\ &= -0.3 < 0.2 \text{ V} \end{aligned}$$

Assumption wrong ! Assume saturation

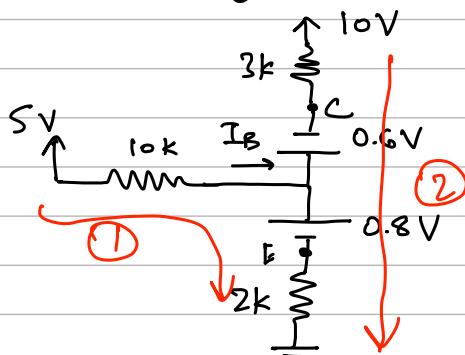

$$\textcircled{1} \rightarrow 10I_B + 0.8 + 2I_E = 5 - 0$$

but,  $I_C \neq \beta I_B$ ,  $I_E \neq (\beta + 1) I_B$   
[not in active]

In saturation,  $I_C \approx I_E$  :  $\textcircled{2} \rightarrow 3I_C - 0.6 + 0.8 + 2I_E = 10 - 0$   
 $\frac{d}{d} \quad \approx I_C$   
(approx.)

$$\Rightarrow 5I_C = 10 - 0.2$$

$$I_C = 1.96 \text{ mA}$$

$$\textcircled{1} \rightarrow 10I_B = 5 - 0.8 - 2 \times 1.96 = 0.28 \Rightarrow I_B = 0.028 \text{ mA}$$

Without approx:

$$\textcircled{1} \rightarrow 10I_B + 0I_C + 2I_E = 9.2$$

$$\textcircled{2} \rightarrow 0I_B + 3I_C + 2I_E = 9.8$$

$$-I_B + I_C + I_E = 0$$

$$I_E = I_B + I_C$$


$$\Rightarrow -I_B - I_C + I_E = 0$$

3 eq's, 3 unknowns  $\rightarrow$  solve

$$I_B = 0.03 \text{ mA}, I_C = 1.95 \text{ mA}, I_E = 1.98 \text{ mA}$$

Mosfet:

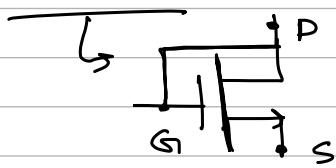(Neaman) n-MOSFET ch3  $\rightarrow$  circuit solve using MAS



$\hookrightarrow$  we use  $k = k'_n \frac{W}{L}$ ,

neaman uses  $k = \frac{k'_n}{2} \frac{W}{L}$

Selva Smith — n MOSFET ch5

BJT:

(Neaman) - BJT ch5  $\rightarrow$  circuit solve using MAS  
(npn)

Selva — BJT ch6