

# CSE251: Electronic Devices and Circuits

Lecture 13 – Zener Diodes

**Prepared By:**

**Shadman Shahid (HAD)**

Lecturer, Department of Computer Science and Engineering, School of Data and Sciences, BRAC University


Email: [ext.shadman.shahid@bracu.ac.bd](mailto:ext.shadman.shahid@bracu.ac.bd)

# Outline

- Voltage Regulators
- Forward Bias (FB) Diodes as Voltage Regulators
- Drawbacks of (FB) Diodes as Voltage Regulators
- Diode Breakdown Region
- Zener Diodes – Introduction and analysis
- Zener Diodes as Voltage Regulators
- Practice Problems
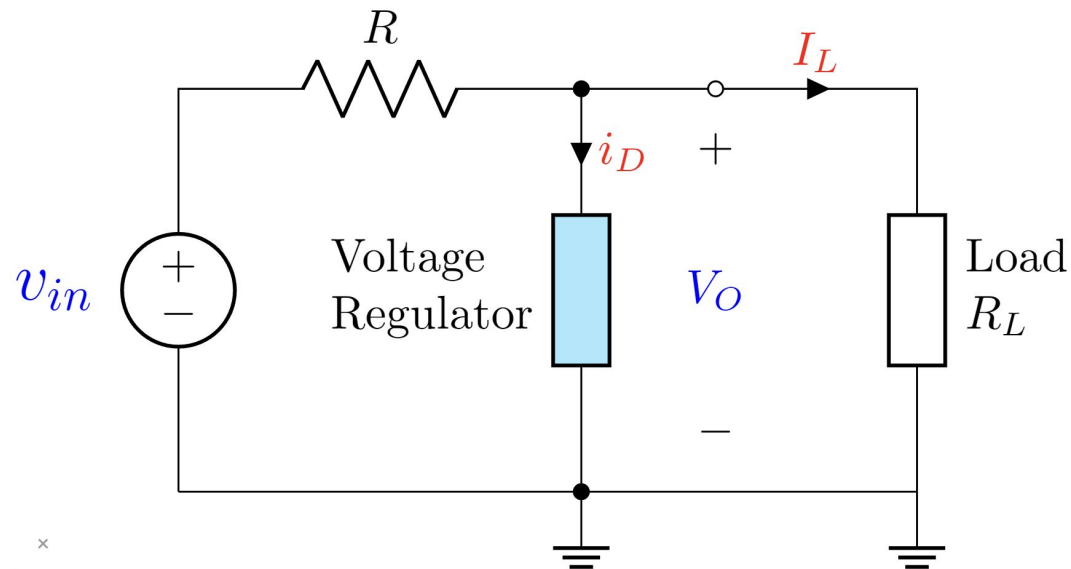
# Voltage Regulators

- **Voltage Regulation** is the measure of how well a system can provide near constant voltage.
- **Voltage Regulators** provide steady voltage independent of how much power is drawn from the power source





**Voltage Regulator:**

Tries to maintain a voltage constant at  $V_O$
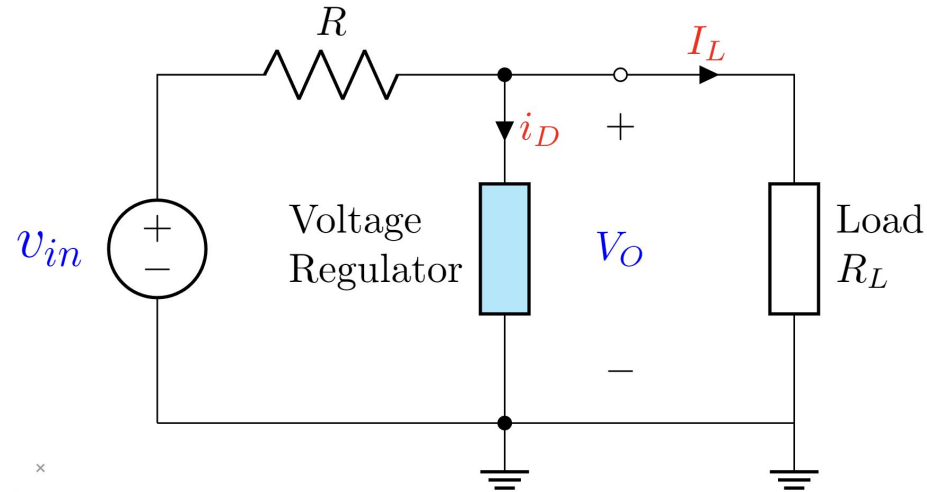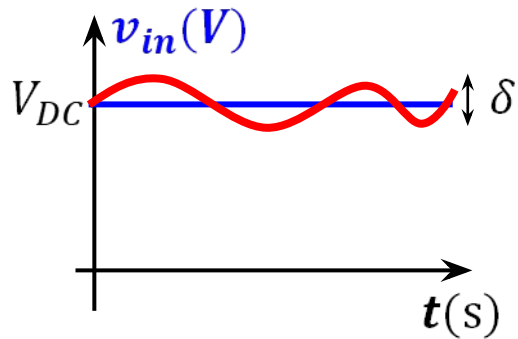
# Voltage Regulators

Let's assume that  $v_{in}$  is not a perfect DC source. It supplies a voltage of  $(V_{DC} \pm \delta)$  V



## Voltage Regulator:

Tries to maintain a voltage constant at  $V_O$  even when  $v_{in}$  is varying.

**Variables:**  $V_O$  should remain constant irrespective of the changes in the following quantities:

1. **Input Voltage:**  $v_{in}$


2. **Load Current:**  $I_L$

3. **VR current:**  $i_D$
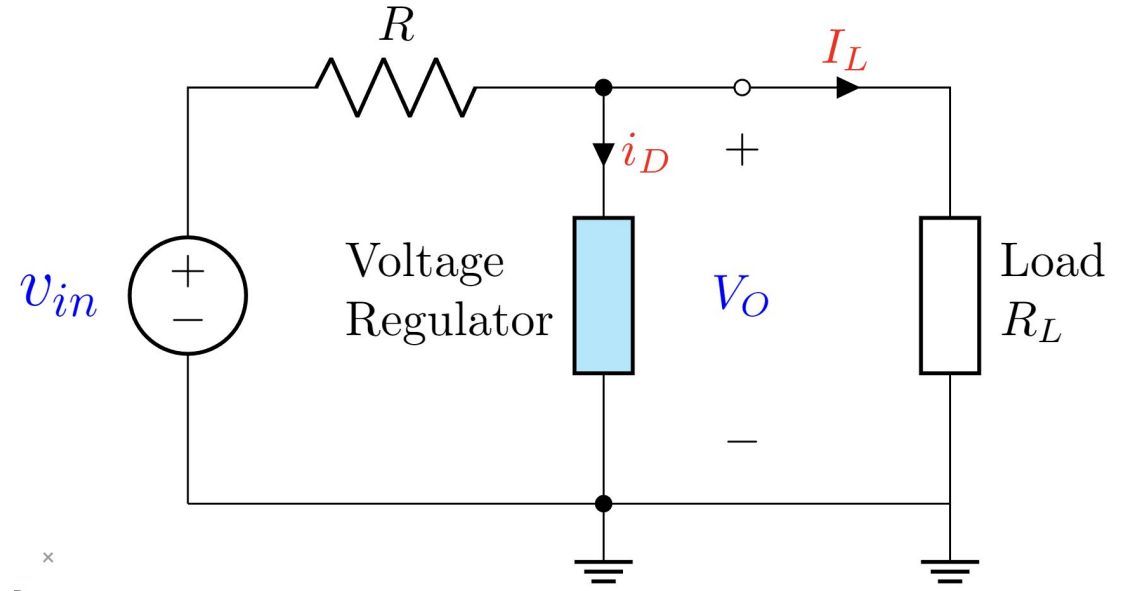
# Voltage Regulator – Worst Case Scenario

**Worst Case Scenario** occurs when the three variables ( $v_{in}$ ,  $I_L$ , and  $i_D$ ) change in such a way, such that maintaining  $V_O$  constant requires the most power (current) from the **Voltage Regulator**.

The **Voltage regulator** is at its maximum capacity at the worst case.




**Worst Case Scenario occurs when**




1. Input Voltage is minimum:  $v_{in}(\min)$
2. Load Current is maximum:  $I_L(\max)$
3. VR current minimum:  $i_D(\min)$
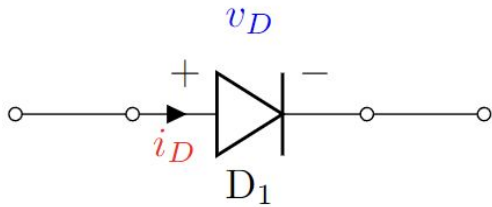
# Diodes as Voltage Regulators

**Diodes** have (IV) characteristics that makes them ideal for voltage regulation.




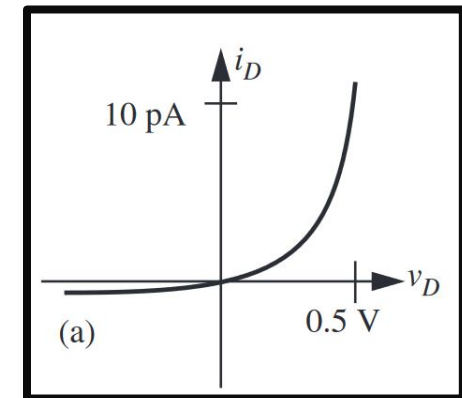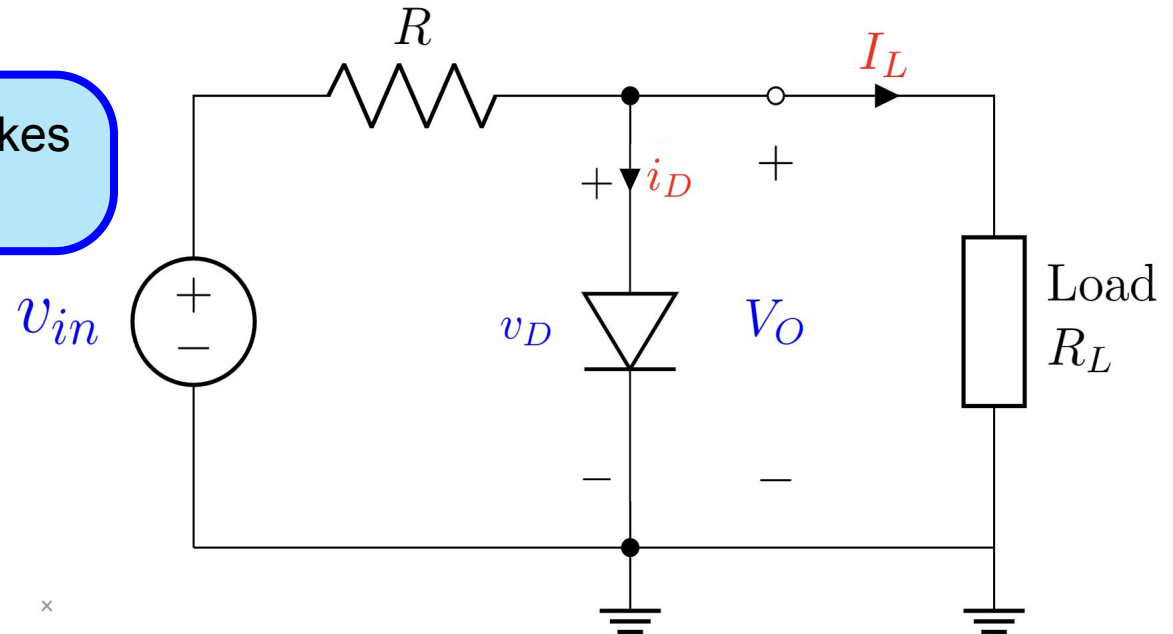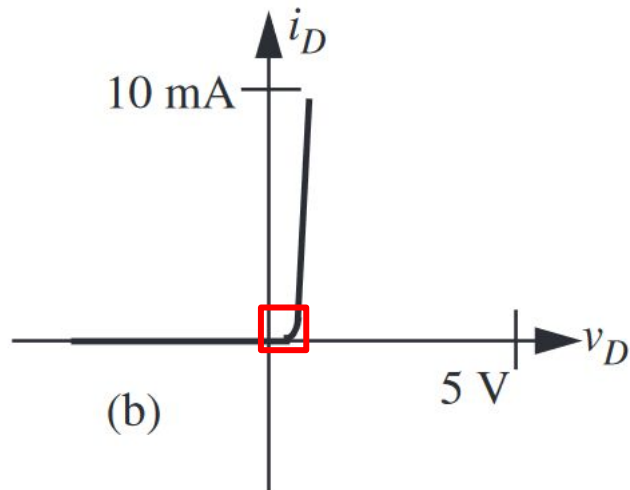**Exponential IV characteristics of diodes**




# Diodes Revisited


Physical Schematic:

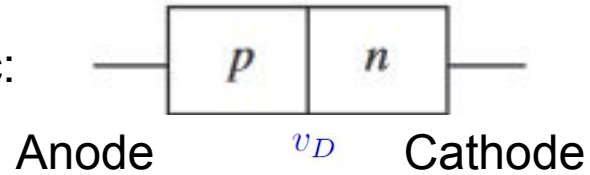

Circuit Schematic:

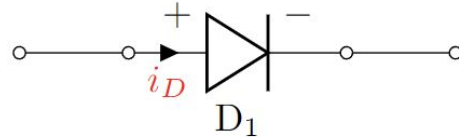

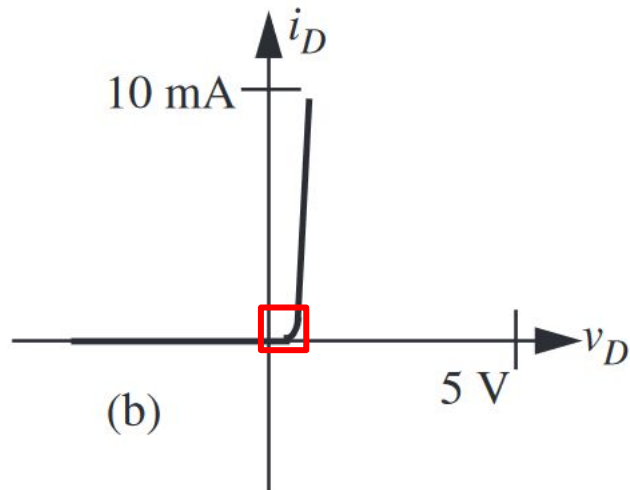**Exponential IV characteristics of diodes**




## Forward Bias

Net positive Voltage across  $p - n$  junction
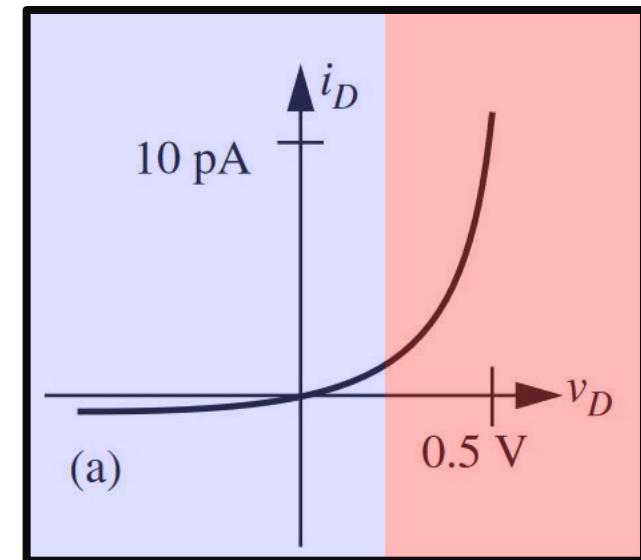
## Reverse Bias

Net negative Voltage across  $p - n$  junction



# Diodes Revisited

1. Ideal Diode Model:
2. Constant Voltage Drop (CVD) Model:
3. Voltage Source in Series with Resistor Model (CVD+R) Model
4. Exponential Model:


$v_D$ : Total Voltage Across diode  
 $v_d$ : AC component of the Voltage  
 $V_d$ : DC component of Voltage

---

$V_{D0}$ : Diode Cut-off voltage

---

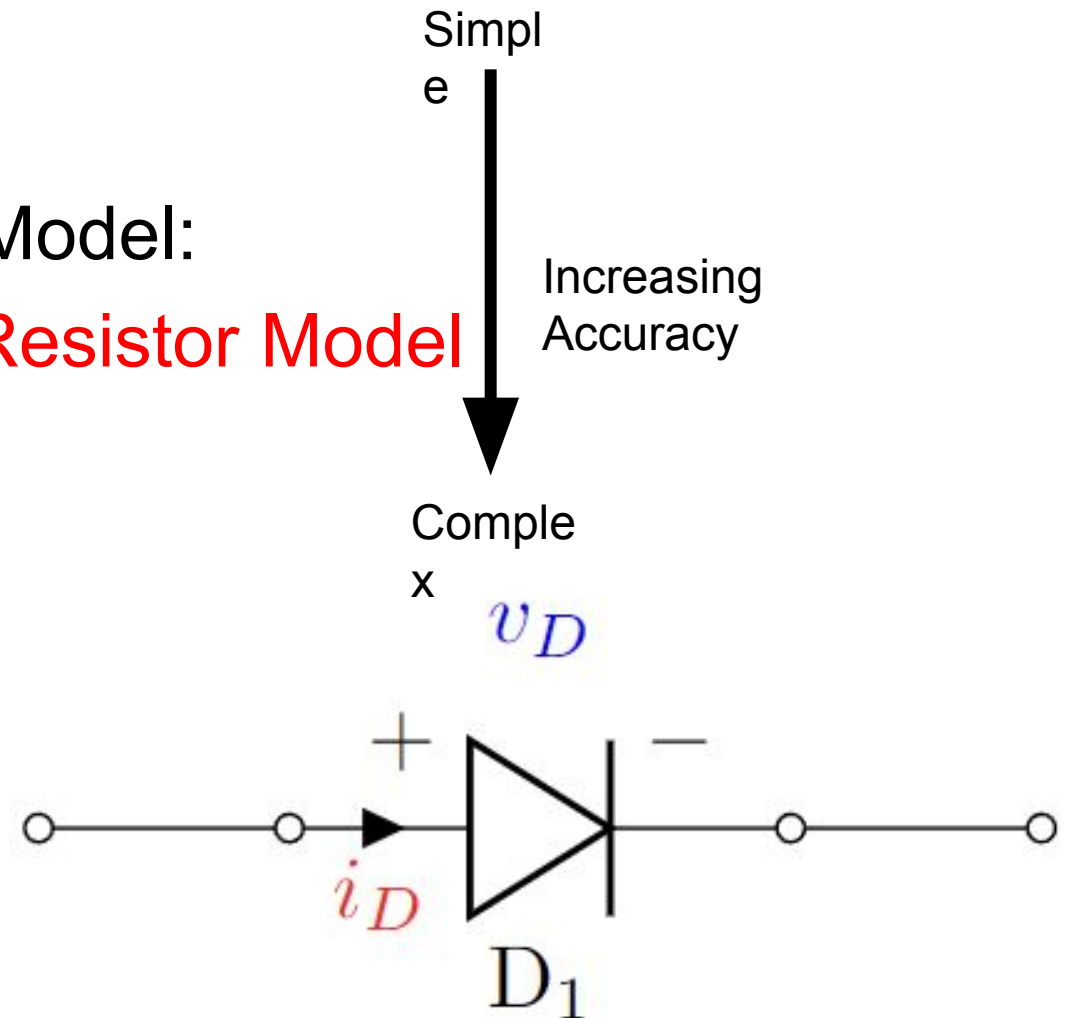
$i_D$ : Total current through diode (Anode to Cathode)






# Diode Models

## 1. Ideal Diode Model:

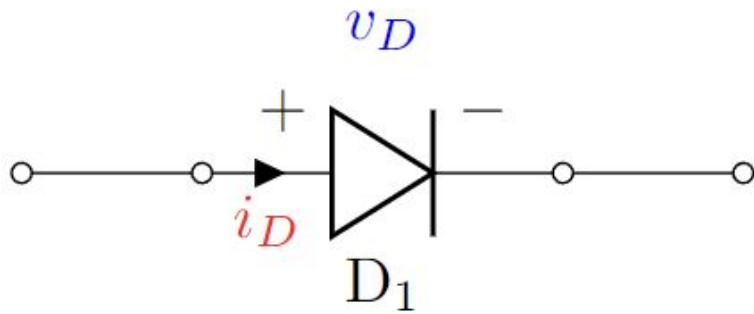


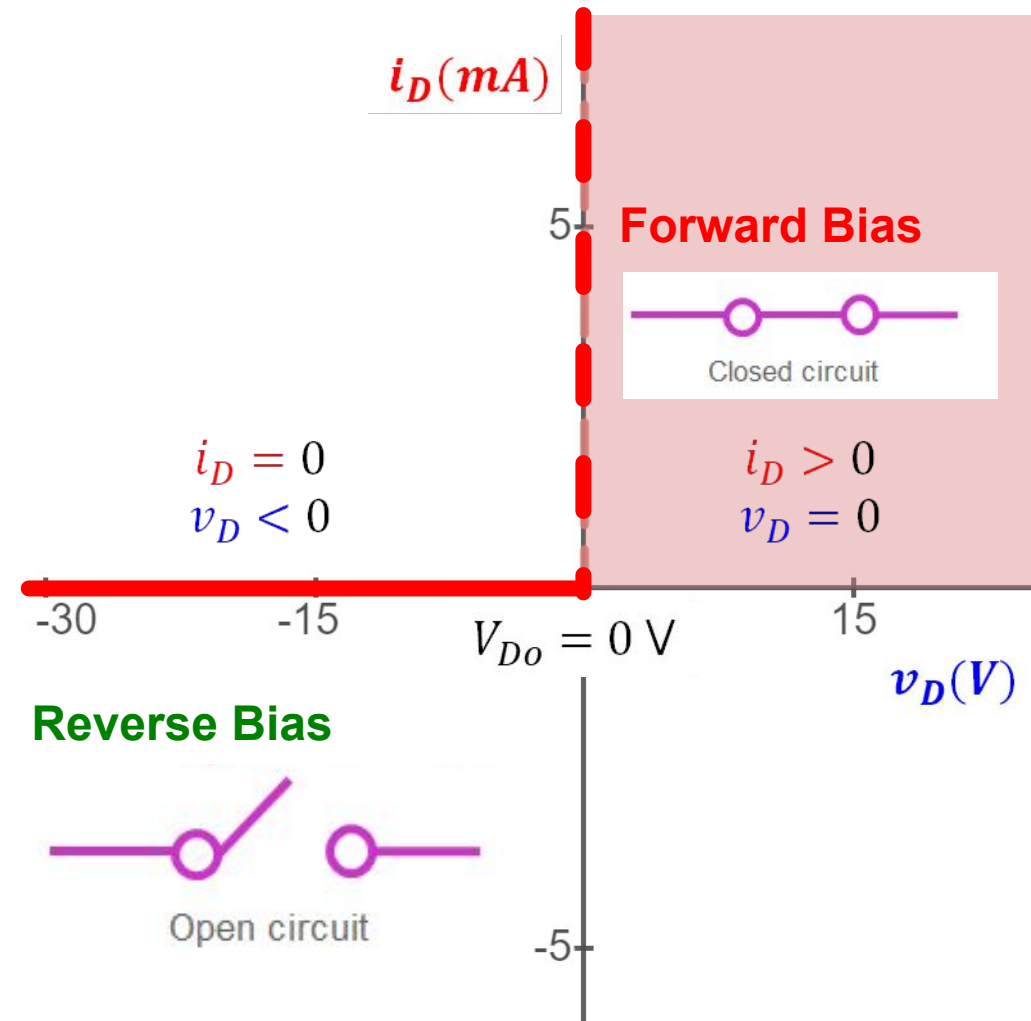Not suitable as  
**VOLTAGE  
REGULATOR**




# Diode Models

## 2. Constant Voltage Drop (CVD) Model:

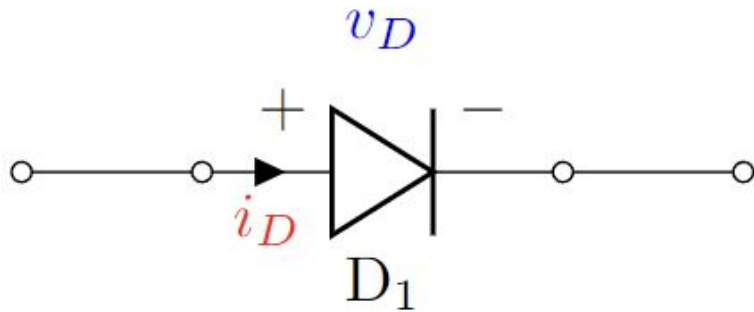

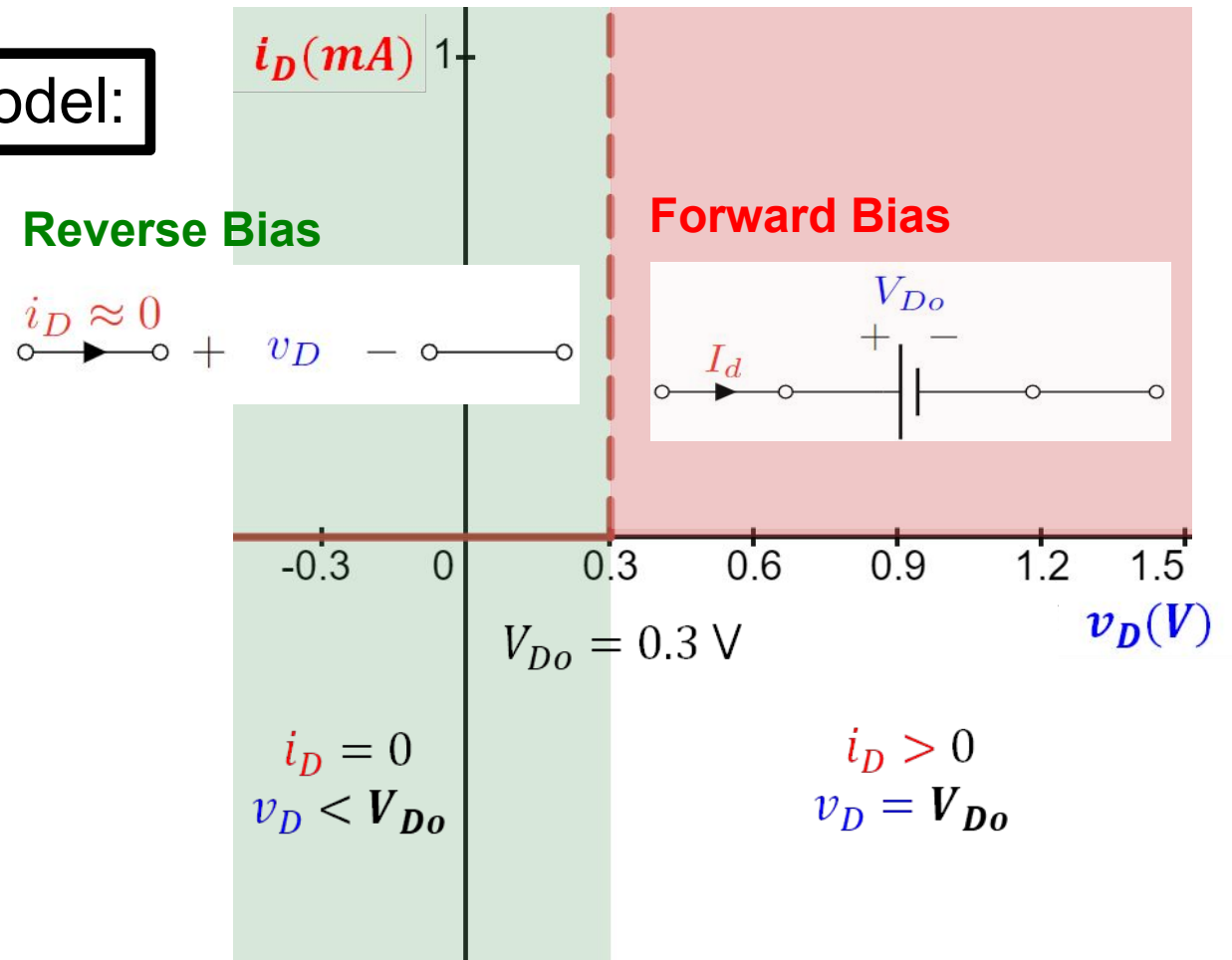Suitable as  
**VOLTAGE  
REGULATOR ?**  
Maybe!



# Diode Models


## 2. Constant Voltage Drop (CVD) Model:

### Reverse Bias




$$\begin{aligned} i_D &= 0 & y &= 0 \\ v_D &< V_{Do} & x &< V_{Do} \end{aligned}$$

### Forward Bias

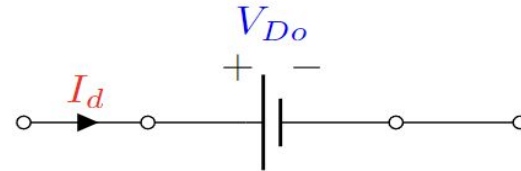
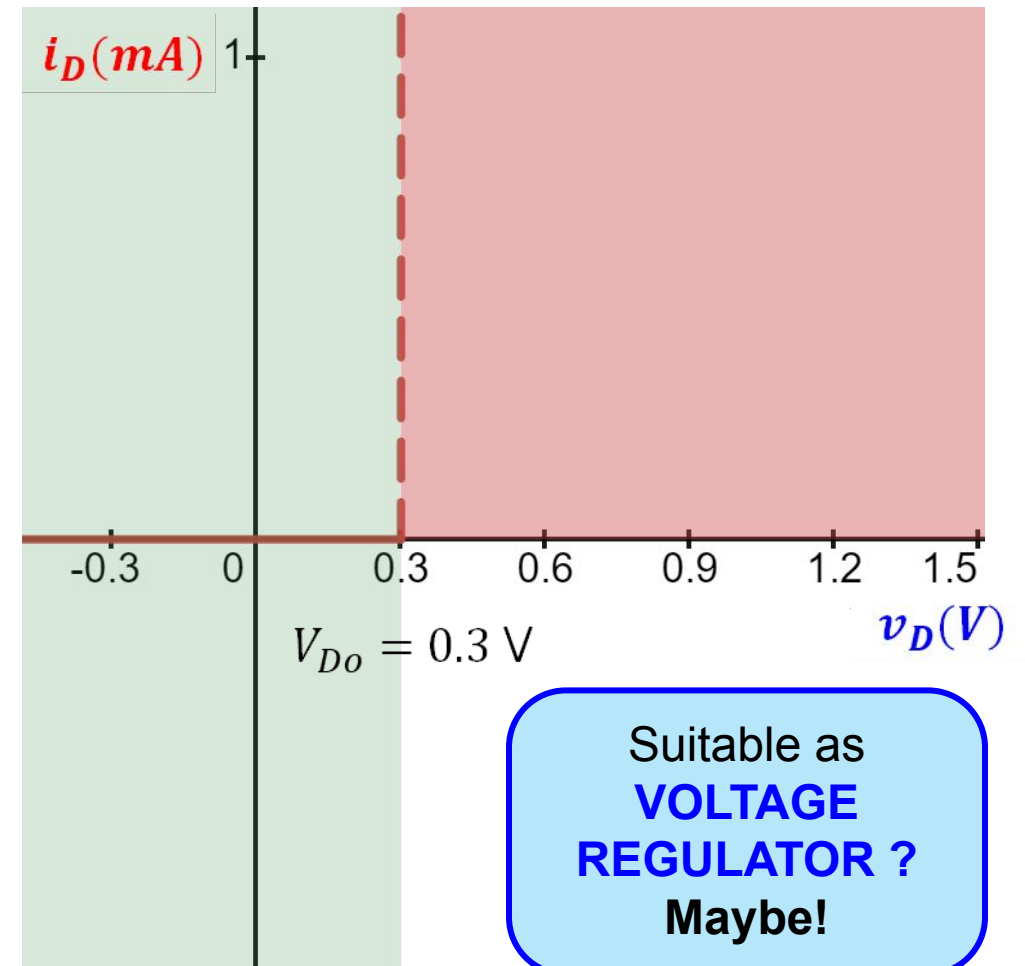
$$\begin{aligned} i_D &> 0 & y &> 0 \\ v_D &= V_{Do} & x &= V_{Do} \end{aligned}$$



# Practice Problem 1


The circuit of the adjacent **Figure** is specified to have the following parameters. The supply voltage  $V_{in}$  is nominally 3 V but can vary by  $\pm 0.1$  V.  $R_L$  can draw a maximum of 10 mA and  $i_D(\text{min}) = 1$  mA.

What is  $R$  for worst case scenario if  $v_D$  ( $V_O$ ) is to be regulated at 0.6 V? [Since  $r_o$  is not provided, you can consider the CVD model.]

**Solution:**

**Worst Case Scenario occurs when**

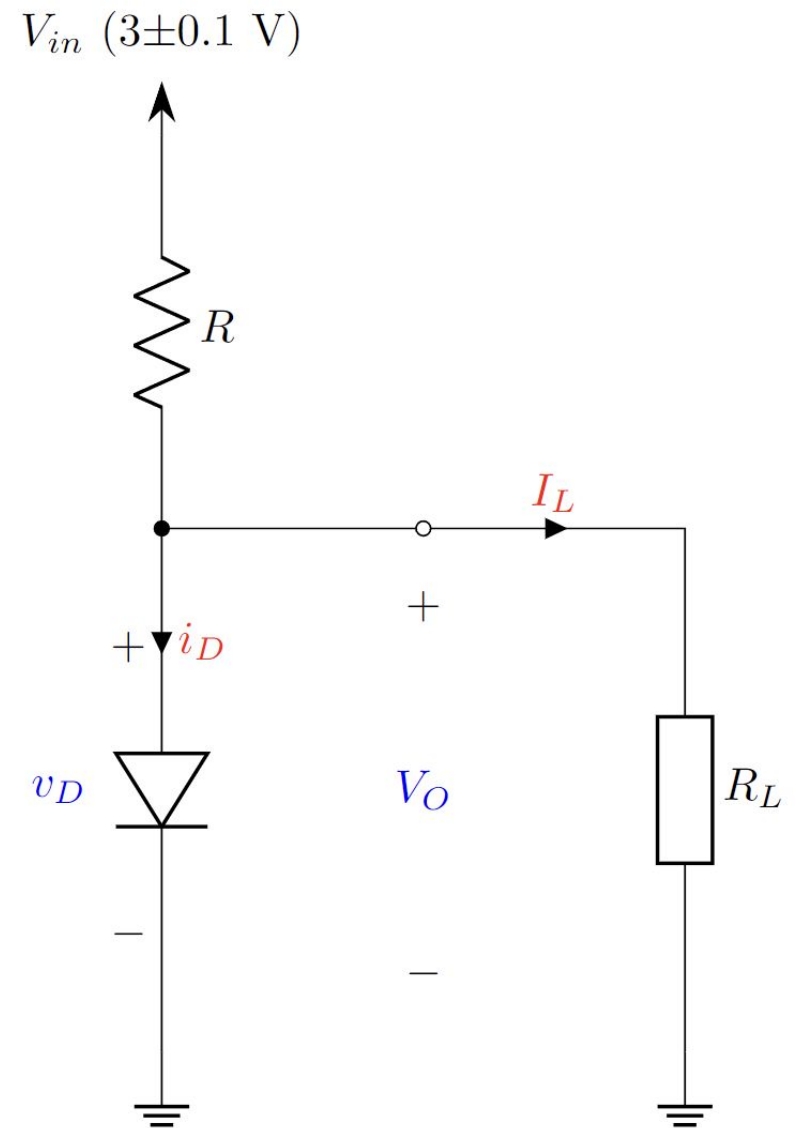1.  $v_{in}(\text{min}) = 3 - 0.1 \text{ V} = 2.9 \text{ V}$
2.  $I_L(\text{max}) = 10 \text{ mA}$
3.  $i_D(\text{min}) = 1 \text{ mA}$




# Practice Problem 1

The circuit of the adjacent **Figure** is specified to have the following parameters. The supply voltage  $V_{in}$  is nominally 3 V but can vary by  $\pm 0.1$  V.  $R_L$  can draw a maximum of 10 mA and  $i_D(\text{min}) = 1$  mA.


What is  $R$  for worst case scenario if  $v_D$  ( $V_O$ ) is to be regulated at 0.6 V? [Since  $r_o$  is not provided, you can consider the CVD model.]

**Solution:**

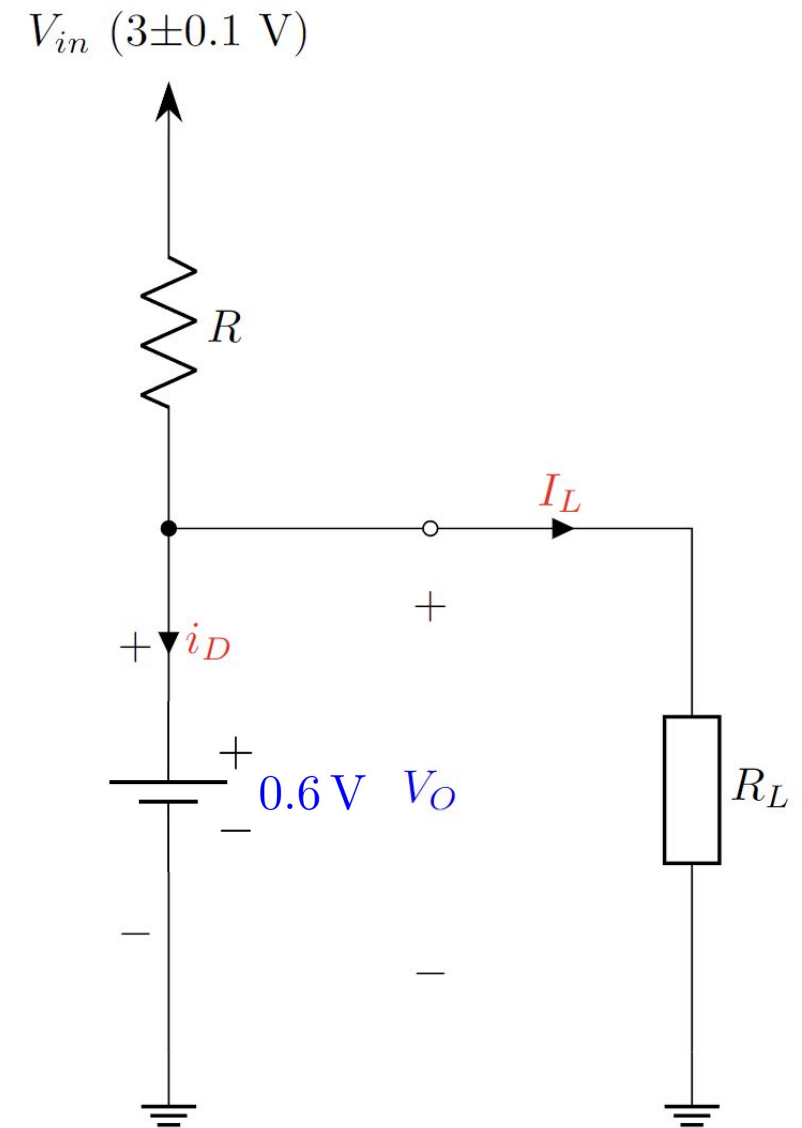
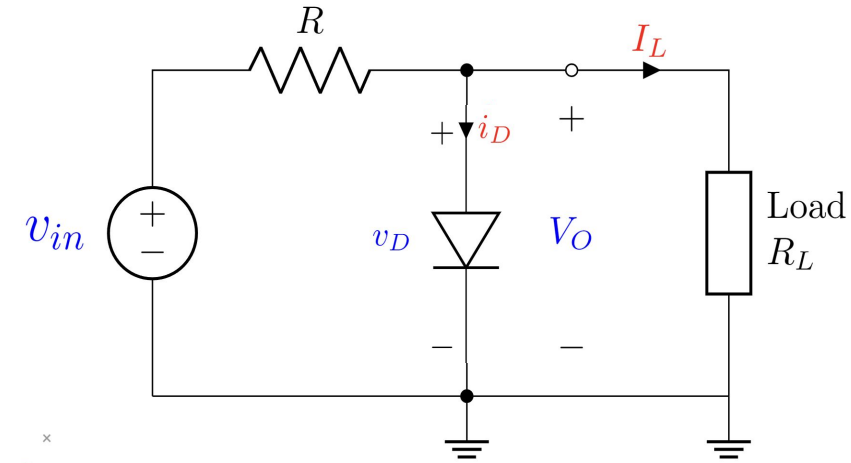
# Drawbacks of Diodes as Voltage Regulators


- Regulation voltage is low:  $\sim V_{DO}$  (0.3 ~ 1 V)
- High  $i_D$  (min)
- $R$  can be low  $\rightarrow$  High power loss


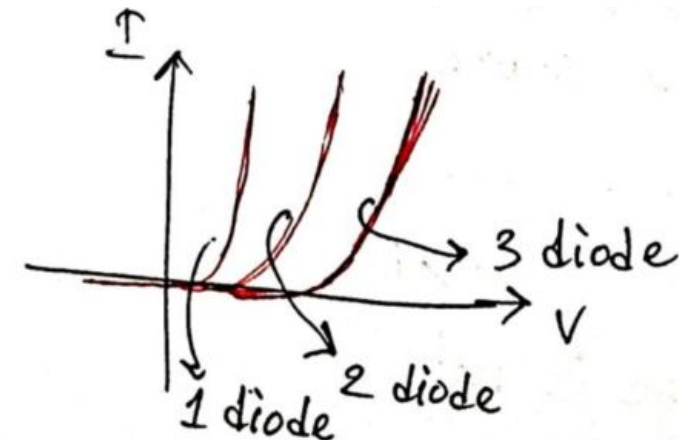
## Possible Solution:


Stacked Diodes in Series: -- Regulation Voltage can be increased to  $n \cdot V_{DO}$  for  $n$  stacked diodes.

However, this can make the diodes deviate more from ideal model. **IV characteristics** become flatter (more lossy).


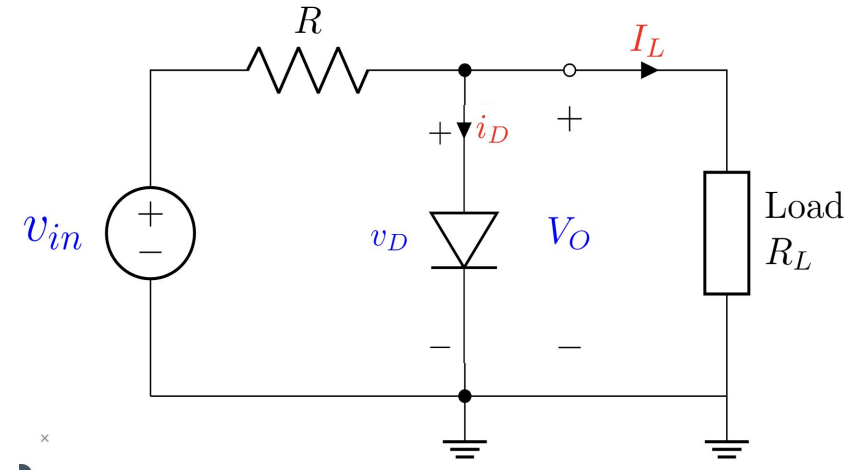
# Drawbacks of Diodes as Voltage Regulators

- Regulation voltage is low:  $\sim V_{DO}$  (0.3 ~ 1 V)
- High  $i_D$  (min)
- $R$  can be low  $\rightarrow$  High power loss



## Better Solution:


Use **Breakdown Region** of diodes as constant voltage source because:

1. **Breakdown Voltage** can be controlled during fabrication
2.  $i_D$  (min) for reverse breakdown is very low!

# Diode Models

4. Exponential model:

The full IV characteristic

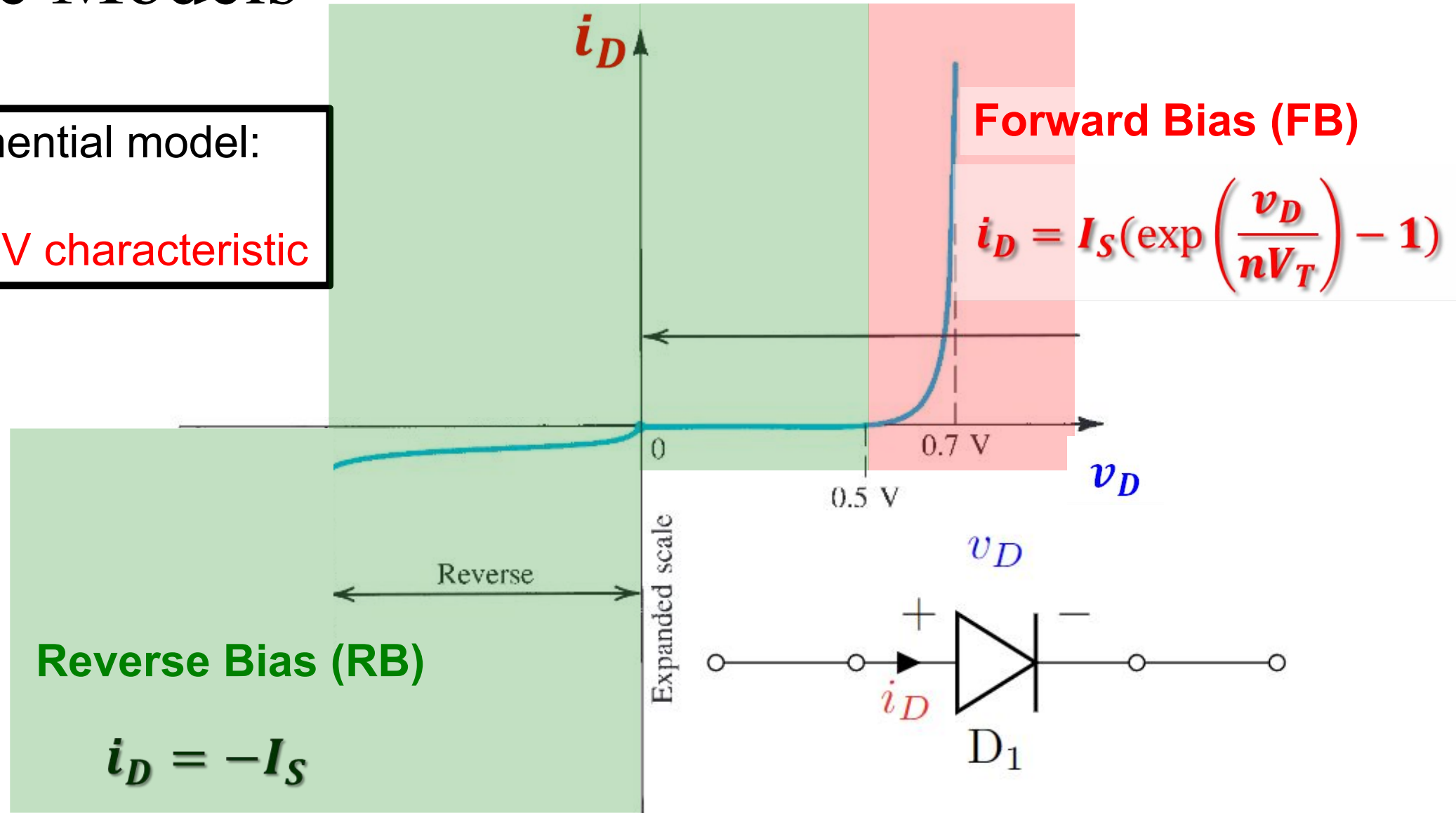




# Diode Models

4. Exponential model:

The full IV characteristic

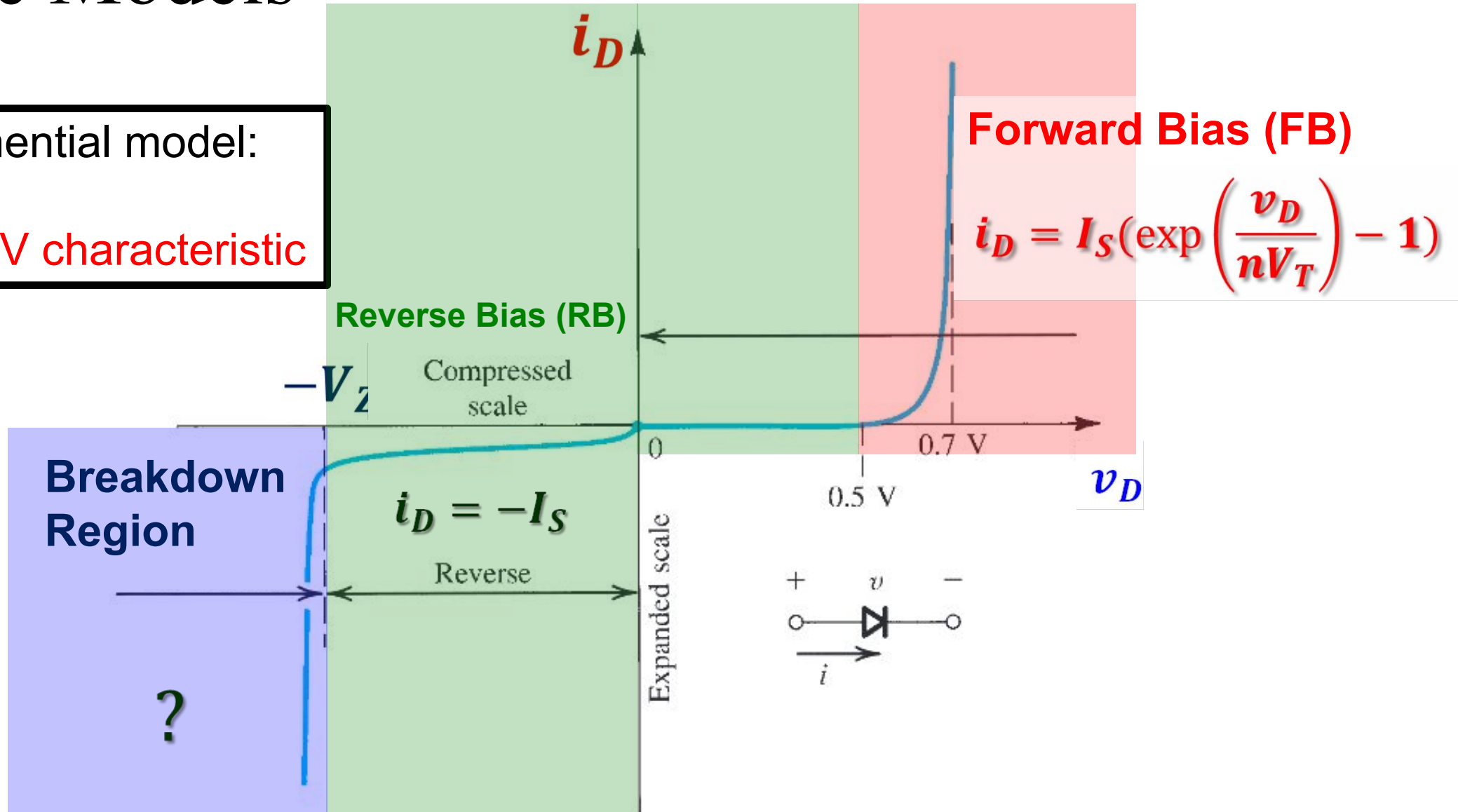


# Diode IV Characteristic

## Reverse Bias (RB)

$i_D = -I_S$   $I_S$  in this case is the reverse leakage current.

$y = -I_S$  For  $v_D < V_{D0}$  there is negligible current flow through the diode.

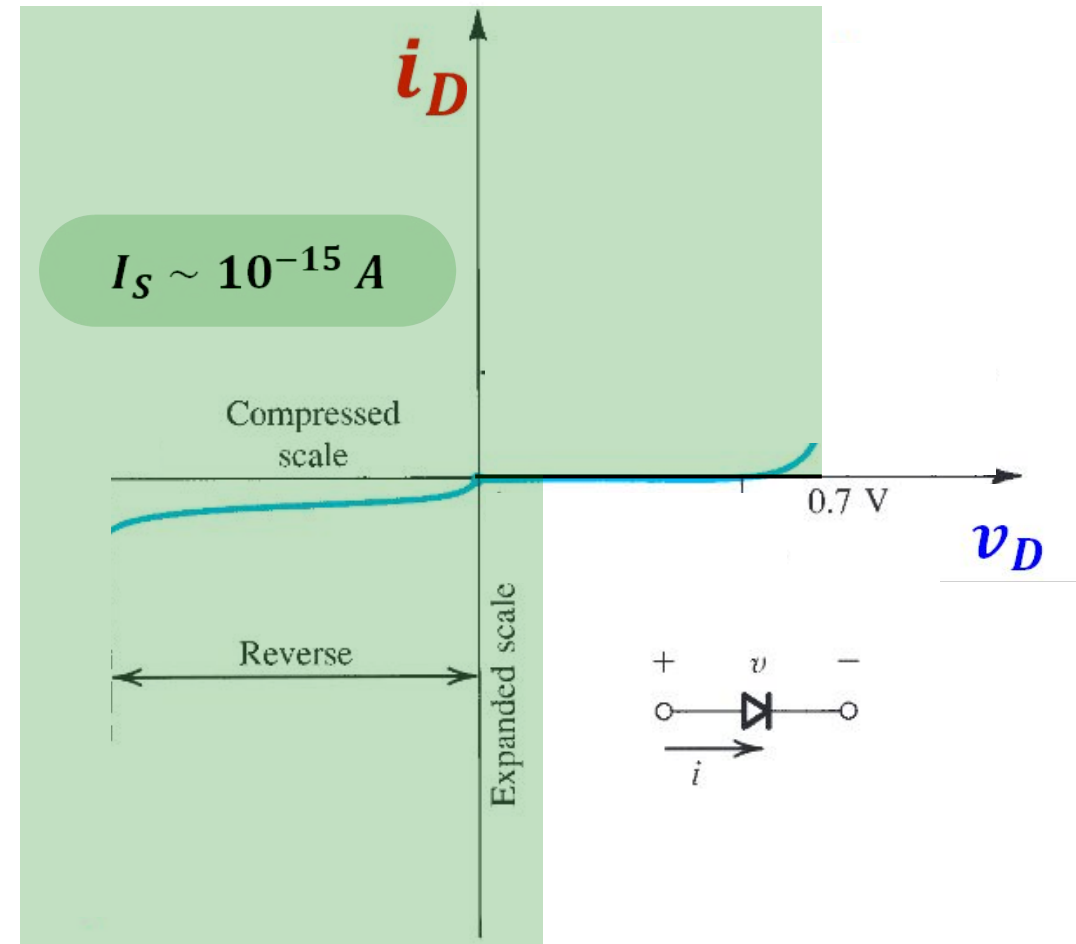Normal diodes cannot tolerate large voltages in reverse bias. **Applying large voltages in reverse bias may damage the diode.**



# Diode IV Characteristic


## Breakdown Region

Normal diodes cannot tolerate large voltages in reverse bias. **Applying large voltages in reverse bias may damage the diode.**

Special classes of diodes exist, that are primed to operate in large reverse bias voltages. These diodes are called
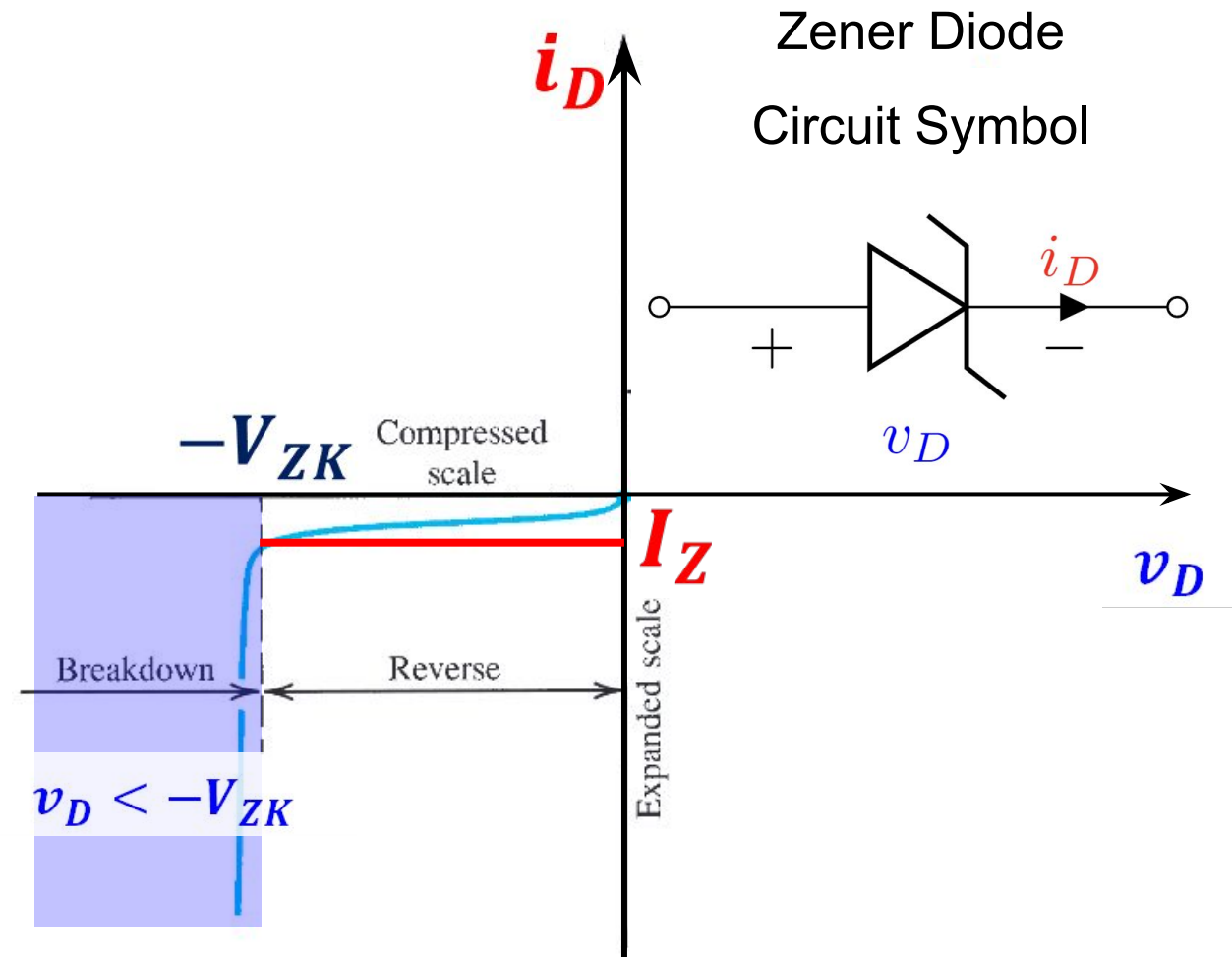
### Zener diodes

In this **Breakdown region**, the diode acts almost like a “**constant voltage source**”.





# Zener Diode IV

## Breakdown Region

**Zener knee voltage ( $-V_{ZK}$ ):** The RB voltage beyond which diode breaks down. The corresponding current is knee current ( $I_{ZK}$ )

For  $v_D < -V_{ZK}$ ,

$$\text{Slope} = \frac{1}{r_z}$$

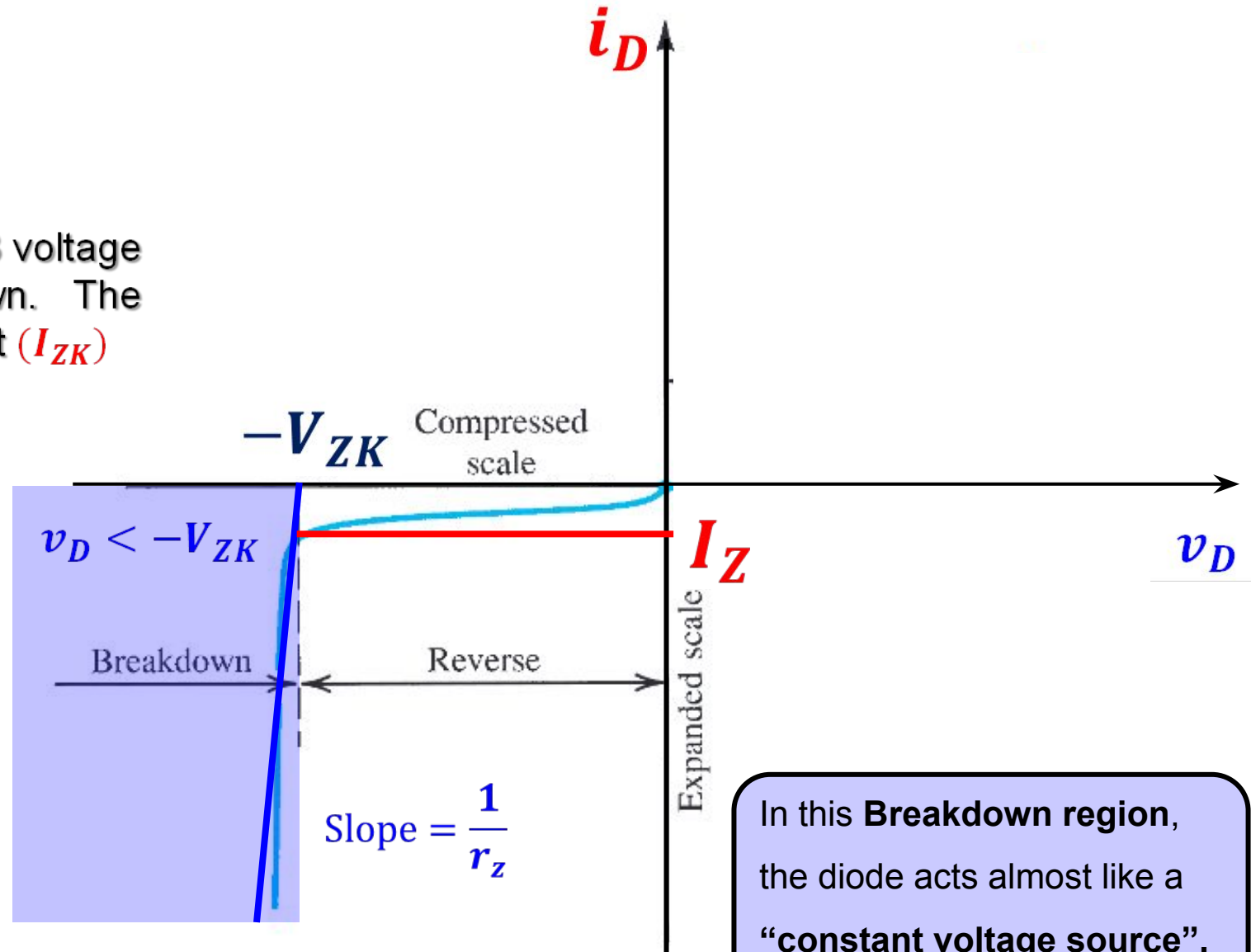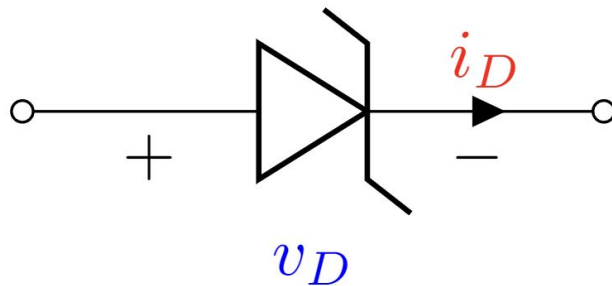

In this **Breakdown** region, the diode acts almost like a "constant voltage source".


# Zener Diode IV

## Breakdown Region


Since this region is like the forward bias region of a normal diode, we invert the signs of voltage and currents across a Zener diode operating at breakdown voltage, to solve Zener diode circuits in a similar way.

For a voltage of  $-V_Z$ , the diode allows a breakdown current of  $-I_Z$ .

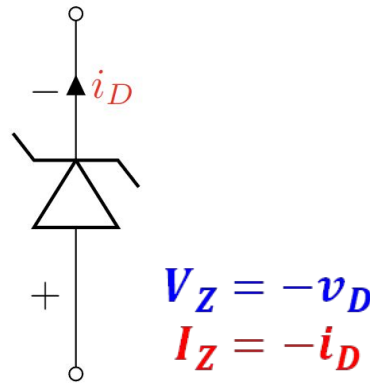The slope at this point of the graph is  $\frac{1}{r_Z}$





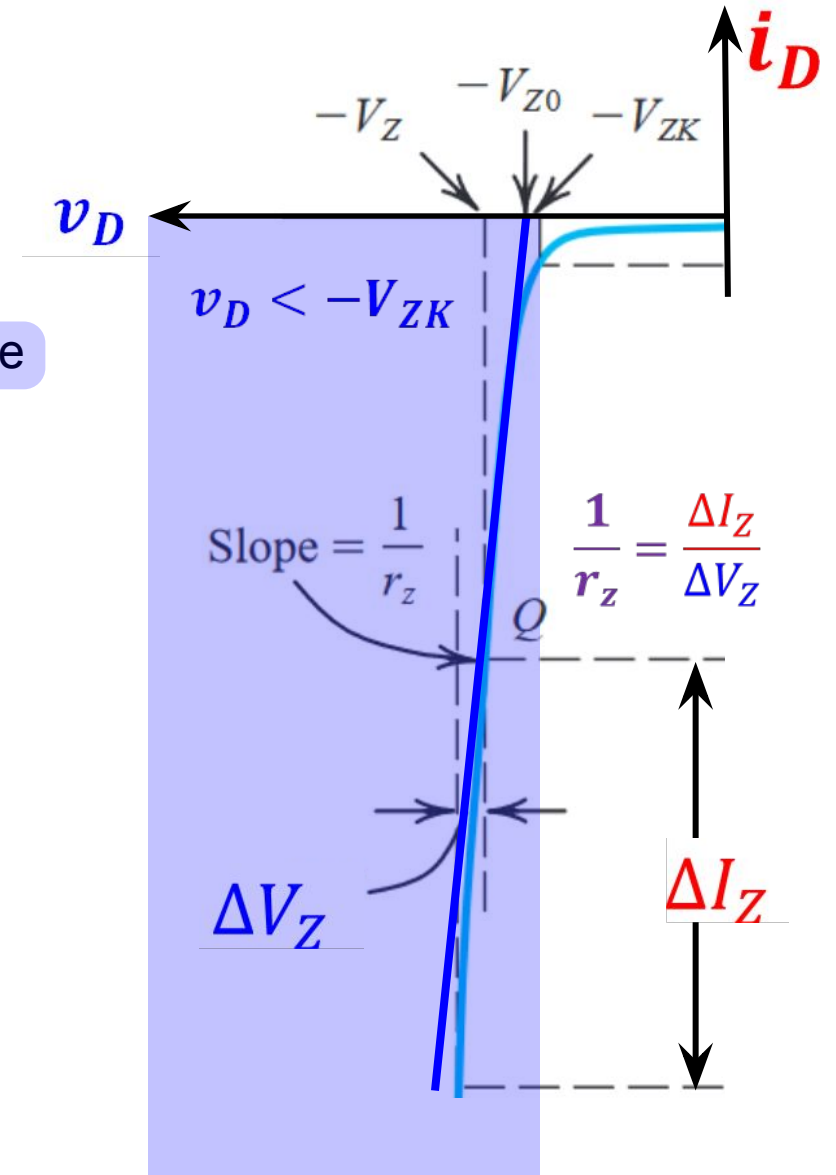
If we extrapolate a straight line from  $(-V_Z, -I_Z)$  point, and extend it towards the  $x$ -axis, ( $i_D = 0$  A), the intersecting point is  $V_{Z0}$ . ( $V_{ZK} \approx V_{Z0}$ )



# Zener Diode IV

**Breakdown Region** ( $V_Z > V_{Z0} \approx V_{ZK}$ )


$$V_Z = V_{Z0} + I_Z r_z$$

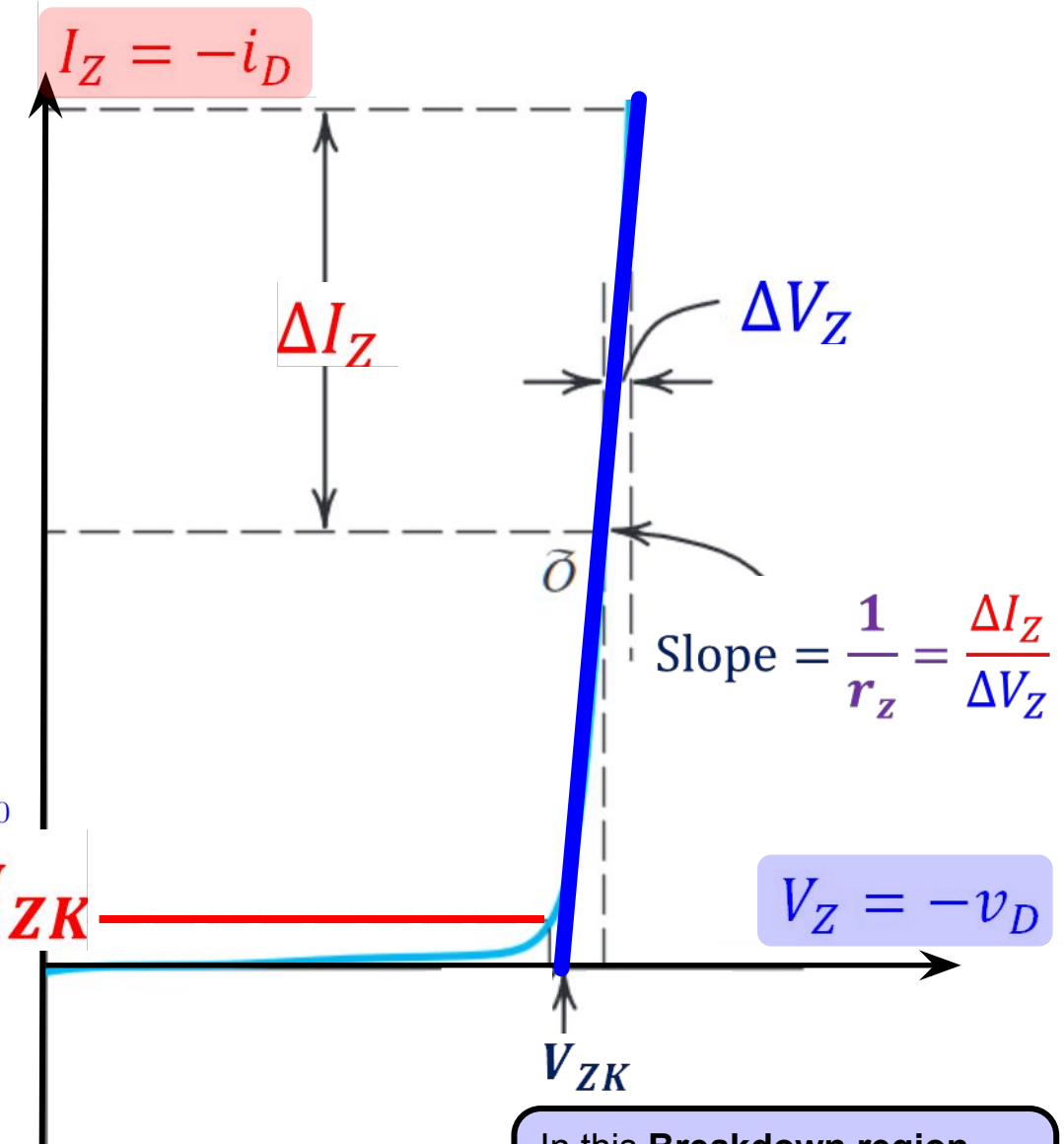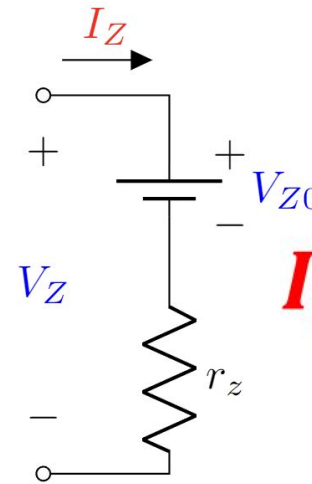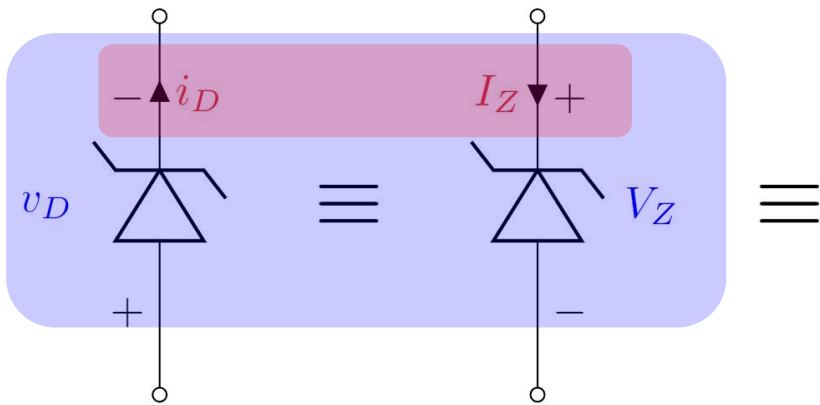

In this **Breakdown region**, the diode acts almost like a “constant voltage source”.

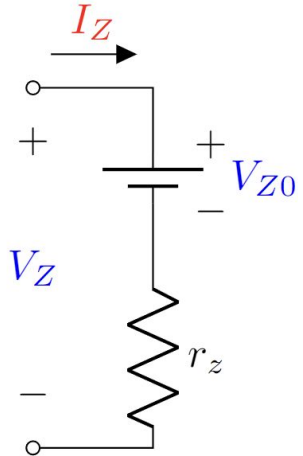
# Zener Diode Breakdown IV Characteristic

**Breakdown Region** ( $V_Z > V_{Z0} \approx V_{ZK}$ )



$$V_Z = V_{Z0} + I_Z r_z$$

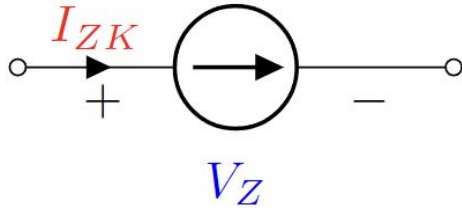
**Reverse Bias Region** ( $V_Z < V_{Z0} \approx V_{ZK}$ )



$$I_Z = I_{ZK}$$

$V_Z$ : Total RB Voltage Across **Zener** diode

$V_{Z0}$ : Zener knee voltage

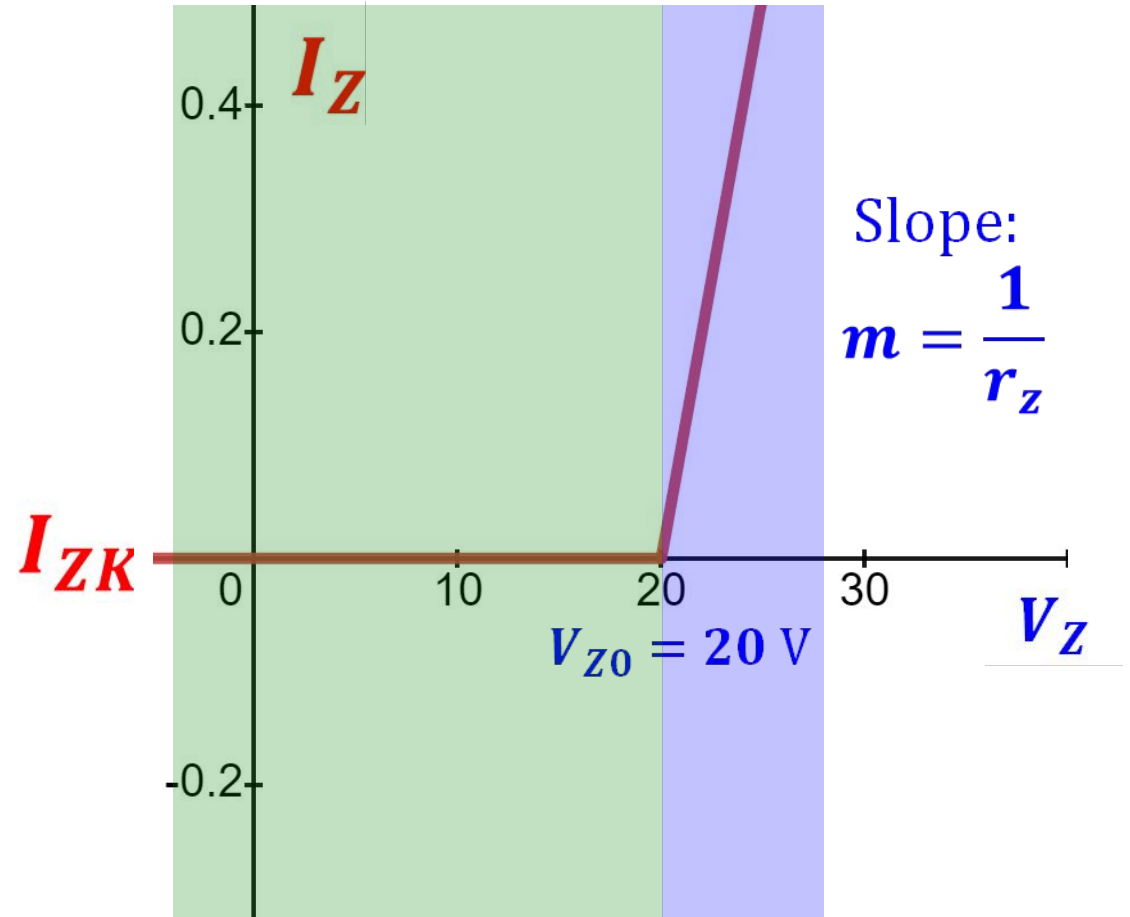

# Practice Problem 2

The  $6.8\text{ V}$  Zener diode in the circuit of **Figure** is specified to have the following parameters. The supply voltage  $V^+$  is nominally  $10\text{ V}$  but can vary by  $\pm 1\text{ V}$ .


$$V^+ = 10 \pm 1\text{ V}$$

$$V_Z = 6.8\text{ V at } I_Z = 5\text{ mA}$$

$$r_z = 20\ \Omega.$$

$$I_{ZK} = 0.2\text{ mA}.$$

- Find  $V_O$  with no load and with  $V^+$  at its nominal value
- (For  $R_L = 0.5\text{ k}\Omega$ ). Find the  $I_Z$ . In this scenario, calculate the Zener voltage  $V_O$ , load current  $I_L$  and input current  $I$
- Find the  $R_L$  that would give rise to worst-case scenario at worst case  $V^+$ . In this worst-case scenario, calculate the Zener voltage  $V_Z$ , load current  $I_L$  and input current  $I$
- (For  $R_L = 2\text{ k}\Omega$ ). Find the  $I_Z$ . In this scenario, calculate the Zener voltage  $V_O$ , load current  $I_L$  and input current  $I$
- Design the circuit, i.e., find the minimum value of the input voltage  $V^+$  such that, voltage regulation is maintained even in the worst-case scenario for  $R_L = 2\text{ k}\Omega$ . (Forget that  $V^+$  is  $10\text{ V}$ )
- Determine whether the circuit will maintain regulation if  $V^+$  is increased. If yes, argue if it should be increased or not.

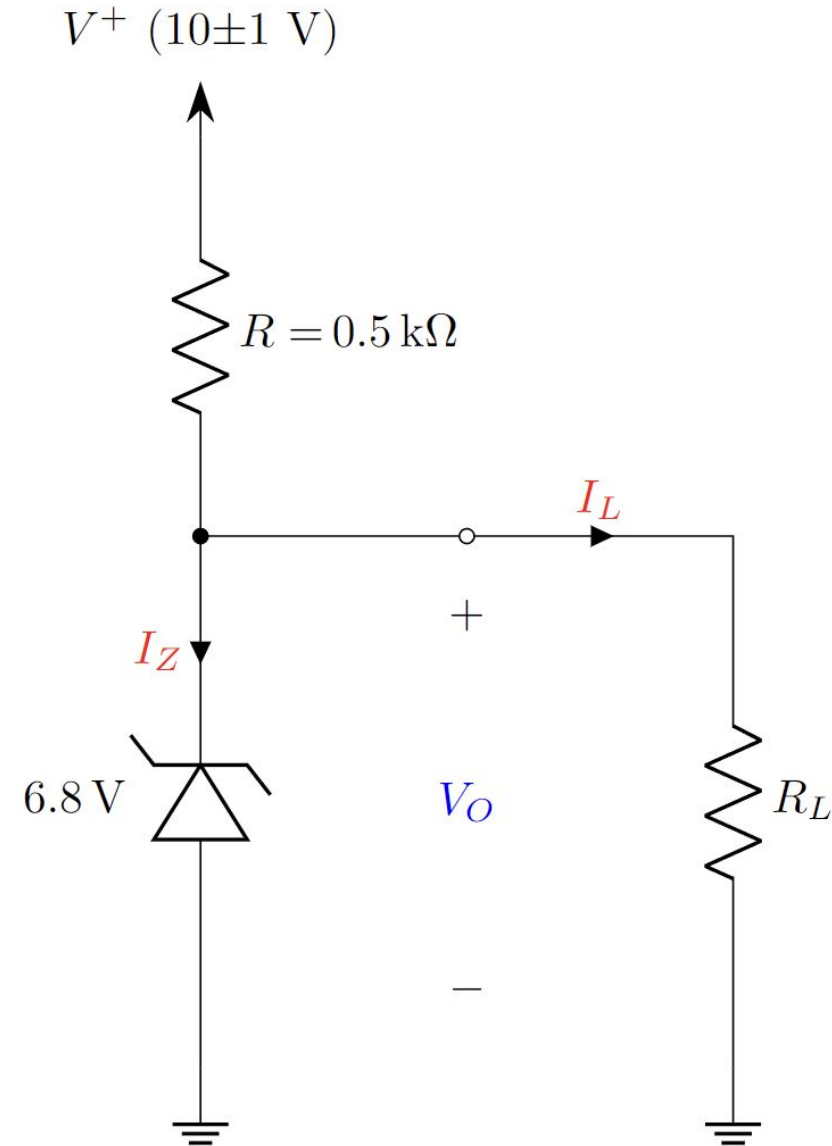




# Practice Problem 2

The  $6.8\text{ V}$  Zener diode in the circuit of **Figure** is specified to have the following parameters. The supply voltage  $V^+$  is nominally  $10\text{ V}$  but can vary by  $\pm 1\text{ V}$ .

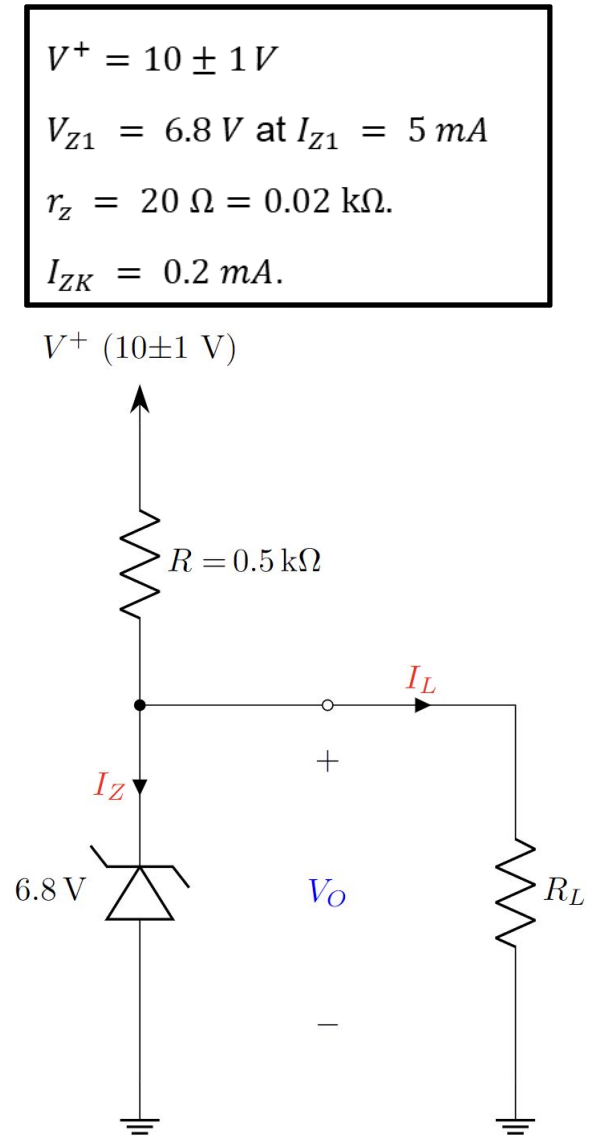(a) Find  $V_O$  with no load and with  $V^+$  at its nominal value



# Practice Problem 2

The 6.8-V Zener diode in the circuit of **Figure** is specified to have the following parameters. The supply voltage  $V^+$  is nominally 10 V but can vary by  $\pm 1$  V.

(a) Find  $V_O$  with no load and with  $V^+$  at its nominal value

## Solution:


Extracting Zener diode's reverse cut-in voltage

$$V_{ZO} = 6.8 - 5 \times 0.02 \text{ V}$$

$$\therefore V_{ZO} = 6.7 \text{ V}$$

Determining current from the 10 V source
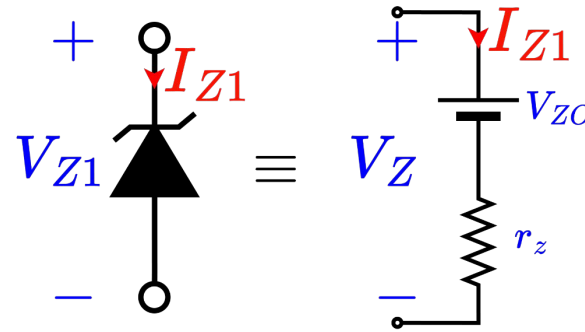
$$I = \frac{10 - 6.7}{0.5 + 0.02} \text{ mA} = 6.346 \text{ mA}$$



Determining output voltage

$$V_O = 6.7 + 6.346 \times 0.02 \text{ V}$$


$$V_O = 6.82692 \text{ V}$$

$$V^+ = 10 \pm 1 \text{ V}$$

$$V_{Z1} = 6.8 \text{ V at } I_{Z1} = 5 \text{ mA}$$

$$r_z = 20 \Omega = 0.02 \text{ k}\Omega.$$

$$I_{ZK} = 0.2 \text{ mA}.$$

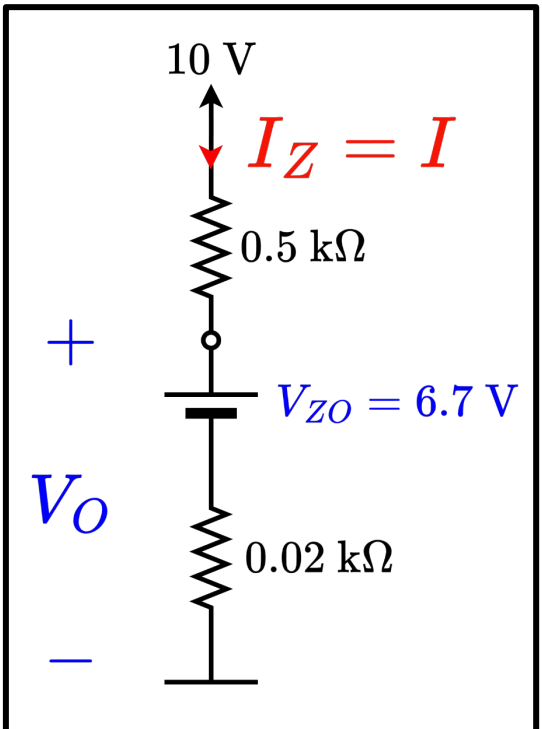

# Practice Problem 2

The  $6.8\text{ V}$  Zener diode in the circuit of **Figure** is specified to have the following parameters. The supply voltage  $V^+$  is nominally  $10\text{ V}$  but can vary by  $\pm 1\text{ V}$ .

(b) (For  $R_L = 0.5\text{ k}\Omega$ ). Find the  $I_Z$ . In this scenario, calculate the Zener voltage  $V_O$ , load current  $I_L$  and input current  $I$

**Solution:**


$$V^+ = 10 \pm 1\text{ V}$$

$$V_Z = 6.8\text{ V at } I_Z = 5\text{ mA}$$

$$V_{ZO} = 6.7\text{ V}$$

$$r_Z = 20\ \Omega.$$

$$I_{ZK} = 0.2\text{ mA}.$$

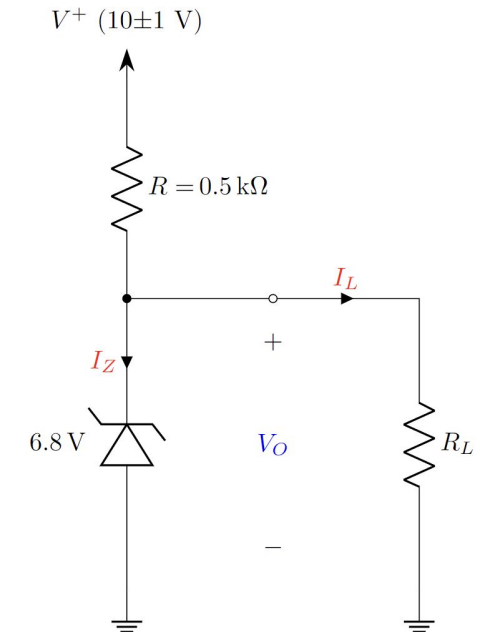

# Practice Problem 2

The  $6.8\text{ V}$  Zener diode in the circuit of **Figure** is specified to have the following parameters. The supply voltage  $V^+$  is nominally  $10\text{ V}$  but can vary by  $\pm 1\text{ V}$ .

(b) (For  $R_L = 0.5\text{ k}\Omega$ ). Find the  $I_Z$ . In this scenario, calculate the Zener voltage  $V_O$ , load current  $I_L$  and input current  $I$

## Solution:

Solving the node equation at  $V_O$ .

$$\begin{aligned}\frac{(10 \pm 1) - V_O}{R} &= \frac{V_O - V_{ZO}}{r_z} + \frac{V_O}{R_L} \\ \frac{(10 \pm 1) - V_O}{0.5} &= \frac{V_O - 6.7}{0.02} + \frac{V_O}{0.5} \\ \therefore V_O &= 6.537 \sim 6.611\text{ V}\end{aligned}$$

As,  $V_O < V_{ZO}$ , the Zener diode will not be in reverse breakdown mode, but in cut off

$$I_Z = I_{ZK}$$


$$V^+ = 10 \pm 1\text{ V}$$

$$V_Z = 6.8\text{ V at } I_Z = 5\text{ mA}$$

$$V_{ZO} = 6.7\text{ V}$$

$$r_z = 20\ \Omega.$$

$$I_{ZK} = 0.2\text{ mA}.$$

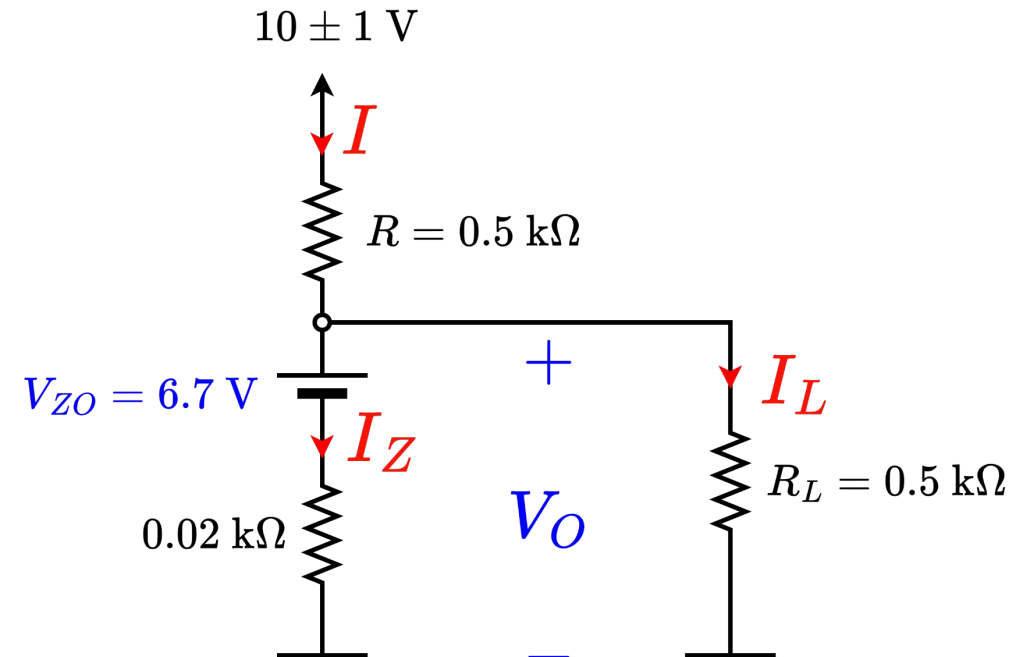

# Practice Problem 2

The  $6.8\text{ V}$  Zener diode in the circuit of **Figure** is specified to have the following parameters. The supply voltage  $V^+$  is nominally  $10\text{ V}$  but can vary by  $\pm 1\text{ V}$ .

(b) (For  $R_L = 0.5\text{ k}\Omega$ ). Find the  $I_Z$ . In this scenario, calculate the Zener voltage  $V_O$ , load current  $I_L$  and input current  $I$

**Solution:**

$$\therefore V_O = 6.537 \sim 6.611\text{ V}$$

As,  $V_O < V_{ZO}$ , the Zener diode will not be in reverse breakdown mode, but in cut off

$$I_Z = I_{ZK}$$

So,

$$V_O \left( \frac{1}{0.5} + \frac{1}{0.5} \right) = \frac{10 \pm 1}{0.5} - 0.2$$

$$V_O = 4.95 \pm 0.5\text{ V}$$

$$I_L = \frac{V_O}{R_L} = \frac{4.95 \pm 0.5}{0.5} \text{ mA} = 9.9 \pm 1 \text{ mA}$$


$$V^+ = 10 \pm 1\text{ V}$$

$$V_Z = 6.8\text{ V at } I_Z = 5\text{ mA}$$

$$V_{ZO} = 6.7\text{ V}$$

$$r_Z = 20\ \Omega.$$

$$I_{ZK} = 0.2\text{ mA}.$$

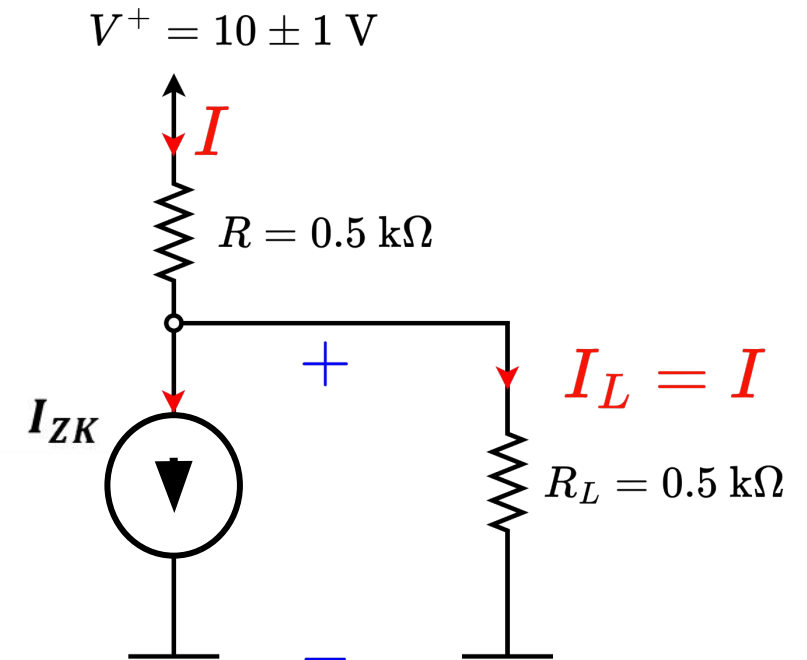

(c) Find the  $R_L$  that would give rise to worst-case scenario at worst case  $V^+$ . In this worst-case scenario, calculate the Zener voltage  $V_Z$ , load current  $I_L$  and input current  $I$

(d) (For  $R_L = 2\text{ k}\Omega$ ). Find the  $I_Z$ . In this scenario, calculate the Zener voltage  $V_O$ , load current  $I_L$  and input current  $I$

(c) The determining factor for worst-case scenario:

$$I_Z \geq I_{ZK}$$

$$\therefore \text{At } I_Z = I_{ZK} \text{ mA}$$



$$V_O = V_{Z0} + I_{ZK} r_Z = 6.704 \text{ V}$$

$$\therefore I = I_L + I_Z$$

(Since  $I_Z = I_{ZK}$ )

$$\therefore I_L = I - I_{ZK}$$

$$\therefore I_L \leq I - I_{ZK}$$

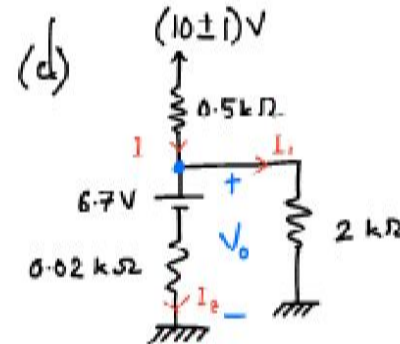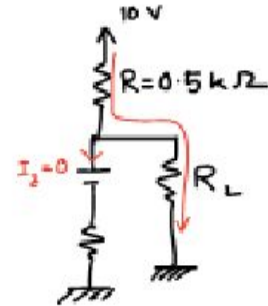

$$I = I_Z + I_L$$

$$\frac{V^+ - V_O}{R} = \frac{V_O - V_{Z0}}{r_Z} + \frac{V_O}{R_L}$$

$$\Rightarrow V_O \left( \frac{1}{R} + \frac{1}{r_Z} + \frac{1}{R_L} \right) - V_{Z0} \left( \frac{1}{r_Z} \right) = \frac{V^+}{R}$$

$$\Rightarrow V_O \left( \frac{1}{0.5} + \frac{1}{2} + \frac{1}{0.02} \right) - 6.7 \left( \frac{1}{0.02} \right) = \frac{10}{0.5}$$

$$\Rightarrow V_O = \frac{355}{54} \text{ V} = 6.76 \text{ V}$$

$$I_Z = \frac{V_O - V_{Z0}}{r_Z} = \frac{6.76 - 6.7}{0.02} = 3.1 \text{ mA} > I_{ZK}$$

So, the zener diode can sustain this load.

$$\frac{V_O}{R_L} \leq \frac{V^+ - V_O}{R} - I_{ZK}$$

$$R_L \geq \frac{6.704}{\frac{10 - 6.704}{0.5} - 0.2} \text{ k}\Omega$$

$$R_L \geq 1.526 \text{ k}\Omega$$

$$R_L \geq 1.526 \text{ k}\Omega$$

$$V_O = 6.704 \text{ V}$$

$$I_L \leq \frac{V_O}{R_L} = 4.392 \text{ mA}$$

$$I \geq I_L + I_{ZK}$$


$$I \geq 4.592 \text{ mA}$$

$$\therefore V_O = 6.76 \text{ V}$$

$$I_Z = 3.1 \text{ mA}$$

$$I_L = \frac{6.76}{2} \text{ mA} = 3.38 \text{ mA}$$

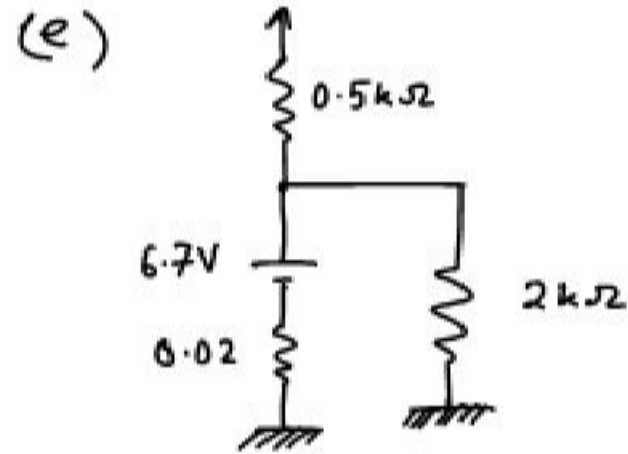(e) Design the circuit, i.e., find the minimum value of the input voltage  $V^+$  such that, voltage regulation is maintained even in the worst-case scenario for  $R_L = 2\text{ k}\Omega$ . (Forget that  $V^+$  is 10 V)



At worst case:  $I_z = I_{zk}$

$$\begin{aligned}\therefore V_o &= V_{zo} + I_{zk} r_z \\ &= 6.7 + 0.2 \times 0.02 = 6.704\text{ V}\end{aligned}$$

For  $R_L = 2\text{ k}\Omega$

$$I_L = \frac{6.704}{2} = 3.352\text{ mA}$$



$$I = I_L + I_{zk}$$

$$I = 3.552\text{ mA}$$

$$\therefore V^+ \geq V_o + IR$$

$$V^+ \geq 8.48\text{ V}$$

# Solving Problems

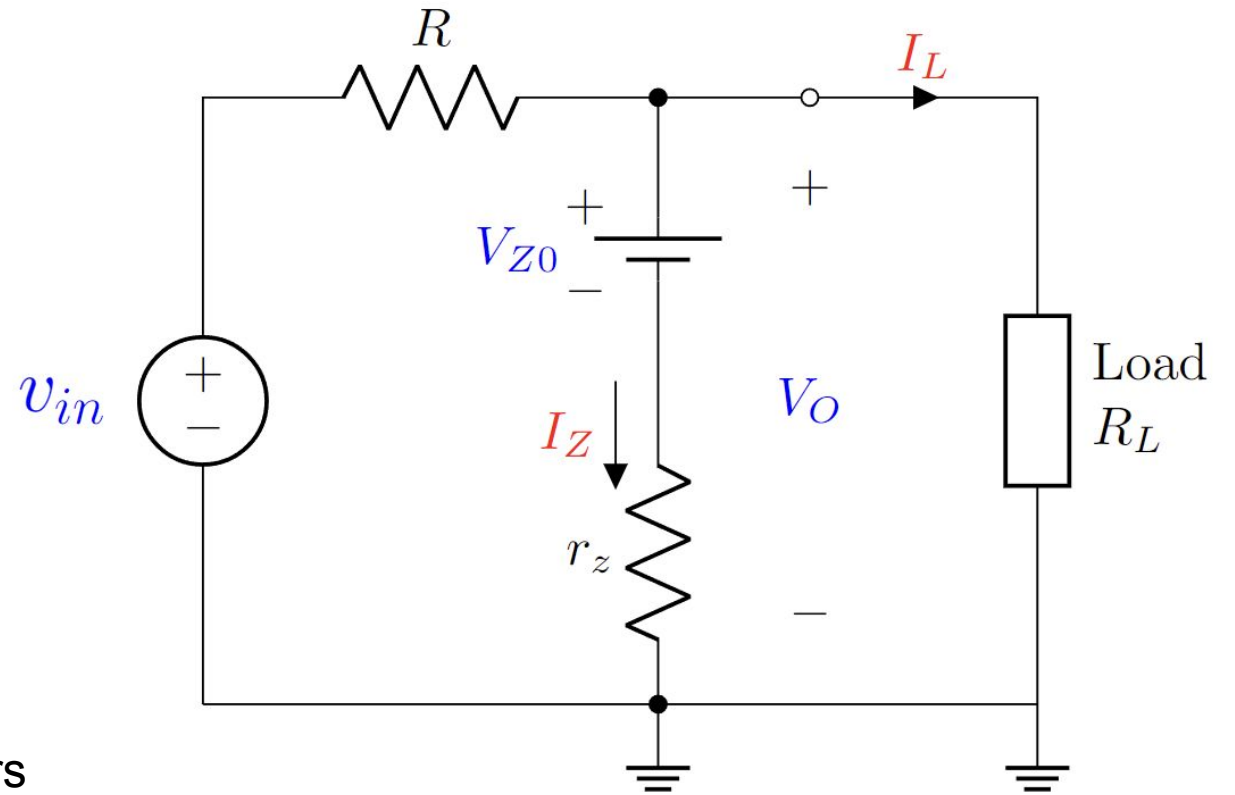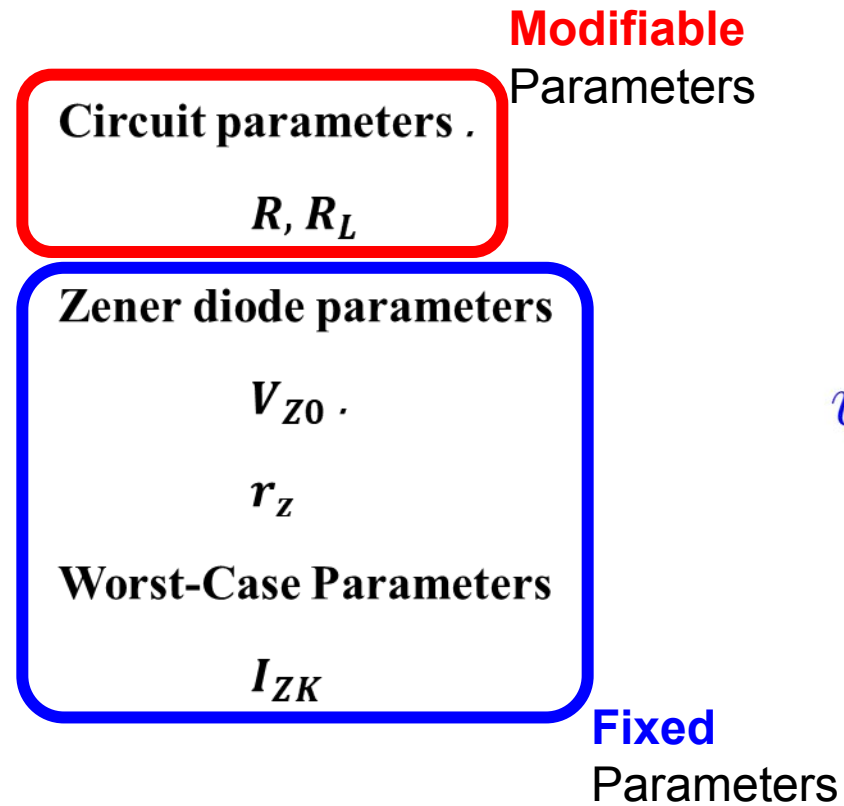



**Obtain the Fixed Parameters first**


$$V_O = V_{ZO} + I_Z r_z$$

$$I_Z = \frac{V_O - V_{ZO}}{r_z}$$

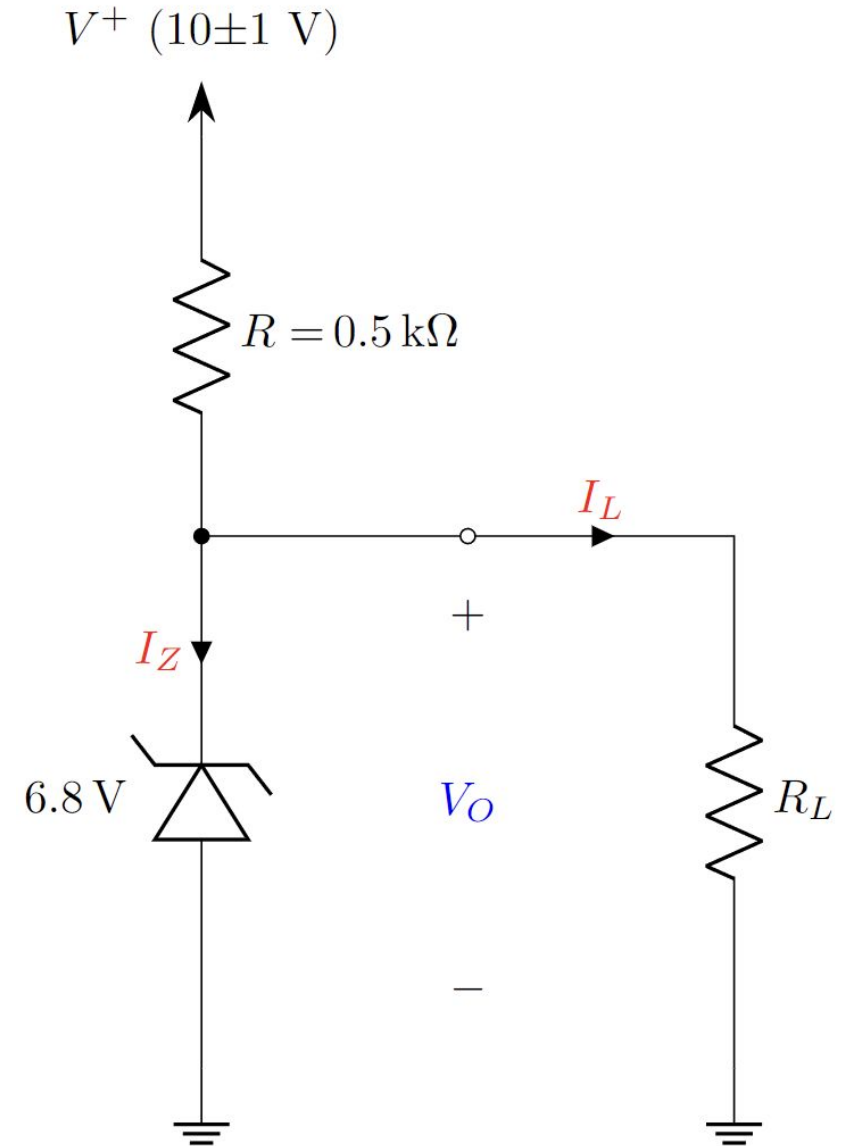
**KCL/Nodal Analysis at node  $V_O$**

$$\frac{v_{in} - V_O}{R} = I_Z + \frac{V_O}{R_L}$$

$$\frac{v_{in} - V_O}{R} = \frac{V_O - V_{ZO}}{r_z} + \frac{V_O}{R_L}$$


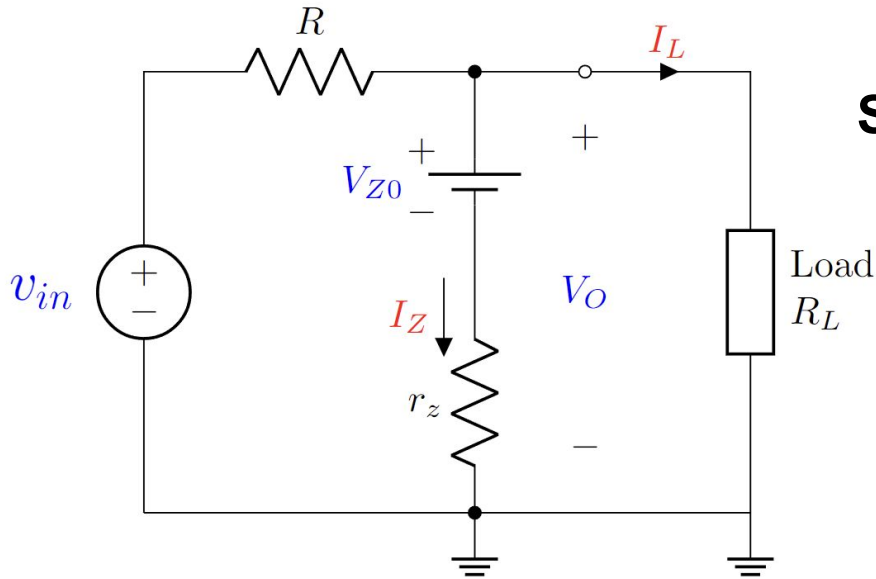
# Measures of Worst-Case Scenario (General)



**Solving:**

$$V_O = V_{ZO} + I_Z r_z$$

$$I_Z = \frac{V_O - V_{ZO}}{r_z}$$

Minimum Current through VR:

$$I_Z(\min) \geq I_{ZK}$$

$$\frac{V_O - V_{ZO}}{r_z} \geq I_{ZK}$$

$$V_O \geq V_{ZO} + I_{ZK} r_z$$

Minimum Input Voltage:

$$v_{in}(\min) > V_{ZO} + I_{ZK}(r_z + R) + I_L R$$

**Worst Case Scenario occurs when**

1. **Input Voltage is minimum:**  $v_{in}(\min)$
2. **Load Current is maximum:**  $I_L(\max)$
3. **VR current minimum:**  $I_Z(\min)$


Maximum Load Current

$$I_L(\max) \leq \frac{v_{in} - V_O}{R} - I_{ZK}$$

# Measures of Voltage Regulation

There are two quantities that grade the performance of voltage regulator.

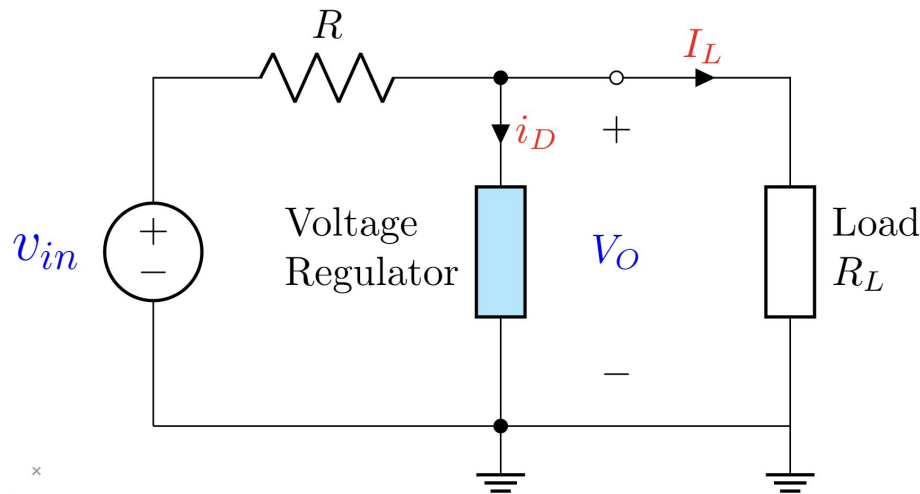
1. **Load Regulation:** Change in output voltage  $V_O$  per unit change in load current  $I_L$ . ( $v_{in}$  is fixed)
2. **Line Regulation:** Change in output voltage  $V_O$  per unit change in supply voltage  $v_{in}$ . ( $R_L$  is fixed)



Mathematically **Load Regulation** is  $\frac{dV_O}{dI_L}$

Mathematically **Line Regulation** is  $\frac{dV_O}{dv_{in}}$

# Measures of Voltage Regulation

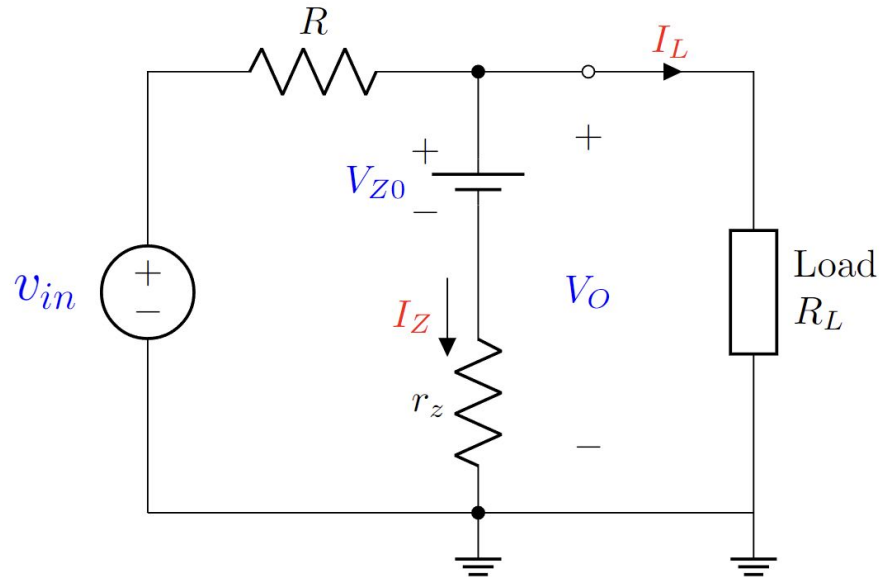

Measuring **Line** Regulation:

$$V_O = V_{ZO} + I_Z r_z$$

$$I_Z = \frac{V_O - V_{ZO}}{r_z}$$

$$\frac{v_{in} - V_O}{R} = I_Z + \frac{V_O}{R_L}$$


$$\frac{v_{in} - V_O}{R} = \frac{V_O - V_{ZO}}{r_z} + \frac{V_O}{R_L}$$

$$V_O \left( \frac{1}{R} + \frac{1}{r_z} + \frac{1}{R_L} \right) = v_{in} \left( \frac{1}{R} \right) + V_{ZO} \left( \frac{1}{r_z} \right)$$

$$\frac{V_O}{R || r_z || R_L} = v_{in} \left( \frac{1}{R} \right) + V_{ZO} \left( \frac{1}{r_z} \right)$$

Express  $V_O$  as a function of  $v_{in}$ .

# Measures of Voltage Regulation

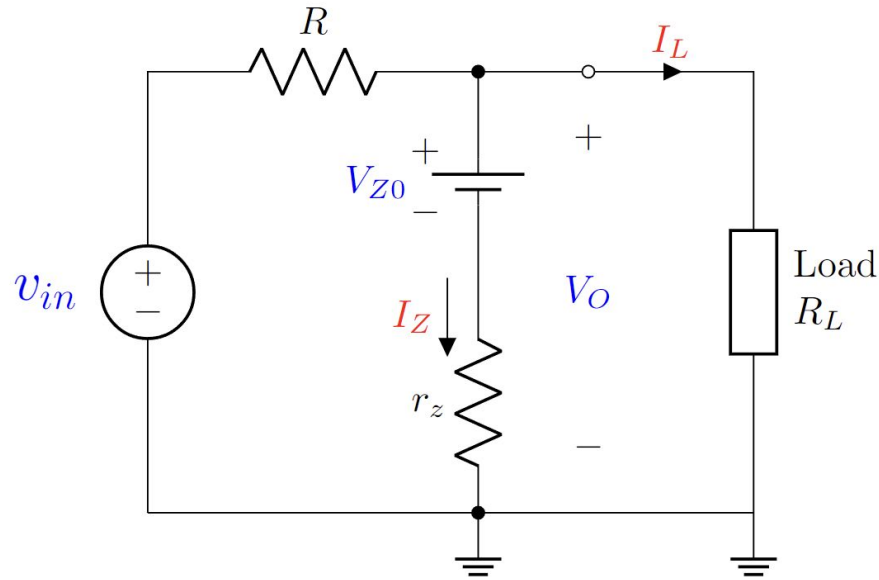

Measuring **Line** Regulation:

$$V_O = v_{in} \left( \frac{R || r_z || R_L}{R} \right) + V_{Z0} \left( \frac{R || r_z || R_L}{r_z} \right)$$


$$V_O \left( \frac{1}{R} + \frac{1}{r_z} + \frac{1}{R_L} \right) = v_{in} \left( \frac{1}{R} \right) + V_{Z0} \left( \frac{1}{r_z} \right)$$

$$\frac{V_O}{R || r_z || R_L} = v_{in} \left( \frac{1}{R} \right) + V_{Z0} \left( \frac{1}{r_z} \right)$$

Express  $V_O$  as a function of  $v_{in}$ .

$$\frac{dV_O}{dv_{in}} = \frac{R || r_z || R_L}{R}$$

# Measures of Voltage Regulation

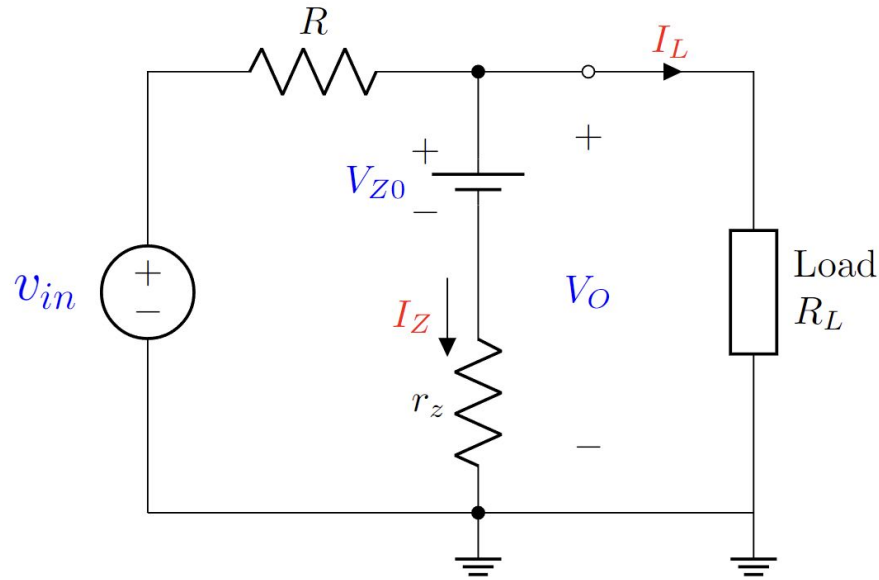

Measuring **Load** Regulation:

$$V_O = V_{Z0} + I_Z r_z$$

$$I_Z = \frac{V_O - V_{Z0}}{r_z}$$

$$\frac{v_{in} - V_O}{R} = I_Z + I_L$$

$$\frac{v_{in} - V_O}{R} = \frac{V_O - V_{Z0}}{r_z} + I_L$$


$$V_O \left( \frac{1}{R} + \frac{1}{r_z} \right) = -I_L + v_{in} \left( \frac{1}{R} \right) + V_{Z0} \left( \frac{1}{r_z} \right)$$

$$\frac{V_O}{R || r_z} = -I_L + v_{in} \left( \frac{1}{R} \right) + V_{Z0} \left( \frac{1}{r_z} \right)$$

Express  $V_O$  as a function of  $I_L$ .

$$\frac{dV_O}{dI_L} = -R || r_z$$

# Measures of Voltage Regulation

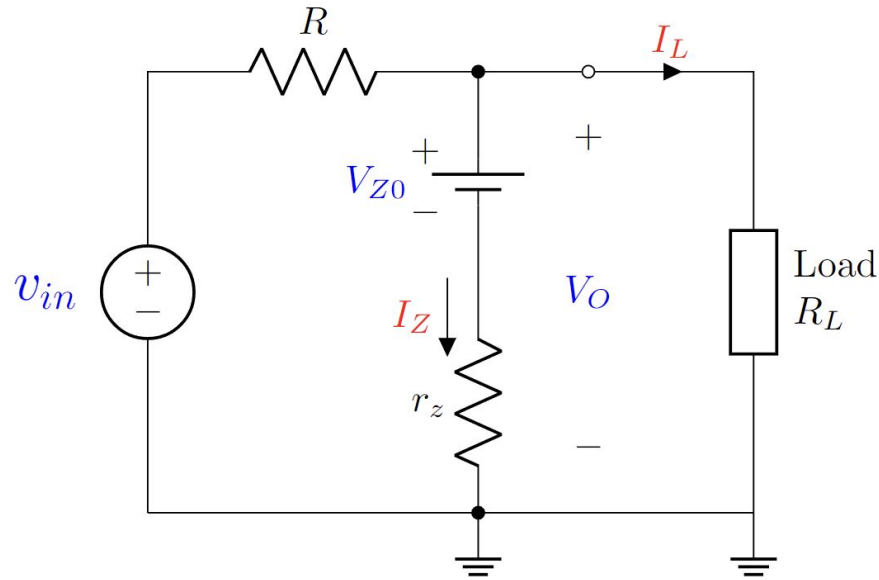

Measuring Load Regulation:

$$V_O = v_{in} \left( \frac{R || r_z || R_L}{R} \right) + V_{Z0} \left( \frac{R || r_z || R_L}{r_z} \right)$$

$$V_O \left( \frac{1}{R} + \frac{1}{r_z} + \frac{1}{R_L} \right) = v_{in} \left( \frac{1}{R} \right) + V_{Z0} \left( \frac{1}{r_z} \right)$$

$$\frac{V_O}{R || r_z || R_L} = v_{in} \left( \frac{1}{R} \right) + V_{Z0} \left( \frac{1}{r_z} \right)$$

$$\frac{dV_O}{dv_{in}} = \frac{R || r_z || R_L}{R}$$

# Practice Problem 3

The Zener diode in the circuit of **Figure** is specified to have the following parameters. The **supply voltage**  $V_{in}$  is nominally 5 V but can vary by  $\pm 10\%$ .

**Load current** can vary from 0 mA to 50 mA.


$$V_{in} = 5\text{ V} \pm 10\%$$

$$V_{Z0} = 3\text{ V}$$

$$r_z = 0\ \Omega$$

$$I_{ZK} = 1\text{ mA}.$$

- Find **minimum and maximum input Voltage**,  $V_{in}(\text{min})$  and  $V_{in}(\text{max})$ , **maximum and minimum load current**  $I_L(\text{max})$  and  $I_L(\text{min})$ , **minimum diode current**  $I_Z(\text{min})$ .
- Find the  $I_Z$ ,  $V_{in}$  and  $I_L$  at worst-case scenario.
- For worst case what is  $I_S$  and  $V_R$ .
- Find  $R$  for which diode maintains regulation at worst case scenario

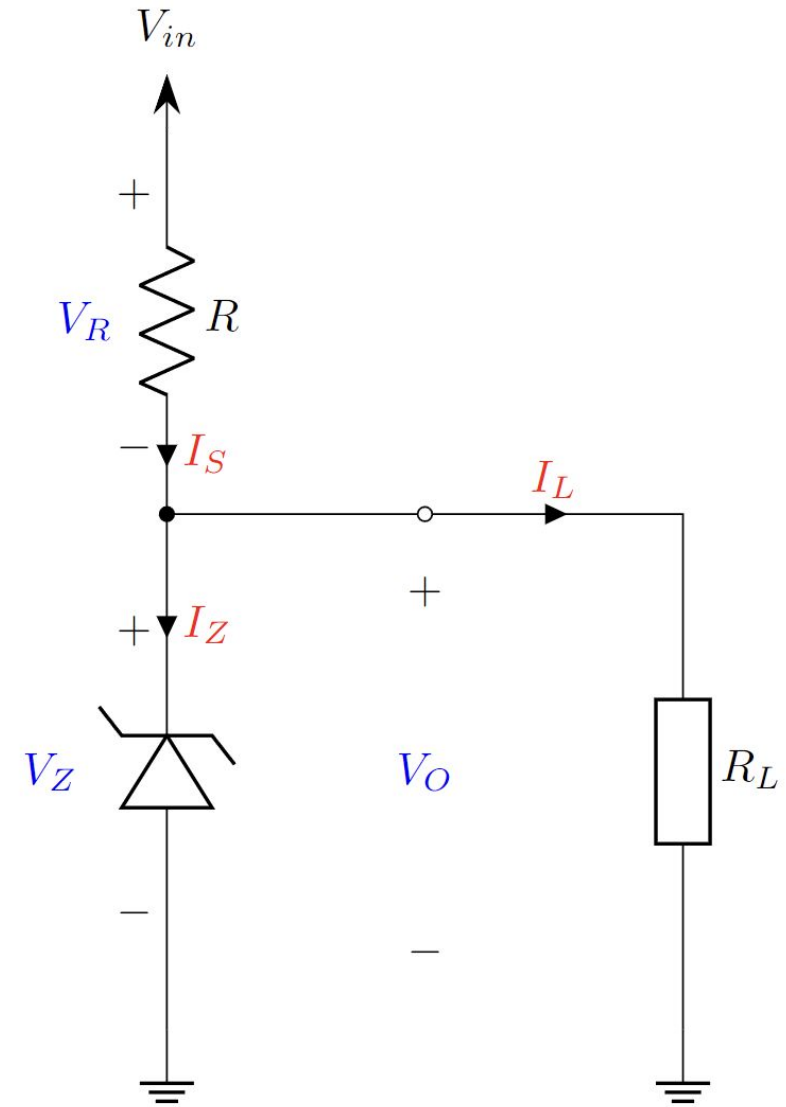



# Practice Problem 4


The Zener diode in the circuit of **Figure** is specified to have the following parameters.

$$V_{Z0} = 3 \text{ V}$$

$$r_z = 20 \, \Omega, 0 \, \Omega$$

$$I_{ZK} = 1 \text{ mA.}$$

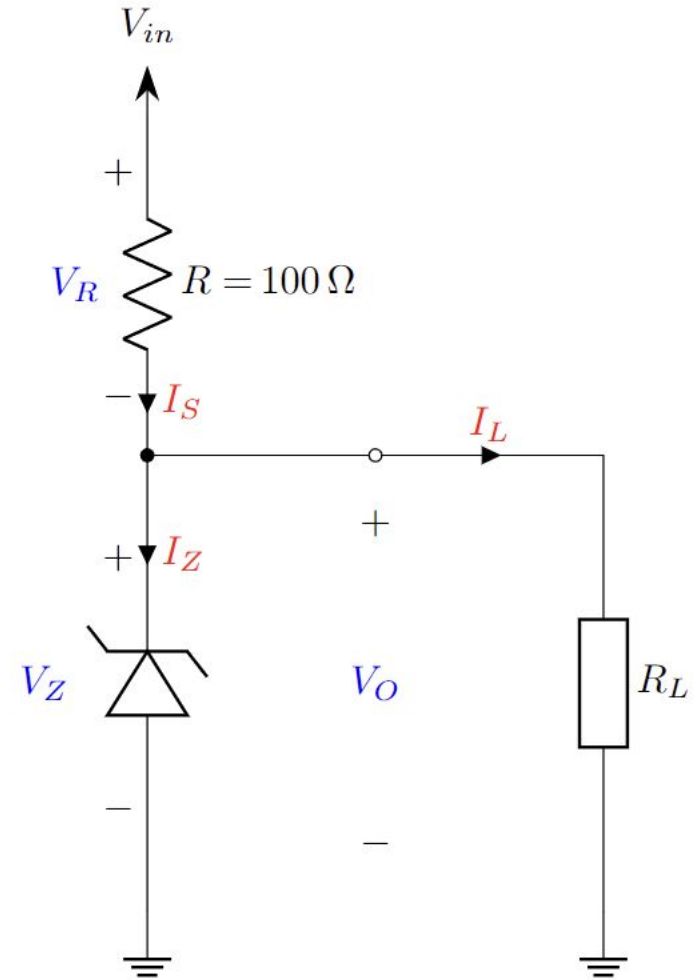- Find **minimum input voltage,  $V_{in}(\text{min})$**  for which the diode maintains regulation, when  $R_L = 10 \text{ k}\Omega$ .
- Find worst case  $R_L$  if the **input voltage  $V_{in}$**  is nominally **5 V** but can vary by  $\pm 10 \%$



# Some important tips

- - If  $V_{ZK}$ ,  $V_{ZO}$  and  $r_Z$  are given, we can calculate  $I_{ZK} = \frac{V_{ZK} - V_{ZO}}{r_Z}$
  - If  $V_{ZO}$  and  $r_Z$  are **not** provided, consider  $V_{ZK} = V_Z = V_{ZO}$
  - Consider  $I_{ZK} = 0$  if not provided

