
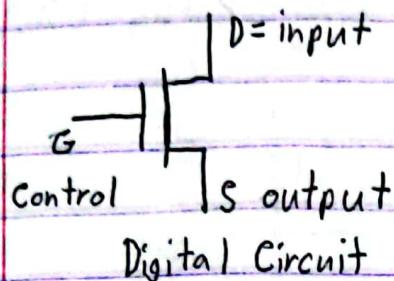


MOSFET Device :

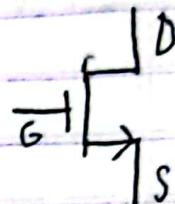


G = Gate
D = Drain
S = Source




Analog Circuit

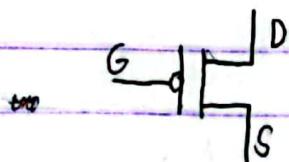- * It is a transistor.
- * The Above type of MOSFET are called NMOS.
- * Another type of MOSFET is PMOS. Its figure;




The Switch, S - Model :

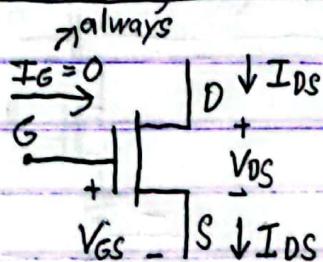


$$V_{DS} = V_D - V_S$$

$$V_{GS} = V_G - V_S$$

$V_{GS} < V_T$

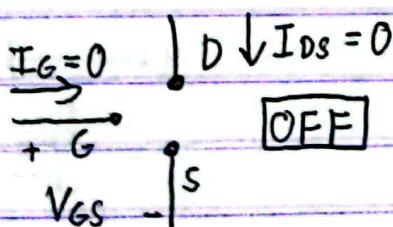


$V_{GS} \gg V_T$

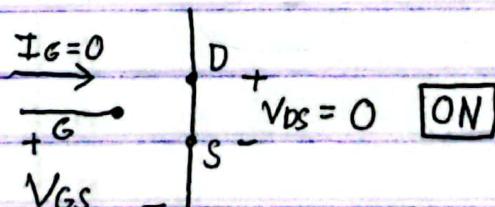


* V_T = Threshold Voltage = $0.5 - 1\text{V}$

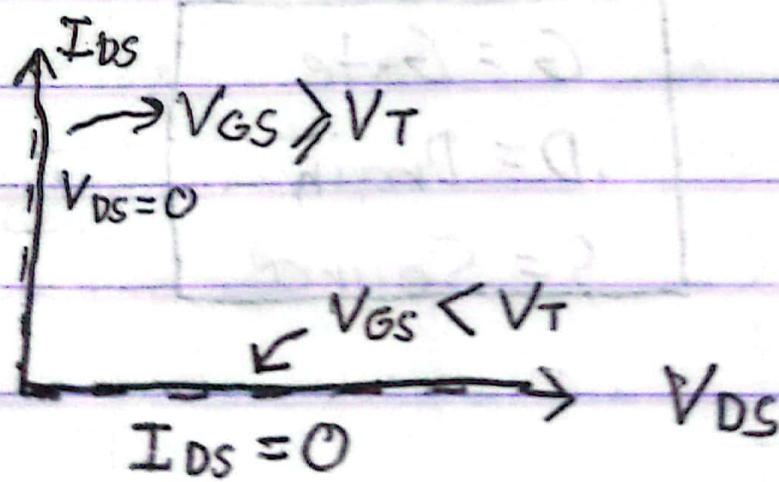- * If $V_{GS} < V_T$ then $I_{DS} = 0$ (Open Circuit)
- * " $V_{GS} \gg V_T$ " $V_{DS} = 0$ (Short ")



MOSFET logic gates [$V_T \sim 1V$]:

① NOT gate / Inverter:

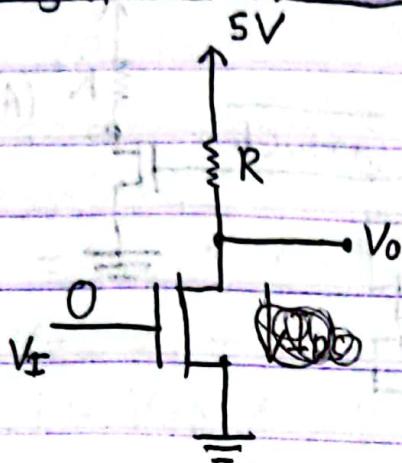


V_I	I	V_o	O
0V	0	5V	1
5V	1	0V	0

$$V_{GS} \gg V_T \rightarrow S.C$$


$$V_{GS} < V_T \rightarrow O.C$$

② NAND Gate:

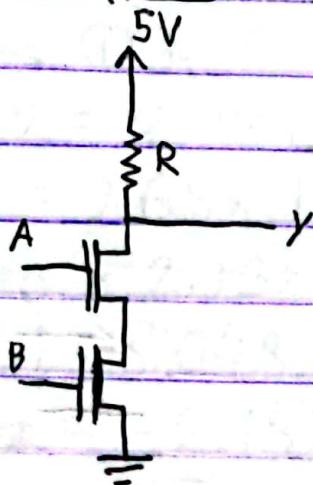

A	B	$y = \overline{AB}$
0	0	1
0	1	1
1	0	1
1	1	0


③ NOR Gate:

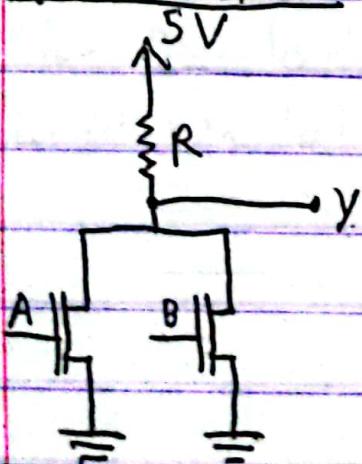


A	B	$y = \overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

Example:


① $\overline{AB + C + D}$

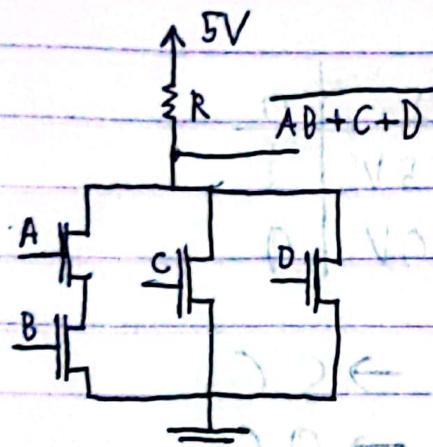

③ $(A+B)CD$

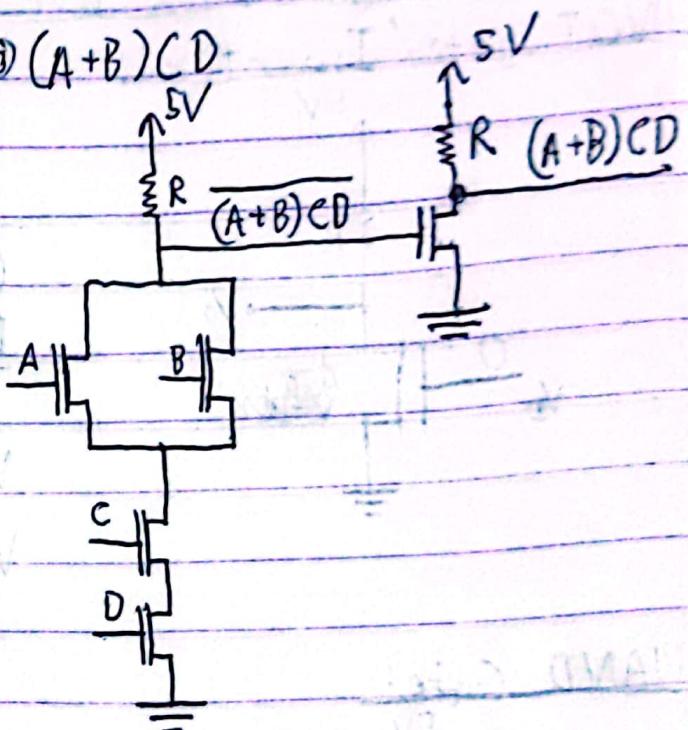


② $AB + C \overline{(A+B)CD}$

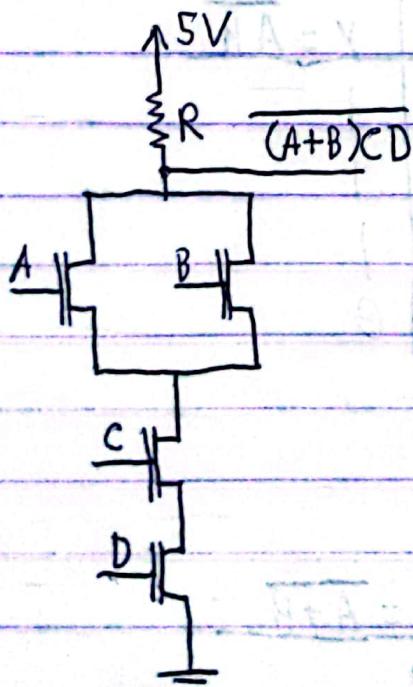

Static analysis:

* MOSFET Inverter (S-model):

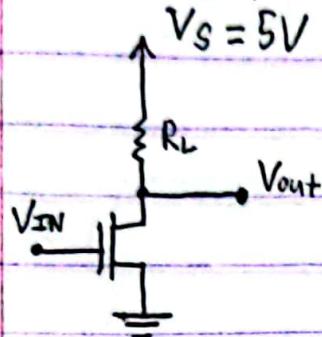


here $V_{IN} = V_{GS}$


assume $V_T = 1V$ and $V_s = 5V$

$$V_{GS} = V_G - V_s = V_G - 5V$$

* $V_{IN} < V_T$:

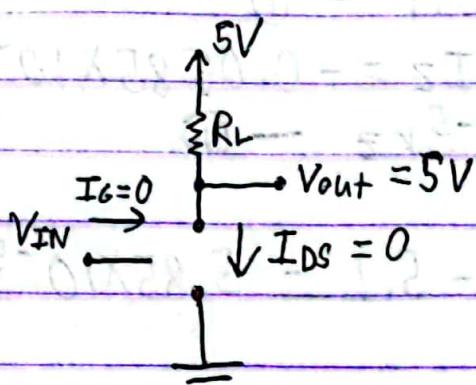

* $V_{IN} > V_T$:

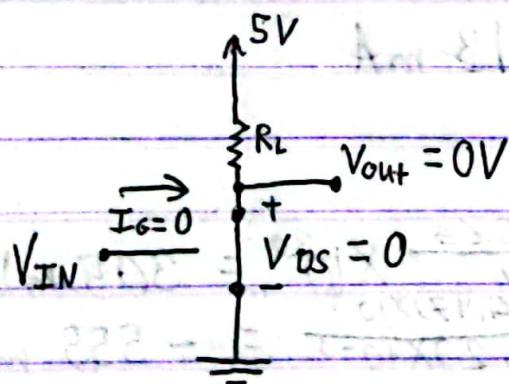

$V_{out}(V)$

V_s



$V_{in}(V)$

* Specification - 1:

$$V_{OH} = 4.5V, V_{OL} = 0.5V, V_{IH} = 4V, V_{IL} = 0.9V$$

- a) Is $V_{OL} < V_{IL}$, $V_{OH} > V_{IH}$
- b) Valid input \rightarrow Valid output } Conditions to be met

For an inverter,

Input

Valid 0 ($V_i < V_{IL}$) \rightarrow

" 1 ($V_i > V_{IH}$) \rightarrow

Output


Valid 1 ($V_o \gg V_{OH}$)

" 0 ($V_o \leq V_{OL}$)

* This specification follows static discipline.

* We cannot change the MOSFET Inverter, we are stuck with what we are given.

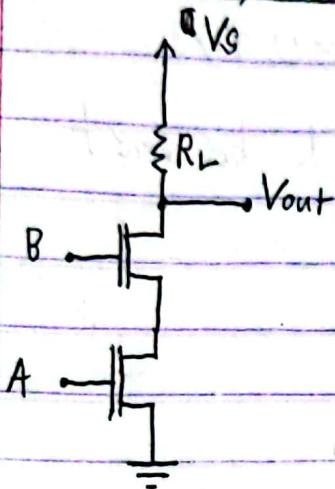Static Analysis of NMOS MOSFET NAND (S-model):



A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

* We can draw the transfer Characteristics graph by considering one input as constant. Like when $A = 0$ or $A = 1$.


* When $A = 0$,

B	Out
0	1
1	1

When $A = 1$,

B	Out
0	1
1	0

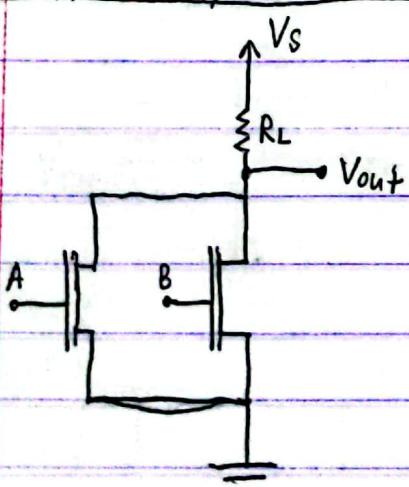State Analysis of NMOS MOSFET NOR (S-model):



A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0


When $A = 0$,

B	Out
0	1
1	0

When $A = 1$,

B	Out
0	0
1	0


+ The S-model:

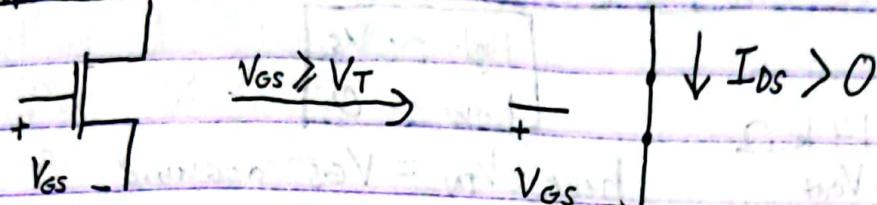

① S-Model, ON mode


* But Material (Si) has non-zero resistance.

The SR-Model:

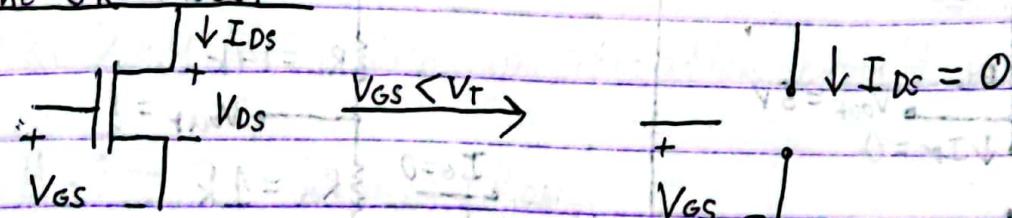

$\downarrow V_{GS} \geq V_T$
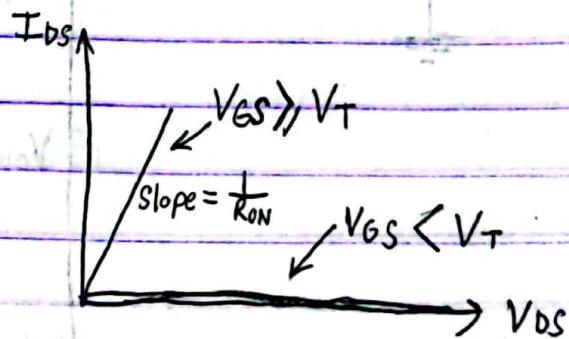
$$\left. \begin{array}{l} \downarrow I_{DS} \\ \downarrow V_{GS} \\ \left\{ \begin{array}{l} R_{ON} \\ \downarrow I_{DS} = \frac{V_{DS}}{R_{ON}} \end{array} \right. \end{array} \right.$$




$$* R_{ON} = \frac{1}{k_n (V_{GS} - V_T)} \quad W, L = \text{Length and Width of the MOSFET}$$

* V_{GS} has 2 values $V_{GS} = \text{Low}$ and $V_{GS} = \text{High}$. Use $V_{GS} = \text{High}$ for calculating R_{ON} .


very smaller

This is true only if $V_{DS} \ll V_{GS} - V_T$ and if ~~$V_{GS} \gg V_T$~~ it is $V_{DS} > V_{GS} - V_T$ then it would act like a current source.


MOSFET Inverter (SR-model):

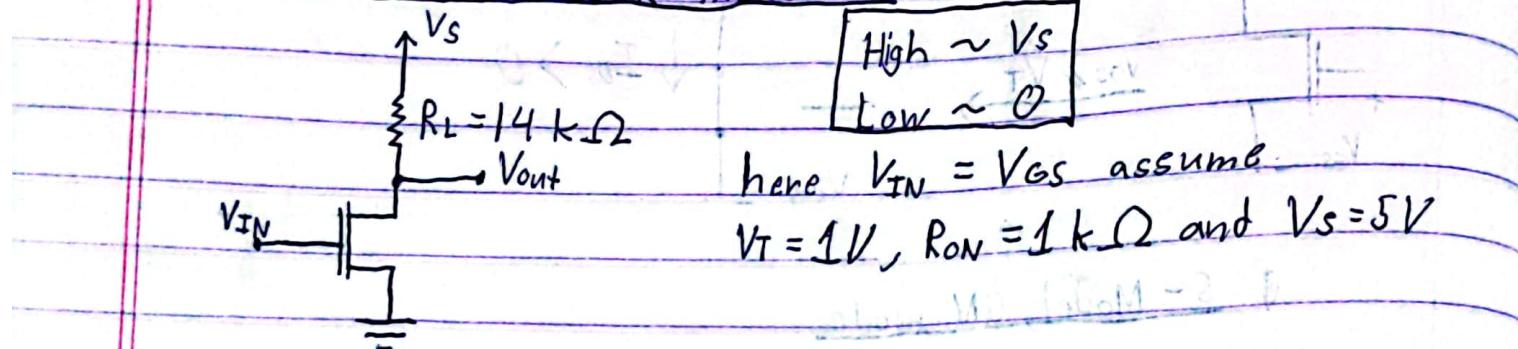

* $V_{IN} < V_T$ (Low)

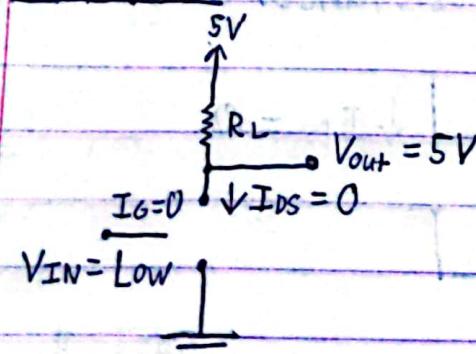

$V_{IN} = \text{High} \geq V_T$

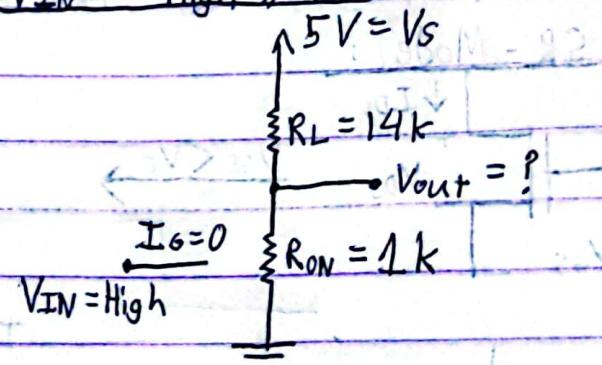

$$V_{out} = \frac{R_{ON}}{R_L + R_{ON}} \times V_S$$

$$= \frac{1k}{1k + 14k} \times 5$$

$$= 0,33V$$

When the input is high,

$\frac{R_{ON}}{R_L + R_{ON}} \times V_S < V_T$ must be maintained.

To make a specification work we can : $\frac{R_{on}}{R_{on} + R_L} \times V_s < V_o$

* Method - 1 : Change R_L

$$\frac{R_{on}}{R_{on} + R_L} \times V_s < V_o$$

$$\Rightarrow \frac{R_{on}}{R_{on} + R_L} < \frac{V_o}{V_s}$$

$$\Rightarrow \frac{R_L + R_{on}}{R_{on}} > \frac{V_s}{V_o}$$

$$\Rightarrow R_L + R_{on} > \frac{V_s}{V_o} R_{on}$$

$$\Rightarrow R_L > \frac{V_s \times R_{on}}{V_o} - R_{on}$$

$$\Rightarrow R_L > \frac{5 \times 1}{0.2} - 1$$

$\Rightarrow R_L > 24 \text{ k}\Omega$ then specification would work.

* Method - 2 : Change R_{on}

$$\frac{R_{on}}{R_L + R_{on}} \times V_s < V_o$$

$$\Rightarrow R_{on} \times V_s < V_o (R_L + R_{on})$$

$$\Rightarrow R_{on} \times V_s - R_{on} \times V_o < V_o \times R_L$$


$$\Rightarrow R_{on} < \frac{V_o \times R_L}{V_s - V_o}$$

$$\Rightarrow R_{on} < \frac{0.2 \times 14}{5 - 0.2}$$



$$\Rightarrow R_{on} < 0.58 \text{ k}\Omega$$
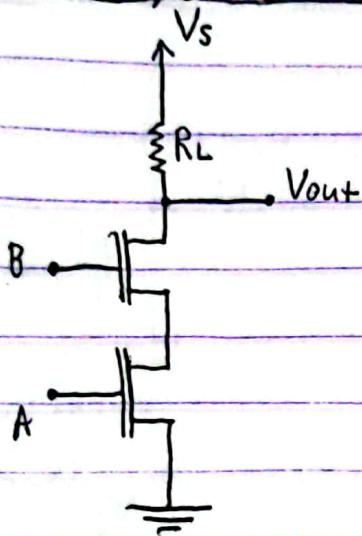
#


Static Analysis of MOSFET NAND (CSR-Model):



A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

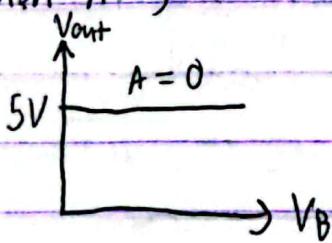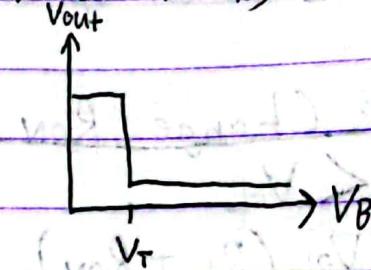
* When $A=0$,When $A=1$,

$$V_S = 5V$$

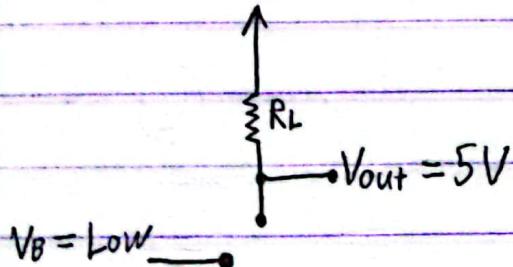

$V_B = \text{Low}$ \rightarrow


$V_A = \text{High} \rightarrow R_{ON}$

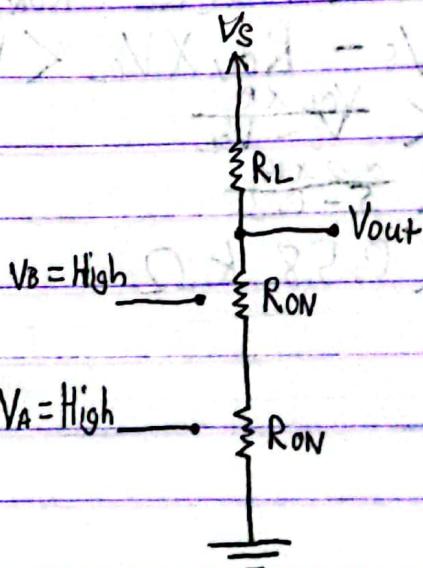

$$R'_{ON} = 2R_{ON}$$


$$V_{out} = \frac{R'_{ON}}{R'_{ON} + R_L} \times V_S$$

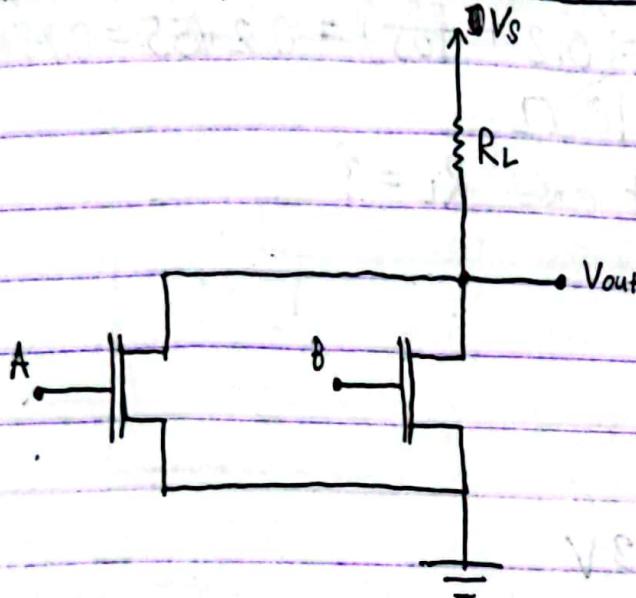Static Analysis of MOSFET NOR (SR-model):




A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0


* When A = Low, B = Low,

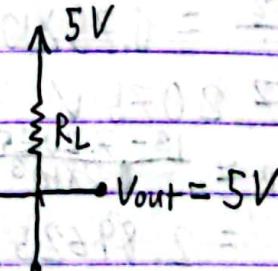

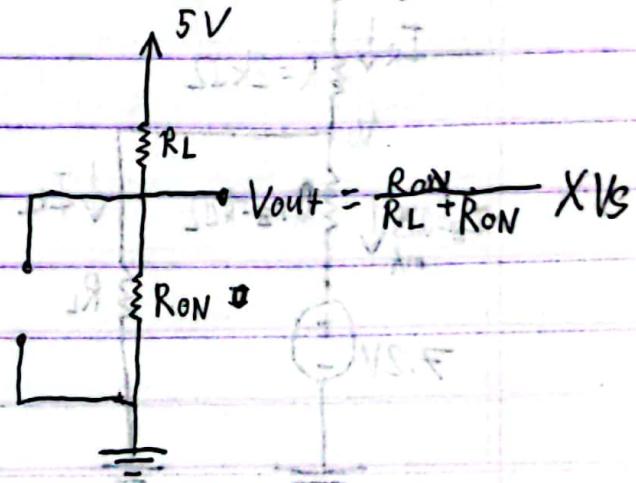
* When $A = \text{Low}$, $B = \text{high}$,



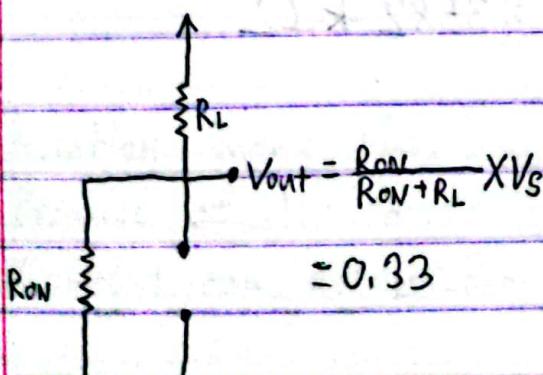
* When $A = \text{High}$, $B = \text{Low}$



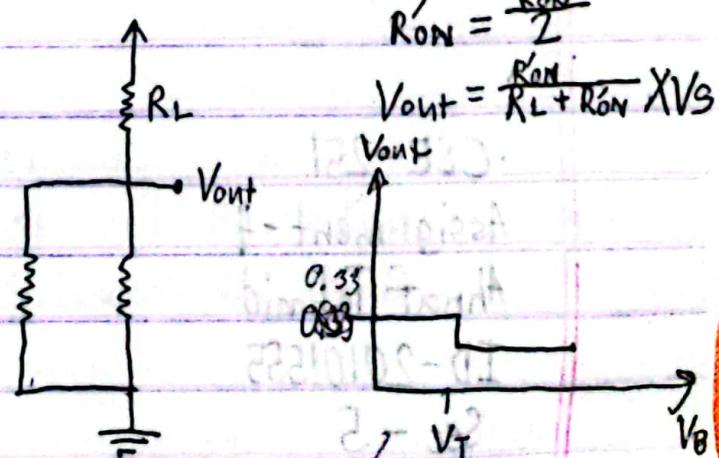When $A = \text{high}$, $B = \text{high}$,



Internal Structure of MOSFET:

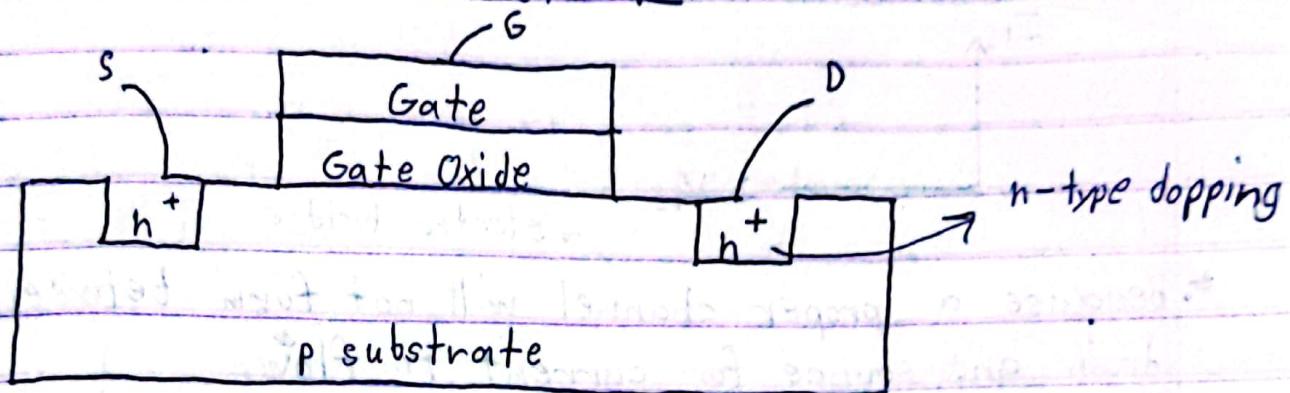


n-type \rightarrow majority electrons ^{with} some holes.

p-type \rightarrow "holes with" electrons.

- * NMOS is made from p-type substrate as a base.

$$W=10 \text{ (L}=15\text{)} \text{ (V}-2)$$

Operation of a MOSFET:

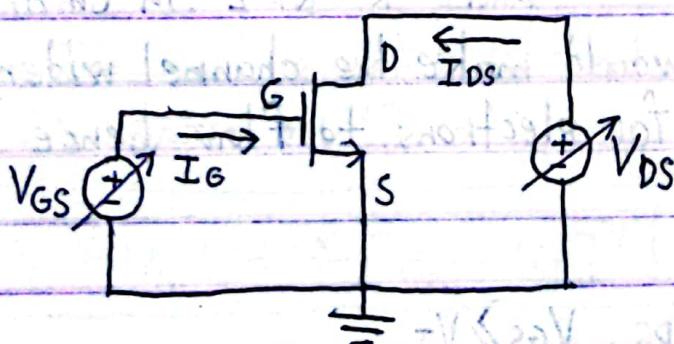


- * Relation among V_{GS} , V_{DS} and I_{DS}

- * Because of the oxide layer I_{GS} will be always $>$ zero.

- * Current can never flow from Source to Drain.

* Case - 1: $0 < V_{GS} < V_T$

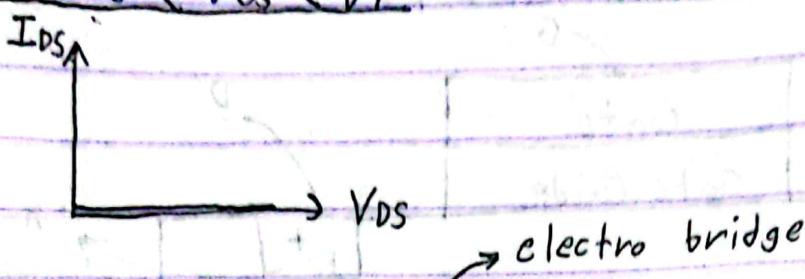


- Because a proper channel will not form between drain and source for current to flow.

* Case - 2: $V_{DS} = 0V, V_{GS} \geq V_T$

- Channel will be created for current to flow.

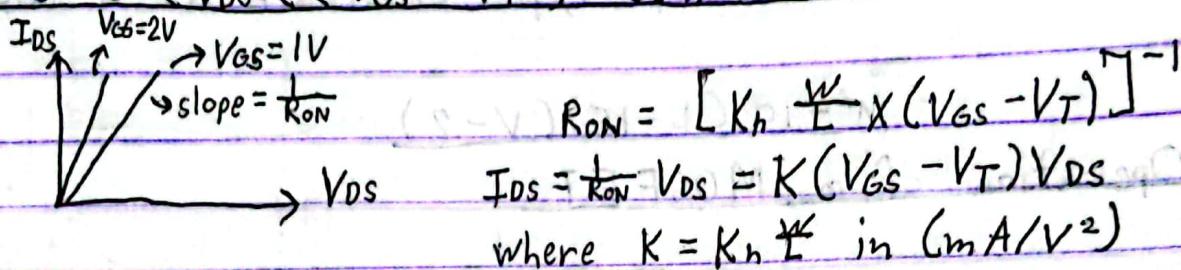* Case - 3: $0 < V_{DS} \ll V_{GS} - V_T, V_{GS} \geq V_T$




- Increasing the V_{GS} would make the channel wider, which would make it easier for electrons to flow hence R_{on} would decrease.

* Case - 4: Increased $V_{DS}, V_{GS} \geq V_T$

- $V_{GS} - V_{DS} \gg V_T$
- $V_{DS} \leq V_{GS} - V_T$
- ∴ If V_{DS} increase a lot the channel will not remain a flat line hence it will stop current from flowing.
- $V_{GS} = V_T + V_{ov}$ [V_{ov} = Voltage Overdrive]
- higher V_{GS} means higher V_{ov} , and wider the channel will be.

Continuation of V-2

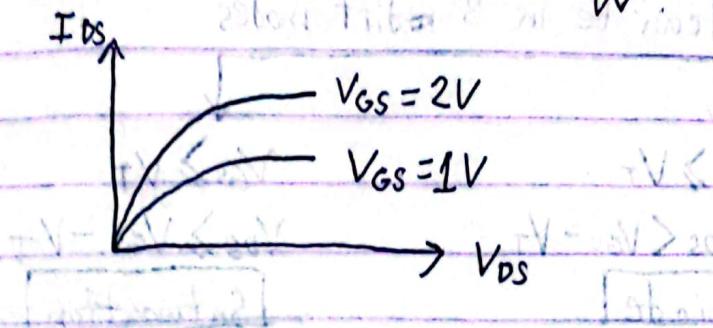- But since V_{DS} is applied V_{ov} will decrease.
- Voltage diff between V_{GS} and V_D , $= V_{GS} - V_D = V_T + (V_{ov} - V_D)$
- $\therefore V_{DS} \leq V_{GS} - V_T$ [This mode is called the triode mode of the MOSFET]
- * $I_{DS} = K_n \frac{W}{L} [V_{ov} \cdot V_{DS} - \frac{1}{2} V_{DS}^2]$ (will be used more)



The relationship between I_{DS} and V_{DS} will non-linear (will be quadratic)


- If V_{DS} is small, we can ignore V_{DS}^2 (mA/V^2)
- * $\therefore I_{DS} = K [V_{ov}] V_{DS} = K [V_{GS} - V_T] V_{DS}$, where $[K = K_n \frac{W}{L} \text{ in } \text{nA/V}^2]$

- * Case-5: $V_{DS} = V_{GS} - V_T = V_{ov}$, $V_{GS} \geq V_T$

- The channel will be pinch offed it will look like a triangle shape.
- Current, I_{DS} can be found by replacing V_{DS} with V_{ov} ,
- $I_{DS} = K [V_{ov} \cdot V_{ov} - \frac{1}{2} V_{ov}^2]$

$$\Rightarrow I_{DS} = \frac{k}{2} V_{ov}^2 = \frac{k}{2} [V_{GS} - V_T]^2$$


- * Case-6: $V_{DS} > V_{GS} - V_T$

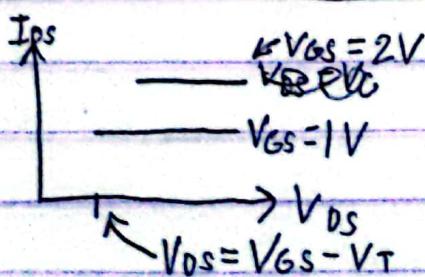

$$I_{DS} = \frac{k}{2} [V_{GS} - V_T]^2$$

- The current is not increasing due to the saturation phenomenon, due to "pinching off of the channel."

Summary:

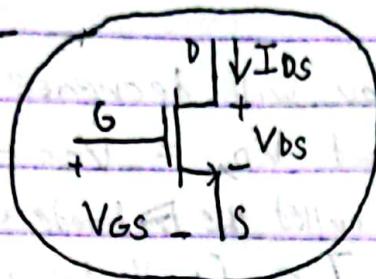

MOSFET

can be in 3 diff modes

$$V_{GS} < V_T$$

Cutoff

$$I_{DS} = 0$$

$$V_{GS} > V_T$$

Triode


$$I_{DS} = K [(V_{GS} - V_T) - \frac{1}{2} V_{DS}] V_{DS}$$

$$V_{DS} > V_{GS} - V_T$$

Saturation

$$I_{DS} = \frac{K}{2} [V_{GS} - V_T]^2$$

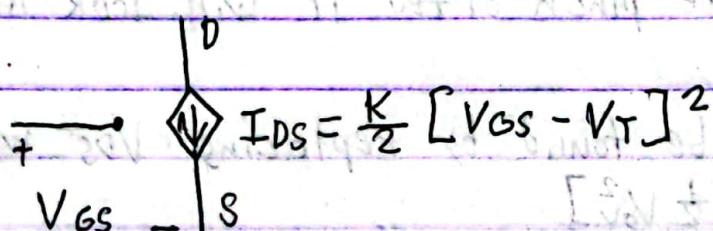- * In the saturation mode MOSFET will behave like a current source acting like a controlled by V_{GS} .




- It is not a linear device.

- * Another condition the MOSFET can have is:

$$V_{DS} \ll V_{GS} - V_T \Rightarrow \boxed{\text{R model}}$$

$$I_{DS} = \frac{1}{R_{ON}} \cdot V_{DS}$$

$$R_{ON} = \frac{1}{K(V_{GS} - V_T)}$$

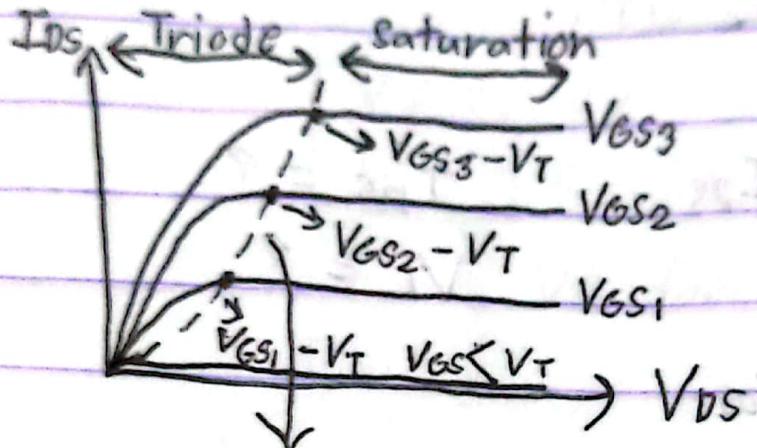

$$V_{GS3} > V_{GS2} > V_{GS1}$$

Separator between triode and saturation region


- This threshold is defined as:

$$V_{DS} = V_{GS} - V_T$$

$$I_{DS} = \frac{K}{2} [V_{GS} - V_T]^2$$

$$I_{DS} = \frac{K}{2} \cdot D V_{DS}^2 \rightarrow \text{eqn of the separator.}$$

MOSFET in a DC circuit:

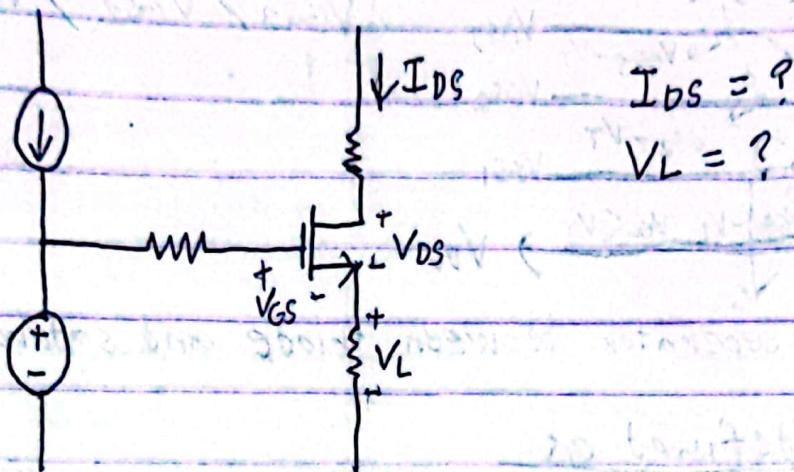

* We need to use Method of Assumed state to solve it.

① Assume:

Cutoff: $I_{DS} = 0$

Triode: $I_{DS} = K[V_{GS} - \frac{1}{2}V_{DS}]V_{DS}$, where, $[V_{GS} = V_{GS} - V_T]$

Saturation: $I_{DS} = \frac{K}{2} [V_{GS} - V_T]^2$

• Start with saturation then triode then Cutoff.

② Solve:

KCL

KVL

③ Verify:


Cutoff: $V_{GS} < V_T$

Triode: $V_{GS} \geq V_T$, $V_{DS} \leq V_{GS} - V_T$

Saturation: $V_{GS} \geq V_T$, $V_{DS} \geq V_{GS} - V_T$

* $I_{G0} = 0$ always for MOSFET

Examples:

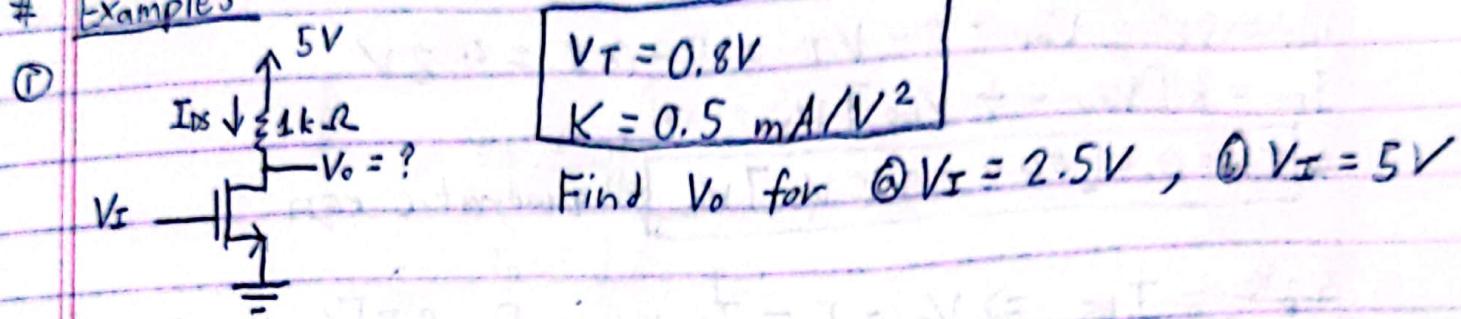

② MOSFET in Saturation mode (assumed)

$$V_S = 0, V_G = V_I = 2.5V, V_{GS} = V_G - V_S = 2.5V$$

$$\therefore I_{DS} = \frac{k[V_{GS} - V_T]^2}{2} = \frac{0.5[2.5 - 0.8]^2}{2} = 0.7725 \text{ mA}$$

$$I_{DS} = \frac{5 - V_o}{R}$$

$$V_o = 5 - I_{DS} \times R = 5 - 0.7725 \times 1 = 4.2275V$$

$$V_{DS} = V_o - V_S = V_o - 0 = V_o = 4.2275V$$

Check:

- $V_{GS} \gg V_T$

$$2.5 \gg 0.8 \text{ (True)}$$

- $V_{DS} \gg V_{GS} - V_T$

$$\Rightarrow V_o \gg V_{GS} - V_T$$

$$\Rightarrow 4.2275 \gg 2.5 - 0.8$$

$$\Rightarrow 4.2275 \gg 1.7 \text{ (True)}$$

} Since both conditions are fulfilled so the assumption is correct.

③ $V_I = 5V, V_{GS} = V_I - V_S = 5V, \text{ Assume Saturation mode:}$

$$\textcircled{1} I_{DS} = \frac{k}{2} [V_{GS} - V_T]^2 = \frac{0.5}{2} [5 - 0.8]^2 = 4.41 \text{ mA}$$

$$V_o = 5 - I_{DS} \times R = 5 - 4.41 \times 1 = 0.59V$$

Checking:

- $V_{GS} \gg V_T$

$$5 \gg 0.8 \text{ (True)}$$

•

$$V_{DS} \gg V_{GS} - V_T$$

$$\Rightarrow V_o \gg V_{GS} - V_T$$

$$\Rightarrow 0.59 \gg 5 - 0.8 \text{ (False)}$$

} Assumption is not true.

* Assume Triode Mode:

$$V_{GS} = 5V, V_{ov} = 5 - V_T = 5 - 0.8 = 4.2V$$

$$I_{DS} = K [V_{ov} - \frac{1}{2} V_{DS}] V_{DS}$$

$$\Rightarrow I_{DS} = 0.5 [4.2 - 0.5 V_o] V_o \quad \text{quadratic eqn}$$

$$\frac{5 - V_o}{R} = I_{DS} \Rightarrow V_o = 5 - I_{DS} \times R = 5 - 0.5 [4.2 V_{DS} - 0.5 V_{DS}^2]$$

$$\Rightarrow V_o = 5 - 2.1 V_{DS} + 0.25 V_{DS}^2$$

$$\Rightarrow 0.25 V_{DS}^2 - 3.1 V_{DS} + 5 = 0 \quad [V_{DS} = V_o]$$

$$\Rightarrow 0.25 x^2 - 3.1 x + 5 = 0$$

$$\Rightarrow x = 1.9V, x = 10.492$$

$$\therefore V_o = 1.9V$$

* Check:

$$V_{GS} > V_T$$


$$5 > 0.8 \text{ (True)}$$

$$V_{DS} < V_{GS} - V_T$$

$$1.9 < 5 - 0.8 \text{ (True)}$$

* ∴ Assumption is correct.

#10 Example:

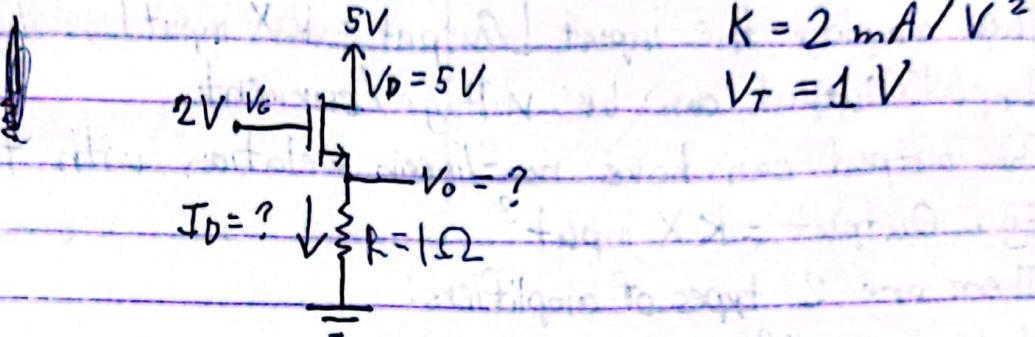

* Assume Saturation mode:

$$V_{GS} = V_G - V_S$$

$$\Rightarrow V_{GS} = 2 - V_0$$

$$I_{DS} = \frac{K}{2} [V_{GS} - V_T]^2$$

$$\Rightarrow I_{DS} = \frac{2}{2} [2 - V_0 - 1]^2$$

$$\Rightarrow I_{DS} = [1 - 2V_0 + V_0^2]$$

$$I_D = \frac{V_0 - 0}{R} \Rightarrow V_0 = I_D R$$

$$\text{Q1) } V_0 = I_{DS} \cdot X R = I_{DS} \times 1 = 1 - 2V_0 + V_0^2$$

$$\Rightarrow V_0^2 - 3V_0 + 1 = 0$$

$$\therefore V_0 = 2.6V \text{ and } V_0 = 0.4V \checkmark$$

$$2 - V_0 > 1V \Rightarrow V_0 < 1V, \therefore V_0 = 0.4V$$

$$\therefore I_{DS} = 0.4mA$$

* Check:

$$\bullet V_{GS} > V_T$$

$$1.6 > 1 \text{ (True)}$$

$$\bullet V_{DS} > V_{GS} - V_T$$

$$\Rightarrow 5 - V_0 - V_S > V_{GS} - V_T$$

$$\Rightarrow 5 - 0.4 > 1.6 - 1$$

$$\Rightarrow 4.6V > 0.6V \text{ (True)}$$

\therefore The assumption is ~~True~~ correct.