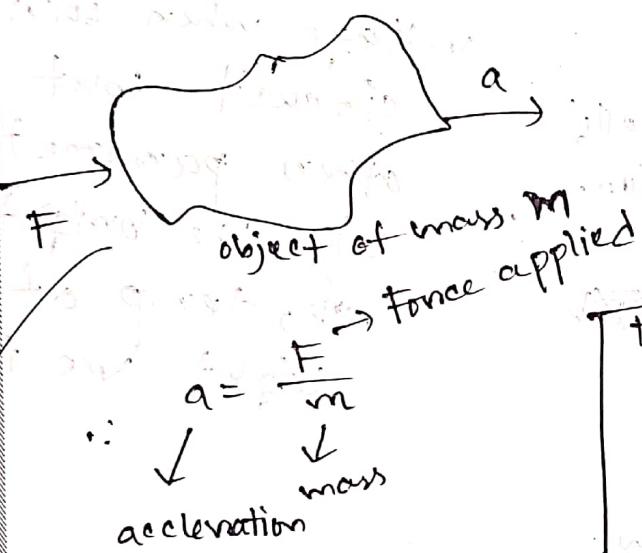


(Lecture 6 Rough)

Lumped Matter Abstraction:

making something easier
or removing something to
make something simple.
[that is just focusing
the important part
and ignoring others
stuff.]




- 1. shape of object
- 2. Temperature
- 3. colour

etc.

only considering mass of object
and ignoring other stuff,
so this is kind of abstraction.
our point mass abstraction.


That's why we
represent them as
a point of mass.

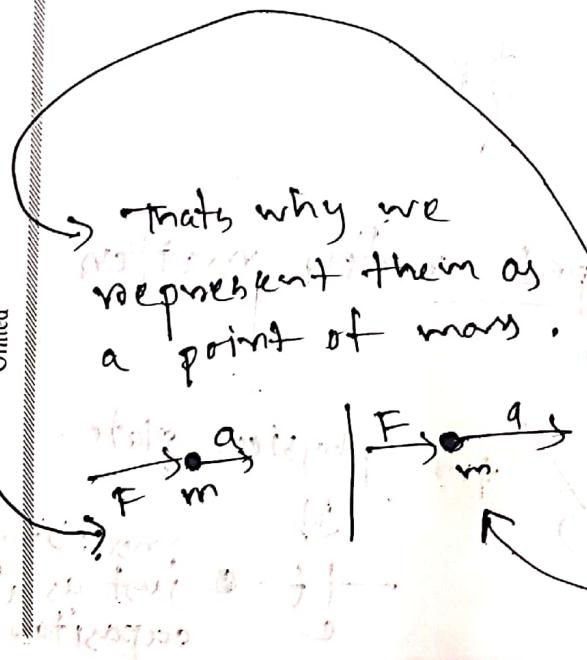suppose now the shape of object
is ~~triangle~~ triangular but
same mass m , so in
this case if F is equal
then a will not
change.



similarly for electrical circuit:

we can find the potential difference in

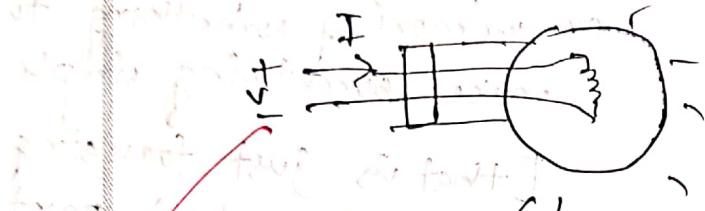

"Actual way" \rightarrow maxwell's
equation.

more general

$$\nabla \times \vec{E} = -\frac{\partial}{\partial t} \vec{B}$$

$$\nabla \times \vec{E} = \frac{\partial \vec{B}}{\partial t}$$

"Easy way" \rightarrow ohm's law:

physical

to convert the circuit

to simplified way with resistors

without considering the materials.

otherwise to build the circuit

is difficult

so we do it

on paper

and draw

the circuit

on paper

Sub.: _____


SAT SUN MON TUE WED THU FRI

DATE: / /


Now How can we characterize the ~~with~~ Capacitance & Resistance R of Resistor?

~~Model~~ itself which is what we want

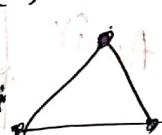For characterization, we need some distinct features.



triangle
↓
3 corners

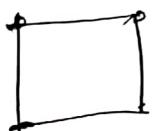

square
↓
4 corners

For example:

If we have 12 resistors
available and want
to make 4 resistors

the question is: For unique characterization
we need clear definition of these
distinct features.

Similarly for circuit elements like resistor,
voltage source, current source, ~~and~~ capacitor,
etc. we ~~not~~ ~~can~~ use I V characteristic
to characterize the element.

Sub.: _____


SAT SUN MON TUE WED THU FRI

DATE: / /

I-V characterization:

Question Is it possible?

lets we make a device Name Ashik.

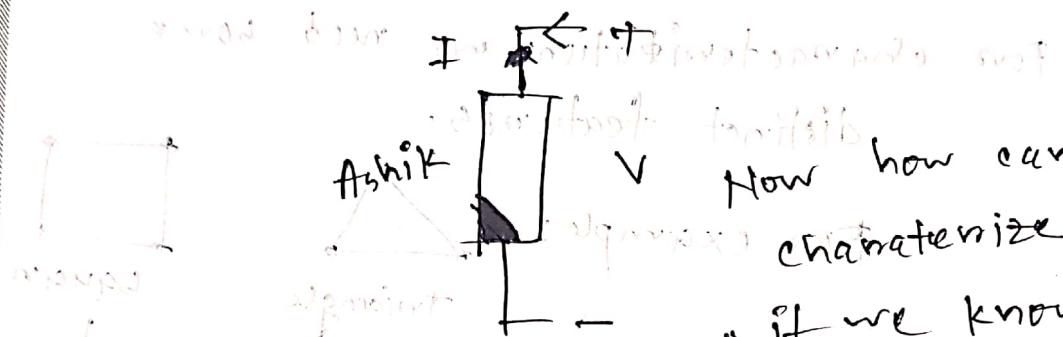

Now how can we characterize Ashik?

⇒ if we know the relation between current I and voltage V we can characterize Ashik.

I-V characteristic is the relation between voltage and current

lets say we get for device Ashik

$$I = \frac{V}{X}$$

And it is similar to $I = \frac{V}{R}$


so we can see its like a resistor. so we can say device Ashik = resistor. (→)

Representation of IV characteristic:

① Tabular form

~~Graphical form~~
not efficient
(what if infinite length table?)


V	I (mA)
1	0.5
2	1
-1	2

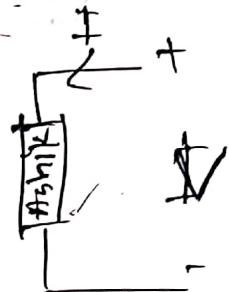

② Functional form


$$I = f(V) \text{ or } V = f(I)$$

* For example.

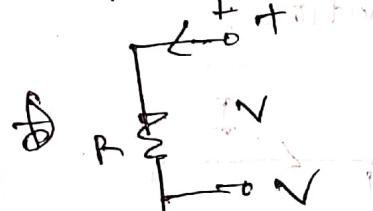

$$f(x) = ?$$

$$I = \frac{1}{R} V$$

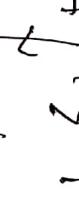


$$I = C \frac{dV}{dt}$$


$$V = L \frac{dI}{dt}$$

induction

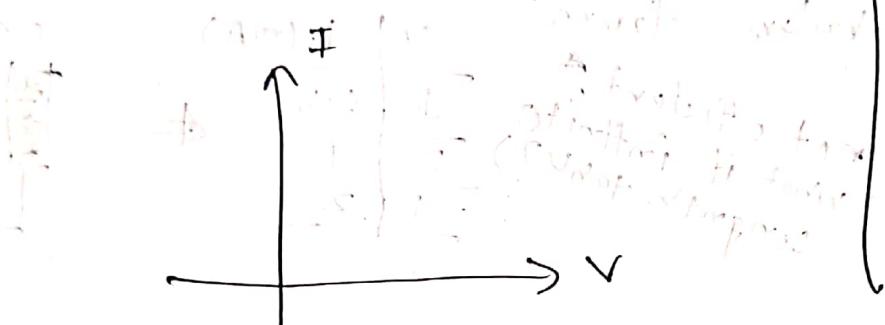③ Graphical form: It can also be drawn from it.




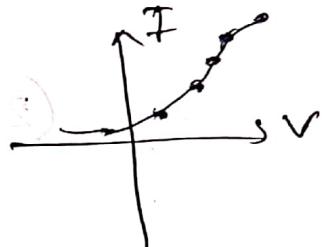We can also draw the graph from Tabular form



$$(T) \rightarrow v \text{ vs } (v) \rightarrow I$$


sign convention:

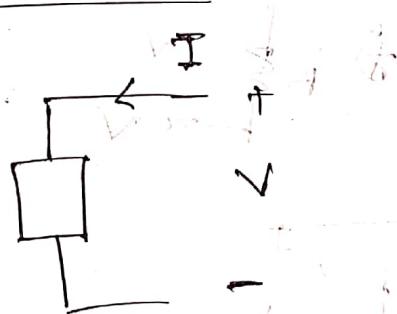


passive sign convention.
→ current flows from positive to negative terminal.

active current enters through the positive terminal.

How to find IV curve:

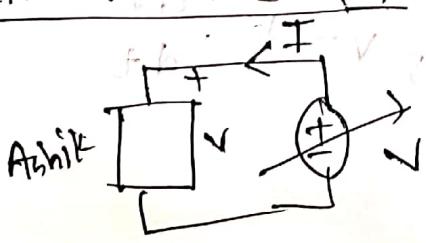


	$I(\text{mA})$
1	1
2	2
3	3
4	4

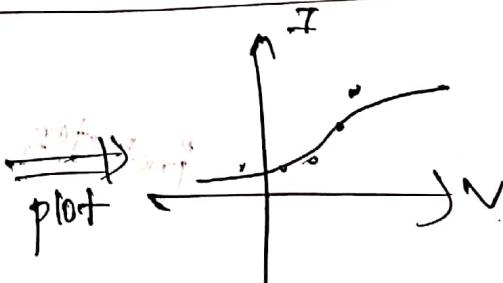

IV characteristic of simple linear device:

why linear \Rightarrow because their IV characteristic can be drawn using single straight line.


(1) IV char. of Resistors

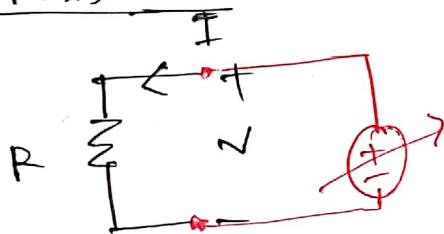

$$I = \frac{V}{R}$$


$$y = mx$$

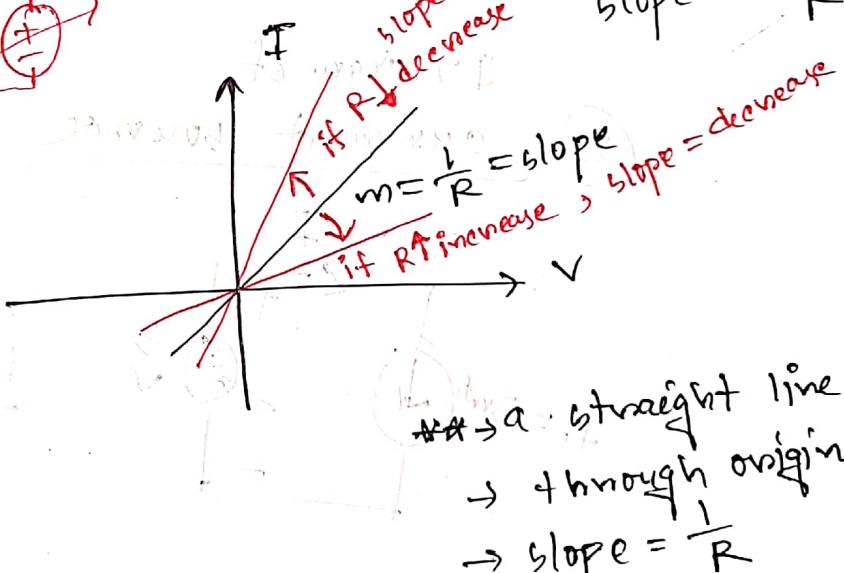slope = $m = \frac{1}{R}$
where slope $m = \frac{1}{R}$



Two extremes

(2) Now if $R = \infty$

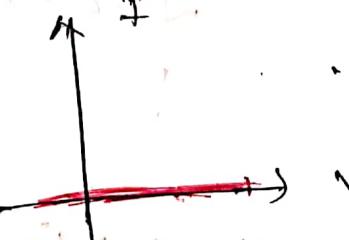

$$\therefore I = 0$$



* if $R = 0$ required to obtain $V = 0$

if $R = 0$ $V = 0$ \Rightarrow $I = 0$ (no current)



I - V char. of current source

(2)

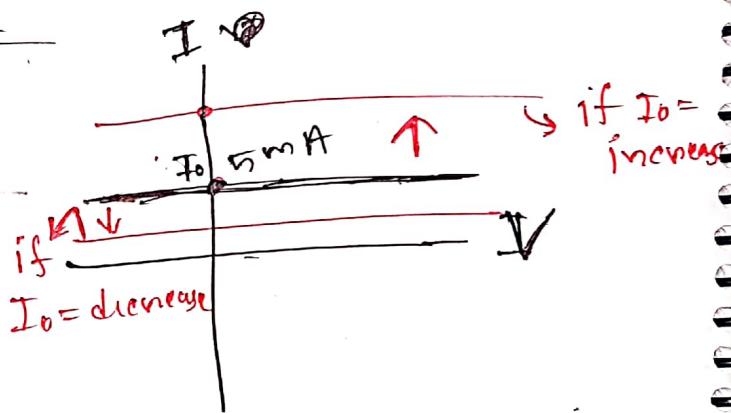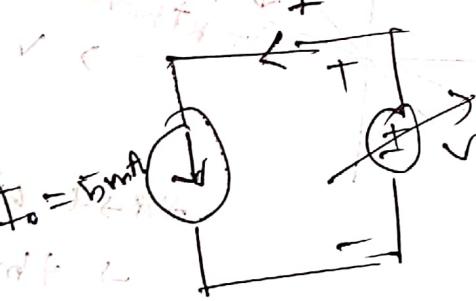

Now if

$$V = 1V, I = 5mA$$

$$V = 2V, I = 5mA$$

$$I = 5mA$$

$$I = 5mA$$

$$I = I_0$$

But here polarity matters.


∴ straight line parallel to x-axis (voltage axis)
→ cuts the y-axis (current axis) at I_0 (value of current source)

Sub.: _____



SAT SUN MON TUE WED THU FRI
□ □ □ □ □ □ □

DATE: / /

lets fit it like:

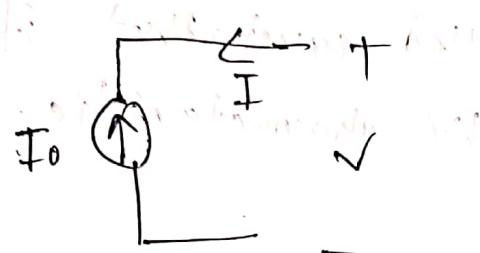

$$I = -I_0$$

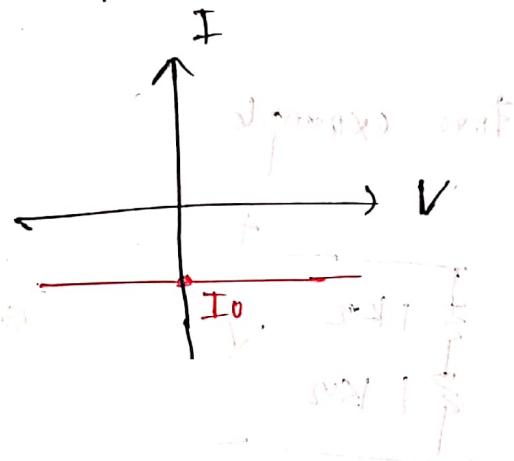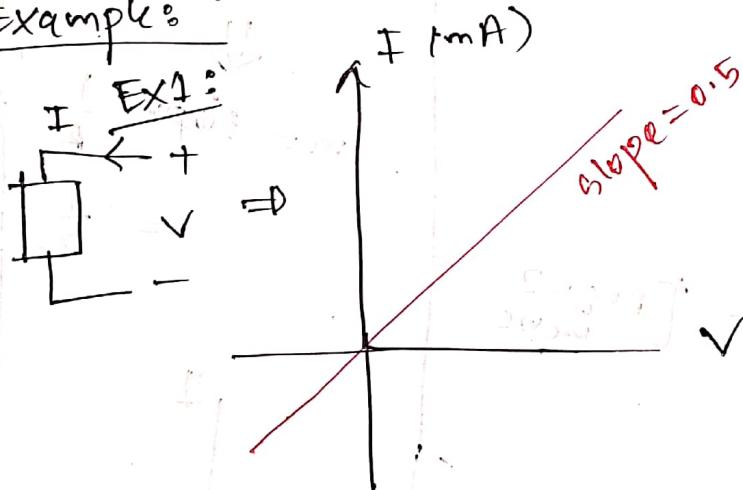Example:

slope = 0.5

\sqrt{V} (volt)

Ques1: what is the model of this device?

Ans: $I = \frac{V}{R}$

Ques2: what are the parameters?

Ans: ~~R~~ parameter, that is R .


$$\therefore R = \frac{1}{\text{slope}} = \frac{1}{0.5} = 2 \text{ k}\Omega$$

since current in mA



Equivalent circuit

★ ★ ★ Two circuit will be called equivalent if they have same IV characteristic.

For example

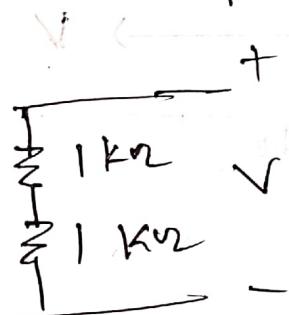

or
or

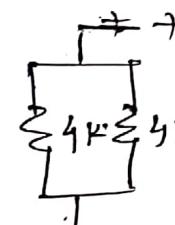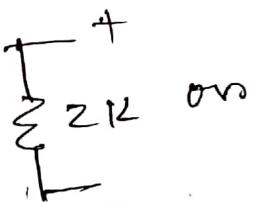

$$m = \text{slope} = \frac{1}{R}$$


$$\text{After } \frac{1}{2V} \quad \text{reg = 2 m/s}$$

$$m = \text{slope} = \frac{1}{R}$$

$$m = \text{slope} = \frac{1}{2}$$


Y-axis shift for 360 m/s in the following graph

Both the graphs of capacitor and resistor are equivalent.

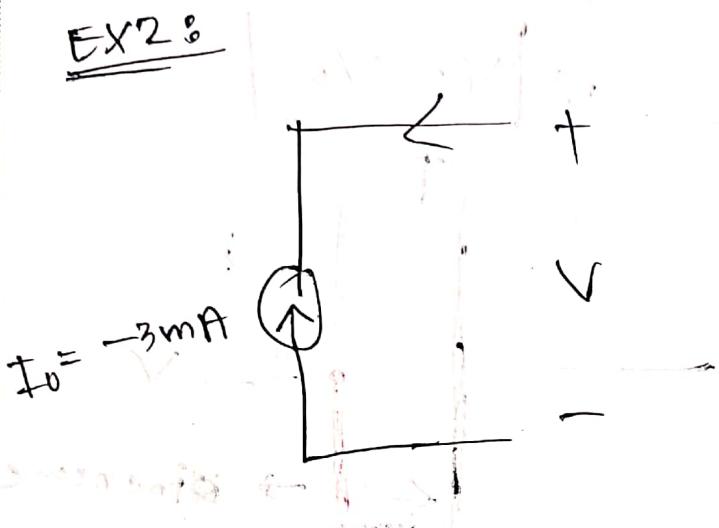~~3. IV char. of~~EX 2:

Q: Draw its IV curve?


Ans: $I = I_0 + \frac{V}{R}$

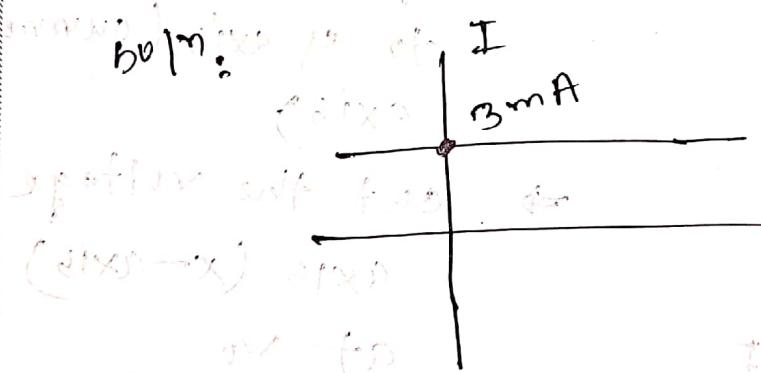


$$\therefore \text{Here } I = -I_0$$

$$= -(-3) \\ = 3 \text{ mA}$$

③ Voltage source?

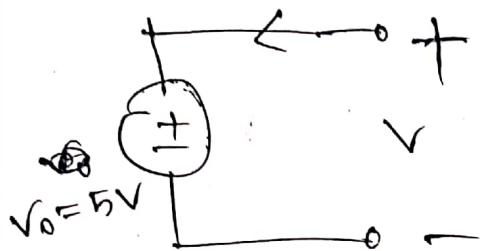

$$V = V_0$$

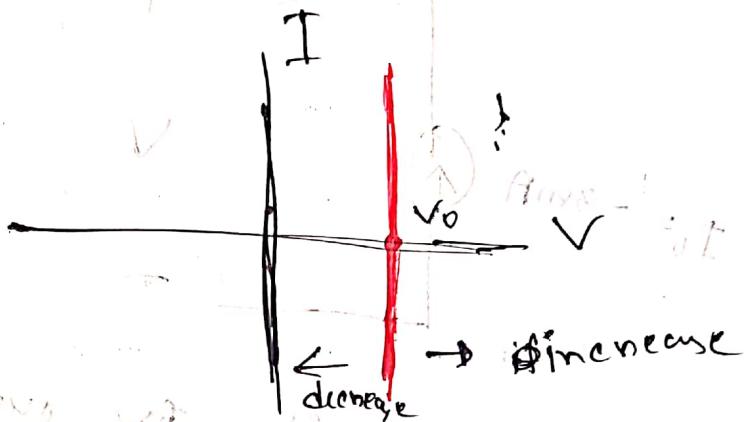


\Rightarrow straight line parallel


\Rightarrow to y axis (current axis)

\Rightarrow cut the voltage axis (x -axis)


at V_0

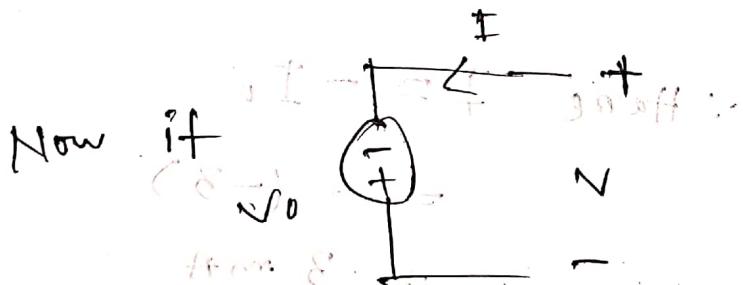


$$V = -V_0$$

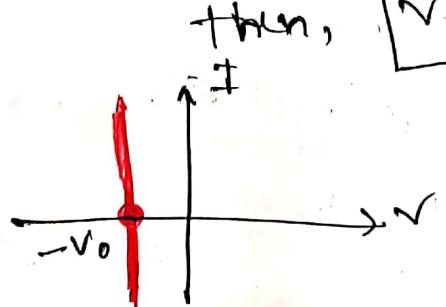

④ IV of short circuit

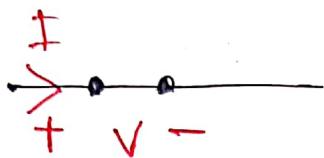

$$V = 0$$

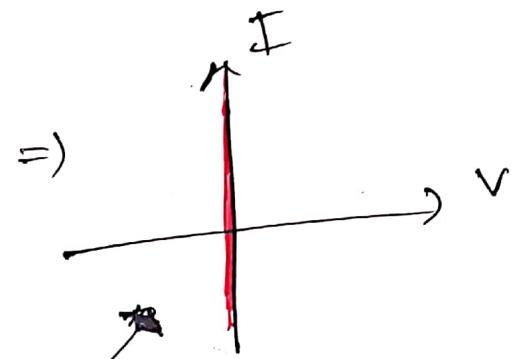


\therefore From resistors

IV char. can
say here

$$R = 0$$

So short circuit,
resistor $R=0$ circuit
and voltage
source $V_0=0$ V
are equivalent
because same IV

⑤ IV of open circuit

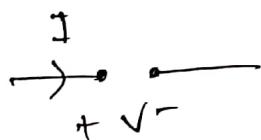

$$I = 0$$




\therefore From resistors
IV char can
say here

$$R = \infty$$





Similarly,
open circuit,
resistor $R=\infty$ circuit
and ~~no~~ current
source with $I_0=0$
are equivalent
circuit [Same IV]

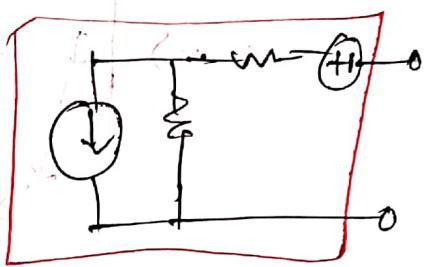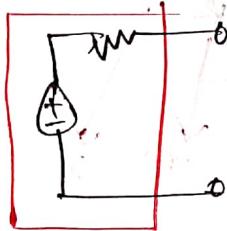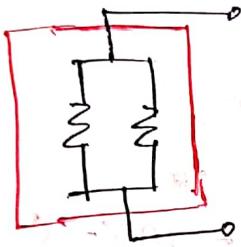IV characteristic of compound nonlinear devices:



→ Go thousands of combination possible.
But if we know just two ~~circuits~~ circuits
IV char. we can then find any others
easily. These two are:
circuit IV

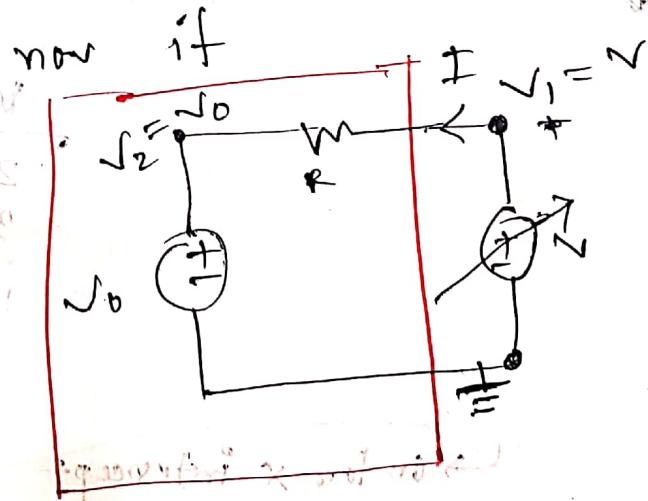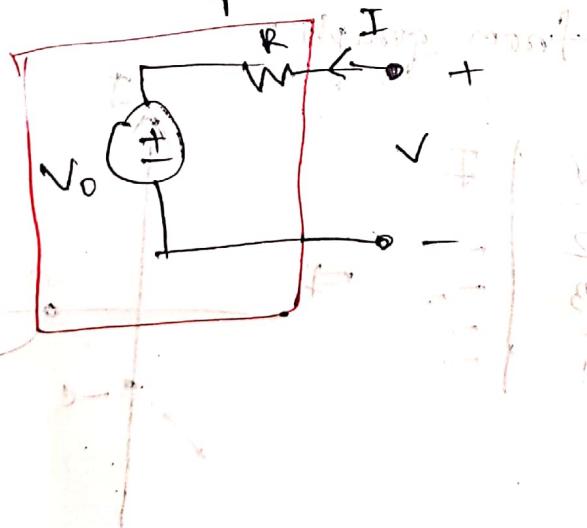
① voltage source in series with resistors.



$$\therefore I = \frac{V_0 - V}{R} = \frac{V_0 - V_0}{R} \text{ if } V_0 \text{ is constant}$$

$$I = \frac{1}{R} V - \frac{V_0}{R}$$

For example:

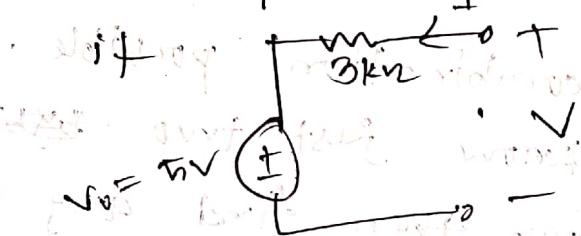


$$\therefore y = mx + c$$

$$m = \text{slope} = \frac{1}{R}$$

$$-c = y \text{ intercept} = -\frac{V_0}{R}$$

$$\therefore I = \frac{1}{3} : \text{V from } \frac{5}{3} \text{ m.s.d.}$$

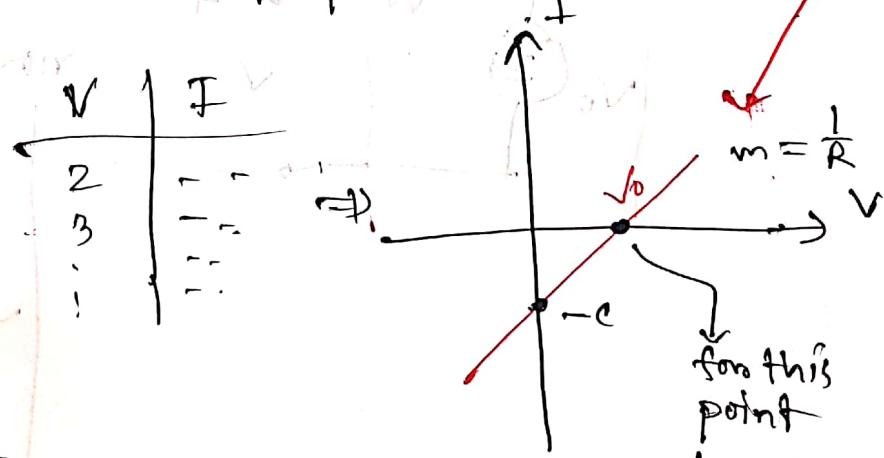From this we can create a table from graph:



For x-intercept:

$$y=0 \text{ on } I=0$$



$$\therefore 0 = mx - c \Rightarrow \frac{V_0 R}{1/R} = V_0 \therefore x = \text{x-intercept at } V_0$$

Sub.: _____

SAT SUN MON TUE WED THU FRI

DATE: / /

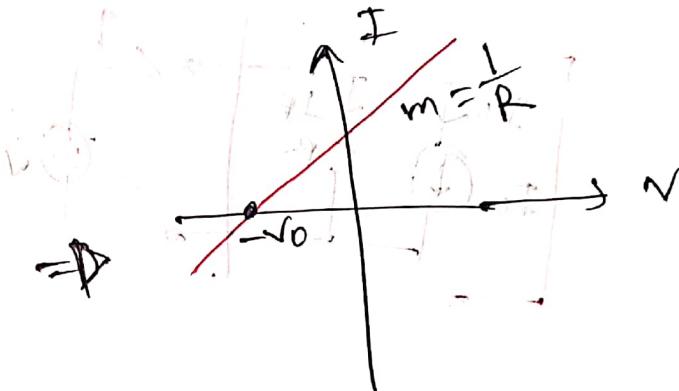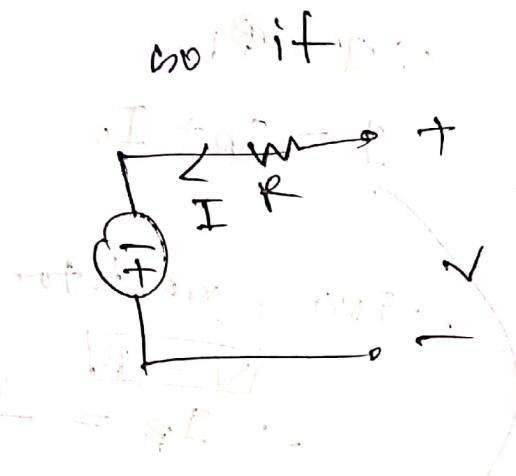~~Efficiency of source~~
Hence polarity of voltage source matters.




$$I + \frac{V_0}{R} = I$$

$$I + \frac{V_0}{R} = I$$

$$I = \frac{V_0}{R}$$

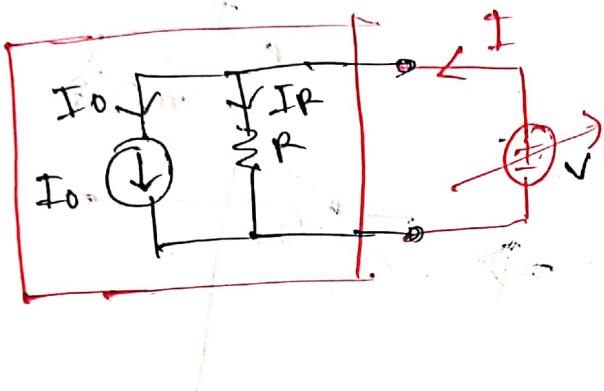② current source in parallel with resistor:



$$\therefore \text{QDPI}$$

$$I = I_R + I_0$$

For resistor


$$V = IR$$

$$\therefore I_R = \frac{V}{R}$$

$$I = \frac{V}{R} + I_0$$

$$\Rightarrow I = \frac{1}{R}V + I_0$$

$$y = mx + c$$

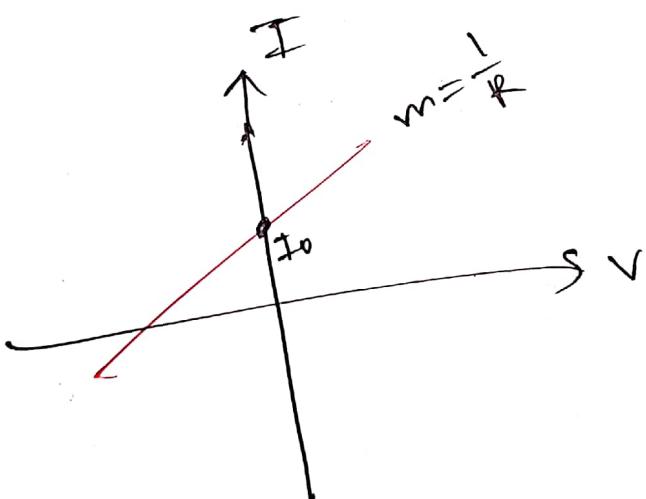

Sub.: _____

SAT SUN MON TUE WED THU FRI



DATE: / /

These two circuits are equivalent. //



cause same IV curve can possible.
by source transformation,
under certain condition.

Source transformation

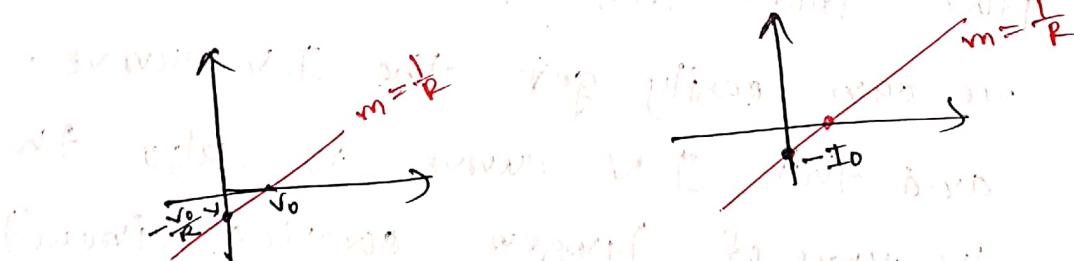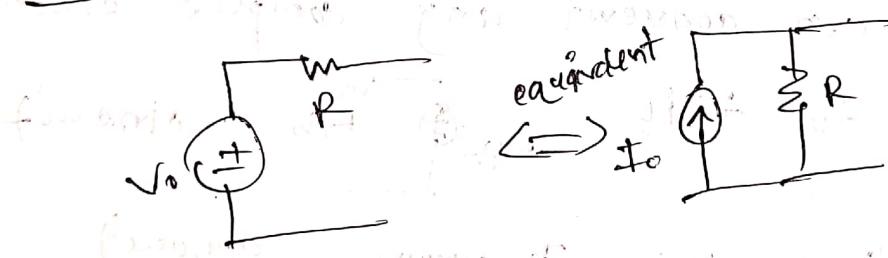


$$\text{and by Ohm's law } \frac{V_0}{R} = I_0$$

therefore


$$\therefore V_0 = I_0 R$$

equation of source transformation.

Thevenine and IV characteristic:

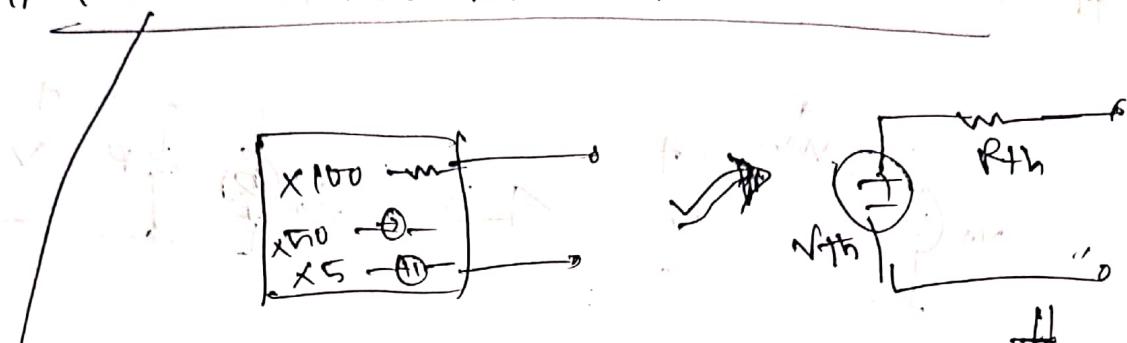

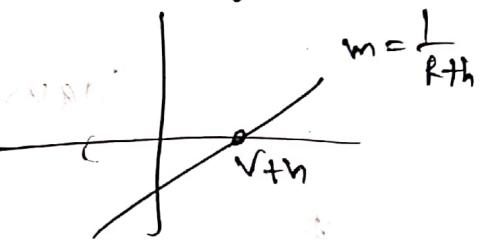Now we can convert this complex circuit into this simple Thevenine circuit by finding Thevenine voltage and Thevenine resistance.



So we can convert any complex circuit into this Thevenine circuit.

Now from this Thevenine circuit we can easily get the IV curve and this IV curve is also the IV curve of larger complex circuit because that larger circuit and the Thevenine circuit are equivalent.