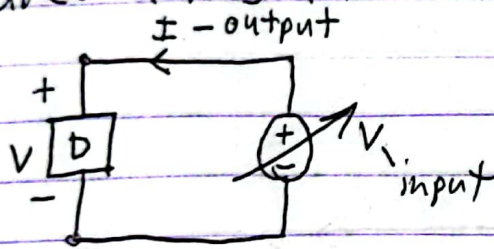



IV Characteristics of a device:

- It is the relationship between current and voltage across a device, it is used to describe the characteristics of the device.
- A table of $I-V$ is made by connecting a voltage source across the device and varying the voltage. Like:



V	I
...	...
...	...
...	...

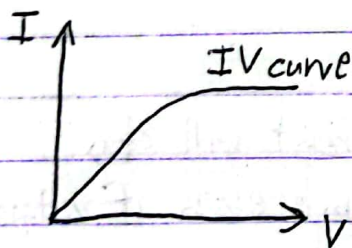- It can also be done using a graph which would look like:




- $I-V$ Char is also known as Input-output relation of a device.

Lecture - 3 (P - 2)

$I-V$ Char of simple linear elements:


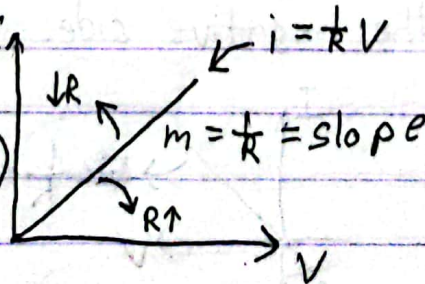
- * A device is linear if the relation between $I-V$ is a straight line graph. eg: resistor ($V=IR$ eqn) $\Rightarrow V \propto I$
- * $I-V$ curve of resistor: $I \propto V$
- If $R=\infty$, $m(\text{slop})=0$ (open circ)
- " $R=0$, " " $=\infty$ (short circ)




I-V Char of independent sources:

* V-source ($V_0 = \text{constant}$):


• Graph:

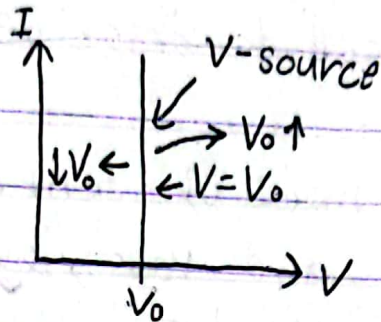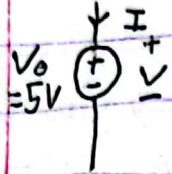

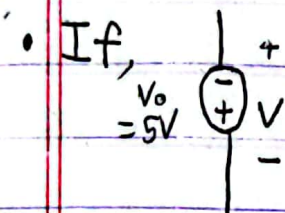• What ever the current is, voltage will always stay the same.





then graph,


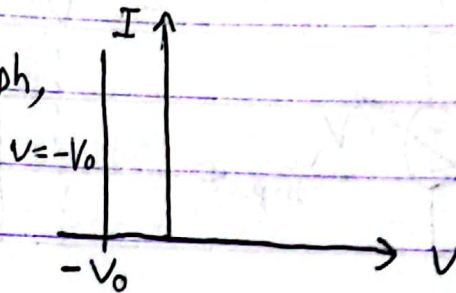


I-Source ($I_0 = \text{constant}$):

• Graph:

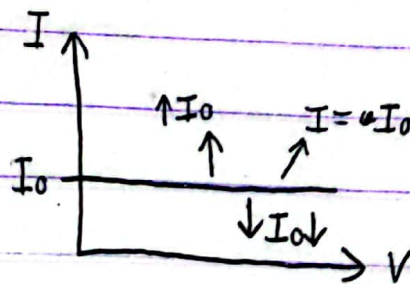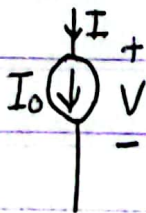


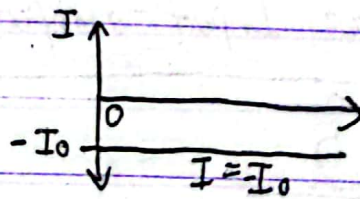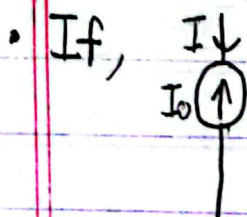• Current will stay same even if voltage changes.




If polarity and source direction ~~is~~ is same then the straight line will be in the positive side otherwise it will be on the negative side.

Resistance:

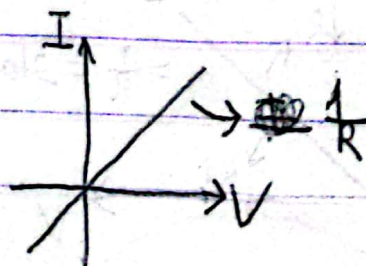


I-V char of Compound elements:

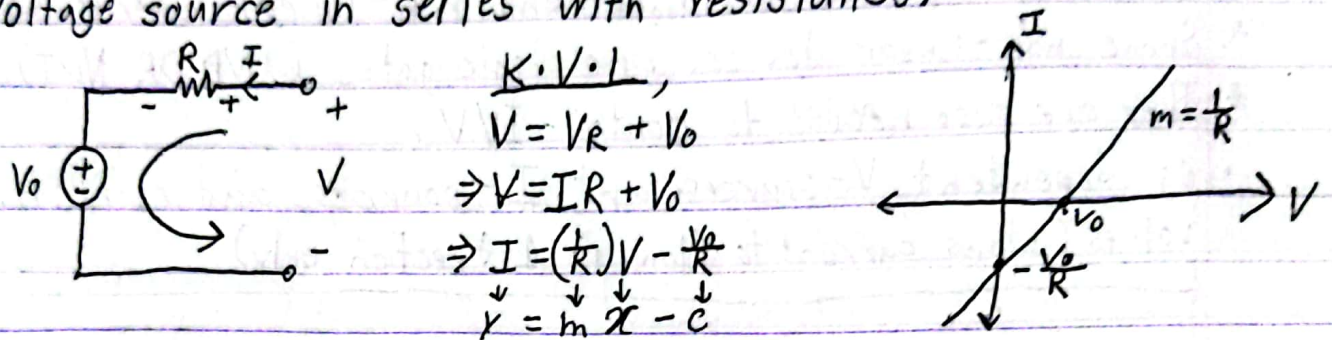- * Compound elements = combination of simple elements.
- * Voltage source in series with resistance.



- To find the x -intercept put $I=0$ in $I = \left(-\frac{1}{R}\right)V - \frac{V_0}{R}$.

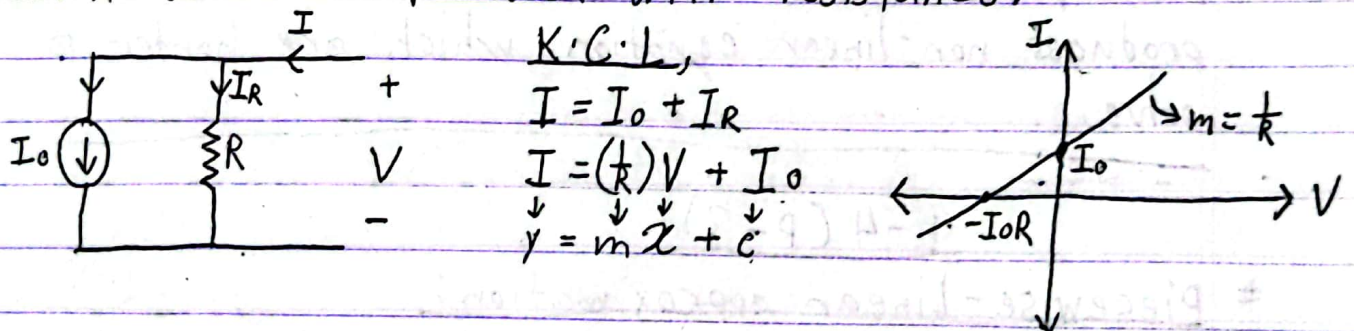- * Current source in parallel with resistance.




- To find the x -intercept put $I=0$ in $I = \left(\frac{1}{R}\right)V + I_0$.
- If I -source is reversed, The eqn becomes, $I = \left(-\frac{1}{R}\right)V - I_0$.
- * If V -source is " , " , " , $I = \left(-\frac{1}{R}\right)V + \frac{V_0}{R}$.

L-3 (P-5)

Equivalent Circuit:

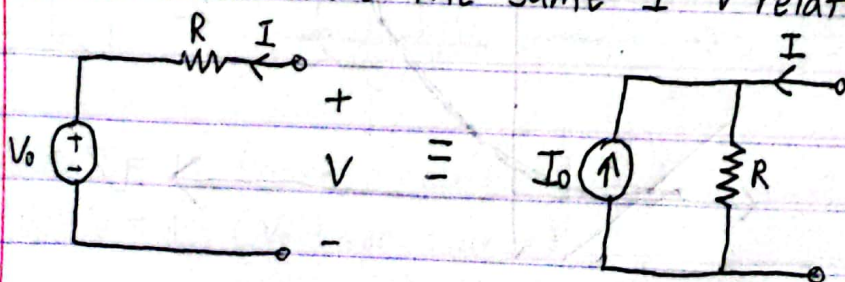- * If 2 devices have the same I-V relation they are called equivalent circuit



if $V_0 = I_0 R$, this is also known as source transformation.

Non-Linear Devices:

- * Devices whose I - V ^{graph} ~~curve~~ is not a ^{single} straight line.
 - * They are required to implement non-Linear operations.
 - * Some non-linear devices are logic gates (AND, OR, NOT)
 - * They are also needed to control I/V .
 - eg: dependent V -sources and I -sources, and switch, valves (allows current to flow in 1 direction only).
-

L-4 (P-2)


Problems with Non-Linear devices:


- * They produce non-linear I - V which ~~intern~~ inturn produces non-linear equation which are harder to solve.
-


L-4 (P-3)

Piecewise-Linear approximation:

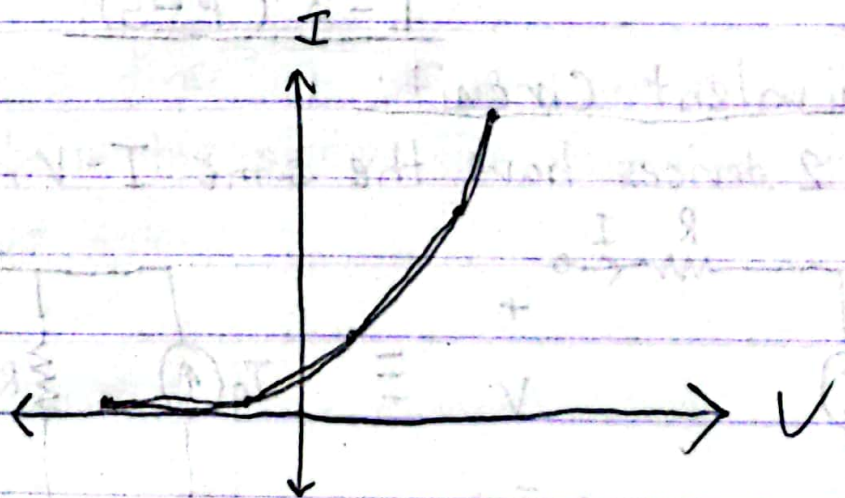- * It is a technique used to solve non-linear eqn.
- * Here a curve is divided into segments of straight lines.
- * The more pieces the graph is broken into the more accurate it is.




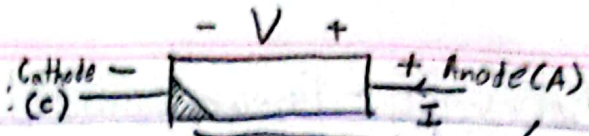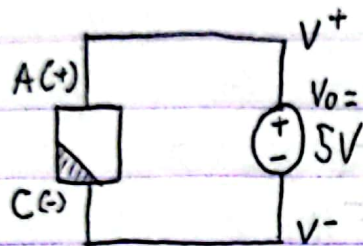- * Symbol of non-linear device:  , $V = V_A - V_C$
- * They have polarity, The (-ve) side is always marked.
- * If $V > 0 \Rightarrow V_A > V_C \Rightarrow$ Forward Bias
- " $V \leq 0 \Rightarrow V_A \leq V_C \Rightarrow$ Reverse "




Forward Bias
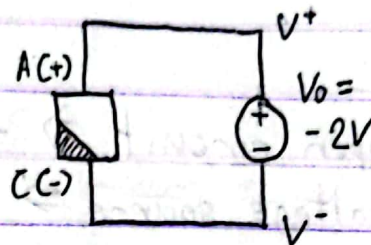
$$\begin{aligned} V_0 &= V^+ - V^- \\ &= V_A - V_C \\ &= 5V \end{aligned}$$




Reverse Bias
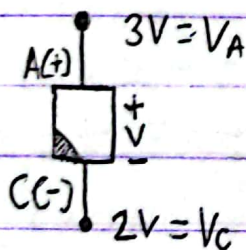
$$\begin{aligned} V_0 &= V^+ - V^- \\ &= V_A - V_C \\ &= -2V \end{aligned}$$



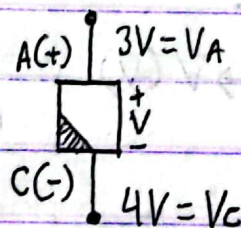
$$\begin{aligned} V &= V_A - V_C \\ &= 1V \text{ (F.B)} \end{aligned}$$



$$\begin{aligned} V &= V_A - V_C \\ &= -1V \text{ (R.B)} \end{aligned}$$

- * In a non-linear device 'I' enters through the anode.



*

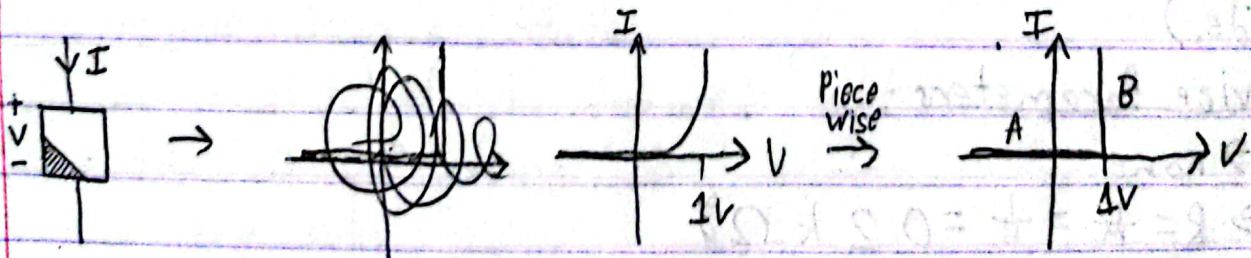

A $\Rightarrow I = 0$, (Open circuit)

B $\Rightarrow V = 1$, (Voltage source)

Piecewise-linear modelling example:

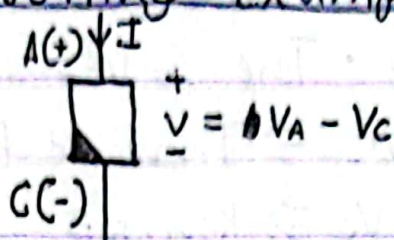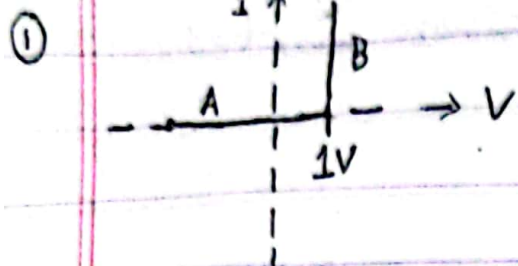

* Device modelling:



A $\Rightarrow V < 1 \Rightarrow$ open circuit \Rightarrow

B $\Rightarrow I > 0 \Rightarrow$ voltage source \Rightarrow

* Device parameters:

A \Rightarrow no parameters

B $\Rightarrow V_0 = 1V$

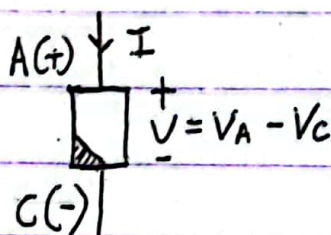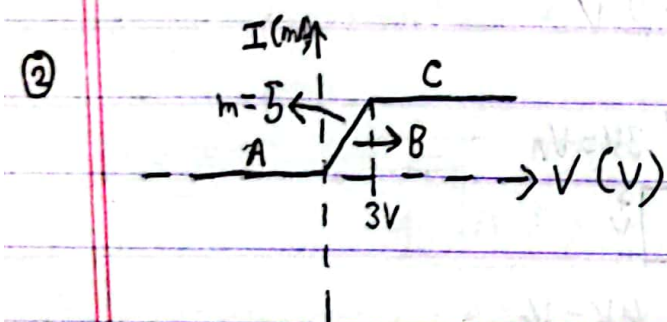

* Dev modelling:

A $\Rightarrow V \leq 0V \Rightarrow$

B $\Rightarrow 0 < V < 3V \Rightarrow$ ($R = \frac{1}{m} = \frac{1}{5} = 0.2 k\Omega$)

C $\Rightarrow V > 3V \Rightarrow$ (Direction of I is Anode to cathode because the line 'C' intercepts the y-axis in the positive side.)



* Device Parameters:

A \Rightarrow none

B $\Rightarrow R = \frac{1}{m} = \frac{1}{5} = 0.2 k\Omega$

C $\Rightarrow y = mx = 5 \times 3 = 15 mA$

③

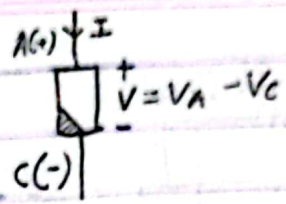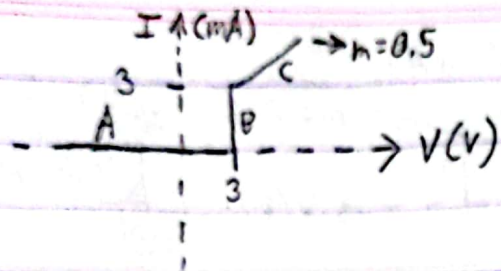

* Device Model:

A $\Rightarrow V \leq 3V \Rightarrow$

B $\Rightarrow 0 < I \leq 3mA \Rightarrow$

C $\Rightarrow V > 3V \Rightarrow$

* Parameters:

A \Rightarrow none

B $\Rightarrow V_0 = 3V$

C $\Rightarrow y = mx + c \Rightarrow 3 = 0.5 \times 3 + c \Rightarrow c = 1.5, \therefore y = 0.5x + 1.5$
 $R = \frac{1}{m} = \frac{1}{0.5} = 2 k\Omega$




- For current source with parallel resistor, put $x = 0$ in $y = 0.5x + 1.5$
 $\therefore y = 1.5, \therefore I = 1.5 mA$
- For voltage source with resistor in series, put $y = 0$ in $y = 0.5x + 1.5$
 $\therefore x = -3V$

L-4 (P-7)


Method of Assumed State:

- Assume a state of the device.
- Solve the circuit using that model.
- Check the soln.
- Repeat (1-3) if mismatch.


Eg:

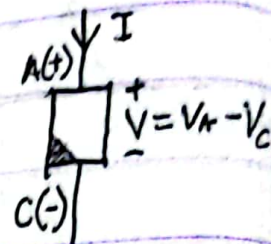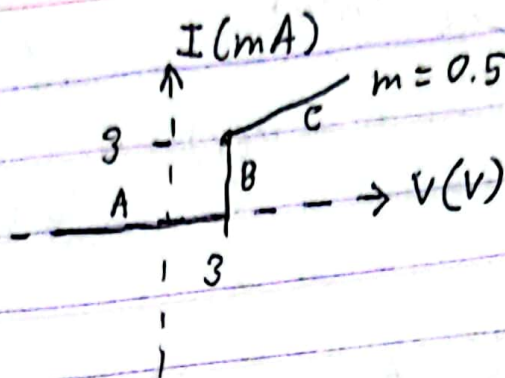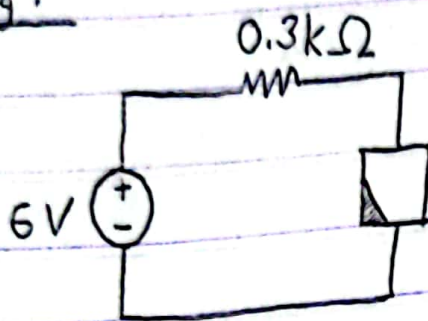

Modeling:

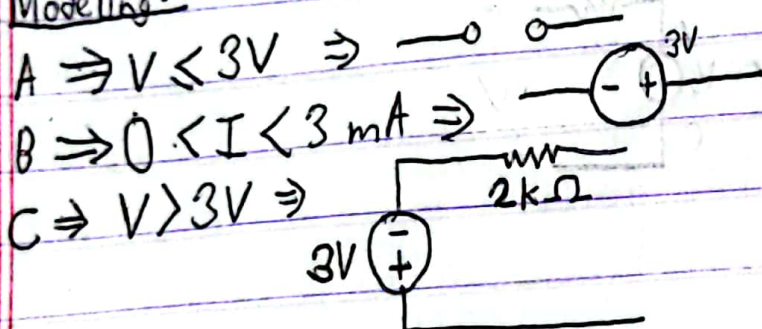

① Assuming device working in B region:

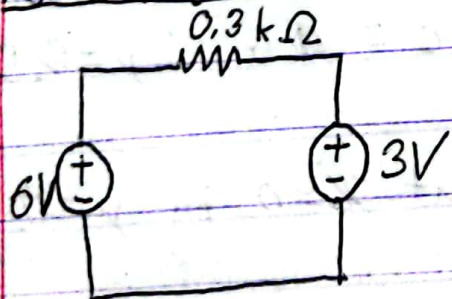


$$I = \frac{6-3}{0.3} = 10 \text{ mA}$$

$$V = 3 \text{ V}$$

• Soln not correct because $0 < I < 3 \text{ mA}$, as it should have been in the B region.
 \therefore Assumption is wrong.

② Assume in C region:

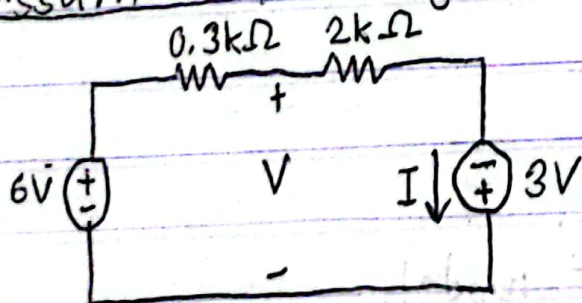

$$I = \frac{6+3}{0.3+2} = 3.6 \text{ mA}$$

$$\text{K.V.L} \Rightarrow V = 2I - 3 = 4.2 \text{ V}$$

Assumption correct as $V > 3 \text{ V}$ in C region.