

CSE 251: Electronic Devices
and Circuits

Summer 24
(Before Mid)

Line Representation

p.3

Loop Representation

p.3

Nodal Analysis in Line Representation

p.6

OP-AMP

p.7

VTC & Wave form of OP- AMP

p.8

Practical vs ideal OP-AMP

p.13

OP-AMP as comparator

p.14

Closed Loop Configuration (OP-AMP)

p.21

Inverting Amplifier

p.25

None -inverting Amplifier

p.28

Inverting Adder

p.30

Differentiator

p.33

Integrator

p.36

Exponentiation

p.37

Logarithm

p.38

Multiplication & Division

p.40

IV-characteristics

p.42

Diode

p.54

Ideal Diode

p.55

Real diode

p.56

Diode's CVD model

p.57

CVD+r model

p.58

Method of Assumption (Diode)

p.61

Logic Gates with Diode

p.68

Ac to DC conversion

p.73

Rectifier

p.73

Using Ideal Diode

p.74

Using CVD Diode



p.76

Full wave Rectifier (CVD Model)


p.79

Half wave vs full wave

p.82



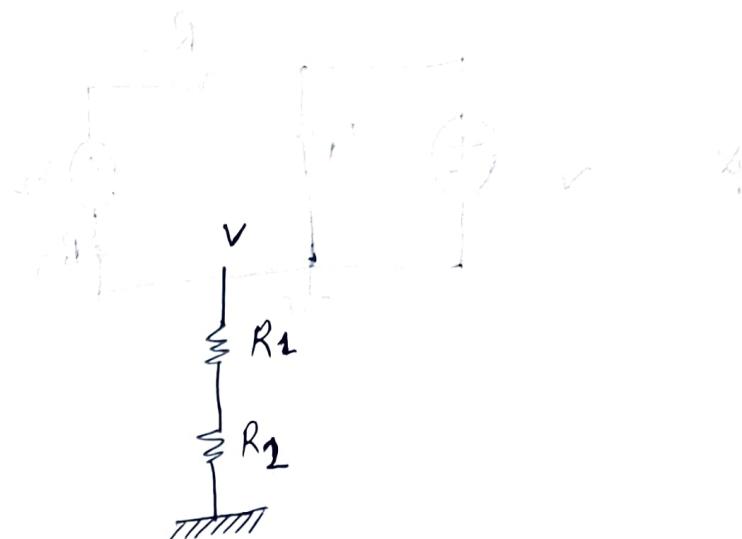
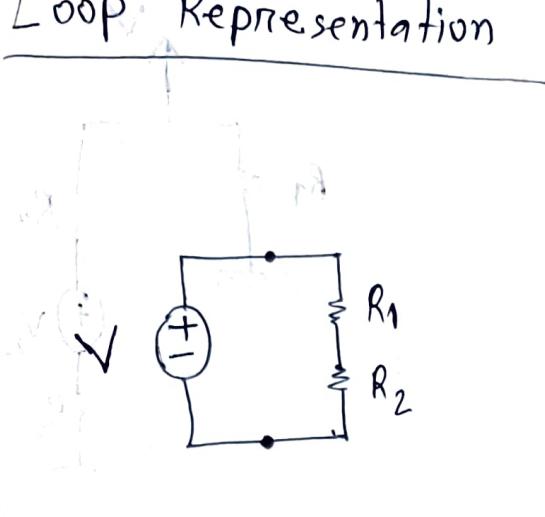
Loop RepresentationRules of Line representation:

① Decide ground

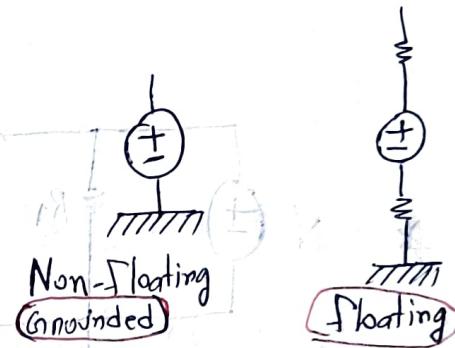





② floating voltage sources should be minimized

③ There is no way to replace a floating voltage source

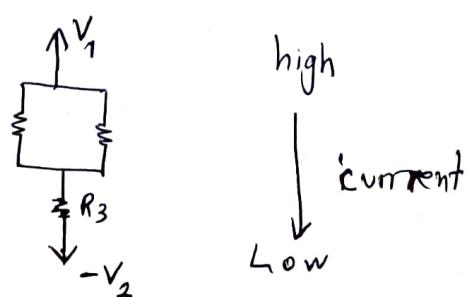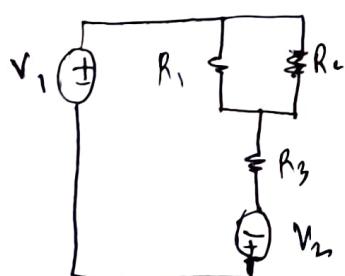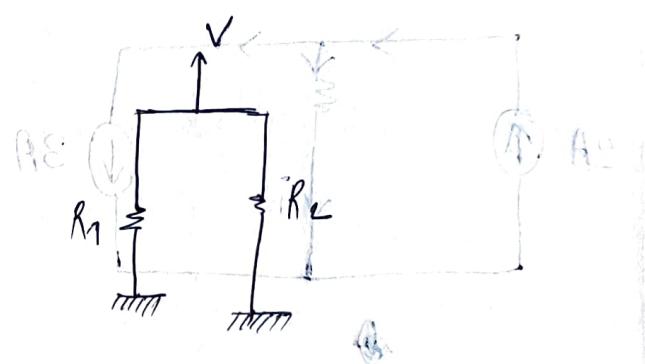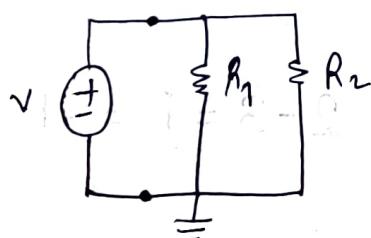
Line Representation

Physik 1

Kapitel 10

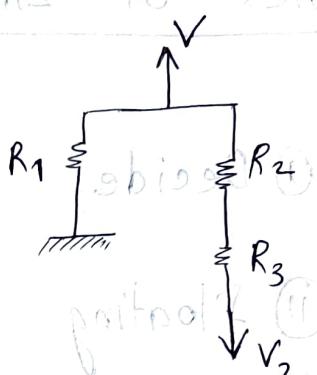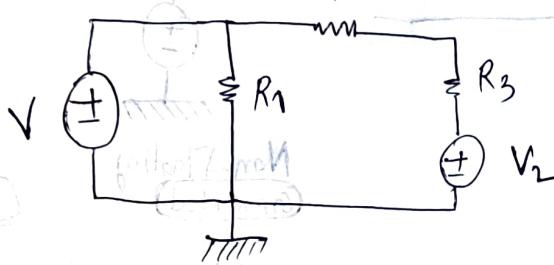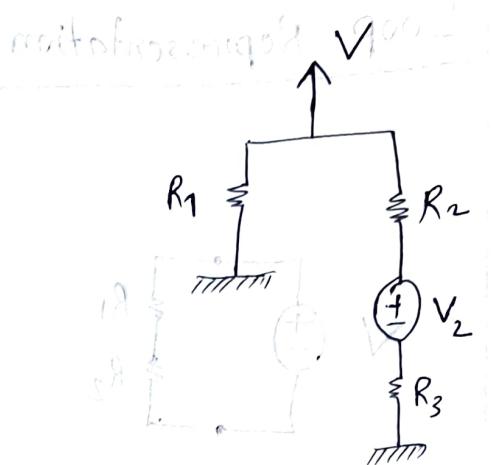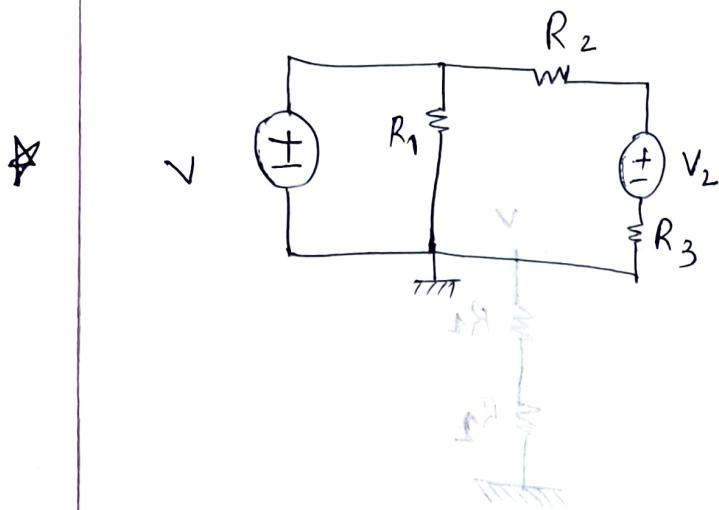


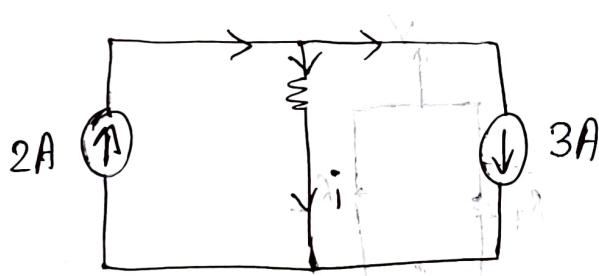Bestimmen Sie die Wirkung von V_1 auf V_2 und i !



$$\Rightarrow 2 - 3 = i = -1$$



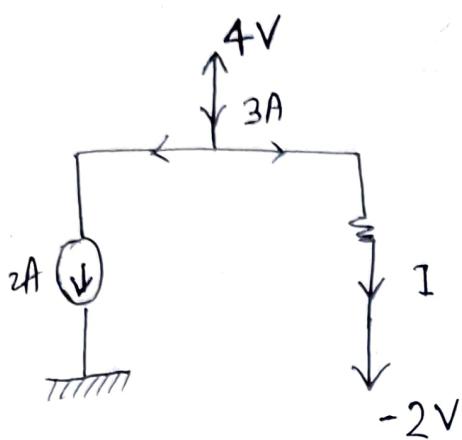


- entering + exiting = 0


$$-3 + 2 + I = 0$$

$$\Rightarrow I = 1$$

KVL

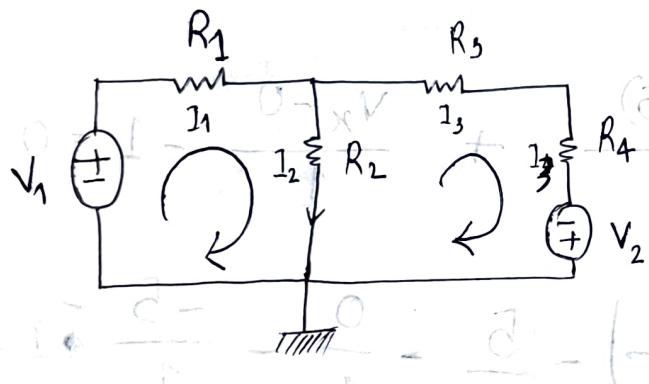
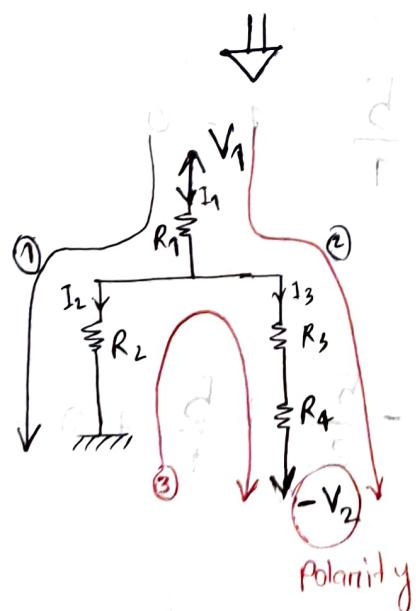
$$\begin{cases} \textcircled{1} \textcircled{1} I_1 R_1 + I_2 R_2 - V = 0 \\ \textcircled{3} \textcircled{1} I_3 R_3 + I_4 R_4 - V - I_2 R_2 = 0 \\ \textcircled{2} \textcircled{1} -V + I_1 R_1 + I_3 R_3 + I_4 R_4 - V_2 = 0 \end{cases}$$



$$\textcircled{1} \textcircled{1} V_1 - 0 = I_1 R_1 + I_2 R_2$$

$$\Rightarrow I_1 R_1 + I_2 R_2 - V_1 = 0$$


$$\textcircled{2} \textcircled{1} V_1 - (-V_2) = I_1 R_1 + I_3 R_3 + I_4 R_4$$

$$\Rightarrow I_1 R_1 + I_3 R_3 + I_4 R_4 - V_1 - V_2 = 0$$

$$\textcircled{1} \textcircled{3} 0 - (-V_2) = -I_2 R_2 + I_3 R_3 + I_4 R_4 = 0$$

$$\Rightarrow I_3 R_3 + I_4 R_4 - I_2 R_2 - V_2 = 0$$

Nodal Analysis


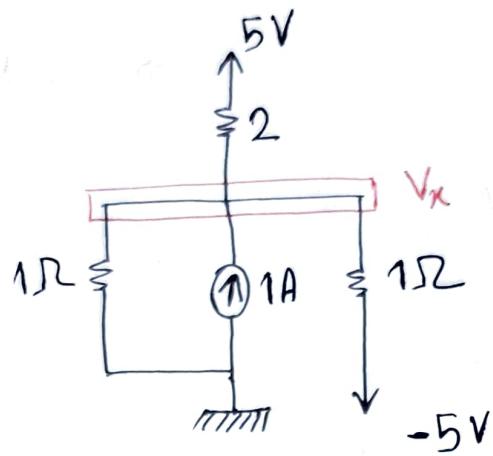


$$\frac{V_x - 5}{2} + \frac{V_x - (-5)}{1} + \frac{V_x - 0}{1} - 1 = 0$$

$$V_x \left(\frac{1}{2} + \frac{1}{1} + \frac{1}{1} \right) - \frac{5}{2} - \frac{0}{1} - \frac{-5}{1} - 1 = 0$$

$$\Rightarrow V_x \left(\frac{1}{2} + 1 + 1 \right) - \frac{5}{2} + \frac{5}{1} - 1 = 0$$
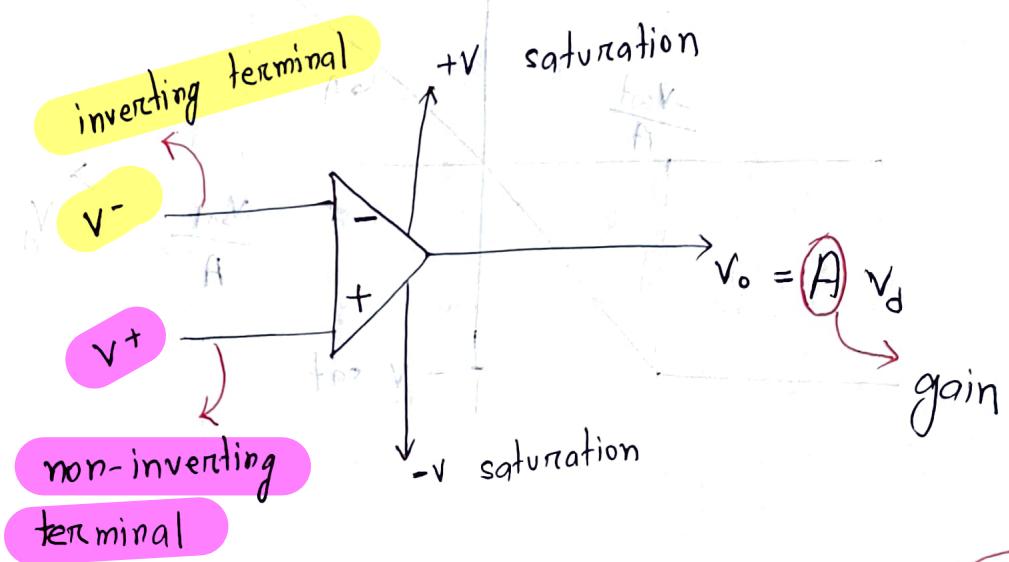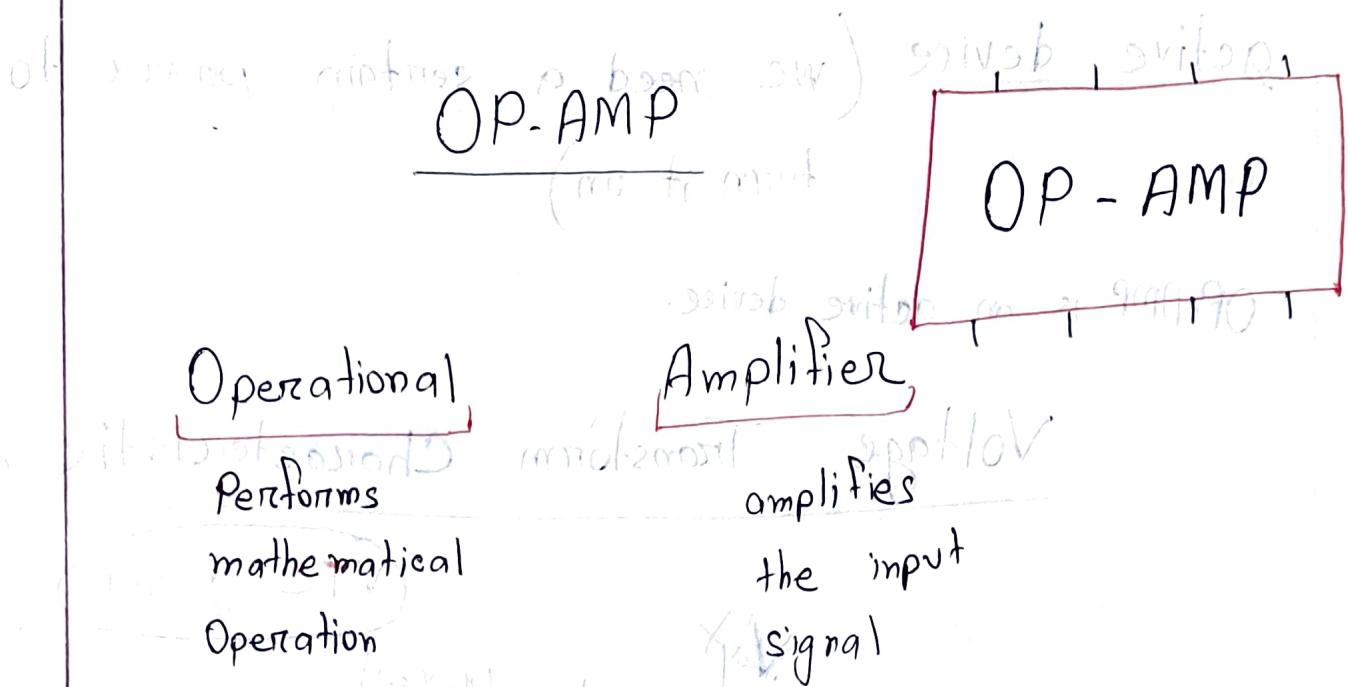
$$\frac{V_x}{2} + \frac{V_x}{1} + \frac{V_x}{1} - \frac{5}{2} + \frac{5}{1} + 0 - 1 = 0$$



$$V_d = (\text{non-inverting} - \text{inverting})$$

$$\Rightarrow V_d = V^+ - V^-$$


difference amplifier

difference के A गरे रखे output देखते

active device (we need a certain power to turn it on)

OP-AMP is an active device.

Voltage Transform Characteristic graph

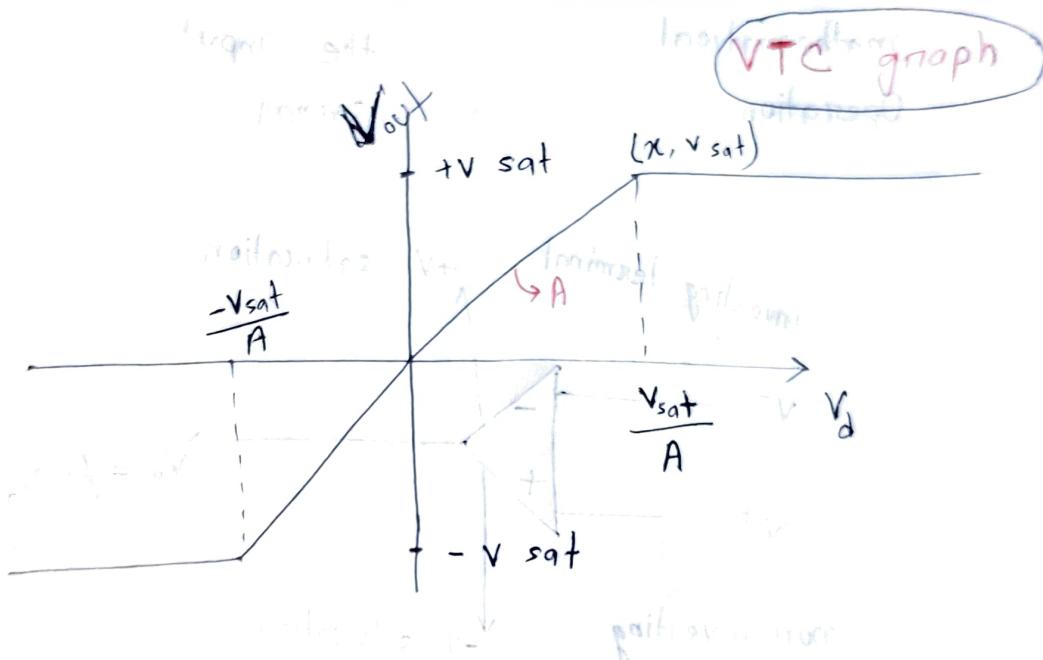



$$V_o = A V_d$$

$$\Rightarrow y = m x$$

$$\Rightarrow x = \frac{y}{m}$$

$$\Rightarrow \frac{V_{sat}}{A}$$

Wave Form (V/I)

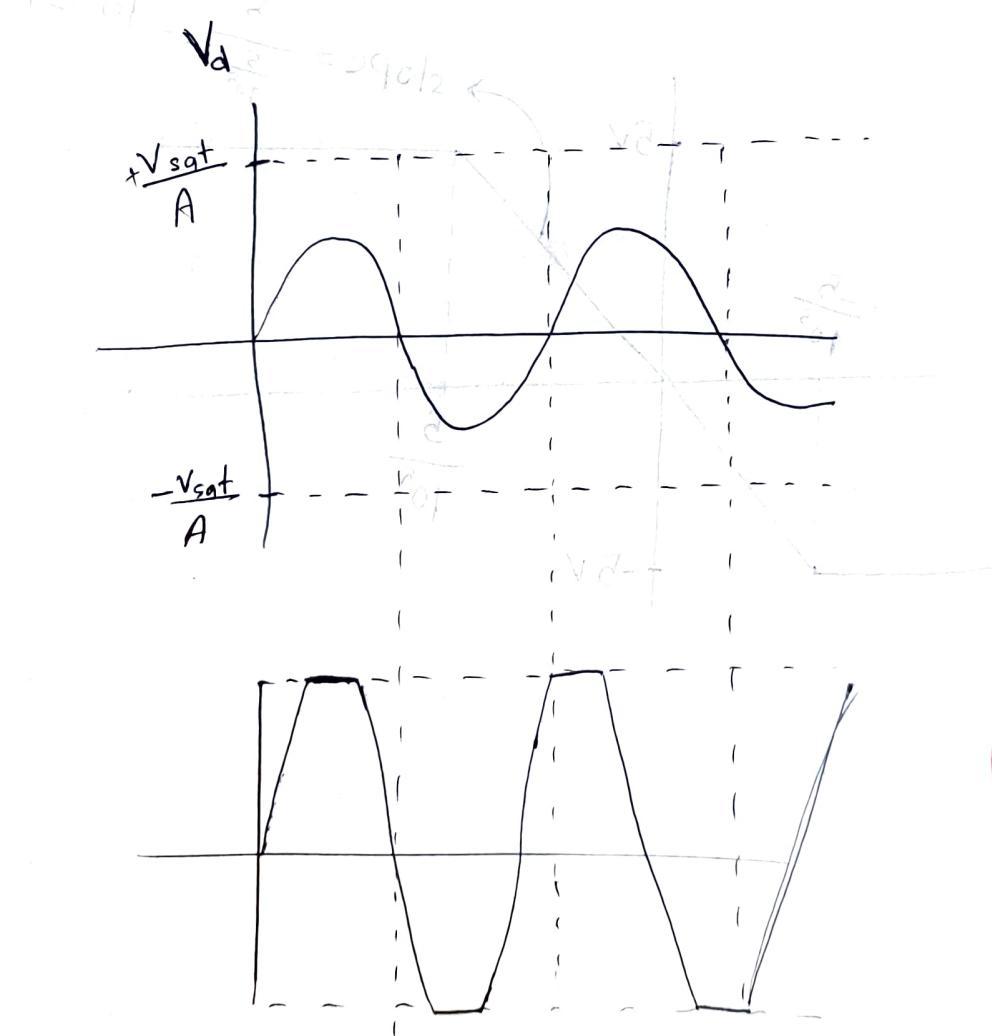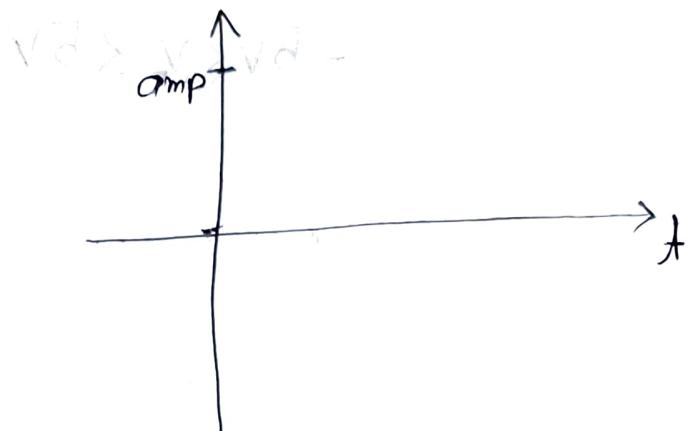

phase is
not correct
It is just a
demo

Ex 1


$$V_o = A V_{in}$$

$$-5V \leq V_o \leq 5V$$

Given,

$$A = 10^5$$

Draw the VTC graph,

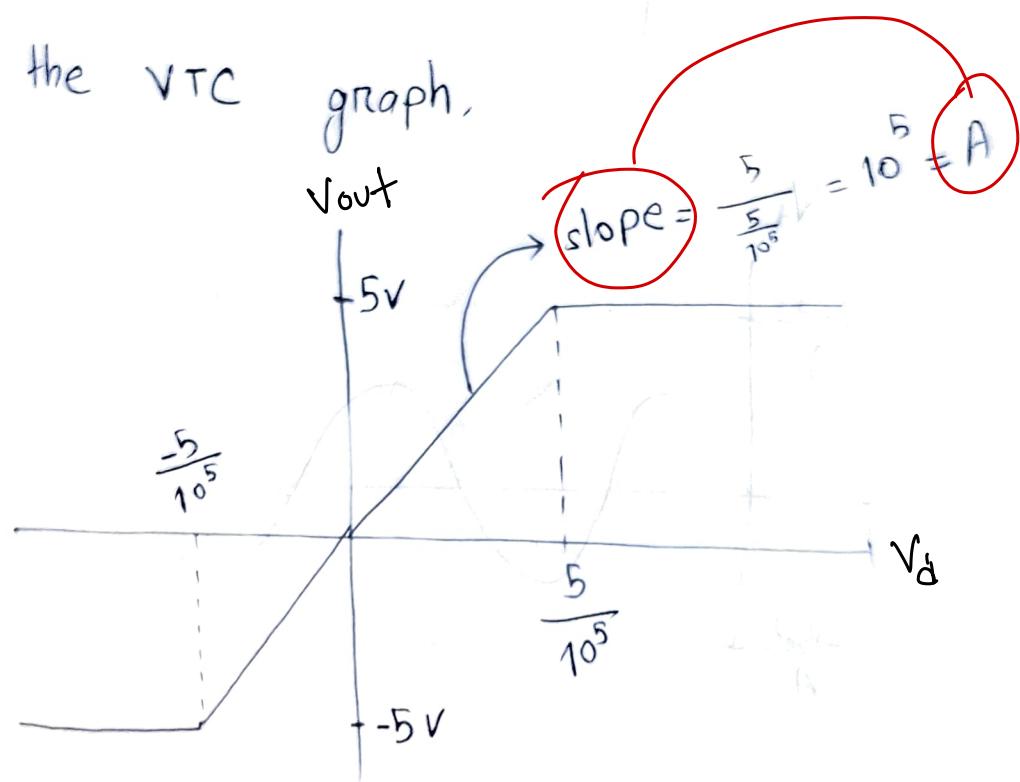


$$\Rightarrow y = mx$$

$$\Rightarrow x = \frac{y}{m} = \frac{5}{10^5}$$

$$\Rightarrow m = \frac{y}{x} = \frac{5}{\frac{5}{10^5}} = 10^5$$

Ex 2

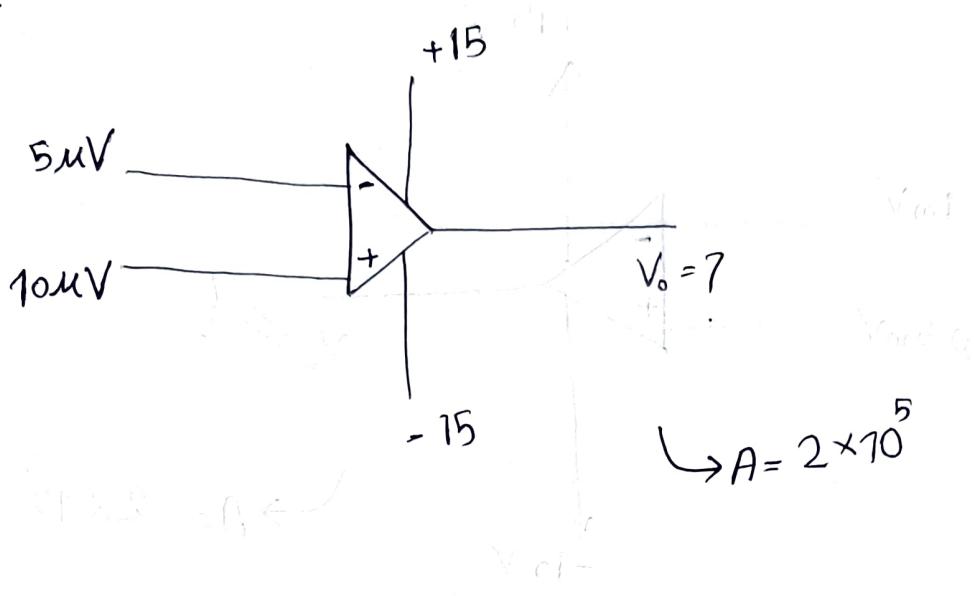

$$V_o = A V_d$$

$$= A (V_+ - V_-)$$

$$= 2 \times 10^5 (10\mu - 5\mu)$$

$$= 2 \times 10^5 \times 5 \times 10^{-6}$$


$$= \frac{10}{10}$$

$$= 1V$$

(Ans)

Feedback $\rightarrow 15V$
Output $\rightarrow 7V$

Ex 3:

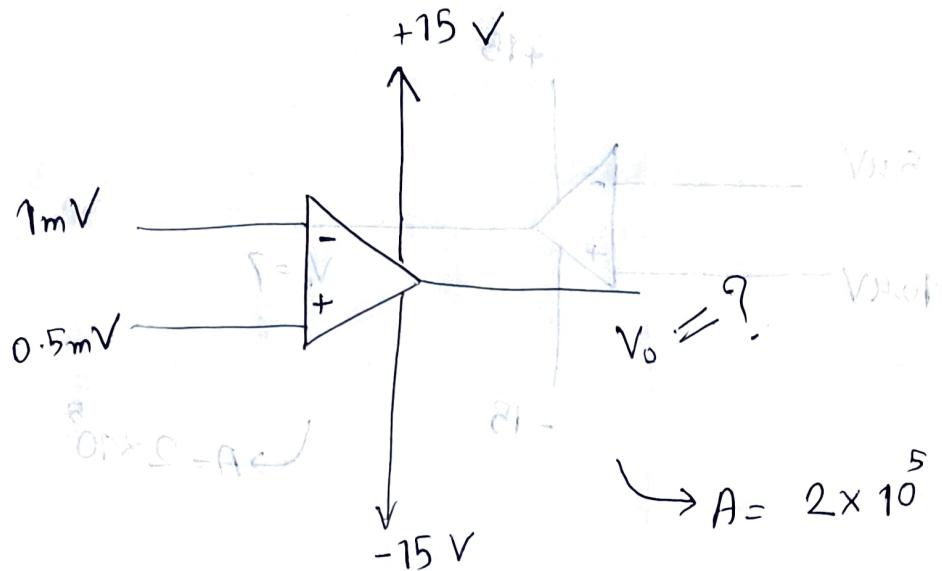

$$V_d = V^+ - V^-$$

$$= (0.5 - 1) \text{ mV}$$

$$= -0.5 \text{ mV}$$

$$= -0.5 \times 10^{-3} \text{ V}$$

$$\therefore V_o = A V_d$$

$$= 2 \times 10^5 \times (-0.5 \times 10^{-3})$$

$$= 2 \times (0.5) \times 10^2$$

$$= -1 \times 10^0$$

$$= -100$$

for $-V$ saturation,
 $V_o = -15$

parameters

gain value = A

Typical range


$10^5 \sim 10^8$

Ideal


$A = \infty$

$R = \infty$

Practical OP-AMP

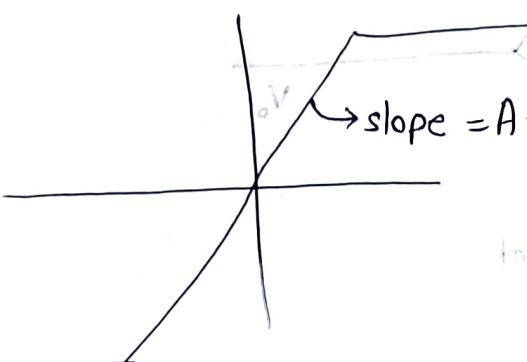

Ideal OP-AMP

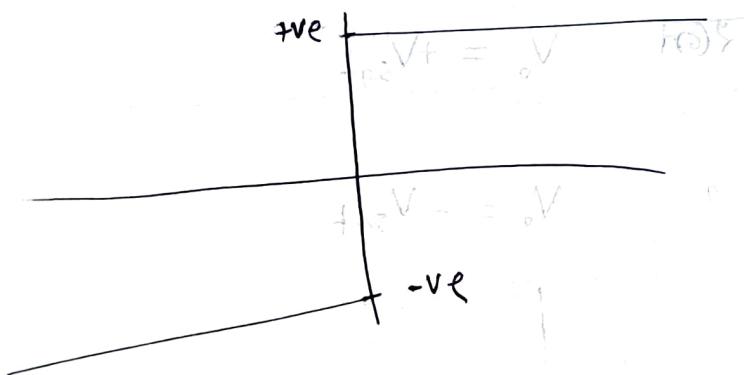


$V_d = +ve$ ৰে \Rightarrow result \Rightarrow ~~+ve~~ $+V_{sat}$

$V_d = -ve$ " " " " " " " " $-V_{sat}$

Comparator

It compares two voltage.

Non-inverting comparator

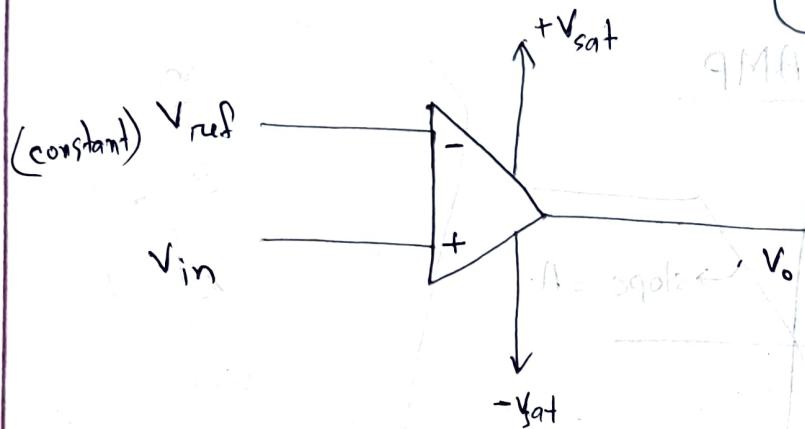

V_{in} या आपापाप
तर अनुगामी नाही ।

$$V_d = V_{in} - V_{ref}$$

$$V_d > 0 \text{ तर } V_o = +V_{sat}$$

$$V_d < 0 \text{ " } V_o = -V_{sat}$$

$$V_d > 0$$

$$V_{in} - V_{ref} > 0$$

$$\therefore V_{in} > V_{ref}$$


$$V_o = +V_{sat}$$

$$V_d < 0$$

$$\Rightarrow V_{in} - V_{ref} < 0$$


$$\Rightarrow V_{in} < V_{ref}$$

$$V_o = -V_{sat}$$

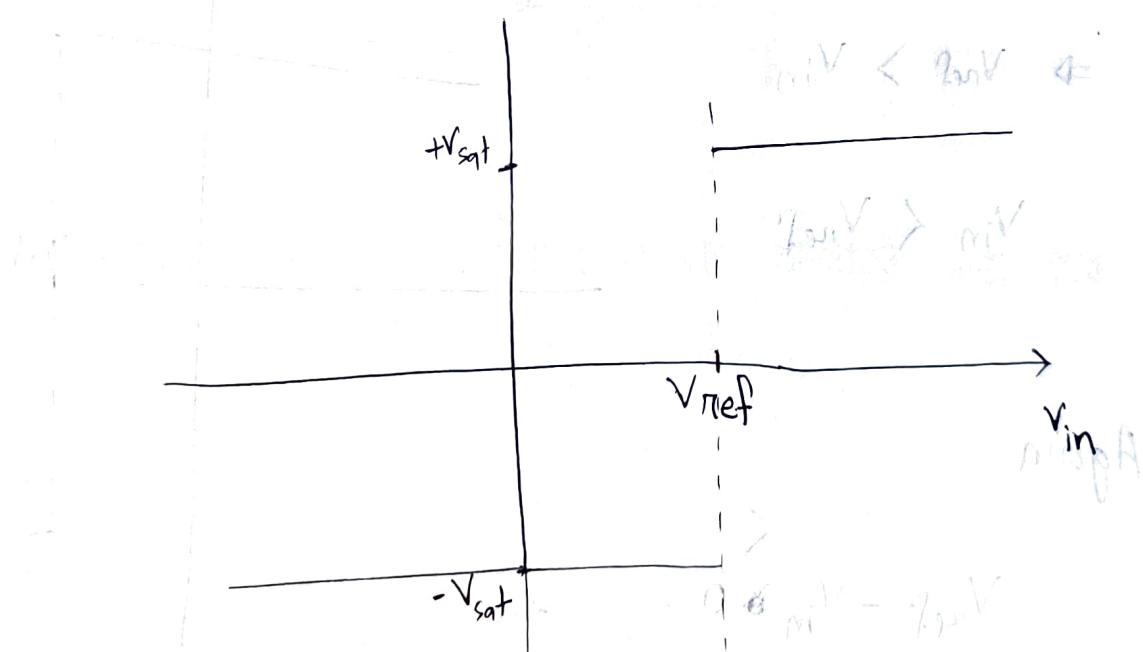

GT5011 swap

Inverting Comparator

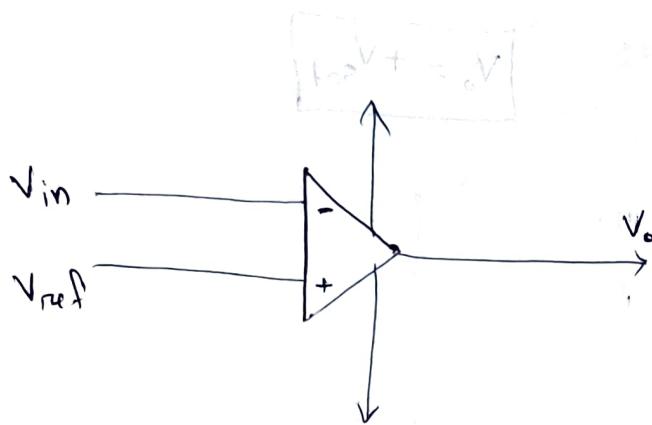

$$V_{ref} - V_{in} > 0, +V_{sat}$$

$$\Rightarrow V_{ref} > V_{in}$$


$$V_{in} < V_{ref}$$

Again,



$$V_{ref} - V_{in} < 0, -V_{sat}$$

$$\Rightarrow V_{ref} < V_{in}$$



$$\Rightarrow V_{in} > V_{ref}$$

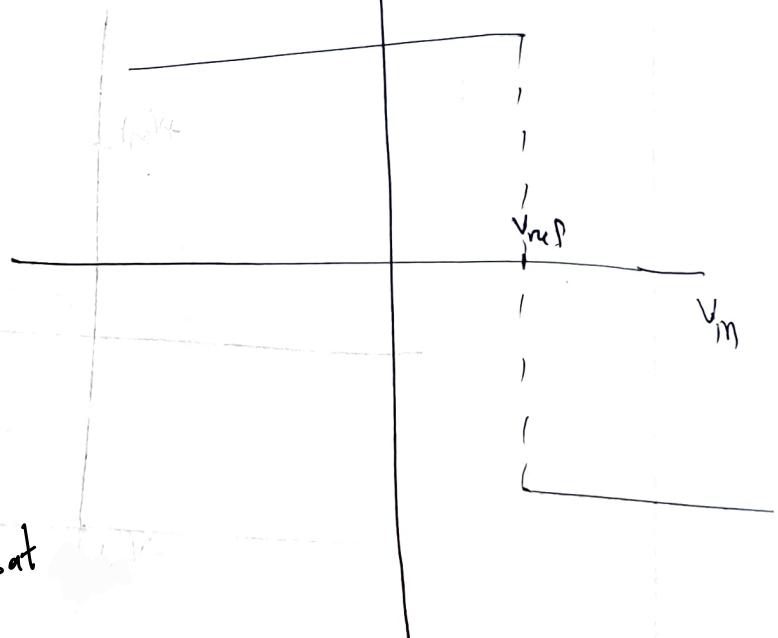


Non-inverting or Comparator

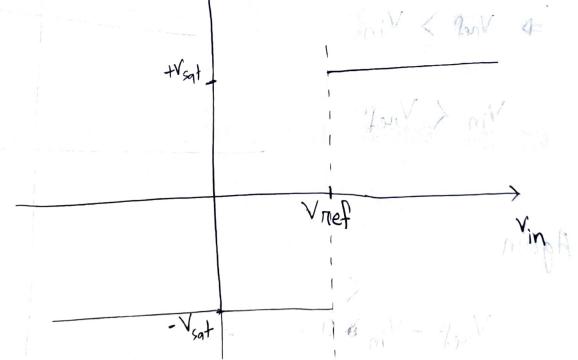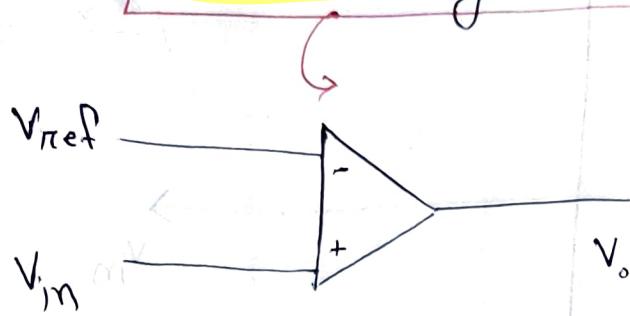


Inverting Comparator

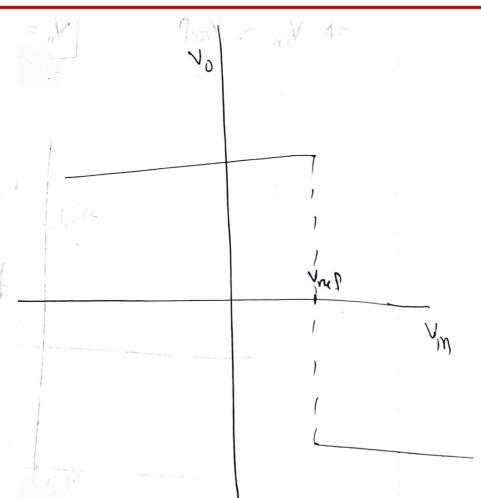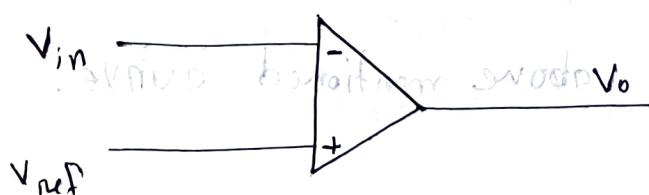


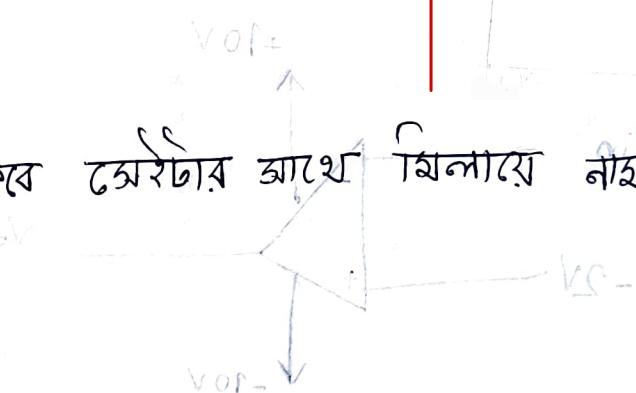V_{in} এটাতে হাবে মেরিটার আথে ঘিলায়ে নাই হবে।



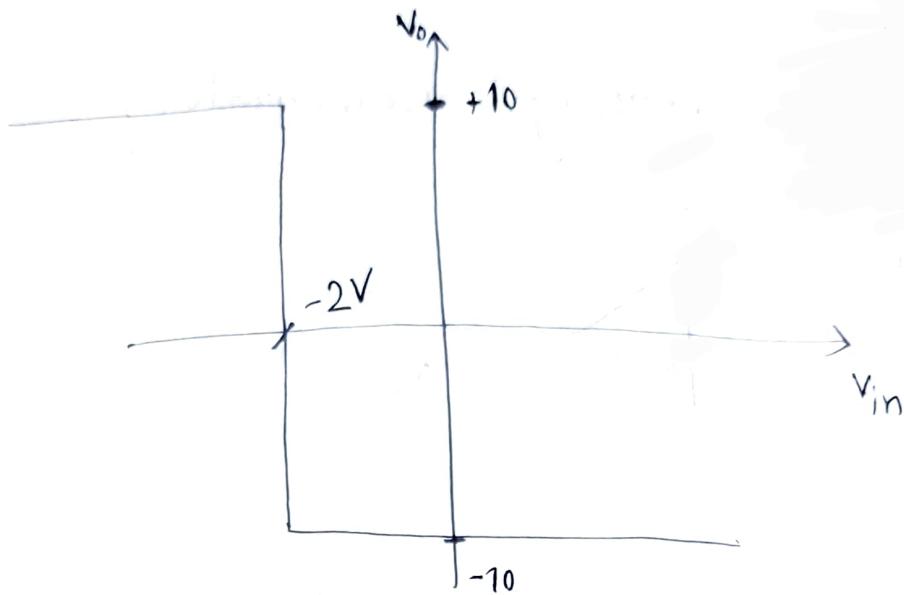

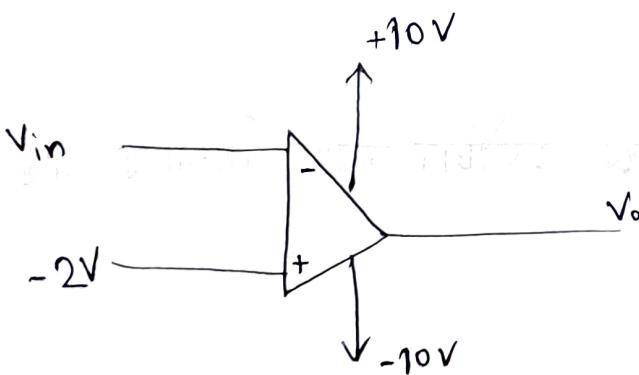① Design an op-amp circuit so that the VTC curve is the above mentioned curve.




Inverting লাভক নন-ইনভিটিং অফিচ্চা বুন্দেল রেখা গ্রাফ দেখো,

Inverting \Rightarrow অফিচ্চা পয়েন্ট এর পর কানেক্ষেনে



নন-ইনভিটিং \Rightarrow " " " " এক্ষেন্ট " "



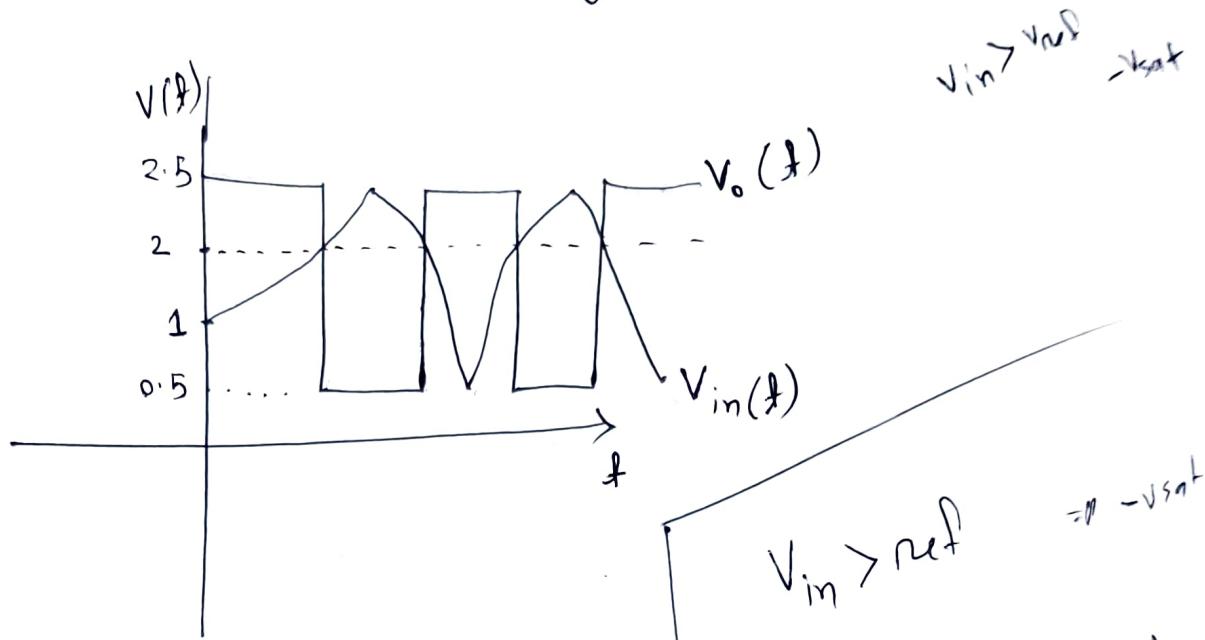$+V_{sat}$ and $-V_{sat}$ ताकि वास्तविक symmetric ताकि रेता मिले।



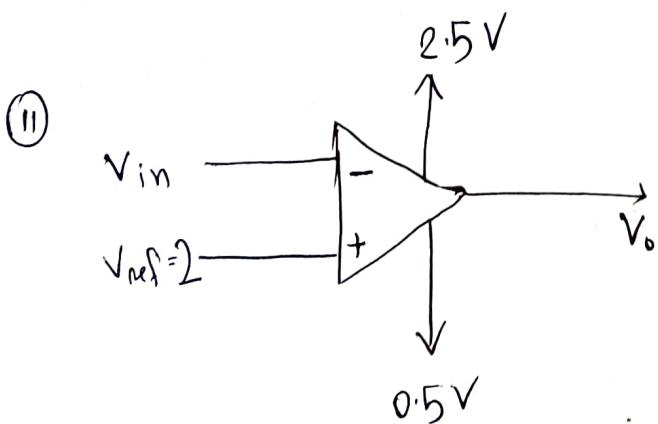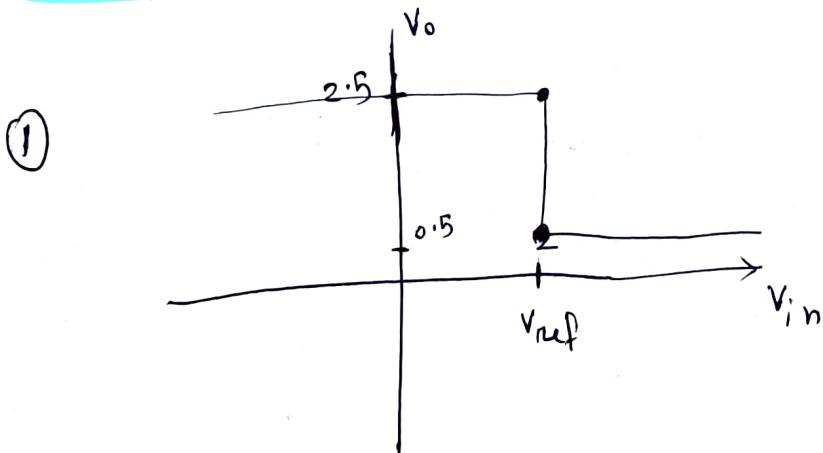
- ① Draw the VTC curve
- ② Design the OP-AMP circuit.



$V_{in} > V_{ref}$ $\Rightarrow V_o > 0$ $+sat$

$V_{in} < V_{ref}$ $\Rightarrow V_o < 0$ $-sat$

inverting compensation

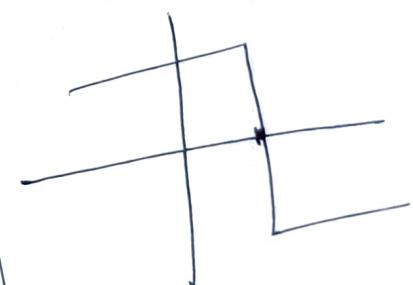


Non inverting

$V_o > 0$ $+sat$



$V_{in} > V_{ref}$

Lecture 3

noninverting input good for ID

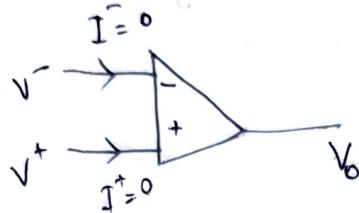

$$V_d = V^+ - V^-$$

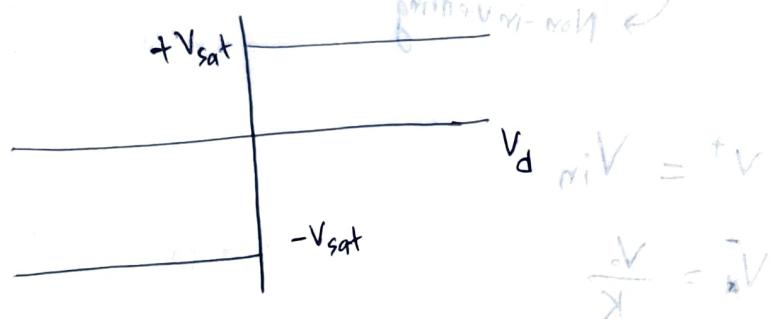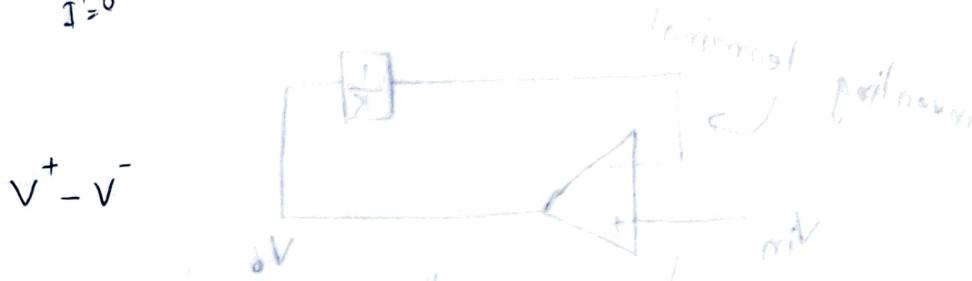

$$V_d = +V$$

$$\frac{V}{V} = \frac{V}{V}$$

Ideal OP-AMP

$$\boxed{A = \infty} \\ \boxed{R_{in} = \infty}$$

characteristics of an ideal OP-AMP

$$(V^+ - V^-) A = V_d$$

$$\therefore I = \frac{V}{R}$$

$$= \frac{V}{\infty}$$


$$(V^+ - V^-) A = V_d$$

$$I = 0$$

\rightarrow output resistance

$\therefore R_o = 0$ \rightarrow Output voltage drop will be 0.

Closed Loop Configuration

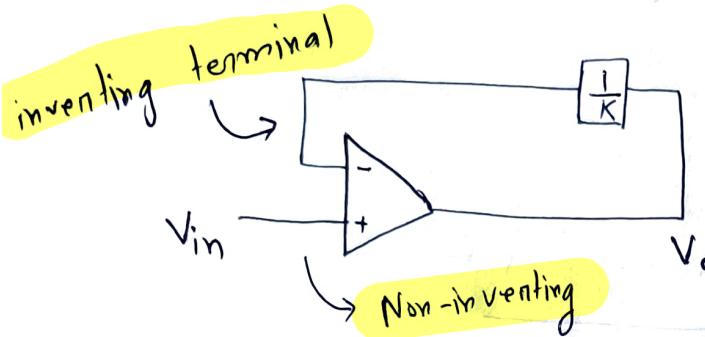

$$V^+ = V_{in}$$

$$V^- = \frac{V_o}{K}$$

$$V_d = V_{in} - \frac{V_o}{K}$$

Non-inverting input $V^+ = V_{in} - V_o$ (inverted)

90A-90
Ans

$$\begin{cases} \alpha_1 = A \\ \alpha_2 = \alpha_1 A \end{cases}$$

$$\therefore V_o = A (V^+ - V^-)$$

$$\Rightarrow V_o = A \left(V_{in} - \frac{V_o}{K} \right)$$

$$\Rightarrow V_o + \frac{AV_o}{K} = A V_{in}$$


$$\therefore V_o \left(1 + \frac{A}{K} \right) = A V_{in} \quad \text{or} \quad V_o = \frac{A V_{in}}{1 + \frac{A}{K}}$$

To graphically determine the value of A

$$\Rightarrow V_o = \frac{A}{(1 + \frac{A}{K})} V_{in}$$

$$\text{if } \frac{A}{K} \gg 1 \Rightarrow \left(1 + \frac{A}{K}\right) \approx \frac{A}{K}$$

for an ideal OP-AMP:

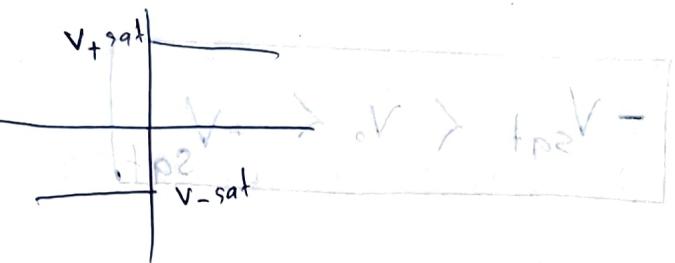

Unstable system

* After closing with a negative feedback, we will get a stable output.

$$V_o = \frac{A}{(1 + \frac{A}{K})} V_{in}$$

$$\Rightarrow V_o = \frac{1}{\left(\frac{1}{A} + \frac{1}{K \cdot P}\right)} V_{in}$$

$$\text{if } K \cdot P \gg 1 \Rightarrow \left(\frac{1}{A} + \frac{1}{K \cdot P}\right) \approx \frac{1}{K \cdot P}$$

$$= \frac{1}{\left(\frac{1}{\infty} + \frac{1}{K}\right)} V_{in}$$

$$\Rightarrow V_o = K V_{in}$$

$$AV = \frac{A}{(A+1)} = AV$$

$$\boxed{A = \infty}$$

in ideal OP-AMP

QMA-90 hasilnya nol

$$\boxed{-V_{sat} < V_o < +V_{sat}}$$

$$V_o = A V_d$$

malesa sifatnya

$$\Rightarrow V_d = \frac{V_o}{A}$$

$$\Rightarrow V_d = \frac{V_o}{\infty} = 0$$

$$\Rightarrow V^+ - V^- = 0$$


$$\Rightarrow V^+ = V^-$$

$$\textcircled{1} \quad I^+ = I^- = 0$$

अब अंदर

\textcircled{2} Closed Loop

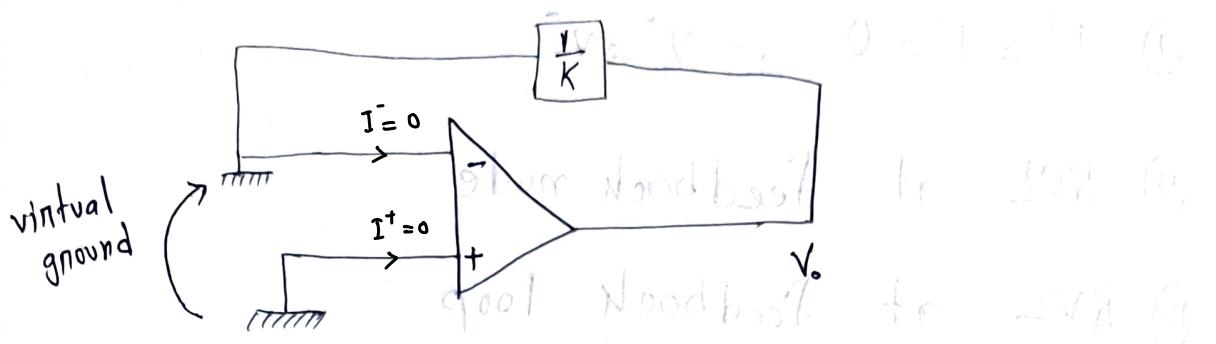
$$V^+ = V^- \quad \left[\begin{array}{l} \text{प्राची जाति थारा अनादि गार} \\ \text{अमान इत्ये} \end{array} \right]$$



$$V^+ = V^- = 0$$

↳ এই অন্তর্ভুক্ত পরিসরে
auto V^- এর মান 0V হবে।

Math operation using OP-AMP

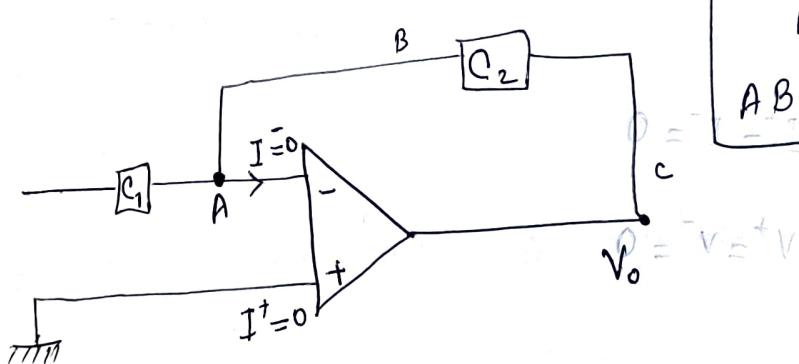


$A = \text{Feedback node}$

$ABC = \text{Feedback loop}$

↳ above Non-invert to 10% (1)

C_1 and C_2 can be

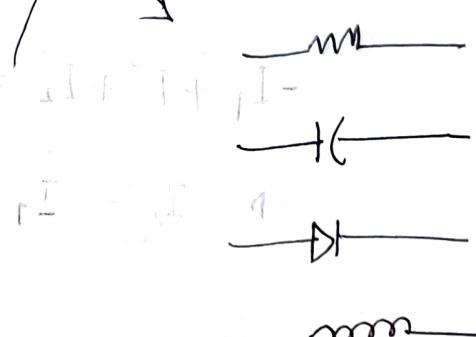


① $I^+ = I^- = 0$, $V^+ = V^-$

② KCL at Feedback node

③ KVL at Feedback loop

Inverting Amplifier

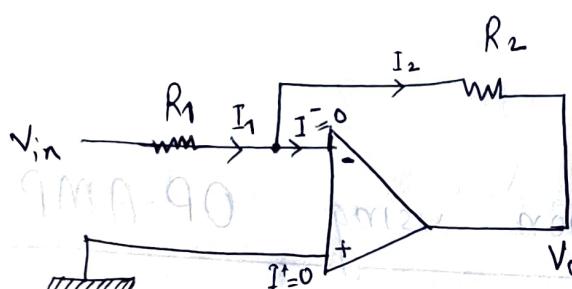

① $I^+ = I^- = 0$

$V^+ = V^- = 0$

② KCL at Feedback node

$$-I_1 + I^- + I_2 = 0$$

$$\Rightarrow I_2 = I_1$$

$$I_1 = \frac{V_{in} - 0}{R_1}$$

$$\Rightarrow I_1 = \frac{V_{in}}{R_1}$$

$$I_2 = \frac{0 - V_o}{R_2}$$

$$\Rightarrow I_2 = \frac{-V_o}{R_2}$$

$$\therefore I_1 = I_2$$

$$\Rightarrow \frac{V_{in}}{R_1} = - \frac{V_o}{R_2}$$

$$\Rightarrow - \frac{V_{in}}{R_1} = + \frac{V_o}{R_2}$$

~~so~~ ~~input~~

$$\Rightarrow V_o = - \left(\frac{R_2}{R_1} \right) V_{in}$$

gain Θ

This amplifier amplifies V_{in} voltage to $\left(-\frac{R_2}{R_1} \right)$


times.

Note that:

amplifies ~~to~~ with a minus sign.

* Design a OP-AMP where


$$V_o = -2.5 V_{in}$$

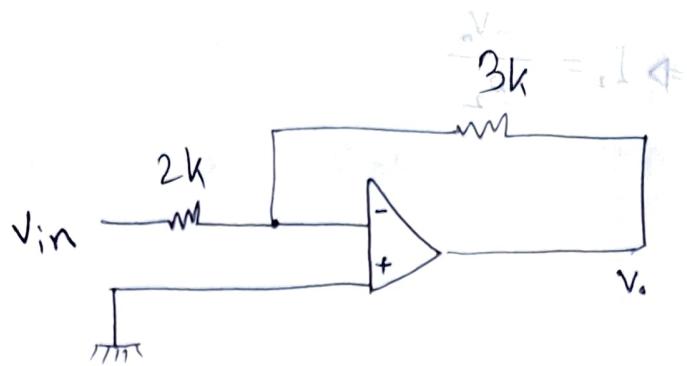

$$\therefore V_o = \frac{3}{2} V_{in}$$

$$= 1.5 V_{in}$$

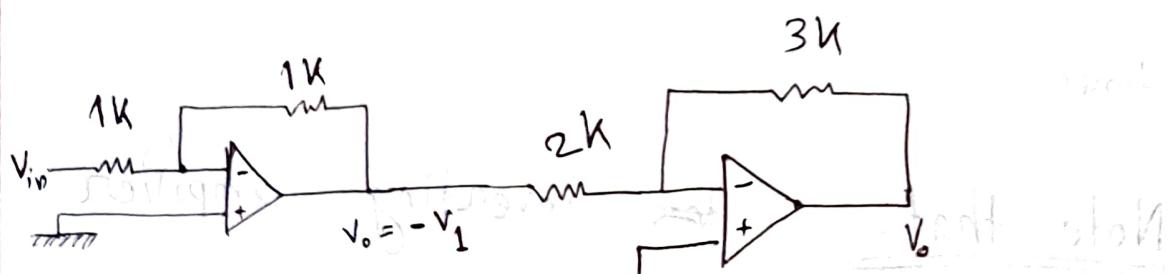
* Design a OP-AMP where $V_o = 2.5 V_{in}$



$$\therefore V_o = \left(\frac{3}{2}\right) (-V_{in})$$

$$V_o = -2.5 V_{in} \text{ (Ans)}$$

Non-inverting amplifier

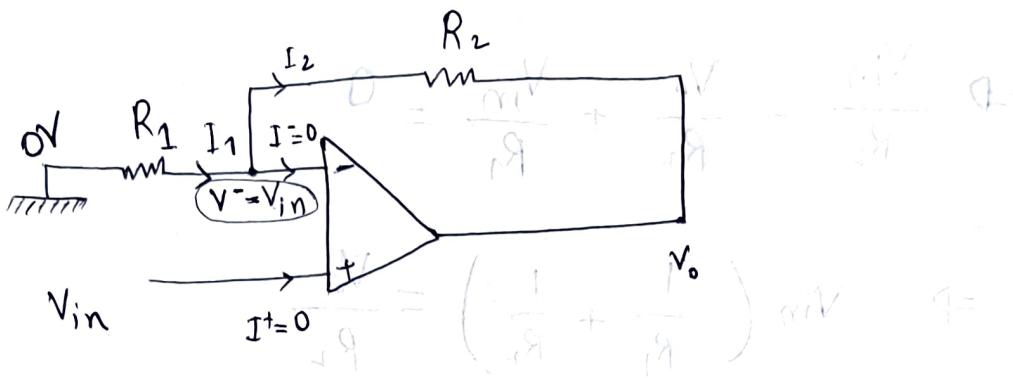

$$V^+ = V^- = V_{in} \quad \frac{V}{V_{in}} = \left(\frac{R_2 + R_1}{R_1} \right) \text{ aV}$$

$$I^+ = I^- = 0$$

$$V = \left(\frac{R_2 + R_1}{R_1} \right) \text{ aV}$$

$$\textcircled{11} \quad I_1 = \frac{0 - V_{in}}{R_1} \left(\frac{R_2 + R_1}{R_1} \frac{V_{in}}{R_1} \right) = \text{aV}$$

$$I_2 = \frac{V_{in} - V_o}{R_2}$$

~~use~~ KCL at the feedback point,

$$-I_1 + I^- + I_2 = 0$$

$$\Rightarrow -I_1 + 0 + I_2 = 0$$

$$\Rightarrow I_2 \neq I_1$$

$$\Rightarrow \frac{V_{in} - V_o}{R_2} = -\frac{V_{in}}{R_1}$$

$$\Rightarrow \frac{V_{in}}{R_2} - \frac{V_o}{R_2} + \frac{V_{in}}{R_1} = 0$$

$$\Rightarrow V_{in} \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V_o}{R_2}$$

$$\Rightarrow V_{in} \left(\frac{R_1 + R_2}{R_1 R_2} \right) = \frac{V_o}{R_2}$$

$$\Rightarrow V_{in} \left(\frac{R_1 + R_2}{R_1} \right) = V_o$$

$$\Rightarrow V_o = \left(1 + \frac{R_2}{R_1} \right) V_{in}$$

gain > 1

$$y = 2.5x$$

$$\Rightarrow \left(1 + \frac{R_2}{R_1} \right) = 2.5$$

$$\Rightarrow \frac{R_2}{R_1} = 1.5$$


∴ It can be

$$\begin{aligned} R_2 &= 15, 30 \\ R_1 &= 10, 20 \end{aligned}$$

$y = -2x \rightarrow$ inverting amplifier

$y = 4x \rightarrow$ non-inverting amplifier
non-inverting signal

Inverting Adder

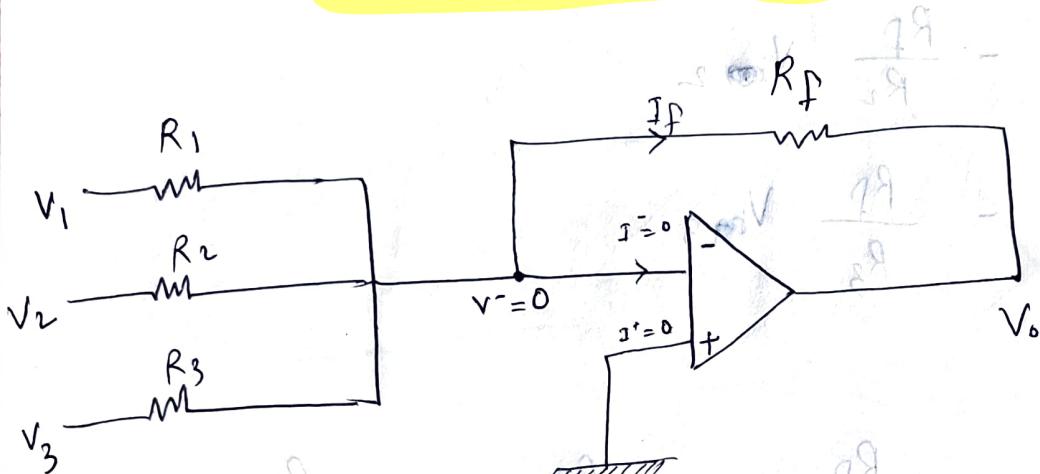

$$I_1 = \frac{V_1 - V^-}{R_1} = \frac{V_1 - 0}{R_1} = \frac{V_1}{R_1}$$

$$I_2 = \frac{V_2 - 0}{R_2} = \frac{V_2}{R_2}$$

$$I_3 = \frac{V_3 - 0}{R_3} = \frac{V_3}{R_3}$$

KCL at feedback point, $I_f = I_1 + I_2 + I_3$

$$-(I_1 + I_2 + I_3) + I_f + I^- = 0$$

$$\Rightarrow I_f = (I_1 + I_2 + I_3)$$

$$I_f = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$

Bulb 1 + Bulb 2 + Bulb 3 = V_f

Super-position

$$V_o = - \frac{R_f}{R_1} V_1$$

parallel

$$V_o = - \frac{R_f}{R_2} V_2$$

parallel

$$V_o = - \frac{R_f}{R_3} V_3$$

parallel



$$\therefore V_o = - \frac{R_f}{R_1} V_1 - \frac{R_f}{R_2} V_2 - \frac{R_f}{R_3} V_3$$

$$\Rightarrow V_o = - \left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right)$$

$$\Rightarrow V_o = -(V_1 + V_2 + V_3)$$

$$\begin{cases} R_f = 1 \\ R_1 = 1 \\ R_2 = 1 \\ R_3 = 1 \end{cases}$$


তাহুলো যাগ আচৰে just (-) কৰে $\overline{f_1(f_2)}$,
আই এন্ডে, তাৰে, inverting adder

$$(01101010)_{2} = 146_{10}$$

Draw a circuit where $f = -2x + 3y - 4z$

$$= -(2x - 3y + 4z)$$
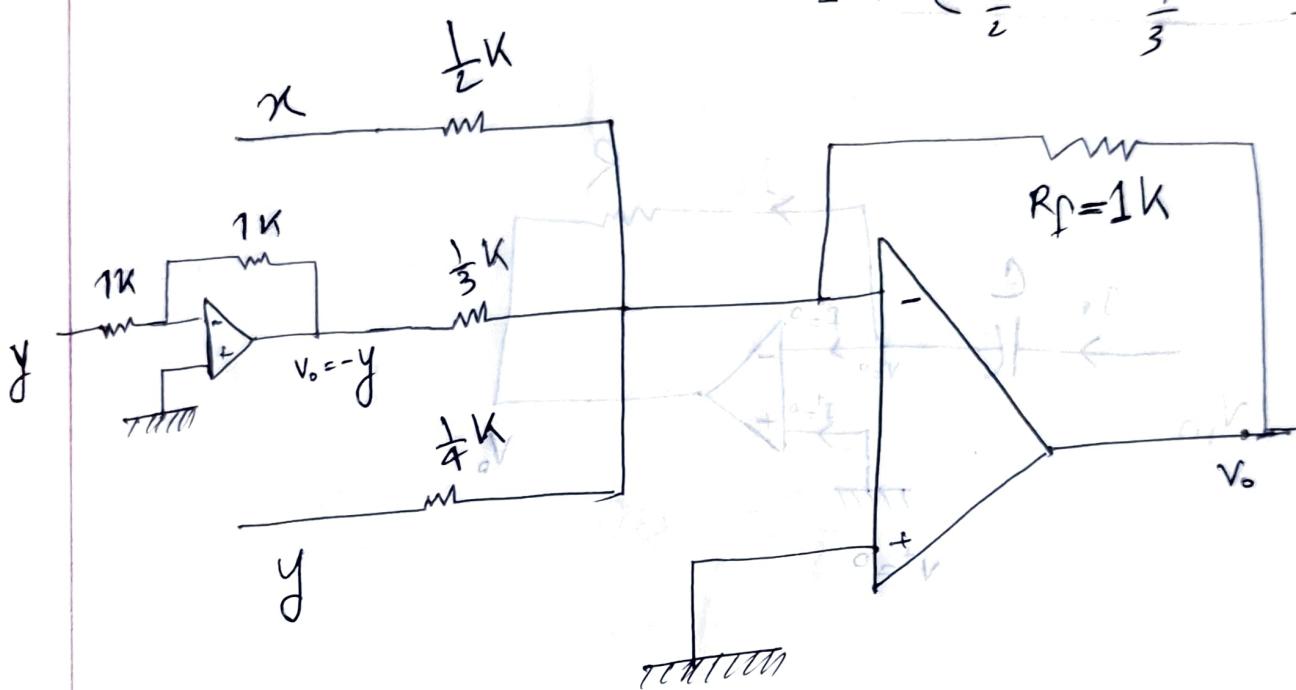
$$= -\left(\frac{1}{2}x + \frac{y}{3} + \frac{z}{4}\right)$$



$$0 = V_o + V$$

$$0 = 1 = [$$

$$V_o = -1$$


$$0 = \frac{1}{2}x + \frac{y}{3} + \frac{z}{4}$$

$$0 = \frac{1}{2}x + \frac{y}{3} + \frac{z}{4}$$

11.06.24

Math operations with OP-AMP

Differentiation:

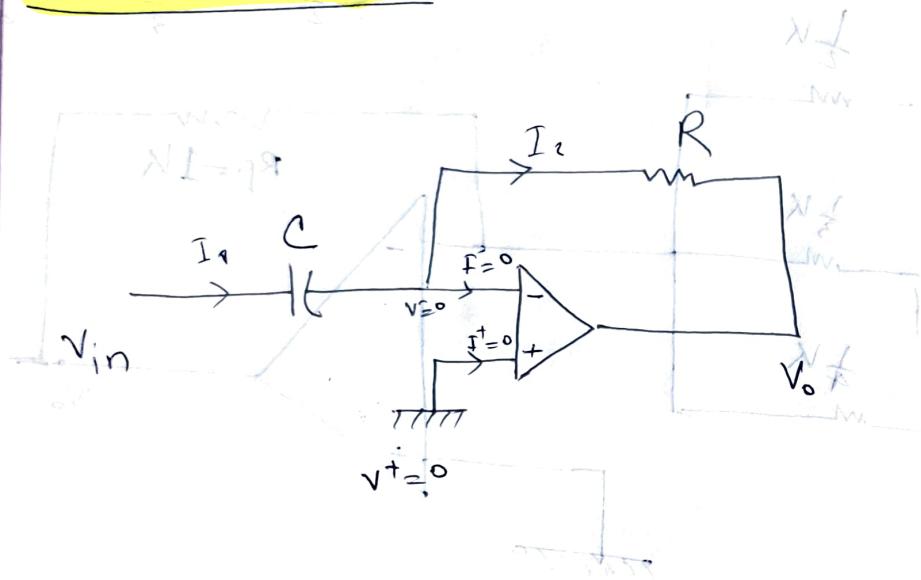

$$\textcircled{1} \quad v^+ = v^- = 0$$

$$I^+ = I^- = 0$$

$$i \rightarrow C$$

$$i = C \frac{dv}{dt}$$

$$\textcircled{11} \quad I_1 = C \frac{dv}{dt}$$

$$= C \frac{V_{in} - 0}{dt}$$

$$= C \frac{V_{in}}{dt}$$

$I_1 = I_2$ + because V_{in} is applied to

$$\Rightarrow I_2 = \frac{0 - V_o}{R} \quad \text{but } E = RL = ?$$

$$\Rightarrow I_2 = -\frac{V_o}{R} \quad \left(\frac{Rb}{fb} E + RL \right) =$$


$\therefore I_1 = I_2$

$$\Rightarrow C \frac{dV_{in}}{dt} = -R \cdot -\frac{V_o}{R}$$

\Rightarrow

$V_o = b \cdot \frac{dV_{in}}{dt}$

Problem

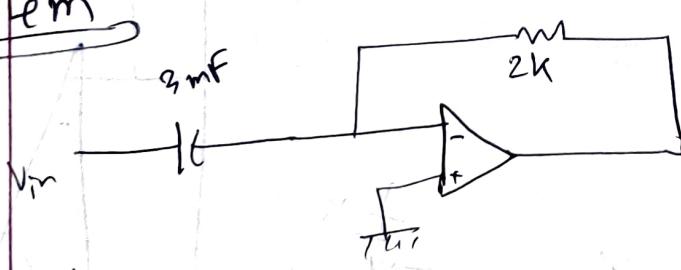

$$V_{in} = 10 \cos 2t$$

$$V_o = -2 \times 10^3 \times 3 \times 10^{-3} \cdot -10 \sin 2t$$

$$= 2 \times 3 \times 2 \times 10$$

$$= 120 \sin 2t$$

Ans


★ Design the OP-AMP circuit :

$$f = -2x - 3 \frac{dy}{dt}$$

$$= -\left(2x + 3 \frac{dy}{dt}\right)$$


$$\frac{V}{R} = 1.5$$

$$\frac{V}{R} = 1.5$$

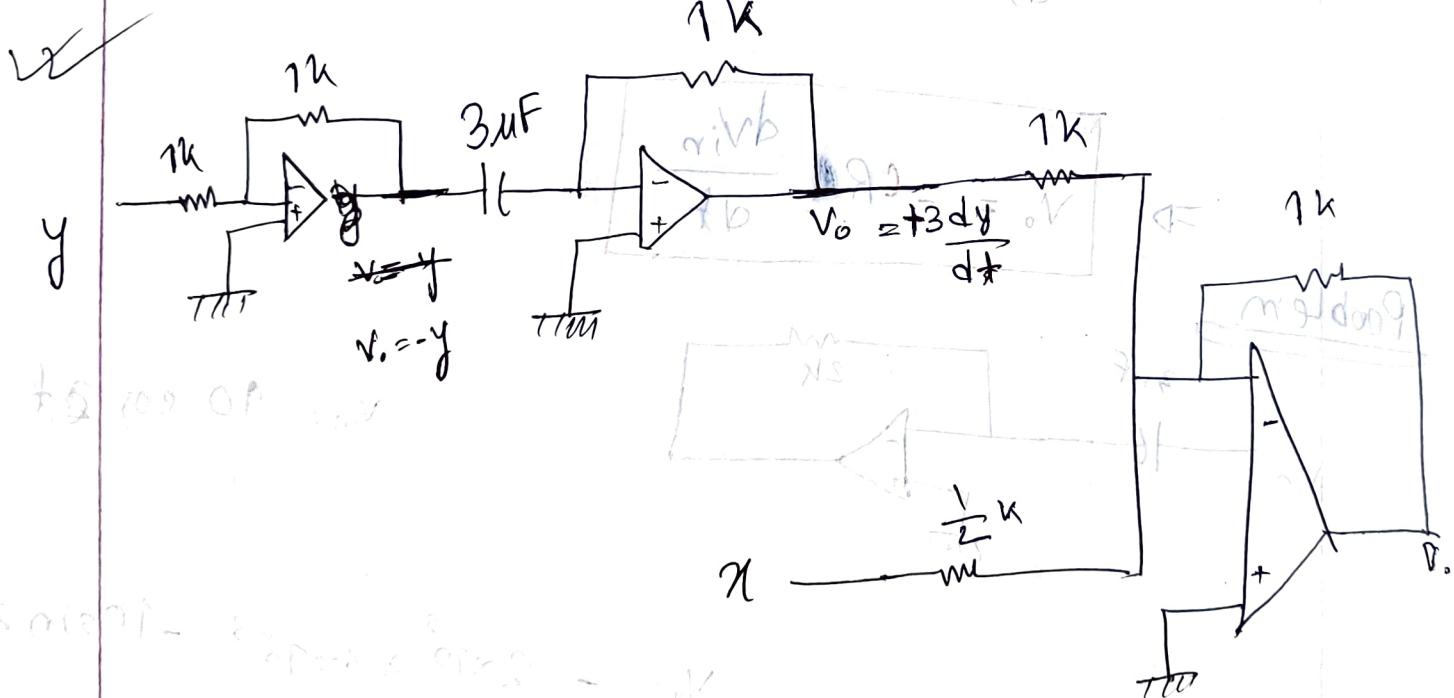


Another

2k

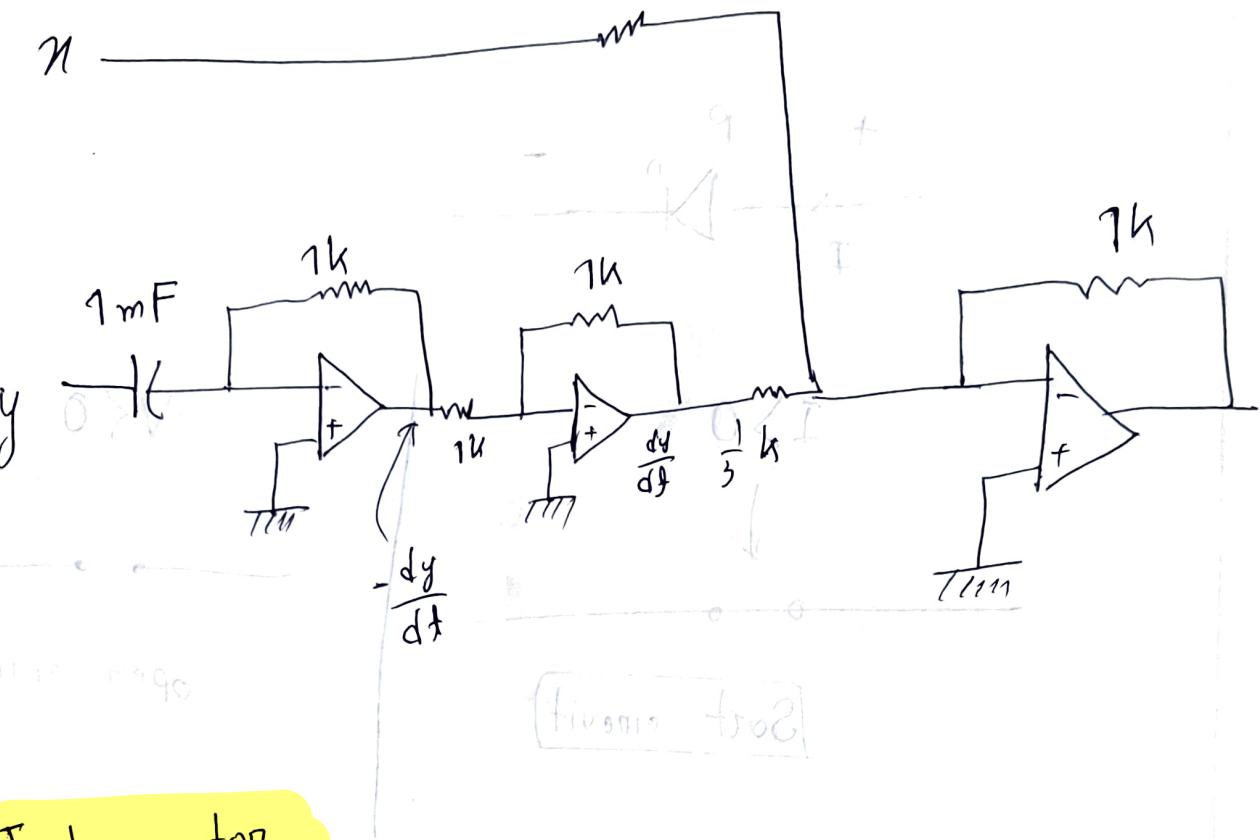


Integrator

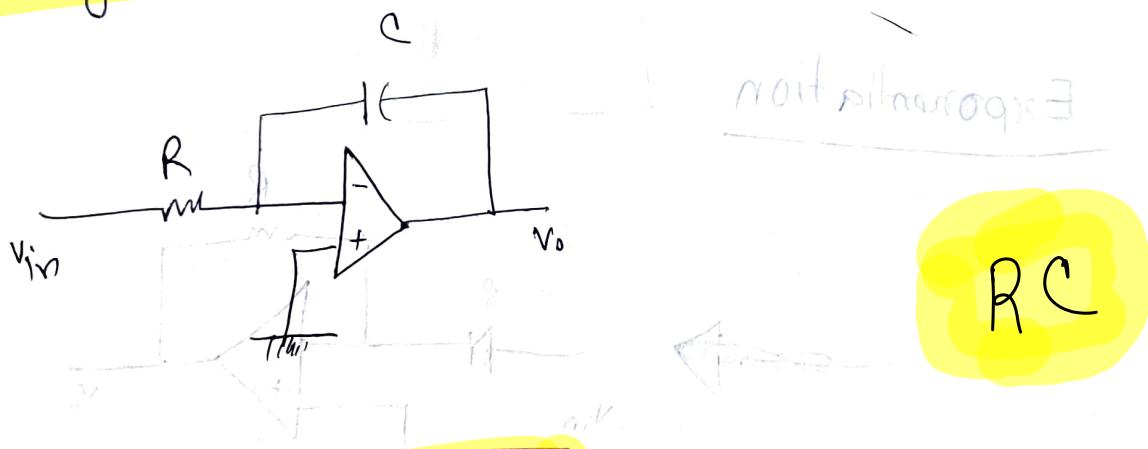

RC

$$V_o = -\frac{1}{RC} \int V_{in} dt$$

Diode

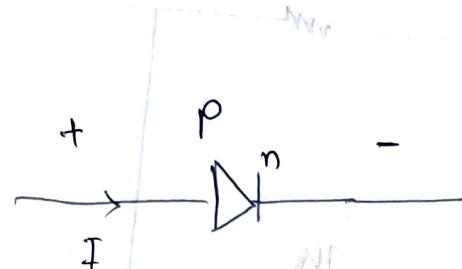

$$I > 0$$


Short circuit

$$V < 0$$

open circuit

Exponentiation


PR

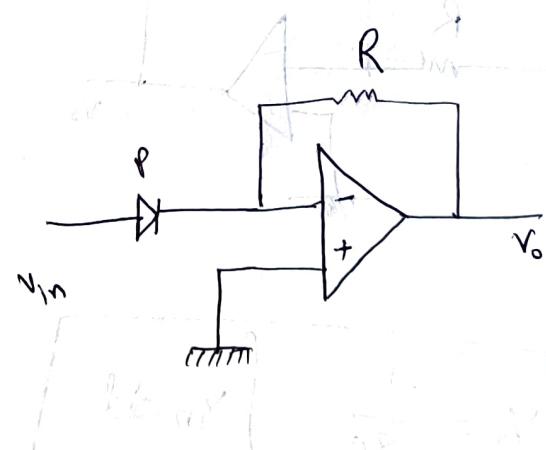

PR

$$v_o = -e^{v_{in}}$$

Logarithm

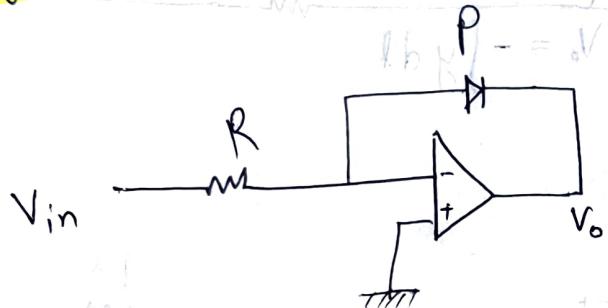

$$V_o = - \log_e (V_{in})$$

$$I_s R = 1$$

$$V_T = 1$$

ଆଶତ୍ରା ଆଜାତ୍ମ ଅଜାର୍ଦ୍ଦିଷ୍ଟ
ଏହିଏ ପ୍ରିଣ୍ଟିଂ.



ଶାନ୍ତି ବୁଝେ ଥାକେନ ଅନ୍ତରେ

ଆପନାହୁରୁ ରାଜୁ ଥଳୀ

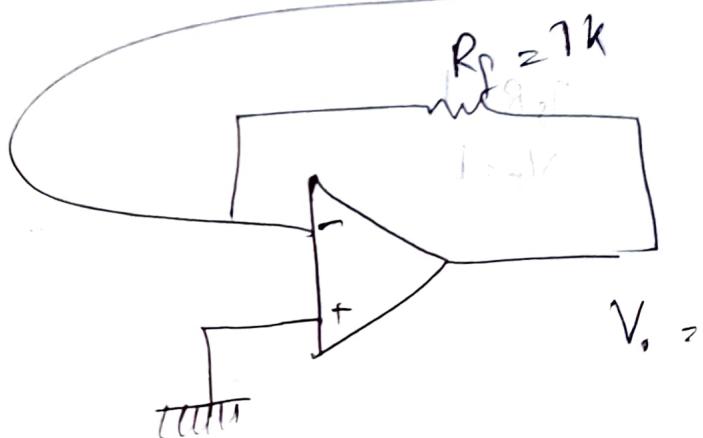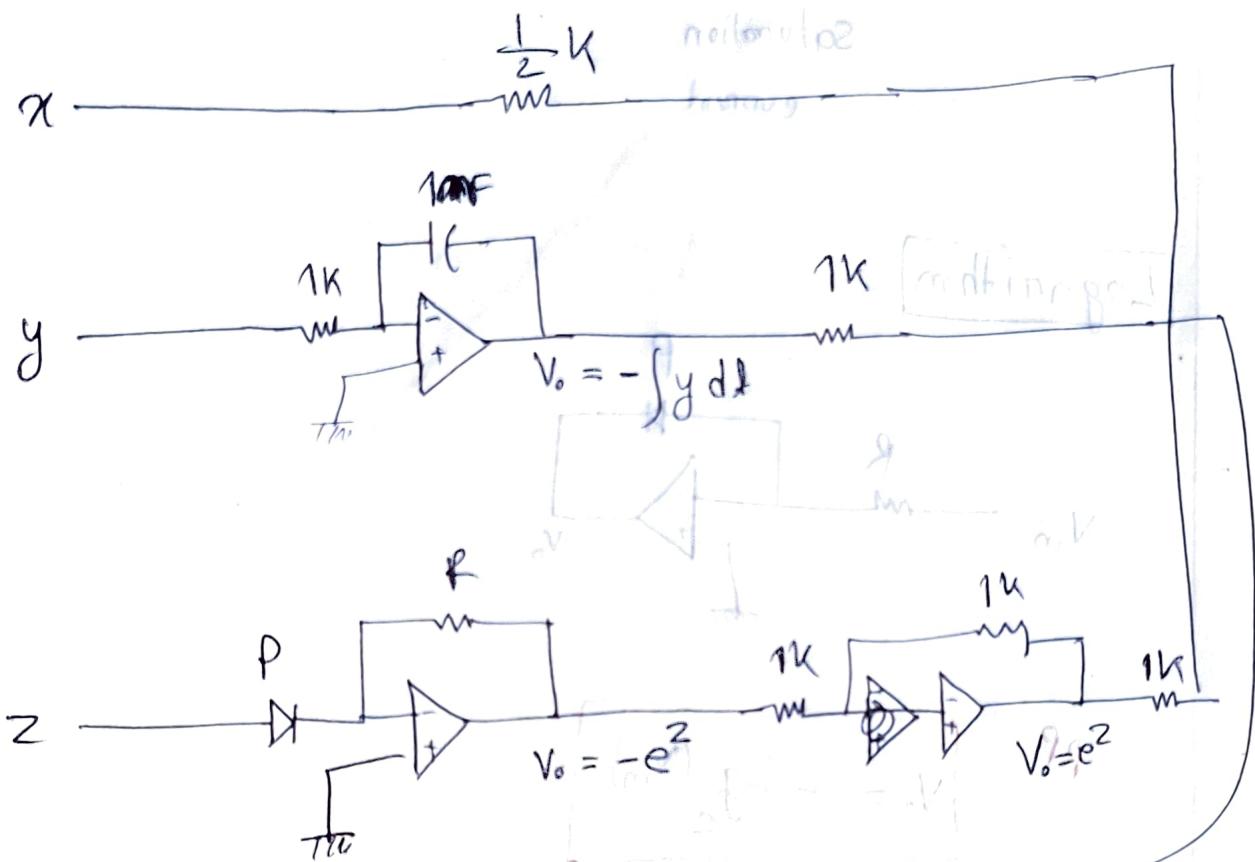problem solve \rightarrow

$$f = -2x + \int y \, dt + e^z$$

$$= - \left(2x - \int y \, dx + e^x \right)$$



$$\text{sub } 20 \leftarrow 150 \text{ (divide)}$$



* Multiplication (xy)

* Division ($\frac{x}{y}$)

$$- \log_e x + \log_e y \\ = (\log_e x + \log_e y)$$

$$\therefore x \rightarrow \log_e x \quad \left(\text{opposite} \right) \quad \frac{1}{10} \cdot 7 \\ \log_e x + \log_e y$$
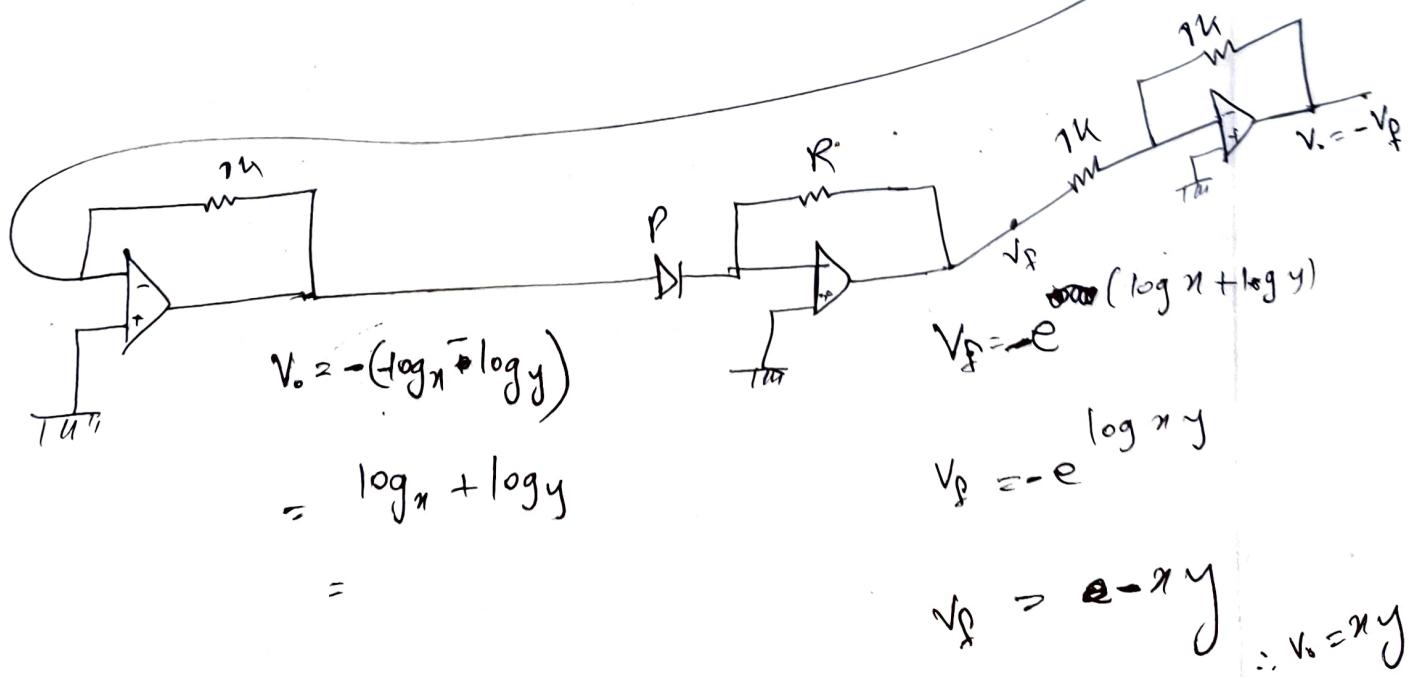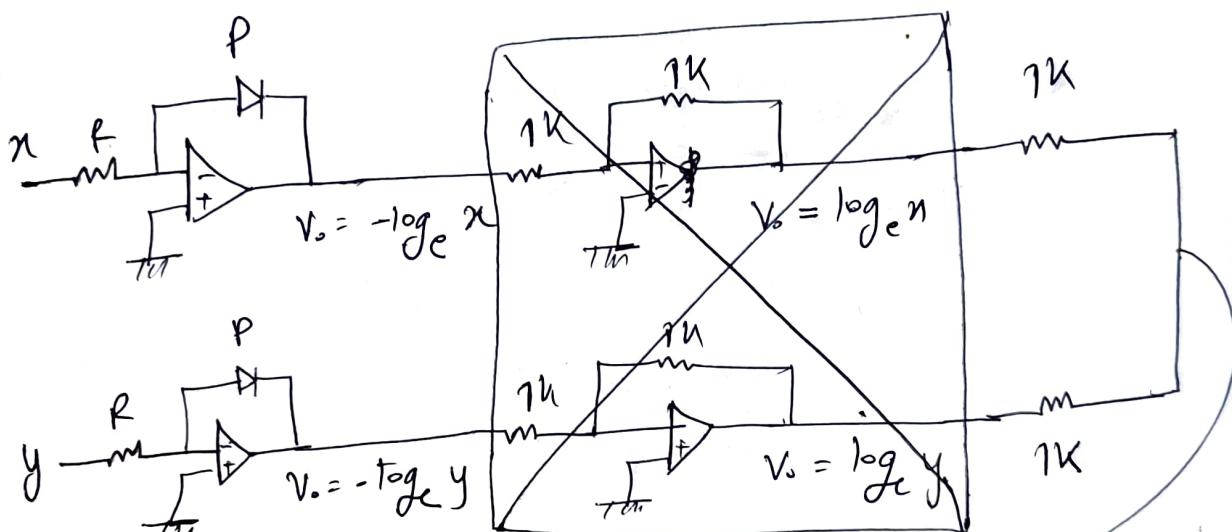
$$y \rightarrow \log_e y \quad \left(\text{opposite} \right) \\ = \log_e (xy) \xrightarrow{\text{opp}} xy$$



Quiz 1 \Rightarrow 25 June
syllabus

H.W


\rightarrow Alternate circuit
 \rightarrow OP-AMP

max complex

$$f = \frac{d}{dt} (\alpha \log \alpha)$$

$V_{out} \propto \alpha$
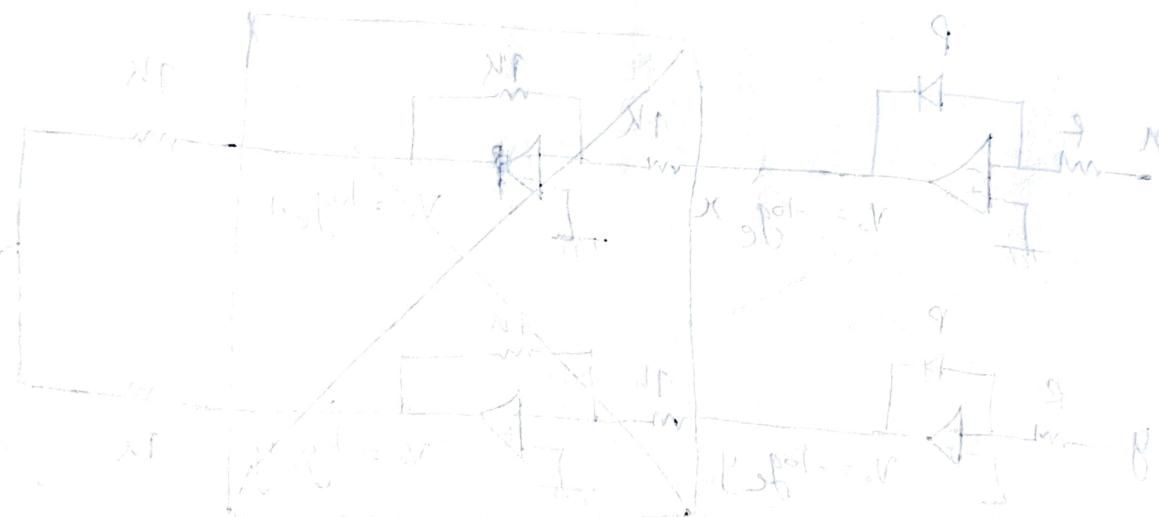
$$f = \frac{d}{dt} (\alpha \log \alpha) = \frac{d}{dt} (\alpha \log V_{out})$$




23.06.24

I-V characteristics


functional form:

$$I = f(V)$$

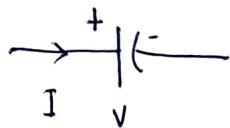


$$i = C \frac{dv}{dt}$$

$$V = g(I)$$

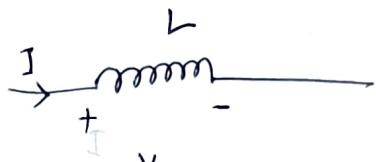


$$V = L \frac{di}{dt}$$

Graphical form:

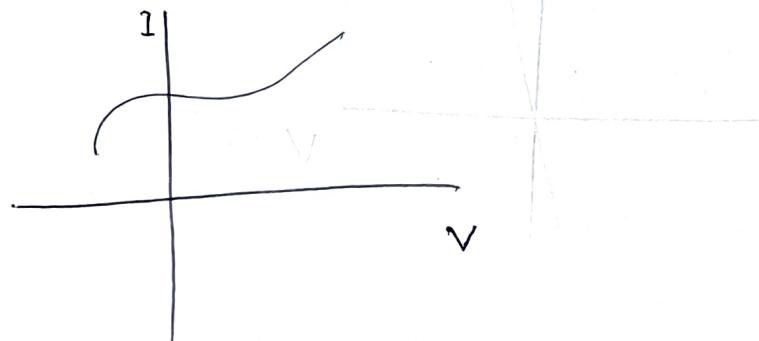

Resistance

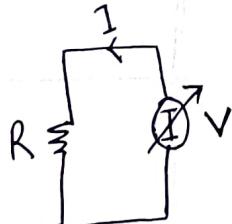


$$V = IR$$


$$\Rightarrow I = \frac{1}{R} V$$

$$\Rightarrow y = mx$$


for ΔV vs ΔI

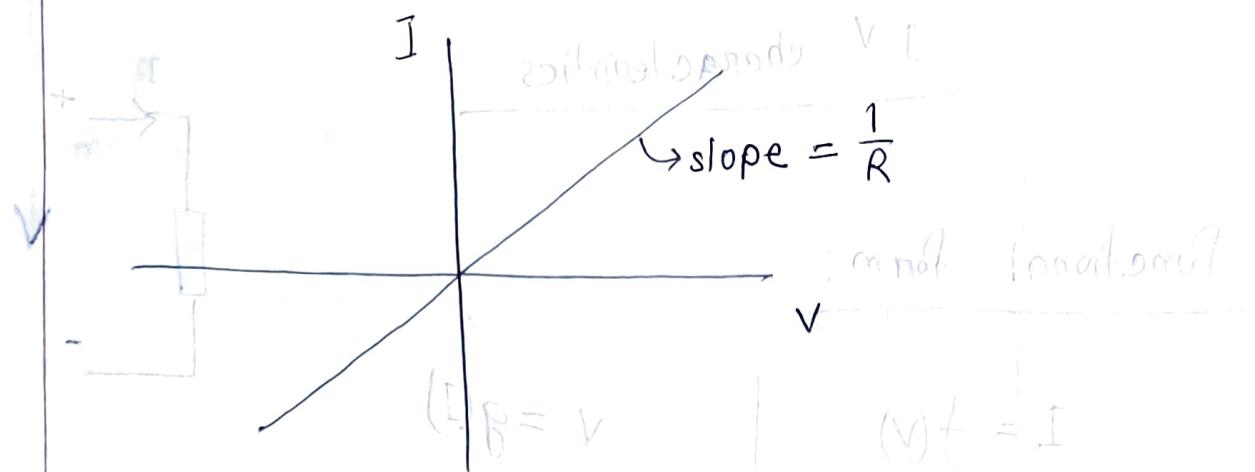


$R \uparrow$

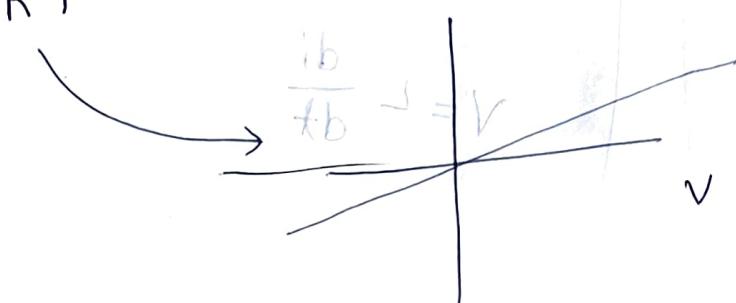


$R \downarrow$

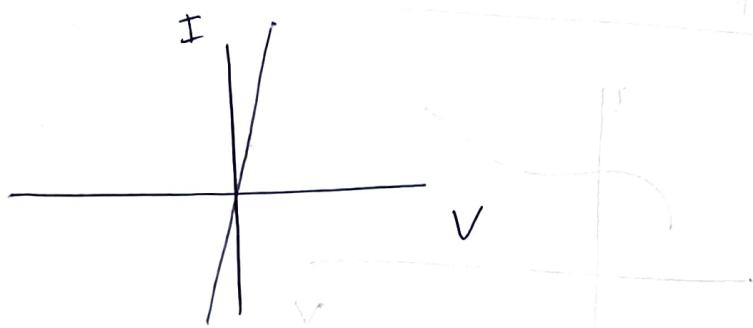




$R = 0$

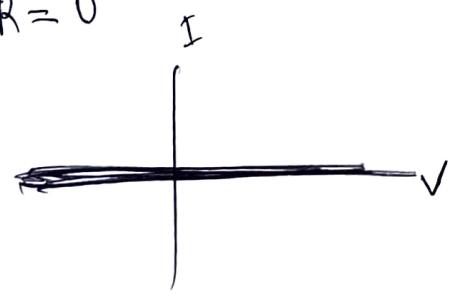


$R = \infty$

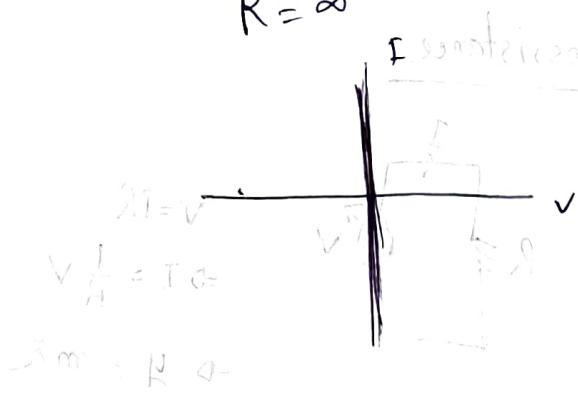


Current source IV curve

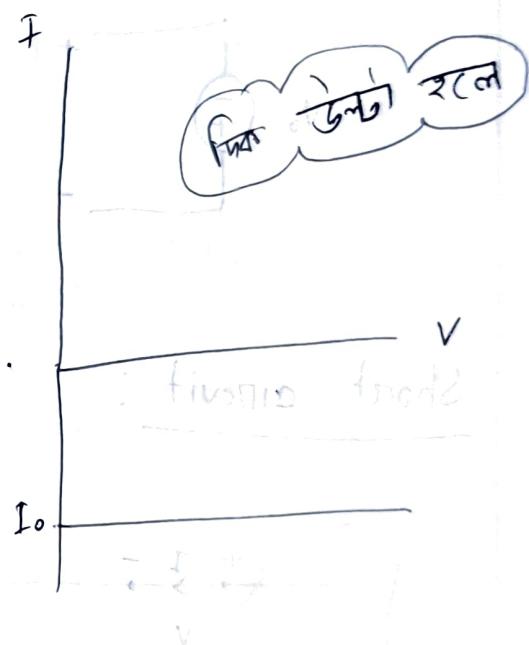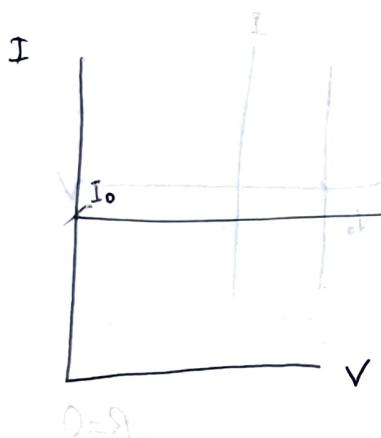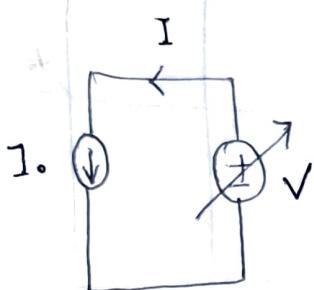




Voltage Source

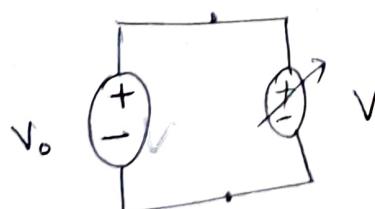

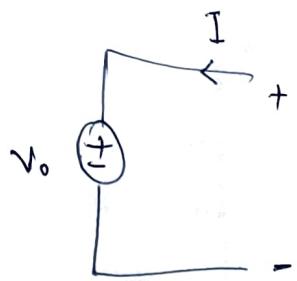goes node is 2nd and 3rd quadrant
 cz it violates KVL,
 $-V_0 + V = 0$



source V_0 is controlled by current I

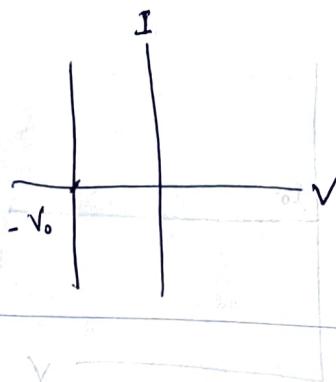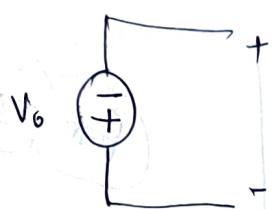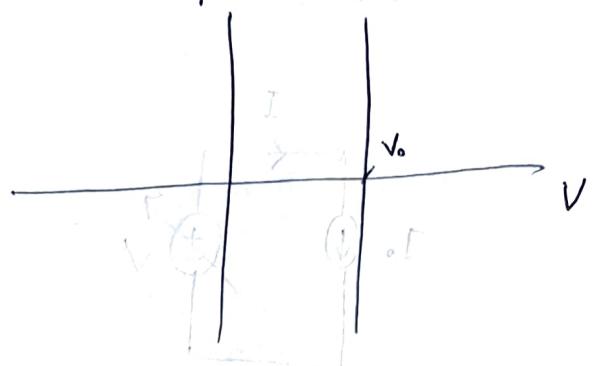

Short circuit:

$$\Delta V = 0$$


$$R = 0$$

$$V = 0$$

$$R = 0$$


$$V = 0$$

$$I$$

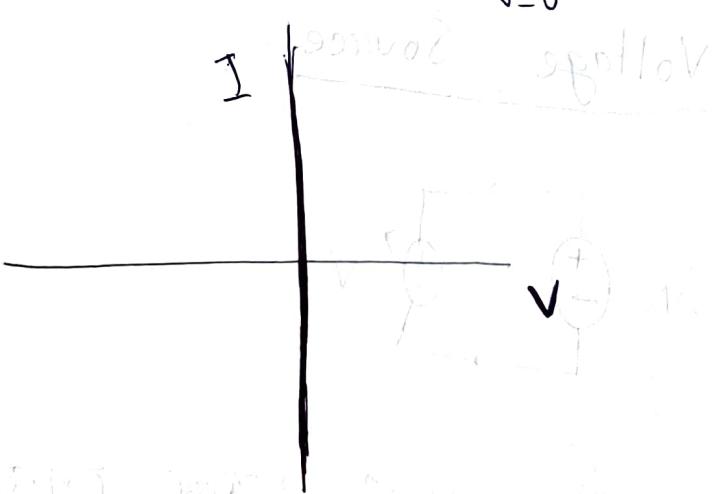



equivalent

Open Circuit :

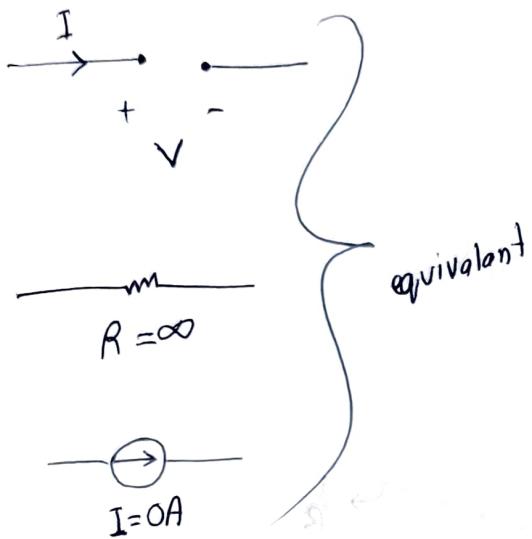


at both ends of the line

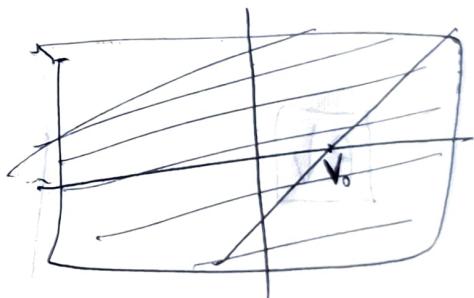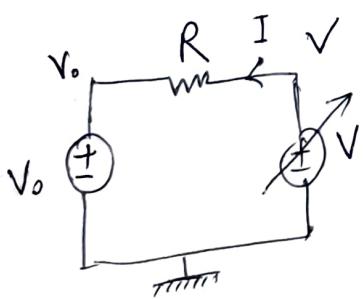
⇒ Voltage Source with series resistance :


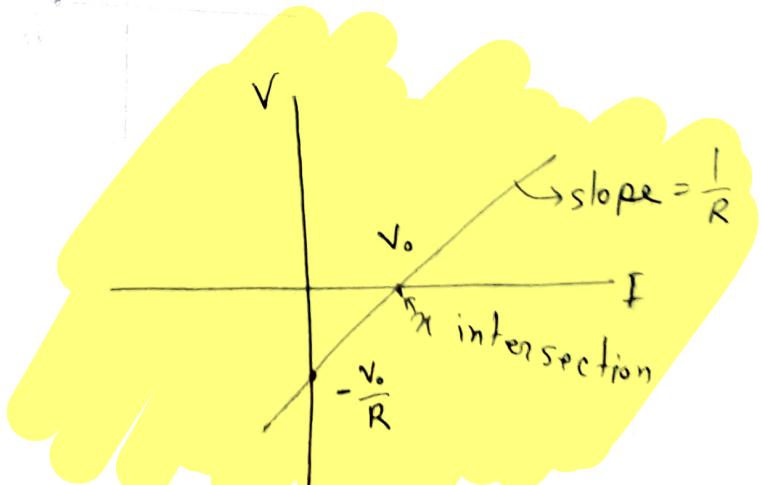
$$\begin{aligned} I &= \frac{(V - V_0)}{R} \\ \Rightarrow I &= \frac{1}{R} (V - V_0) \\ \Rightarrow I &= \frac{1}{R} V - \frac{V_0}{R} \\ \Rightarrow y &= mx + c \end{aligned}$$



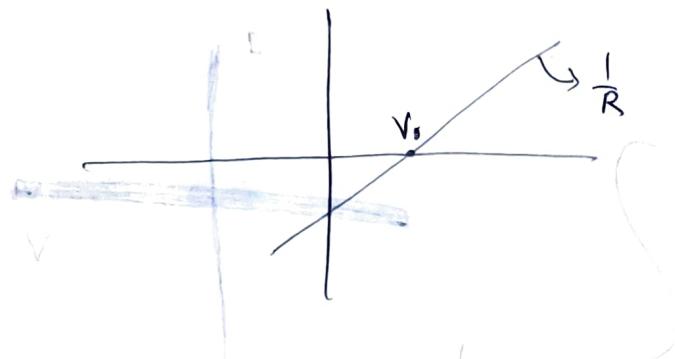
$$0 = \frac{1}{R} V = \frac{V_0}{R} \Rightarrow V = V_0$$




Introducing mag

just $\boxed{R \uparrow}$ with fixed V_0

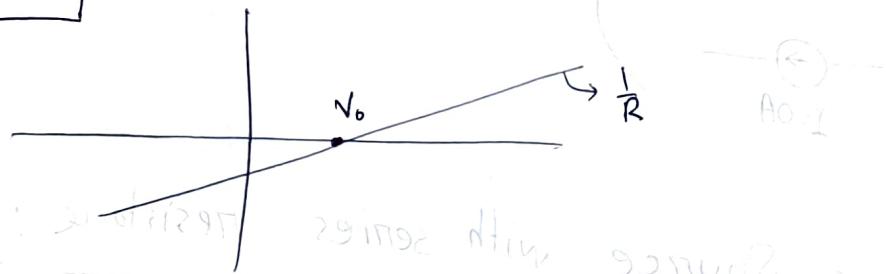

more options

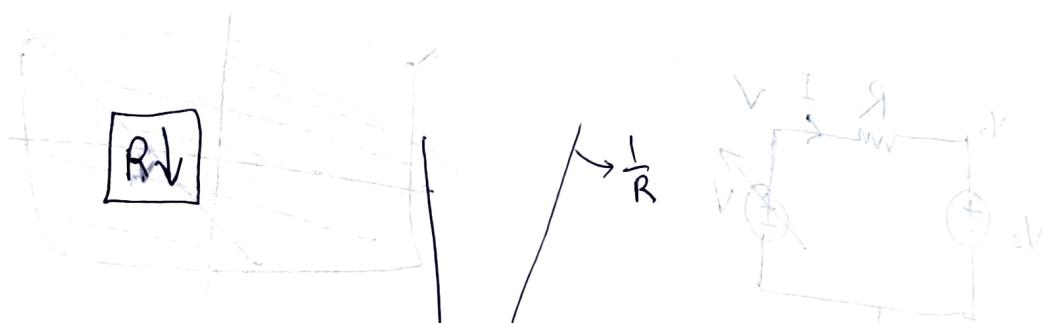

is possible

with $V_0 = 10$

with $I_0 = 10$

$$\boxed{V = V_0 + \frac{I}{R} I_0}$$


$$V = V_0 + \frac{I}{R} I_0$$

$$(V - V_0) = \frac{I}{R} I_0$$

$$\frac{V - V_0}{I_0} = \frac{1}{R} I$$



$$V = V_0 + \frac{1}{R} I_0 I$$

$V_o \uparrow$ with fixed R

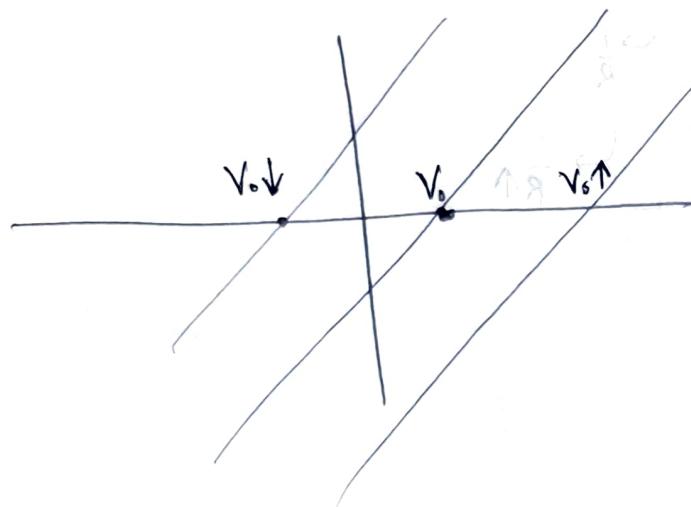

$V_o \uparrow$ and $I_o \uparrow$


Current source with parallel Resistance:

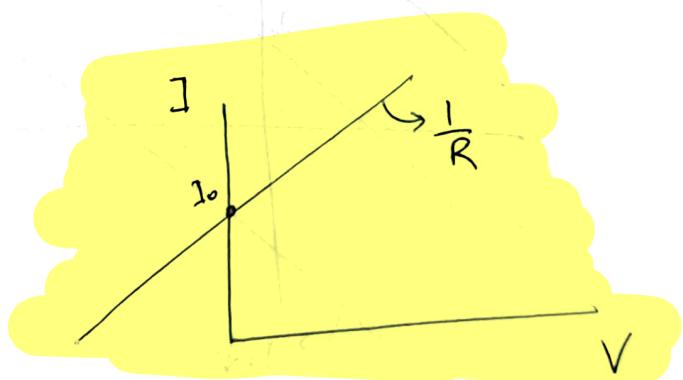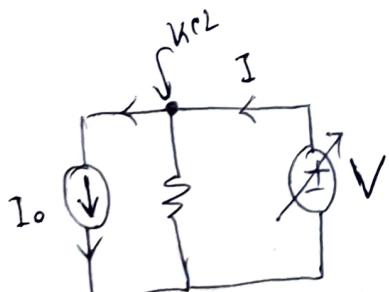


$$I = I_o + \frac{V}{R}$$

$$\Rightarrow I_o = \frac{1}{R}V + I_o$$

$$\Rightarrow y = mx + c$$


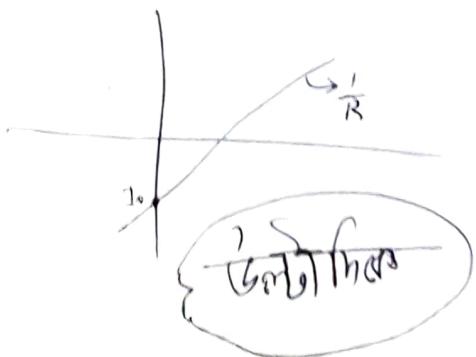


$R \uparrow$ on $R \downarrow$

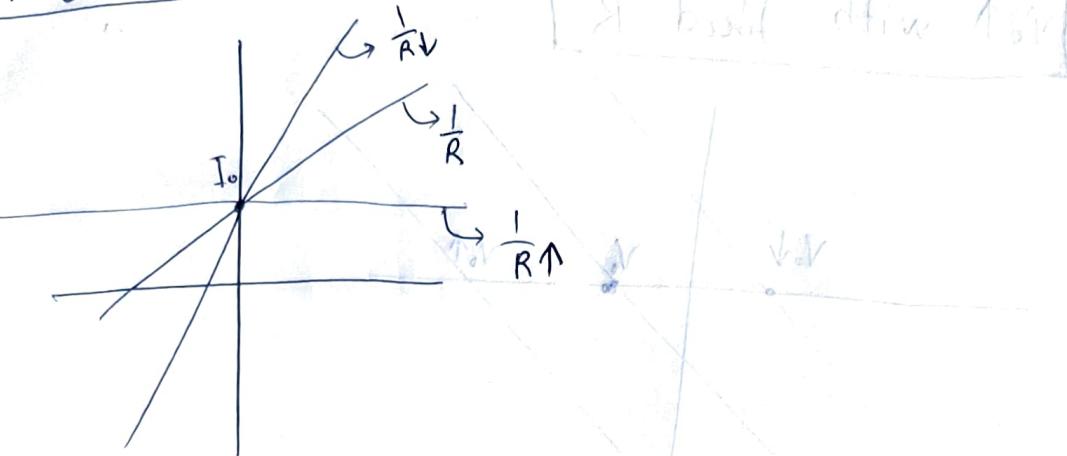

[δ is small, effective A_{eff}]

$I_0 \uparrow$ or $I_0 \downarrow$

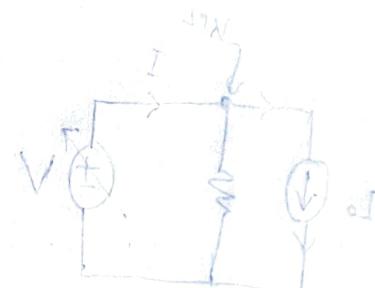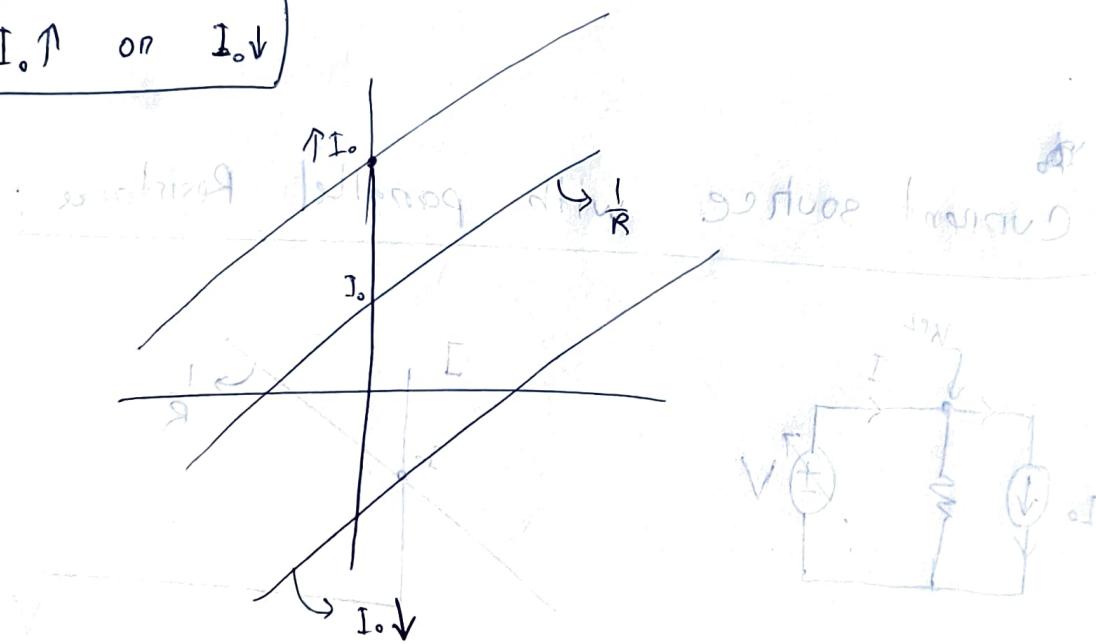

$$\frac{V}{R} + I = I$$

$$I = \frac{V}{R}$$

$$I = \frac{V}{R}$$

ଏ ବର୍ତ୍ତି ଆପାଦନ କରନ୍ତି
କିମ୍ବା କାହାର!

ଏ ବର୍ତ୍ତି ଆପାଦନ କରନ୍ତି
କିମ୍ବା କାହାର!



design \Rightarrow

Resistance ~~is~~ parallel with ~~not~~ VS..





No change


$$V_0 R = V_0 = 0$$

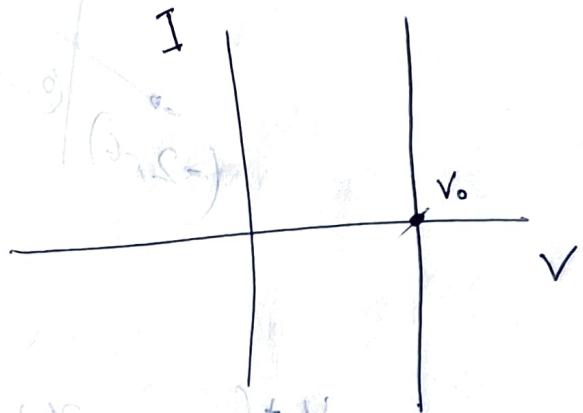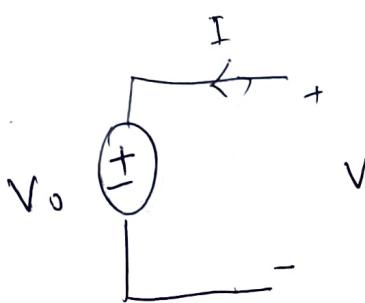


Resistance series with CS :

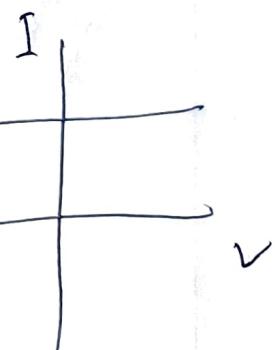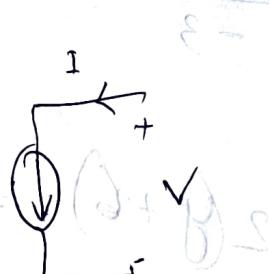

Design the circuit from the I.V graphs

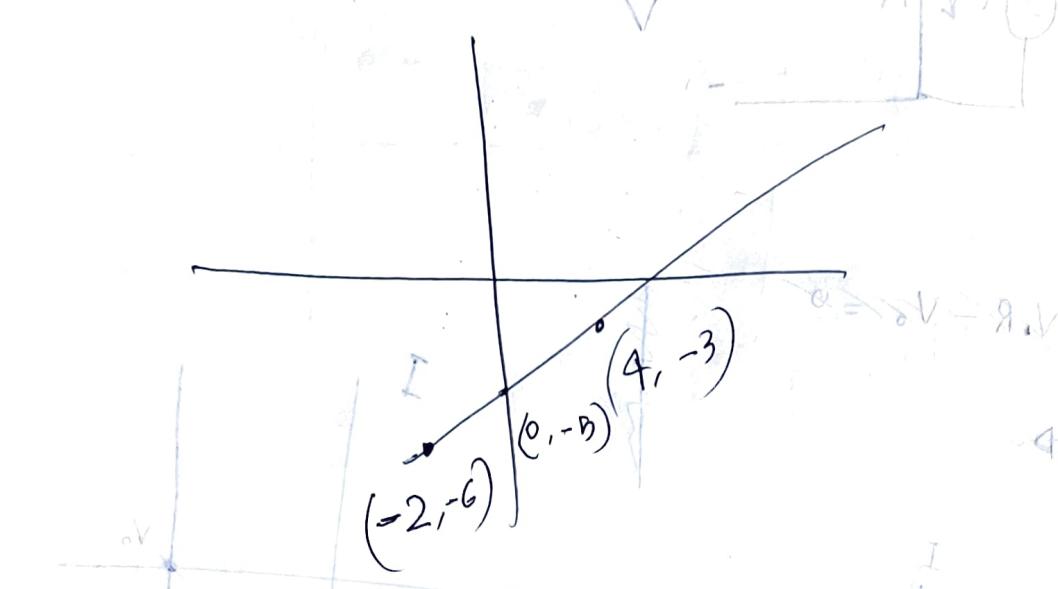

$$\frac{y+6}{-6+3} = \frac{x+2}{-2-4}$$

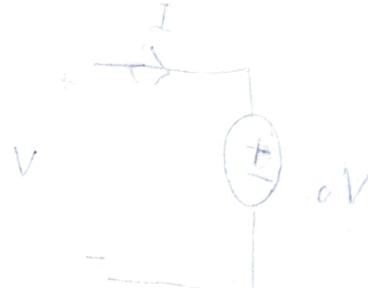



$$\Rightarrow \frac{y+6}{-3} = \frac{x+2}{-6}$$

$$\Rightarrow 2(y+6) = x+2$$


$$\Rightarrow 2y + 12 = x + 2$$

$$\Rightarrow y = \frac{1}{2}x - \frac{10}{2}$$



$$\therefore y = \frac{1}{2}x - 5$$

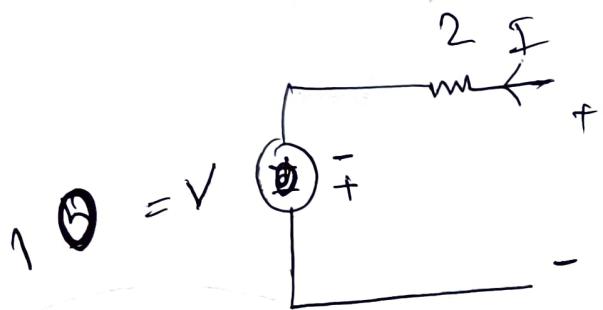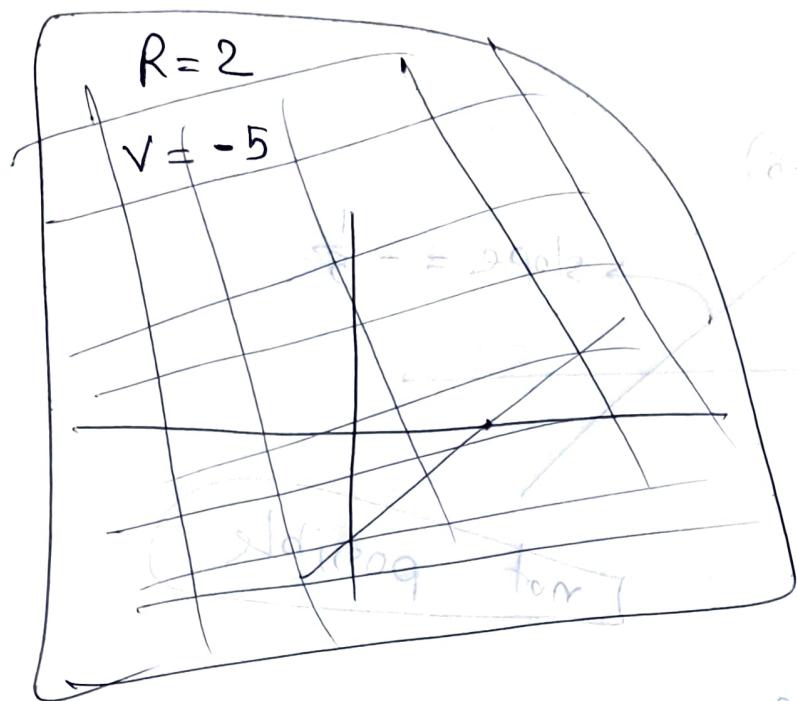

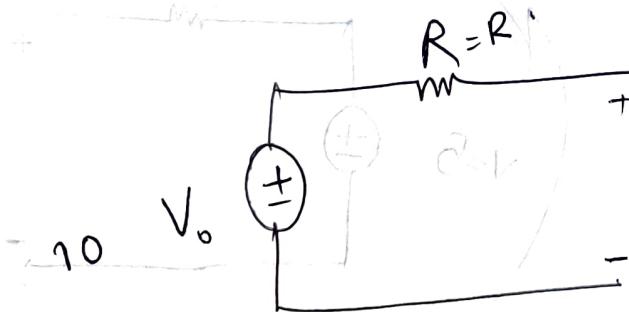
$$V + \frac{RI}{R} = V \Rightarrow 0 = \frac{1}{2}x - 5 \Rightarrow x = 10$$


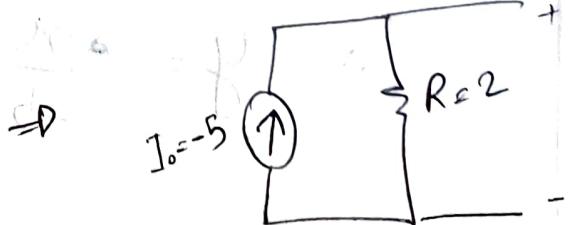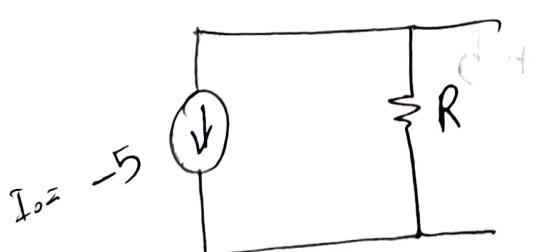
$$V_0 + \frac{RI}{R} = V_0 \Rightarrow 0 = \frac{1}{2}x - 5 \Rightarrow x = 10$$



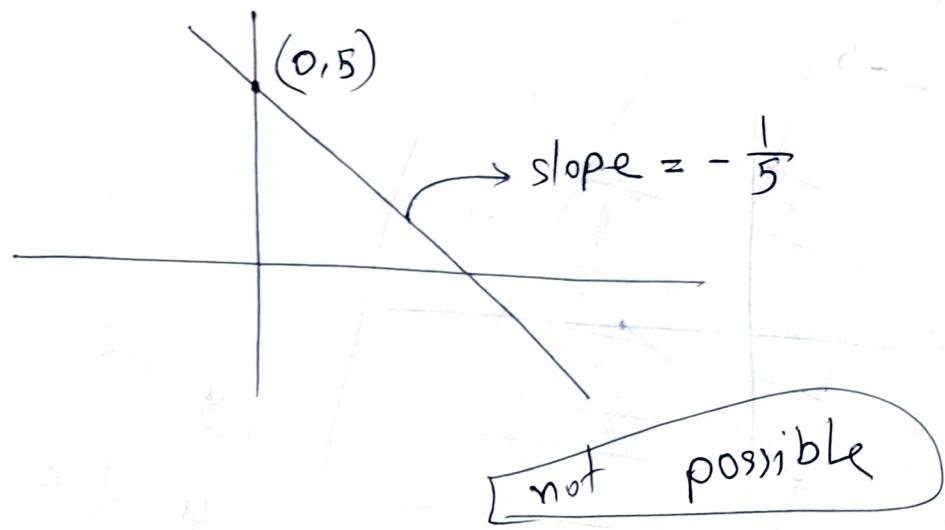

$$y = mx + c$$


$$\Rightarrow y = -\frac{x}{5} + c$$

$$\therefore (0, 5) \Rightarrow$$

$$5 = 0 + c$$


$$\Rightarrow c = 5$$

$$y = -\frac{x}{5} + 5$$


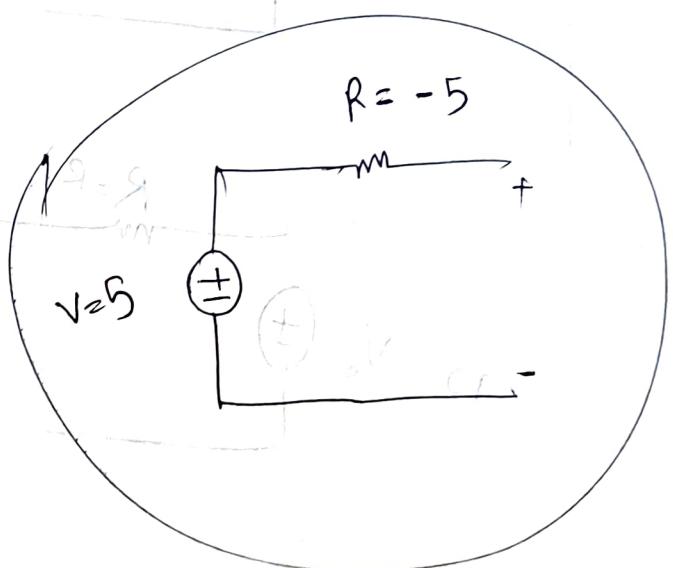


25.6.24


(24) 25.6.24
Diode

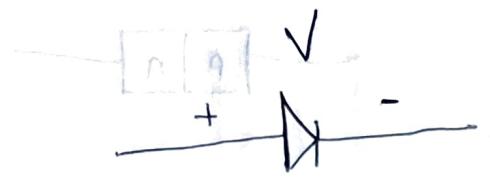

positive

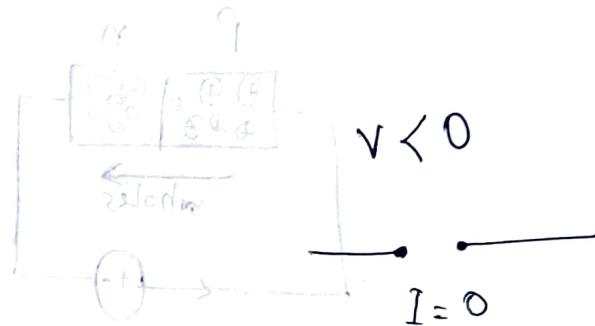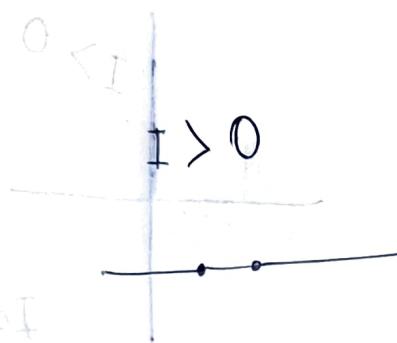

Graph of I vs V

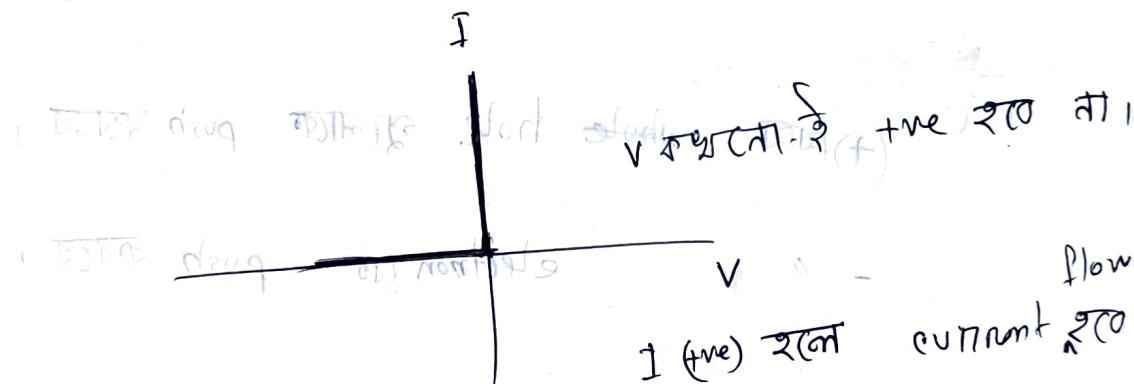

Graph of I vs V
 $V < 0$
 $V > 0$
 $I = 0$ for $V < 0$
 $I > 0$ for $V > 0$

Semiconductor (Si, Ge)

Graph of I vs V
 $V < 0$
 $V > 0$
 $I = 0$ for $V < 0$
 $I > 0$ for $V > 0$

doping

(Al) III


p-type

V (p)

n type.


Ideal Diode

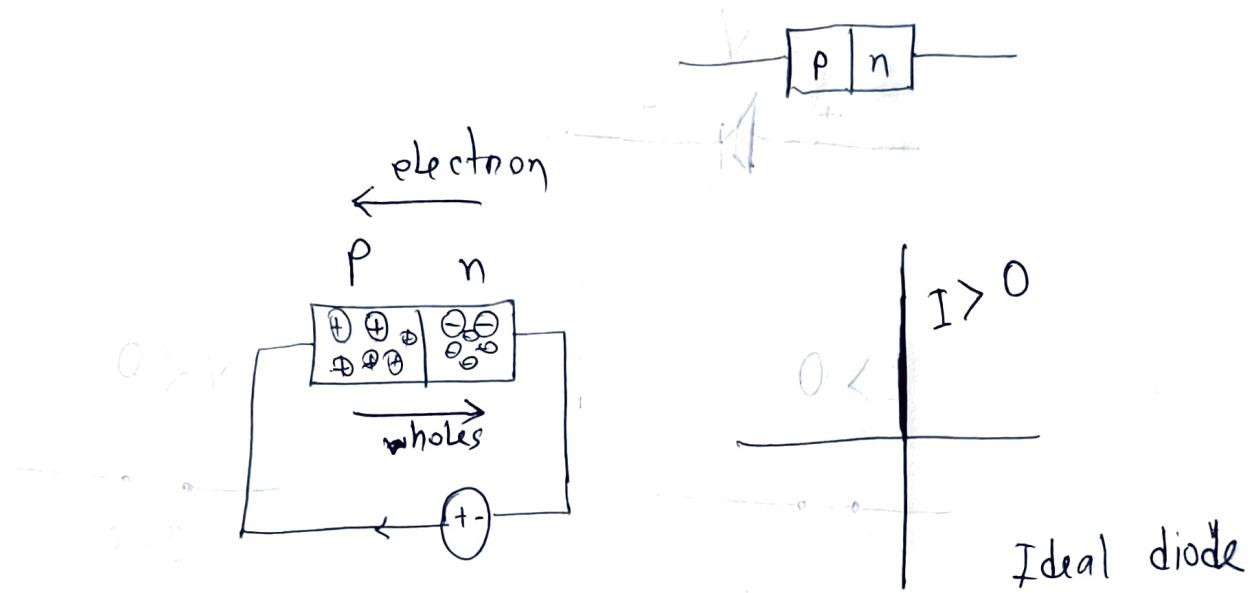p type \rightarrow majority carrier holes (+ve)



(+) যদি ~~hole~~ hole সূলতে push করবে ,


- " V electron কে push করবে ,

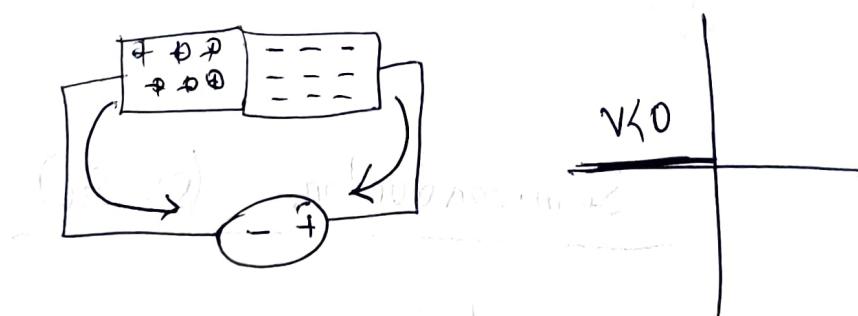

Ideal diode

Real diode:

15 Jan 1985

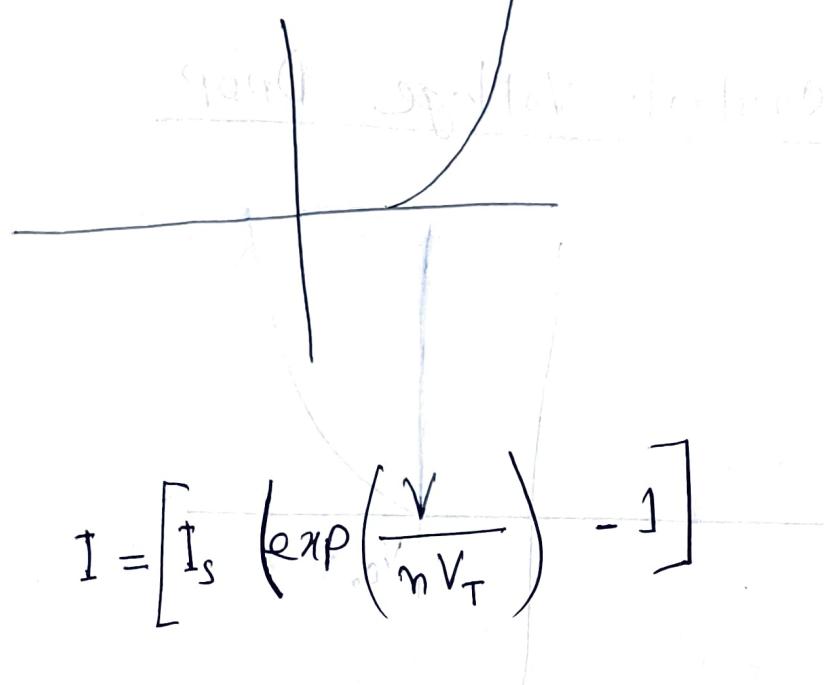

$$I = \left[I_S \left(\exp \left(\frac{V}{nV_T} \right) - 1 \right) \right]$$

I_s = reverse saturation current $(10^{-9} A)$

$n = \text{ideality factor } (1/2) = \sqrt{e} \approx 0.707$

$$V_T = \text{thermal voltage} \left(\frac{kT}{qV} \right), 26mV \text{ for room temp}$$


diode ରାତାନୋର କର୍ମ୍ୟ ଏହି ପ୍ଲାଟି ମିଳିବାରେ କାହିଁ ହେଲାଯାଇଥାଏ ।

ଗ୍ରାମ ପାଇଁ ଆଏ change କରା ଯାଏ ନାହିଁ ।

CVD model

leibniz

Constant Voltage Drop

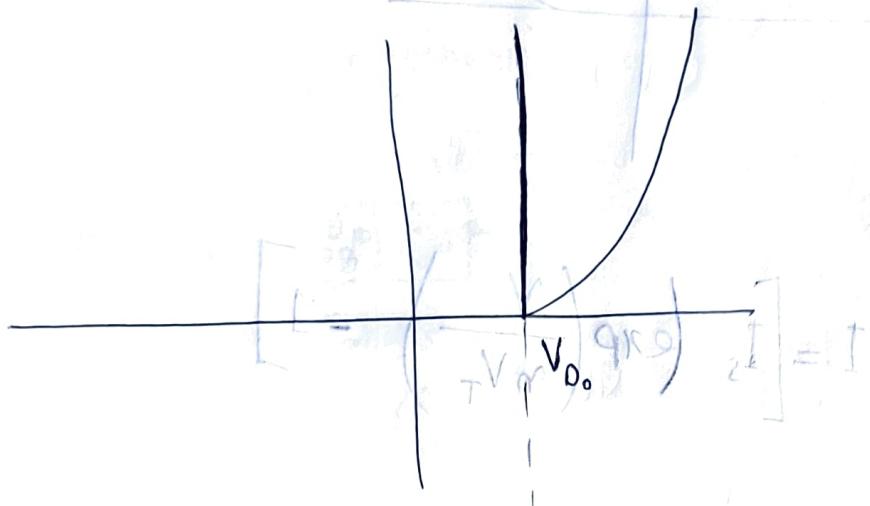

$$f_{on} \rightarrow S_i \rightarrow V_{D0} = 0.7V$$

$$f_{on} \rightarrow Ge \rightarrow V_{D0} = 0.2V$$

When $I > 0$, $V < V_{D0}$




When $I < 0$, $V > V_{D0}$

With this bias, it is possible to use this

~~CVDr~~


CVDr + r model

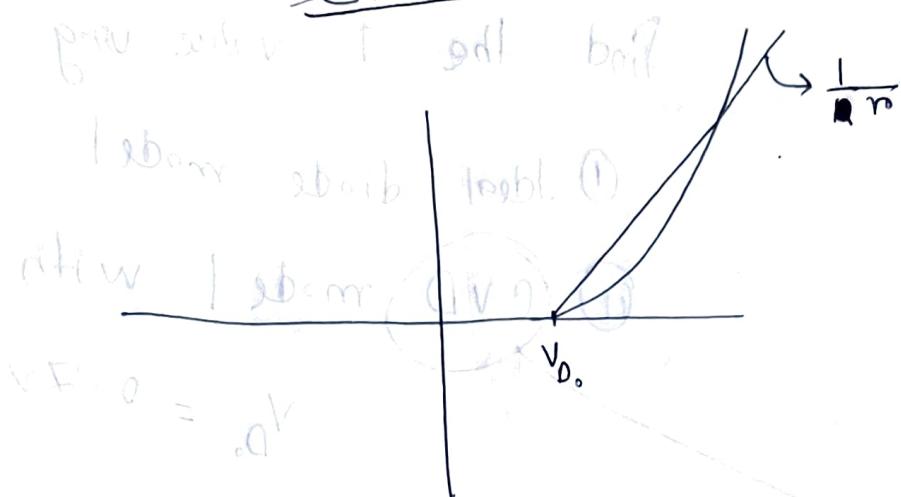

when,

$I > 0$,

$$V_F = 0V$$

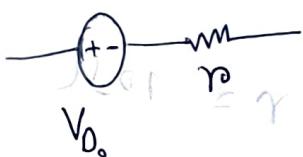

STB are ∞
trans. ∞
 $0V$

2. trans. normal, STB trans. normal abo, ①

when,

CVDr + r \neq 0

$$V < V_D$$



①



Find the I value using

① Ideal diode model

② CVD model with

$$V_{D_0} = 0.7V$$


③ CVD_{nr} model with

$$V_{D_0} = 0.7V$$

$$r = 10\Omega$$

କିଛି ହାଲ ମାତ୍ର
ମାତ୍ର କାମାଳ
CVD

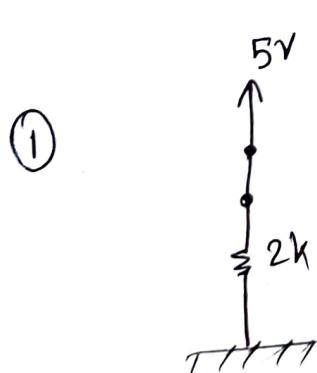
① Diode linear component ହାଇ, linear component କାମାଳ
convert କାମେ କିମ୍ବା କିମ୍ବା



$$I = \frac{5-0}{2} = 2.5$$

behaves like a voltage source
but not exactly voltage source,
passive

11

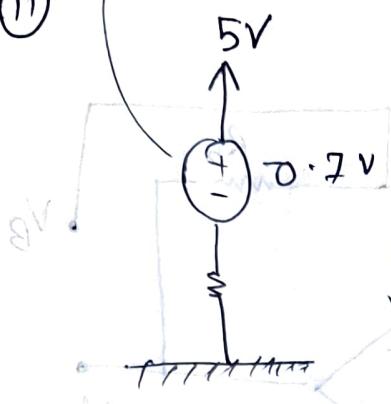

KVL


$5 - 0.7 = 0.7 + 1 \cdot I$ \Rightarrow step voltage drop

$$5 - 0 = 0.7 + 1 \cdot I^2$$

$$\Rightarrow I = 2.15 \text{ mA}$$

(Ans)

11

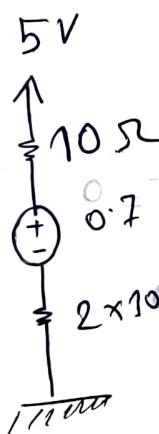

$$0 = -10I$$

$$0.7 = 10I \Rightarrow I = 0.07 \text{ A}$$

$$0 = +10I \Rightarrow I = 0 \text{ A}$$

$$0 = +10I \Rightarrow I = 0 \text{ A}$$

$$0 = +10I \Rightarrow I = 0 \text{ A}$$

$$5 - 0 = 10I + 0.7 + \cancel{2 \times 10^3 \Omega \cdot I}$$


$$5 = 0.01I + 0.7 + 2I$$

$$I = 2.139$$

$$I \approx 2.14$$

CVD + n

30/06/24

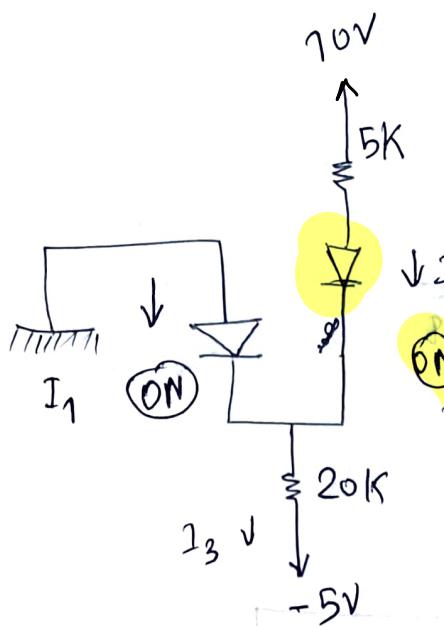

current high \rightarrow low $I_{1/2}$

OFF

ON

current the outside

Find I_1, I_2, I_3

Assume CVD diode model, with $V_{D_0} = 1\text{V}$

To know I_D , we need to know diode ON/OFF

To know ON/OFF, we need to know I .

Method of Assumed State

Step 1:

Assume

ON
OFF



Step 2:

ON



OFF



Solve the circuit, Find I_D , V_D for All diode

Step 3:

ON, $I > 0$

OFF $V < 0$

Assume that,

$D_1 \rightarrow$ ON

$D_2 \rightarrow$ OFF \rightarrow ON

$10V$
 \uparrow
 $5K$

$1V$
 \uparrow
 $20K$

$-5V$
 \uparrow
 3_3

$$10 - (-5) = 5I_2 + 1 + 20I_3$$

$$\Rightarrow 15 = 5I_2 + 20I_3 + 1$$

$$0 - (-5) = 1 + 20I_3$$

$$\Rightarrow 20I_3 = 4$$

$$\Rightarrow I_3 = \frac{4}{20} = \frac{1}{5} \Rightarrow I_3 = 0.2$$

$$I_1 + I_2 = I_3$$

$$\Rightarrow I_1 + I_2 - I_3 = 0$$

$$I_1 = -\frac{9}{5} = -1.8 \text{ mA} \neq 0$$

OFF হওয়া হচ্ছে

But বিকর্তৃ অ রেল
মাছে না।


$$I_2 = 2 \text{ mA} > 0$$

$$I = 0.2 \text{ mA}$$

Assume

D_1 OFF

D_2 ON

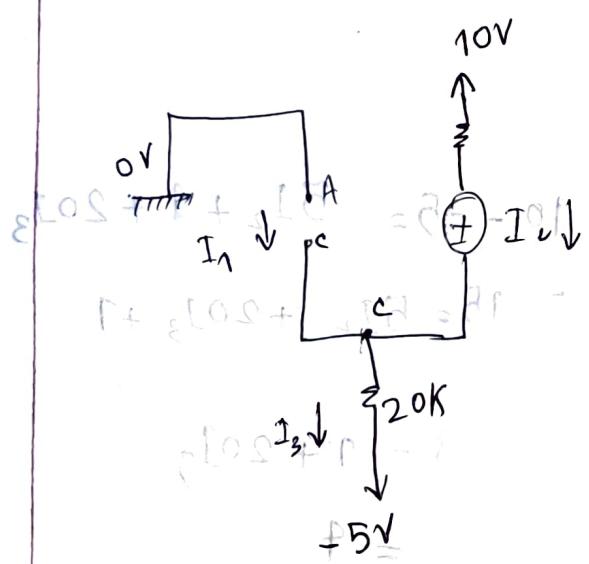

$$I_1 = 0$$

$$I_2 = I_3$$

$$10 - (-5) = 5I_2 + 1 + 20I_3$$

$$\Rightarrow 5I_2 + 20I_3 = 14$$

$$\Rightarrow 25I_2 = 14$$

$$\therefore I_2 = 0.56$$

$$I_1 = 0$$

$$I_2 = 0.56 \text{ mA} > 0$$


$$I_3 = 0.56 \text{ mA}$$

$$\frac{V_c - (-5)}{20} = 0.56$$

$$\Rightarrow V_c = -6.2 < 0$$

\therefore Assumption verified.


(Ans)

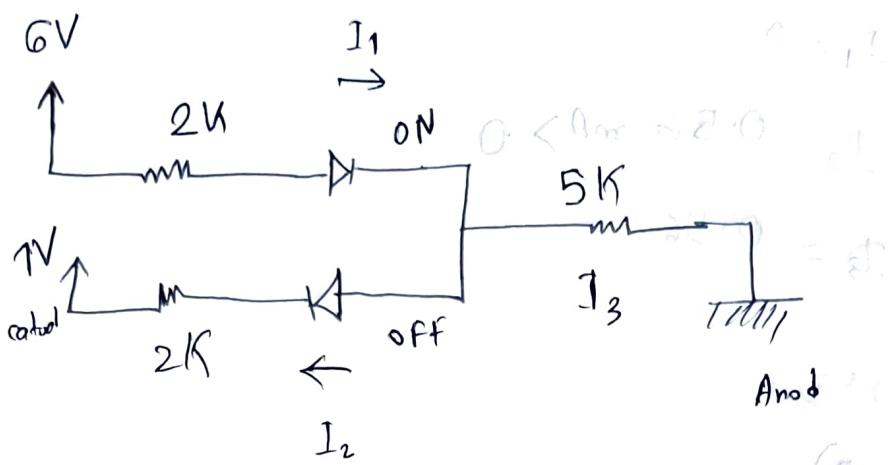

6 জায় 0 থেকে মাত্র হচ্ছে I_1 +ve হতে পারে।

$$D_1 = \text{ON}$$

$$D_2 = \text{OFF}$$

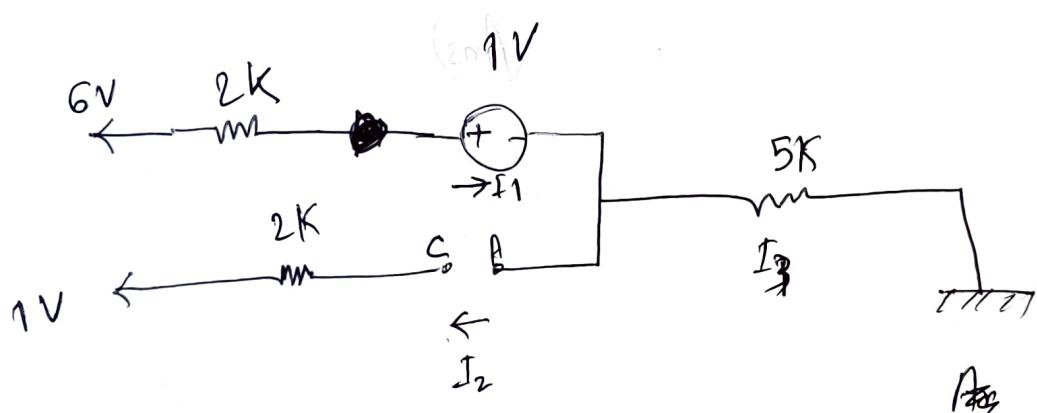

$$I_2 = 0$$

$$I_3 = I_1$$

$$6 - 0 = 2I_1 + 1 + 5I_3$$

$$\Rightarrow 2I_1 = 5 \Rightarrow I_1 = 0.71$$

$$J_1 = 0.71 > 0$$

$$J_2 = 0$$

$$J_3 = 0.71$$

~~$$J_1 = \frac{V_A - 0}{5} = 0.71$$~~

$$= \frac{V_A - 0}{5} = 0.71$$

$$= 3.55$$

$$V = V_A - V_c$$

$$= 3.55 - 1$$

$$= 2.5 \text{ kV}$$

$$J_2 = 0$$


$$J_3 = 0$$

Assumption wrong. $J_1 + J_2 = 0.1$

$$J_1 = 3.55 + 0.1 = 3.65$$

$$J_1 + J_2 = 0.1$$

$$J_1 = 3.55 + 0.1 = 3.65$$

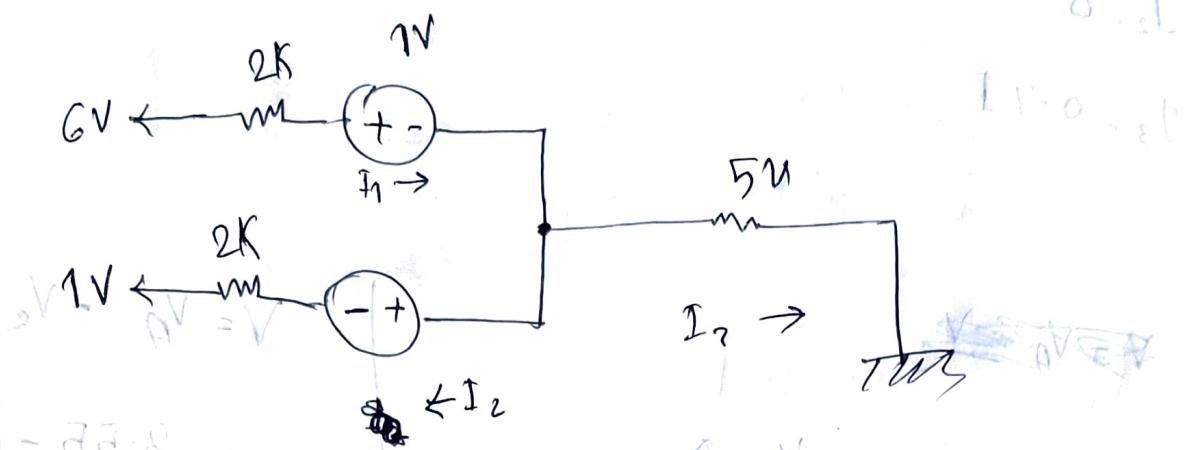

$$6 - 0 = 2I_1 + 1 + 5I_3$$

$$\Rightarrow 2I_1 + 5I_3 = 5$$

$$I_1 = \frac{5}{7} = 0.71$$

$$I_2 = \frac{3}{4} = 0.75$$

$$I_3 = \frac{1}{2} = 0.5$$

$$1 - 0 = -2I_2 + 5I_3 - 1$$

$$\Rightarrow -2I_2 + 5I_3 = 1$$

$$I_1 = I_2 + I_3$$

$$\Rightarrow I_1 - I_2 - I_3 = 0$$

Anode \rightarrow cathode

$$I_1 = 1.04 \text{ mA} > 0$$

$$I_2 = 0.95 \text{ mA} > 0$$


$$I_3 = 0.58 \text{ mA}$$

Connect!



$(V_{DD} = 5V)$ \rightarrow true
Logic gate with Diodes

(Ideal diode)


OR gate op circuit

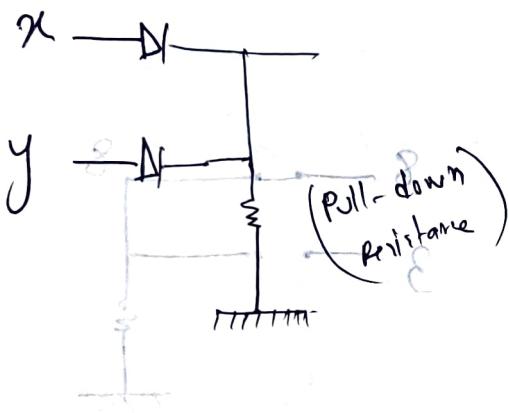

x	y	Vout
0	0	0
0	1	1
1	0	1
1	1	1

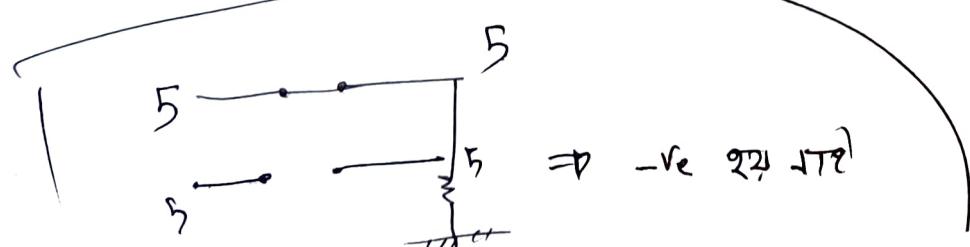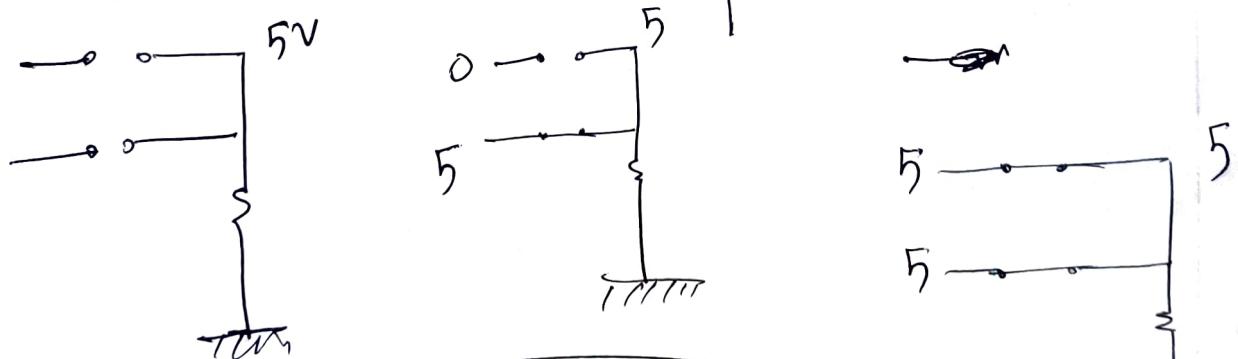


abortion - ~~the~~ - ~~the~~ - ~~the~~

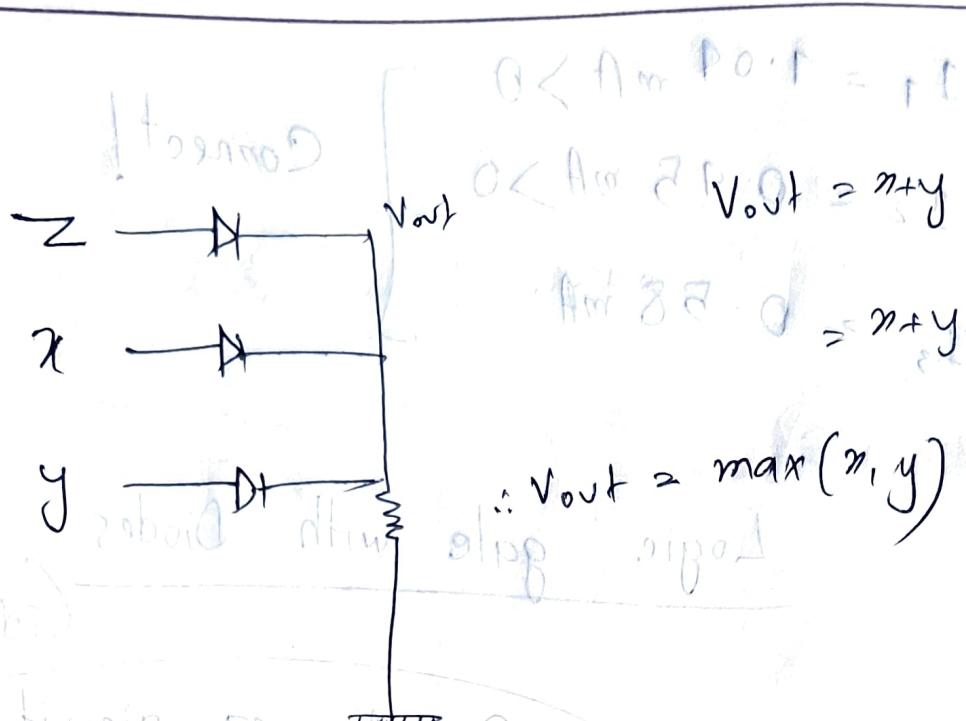

1803 3 1000

6 hours 92 5761 90 18 285 5

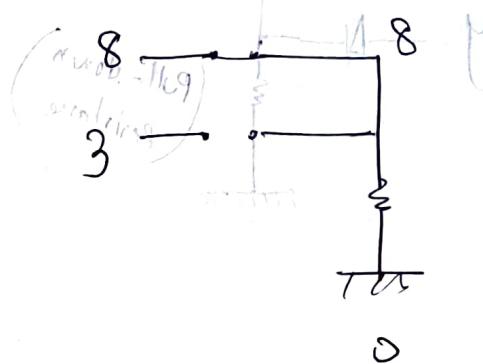


144 *Journal of Health Politics*



3. What is the name of the author?

$x_1, y_1, z_1 \geq 0$ $25^\circ C$
 $x_2, y_2, z_2 \geq 0$ $25^\circ C$ $25^\circ C$

And gate circuit

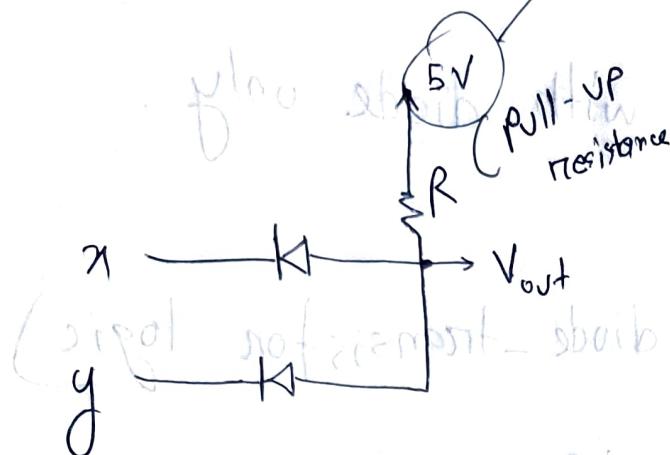


state		V_{out}
x	y	
0	0	0
0	1	0
1	0	0
1	1	1

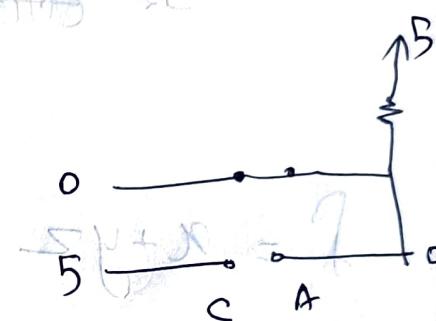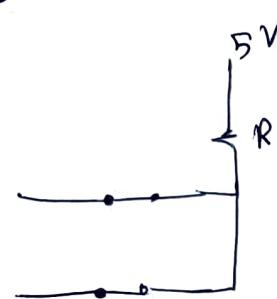

ON STATE +ve current flow through R

$$-V_c = -5$$

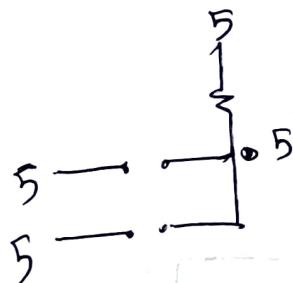

$$V = xy$$

$$V_{out} = xyz$$

$$x = 3V$$

$$y = 7V$$

$$V_{out} = \min(x, y, z)$$

Not Gate



laminating

Not possible


with diode only.

DTL (diode-transistor logic)

$$f = x + yz$$

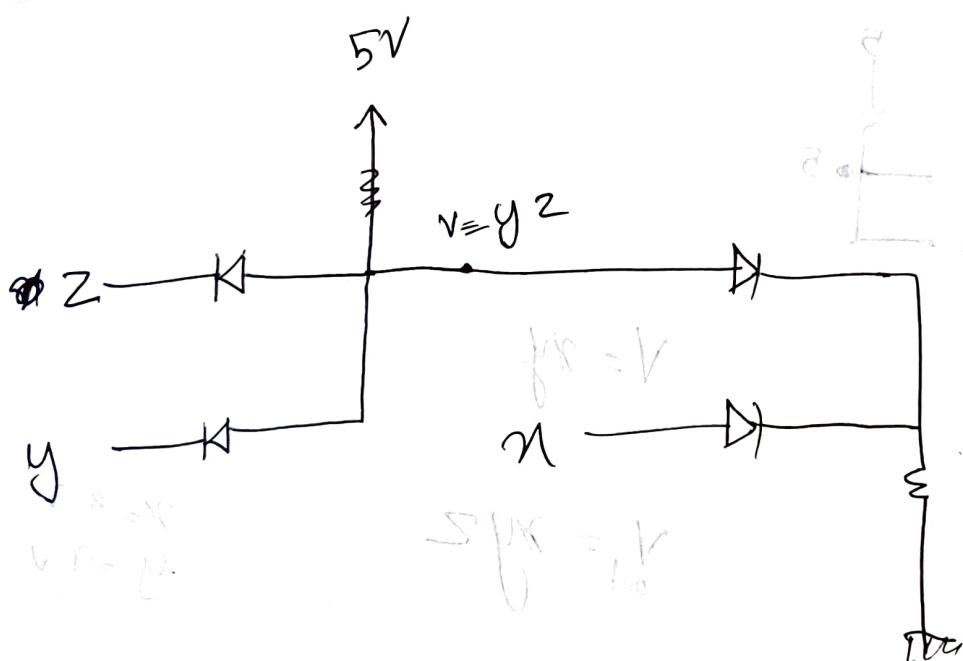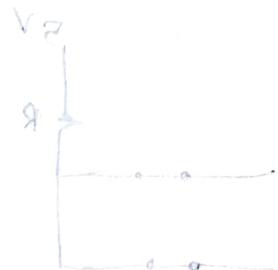

$$(f_{\text{out}})_{\text{max}} = 1.0V$$

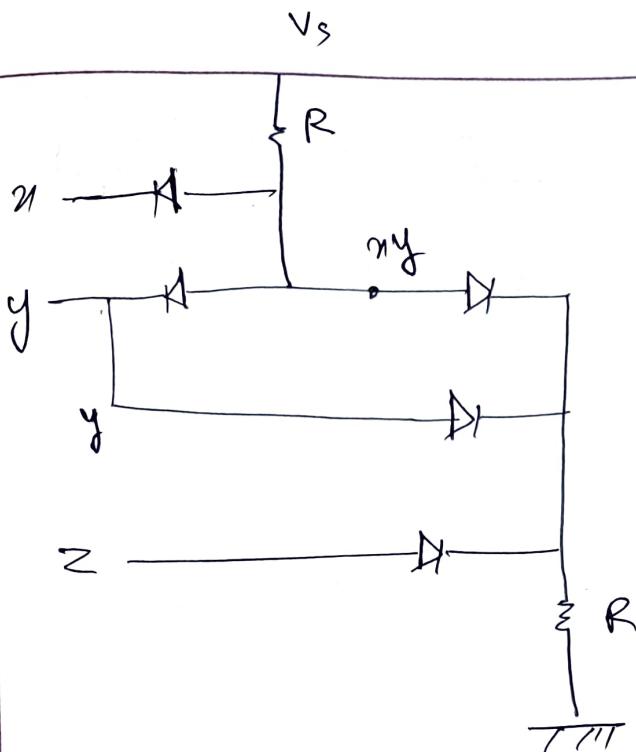

$$\begin{aligned}
 f &= x'y + y + z \\
 &= y(x+1) + z \\
 &= y + z
 \end{aligned}$$

Ans

Quiz 2

আজকের প্রতি ~~ব্যবহার~~ \rightarrow ~~বিদেশ~~

① IV characteristic

② Diode


07 July

02.07.24


Half

Rectifier works as a half-bridge



AC to DC conversion

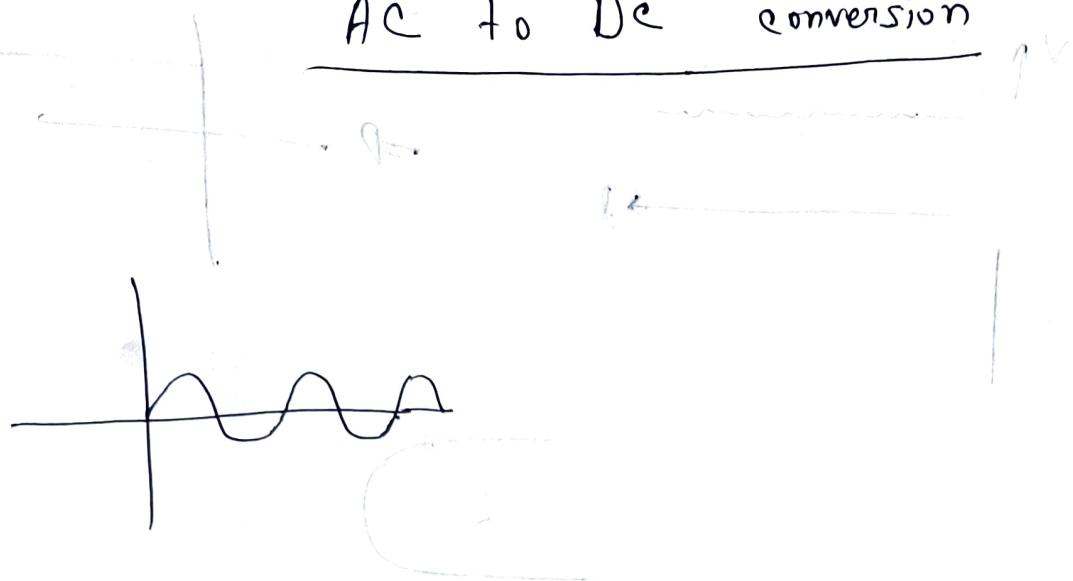

Rectification

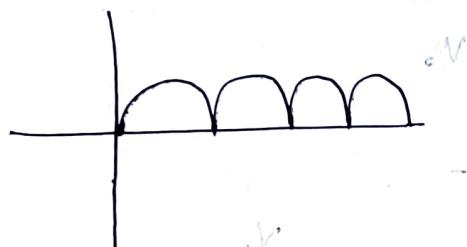

Filtering

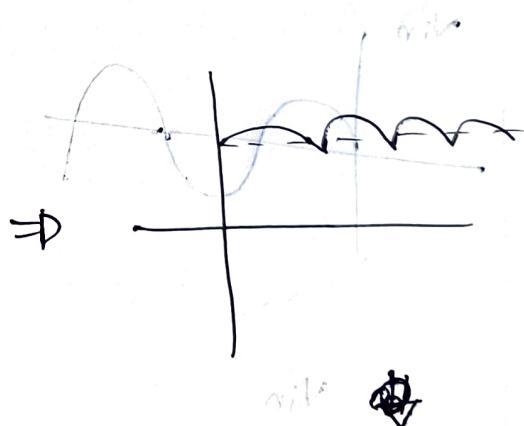
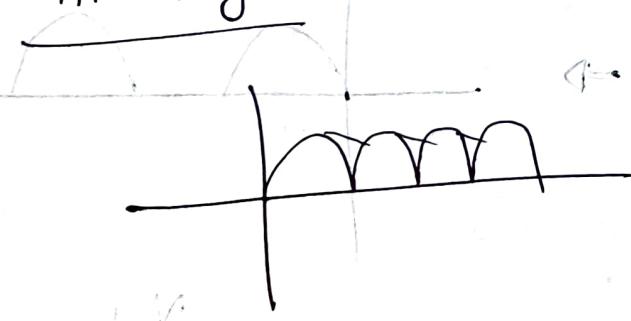


Half-bridge rectifier


AC to DC conversion

40-50-10



regulation \Rightarrow zener diode foot

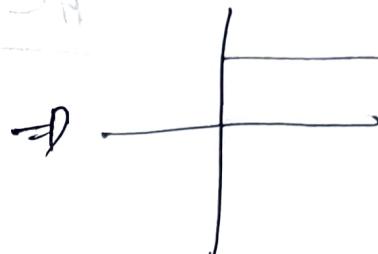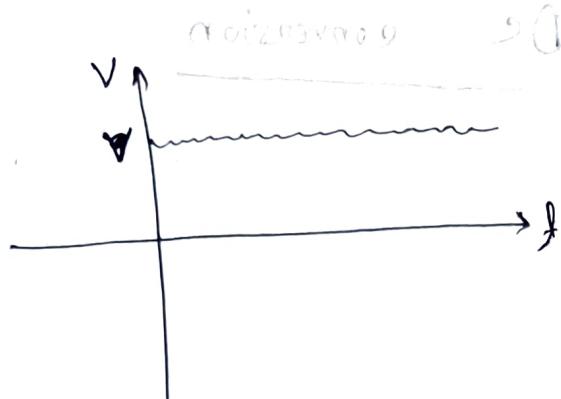

Ideal diode

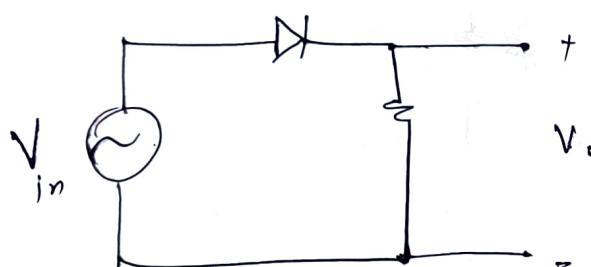

mitpositifog8

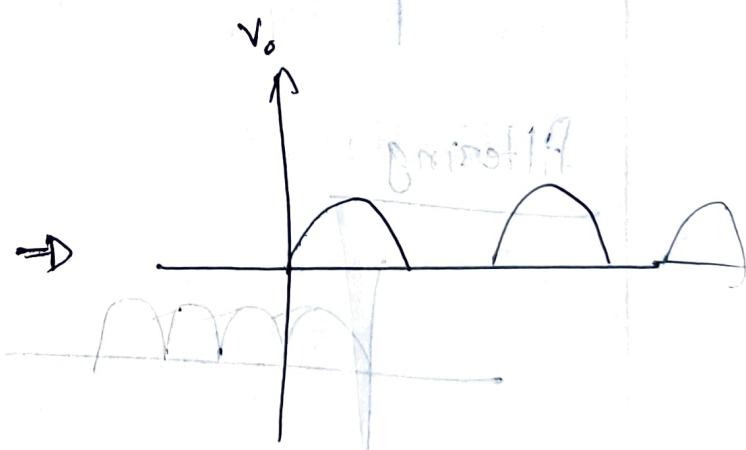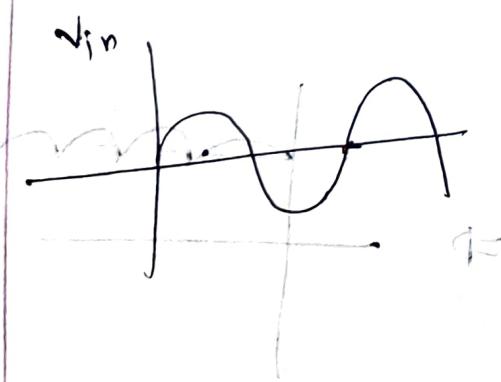


V_{in}

V_{out}


$V_{in} > 0$ und $V_{in} = V_{out}$

$V_{in} < 0$ \Rightarrow $V_{out} = 0$


ON

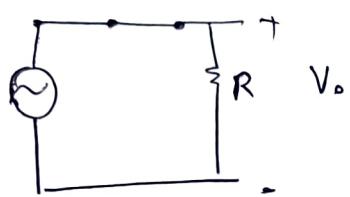


OFF

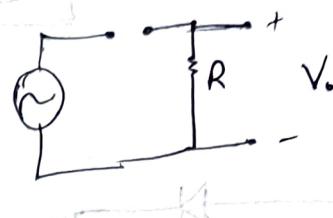


► Transfer characteristics

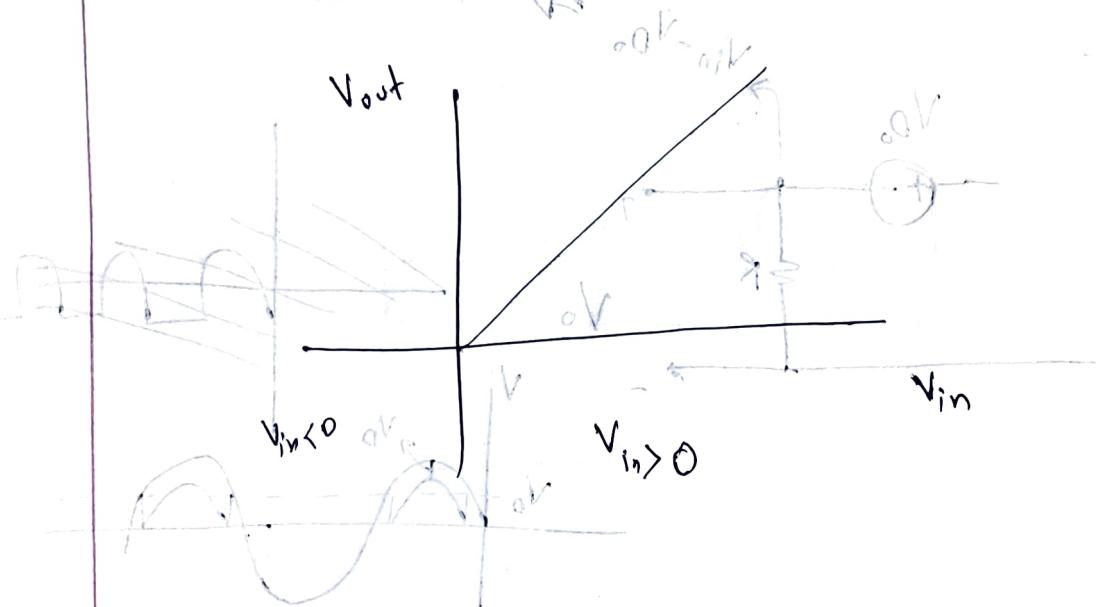

Voltage of Diode

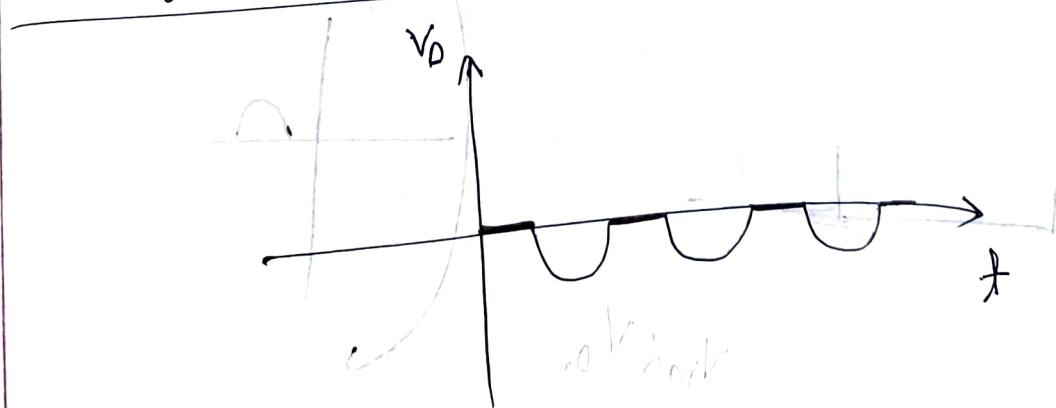


CVD diode

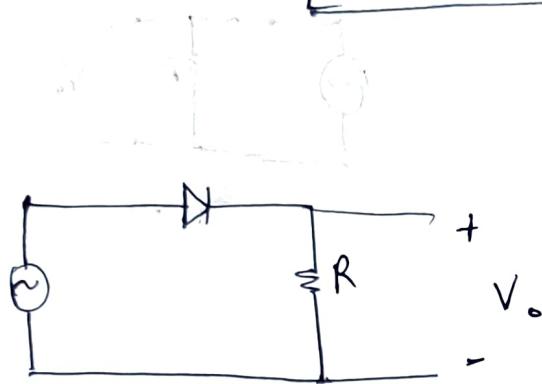

With this observation $\Rightarrow V_{in} > V_{D_0}$

Diode ON

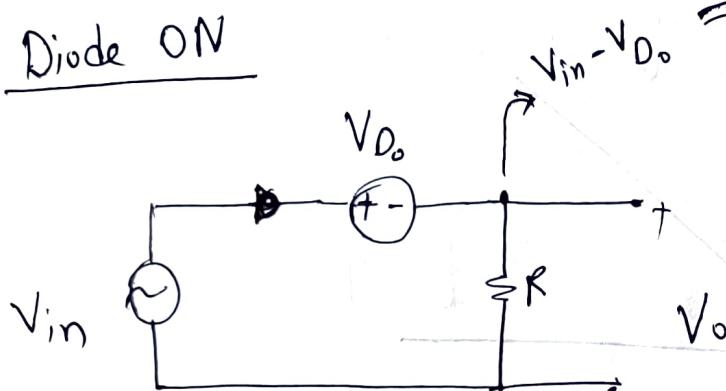

$V_{in} - V_{D_0}$

V_o

V_o


V

V

V_{D_0}

V

Diode OFF

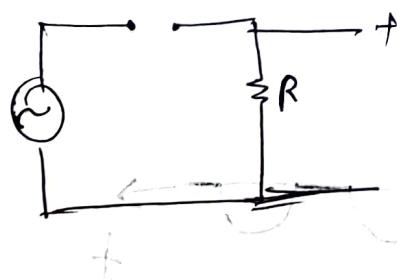

$V_{in} < V_{D_0}$


obtaining the graph

V_{avg}

$$\therefore V_{avg} = \frac{1}{T} \int_0^T V_o dt$$


$$(V_{max} \text{ of } V_o) = \frac{V_m}{2} - \frac{V_{D_0}}{2}$$

Transistor Characteristics

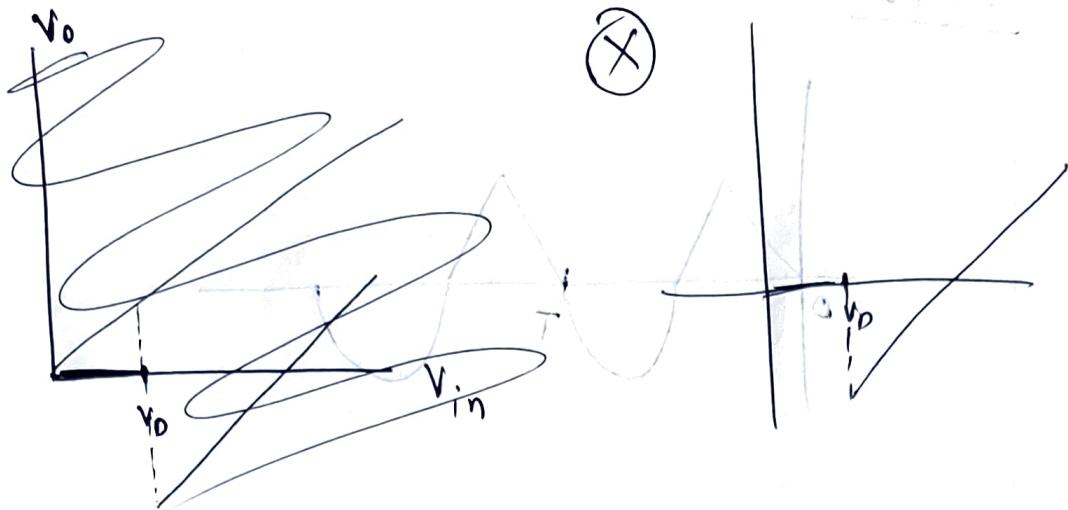


$$V_{out} = V_{in} - V_o$$

$$\Rightarrow y = x - c$$

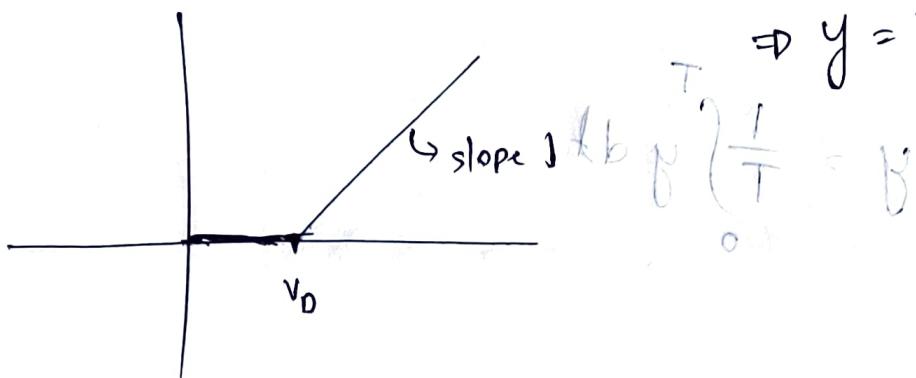

Example

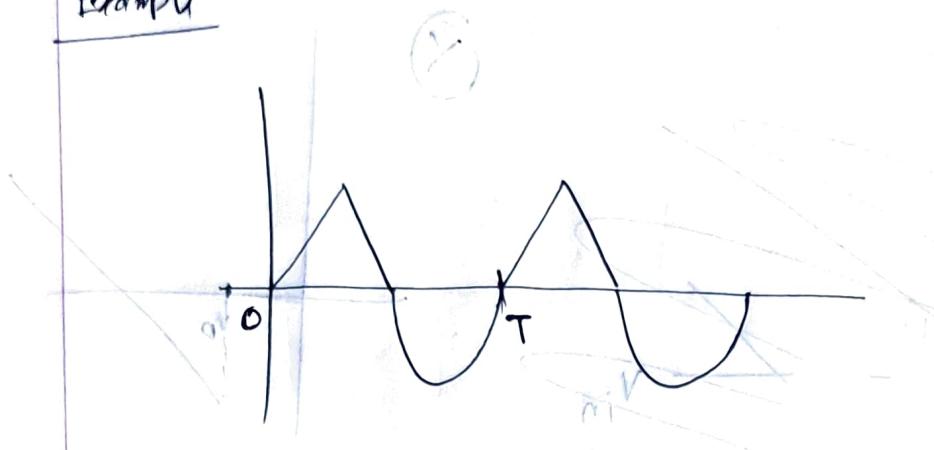


average value of $y = ?$

$$y = \bar{y} = \int_0^T y dt$$

$$y = \frac{1}{T} \int_0^T y dt$$


Full-wave rectifier

(CVD mod)

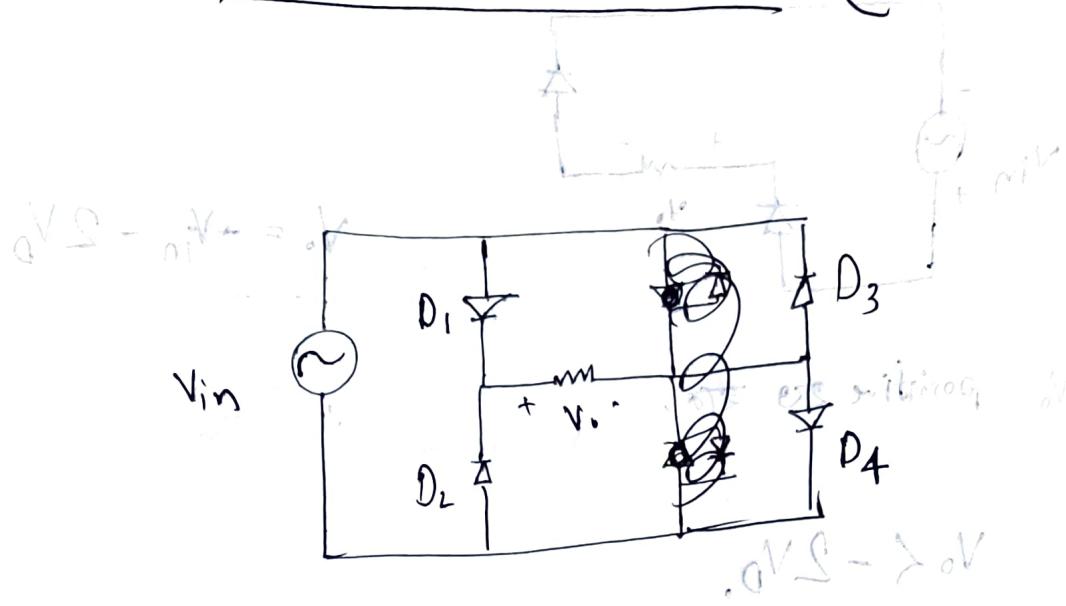

Positive Half cycle


$$0V < nV < 0V$$

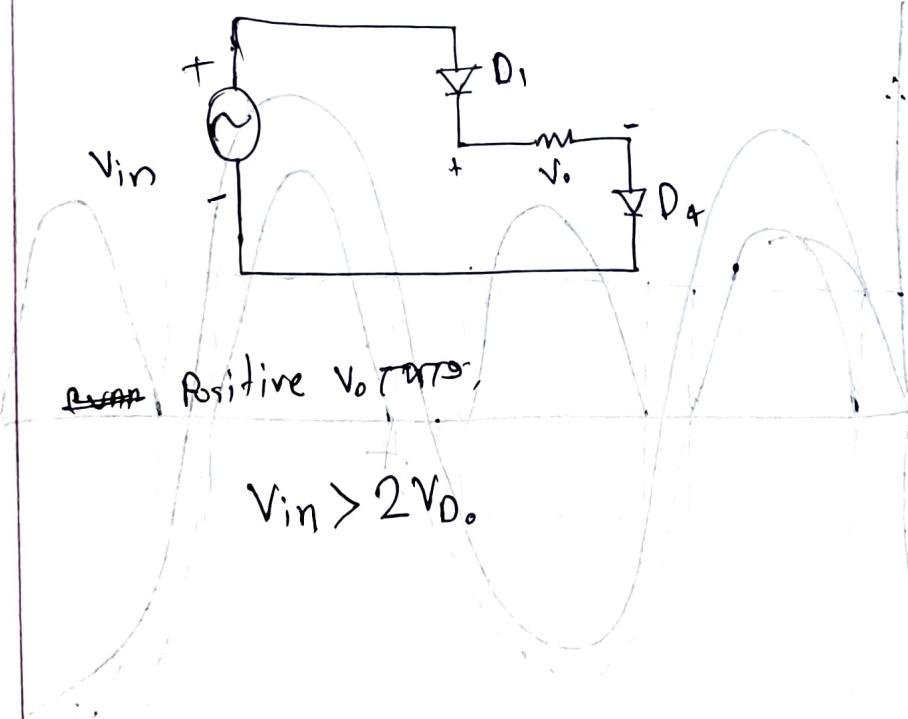

$$\therefore V_0 = V_{in} - V_{D1} - V_{D4}$$

$$\Rightarrow V_0 = V_{in} - 2V_D$$

(Working region) Amplifier circuit (b)

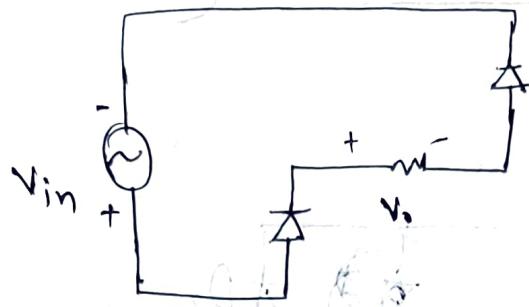


$$V_o = -V_{in} - 2V_D$$

V_o positive $2V_D$ $2V_D$



$$V_o < -2V_D$$

$$\therefore -2V_D < V_{in} < 2V_D$$

float voltage
at 0

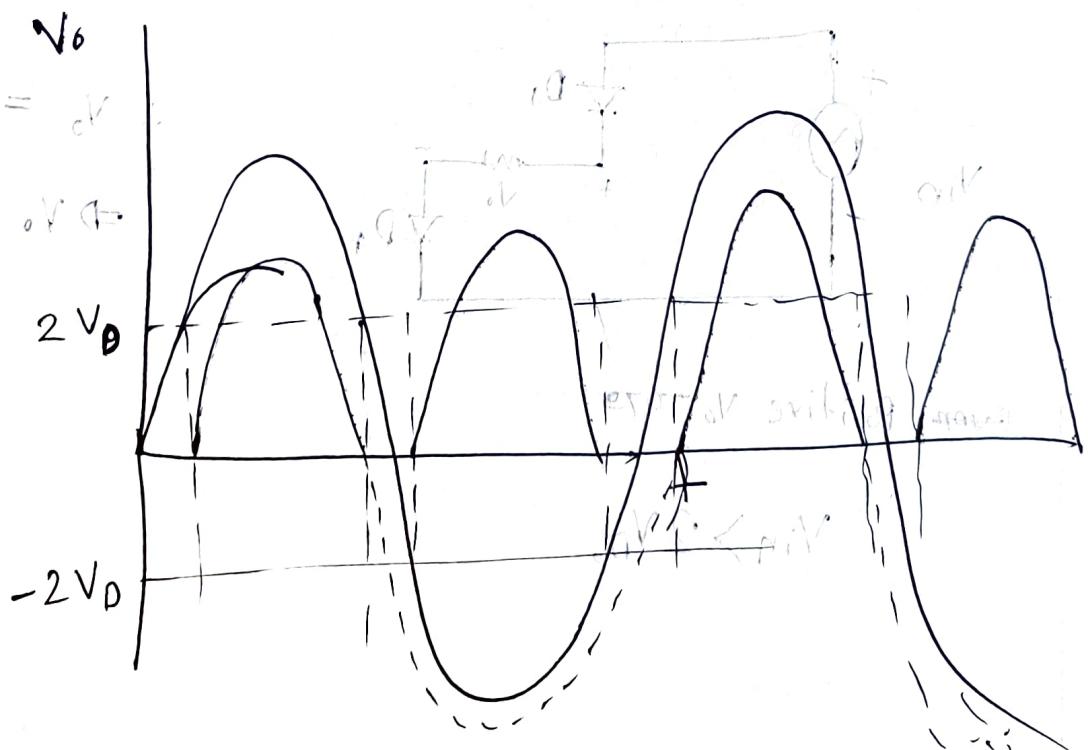

Transfer characteristic graph

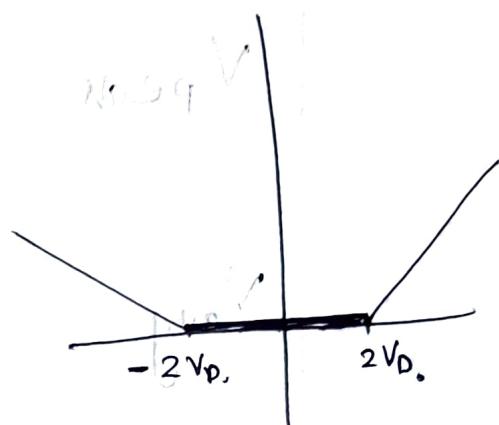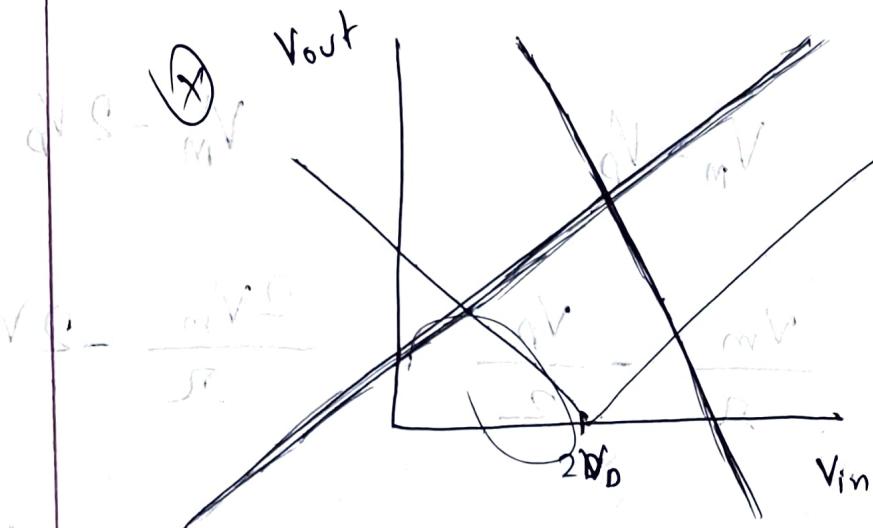

$$V_{out} = V_{in} - 2V_D$$

$$\Rightarrow y = x - c$$

$$V_{out} = -V_{in} - 2V_D$$

$$\Rightarrow y = -mx - c$$

average value

$$V_{avg} = \frac{1}{T} \int_0^T V_o dt = \frac{2V_m}{\pi} - 2V_D$$

Half-wave Full-wave

V_{peak}

V_{avg}

$V_m - V_p$



$V_m - 2V_p$

$$\frac{V_m}{2} - \frac{V_p}{2}$$



$$\frac{2V_m}{2} - 2V_p$$

~~2010.07.24~~

Practice for Quiz 2

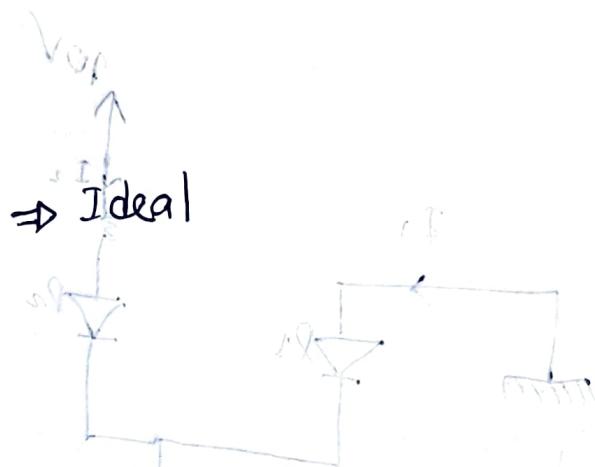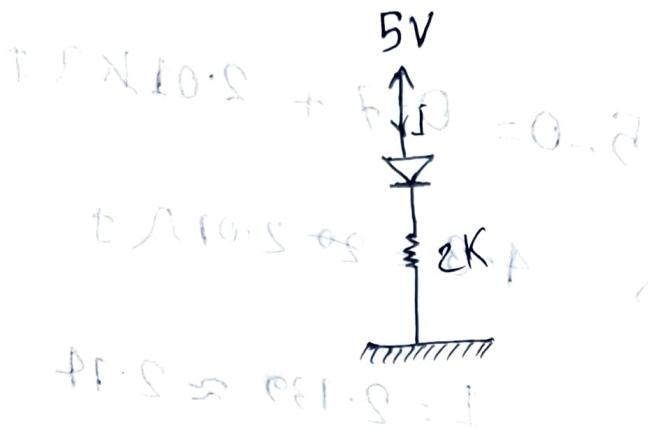

$$\therefore 5 - 0 = 2^1 \text{ nos}$$

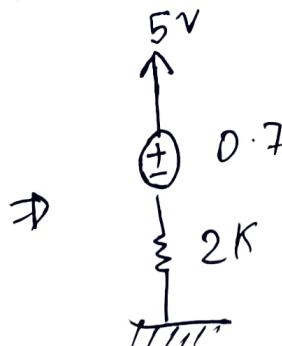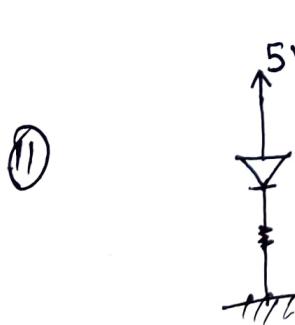

$$\Rightarrow 5 - 0 = 0.7 + 2I$$



$$\Rightarrow 4.3 = 2I$$

$$\Rightarrow I = 2.15 \text{ mA}$$


Seite 12 2016-2017

$\frac{10}{1000}$
0.01

⑩

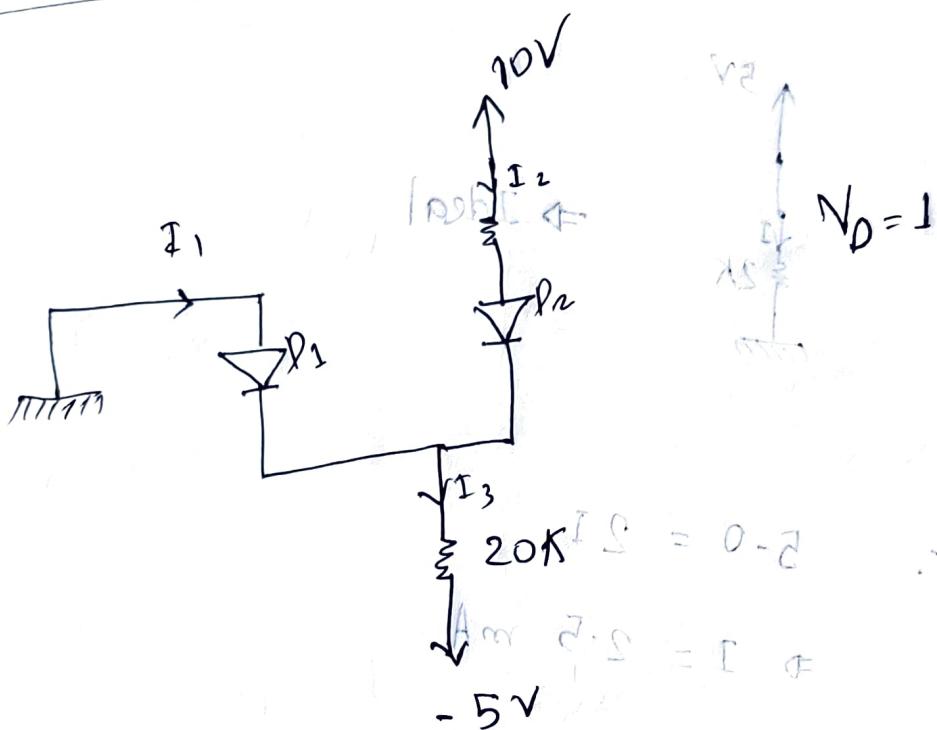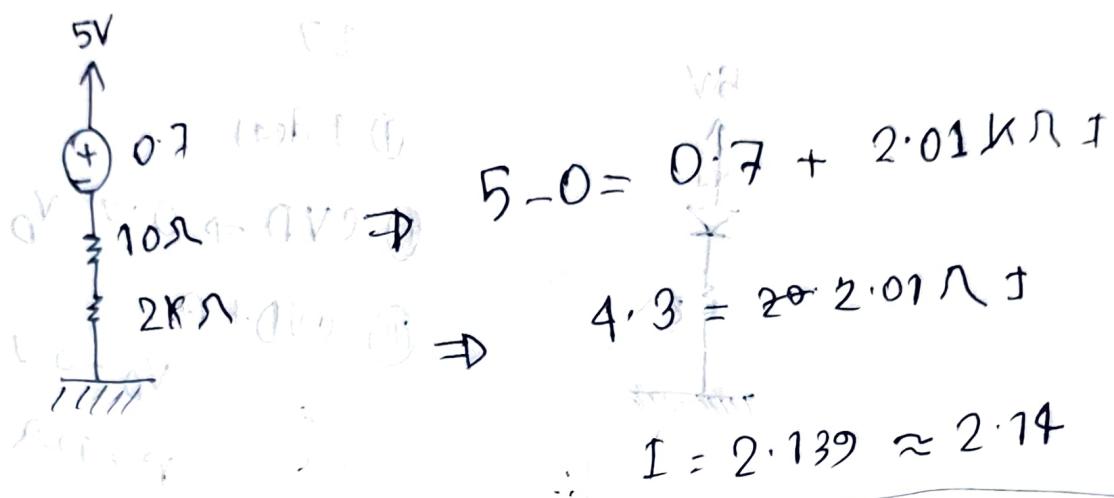

I₁ = ? = 0.01
I₂ = ?
I₃ = ?

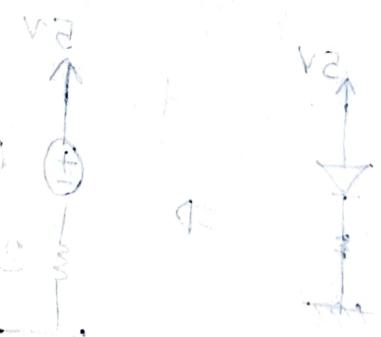


⑫

Let's assume that

$$D_1 = \text{ON}$$

$$D_2 = \text{ON}$$

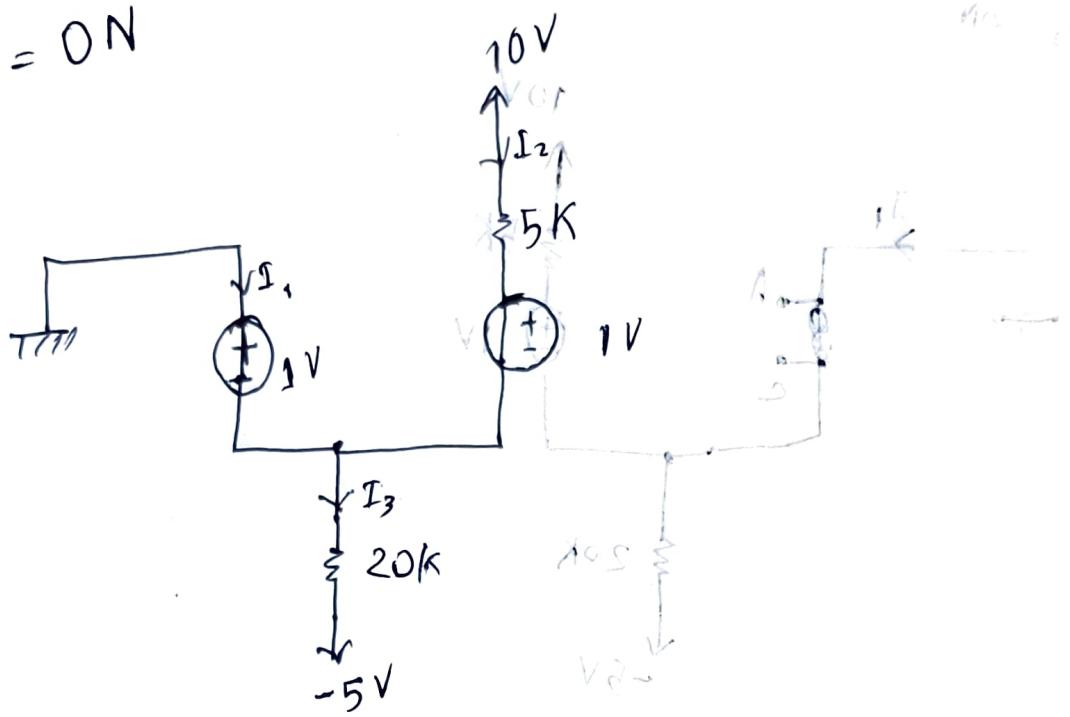

$$10 - (-5) = 5I_2 + 1 + 20I_3$$

$$0 = I$$

$$5I_2 + 20I_3 = 14 \quad \text{--- (1)}$$

$$\Rightarrow 5I_2 + 1 + 20I_3 = 14 \quad \cancel{5} \quad \cancel{5} \quad \cancel{5} \quad \cancel{5}$$

$$0 - (-5) = 1 + 20I_3 \quad I_1 = 2 \text{ mA}$$

$$\Rightarrow I_3 = 0.2 \text{ mA}$$

$$I_1 + I_2 - I_3 = 0 \quad \text{--- (2)}$$

$$\Rightarrow I_1 = I_2 - I_3$$
$$I_1 = 0.2 - 2 = -1.8 \text{ mA}$$


$D_1 = \text{OFF}$

$D_2 = \text{ON}$

left common rail

$u_0 = 10$

$u_0 = 0$

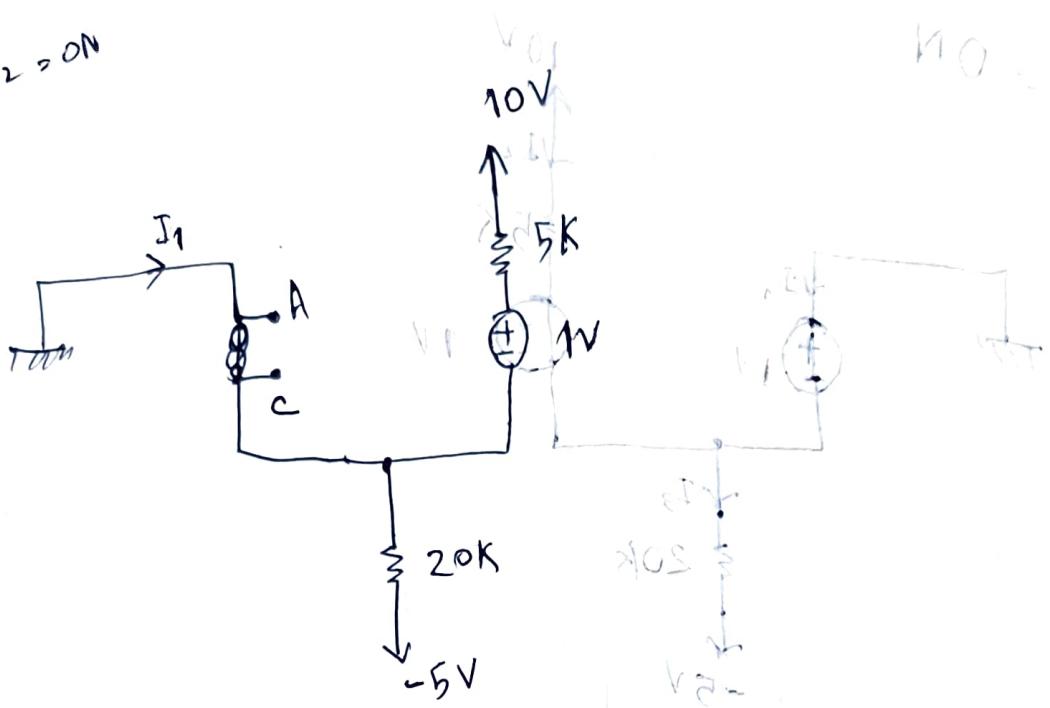

$$I_1 = 0$$

$$e^{10.5} + 1 + 20I_3 = (2) - 0 \Rightarrow$$

$$10 + 5 = 5I_2 + 1 + 20I_3$$


$$\Rightarrow 5I_2 + 20I_3 = 14 = (2) - 0$$

$$25I_2 = 14$$

$$25I_2 = 14$$

$$\Rightarrow I_2 = 0.56 > 0$$

$$\text{for } I_1 = -2 - 5.0 = 2$$

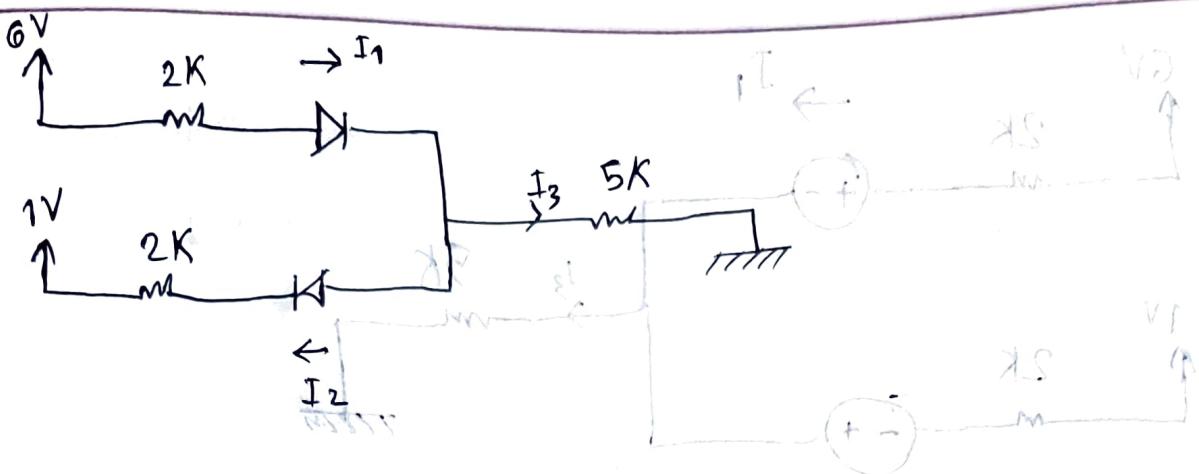

$$D_1 = 0.7V$$

$$D_2 = \text{OFF}$$

$$6 - 0 = 2I_1 + 1 \quad \text{and} \quad 6 - 0 = 2I_1 + 1 + 2I_3 \quad \text{and} \quad 6 - 0 = 2I_1 + 5I_3$$

$$2I_1 + 5I_3 = 6 \quad \text{and} \quad 2I_1 + 5I_3 = 6$$

$$2I_1 + 5I_3 = 6 \quad \text{and} \quad 2I_1 + 5I_3 > 6$$

$$f = 0 = -2I_2 - 1 + 5I_3$$

$$\Rightarrow -27_2 + 57_3 = 2$$

$$I_2 = 0$$


Q \leftarrow \varnothing : f \rightarrow I

$$\frac{\sqrt{A} - 0}{0} = 0.71$$

52.0

$$I_1 = I_2 + I_3$$

$$\uparrow = \uparrow 3$$

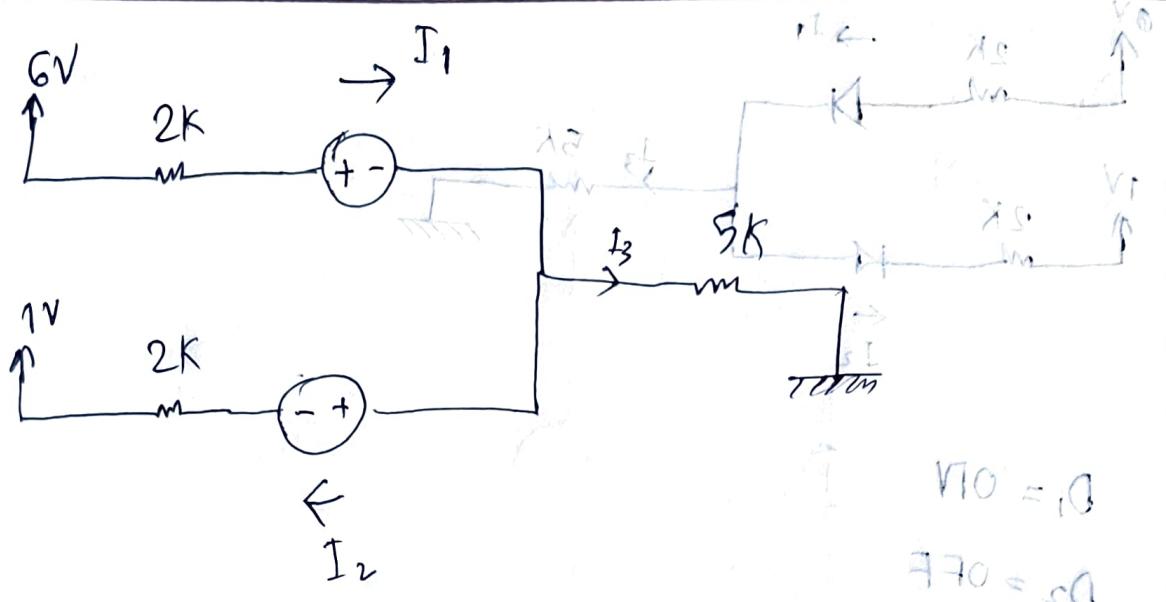

$$\begin{aligned}
 \text{MG} & \quad 6-0 = 2I_1 + 1 + 5I_3 \quad | \quad 1-0 = -2I_2 - 1 + 5I_3 \\
 \text{MG} & \quad 2I_1 + 5I_3 = 5 \quad | \quad -2I_2 + 5I_3 = 2 \\
 \text{MG} & \quad 2I_1 + 5I_3 = 5 \quad | \quad -2I_2 + 5I_3 = 2
 \end{aligned}$$

$$I_1 - I_2 - I_3 = 0$$

assumption verified.

$$0 = gI$$

$$I_1 = 1.04 > 0$$


$$I_2 = 0.45 > 0$$

$$I_3 = 0.58$$


$$g + gI = gI$$

$$gI = 1$$


OR

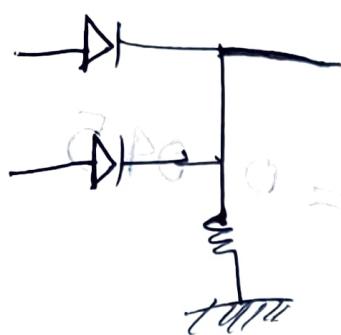

AN

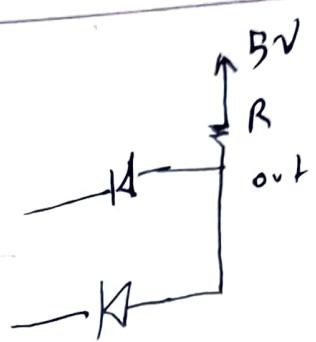

$$f = xy + y + z$$

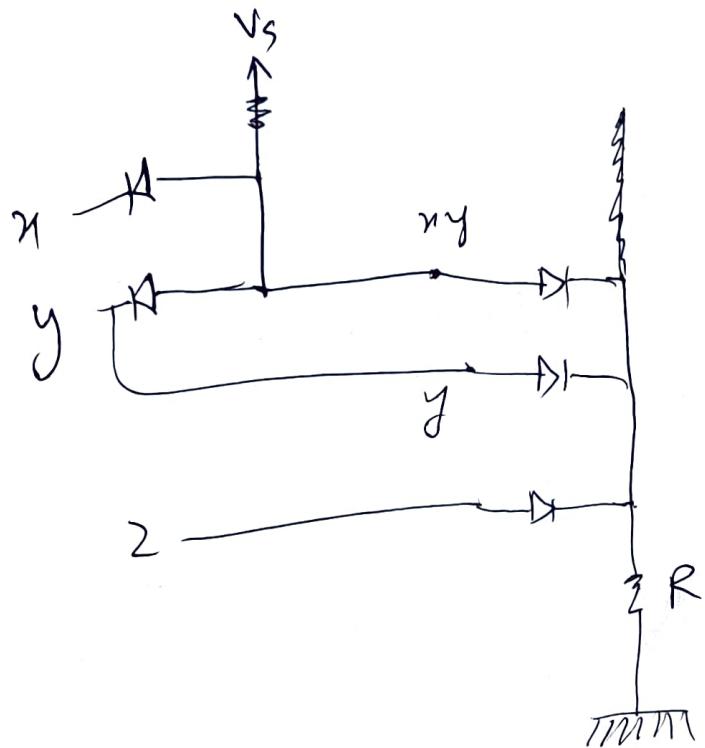

$$x + y + z$$

