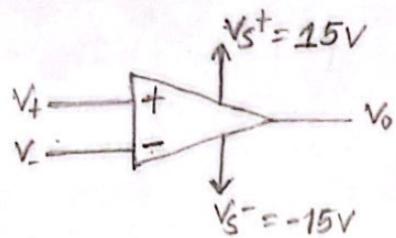


OP-Amp

Q-1





$$\textcircled{i} \quad V_d = V_+ - V_- = (10 \times 10^{-6}) - (5 \times 10^{-6}) \\ = 5 \times 10^{-6} \text{ V}$$

$$\therefore V_o = AV_d = 2105 \times 5 \times 10^{-6} \\ = 0.012 \text{ V} \quad (\text{Ans})$$


$$\textcircled{ii} \quad V_d = V_+ - V_- = (10 \times 10^{-3}) - (0.2 \times 10^{-3}) \\ = 8 \times 10^{-4} \text{ V}$$

$$\therefore V_o = AV_d = 2105 \times 8 \times 10^{-4} \\ = 1.684 \text{ V} \quad (\text{Ans})$$

Q-2

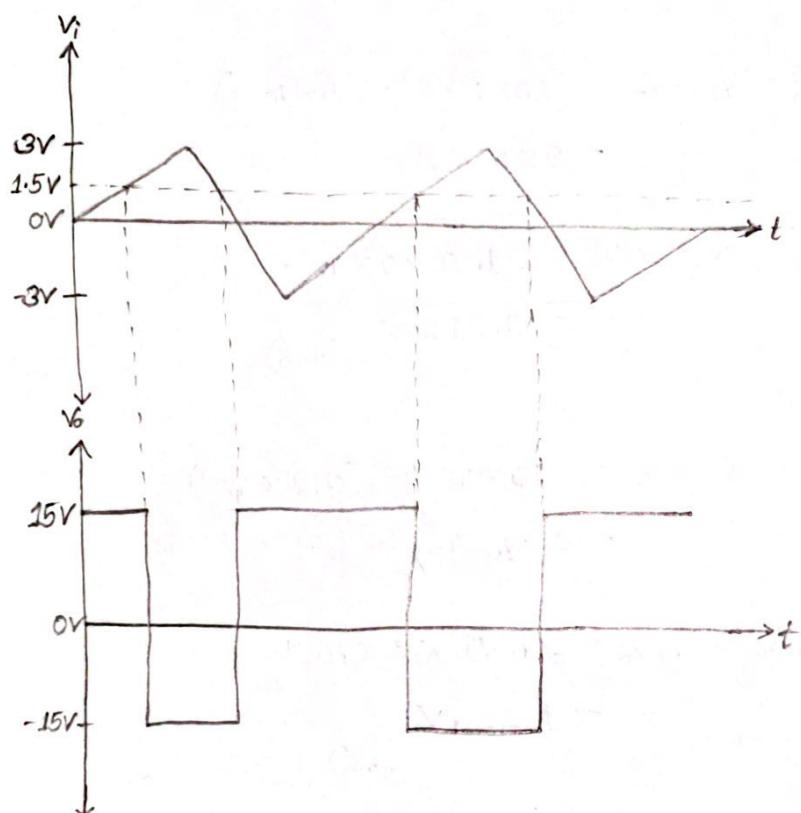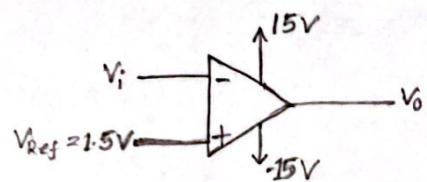

Q-3

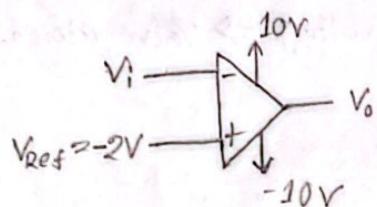

Q-5

i) Hence,

$$\begin{aligned} p &= h \rho g \\ &= 10 \times 1000 \times 9.8 \\ &\approx 98000 \text{ Pa} \end{aligned}$$

In atm,

$$\frac{98000}{101325}$$

$$\approx 0.967 \text{ atm}$$

Voltage difference,

for 1 atm pressure change ΔV is $2.5 \times \frac{2.5}{0.5} V$

$$\therefore n (0.967 - 0.5) \text{ atm} \quad n \quad n \quad n \quad \frac{2.5 \times (0.967 - 0.5)}{0.5}$$


$$= 2.335 V$$

$$\therefore \text{Voltage at } 0.967 \text{ atm} = (2.335 + 0.5) V$$


$$= 2.835 V$$

High pressure \Rightarrow High input voltage \Rightarrow Valve open, $V_{S^+} = 1V$

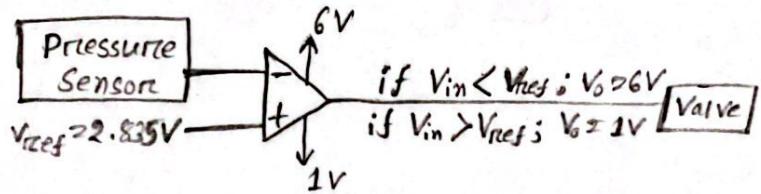Low pressure \Rightarrow Low input voltage \Rightarrow Valve closed, $V_{S^+} = 6V$



(ii)

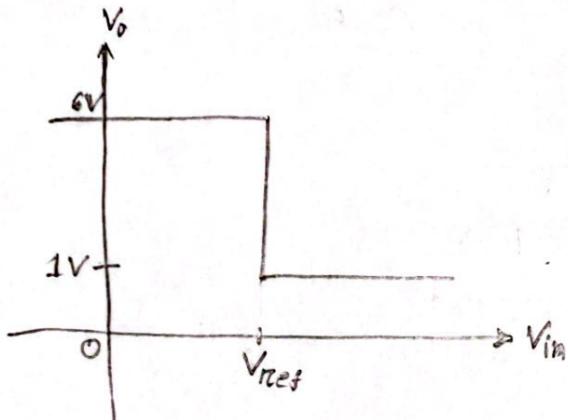

Q-6

(i) We know,

$$V_o = AV_f$$

$$\Rightarrow V_d = \frac{V_o}{A}$$

$$\Rightarrow V_d = \frac{V_o}{\infty}$$

$$\Rightarrow V_+ - V_- = 0$$

$$\therefore V_+ = V_-$$


As, $V_+ = 0V$ (Grounded)

$$\therefore V_- = 0V$$

This is called virtual ground

(Ans)

(ii)

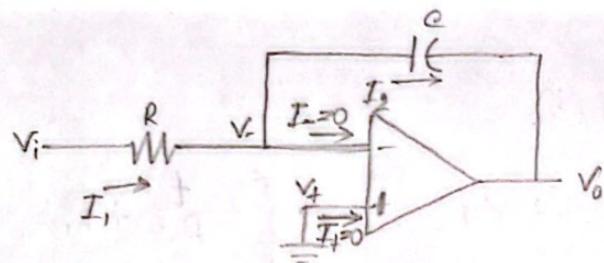

Hence,

$$I_+ = I_- = 0$$

$$\therefore I_1 = I_2$$

$$\Rightarrow \frac{V_i - V_+}{R} = C \frac{d(V_- - V_o)}{dt}$$

$$\Rightarrow \frac{V_i}{R} = -C \frac{dV_o}{dt} \quad [\because V_- = 0V]$$

(Ans)

(iii)

That's an integrator circuit.

$$\therefore I_+ = I_- = 0$$

$$\therefore I_1 = I_2$$

$$\Rightarrow \frac{V_i - V_+}{R} = C \cdot \frac{d(V_- - V_o)}{dt}$$

$$\Rightarrow \frac{V_i}{R} = -C \frac{dV_o}{dt} \quad [\because V_- = 0V]$$

$$\Rightarrow \frac{d}{dt} V_o = -\frac{V_i}{RC}$$

$$\Rightarrow V_o = - \int \frac{V_i}{RC} dt$$

$$\therefore V_o = -\frac{1}{RC} \int V_i dt$$

~~(Ans)~~

From Fig. 1(b),

$$v_i = \begin{cases} 1, & 0 \leq t < 1 \\ -1, & 1 \leq t < 2 \\ 1, & 2 \leq t < 3 \\ -1, & 3 \leq t < 4 \end{cases}$$

$$v_o = \begin{cases} -\frac{t}{RC} + k_1, & 0 \leq t < 1 \\ -\frac{t}{RC} + k_2, & 1 \leq t < 2 \\ -\frac{t}{RC} + k_3, & 2 \leq t < 3 \\ \frac{t}{RC} + k_4, & 3 \leq t < 4 \end{cases}; \quad [k's \text{ are constant}]$$

(iv) Hence,

$$R \approx 10k\Omega$$

$$C \approx 0.1 \mu F$$


$$t = 1ms$$

$$\therefore v_o = \frac{-1 \times 10^{-3}}{10 \times 10^3 \times 0.1 \times 10^{-6}} + k_1$$

$$= -1 + k_1 \quad (\text{Ans})$$

$$(v) f = \frac{1}{4}x + 7y - \frac{d}{dt}(z)$$
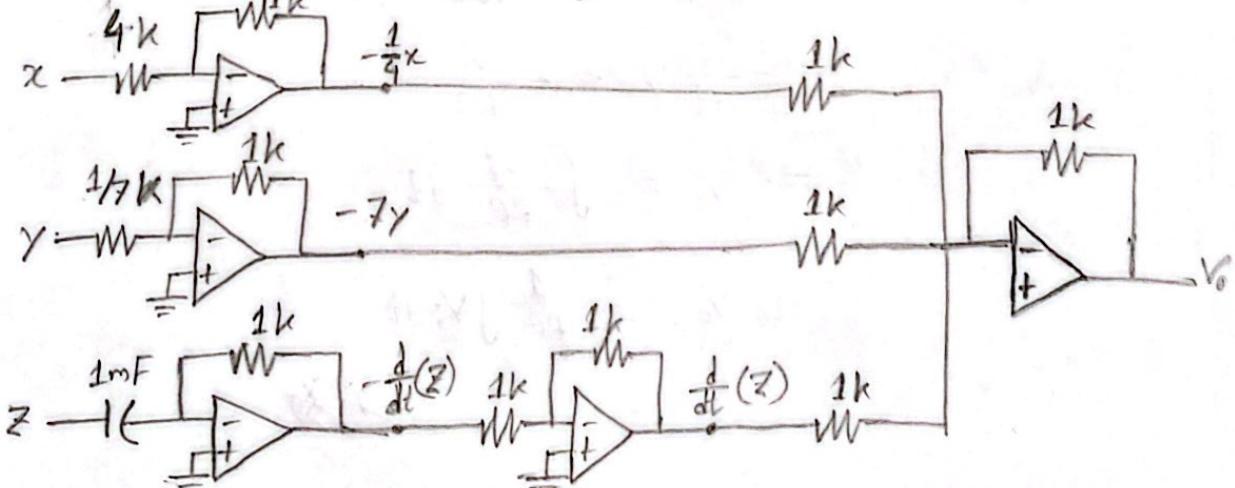
$$= -\left(\frac{1}{4}x - 7y + \frac{d}{dt}(z)\right)$$



$$\therefore v_o = -\left(-\frac{1}{4}x\right) - (-7y) - \frac{d}{dt}z$$

$$= \frac{1}{4}x + 7y - \frac{d}{dt}z \quad (\text{Ans})$$

Q-7

(a) We know,

$$V_o = A V_d$$

$$\Rightarrow V_d = \frac{V_o}{A}$$

$$\Rightarrow V_d = \frac{V_o}{\infty}$$

$$\Rightarrow V_+ - V_- = 0$$

$$\therefore V_+ = V_-$$

As, $V_+ = 0V$

$$\therefore V_- = 0V$$

(Ans)

(b) Hence, $I_+ = I_- = 0$

$$\therefore i_2 = i_D$$

From the circuit,

$$i_2 = -\frac{V_o}{R}$$


$$i_D = I_s e^{\frac{V_o}{V_T}}$$

$$\therefore -\frac{V_o}{R} = I_s e^{\frac{V_o}{V_T}}$$

This indicates that the current through the resistor R is the same as the current through the diode, which follows an exponential relationship with the output voltage V_o .

(Ans)

③

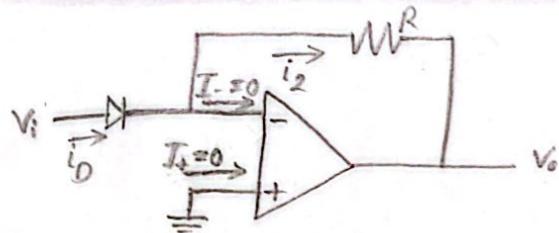

$$i_1 = i_2$$

$$\Rightarrow I_s e^{\frac{v_o}{R}} = \frac{0 - v_o}{R}$$

$$\therefore v_o = -I_s R e^{\frac{v_o}{R}}$$

(Ans)

④

Expression is not given.

Q-8

$$\textcircled{a} \quad V_{I_1} = -RC \cdot \frac{d}{dt} V_i \\ = -(1 \times 10^6 \times 1 \times 10^{-6}) \cdot \frac{d}{dt} y \\ = -\frac{d}{dt} y$$

$$V_{I_2} = -\frac{R_2}{R_1} V_i \\ = -\frac{5}{5} \left(-\frac{d}{dt} y \right) \\ = \frac{d}{dt} y$$

$$V_T = -\frac{1}{RC} \int V_i dt \\ = -\frac{1}{1 \times 10^6 \times 1 \times 10^{-6}} \int x dt \\ = -\int x dt$$

$$\therefore f = -5 \left(\frac{-\int x dt}{5} + \frac{\frac{d}{dt} y}{5} \right) \\ = \int x dt - \frac{d}{dt}(y) \\ (\text{Ans})$$

(b) We know,

$$V_o = -\frac{R_2}{R_1} V_i$$


Hence,

$$\text{Gain, } k = -\frac{R_2}{R_1}$$

$$\therefore -\frac{R_2}{R_1} = 4$$

$$\Rightarrow \frac{R_1}{R_2} = \frac{1}{4}$$


$$\therefore R_1 : R_2 = 1 : 4$$

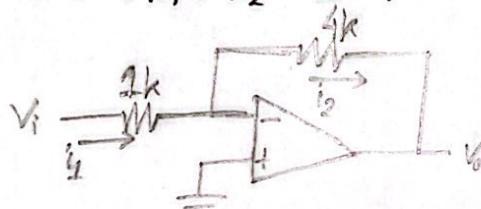

(c) Output Amplitude = |gain| \times input amplitude

$$= |-4| \times 0.5$$
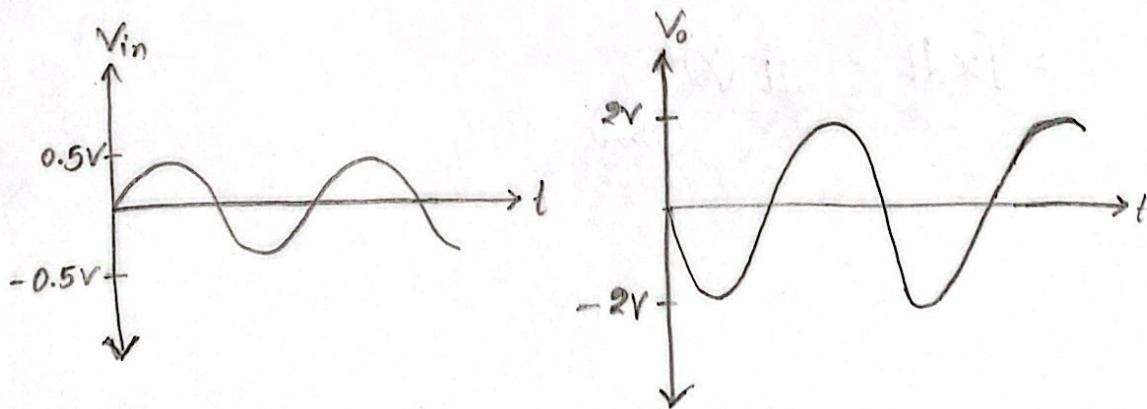
$$= 2 \text{ V } (\cancel{\text{peak-to-peak}})$$



④ Hence,

$$i_1 = 0.5 \mu A$$

$$V_{in} = 0.5 V$$

Now,

$$i_1 = \frac{V_{in} - 0}{R_1}$$

$$\Rightarrow R_1 = \frac{0.5 V}{0.5 \mu A} = \frac{0.5}{0.5 \times 10^{-6}}$$

$$\therefore R_1 = 1 \times 10^6 \Omega \\ = 1 M\Omega$$


\therefore We need to set, $R_1 = 1 M\Omega$ instead of $1 k\Omega$

$$R_2 = 4 M\Omega \quad n \quad n \quad 4 k\Omega$$


(Ans)

Q-9

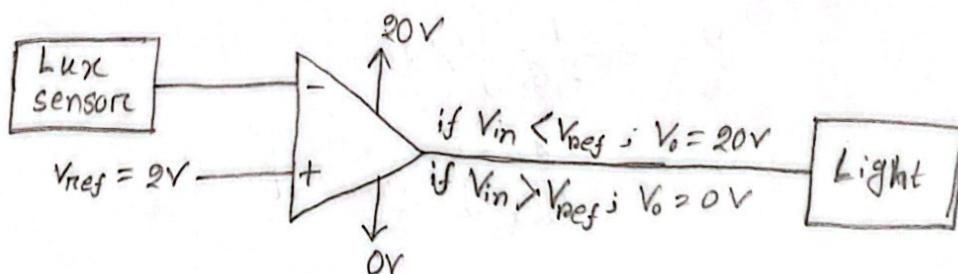- ② High brightness \Rightarrow High input voltage \Rightarrow Light OFF, $V_{S^-} = 0V$
 Low brightness \Rightarrow Low input voltage \Rightarrow Light ON, $V_{S^+} = 20V$



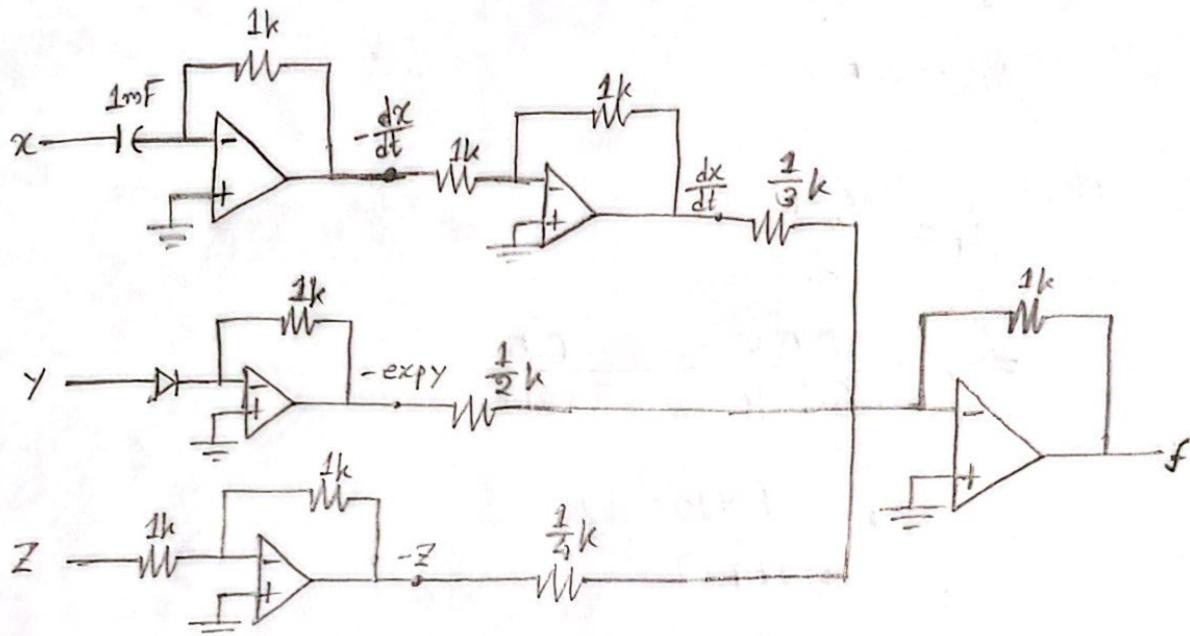
$$\textcircled{b} \quad f = -3 \frac{dx}{dt} + 2 \exp y + 4z$$



$$\therefore f = -3 \frac{dx}{dt} + 2 \exp y + 4z$$

(Ans)

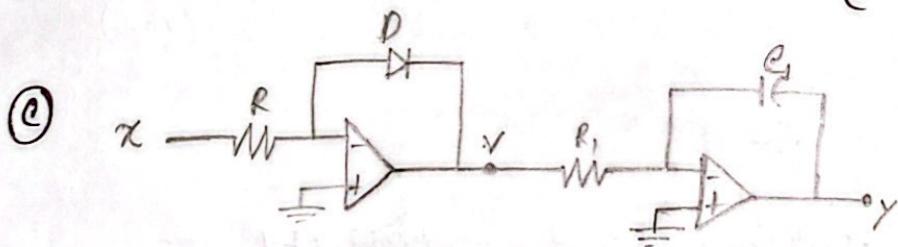


$$v = -\ln x$$

$$y = -\frac{1}{R_1 C_1} \int v dt$$

$$\Rightarrow y = -\frac{1}{R_1 C_1} \int -\ln x dt$$

$$\therefore y = \frac{1}{R_1 C_1} \int \ln x dt$$

(Ans)

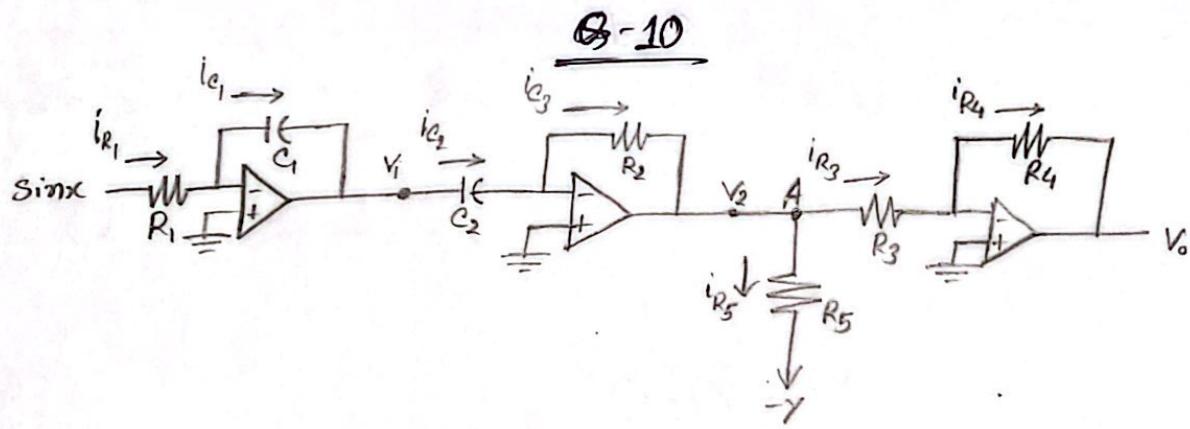

Hence,

$$V_1 = -\frac{1}{R_1 C_1} \int \sin x \, dt$$

$$V_2 = -\frac{R_2 C_2}{R_1 C_1} \cdot \frac{d}{dt} \left(-\frac{1}{R_1 C_1} \int \sin x \, dt \right)$$

$$= \sin x$$

Applying KCL at node A,

$$-i_{C_3} + i_{R_3} + i_{R_5} = 0$$

$$\Rightarrow -\frac{0 - \sin x}{R_2} + i_{R_4} + \frac{\sin x + y}{R_5} = 0 \quad [\because i_{R_3} = i_{R_4}]$$

$$\Rightarrow \frac{\sin x}{R_2} + \frac{0 - V_o}{R_4} + \frac{\sin x + y}{R_5} = 0$$


$$\Rightarrow \frac{V_o}{R_4} = \frac{\sin x}{R_2} + \frac{\sin x + y}{R_5}$$

$$\therefore V_o = \frac{R_4}{R_2} \sin x + \frac{R_4}{R_5} (\sin x + y)$$

(Ans)

Qs-11


a)

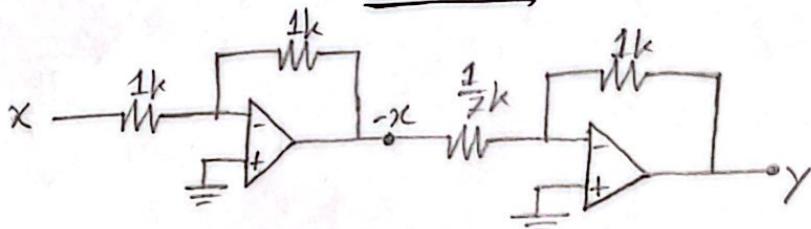

$$Y = -7(-x)$$

$$\Rightarrow Y = 7x \quad (\text{Ans})$$

b)

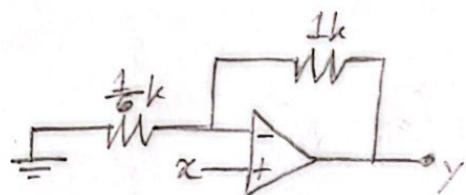

$$Y = \left(1 + \frac{1}{2k}\right)x$$

$$\Rightarrow Y = (1+6)x$$

$$\therefore Y = 7x \quad (\text{Ans})$$

Qs-12

a) We know,

$$V_o = -\frac{R_2}{R_1} V_i$$


Hence,

$$\text{Gain}_s = -\frac{R_2}{R_1}$$

$$\therefore -\frac{R_2}{R_1} = -5$$

$$\Rightarrow \frac{R_1}{R_2} = \frac{1}{5}$$

$$\therefore R_1 : R_2 = 1 : 5$$

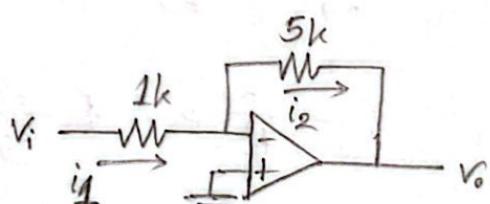

⑥ Hence,

$$I_{1\max} = 5 \text{ mA}$$

$$V_{1\max} = 0.1 \text{ V}$$

Now,

$$i_1 = \frac{V_i - 0}{R_1}$$

$$\Rightarrow R_1 = \frac{0.1 \text{ V}}{5 \text{ mA}} = \frac{0.1}{5 \times 10^{-3}} \Omega$$

$$\therefore R_1 = 20 \times 10^3 \Omega$$

$$= 20 k\Omega$$

Gain,

$$-\frac{R_2}{R_1} = -5$$

$$\Rightarrow \frac{R_2}{20} = 5$$

$$\therefore R_2 = 100 k\Omega$$

\therefore We need to set, $R_1 = 20 k\Omega$ instead of $1 k\Omega$

$$R_2 = 100 k\Omega \quad n \quad n \quad 5 k\Omega$$

(Ans)

⑦ Hence,


$$V_1 = 1 \text{ V}$$

$$V_2 = 2 \text{ V}$$

$$V_3 = 1.5 \text{ V}$$

$$R_F = R_{in}$$

Q-13

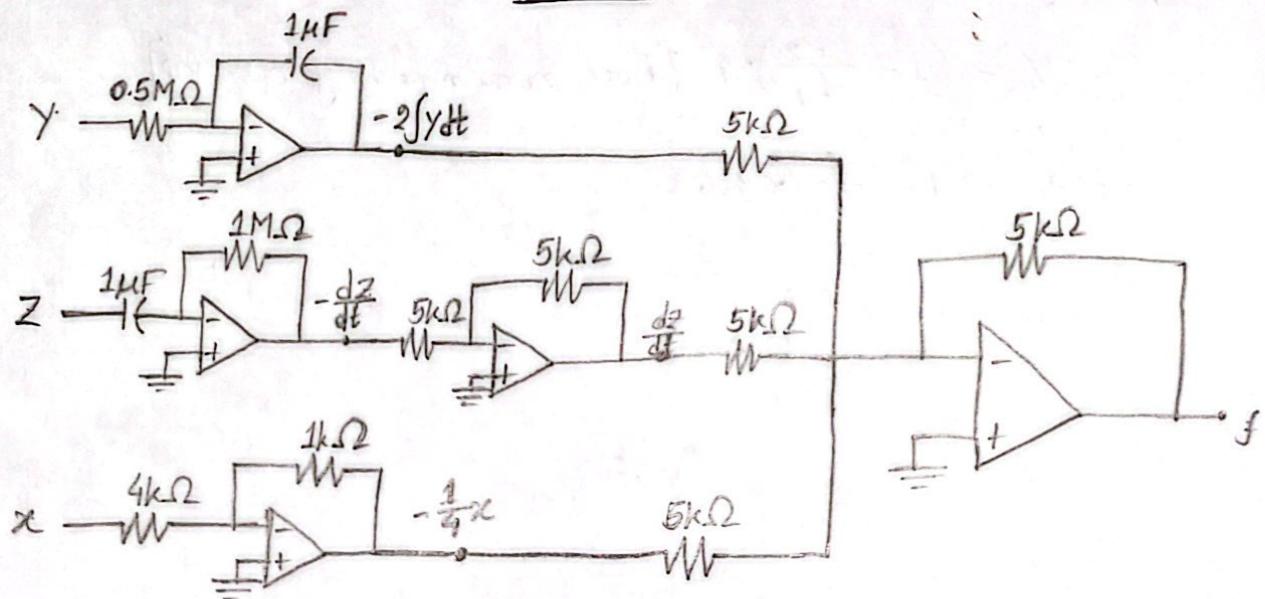


$$f = -(-2 \int y dt + \frac{d^2 z}{dt^2} - \frac{1}{4} x)$$

$$= 2 \int y dt - \frac{d^2 z}{dt^2} + \frac{1}{4} x$$

(Ans)

Q-14

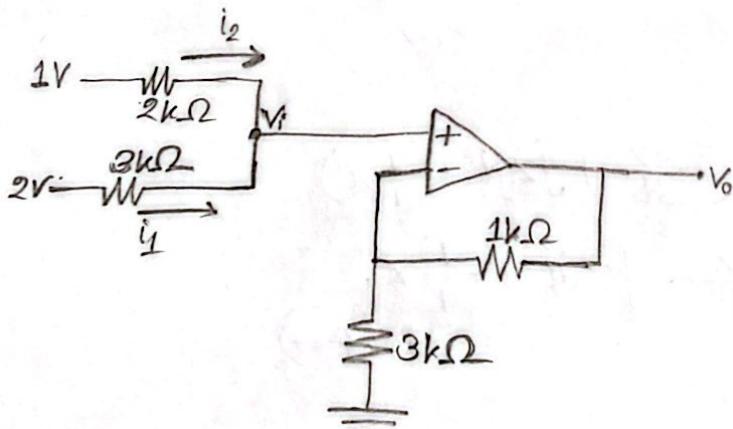

Applying KCL at node V_1 ,

$$\bullet i_1 + i_2 = 0$$

$$\Rightarrow \frac{2-V_1}{3} + \frac{1-V_1}{2} = 0$$

$$\Rightarrow \frac{4-2V_1+3-3V_1}{6} = 0$$

$$\Rightarrow 5V_1 = 7$$

$$\therefore V_1 = 1.4V$$


We know,

$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_i \quad [\text{For non-inverting op-amp}]$$

$$\Rightarrow V_o = \left(1 + \frac{1}{3}\right) \times 1.4$$

$$\therefore V_o = 1.867V \quad (\text{Ans})$$

Q-15

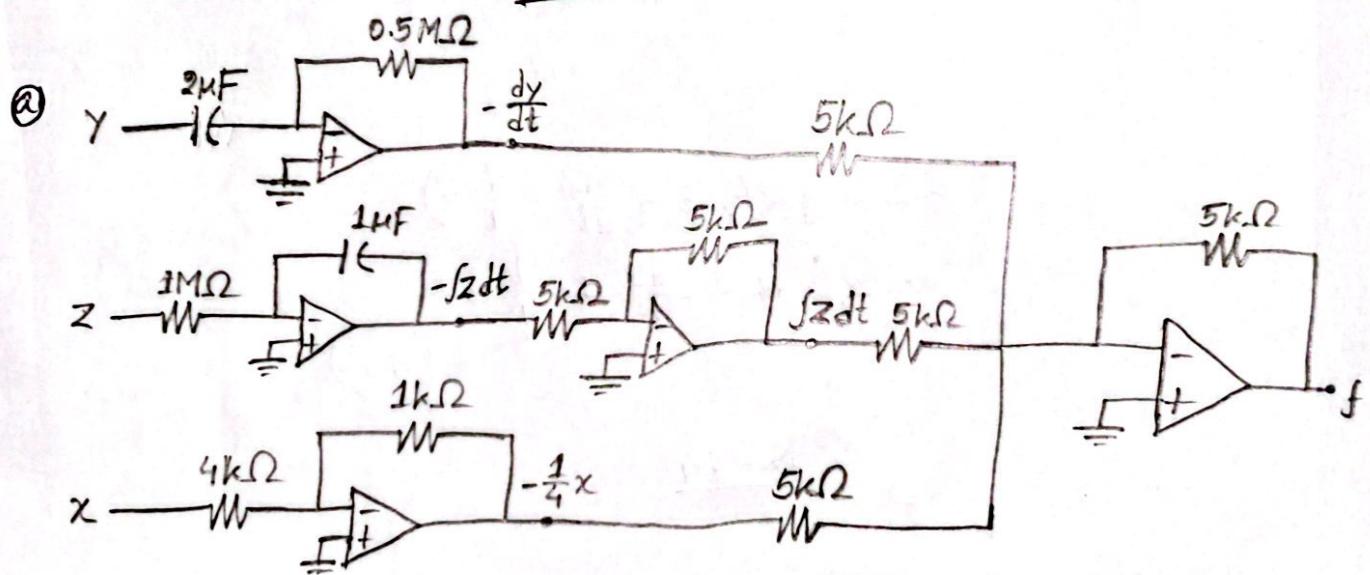

$$f = -\left(-\frac{dy}{dt} + \int z dt - \frac{1}{4}x\right)$$

$$= \frac{dy}{dt} - \int z dt + \frac{1}{4}x.$$


(Ans)

(b) We know,

$$V_o = -\frac{R_2}{R_1} \cdot V_i$$

$$\text{Hence, } \text{Gain} = -\frac{R_2}{R_1} = -4$$
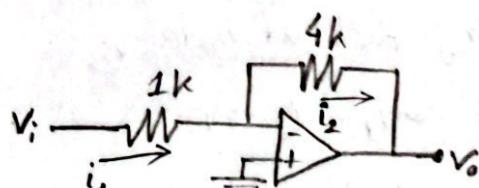
$$\Rightarrow \frac{R_1}{R_2} = \frac{1}{4}$$



$$\therefore R_1 : R_2 = 1 : 4$$


③ Assume that,

$$V_i \approx \sin t$$

Output amplitude = | gain | \times input amplitude

$$= |-4| \times 1$$

$$= 4V$$

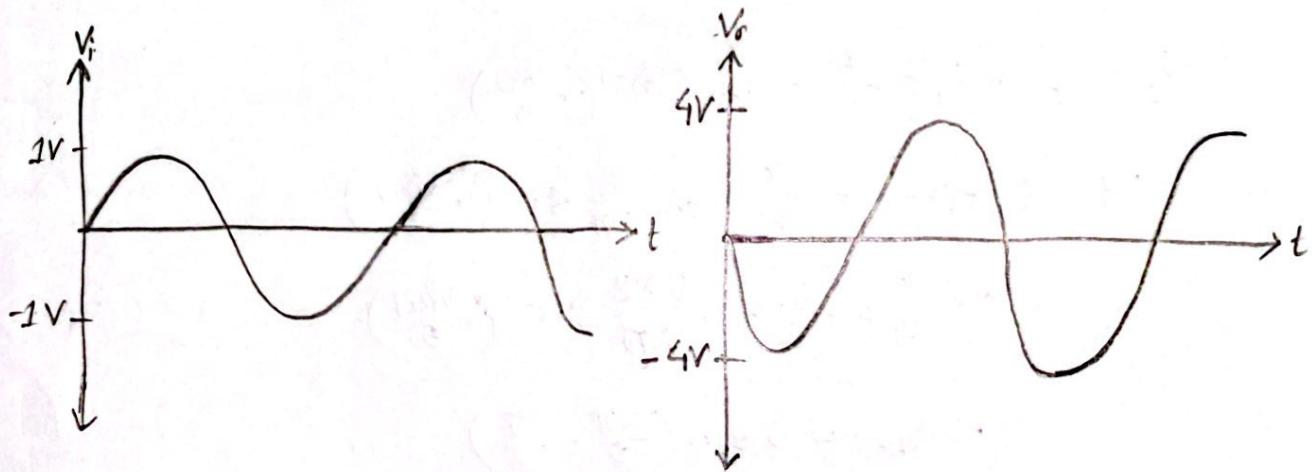

④ Hence,
 $I_{1\max} = 4 \text{ mA}$

$$V_{i\max} = 0.1V$$

$$\text{Now, } I_1 = \frac{V_i - 0}{R_1}$$

$$\Rightarrow R_1 = \frac{0.1V}{4 \text{ mA}} = \frac{0.1}{4 \times 10^{-3}}$$

$$\therefore R_1 = 25 \times 10^3 \Omega$$

$$= 25 \cancel{k\Omega} \approx 25 k\Omega$$

$$\text{Gain, } -\frac{R_2}{R_1} = -4$$

$$\Rightarrow \frac{R_2}{25} = 4$$

$$\therefore R_2 \approx 100 k\Omega$$

We need to set,

$$R_1 = 25 k\Omega \text{ instead of } 1 k\Omega$$

$$R_2 = 100 k\Omega \quad \text{u u } 4 k\Omega$$

(Ans)

Q-16

$$\text{i) } t_1 = \frac{T}{4} = \frac{5}{4} = 1.25 \text{ ms}$$

$$t_2 = \frac{3T}{4} = \frac{3 \times 5}{4} = 3.75 \text{ ms}$$

$$\text{ii) } t_1 = \frac{5}{2\pi} \sin^{-1}\left(\frac{V_{Ref}}{5}\right)$$


$$t_2 = \frac{T}{2} - t_1 = \frac{5}{2} - \frac{5}{2\pi} \sin^{-1}\left(\frac{V_{Ref}}{5}\right)$$

$$\therefore t_2 - t_1 \Rightarrow \frac{T}{4} = \frac{5}{2} - 2 \cdot \frac{5}{2\pi} \sin^{-1}\left(\frac{V_{Ref}}{5}\right)$$

$$\Rightarrow \frac{5}{4} = \frac{5}{2} - \frac{5 \times 2}{2\pi} \sin^{-1}\left(\frac{V_{Ref}}{5}\right)$$


$$\Rightarrow V_{Ref} = 5 \sin\left(\frac{2\pi}{5} \cdot \frac{5}{8}\right)$$
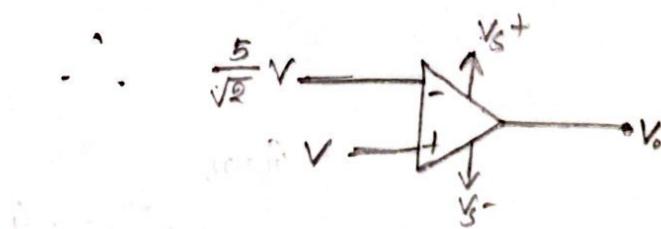
$$\therefore V_{Ref} = \frac{5}{\sqrt{2}} V$$



(Ans)

Miscellaneous

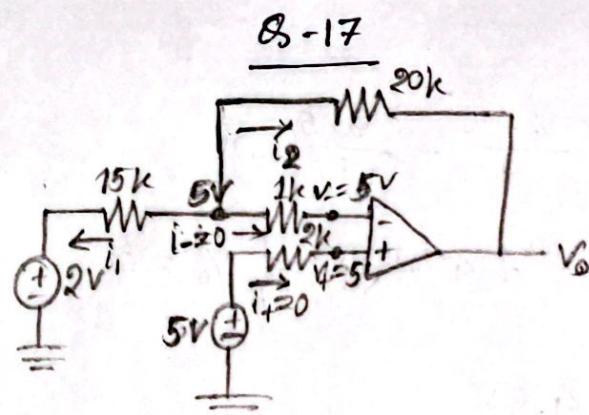

Hence,


$$i_1 + i_2 = 0$$

$$\Rightarrow \frac{5-2}{15} + \frac{5-V_o}{20} = 0$$

$$\Rightarrow \frac{5-V_o}{20} = -\frac{1}{5}$$

$$\Rightarrow 5 - V_o = -4$$
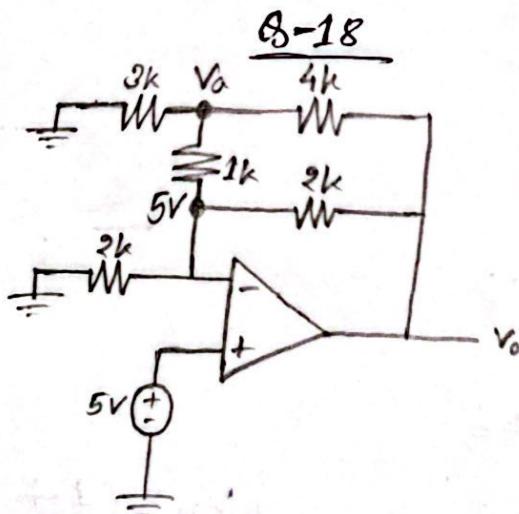
$$\therefore V_o = 9V \quad (\text{Ans})$$



KCL at V_- ,

$$\frac{5-0}{2} + \frac{5-V_o}{2} + \frac{5-V_o}{1} = 0$$

$$\Rightarrow V_o + \frac{1}{2} V_o = 10 \dots \dots \textcircled{1}$$

KCL at V_a ,

$$\frac{V_a - 0}{3} + \frac{V_a - V_o}{4} + \frac{V_a - 5}{1} = 0$$


$$\Rightarrow V_a(3^{-1} + 4^{-1} + 1) - \frac{1}{4} V_o = 0$$

$$\therefore V_a = 4.8V$$

$$V_o = 10.4V$$

(Ans)

Q-19

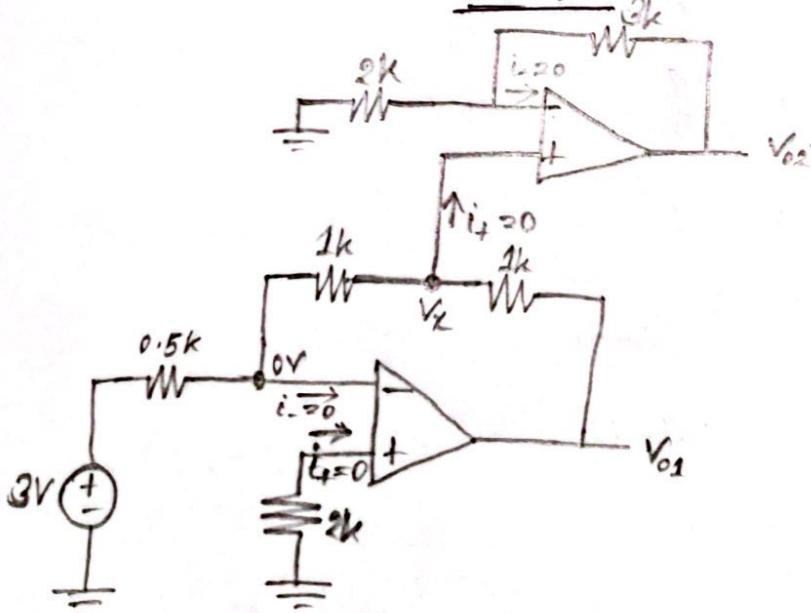

$$V_{o1} = \left(-\frac{1+1}{0.5}\right) \cdot 3$$

$$= -12V$$

(Ans)

KCL at V_x ,

$$\frac{V_x - 0}{1} + \frac{V_x + 12}{1} = 0$$

$$\Rightarrow 2V_x = -12$$

$$\therefore V_x = -6V$$


(Ans)

$$V_{o2} = \left(1 + \frac{3}{2}\right)(-6)$$

$$= -15V$$

(Ans)

Q-#20

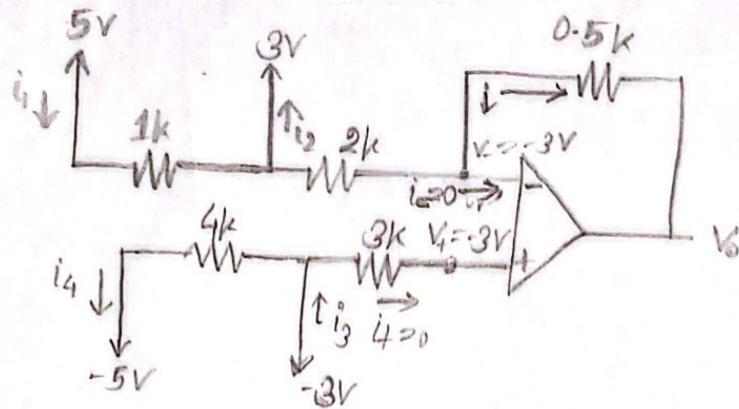

$$i_1 = \frac{5-3}{1}$$

$$= 2 \text{ mA}$$

$$i_2 = \frac{-3-3}{2} \quad i_1 - i_2 = 2 - \frac{-3+4.5}{0.5}$$

$$= -3 \text{ mA} \quad = -1 \text{ mA}$$

$$i_3 = i_4 = \frac{-3+5}{4}$$

$$= 0.5 \text{ mA}$$

(Ans)

KCL at V_- ,

$$\frac{-3-V_0}{0.5} + \frac{-3-3}{2} = 0$$

$$\Rightarrow V_0 = -4.5 \text{ V} \quad (\text{Ans})$$

~~$$i = -i_2$$~~


$$= 3 \text{ mA}$$

No w,

$$\frac{-3-V_0}{0.5} = 3$$

$$\Rightarrow -3-V_0 = 1.5$$
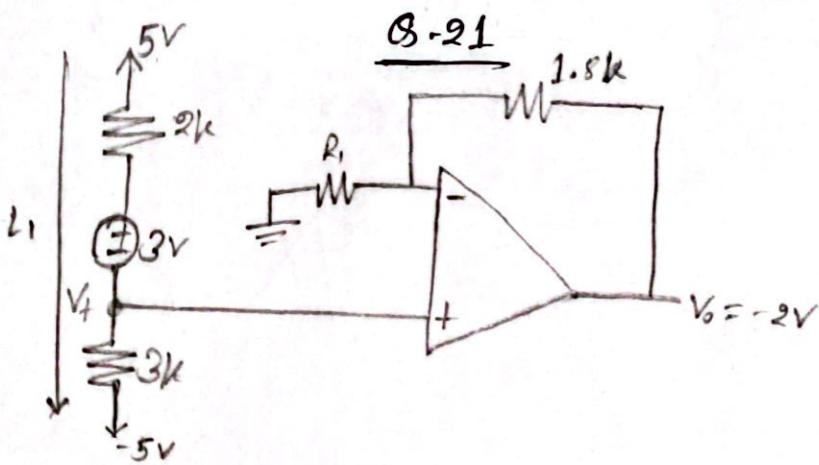
$$\therefore V_0 = -4.5 \text{ V} \quad (\text{Ans})$$



KVL on L_1 ,

$$5 + 5 = 2I + 3 + 3I$$

$$\Rightarrow 5I = 7$$

$$\therefore I = \frac{7}{5} \text{ mA}$$

Now,

$$\frac{V_4 + 5}{3} = \frac{7}{5}$$

$$\Rightarrow V_4 = \frac{7 \times 3}{5} - 5$$

$$\therefore V_4 = -0.8 \text{ V}$$

We know,

$$V_o = \left(1 + \frac{R_o}{R_i}\right) V_{in}$$


$$\Rightarrow -2 = \left(1 + \frac{1.8}{R_i}\right) \times (-0.8)$$

$$\Rightarrow \frac{1.8}{R_i} = \frac{-2}{-0.8} - 1$$

$$\Rightarrow \frac{1.8}{R_i} = \frac{3}{2}$$

$$\Rightarrow R_i = \frac{2 \times 1.8}{3}$$
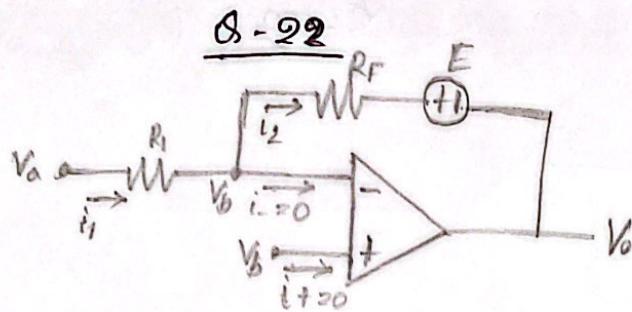
$$\therefore R_i = 1.2 \text{ k}\Omega \quad (\text{Ans})$$



$$i_1 = \frac{V_a - V_b}{R_1}$$

$$i_2 = \frac{V_b - E - V_o}{R_f}$$

$$\Rightarrow \frac{V_b - (E + V_o)}{R_f}$$

Now,
 $i_1 = i_2$

$$\Rightarrow \frac{V_a - V_b}{R_1} = \frac{V_b - E - V_o}{R_f}$$


$$\Rightarrow (V_a - V_b) R_f = (V_b - E) R_1 - V_o R_1$$

$$\Rightarrow V_o R_1 = (V_b - E) R_1 - (V_a - V_b) R_f$$

$$\therefore V_o = V_b - E - \frac{R_f}{R_1} (V_a - V_b)$$

(Ans.)

Q-23

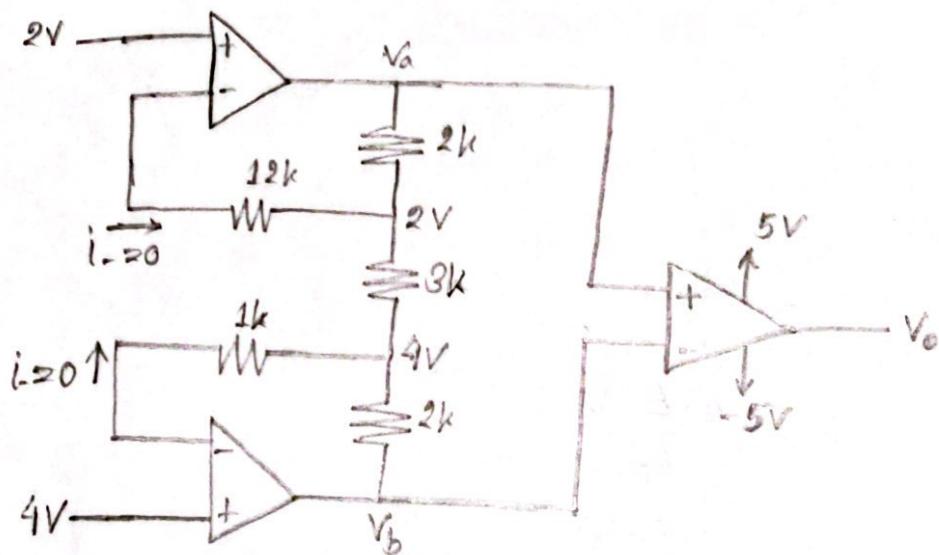

KCL at 2V node,

$$\frac{2-V_a}{2} + \frac{2-4}{3} = 0$$

$$\Rightarrow \frac{2-V_a}{2} = \frac{2}{3}$$

$$\therefore V_a = 0.67V$$

KCL at 4V node,

$$\frac{4-2}{3} + \frac{4-V_b}{2} = 0$$


$$\Rightarrow \frac{4-V_b}{2} = -\frac{2}{3}$$

$$\therefore V_b = 5.33V$$

$$\text{Now, } V_i = (0.67 - 5.33)V$$

$$= -4.66V$$
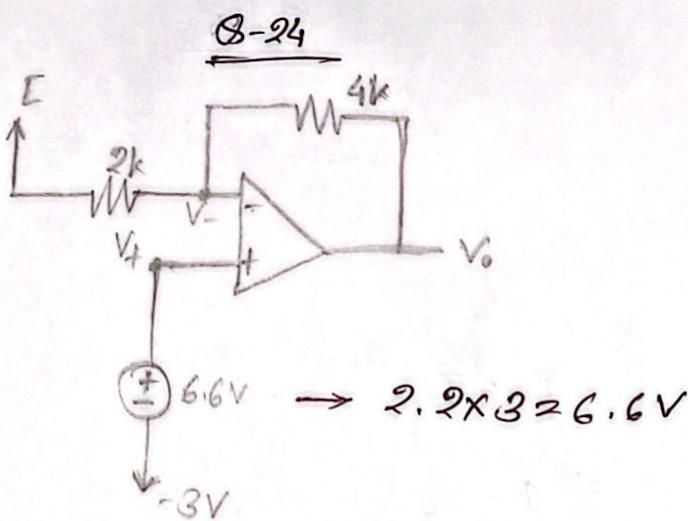
$$\therefore V_o = -5V \quad (\text{Ans})$$



$$\therefore V_+ = (6.6 - 3) \text{ V}$$

$$\approx 3.6 \text{ V}$$

$$\therefore V_- \approx 3.6 \text{ V}$$

When, $E \approx 2.2 \text{ V}$,


$$\frac{3.6 - 2.2}{2} + \frac{3.6 - V_o}{4} > 0$$


$$\therefore V_o = 6.4 \text{ V}$$

When, $E \approx 1.8 \text{ V}$,

$$\frac{3.6 - 1.8}{2} + \frac{3.6 - V_o}{4} > 0$$

$$\therefore V_o = 7.2 \text{ V}$$

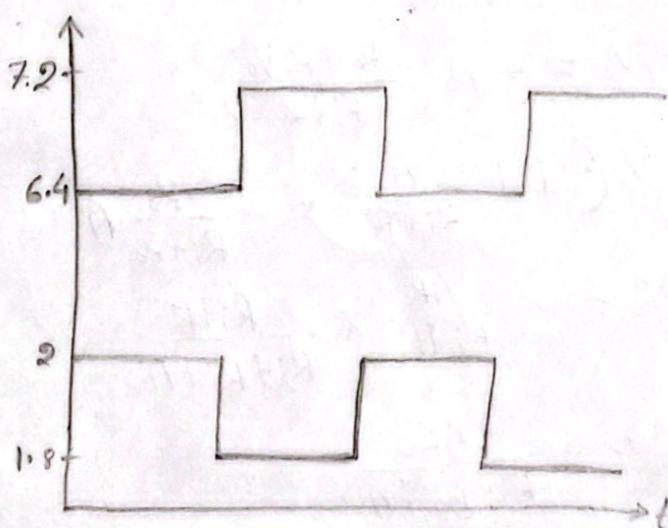

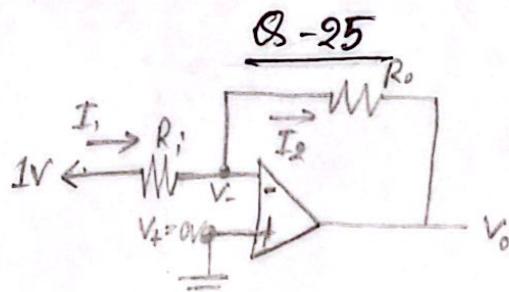

$$I_1 = I_2$$

$$\Rightarrow \frac{1 - V_-}{R_i} = \frac{V_- - V_o}{R_o}$$

$$\Rightarrow \frac{R_o}{R_i} (1 - V_-) = V_- - V_o$$

$$\Rightarrow V_- + \frac{R_o}{R_i} V_- = V_o + \frac{R_o}{R_i}$$

$$\Rightarrow V_- \left(1 + \frac{R_o}{R_i}\right) = V_o + \frac{R_o}{R_i}$$

$$\Rightarrow V_- = \frac{V_o R_i + R_o}{R_i} \times \frac{R_i}{R_i + R_o}$$

$$\therefore V_- = \frac{R_o + R_i V_o}{R_i + R_o}$$

We know,

$$V_o = A(V_+ - V_-)$$

$$\Rightarrow V_o = -AV_-$$

$$\Rightarrow V_o = -A \left(\frac{R_o + R_i V_o}{R_i + R_o} \right)$$

$$\Rightarrow V_o \left(1 + \frac{A}{R_i + R_o}\right) = -\frac{R_o}{R_i + R_o} \cdot A$$

$$\Rightarrow V_o = -\frac{A R_o}{R_i + R_o} \times \frac{R_i + R_o}{R_i + R_o + A}$$

$$\therefore V_o = -\frac{A R_o}{R_i + R_o + A}$$

(Ans)

Q-26

1. $\frac{1}{2} \times 10^3$

2. $10^3 \times 10^{-3}$

3. 10^3

4. 10^3

5. 10^3

6. 10^3

7. 10^3

8. 10^3

9. 10^3

10.

11.

12.

13.

14.

15.

16.

17.

18.

19.

20.

21.

22.


23.

24.

25.

26.

Q-27

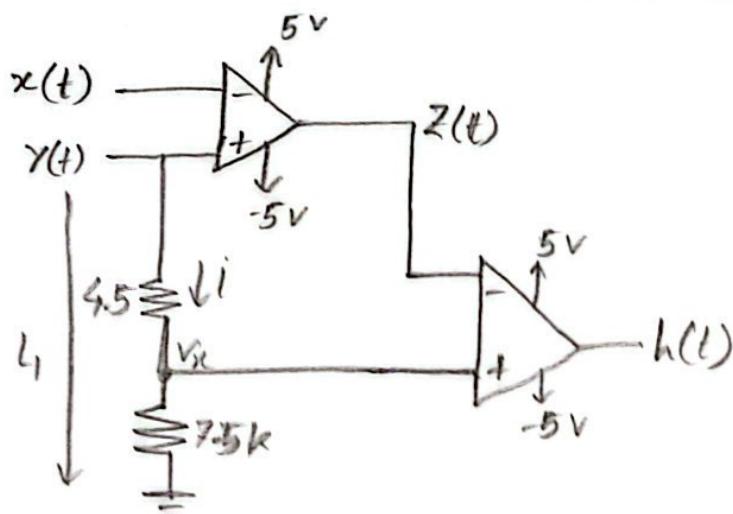

KVL on L_1 ,

$$Y(t) - 0 = 4.5i + 7.5$$

$$\Rightarrow 12i = Y(t)$$

$$\therefore i = \frac{Y(t)}{12}$$




$$\frac{V_x - 0}{7.5} = \frac{Y(t)}{12}$$

$$\Rightarrow V_x = \frac{7.5}{12} Y(t)$$

$$\Rightarrow V_x = 0.625 Y(t)$$


$Y(t)$ has amplitude 8V
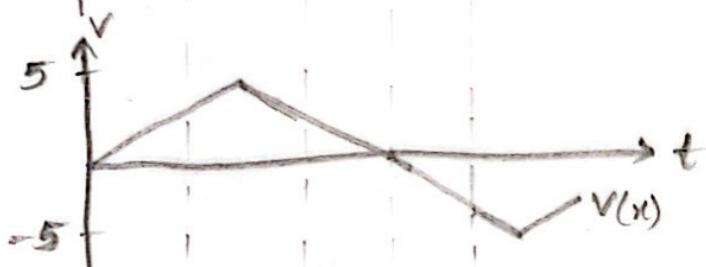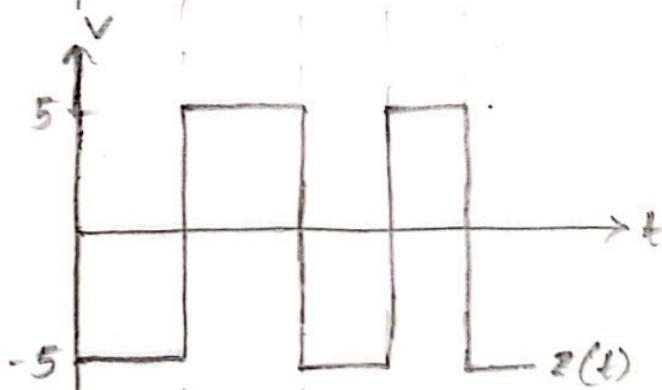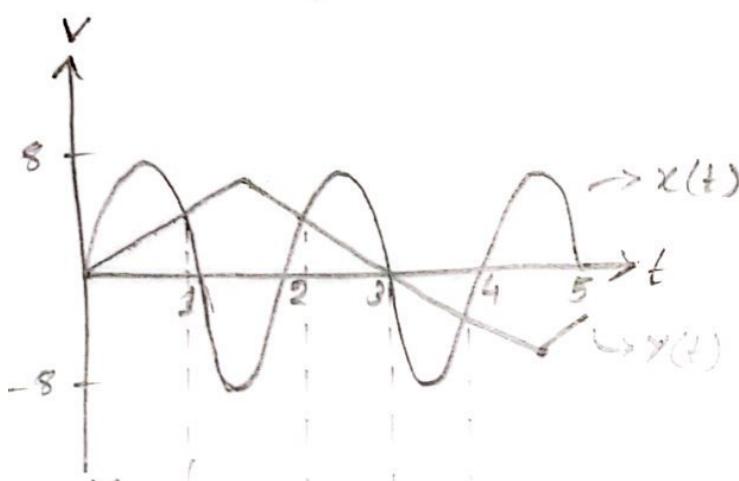
$$\therefore V_x \text{ has } n \text{ of } 8 \times 0.625 \\ = 5V$$





$$\therefore h(t) = -z(t)$$

(Ans)

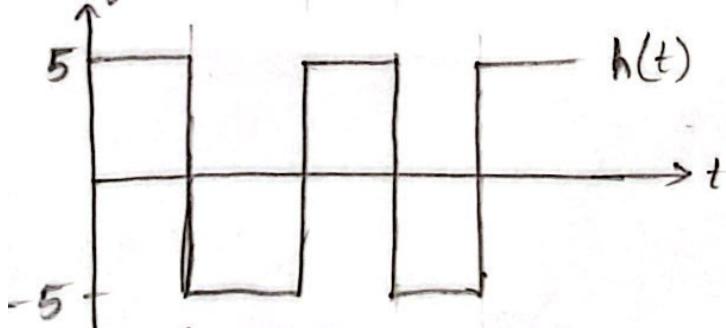



\oplus Inverting Amp
 ~~$2R_1 = R_f$~~

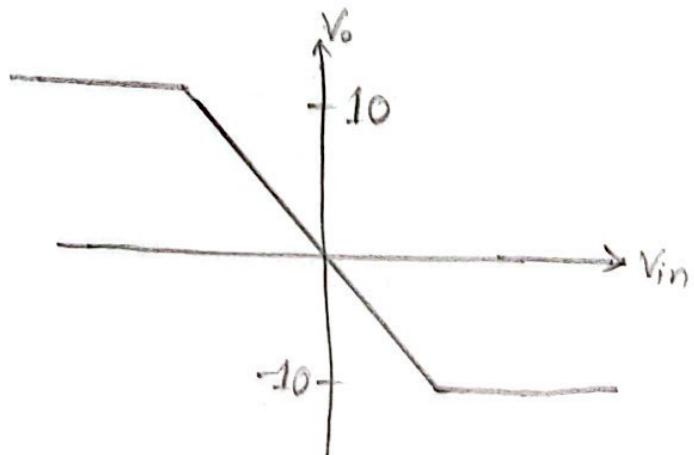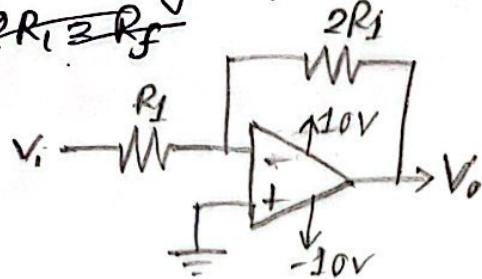

$$V_o = -\frac{2R_1}{R_1} (V_{in})$$

$$= -2 V_{in}$$

Non-inverting amp

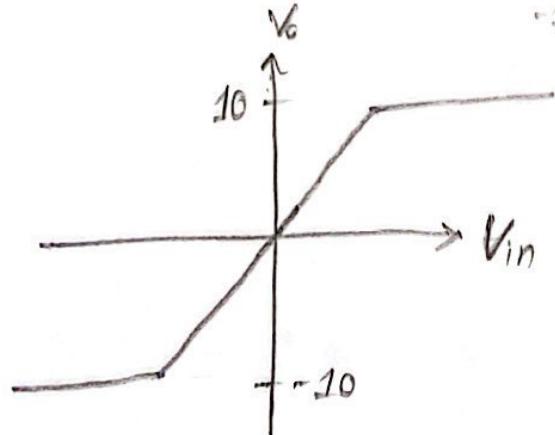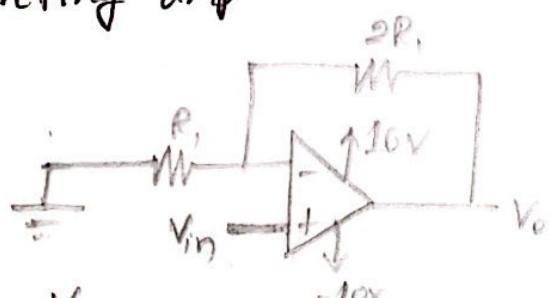

$$V_o = \left(1 + \frac{2R_1}{R_1}\right) V_{in}$$

$$= 3 V_{in}$$

(Ans)

IV

Q-1

(a), (b) & (c) are non-linear

(d) is linear

Q-2

(a) $|AB| < |BC| < |CD| < |DA|$

(b) AB & CD \rightarrow slope = infinity

$\therefore |BC| < |DE| < |AB|$

Q-3

$$|AB| = \text{slope} = \frac{0+7}{-4+4} = \infty$$

$$|BC| = \frac{-4+7}{0+4} = 0.75$$

$$|CD| = \frac{0-0}{0-0} = \infty$$

$$|DE| = \left| \frac{0-0}{0-7} \right| = 1 \quad (\text{Ans})$$

Q-4

$$C(0, -4)$$

Hence,



$$-\frac{V_0}{R} = I_o = C = -4$$

(Ans)

Q3-5



i) $V_o = 5V, m = 2/k\Omega$

$$R = \left| \frac{1}{m} \right| = \frac{1}{2} k\Omega, \alpha = -\frac{V_o}{R} = -\frac{5}{0.5} = -2.5 \text{ mA}$$

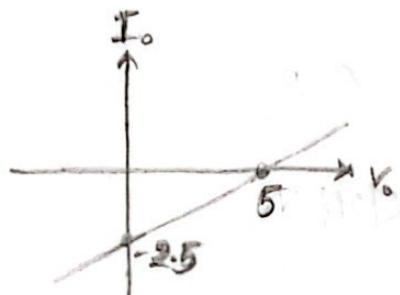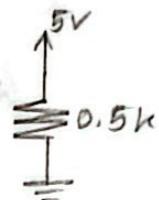



ii) $V_o = 3.5V, m = -2.5/k\Omega$

$$R = \left| \frac{1}{-2.5} \right| = 0.4 k\Omega, \alpha = -\frac{V_o}{R} = -\frac{3.5}{0.4} = -8.75 \text{ mA}$$

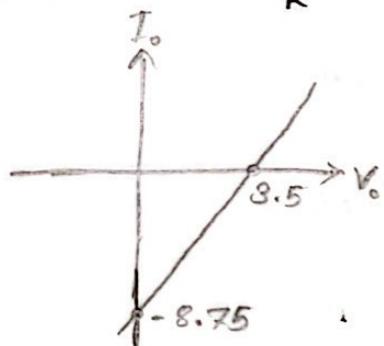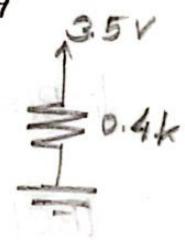

iii) $V_o = -5V, m = 5/k\Omega$

$$R = \left| \frac{1}{5} \right| = 0.2 k\Omega, \alpha = -\frac{V_o}{R} = -\frac{-5}{0.2} = 25 \text{ mA}$$

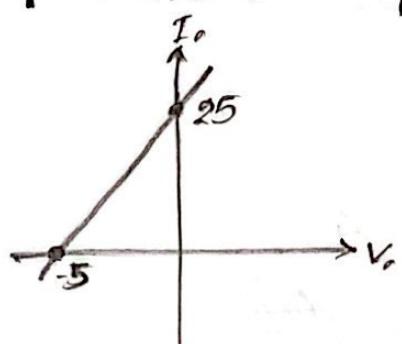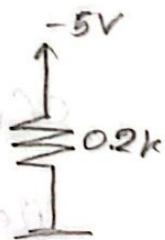

Q-6

i) $\text{Q} = / - 4 \text{ mA}$ $\text{C} = 5 \text{ mA}$
 $V_o = 1.5 \text{ V}$ $-V_o = -25$
 $\Rightarrow V_o = 25 \text{ V}$

ii) ~~$\text{Q} = -5 \text{ mA}$~~ $\text{C} = -5 \text{ mA}$
 ~~$V_o = 2 \text{ V}$~~ $V_o = 1.2 \text{ V}$ (Ans)

Q-7

Same as Q-5.

Q-8

i) AB \rightarrow Voltage Source in series with a resistor / Current Source in parallel with a resistor.

BC \rightarrow Voltage Source.

CD \rightarrow Current Source.

DEF \rightarrow Voltage Source in series with a resistor / Current Source in parallel with a resistor.

FG \rightarrow Voltage Source.

GH \rightarrow Open circuit (Not a device).


Q-9

$$\textcircled{i} \quad I = \frac{1}{R} V - \frac{V_0}{R}$$

$$\textcircled{ii} \quad m = \left| \frac{1}{R} \right| = \frac{1}{3}$$

$$C = -\frac{V_0}{R} = -\frac{10}{3}$$

\textcircled{iii}

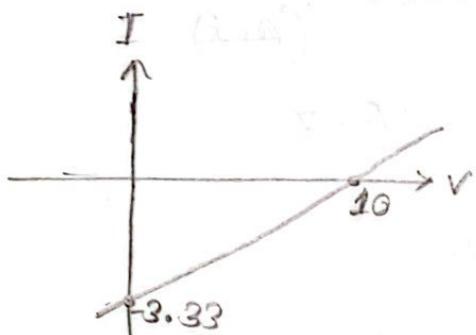
Q-10

$$\textcircled{i} \quad I = \frac{1}{R} V + \frac{V_0}{R}$$

$$\textcircled{ii} \quad m = \left| \frac{1}{R} \right| = \frac{1}{3}$$

$$C = \frac{V_0}{R} = \frac{10}{3} = \frac{10}{3}$$

\textcircled{iii}

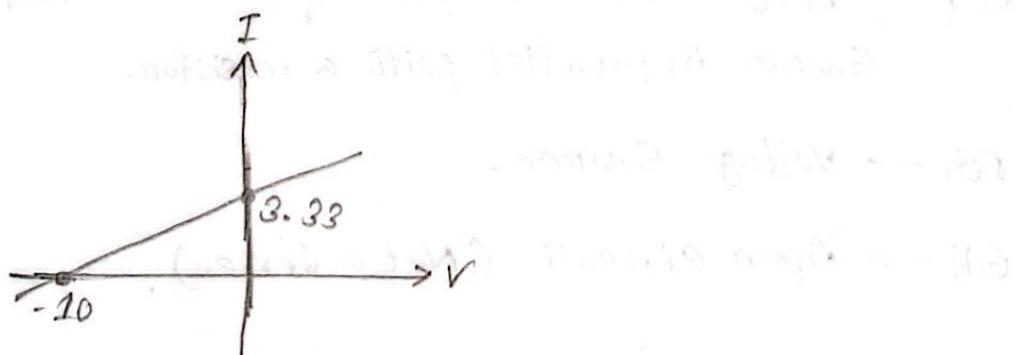


Q-11

$$\text{i) } I = I_0 + \frac{1}{R} V$$


$$\text{ii) } m = \left| \frac{1}{R} \right| = \frac{1}{5}$$

$$C = I_0 = 5$$

iii)

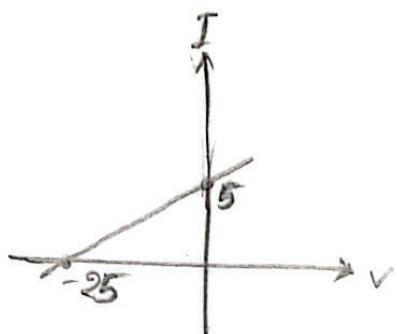


Q-12

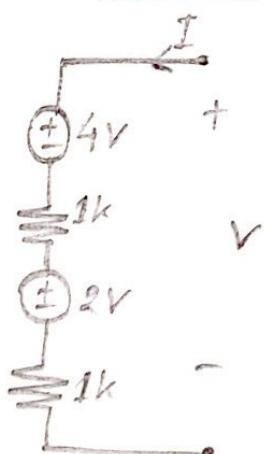


Diode Logic Gates

Q-1


(i)

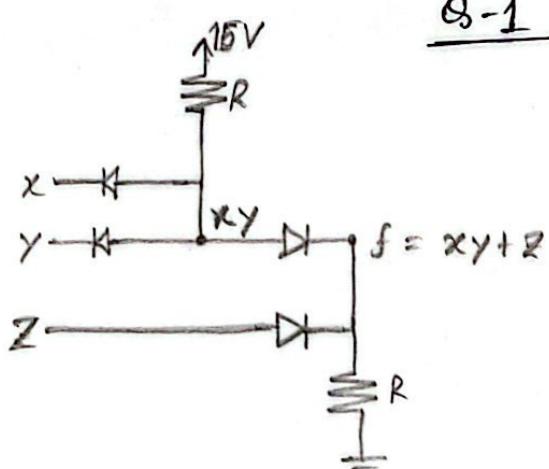

(ii)

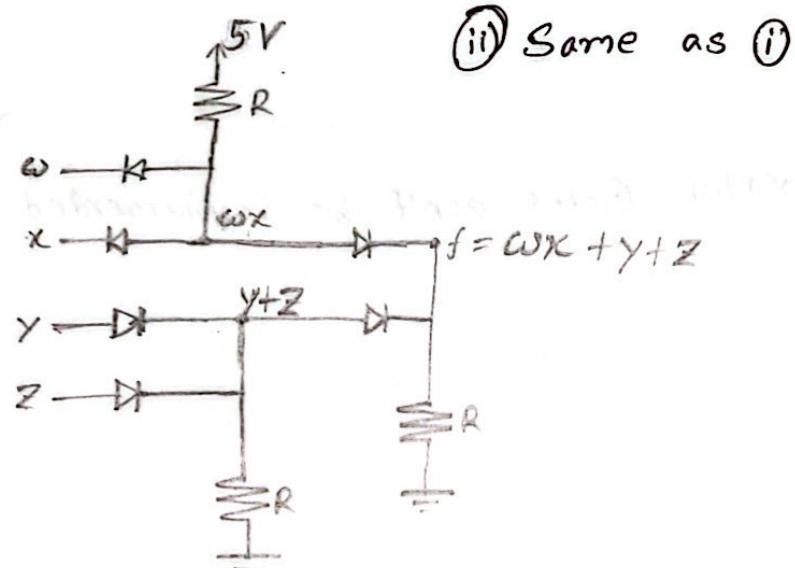


(iv)

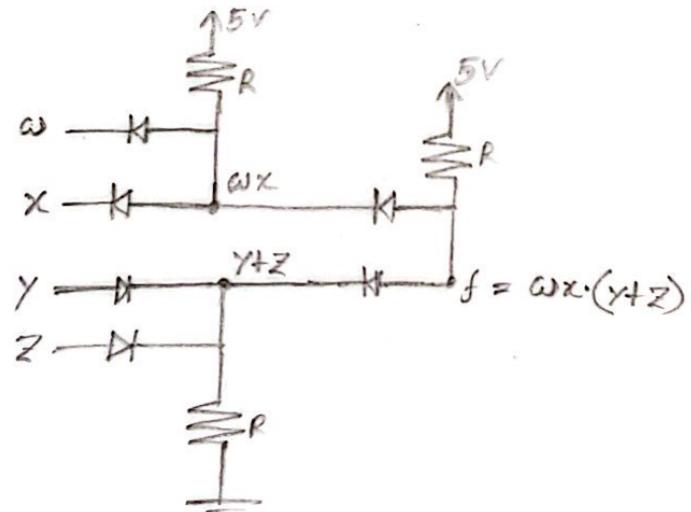


Q-2



i) $xy + yz$

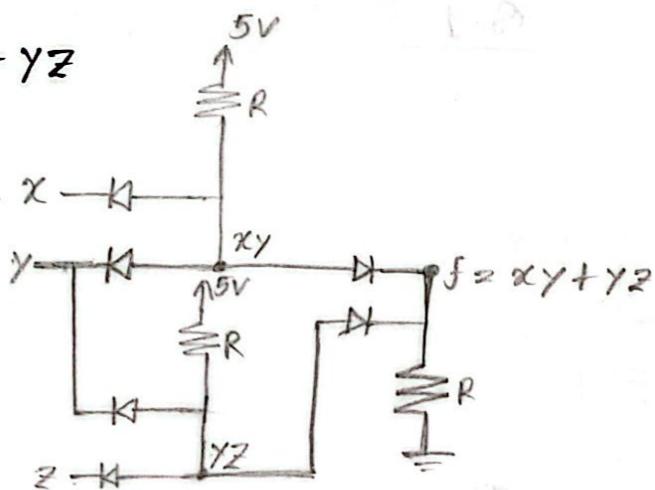

ii) & iii) XOR, XNOR Gates can't be implemented by diodes.


iv) $(A+B)XY$

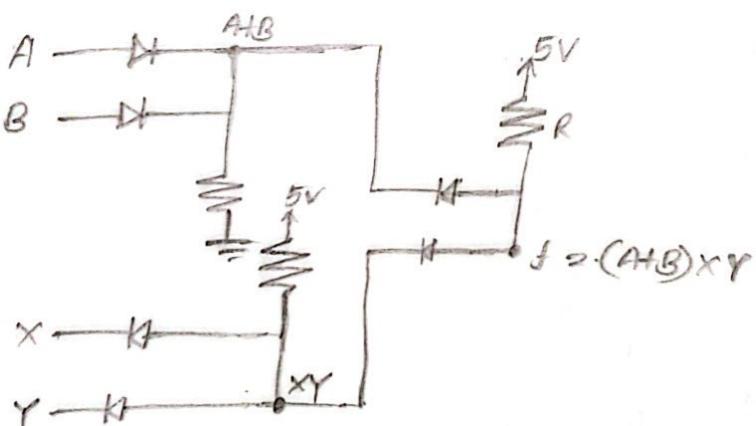

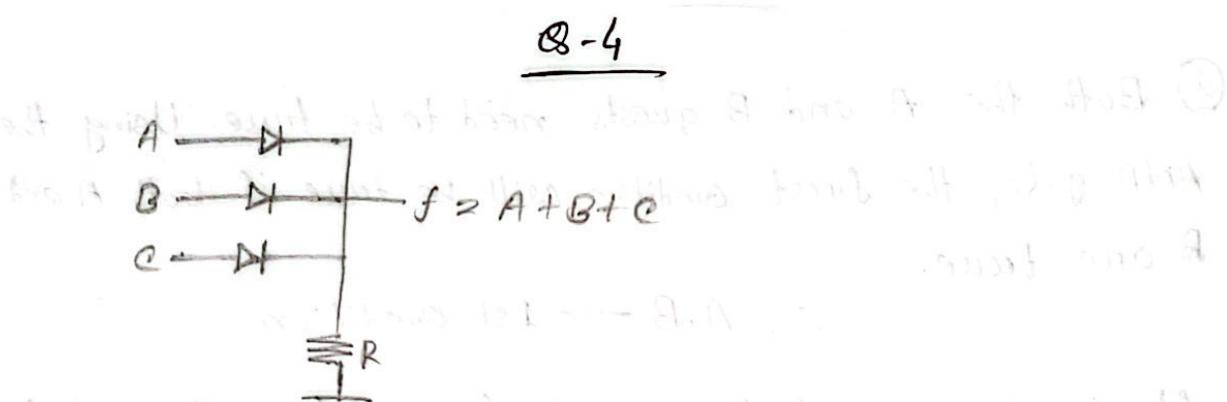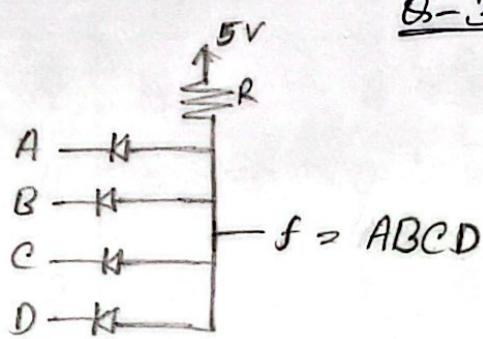

at above 3 inputs must pass all to one load (A)

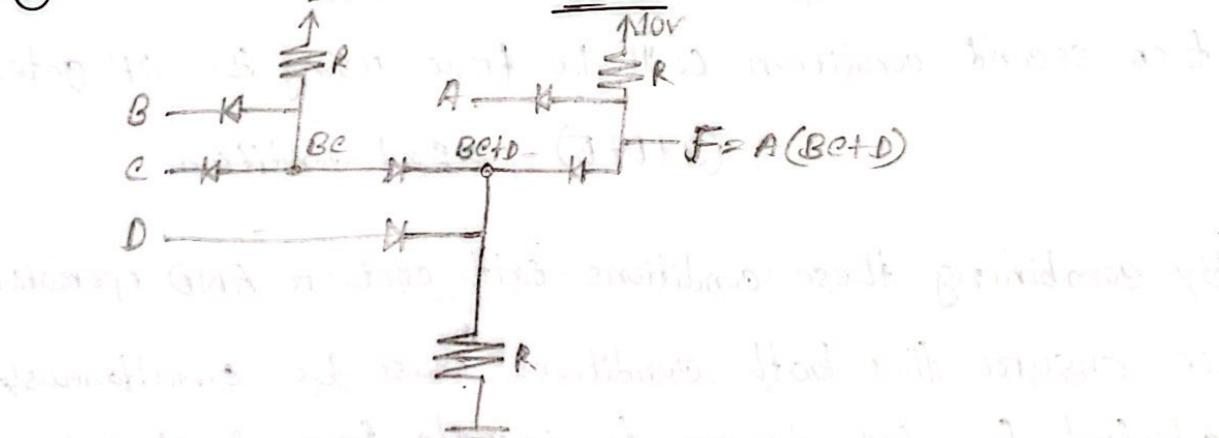(a) if input 10V & no B Q-5 in fig. If input A,




(b)

A	B	C	D	F
4V	3V	4V	6V	4V
5V	3V	4V	2V	3V
13V	3V	4V	15V	10V

→ As, $F = 13V$ which is greater than V_{dd}

$$\textcircled{C} \quad f = (x+y)z$$

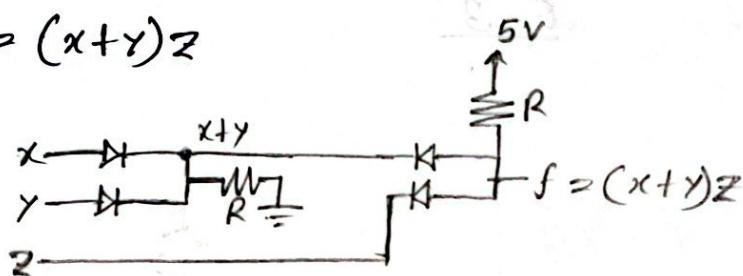

B-6

\textcircled{a} Both the A and B quests need to be true. Using the AND gate, the first condition will be true if both A and B are true.

$$\therefore A \cdot B \rightarrow \text{1st condition}$$

At least one of the quests from C, D, or E needs to be true. If only one of C, D, or E is true, then the second condition will be true using the OR gate.

$$\therefore (C + D + E) \rightarrow \text{2nd condition}$$


By combining these conditions with another AND operation, we ensure that both conditions must be simultaneously satisfied for the players to upgrade from level-1 to level-2.

$$\therefore F = AB(C + D + E)$$

(Ans)

(b)

A	B	C	D	E	F
0	0	1	0	1	0
0	1	1	1	0	0
1	0	0	0	0	0
1	1	1	0	0	1

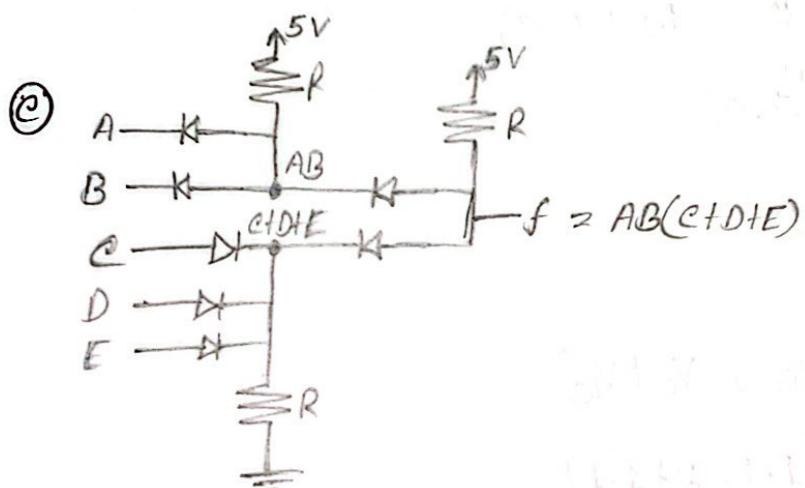

(d) Designing a NAND gate using si diodes alone is not achievable because diodes are passive components that can only conduct current in one direction. They lack the ability to perform the inversion or NOT operation required for the NAND gate's logic function.

Q-7

$$\text{i) } V_5 = \min(V_1 + V_{D_1}, V_2 + V_{D_2})$$

$$= \min(2+0.3, 1.7+0.5)$$

$$= \min(2.3, 2.2)$$

$$= 2.2V \quad (\text{Ans})$$

$$V_6 = \min(V_3 + V_{D_3}, V_4 + V_{D_4})$$

$$= \min(1.5+0.7, 1.1+0.9)$$

$$= \min(2.2, 2.0)$$

$$= 2V$$

(Ans)

$$\text{ii) } V_0 = \max(V_5 + V_{D_5}, V_6 + V_{D_6})$$


$$= \max(2.2+1.1, 2+1.1)$$

$$= \max(3.3, 3.1)$$

$$= 3.3V$$

(Ans)

(iii)

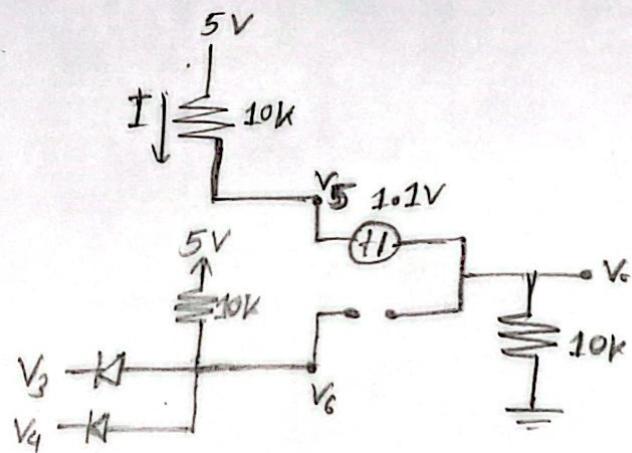

Assuming that V₅ is higher.

$$I = \frac{5 - 1.1}{10 + 10} = 0.195 \text{ mA}$$

$$V_5 = 5 - 10I = 3.05 \text{ V}$$

$$V_6 = 2 \text{ V} \quad (\text{from (i)})$$

$\therefore V_5 > V_6$. So, assumption was correct.

$$V_6 = 3.05 - 1.1 \text{ V}$$


$$= 1.95 \text{ V}$$

(Ans)

Diode : Method of Assumed states

Q-1

①

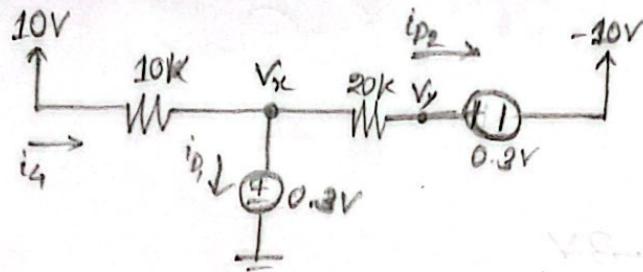

Assumption:

$$D_1 = \text{ON}$$

$$D_2 = \text{ON}$$

$$V_x = 0.3V$$

$$\begin{aligned} i_4 &= \frac{10 - 0.3}{10} \\ &= 0.97 \text{ mA} \end{aligned}$$

$$\begin{aligned} i_{D_2} &= \frac{0.3 + 9.7}{20} \\ &= 0.5 \text{ mA} \end{aligned}$$

$$\left| \begin{array}{l} V_y + 10 = 0.3 \\ \therefore V_y = -9.7V \end{array} \right.$$

$$i_4 = i_0 + i_{D_2}$$

$$\Rightarrow 0.97 = 0.5 + i_0,$$

$$\therefore i_0 = 0.47 \text{ mA}$$

Verification:


$$i_{D_1} > 0$$

$$i_{D_2} > 0$$

\therefore my assumption was correct.

(Ans)

ii)

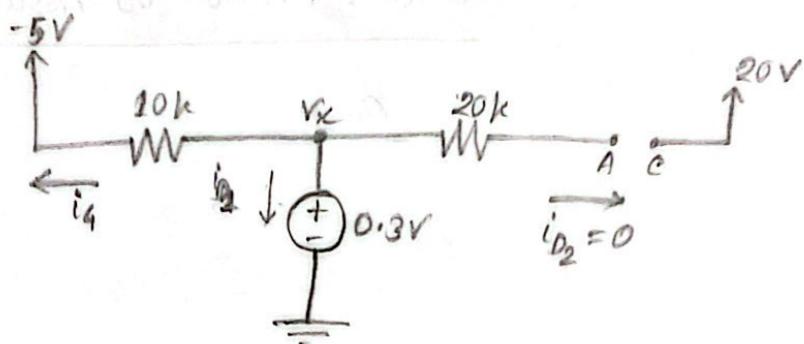

$$V_x = 0.3V$$

Assumption:

$$D_1 = ON$$

$$D_2 = OFF$$

$$V_x = 0.3V$$

$$i_4 = \frac{0.3 + 5}{10}$$

$$= 0.53mA$$

$$i_{D_1} = i_4 = 0.53mA$$

$$i_{D_2} = 0mA$$

$$V_B = V_A - V_D = 0.3 - 20 \\ = -19.7V$$

Verification:


$$I_D > 0$$

$$I_{D_2} > 0$$

$$V_D < V_{D_s}$$

∴ Assumption was correct.

(Ans)

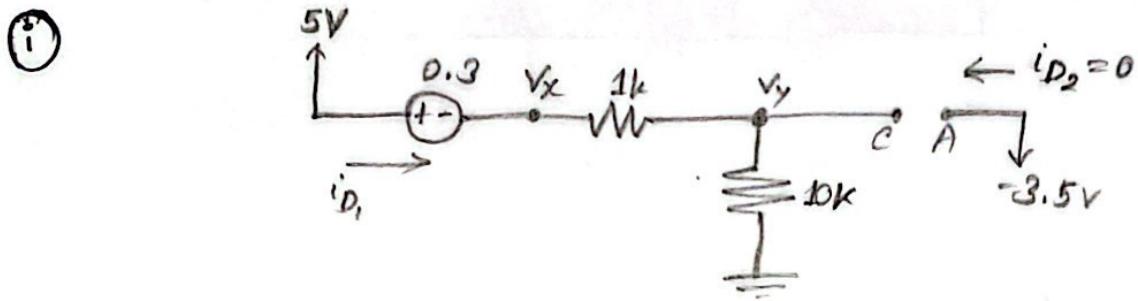Assumption:

$$5 - V_x = 0.3$$

$$\therefore V_x = 4.7V$$

Applying KVL,

$$5 - 0 = 0.3 + I_{D_1} + 10I_A$$

$$\Rightarrow 11I_{D_1} = 4.7$$

$$\therefore I_{D_1} = 0.43 \text{ mA}$$

$$\therefore V_y = 0.43 \times 10 \\ = 4.3V$$

$$V_D = V_A - V_C = -3.5 - 4.3 \\ = -7.8V$$

Verification:

$$I_{D_1} > 0$$


$$I_{D_2} > 0$$

$$V_D < V_{D_0}$$

\therefore Assumption was correct

(Ans)

(ii)

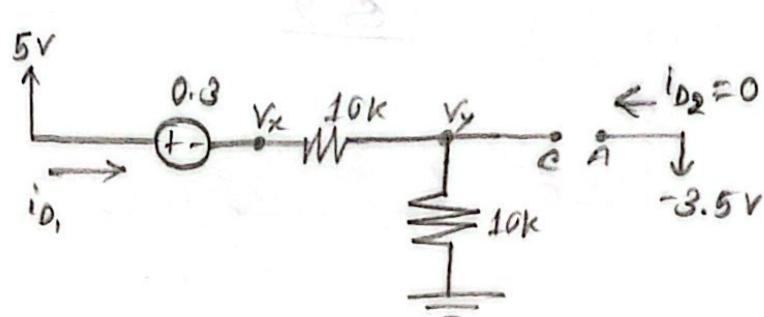Assumption:

$$D_1 = ON$$

$$D_2 = OFF$$

$$\therefore V_x = 4.7V$$

Applying KVL,

$$5 - 0 = 0.3 + 10i_{D_1} + 10i_{D_2}$$

$$\Rightarrow i_{D_1} = 0.235 \text{ mA}$$

$$\therefore V_y = 0.235 \times 10 \\ = 2.35V$$

$$V_D = V_A - V_C = -3.5 - 2.35 \\ = -5.85V$$

Verification:-

$$I_{D_1} > 0$$

$$I_{D_2} \neq 0$$


$$V_D < V_{D_0}$$

\therefore Assumption was correct


(Ans)

B-3

④

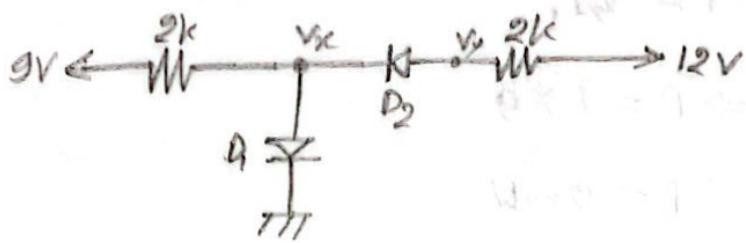

⑤

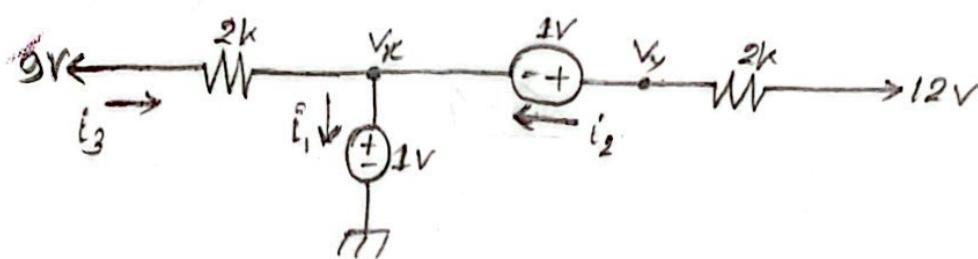Assumption:-

$$D_1 = ON.$$

$$D_2 = ON$$

$$V_x = 1V$$

$$V_y - V_x = 1$$

$$\therefore V_y = 2V$$

$$i_2 = \frac{12 - 2}{2} = 5mA$$

$$i_3 = \frac{9 - 1}{2} = 4mA$$

$$i_1 = i_2 + i_3$$

$$= 5 + 4$$

$$= 9mA$$

Verification:-

$$i_{D_1} > 0$$

$$i_{D_2} > 0$$

\therefore Assumption was correct.

② We know,


$$P = VI$$

$$\Rightarrow P = 1 \times 9$$

$$\therefore P = 9 \text{ mW}$$

$\therefore P$ is consuming power

(Ans)

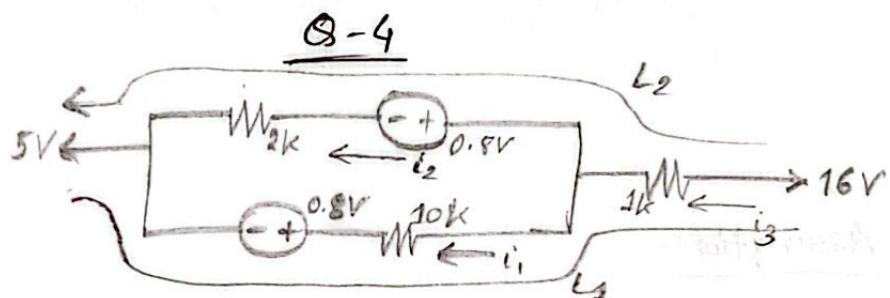

Assumption:-

$$D_1 = 0N$$

$$D_2 = 0N$$

$$i_1 = i_3 - i_2$$

KVL on L_1 ,

$$16 - 5 = i_3 + 10(i_3 - i_2) + 0.8$$

$$\Rightarrow -10i_2 + 11i_3 = 10.2 \dots \textcircled{1}$$

KVL on L_2 ,

$$16 - 5 = i_3 + 0.8 + 2i_2$$

$$\Rightarrow 2i_2 + i_3 = 10.2 \dots \textcircled{2}$$

$\textcircled{1} \& \textcircled{2} \Rightarrow$

$$i_2 = 3.19 \text{ mA}$$

$$i_3 = 3.83 \text{ mA}$$


$$\therefore i_1 = 3.83 - 3.19 = 0.64 \text{ mA}$$

Verification:-

$$i_1 > 0$$

$$i_2 > 0$$

\therefore Assumption was correct (Ans)

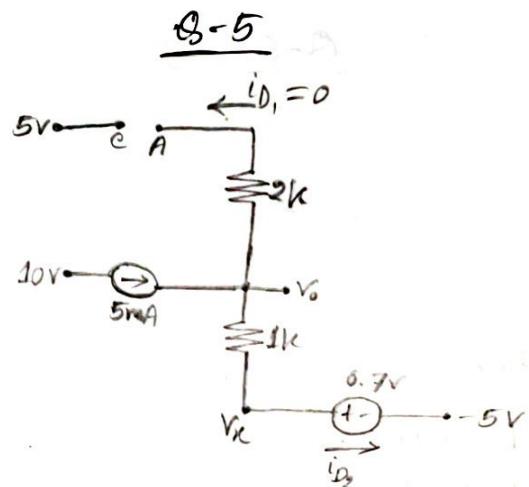

Assumption:-

$$D_1 = \text{OFF}$$

$$D_2 = \text{ON}$$

$$\star V_x + 5 = 0.7$$

$$\therefore V_x = -4.3V$$

$$i_{D_2} = 5\text{mA}$$

$$\Rightarrow \frac{V_o - V_x}{1} = 5$$

$$\Rightarrow V_o + 4.3 = 5$$

$$\therefore V_o = 0.7V$$

$$V_D = V_A - V_o$$

$$= 0.7 - 5$$

$$= -4.3V$$


Verification:-

$$i_{D_2} > 0$$

$i_{D_2} > 0 \quad \therefore \text{Assumption was correct}$

$$V_o < V_{D_0}$$

(Ans)

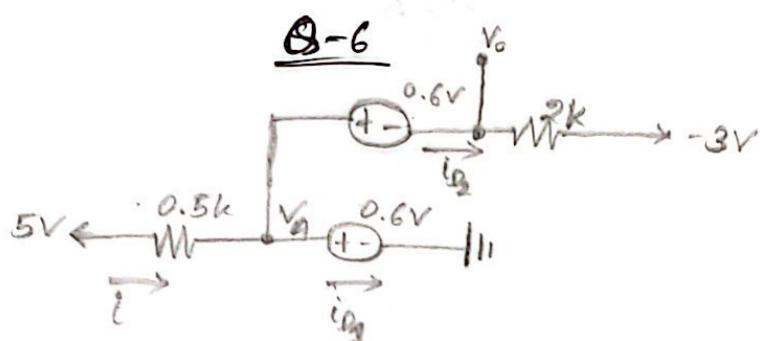

Assumption:-

$$D_1 = ON$$

$$D_2 = ON$$

$$V_A = 0.6V$$

$$V_A - V_o = 0.6$$

$$\therefore V_o = 0V$$

$$i_{D_2} = \frac{0+3}{2} = 1.5mA$$

$$i_b = \frac{5 - 0.6}{0.5}$$

$$= 8.8mA$$

$$i_{D_1} = 8.8 - 1.5$$

$$= 7.3mA$$

Verification:-


$$i_{D_1} > 0$$

$i_{D_2} > 0 \quad \therefore \text{Assumption was correct.}$

①

Assumption:-

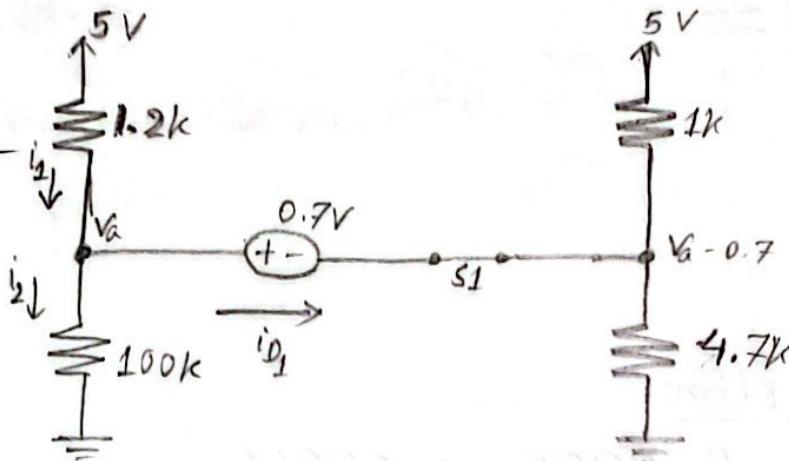$D_1 = ON$
 $S_2 \text{ open}$ $D_2 = OFF$
 $P_3 = OFF$



Applying KCL,

$$\frac{Va - 5}{1.2} + \frac{Va - 0.7}{100} + \frac{Va - 0.7 - 0}{4.7} + \frac{Va - 0.7 - 5}{1} = 0$$

$$\therefore Va = 4.871 V$$

$$i_1 = \frac{5 - 4.871}{1.2} = 0.108 \text{ mA}$$

$$i_2 = \frac{4.871 - 0}{100} = 0.049 \text{ mA}$$


$$\therefore i_{D_1} = 0.108 - 0.049 \\ = 0.059 \text{ mA}$$

$\therefore 0.049 \text{ mA}$ current is passing through the $100\text{k}\Omega$

resistor.

(Ans)

(ii)

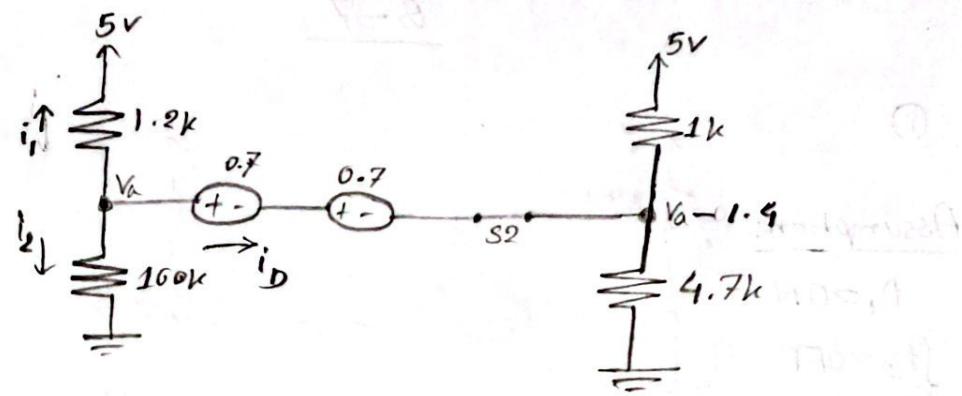Assumption:

$$D_1 = \text{OFF} \text{ as } S_1 = \text{OFF}$$

$$D_2 = D_3 = \text{ON}$$

Applying KCL,

$$\frac{V_a - 5}{1.2} + \frac{V_a - 0}{100} + \frac{V_a - 1.4 - 5}{1} + \frac{V_a - 1.4 - 0}{4.7} = 0$$

$$\therefore V_a = 5.284 \text{ V}$$

$$I_D = \frac{5 - 5.284}{1.2} + \frac{5.284 - 0}{100}$$

$$\Rightarrow i_D + i_1 + i_2 = 0$$

$$\Rightarrow i_D = - \left(\frac{5284 - 5}{1.2} + \frac{5.284}{100} \right)$$

$$\therefore i_D = -0.29 \text{ mA}$$

$$\therefore i_D < 0$$

\therefore Assumption was wrong.


Assumption. I-

$$D_2 = D_3 = 0 \text{ FF}$$

KVL on L_1 ,

$$5 - 0 = 1.2I + 100I$$

$$\therefore I = 0.049 \text{ mA.}$$

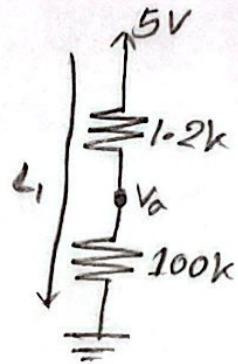

$\therefore 0.049 \text{ mA}$ current is passing through the $100\text{k}\Omega$ resistor.

(Ans)