
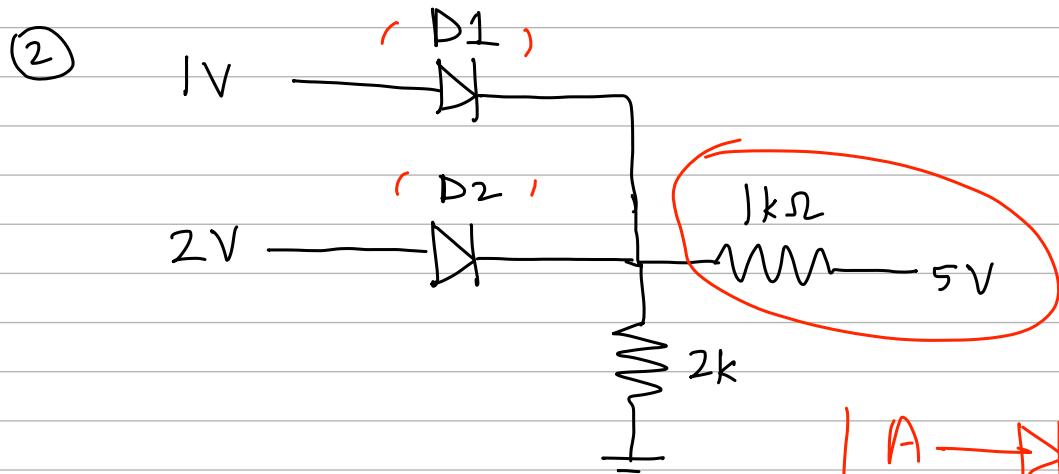


## Assumed states examples :-

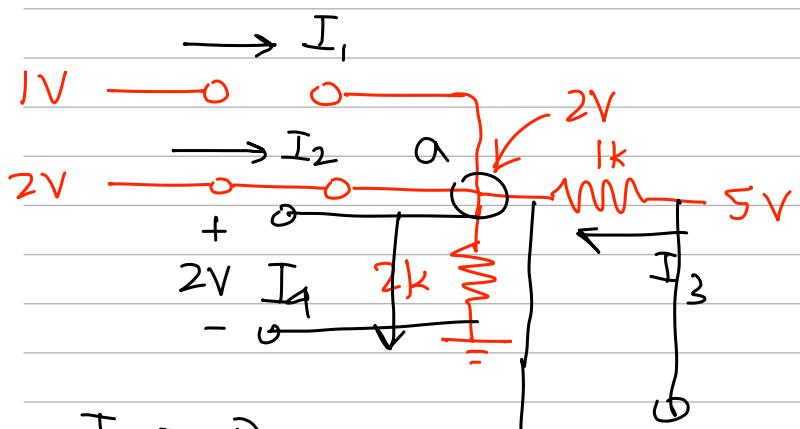

Assume diodes ideal.

① D2 on, D1 off:



$$I_1 = 0$$


$$I_3 = \frac{5 - 2}{1k} = 3 \text{ mA}$$

$$I_4 = \frac{2 - 0}{2k} = 1 \text{ mA}$$


Node a :

$$I_2 = -2 \text{ mA} \quad I_3 = 3 \text{ mA}$$



$$I_4 = 1 \text{ mA}$$

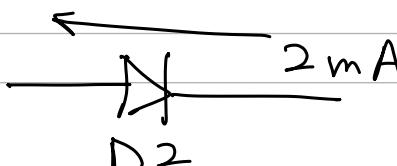


Assumption  
is: wrong

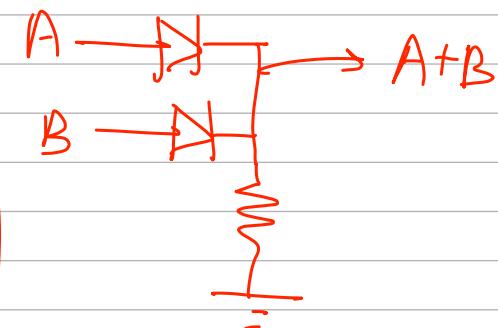

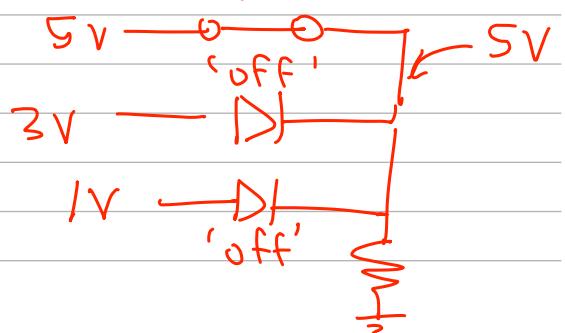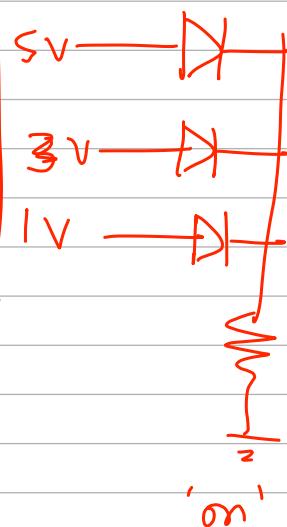A, B voltage different  
→ higher voltage  
diode on.  
→ other diodes off




IF  $D_1$  on :

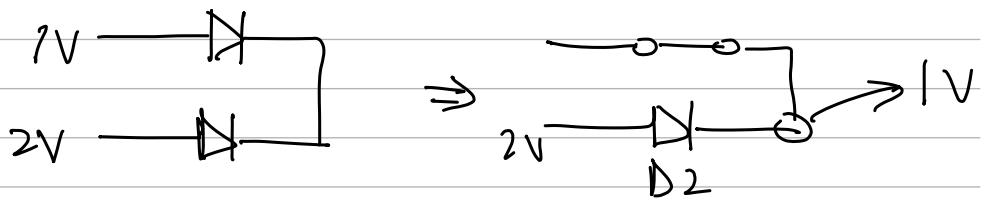

So  $D_1$  cannot be on.


$\therefore D_2$  OFF,  $D_1$  OFF :

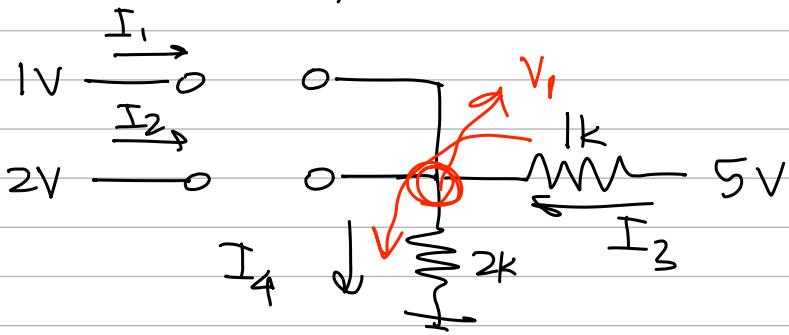

$$I_1 = 0$$

$$I_2 = 0$$

$$I_3 = I_4 = \frac{5}{1+2}$$

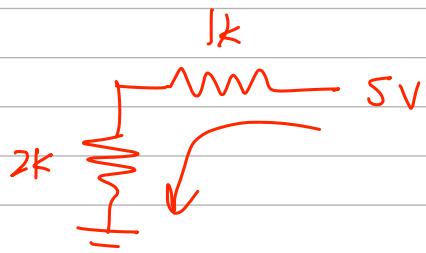

KVL :


$$-5 + 1I_3 + 2I_4 = 0$$

$$3I_3 = 5$$

$$I_3 = \frac{5}{3}$$

$$V_1 = 2 \times I_4 = 2 \times \left(\frac{5}{3}\right)$$

$$= \frac{10}{3} = 3.33 \text{ V}$$

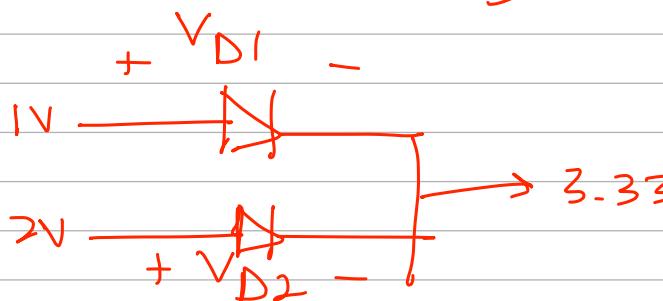


$$V_{D1} = 1 - 3.33$$

$$= -2.33 \text{ V}$$




$$V_{D2} = 2 - 3.33$$

$$= -1.33 \text{ V}$$

W/ assumption correct

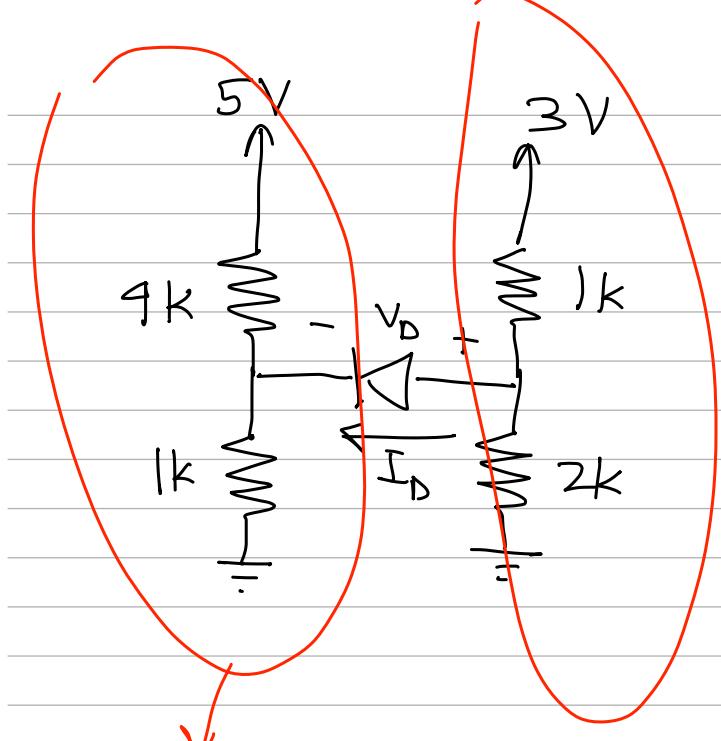

Use CVD model with  
 $V_D = 0.7V$ .

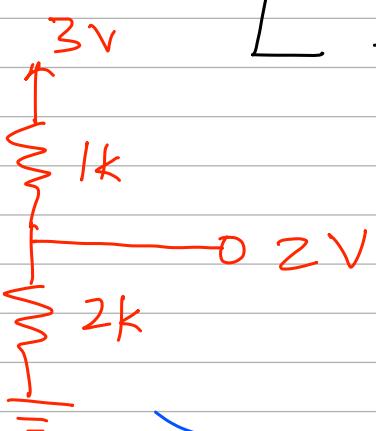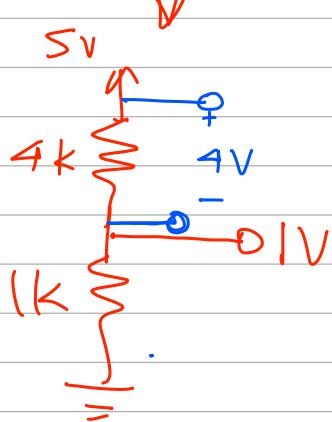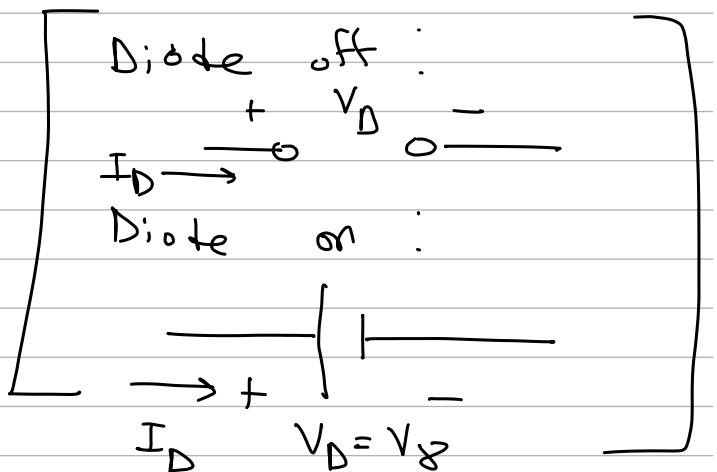

$$V_D = 2 - 1 = 1V$$

$$\hookrightarrow V_{4k} = \frac{1}{1+4} \times 5 = 1V$$

$$= 4V$$

$$V_{1k} = \frac{1}{1+2} \times 3 = 1V$$

$$V_{2k} = \frac{2}{1+2} \times 3 = 2V$$

$$V_{1k} = \frac{1}{1+4} \times 5 = 1V$$


$\therefore$  Diode should be ON!

Super node

$$\frac{V_1 - 5}{4} + \frac{V_1 - 0}{1} + \frac{V_2 - 3}{1} + \frac{V_2 - 0}{2} = 0$$

$$V_2 - V_1 = 0.7V$$
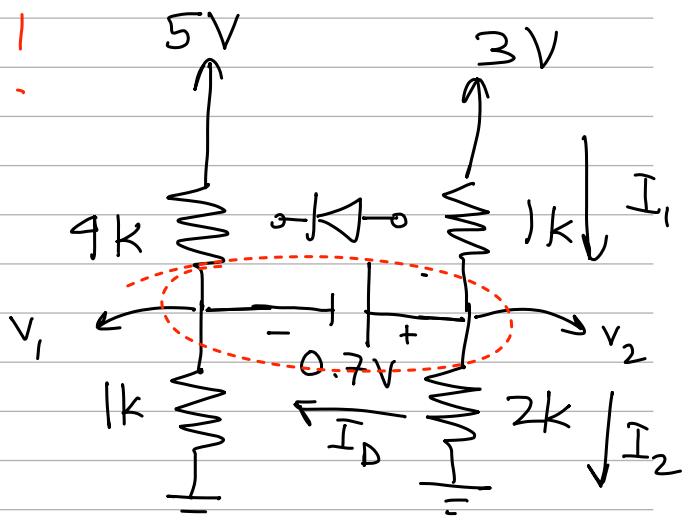
$$\textcircled{1} \quad \textcircled{II}$$



Solving ① and ⑪ :

$$V_1 = 1.163 \text{ V}$$


$$V_2 - V_1 = 0.7 \text{ V}$$

$$V_2 = 1.863 \text{ V}$$


$$I_1 = \frac{3 - V_2}{1k} = 1.163 \text{ mA}$$

$$I_2 = \frac{V_2 - 0}{2k} = 0.932 \text{ mA}$$
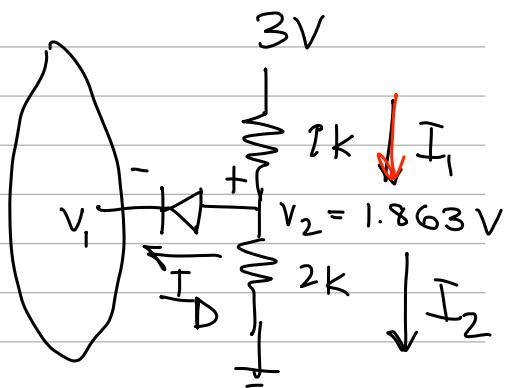
$$I_D = I_1 - I_2 \\ = 0.205 \text{ mA}$$



$$I_1 = I_2 + I_D$$

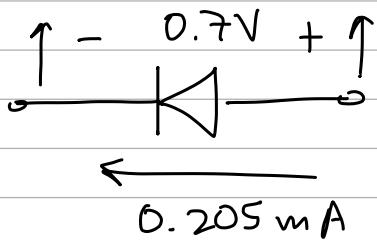

For 'ON' diode:

$$\rightarrow V_D = V_S [+ve]$$

$$\rightarrow I_D \text{ +ve}$$

Assumption must be changed if :

$$\rightarrow I_D \text{ -ve.}$$

For 'OFF' diode :

$$\rightarrow V_D \geq -ve$$


$$\rightarrow I_D '0'$$

Assumption must be changed if :

$$\rightarrow V_D \rightarrow +ve \left[ \begin{array}{l} \text{no matter} \\ \text{how small} \\ \text{or big} \end{array} \right]$$

$$I_D \rightarrow +ve$$

Q.

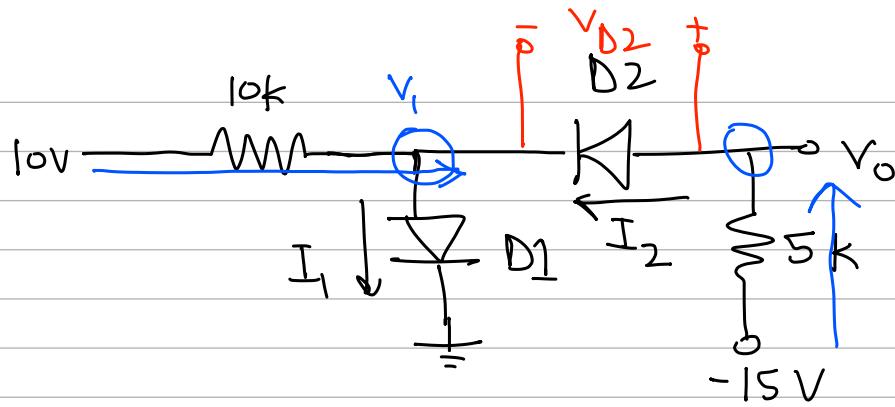

$$\boxed{V_{D2} \approx 0.7V}$$

Find  $V_0$ ,  $I_1$ ,  $I_2$ .

$V_1$  should be +ve

$[V_1 < 10$  for current to flow across  $10k]$

$V_0$  must be  $< -15V$  for current to flow from  $-15V$ .  
 $\therefore V_1$  should be greater than  $V_0$

Then  $V_1$  should be  $-V_{D2} - V_C$  greater than 0.

$\therefore V_{D1}$  +ve  $\rightarrow D1$  ON

### ① D1 ON, D2 OFF:

$$I_2 = 0$$


$$I_1 = \frac{10 - 0.7}{10} = 0.93 \text{ mA}$$

$$V_{D1} = 0.7V$$

$$V_{D2} = (-15) - (V_1)$$

$$= -15 - 0.7 = -15.7V$$

$$V_0 = -15V$$

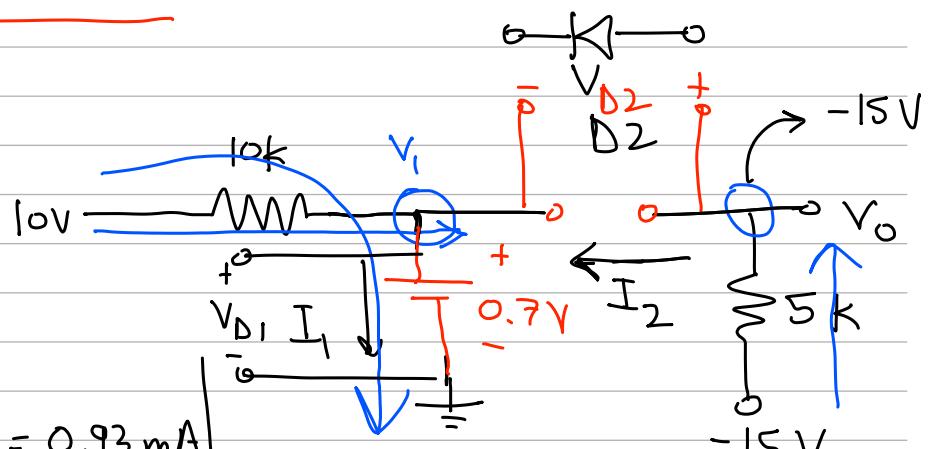


$$-10 + 10I_1 + 0.7 = 0$$

$$\text{or, } I_1 = \frac{10 - 0.7}{10}$$

$$= 0.93 \text{ mA}$$

✓

Q.

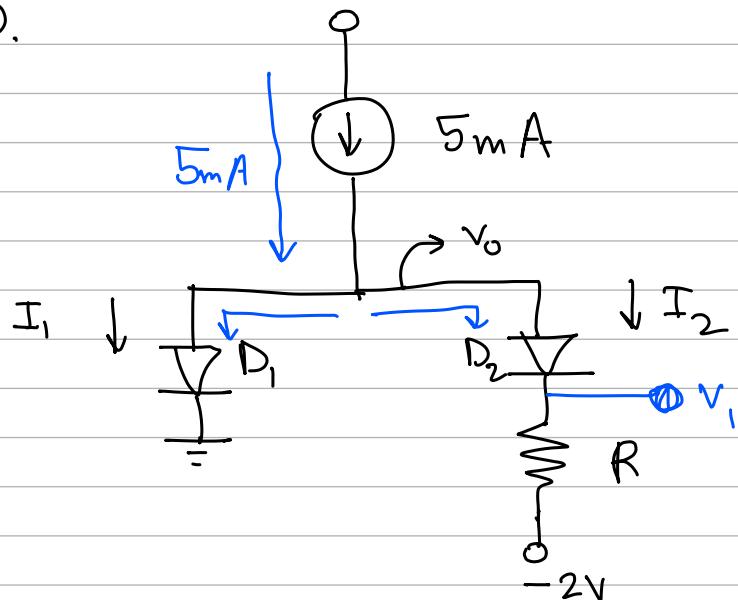

$$(a) R = 100 \text{ K}$$

$$(b) R = 0.2 \text{ K}$$

Use CVD model with

$$V_S = 0.7 \text{ V}$$

(a) 100 K :

Assume both diodes ON :

$$\boxed{5 = I_1 + I_2}$$


$$V_0 = 0.7 \text{ V}$$

$$V_0 - V_1 = 0.7 \text{ V}$$

$$V_1 = 0 \text{ V}$$

$$I_2 = \frac{0 - (-2)}{100} = 0.02 \text{ mA}$$

$$I_1 = 5 - I_2 = 4.98 \text{ mA}$$

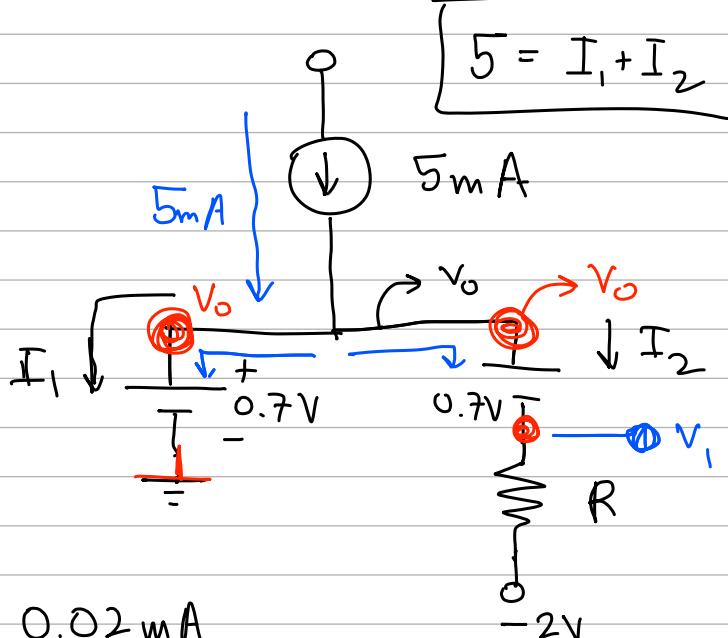



$$\textcircled{b} \quad R = 0.2 \text{ k}$$

$$V_o = 0.7 \text{ V}$$

$$V_i = 0 \text{ V}$$

$$I_2 = \frac{0 - (-2)}{0.2}$$

$$= \frac{2}{0.2} = 10 \text{ mA}$$

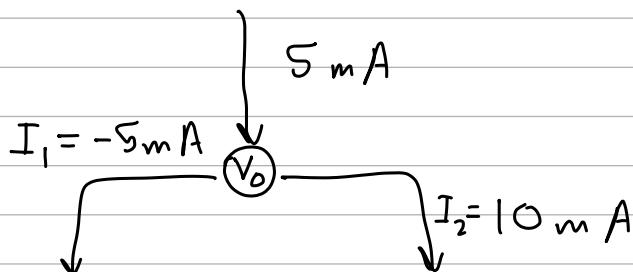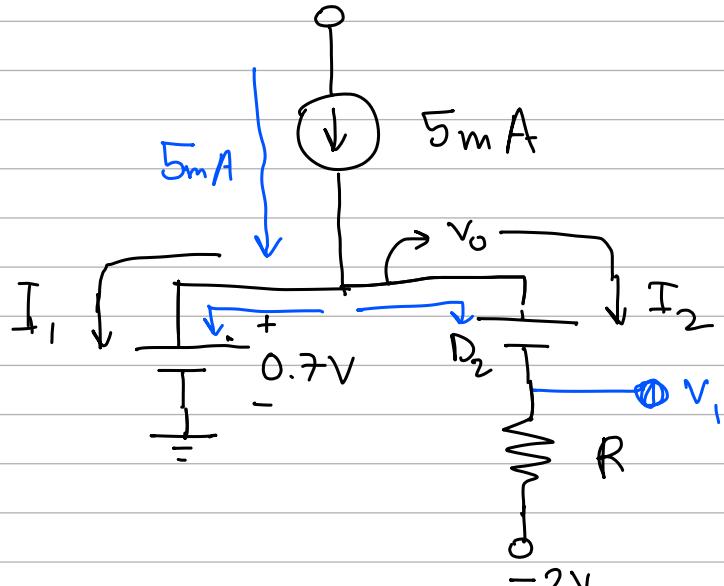

Then  $\overline{I_{D1}} \rightarrow -\text{ve. Assumption wrong}$


$\Rightarrow \textcircled{D1} \rightarrow \text{assumption change : 'ON' to 'OFF'}$

$D_1$  off,  $D_2$  on :

$$I_1 = 0 = I_{D1}$$

$$I_2 = 5 \text{ mA} = I_{D2}$$

$$V_R = 0.2 \times 5 \\ = 1 \text{ V}$$

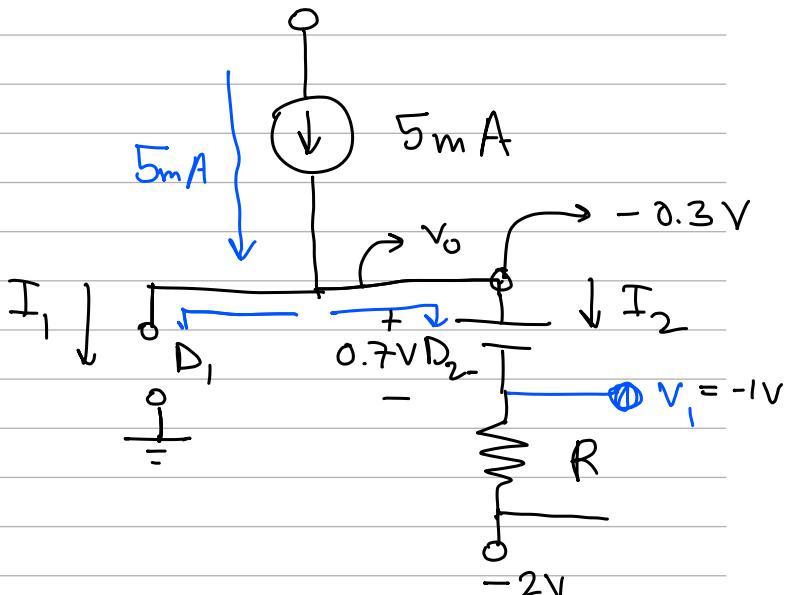

$$V_i - (-2) = 1 \text{ V} \Rightarrow V_i + 2 = 1 \text{ V}$$

$$V_i = 1 - 2 = -1 \text{ V}$$

$$V_o = -1 \text{ V} + 0.7 \text{ V} = -0.3 \text{ V}$$

$$V_{D_1} = V_o - 0 = -0.3 \text{ V}$$

$$I_{D_1} = 0$$

$$V_{D_2} = 0.7 \text{ V}$$

$$I_{D_2} = 5 \text{ mA}$$

Nernstmann chapter-2 exercise, lots of diode  
assumed states problem.