



# CSE251: Electronic Devices and Circuits

Diodes - 2

Prepared By:

**Shadman Shahid (SHD)**


Lecturer, Department of Computer Science and Engineering, School of Data and Sciences, BRAC University

*Email: [shadman9085@gmail.com](mailto:shadman9085@gmail.com)*


# Outline

- **Diode Models and IV Characteristics: Review**
- **Diode Logic OR operation**
- **Diode Logic AND operation**



# Review: Ideal Diode Model

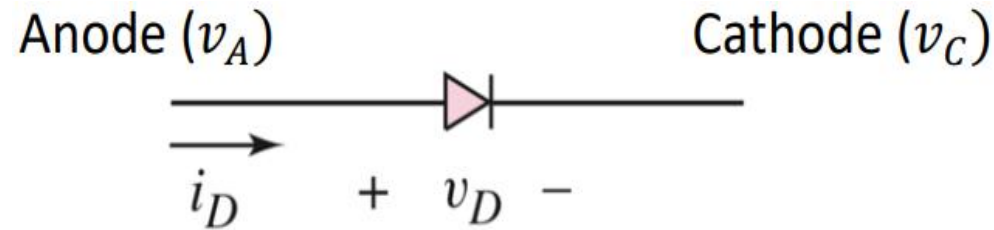

**OFF State: Open circuit**

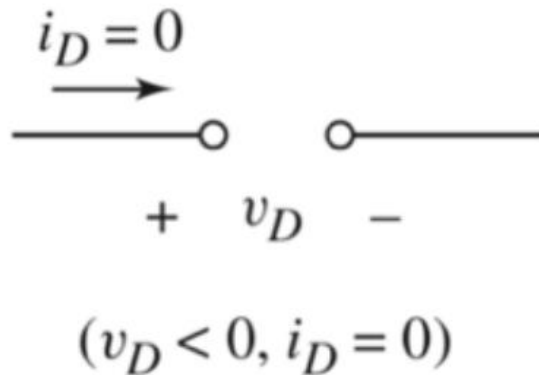


**ON State: Short circuit**

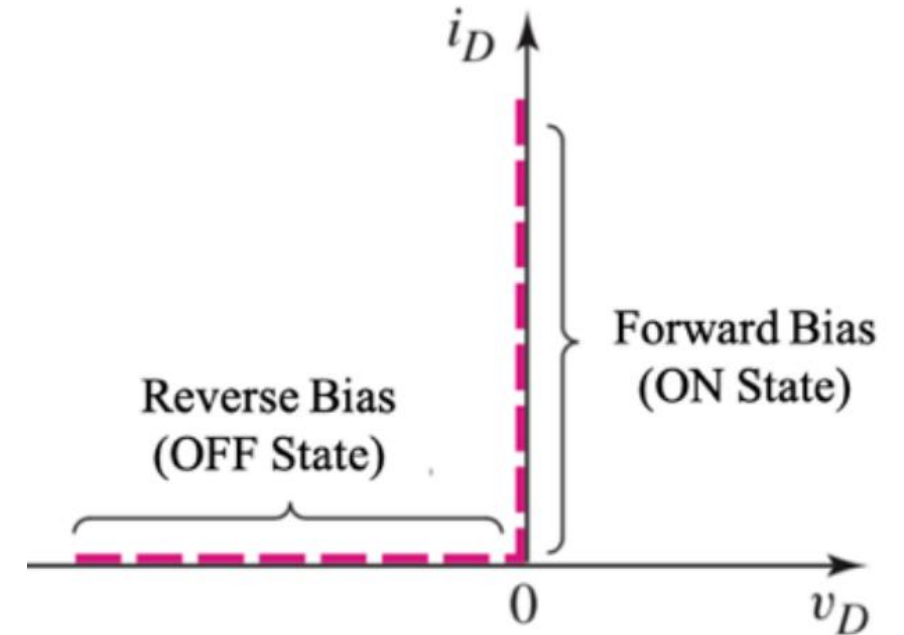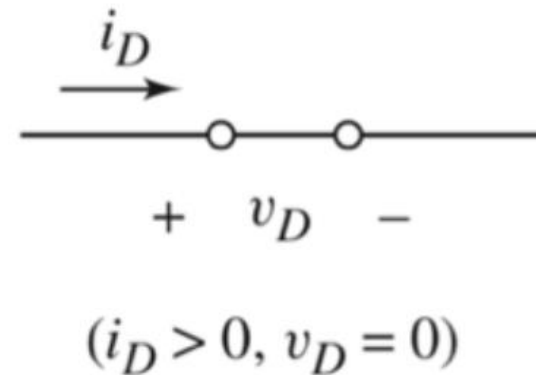


# Modeling the real diode

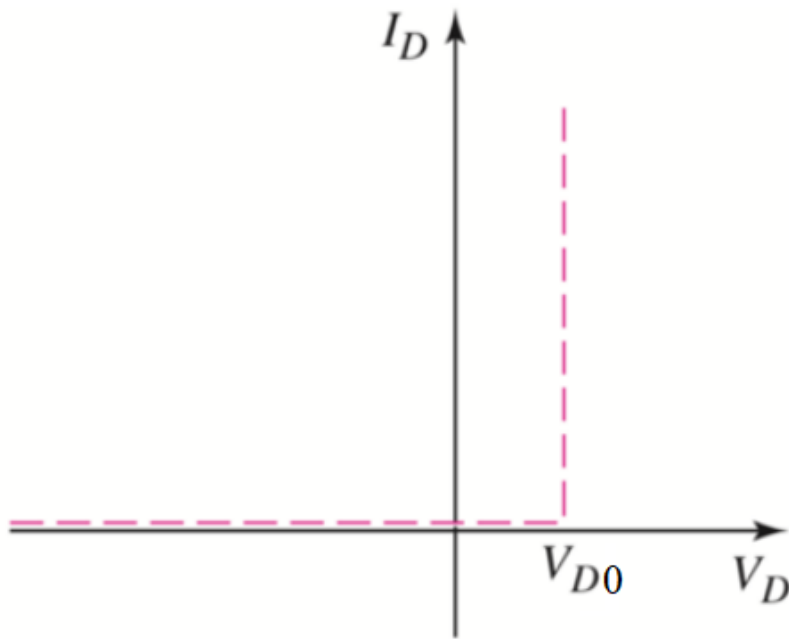1. Ideal diode model
- 2. Constant voltage drop (CVD) model**
3. CVD+R model




**OFF State: Open circuit**

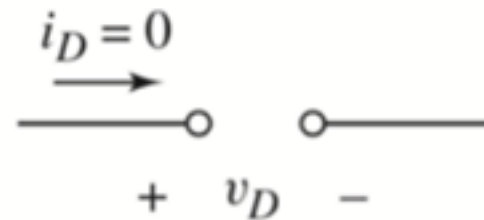

$$(v_D < V_{D0}, i_D = 0)$$


**ON State: Voltage source**

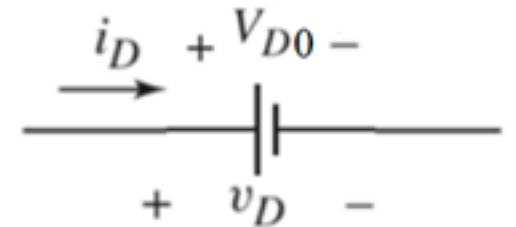


$$(i_D > 0, v_D = V_{D0})$$

# Modeling the real diode

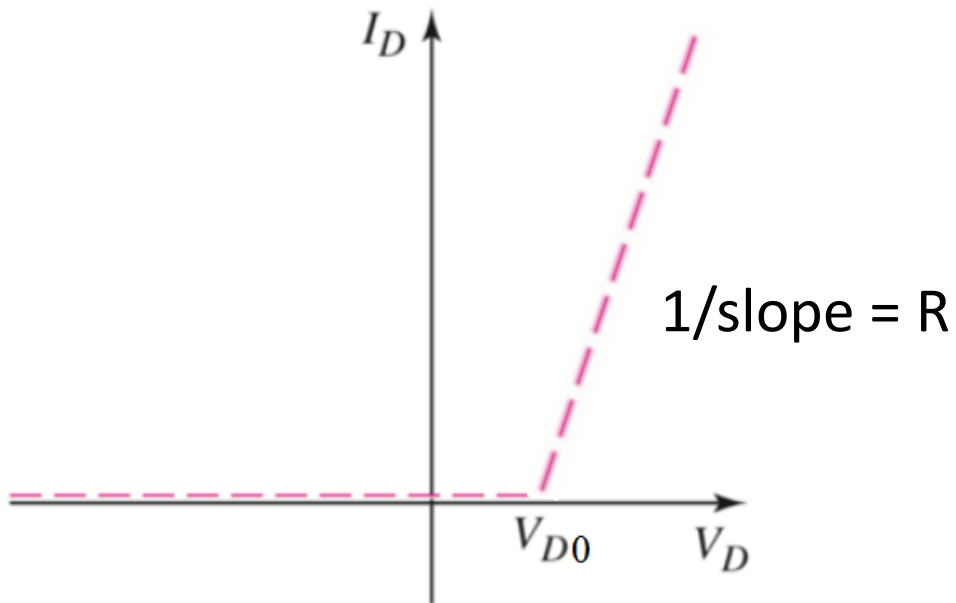1. Ideal diode model
2. Constant voltage drop (CVD) model
- 3. CVD+R model**




**OFF State: Open circuit**

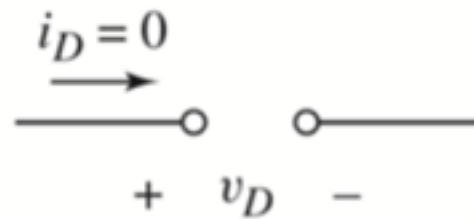

$$(v_D < V_{D0}, i_D = 0)$$

**ON State: Voltage source**

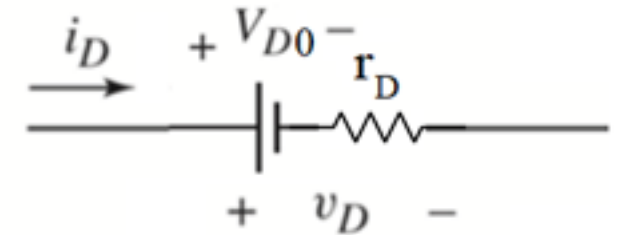

$$(i_D > 0, v_D = V_{D0} + i_D r_D)$$

# Digital Representation

- Binary  $\rightarrow$  Two states (0/False, 1/True)
- Binary variables in circuit, need to use two states of device/parameters

Voltage	Current	State
5V $\rightarrow$ 1		
0V $\rightarrow$ 0		

# Logical Operations with Diode (OR)

Logic Truth Table

INPUTS		OUTPUT
X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

Voltage Truth Table

INPUTS		OUTPUT
X	Y	Z
0 V	0 V	0 V
0 V	5 V	5 V
5 V	0 V	5 V
5 V	5 V	5 V

Logic Levels:

Corresponding voltage levels:

Low/False

0

0V

High/True


1

5V

# Logical Operations with Diode (OR)

Voltage Truth Table

INPUTS		OUTPUT
X	Y	Z
0 V	0 V	0 V
0 V	5 V	5 V
5 V	0 V	5 V
5 V	5 V	5 V

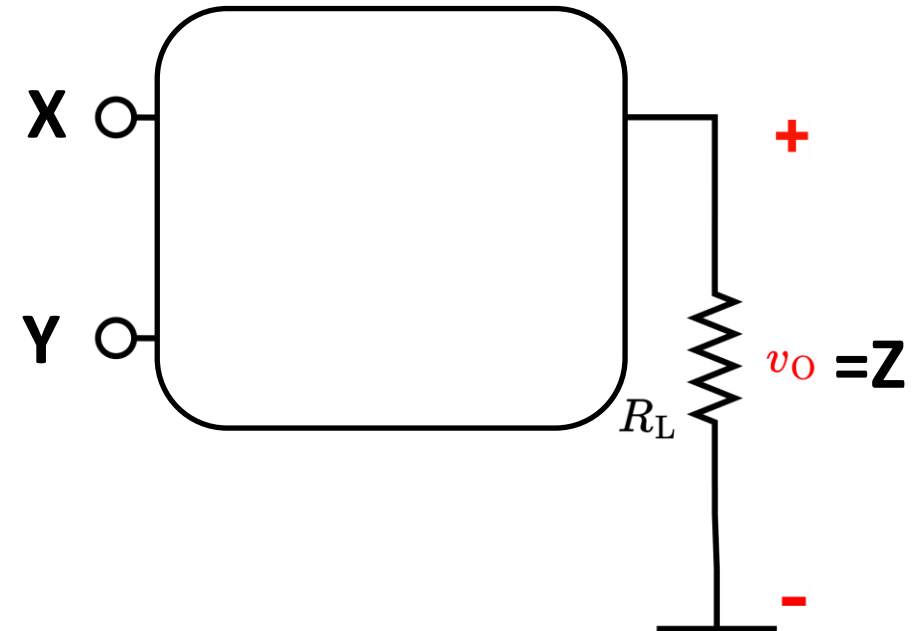

## PULL DOWN NETWORK



When all inputs are completely disconnected,  $v_O$  is pulled down to **GND**

Degrades the HIGHEST output voltage



# Logical Operations with Diode (OR)

## Ideal diode

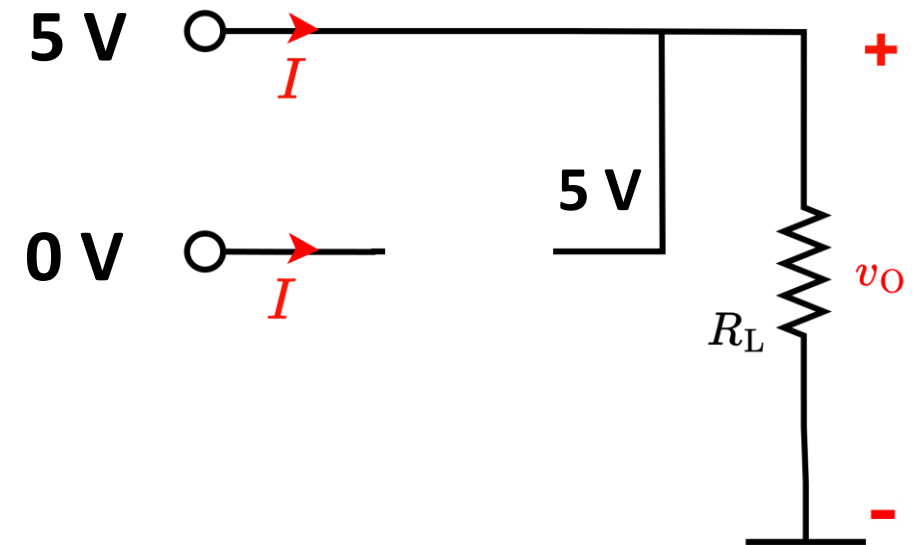
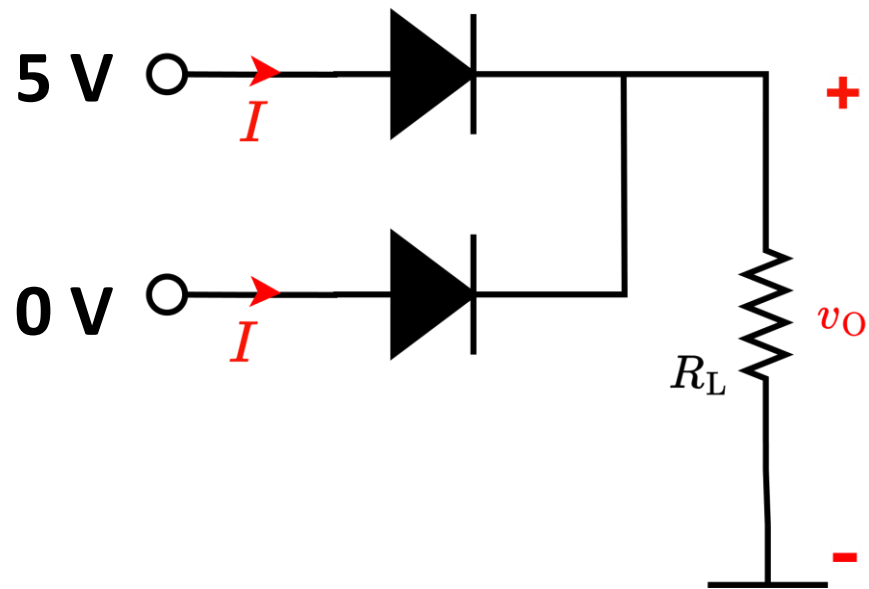


$$Z = 5\text{ V}$$



# Logical Operations with Diode (OR)

## CVD diode

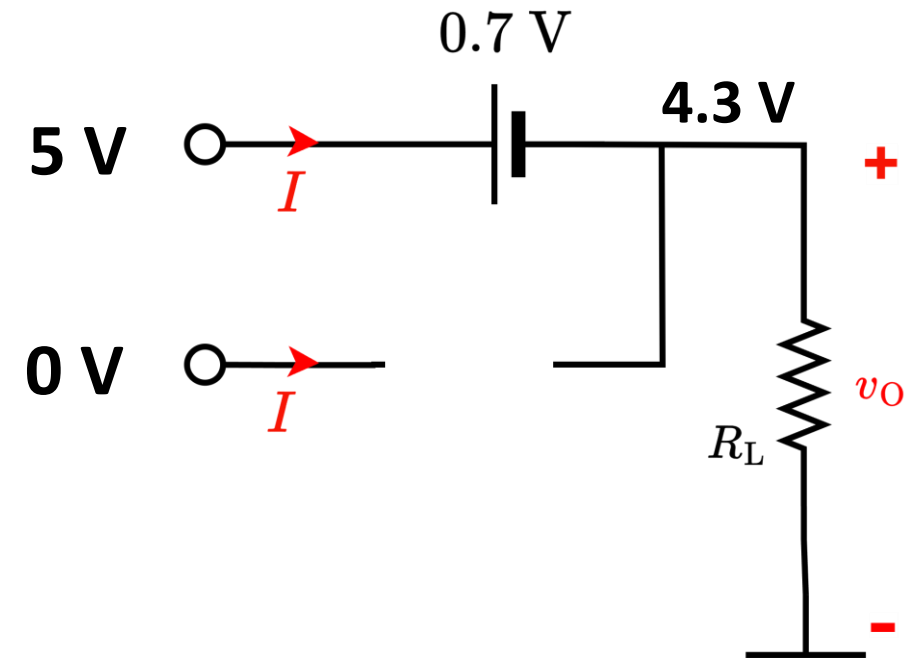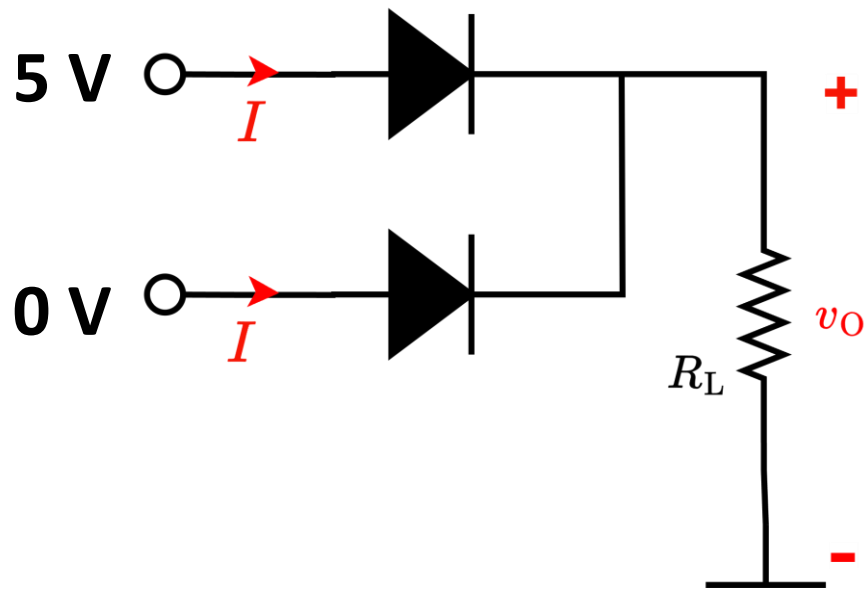



$$Z = 4.3\text{ V}$$

Degraded  $5\text{ V}$



# Logical Operations with Diode (OR)

## Ideal diode

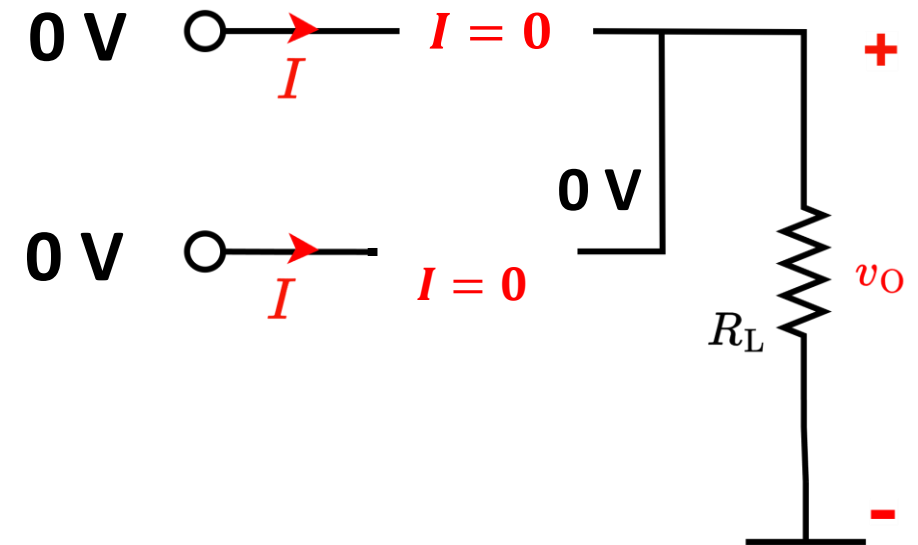
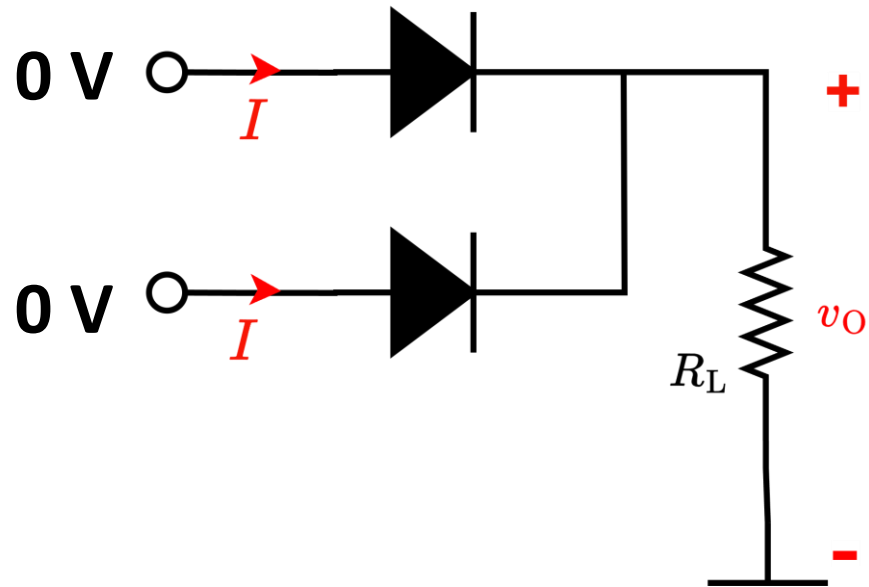


$$Z = 0\text{ V}$$



# Logical Operations with Diode (OR)

## CVD diode

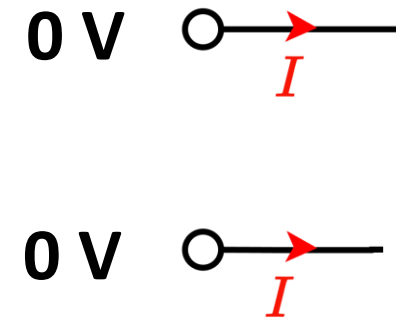
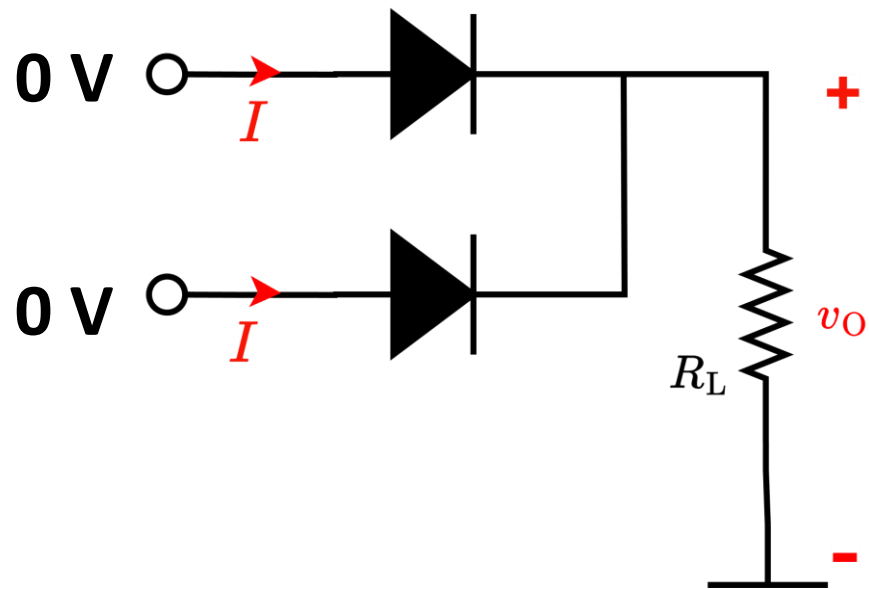


$$Z = 0\text{ V}$$



# Logical Operations with Diode (OR)

## Ideal diode

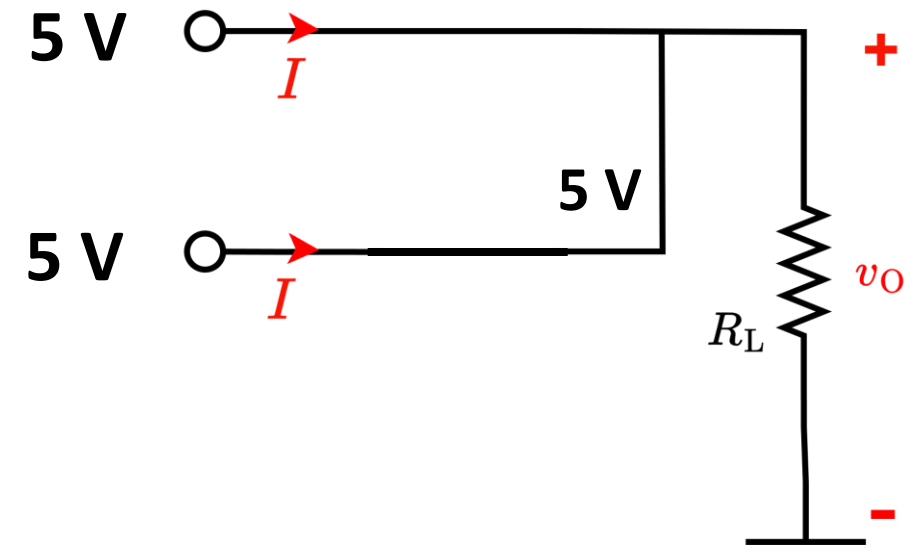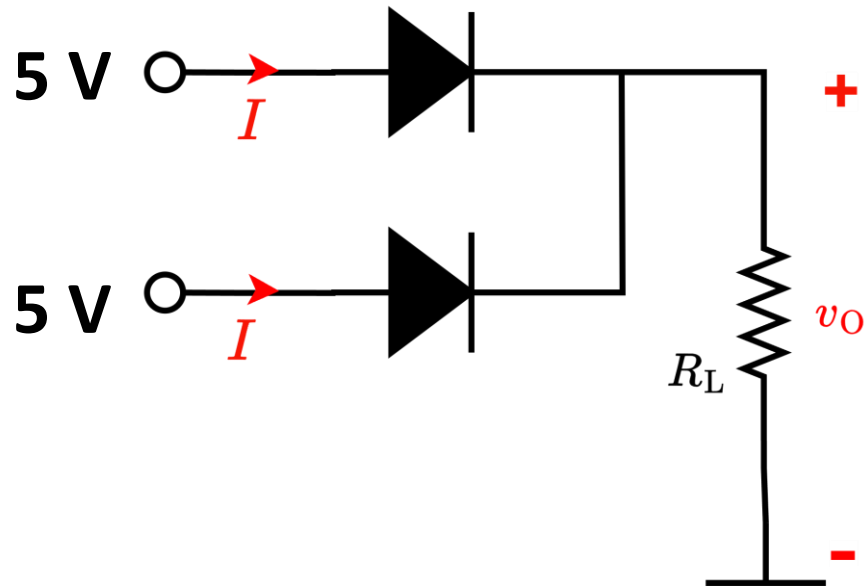


$$Z = 5 \text{ V}$$



# Logical Operations with Diode (OR)

## CVD diode

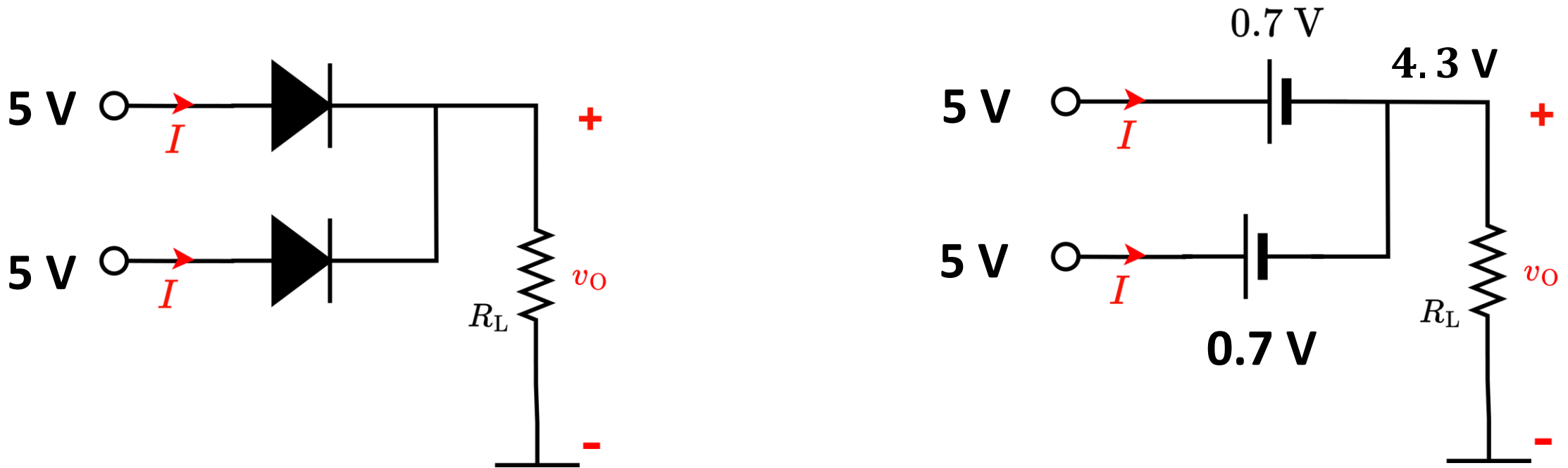

$$Z = 4.3 \text{ V}$$

Degraded 5 V

Both diodes have same  $V_{DO}$

# Logical Operations with Diode (OR)


## CVD diode

What if the diodes have different  $V_{DO}$ ?

$$V_{D1} = 1 \text{ V}$$

$$V_{D2} = 0.7 \text{ V}$$

$$V_{D3} = 0.5 \text{ V}$$

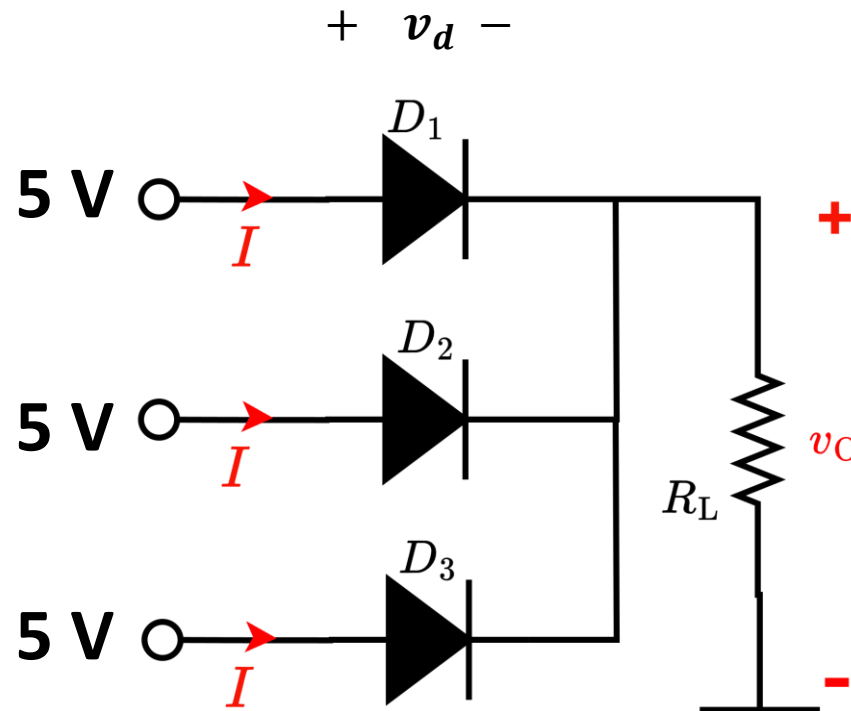

# Logical Operations with Diode (OR)


## CVD diode

What if two diodes have different  $V_{D0}$ ?

$$V_{D1} = 1 \text{ V}$$

$$V_{D2} = 0.7 \text{ V}$$

$$V_{D3} = 0.5 \text{ V}$$

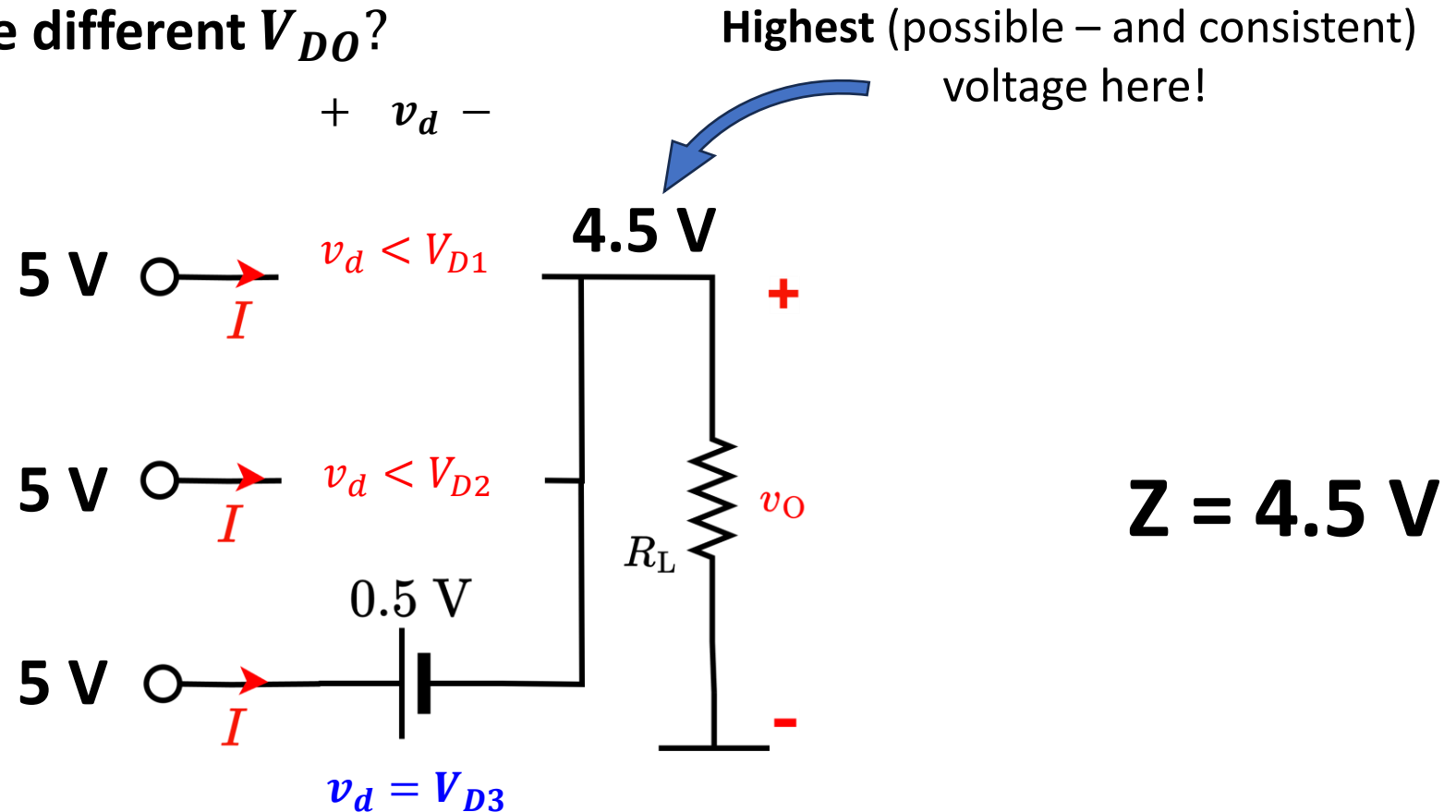



# Logical Operations with Diode (OR)


## CVD diode

What if the input voltages are different?

$$V_{D1} = 1 \text{ V}$$

$$V_{D2} = 0.7 \text{ V}$$


$$V_{D3} = 0.5 \text{ V}$$

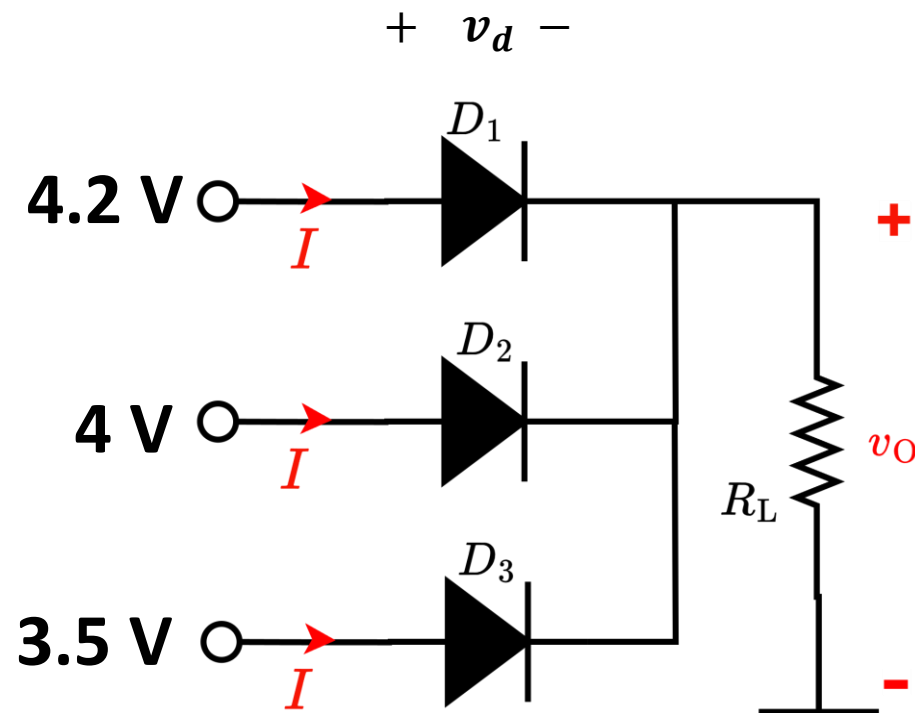

# Logical Operations with Diode (OR)
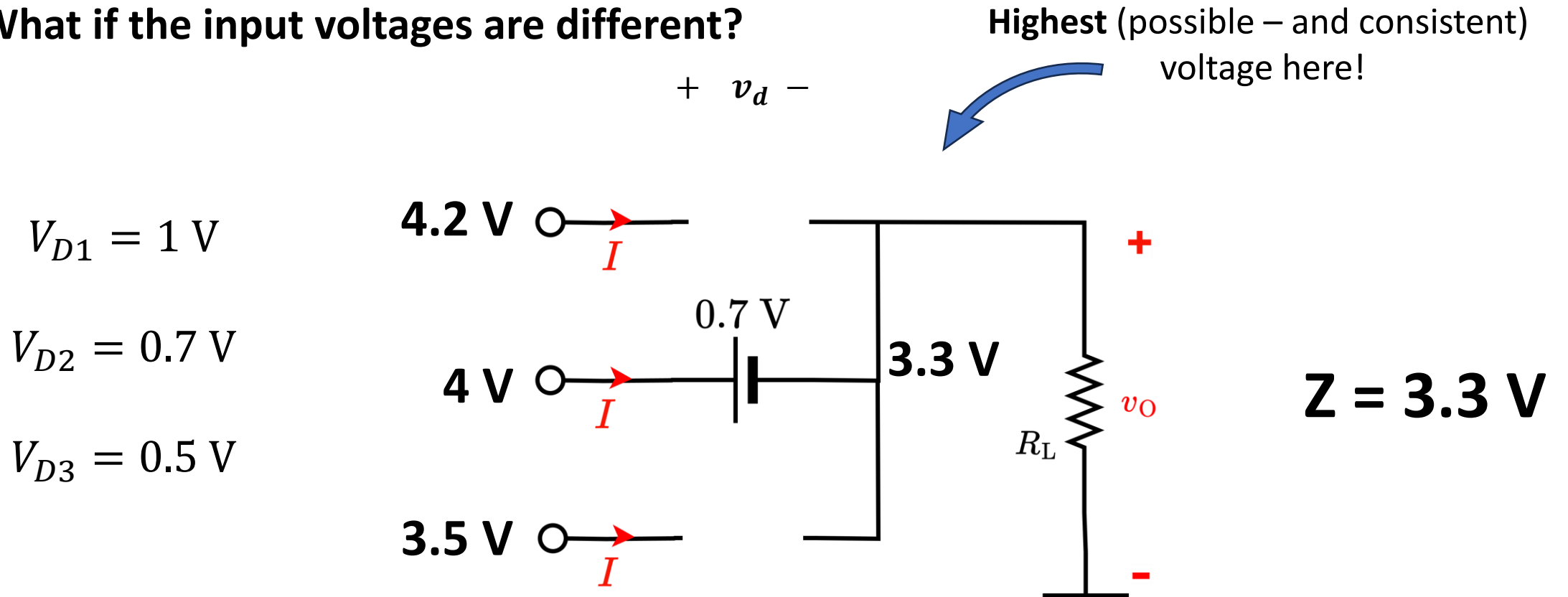
## CVD diode

What if the input voltages are different?



# Logical Operations with Diode (AND)

Logic Truth Table

INPUTS		OUTPUT
X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

Logic Levels:

Corresponding voltage levels:

Low/False

0

0V

Voltage Truth Table

INPUTS				OUTPUT
X		Y		Z
0	V	0	V	0 V
0	V	5	V	0 V
5	V	0	V	0 V
5	V	5	V	5 V

High/True


1

5V

# Logical Operations with Diode (AND)

Voltage Truth Table

INPUTS				OUTPUT
X		Y		Z
0 V	0 V	0 V	0 V	0 V
0 V	5 V	5 V	0 V	0 V
5 V	0 V	0 V	5 V	0 V
5 V	5 V	5 V	5 V	5 V

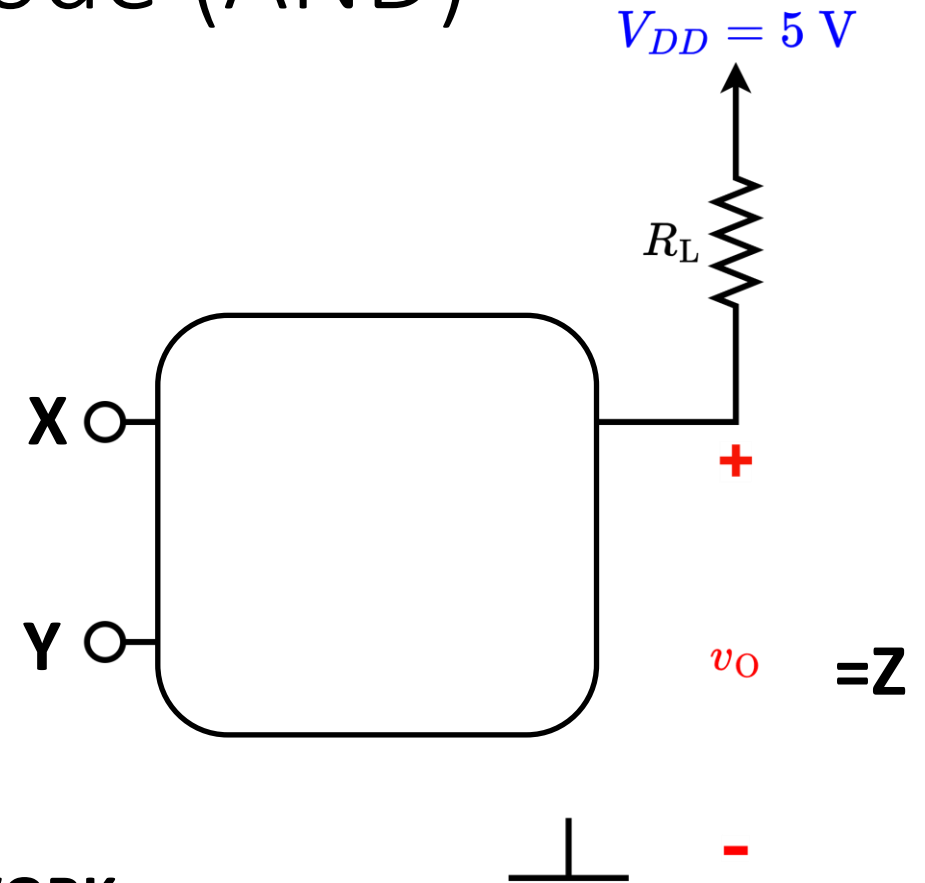


## PULL UP NETWORK

When all inputs are completely disconnected,  $v_O$  is pulled up to  $V_{DD}$


Degrades the LOWEST output voltage

# Logical Operations with Diode (AND)

## Ideal diode

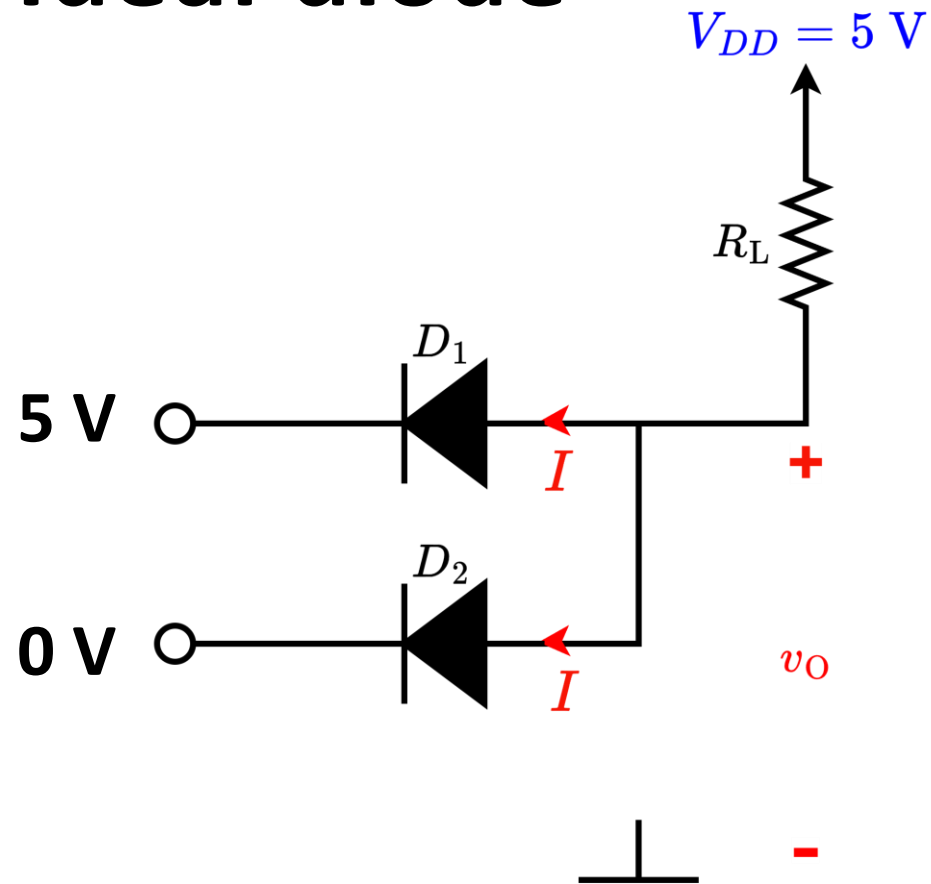


$$Z = 0\text{ V}$$

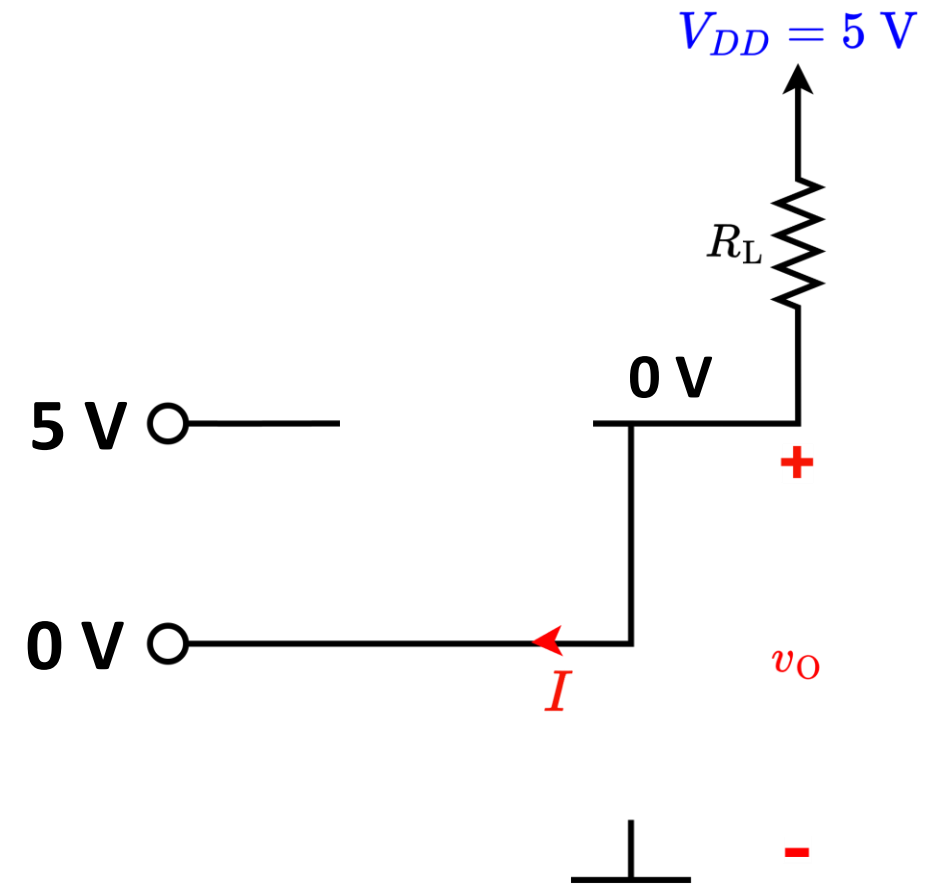


# Logical Operations with Diode (AND)

## CVD diode

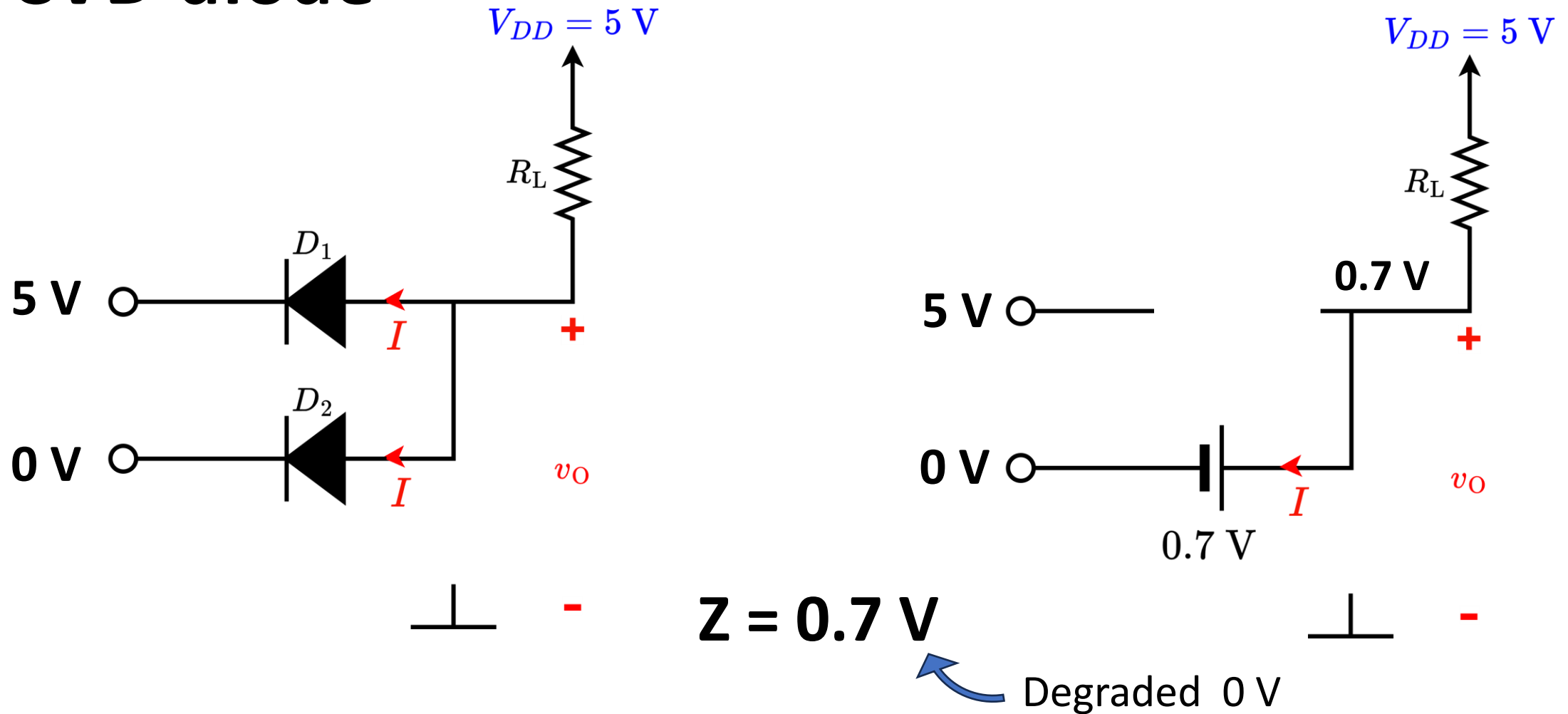


# Logical Operations with Diode (AND)

## Ideal diode


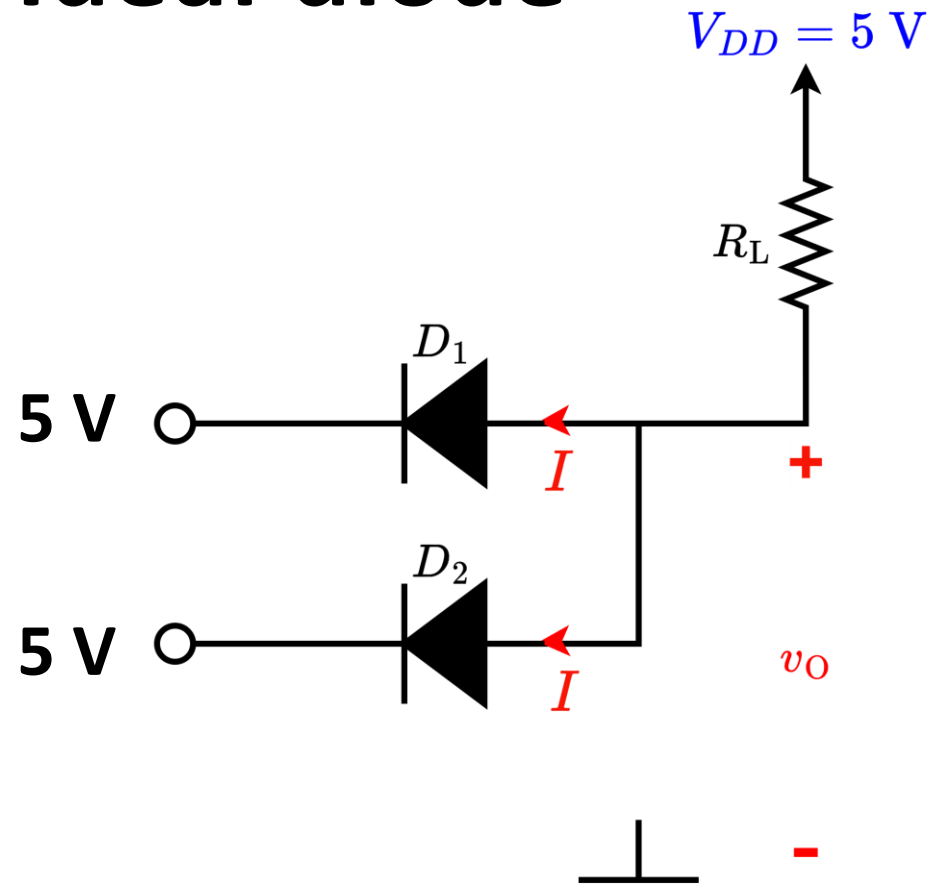


$$Z = 5\text{ V}$$

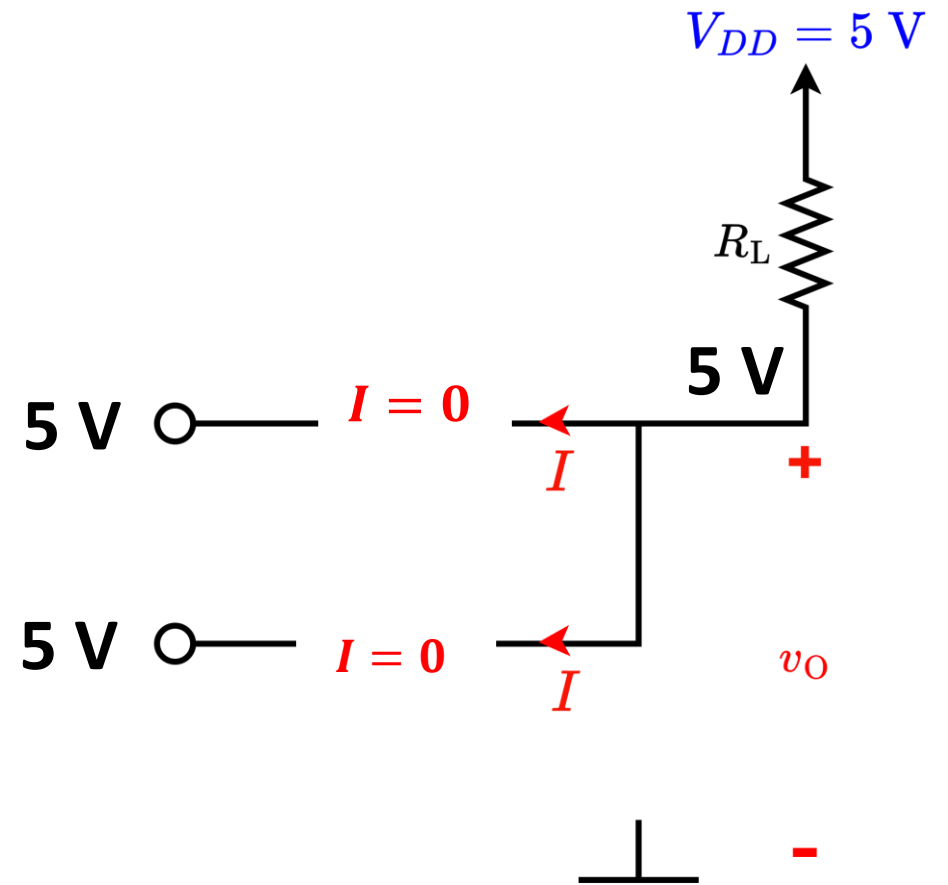

# Logical Operations with Diode (AND)



## CVD diode

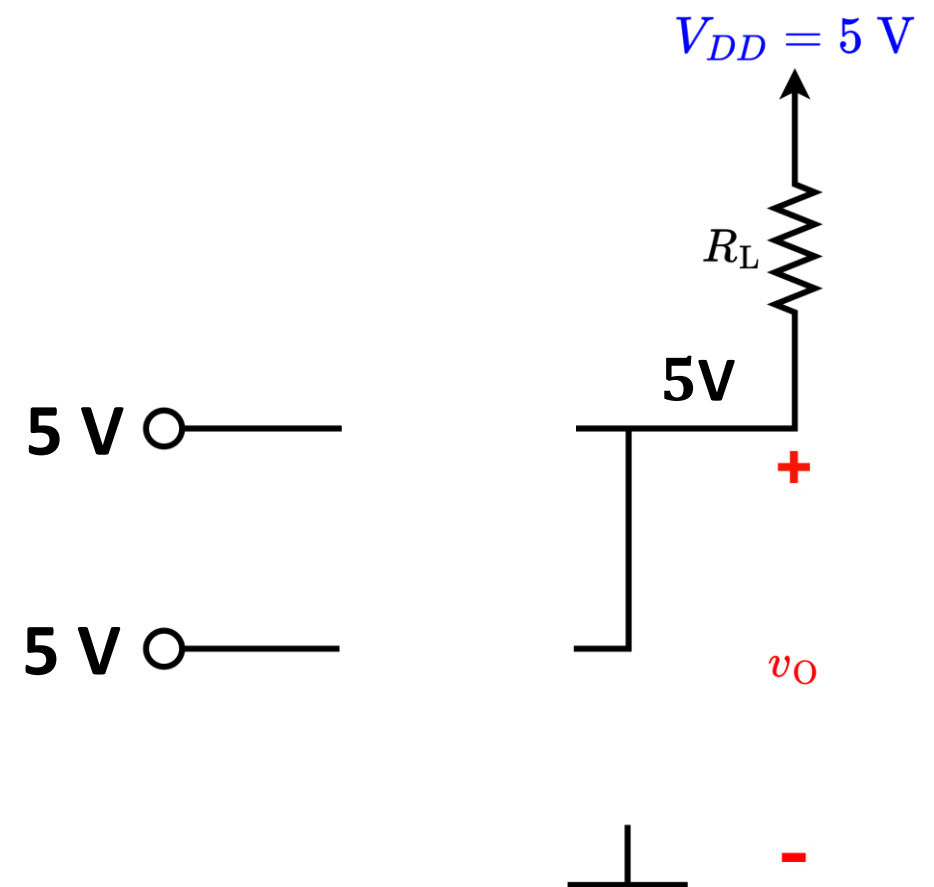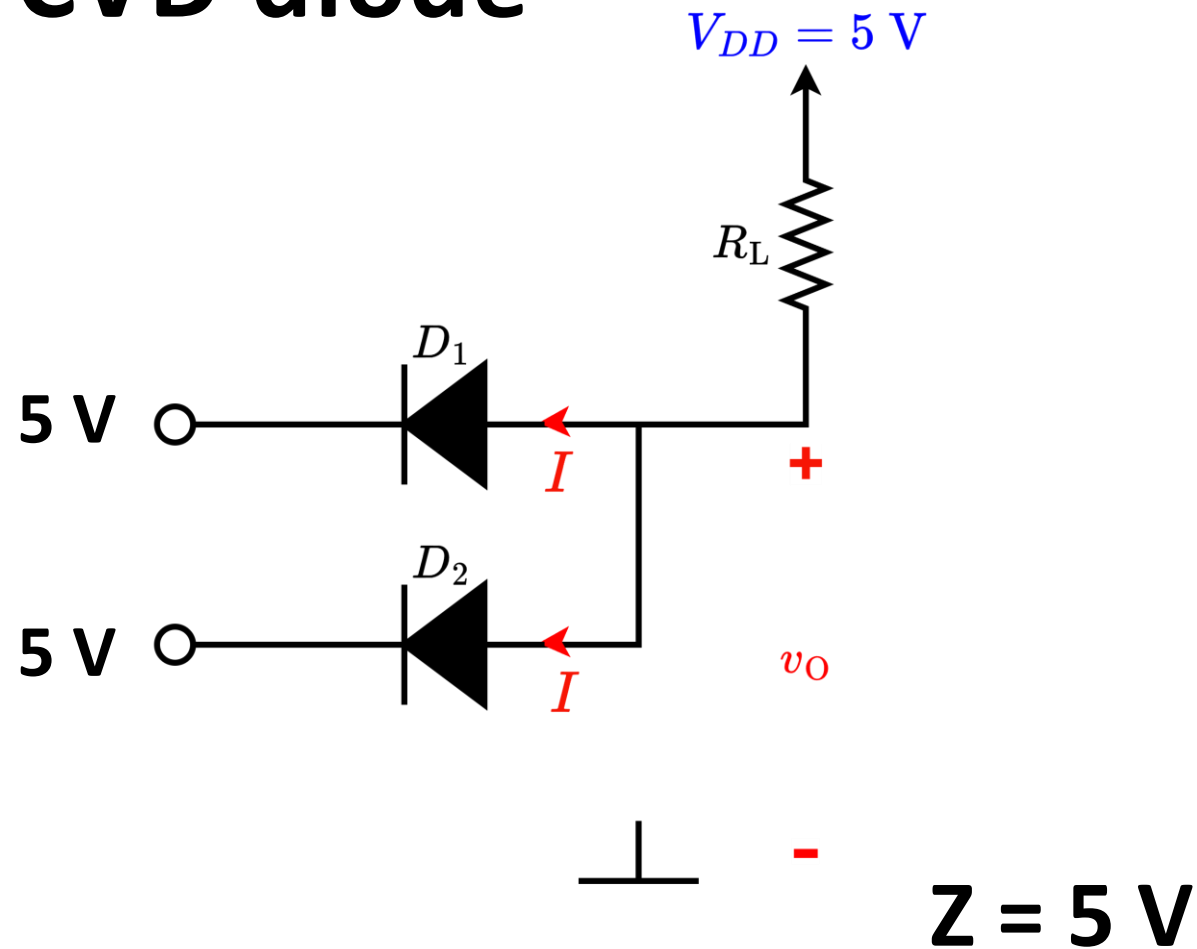



# Logical Operations with Diode (AND)


## Ideal diode

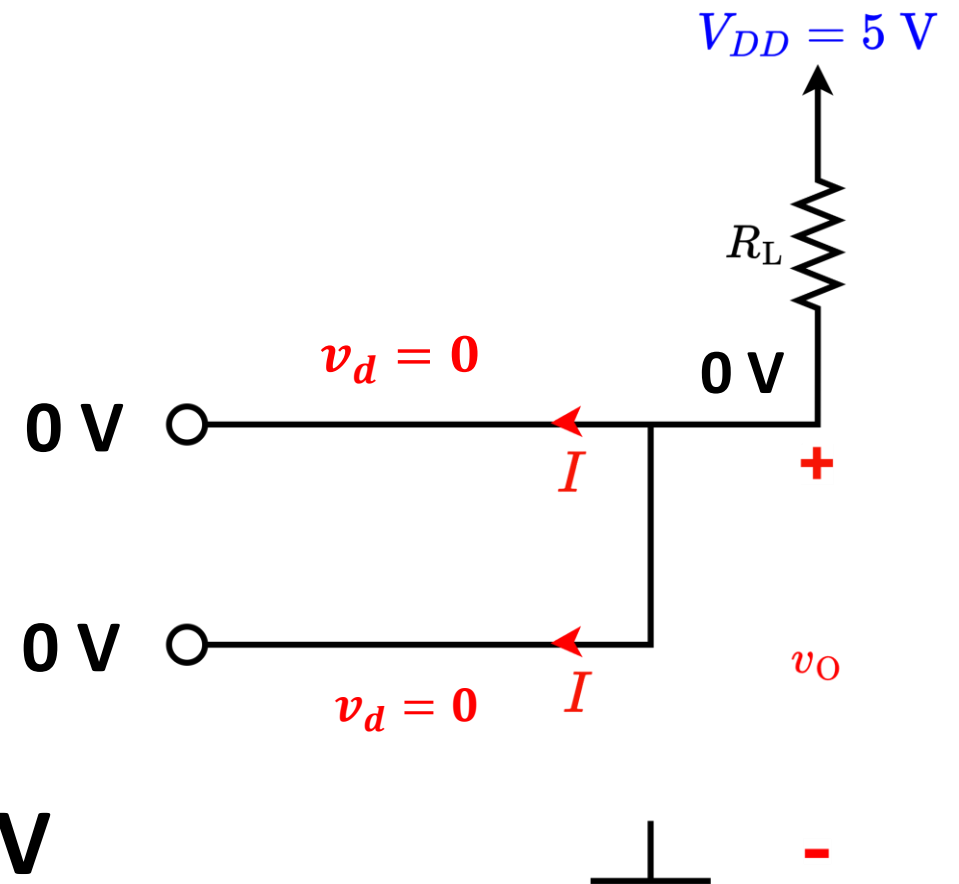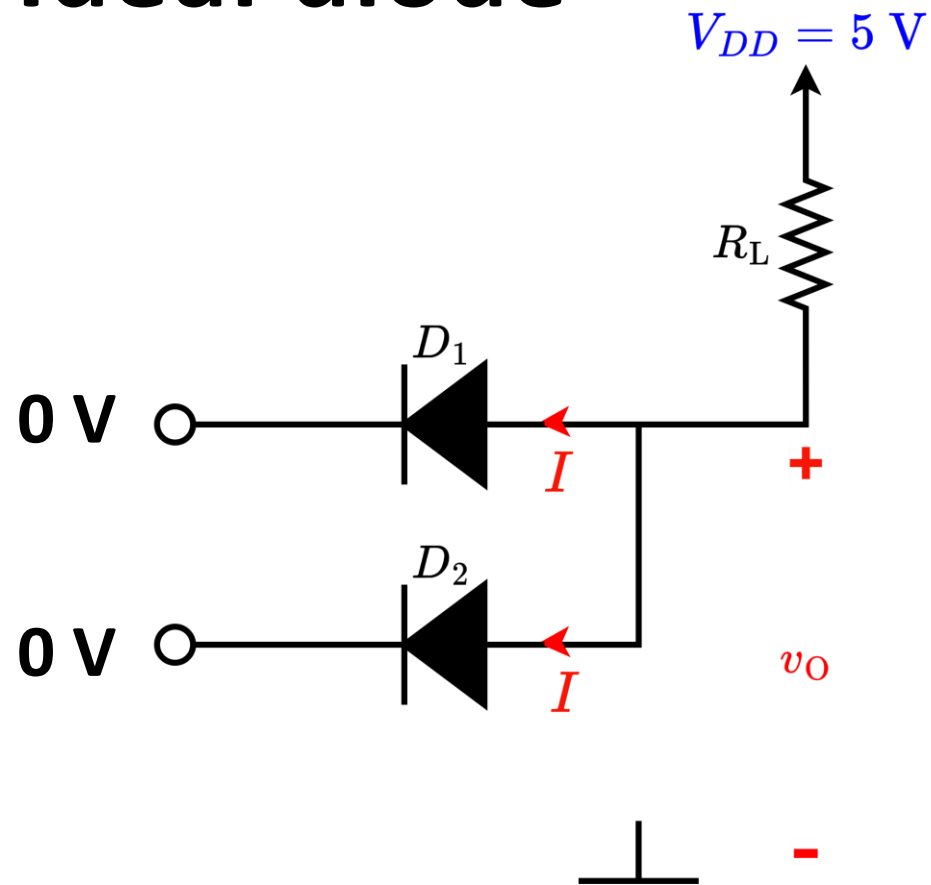


$$Z = 0\text{ V}$$

# Logical Operations with Diode (AND)

## CVD diode

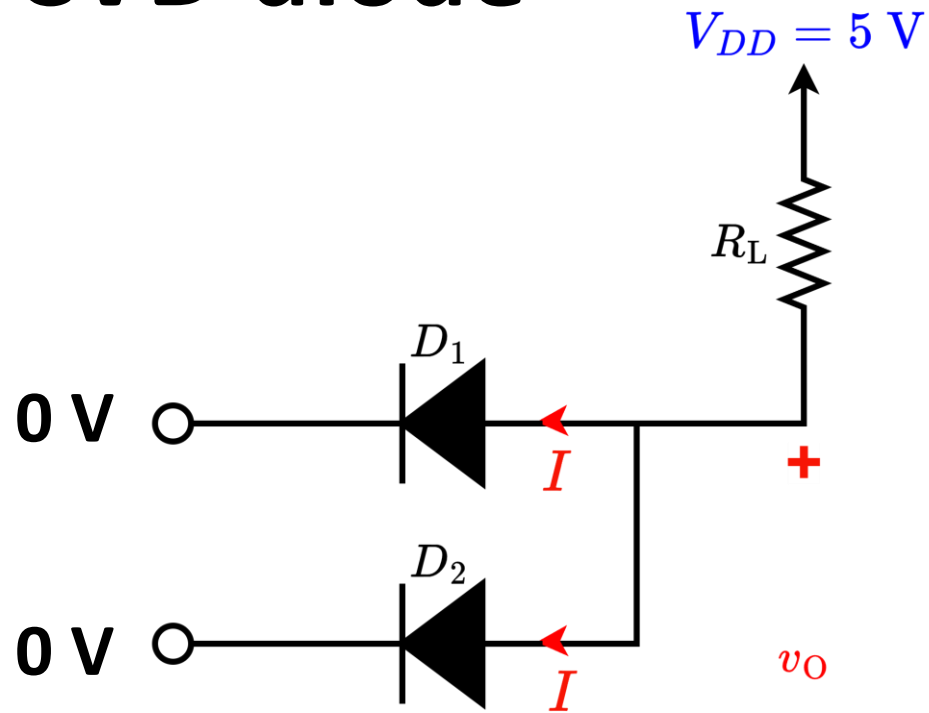

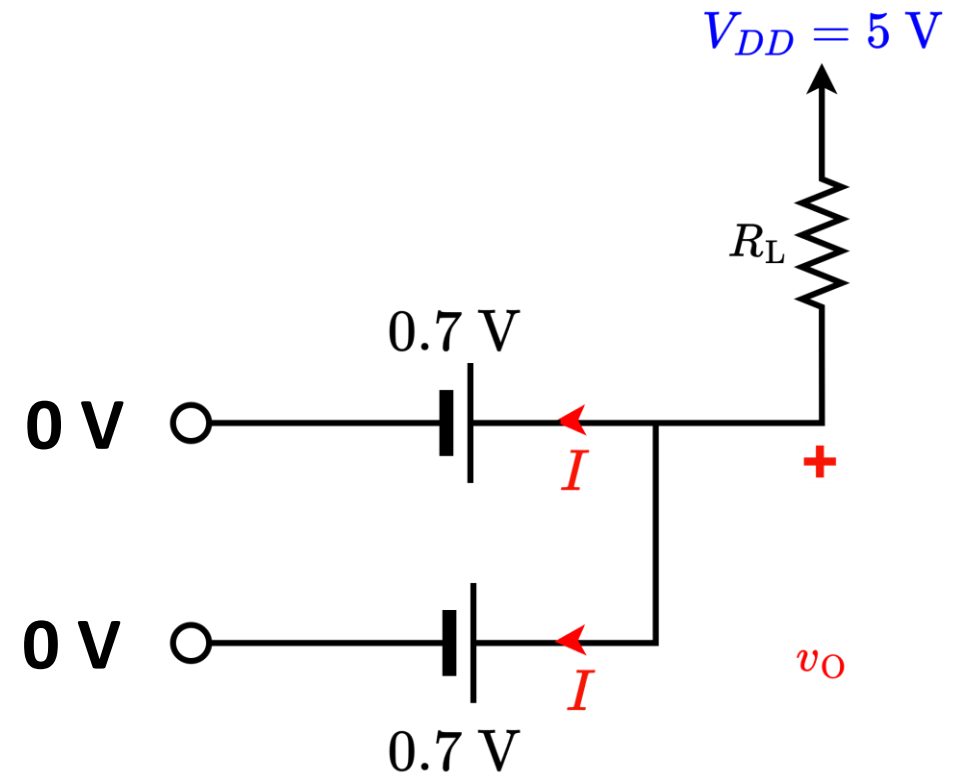$\perp$  -  **$Z = 0.7\text{ V}$**   
Degraded  $0\text{ V}$



$\perp$  - Both diodes have same  $V_{DO}$

# Logical Operations with Diode (AND)


## CVD diode

What if the diodes have different  $V_{DO}$ ?

$$V_{D1} = 1 \text{ V}$$

$$V_{D2} = 0.7 \text{ V}$$

$$V_{D3} = 0.5 \text{ V}$$

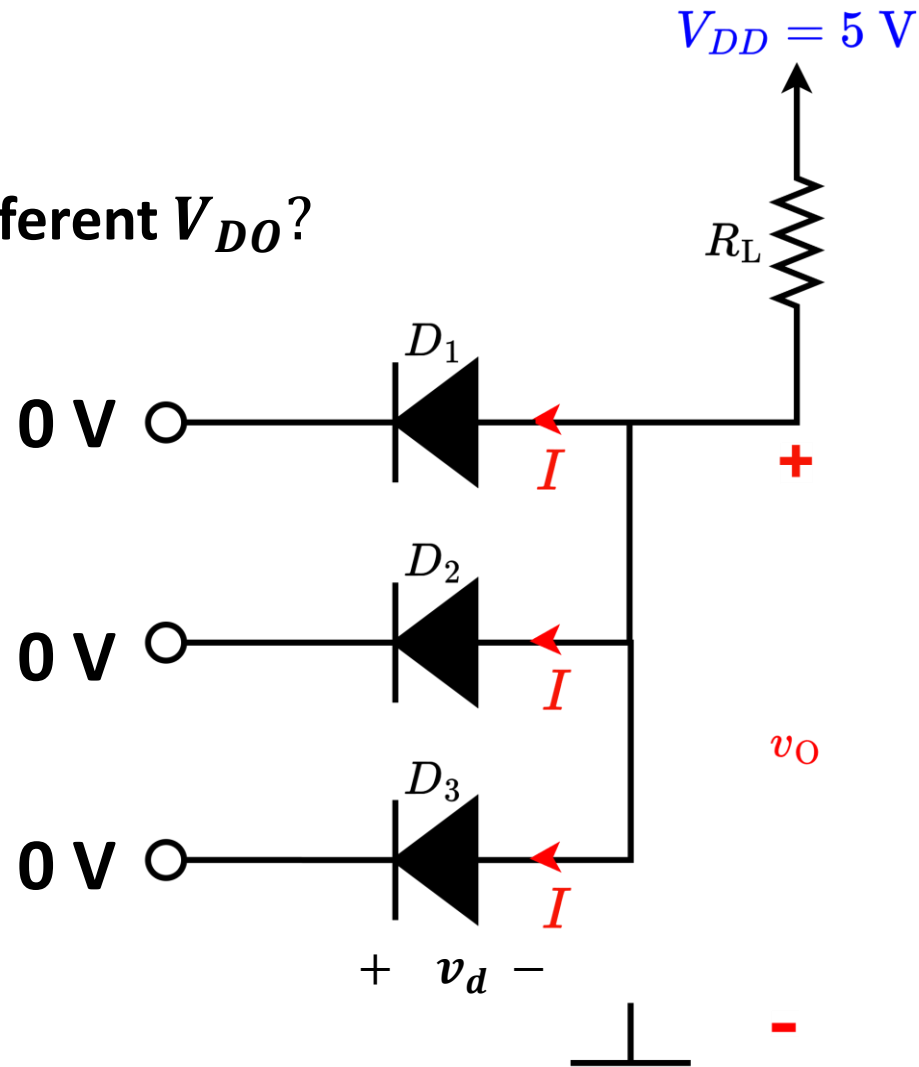

# Logical Operations with Diode (AND)


## CVD diode

What if the diodes have different  $V_{DO}$ ?

$$V_{D1} = 1 \text{ V}$$

$$V_{D2} = 0.7 \text{ V}$$

$$V_{D3} = 0.5 \text{ V}$$

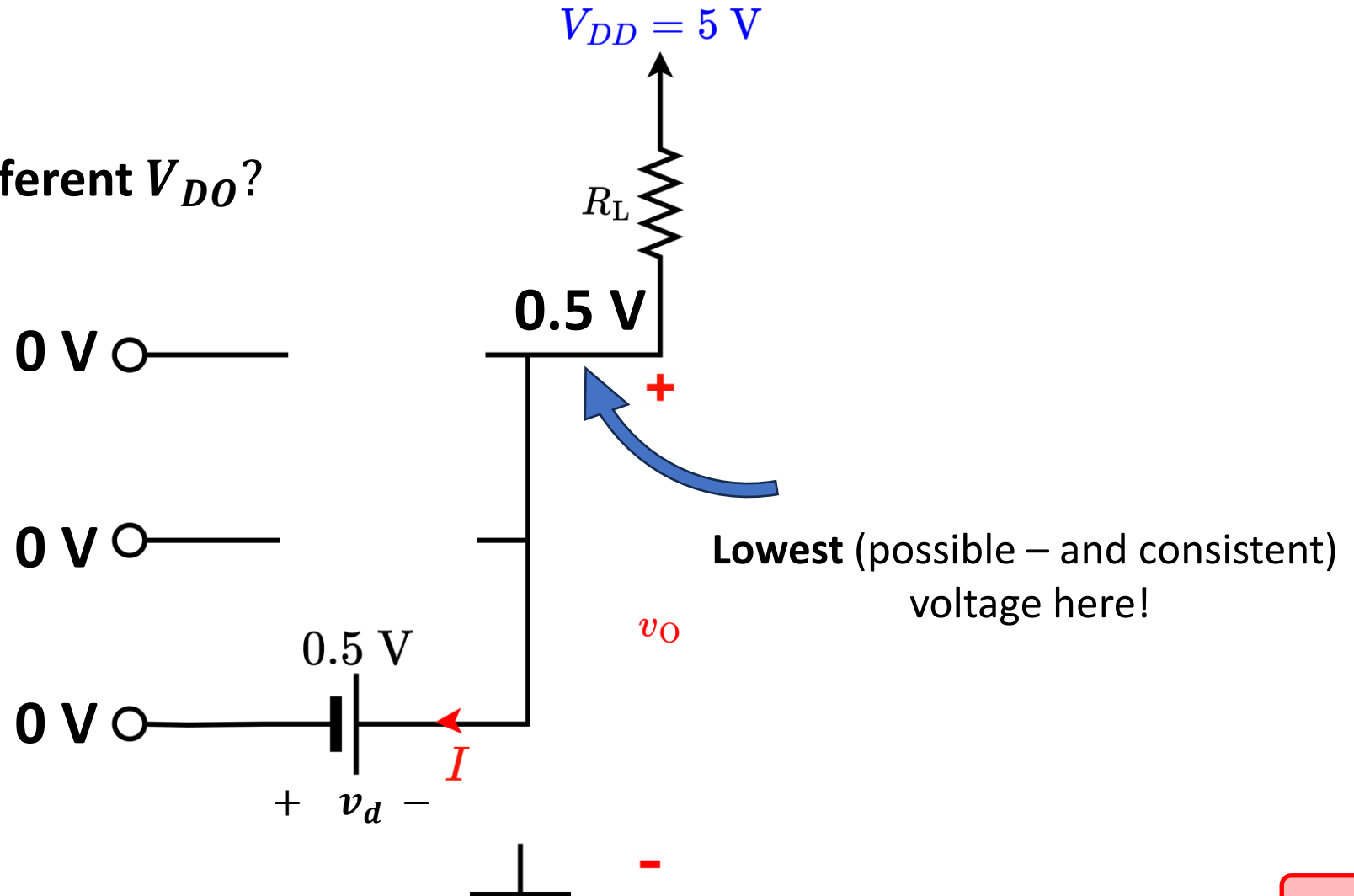


Part 1 ends here

# Outline

- **Diode Logic Gates – Examples and combined operation**

# Effect of input Voltage Variation in Logic Gates (AND)

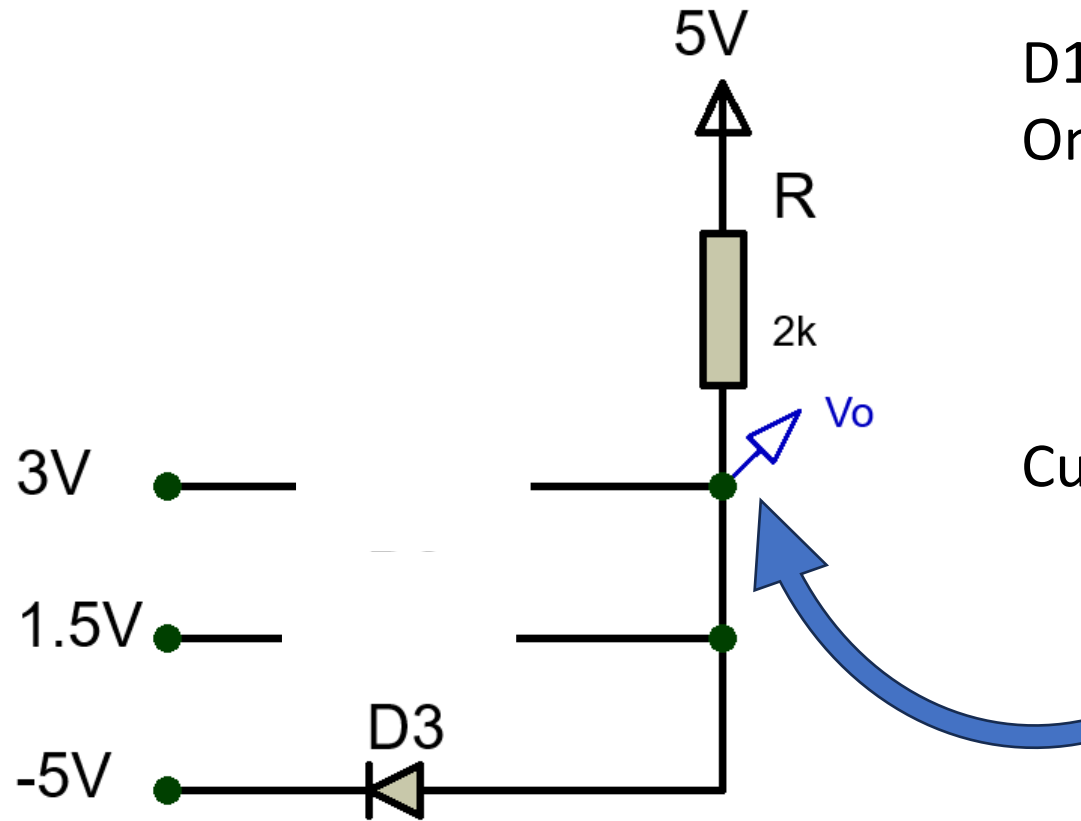Example 1: Find the value of  $V_o$  (All the diodes are ideal diodes)




D1 and D2 are OFF  $\rightarrow$  Open Circuit  
Only D3 is ON  $\rightarrow$  Short Circuit

$$V_o = -5 \text{ V}$$

$$\text{Current, } I = \frac{5 \text{ V} - (-5 \text{ V})}{2 \text{ k}\Omega} = 5 \text{ mA}$$

**Lowest** (possible – and consistent)  
voltage here!

# Combined Logic Circuits

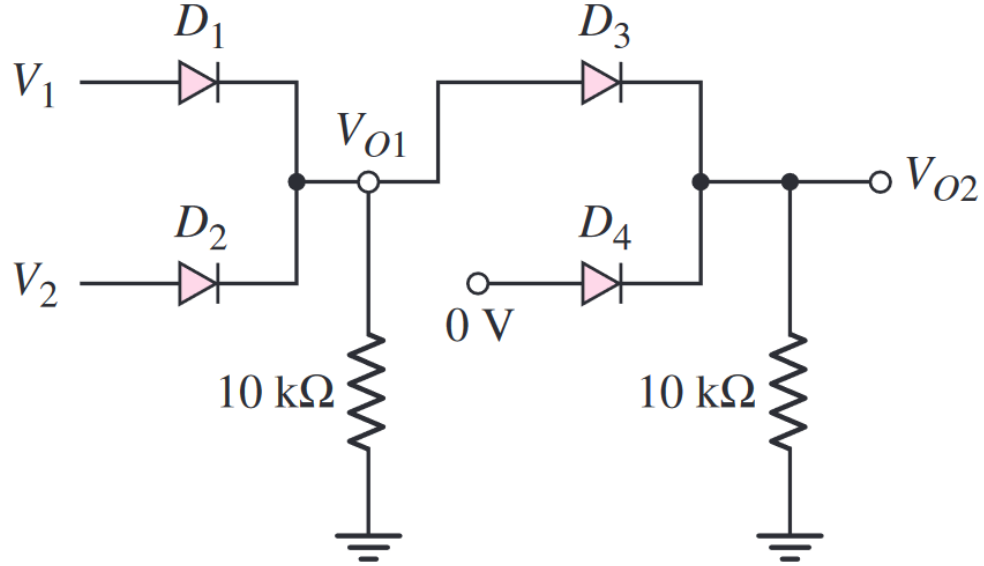


$$V_{O1} = V_1 \text{ OR } V_2 = V_1 | V_2$$

$$V_{O2} = (V_{O1} \text{ OR } 0) = V_{O1} = V_1 | V_2$$



# Combined Logic Circuits

Example 2:

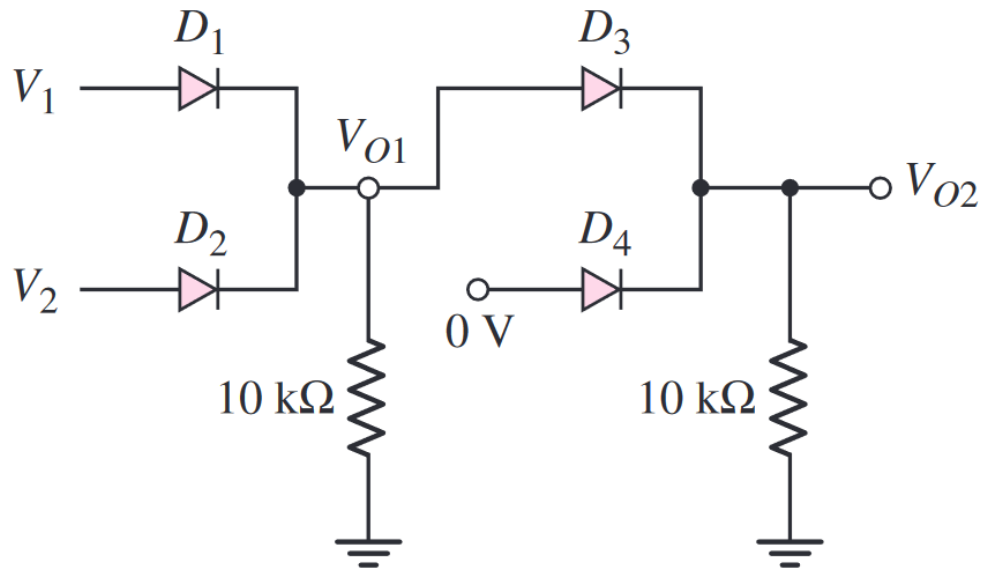

\*\* In CVD diode models, we are assuming that all diodes have equal drop.

**Suppose:  $V_1 = 3\text{ V}$ ,  $V_2 = 2\text{ V}$ .**

**For Ideal diodes assumption:**

$$V_{O1} = V_1 \text{ OR } V_2 \rightarrow \text{Largest Value of the inputs}$$

$$\therefore V_{O1} = 3\text{ V}$$

$$V_{O2} = (V_{O1} \text{ OR } 0) = V_{O1} = 3\text{ V}$$


**For CVD diodes assumption:**

$$V_{O1} = V_1 \text{ OR } V_2 \rightarrow \text{Largest Value of the inputs} - V_{DO}$$

$$\therefore V_{O1} = (3 - V_{DO})\text{ V}$$

$$V_{O2} = (V_{O1} \text{ OR } 0) = V_{O1} - V_{DO} = (3 - 2 V_{DO})\text{ V}$$

# Combined Logic Circuits

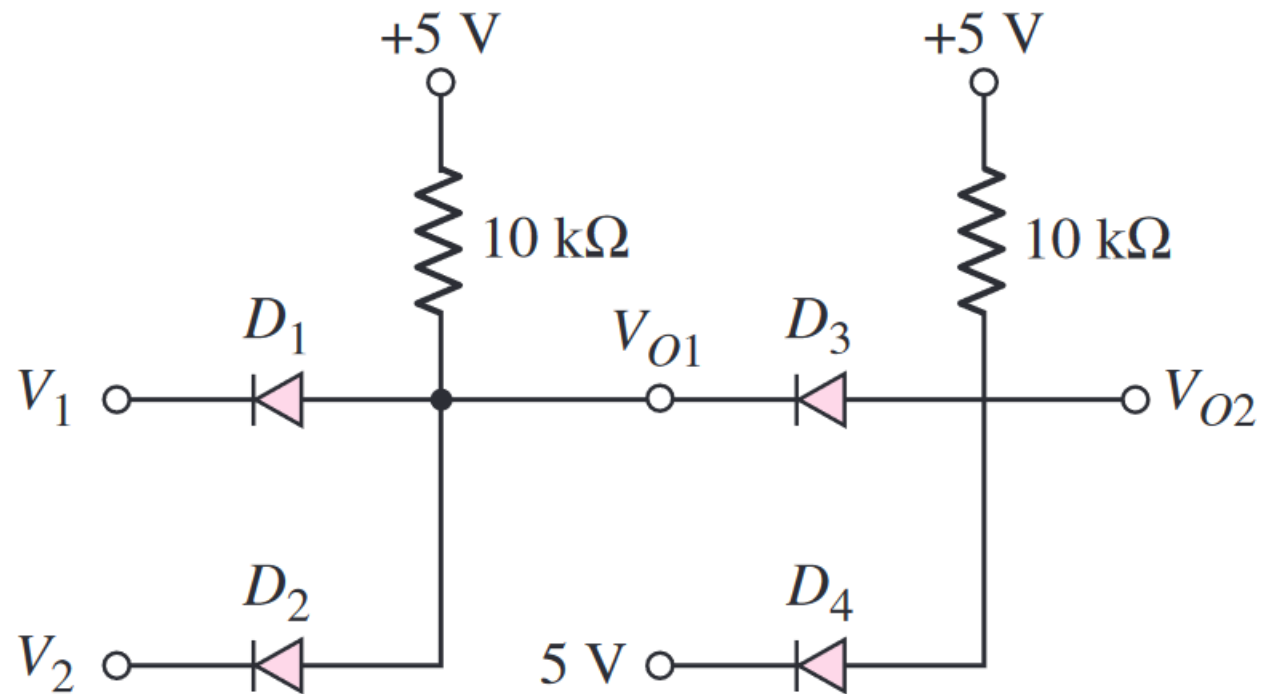


$$V_{O1} = V_1 \text{ AND } V_2 = V_1 \cdot V_2$$

$$V_{O2} = (V_{O1} \text{ AND } 5) = V_{O1} = V_1 \cdot V_2$$

# Combined Logic Circuits

Example 3:

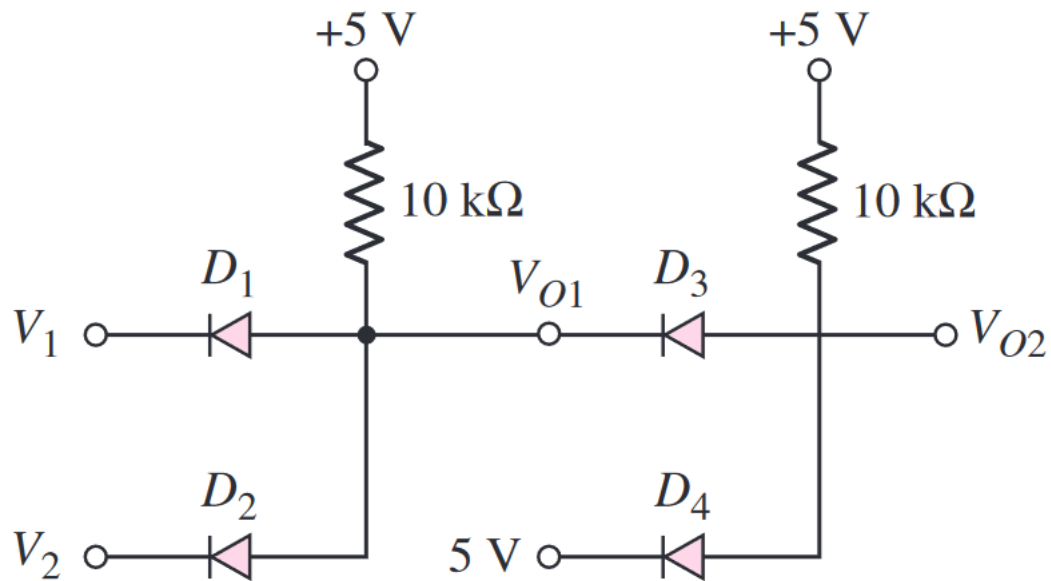

\*\* In CVD diode models, we are assuming that all diodes have equal drop.

**Suppose:  $V_1 = 3\text{ V}$ ,  $V_2 = 1.5\text{ V}$ .**

**For Ideal diodes assumption:**

$V_{O1} = V_1 \text{ AND } V_2 \rightarrow \text{Smallest Value of the inputs}$

$$\therefore V_{O1} = 1.5\text{ V}$$

$$V_{O2} = (V_{O1} \text{ AND } 5) = V_{O1} = \mathbf{1.5\text{ V}}$$

**For CVD diodes assumption:**


$V_{O1} = V_1 \text{ AND } V_2 \rightarrow \text{Smallest Value of the inputs} + V_{DO}$

$$\therefore V_{O1} = (1.5 + V_{DO})\text{ V}$$

$$V_{O2} = (V_{O1} \text{ AND } 5) = V_{O1} + V_{DO} = (\mathbf{1.5 + 2 V_{DO}})\text{ V}$$

# Combined Logic Circuits

Example 4:

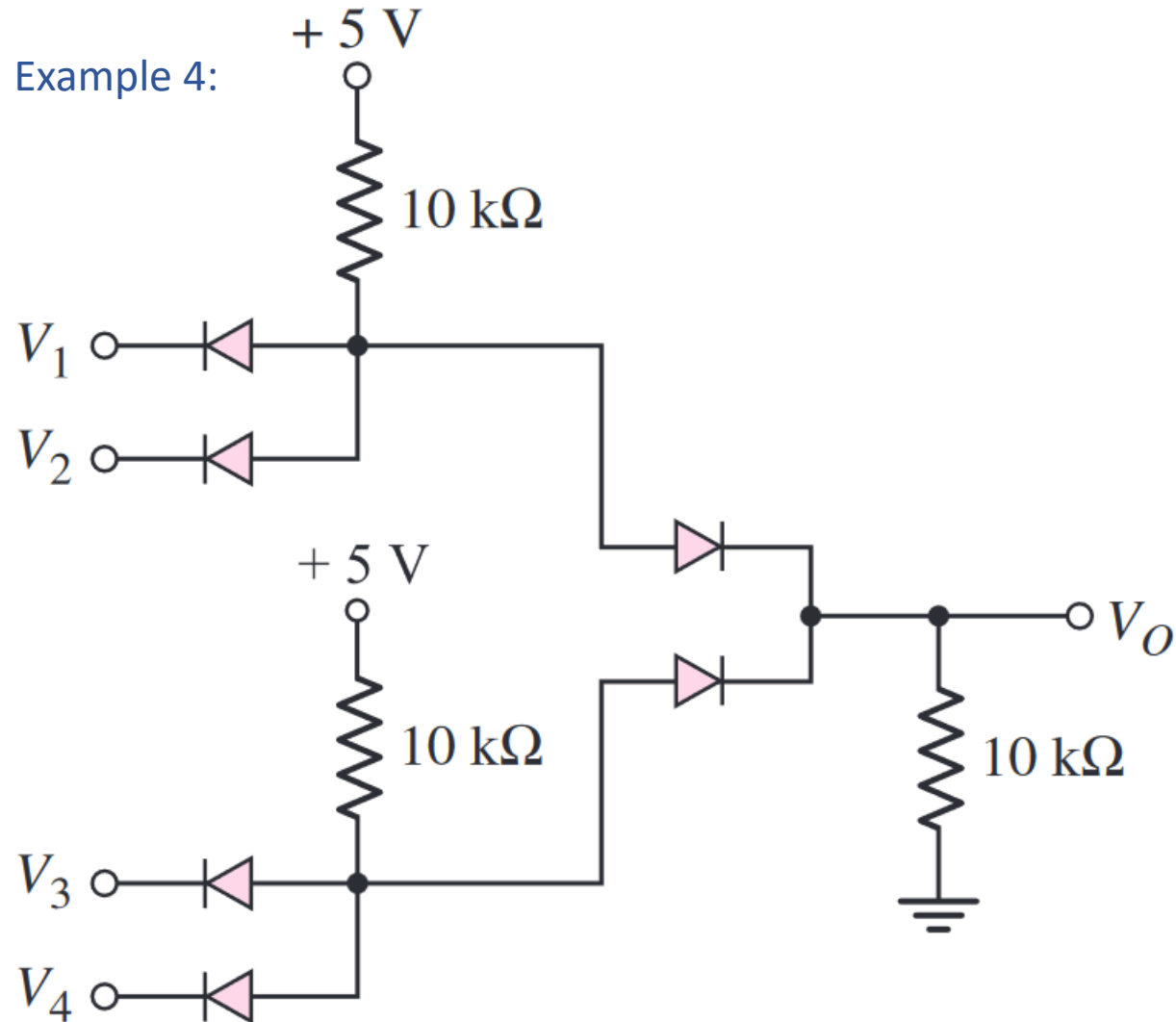

*Express  $V_O$  as a Boolean expression of  $V_1, V_2, V_3$  and  $V_4$*

$$V_O = (V_1 \cdot V_2) | (V_3 \cdot V_4)$$

$$V_O = (V_1 \text{ AND } V_2) \text{ OR } (V_3 \text{ AND } V_4)$$


Part 2 ends here

# Outline

## Op-Amp + Diodes

1. Exponential Converter
2. Logarithmic Converter
3. Multiplier
4. Divider
- 5. Hybrid Problems**


# Real diode

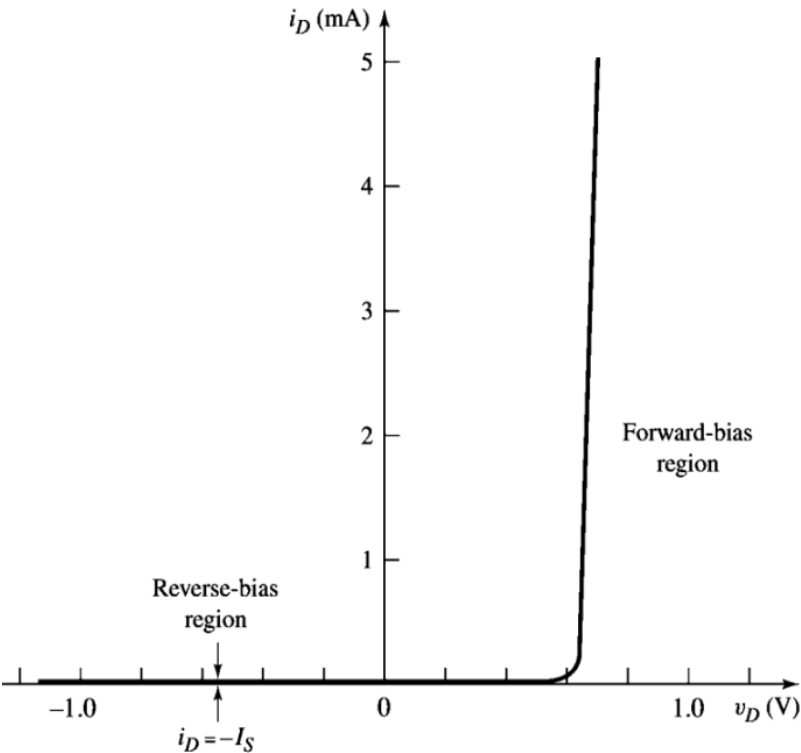

**I-V characteristics of a  
real diode**


Relation between diode current and diode voltage:
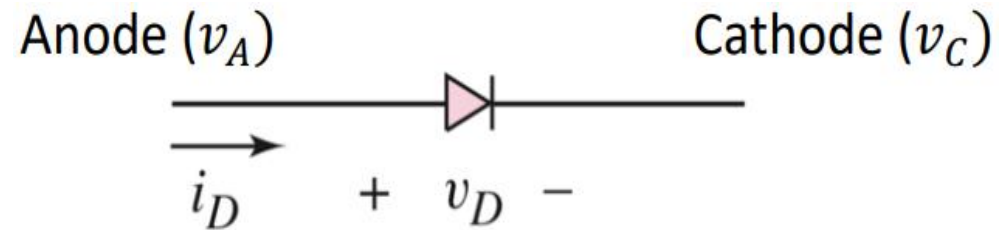
$$i_D = I_S \left( e^{\frac{v_D}{\eta V_T}} - 1 \right)$$



$\eta$  is called the ideality factor (try to recall, you measured this in the lab!)

# Exponential (Anti-log) Converter

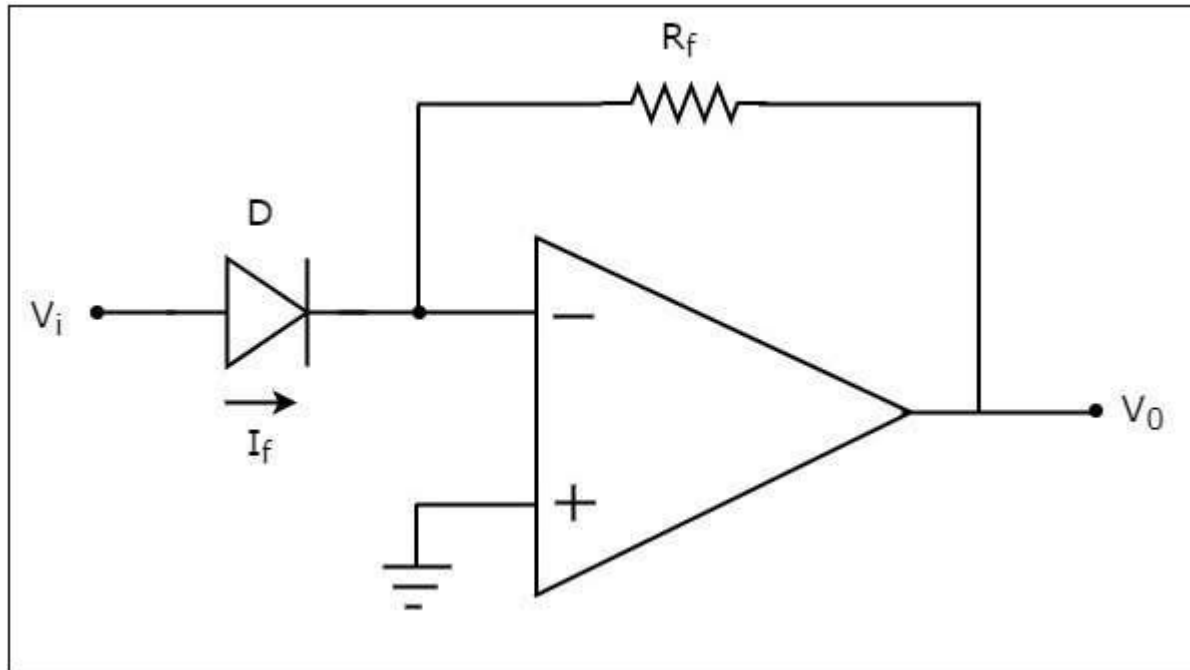


$$I_f = I_S \exp\left(\frac{V_i - 0}{V_T}\right)$$

$$\frac{0 - V_o}{R_f} = I_S \exp\left(\frac{V_i}{V_T}\right)$$

$$V_o = I_S R_f \cdot \exp\left(\frac{V_i}{V_T}\right)$$



# Logarithmic Amplifier

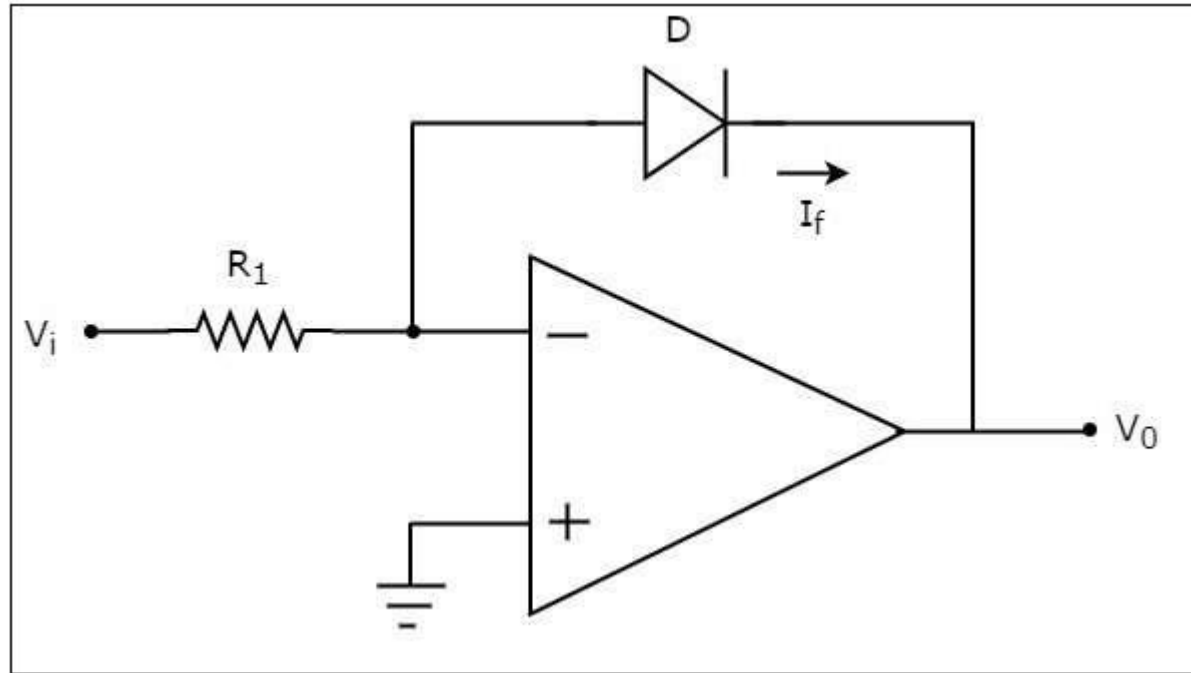

$$I_f = I_S \exp\left(-\frac{V_O}{V_T}\right)$$

$$\frac{V_i}{R_1} = I_S \exp\left(-\frac{V_O}{V_T}\right)$$

$$\frac{V_i}{I_S R_1} = \exp\left(-\frac{V_O}{V_T}\right)$$

$$V_O = -V_T \cdot \ln\left(\frac{V_i}{I_S R_1}\right)$$

# APPLICATIONS:


Implementing operational functions

$$V_T = 0.025 \text{ V}$$

$$I_s R_F = 1 \text{ V}$$

$$\therefore R_F = \frac{1}{I_s} \text{ k}$$
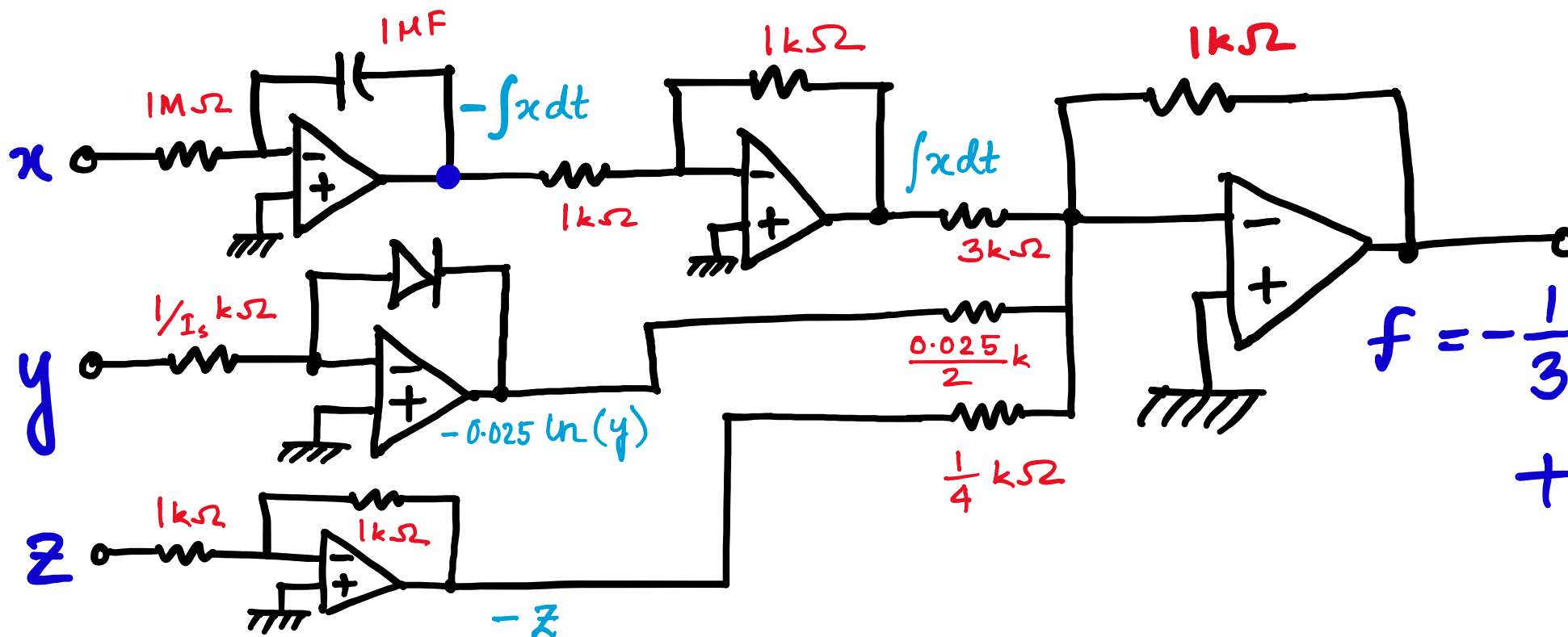
$$f = -\frac{1}{3} \int x \cdot dt + 2 \ln y + 4z = -\left(\frac{1}{3} \int x dt - 2 \ln(y) - 4z\right)$$




$$f = -\frac{1}{3} \int x dt + 2 \ln y + 4z$$

# APPLICATIONS:

Implementing operational functions

- $f = -3 \frac{dx}{dt} + 2 \exp(y) + 4z$
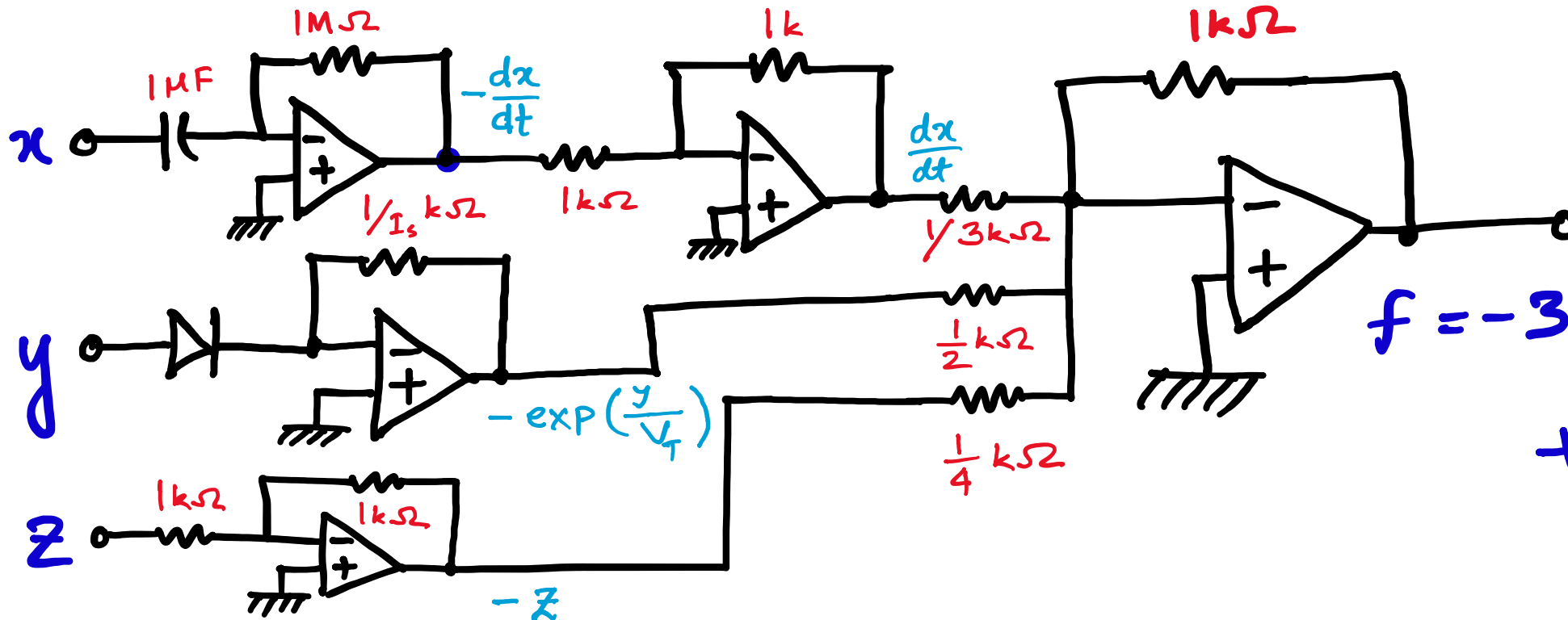
$$V_T = 1 \text{ V}$$
$$I_s R_f = 1 \text{ V}$$



$$f = -3 \frac{dx}{dt} + 2 \exp(y) + 4z$$

# Multiplier

$$f = xy$$


$$\ln(f) = \ln(xy) = \ln(x) + \ln(y)$$

$$f = \exp(\ln(x) + \ln(y))$$

$$V_T = 1\text{ V}$$
$$I_s R_f = 1\text{ V}$$

So,
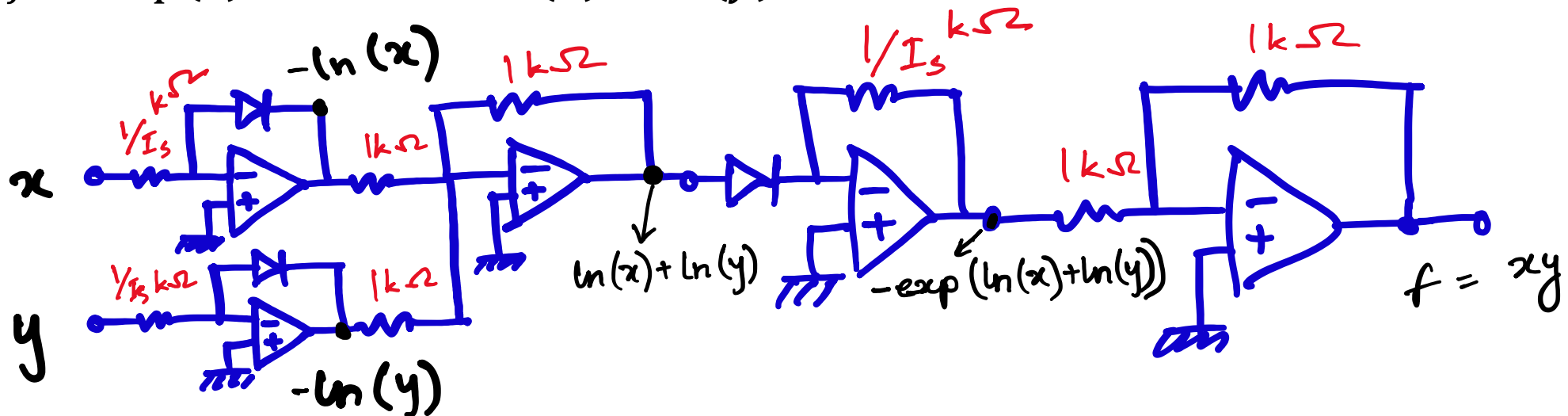
$$f = \exp(z) \text{ where } z = \ln(x) + \ln(y)$$



# Divider

$$f = xy/z$$

$$\ln(f) = \ln(xy/z) = \ln(x) + \ln(y) - \ln(z)$$


$$f = \exp(\ln(x) + \ln(y) - \ln(z))$$

So,

$$f = \exp(z) \text{ where } z = \ln(x) + \ln(y) - \ln(z)$$


$$V_T = 1 \text{ V}$$

$$I_s R_f = 1 \text{ V}$$

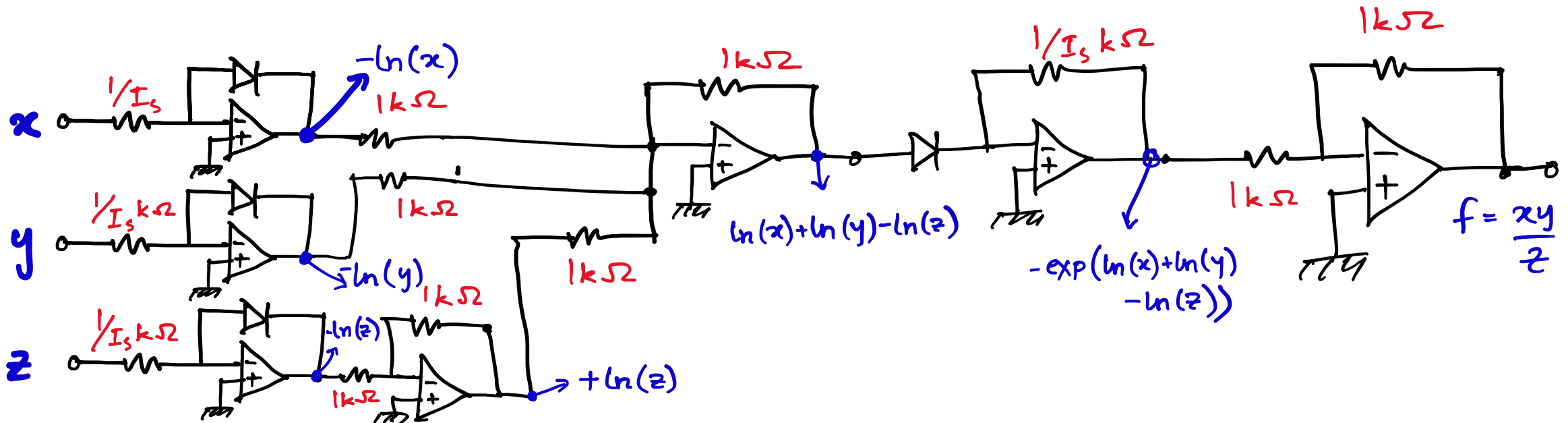


# Hybrid Problems

Example 1:

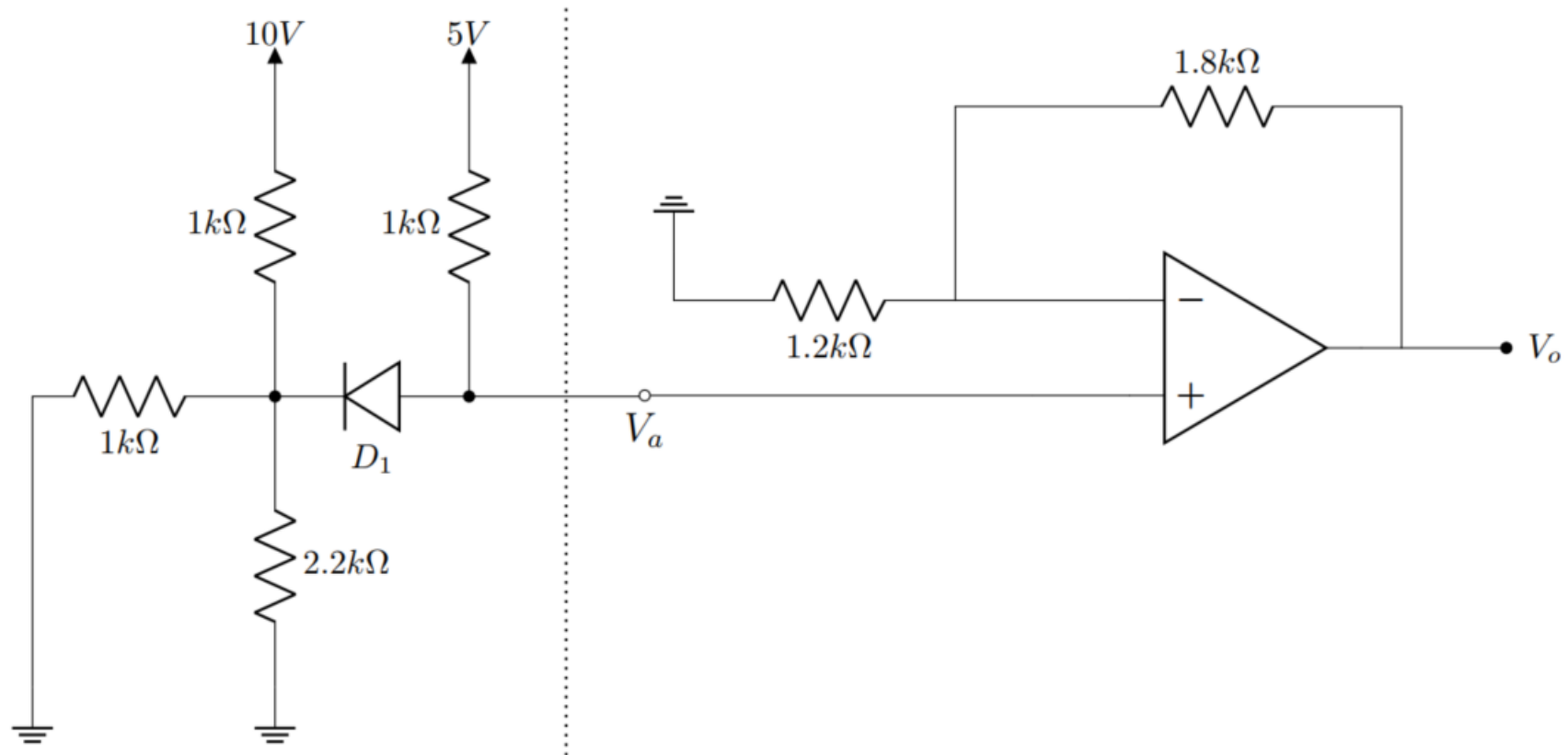

# Hybrid Problems

Example 2:

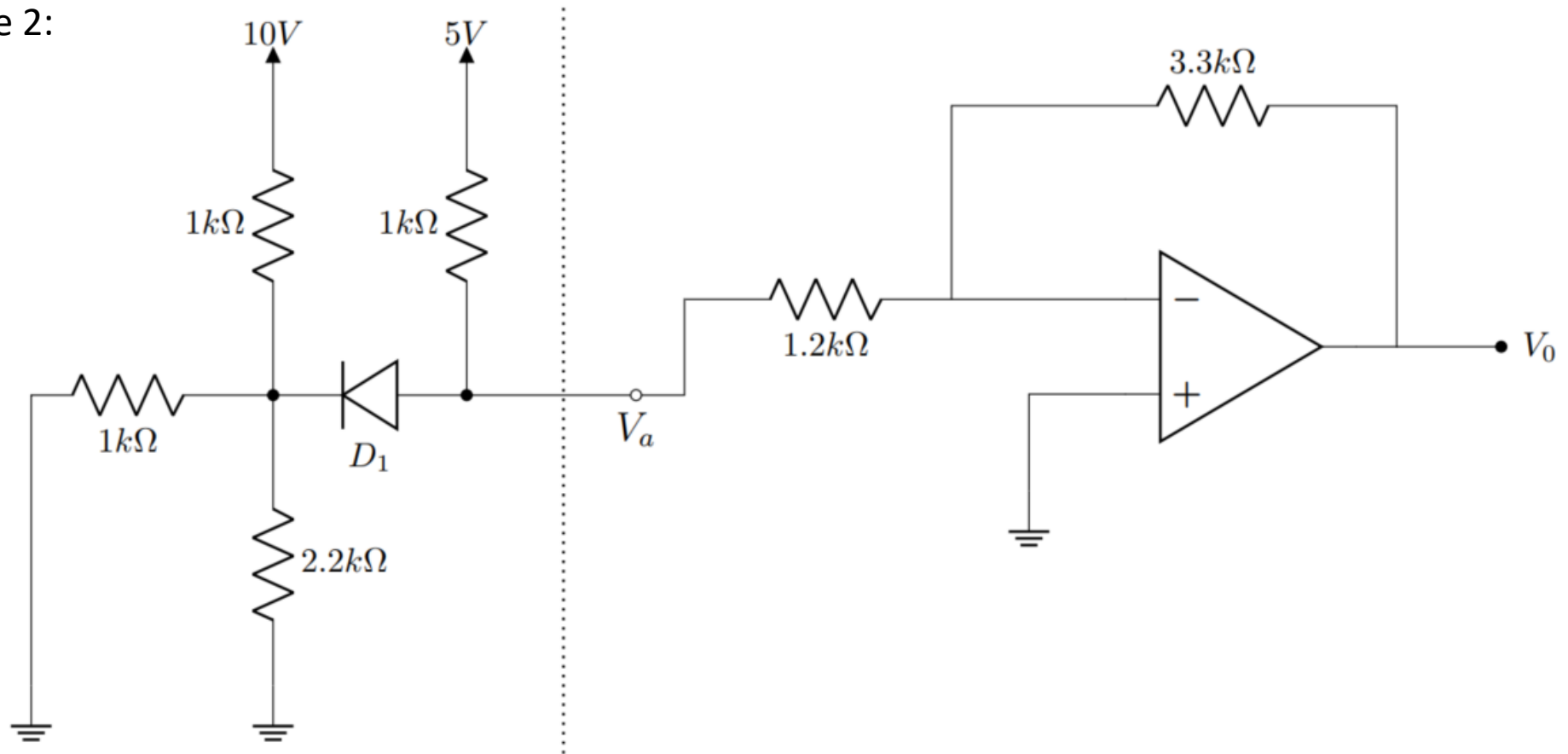

Thank You!