

# **Assignment - 4**

**Name:** Md. Minhazul Mowla

**ID:** 23201390


**Section:** 01

**Course:** CSE251

**Submission Date:** 6/9/25

Ans to the Ques. No. - 1

$$V_G = V_{DD} = 10 \text{ V}$$

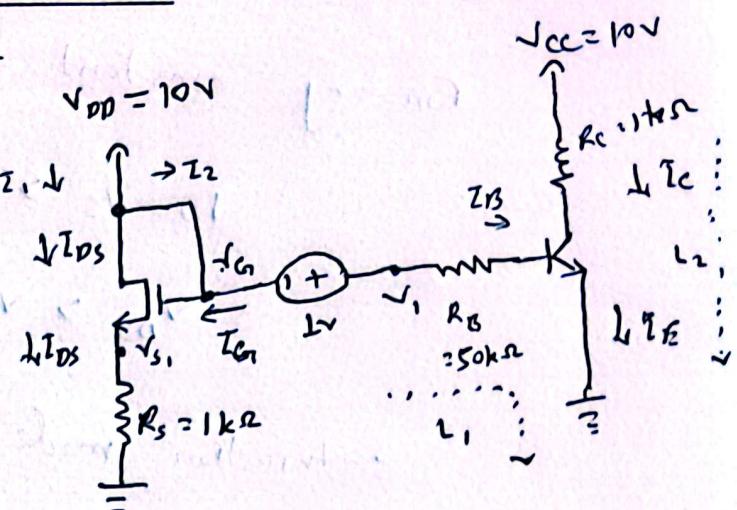

b

$$V_I - V_G = 2$$

$$\Rightarrow V_I = 2 + V_G$$

$$= 2 + 10 \\ \approx 12 \text{ V}$$

c

$$V_{GS} = V_G - V_S \approx 10 - V_S$$

$$V_{DS} = V_D - V_S = 10 - V_S \quad [V_D = V_{DD}]$$

$$V_{DS} = V_G - V_T = 10 - 0.9 \quad [V_T = 0.9 \text{ V}]$$

$$V_{DS} = V_{GS} - V_T = 10 - V_S - 0.9 \quad [V_T = 0.9 \text{ V}]$$

$$= 9.1 - V_S$$

Q  
For any constant value of  $v_s$ ,

$$10 - v_s > 4 \cdot 1 - v_s$$

$$\therefore v_{DS} > v_{OV}$$

$\therefore$  saturation mode

e

From Q,  
 $v_m \rightarrow$  saturation

$$\begin{aligned} I_{DS} &\sim \frac{1}{2} k (v_{OV})^2 \sim \frac{1}{2} \times 4 \times (9.1 - v_s)^2 \\ &= 2(9.1 - v_s)^2 \\ &= 2(82.8) - 18.2 v_s + v_s^2 \\ &= 165.62 - 36.4 v_s + 2v_s^2 \dots (i) \end{aligned}$$

Ohm's law on  $R_S$ ,

$$\frac{v_{SG} - 0}{2} = I_{DSB}$$

$$\therefore \Rightarrow I_{DS} = v_s \dots (ii)$$

(i), (ii),

$$v_s = 165.62 - 36.4 v_s + 2v_s^2$$

$$\Rightarrow 2v_s^2 - 35.4v_s + 165.62 = 0$$

$$\therefore v_s =$$

$$\Rightarrow 2v_s^2 - 37.4v_s + 165.62 = 0$$

$$v_s = 11.5 \text{ on}$$

$$v_s = 7.2$$

$$\therefore v_{DS} = 10 - 7.2$$

$$\Rightarrow \therefore v_{DS} = 10 - 11.5$$

$$= 2.8 \text{ V}$$

$$= 1.5 \text{ V}$$

$v_s = 7.2$  makes more accurate for saturation

$$\therefore I_{DS} = \frac{7.2 - 0}{1} = 7.2 \text{ mA}$$

$$\therefore v_{DS} = 2.8 \text{ V}$$

f

Assumption - I,

bjt in saturation

$$V_{BE} = 0.8 \text{ V}$$

$$V_{CE} = 0.2 \text{ V}$$

KVL along L<sub>1</sub>,

$$11 - 0 = 50 I_B + V_{BE}$$

$$\Rightarrow 11 = 50 I_B + 0.8$$

$$\therefore I_B = 0.216 \text{ mA}$$

KVL along  $L_2$ ,

$$10 - 0 = I_C + V_{CE}$$
$$\Rightarrow 10 - 0.2 = I_C$$
$$\therefore I_C = 9.8 \text{ mA}$$

$$I_E = I_B + I_C = 0.216 + 9.8 = 10.016 \text{ mA}$$

Verification:

$$I_B, I_C, I_E > 0$$

$$\frac{I_C}{I_B} = \frac{9.8}{0.216} \approx 45.37 < \beta = 100$$

$\therefore$  Assumption 1 correct


$$I_B = 0.216 \text{ mA}$$

$$I_C = 9.8 \text{ mA}$$


$$I_E = 10.016 \text{ mA}$$

Ans. to the Ques. No. - 2

a  
BJT during active -

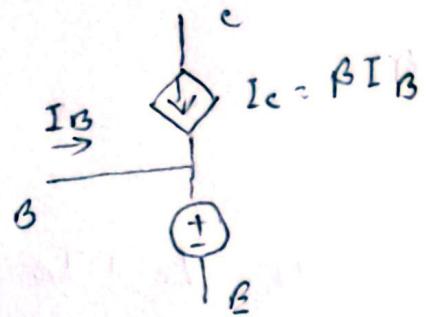

b  
BJT during saturation -

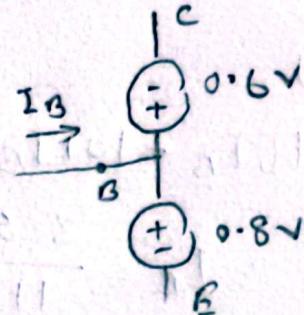


Assumption-1,

BJT is active

$$V_{BE} = 0.7$$

$$\frac{I_c}{I_B} = \beta = 100$$

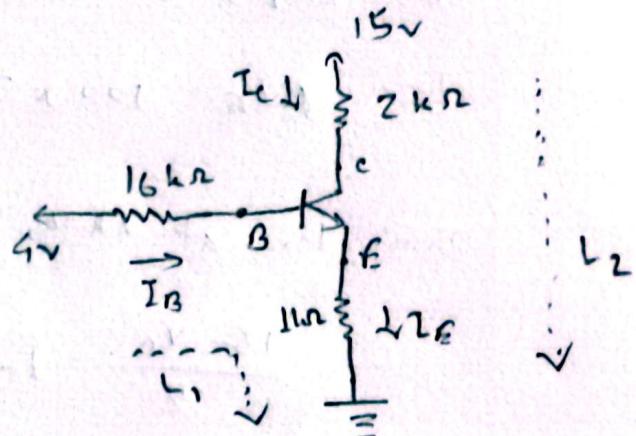

$$I_C = \alpha I_E$$

$$R_{th} = \frac{20 \times 80}{20 + 80} = 16 \text{ k}\Omega$$

$$I_E = I_C + I_B$$

$$V_{th} = 5 \times \frac{80}{20 + 80} = 4 \text{ V}$$

KVL along L<sub>1</sub>,

$$4 - 0 = 16 I_B + V_{BE} + I_E$$

$$\therefore 16 I_B + I_E - 3.3 = 0. - \text{ (i)}$$

KVL along L<sub>2</sub>,

$$15 - 0 = 2I_C + V_{CE} + I_E \\ \Rightarrow \therefore 2I_C + I_E + V_{CE} = 15 - 0 \dots (\text{iii})$$

$$I_E = I_C + I_B = \beta I_B + I_B = I_B (\beta + 1) = (100 + 1) I_B \\ = 101 I_B \dots (\text{iv})$$

(i), (iii),

$$16I_B + 101I_B = 3.3$$

$$\therefore I_B = \frac{3.3}{117} = 0.028 \text{ mA}$$

$$I_E = 101 \times 0.028 \text{ mA} = 2.828 \text{ mA}$$

$$I_C = \beta I_B = 100 \times 0.028 = 2.82 \text{ mA}$$

Ohm's law at 2kΩ,

$$\frac{15 - V_C}{2} = I_C$$

$$\Rightarrow 15 - V_C = 2I_C$$

$$\Rightarrow 15 - V_C = 2 \times 2.82$$

$$\therefore V_C = 9.36 \text{ V}$$

Ohm's law at 1kΩ,

$$\frac{V_E - 0}{2} = I_E \\ \therefore V_E = I_E = 2.828 \text{ mA}$$

$$\therefore V_{CE} = V_C - V_E = 9.36 - 2.828 = 6.532 \text{ V}$$

### Verification

$$I_C, I_B, I_E > 0$$

$$V_{CE} = 6.5 > 0.2$$

$\therefore$  Assumption correct

c

$$V_{BB} = 5.1 \text{ V}$$

$$V_H = 5.1 \times \frac{80}{20+80} = 4.08 \text{ V}$$

$$R_H = 16 \text{ k}\Omega \text{ using}$$

Assump

Assumption-1: ~~Active~~

BJT is active

KVL along  $L_1$ ,

$$4.08 - 0 = 16 I_B + V_{BE} + I_E$$

$$\Rightarrow 16 I_B + I_E - 3.38 = 0 \dots (i)$$

KVL along  $L_2$ ,

$$15 - 0 = 2 I_C + V_{CE} + I_E$$

$$\Rightarrow 2 I_C + I_E + V_{CE} = 15$$

$$\therefore 2 I_C + I_E + V_{CE} - 15 = 0 \dots (ii)$$

$$I_B = I_C + I_B = \beta I_B + I_B = (1 + \beta) I_B = 101 I_B$$

(i),  $16 I_B + 1001 I_B = 3.38$

$$\therefore I_B = \frac{3.38}{117} = 0.028 \text{ mA}$$

$$I_C = \beta I_B = 2.89 \text{ mA}$$

$$I_E = 101 I_B = 1001 \times 0.028 = 2.828 \text{ mA}$$

(ii),

$$2 \times 2.8 + 2.828 + V_{CE} = 15$$

$$\therefore V_{CE} = 6.572$$

### Verification

$$I_C, I_B, I_E > 0$$

$$V_{CE} > 0.2$$

Assumption-1 connect.

Ohm's law at 2h<sup>2</sup>,

$$\frac{15 - V_C}{2} = I_C$$

$$\Rightarrow 15 - V_C = 2.89 \times 2$$

$$\therefore V_C = 9.22 \text{ V}$$

$$\Delta I_C = I_{C_{\text{new}}} - I_{C_{\text{old}}} = 2.89 - 2.82 = 0.07 \text{ mA}$$

J


Due to a small change in the input, it produces a small amount of change in base current. Multiplying it by gain ( $\beta$ ) makes it big. This can be used in order to amplify signals, driving huge loads with small amount of power.

Ans. to the ques. No. - 3

a

$$V_G = 0V$$

$$I_{DS} = 4mA$$

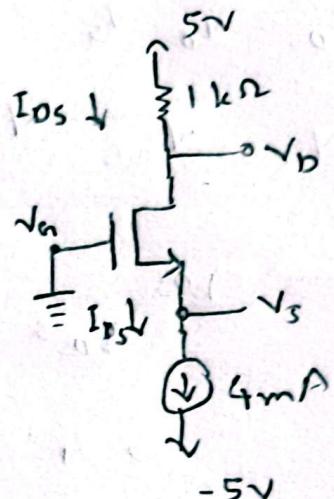

b

Ohm's law on  $1k\Omega$ ,

$$\frac{5 - V_D}{1} = I_{DS}$$

$$\Rightarrow 5 - V_D = 4$$

$$\therefore V_D = 1V$$

c

Assuming,

(i)  $m \rightarrow \text{saturation}$

$$V_{GS} \geq V_T$$

$$V_{DS} \geq V_{OV}$$

$$V_{GS} = V_G - V_S = 0 - V_S = -V_S$$

$$V_T = 1 \text{ V}$$

$$V_{DS} = V_D - V_S = 1 - V_S$$

$$V_{OV} = V_{GS} - V_T = \cancel{-} - V_S - 1$$

From eqn,

$$I_{DS} = \frac{1}{2} \times k \times (V_{OV})^2$$

$$\Rightarrow 4 = \frac{1}{2} \times 4 \times (-V_S - 1)^2$$

$$\Rightarrow 4 = 2(-V_S - 1)^2$$

$$\Rightarrow 4 = 2V_S^2 + 4V_S + 2$$

$$\Rightarrow V_S^2 + 2V_S + 1 = 2$$

$$\Rightarrow V_S^2 + 2V_S - 1 = 0$$

$$\therefore V_S = 0.414 \text{ on } V_S = -2.414$$

considering  $V_S = -2.414 \text{ V}$ ,

$$V_{GS} = -V_S = 2.414 \Rightarrow V_T = 1 \text{ V}$$

$$V_{DS} = 1 - V_S = 1 - (-2.414) = 3.414$$

$$V_{OV} = -V_S - 1 = -(-2.414) - 1 = 1.414$$

$$\therefore V_{DS} \geq V_{OV}$$

$\therefore$  Assumption correct

$$\therefore V_S = u = -2.414 \text{ V}$$

Ans to the que. No. 4

a

$i_{g_1} = I_{G_1} = 0 \text{ mA}$ ; [no current flow in the gate]


$i_{g_2} = I_{G_2} = 0 \text{ mA}$ ; [no current flow in the gate]

b

- i. S model is asymmetric. SR model is symmetric.
- ii. S model has poor bidirectional current but SR model has excellent bidirectional current
- iii S model has low (static) body effect accuracy but SR model has high (dynamic) body effect accuracy
- iv. S model has inaccurate analog switch use but SR has accurate.
- v. S model has poor simulation convergence but SR model has better.

Q. \*

e

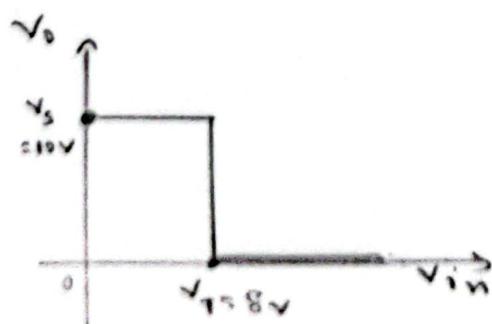

C

Assumption,

 $B_1, B_2$  in saturation

$$\beta = 100$$

$$V_{BE} = 0.8 \text{ V}$$

$$I_B \approx \sqrt{B} I_D$$

$$V_{CE} = 0.2 \text{ V}$$

Hence to start,

 $B_1$ ,  $B_2$ .

$$V_{E_1} = V_{B_1} - V_{BE}$$

$$= 5 - 0.8$$

$$= 4.2 \text{ V}$$

$$I_{E_1} = \frac{V_{E_1}}{2 \text{ k}\Omega} = \frac{4.2}{2} = 4.2 \text{ mA}$$

$$I_{E_1} = I_C + I_{B_1} = \beta I_{B_1} + I_{B_1} \Rightarrow ; [I_C = \beta I_{B_1}]$$

$$= (101) I_{B_1}$$

$$I_{E_1} = I_C + I_{B_1} = I_C + \frac{I_{C_1}}{\beta} ; [I_C = \beta I_{B_1}]$$

$$\Rightarrow 4.2 = I_{C_1} \left( 1 + \frac{1}{100} \right)$$

$$\therefore I_{C_1} = 4.16 \text{ mA}$$

$$\therefore I_{B1} = \frac{I_{C1}}{\beta} = \frac{4.16}{100} = 0.0416 \text{ mA}$$

$B_2$ ,

$$V_{E2} = V_{C2} - 0.2 = 8 - 0.2 = 7.8 \text{ V}$$

$$I_{E2} = \frac{V_{E2}}{R_E 1k\Omega} = \frac{7.8}{1} = 7.8 \text{ mA}$$

again,

$$I_{E2} = I_{C2} \left(1 + \frac{1}{100}\right); [\beta = 100]$$

$$\therefore I_{C2} = \frac{7.8}{1.01} = 7.72 \text{ mA}$$

f

$B_1$  in  $B_2$  act forward active.

$$V_{BE} = 0.7 \text{ V}$$

$$V_{B1} = 5 \text{ V}$$

$$V_{E1} = V_{B1} - V_{BE} = 5 - 0.7 = 4.3 \text{ V}$$

$$I_{E1} = \frac{V_{E1}}{1k\Omega} = \frac{4.3}{1} = 4.3 \text{ mA}$$

$$I_{E1} = I_{C1} + I_{B1}$$

again,

$$I_{E1} = I_{C1} \left(1 + \frac{1}{\beta}\right)$$

$$\Rightarrow I_{C1} = \frac{4.3}{\left(1 + \frac{1}{100}\right)} = 4.257 \text{ mA}$$

$$I_{B_1} = \frac{I_{C_1}}{\beta} = \frac{4.257}{100} = 0.0426 \text{ mA}$$

$$V_{C_1} \approx 10V - (I_{C_1} \times 1k\Omega)$$

$$\approx 10 - 4.257$$

$$\approx 5.743 V$$

$$V_{in} \approx V_{C_1} = 5.74 V$$